

# Home Work Assignment #1

## Analog Integrated Circuit Design

University of Rhode Island, Kingston, RI 02881-0805, U.S.A.

---

### Parameters, Equations:

Physical Constants:

$$\begin{aligned}q &= 1.6 \times 10^{-19} C & \epsilon_o &= 8.85 \times 10^{-14} F/cm \\ \epsilon_{ox} &= 3.9 \epsilon_o = 3.45 \times 10^{-13} F/cm & \epsilon_{Si} &= 11.7 \epsilon_o = 1.04 \times 10^{-12} F/cm \\ n_i &= 1.45 \times 10^{10} cm^{-3} & \phi_T &= 26 mV\end{aligned}$$

AMI C5 Process Parameters:

$$\begin{aligned}CGDO &= CGSO \approx .2 fF & t_{ox} &= 13.9 nm \\ \text{nMOS} & & \text{pMOS} & \\ \mu_n &= 453 cm^2/[V \cdot sec] & \mu_p &= 201 cm^2/[V \cdot sec] \\ V_{Tn} &= 0.669 V & V_{Tp} &= -0.915 V \\ C_{j-sw} &= 0.34 fF/\mu m & C_{j-sw} &= 0.23 fF/\mu m \\ C_{j-A} &= 0.41 fF/\mu m^2 & C_{j-A} &= 0.64 fF/\mu m^2\end{aligned}$$

- 
- 1) Find the expressions to estimate the pole frequencies,  $f_{p1}$  &  $f_{p2}$  and the zero frequency,  $f_z$ , for the common source amplifier shown in figure 1. Include the voltage source resistance,  $R_S$ , in the expressions derived for each frequency as shown in figure 2.
- a) Show that

$$\begin{aligned}f_{p1} &\approx \left(\frac{1}{2\pi}\right) \frac{1}{g_{m1} C_{gd1} R_s(r_{o1} || R_{oP})} \\ &\& \\ f_{p2} &\approx \left(\frac{1}{2\pi}\right) \frac{g_{m1} C_{gd1}}{C_{gd1} C_{gs1} + C_o(C_{gd1} + C_{gs1})}\end{aligned}$$

- b) Find an expression for  $R_{op}$ .
- c) Assuming that we concern ourselves only with gate-source and gate-drain capacitances, which capacitor is  $C_o$  (in M2) ?

 


Figure 1. nMOS Common source with active pMOS load.

 


Figure 2. Small signal Equivalent Circuit.

- 2) Simulate the circuits in figures 1 and 2.
  - a) Determine  $I_D$  directly from the simulation for your values of  $W_n$ ,  $W_p$  &  $L$ .
  - b) Compute  $C_{ox}$ ,  $k_n$ ,  $\beta_n$ ,  $k_p$ , &  $\beta_p$  using the values provided (and your device geometries).
  - c) Estimate the values of  $C_{gs1}$ ,  $C_{gd1}$  &  $C_o$ .  
 note: gate drain capacitance (for M1 in saturation) is computed from  $C_{gd1} \approx C_{ox}W_nL_{diff} = CGDO \times W_n$   
 where  $CGDO$ , is spice parameter for the gate-drain overlap capacitance, defined as  $CGDO = C_{ox}L_{diff}$  and  $L_{diff}$  is lateral diffusion (the amount of the implant that diffuses under the gate).
  - d) Plot the gain and phase of the amplifier using the ac analysis.
  - e) Draw the small signal equivalent circuit schematic (in the virtuoso schematic editor); use vccs and assign the  $g_{m1}$  value to it. Run the ac analysis for this circuit.
  - f) Compute  $f_{p1}$ ; compare the computed value with each of the ac simulation plots in ADE.

- 3) Find an approximate expression for  $f_{p1}$  for the cascode amplifier shown in figure 3.

 


Figure 3. Telescopic Cascode Amplifier with an active load.

- Draw the small signal equivalent circuit. (*Please note that the pMOS cascode section can be replaced with a resistor,  $R_{oP}$ .*)
- Find an expression for the mid-frequency input impedance of the common gate transistor (M2); ignore the body effect (e.g. do not include  $g_{mb}$ ).
- Find expressions for the mid-frequency amplifier gain,  $\left(\frac{V_{o1}}{V_{in}}\right)$  &  $\left(\frac{V_o}{V_{o1}}\right)$ ; use these expressions to find:  $\left(\frac{V_o}{V_{in}}\right)$ .
- Use Miller's Theorem to compare the dominant pole frequency,  $f_{p1}$ , of the telescopic cascode amplifier with that of the common source amplifier.