

# Home Work Assignment #2

## Analog Integrated Circuit Design

*University of Rhode Island, Kingston, RI 02881-0805, U.S.A.*

---

- 1) Analyze, investigate, the single-ended folded cascode OTA with a p-channel input. This cell, named,  $ota_{fc_p}chin_tsmc180$  has been placed in the library  $otaAmps_tsmc180x$ . The circuit simulation cell, named  $Ota_{p}chin_GBWt_tsmc180$ , already created is what you will need to use to simulate this circuit.
  - a) Plot the open loop gain and phase. Record the phase margin.
  - b) Record the bandwidth, low frequency amplifier gain, unity gain bandwidth and the phase margin for each of the following loads:  $20fF$ ,  $100fF$ ,  $500fF$ ,  $1.0pF$ ,  $2.5pF$ , &  $5pF$ .
  - c) Based upon your measurements, how is  $C_L$  related to the bandwidth, unity gain frequency and stability of the OTA ?
- 2) Using the same OTA, determine an amplifier configuration to measure the slew rate.
  - a) Create the test set up for the slew rate measurement.
  - b) Measure the slew rate of a pulse that starts at 0V and transitions from 0V to 1.8V for the following capacitive loads:  $20fF$ ,  $100fF$ ,  $500fF$ ,  $1.0pF$ ,  $2.5pF$ , &  $5pF$ .
  - c) Since the slew rate is defined as  $I_o/C$ , find a relationship between this  $C$  &  $C_L$ , the load capacitor (hint, measure  $I_o$ ).
  - d) Measure the slew rate for pulse that transitions from 1.8V to 0V using the same  $C_L$  values used earlier.
  - e) Are the slew rates different for a positive and negative transition ?
- 3) Construct a non-inverting amplifier test schematic using this amplifier. Use a  $1K\Omega$  resistor for the connection between the inverting input and analog ground. Set  $C_L = 2.5pF$ .

- a) Measure the gain, bandwidth and unity gain frequency for the following gains: 2, 4, 10.
- b) Set up a transient analysis simulation. With the gain set to 2, determine the maximum input signal amplitude for a sinusoidal input.