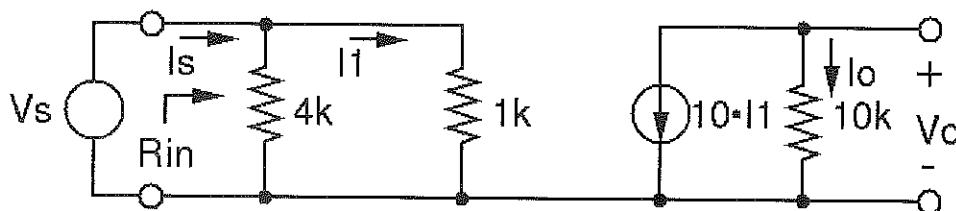


Name



1) Linear Circuit Theory



V_s is an ideal dc or ac voltage source.

- Find a value for the equivalent input resistance R_{in} seen by the source V_s .
- What is the value of the output voltage V_o if $V_s=50 \text{ mV}$?
- Derive a value for the current ratio I_o/I_s as determined by the given circuit elements.


2) Voltage Limiter with Zener Diode

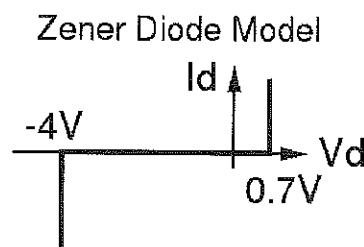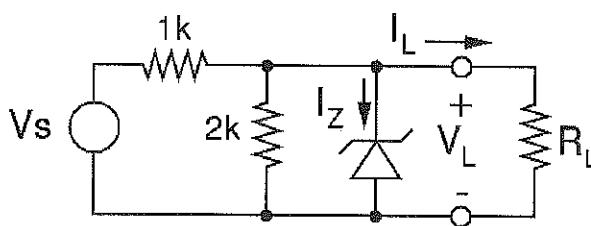

V_s is a sinusoidal voltage source of 10 V amplitude.

- What is the minimum value of the current I_L if $R_L=2 \text{ k}\Omega$?
- Find a value for the current I_Z flowing through the Zener diode if the source voltage is at its peak of 10 V ($R_L=2\text{k}\Omega$).
- Determine the peak power provided by the source V_s if $R_L=2 \text{ k}\Omega$ (Hint: look at both the positive and the negative peak of the source voltage).

3) BJT Biasing

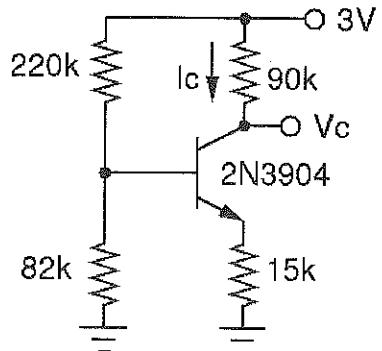

@ T=300K
 $V_{BEQ} = 0.65 \text{ V}$
 $\beta = 150$
 $V_T = 26 \text{ mV}$

- a) Find values for the current I_c and the power P_T dissipated by the 2N3904 transistor.
- b) If we know that V_{BE} drops by approx. 1.7 mV per degree C increase in temperature, what is the value of I_c at 330 K?
- c) Derive an expression for the differential quotient dV_C/dT and find its value for the given resistor values and transistor parameters. (Hint: relate the quotient dV_C/dT to the known temperature coefficient of V_{BE} , i.e., $dV_{BE}/dT = -1.7 \text{ mV/C}$).

4) Quick Answer Questions

- a) The output port of a BJT behaves like a

Answer *(controlled) current source*

3

- b) Diodes can be used to (mark all that apply)

A) Amplify signals

1

B) Limit voltage excursions

1

C) Illuminate a room

1

D) Sense light

1

- c) In order to quadruple (times 4) the current of a silicon diode at room temperature (assume $V_T = 26 \text{ mV}$), the diode voltage has to be increased by

Answer

56 mV

4

10

1) a) $\| R_{in} = 4k \parallel 1k = 800 \Omega \|$ 2

b) $\left| \begin{array}{l} V_o = -10 \cdot I_1 \cdot 10k \\ I_1 = \frac{V_S}{1k} \end{array} \right| \quad (1)$

(2)

$$\therefore | V_o = -10 \cdot V_S \frac{10k}{1k} = -100 V_S |$$

$$\text{If } V_S = 50 \text{ mV} \quad | V_o = -5 \text{ V} |$$

3

c) $\left| \begin{array}{l} I_o = -10 \cdot I_1 \\ I_S \cdot R_{in} = I_1 \cdot 1k \end{array} \right| \quad (1)$

(2)

2

$$\text{From (2)} \quad | I_1 = I_S \cdot \frac{R_{in}}{1k} = 0.8 \cdot I_S |$$

$$\therefore | I_o = -10 \cdot I_S \cdot \frac{R_{in}}{1k} |$$

or

$$\| \frac{I_o}{I_S} = -10 \frac{R_{in}}{1k} = -8 \| \quad 2$$

10

2) a) $I_{L\min} \therefore V_C = V_{S\min} = -10V$

$$R_L = 2k \therefore V_C = -0.7V$$

$$\left\| I_{L\min} = \frac{V_L}{R_L} = -0.35mA \right\|$$

3

b) $V_S = 10V$ and $R_C = 2k$

$$\therefore |V_L = 4V|$$

$$I_S = \frac{V_S - V_L}{1k} = 6mA$$

$$I_2 = \frac{V_L}{2k} = 2mA$$

$$I_C = \frac{V_L}{R_L} = 2mA$$

$$\left\| I_2 = I_S - I_1 - I_C = 2mA \right\|$$

3

c) $V_C = +10V \therefore I_S = 6mA$

2

$$V_S = -10V \quad I_S = \frac{-10V + 0.7V}{1k} = -9.3mA$$

$$\therefore \left\| P_{S\max} = 93mW \right\|$$

2

(10)

$$3) a) \quad | I_c = \frac{V_{cc} \cdot \frac{82k}{302k} - V_{BE}}{\frac{R_E}{\beta} + R_E(1 + \frac{1}{\beta})} = \frac{0.815 - 0.650}{0.4k + 15.1k} | \quad |$$

$$| I_c = 10.6 \mu A |$$

$$| P_T \approx [V_{cc} - I_c(R_c + R_E)] \cdot I_c = 20 \mu W |$$

3

$$5) \quad | I_c(370h) = \frac{0.815 - 0.599}{0.4k + 15.1k} \approx 13.9 \mu A |$$

2

$$c) \quad | V_c = V_{cc} - I_c R_c |$$

$$| \frac{dV_c}{dT} = - \frac{dI_c}{dT} R_c + \frac{\frac{dV_{BE}}{dT} R_c}{\frac{R_E}{\beta} + R_E(1 + \frac{1}{\beta})} |$$

2

$$\therefore | \frac{dV_c}{dT} = -1.7 \frac{mV}{C} \cdot \frac{50k}{0.4k + 15.1k} = -9.9 \frac{mV}{C} |$$

2

10