

Home Work Assignment #1B

ELE 447

University of Rhode Island, Kingston, RI 02881-0805, U.S.A.

Physical Constants:

$$q = 1.6 \times 10^{-19} \text{ C} \qquad \epsilon_o = 8.85 \times 10^{-14} \text{ F/cm} \qquad \epsilon_{Si_3N_4} = 7.5 \epsilon_o$$

$$\epsilon_{ox} = 3.9 \epsilon_o = 3.45 \times 10^{-13} \text{ F/cm} \qquad \epsilon_{Si} = 11.7 \epsilon_o = 1.04 \times 10^{-12} \text{ F/cm}$$

- 1) Find the capacitance of the parallel plate capacitor shown in figure 1 using dielectrics of air, SiO_2 , Si and Si_3N_4 for each of the geometries provided:

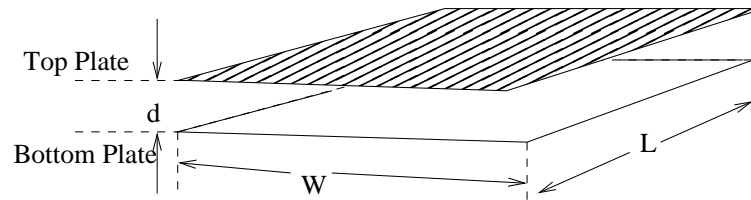


Figure 1. Circuit for Problem 1.

- a) $d = 2\text{mm}$, $L = 40\text{mm}$ and $W = 30\text{mm}$
- b) $d = 10^{-2}\mu\text{m}$, $L = 0.6\text{mm}$ and $W = 0.3\text{mm}$
- c) $d = 20\text{\AA}$, $L = 3\mu\text{m}$ and $W = 8\mu\text{m}$
- d) Find the capacitance of the parallel and series combination of a 850 fF, 30fF and a 130 fF capacitor.
- 2) Find the electric field between the top and bottom plates for the capacitor shown in figure 1 for distances given (assume that the voltage across the terminals is 5V):
- a) $d = 2\text{mm}$

¹ Tel: (401) 874-5482; fax: (401) 782-6422; e-mail: davis@ele.uri.edu

b) $d = 10^{-2} \mu m$

c) $d = 20 \text{ \AA}$

- 3) The definition of the rise is defined as time difference between the time V_o changes from 10% to 90% of the maximum output level. Conversely, the definition for the fall time is defined as the time difference between the time that V_o changes from 90% to 10% of the maximum output level.

- a) Using a simple "pull-up" RC model, show that:

$$t_{rise} = 2.2RC.$$

- b) Using a simple "pull down" RC model, show that:

$$t_{fall} = 2.2RC.$$

- c) Suppose that V_{dd} changes from 5 Volts to 3.3 Volts. How do the expressions for rise time and fall time change ?
- d) Suppose the rise time was re-defined to be the time difference between the time V_o changes from 0 Volts to 70% of the maximum level of 5 volts. Also assume that the fall time is again the converse (e.g. V_o from 70% to 0 Volts). How do the expressions for rise and fall time change ?
- e) Repeat part (d) for a maximum level of 3.3 volts.