

# ELE 448 Lab 5

Due by 18 March, 2019

1. Finish Lab 4
  - a. XOR
    - i. schematic, simulation, and layout
  - b. Negative Level D-Latch
    - i. Schematic, simulation, and layout
  - c. Positive Level D-Latch
    - i. Schematic, simulation, and layout
  - d. Positive Level D-Latch with Reset
    - i. Schematic, simulation, and layout
2. XNOR; Please refer to the XOR from (1). The XOR can be made into an XNOR by adding an inverter; however, one can invert the operation by:
  - a. Copy XOR-> XNOR
  - b. Find a way, using the same architecture (2 inverters, & the 2 pass transistors) to implement the XNOR function; verify that it functions properly
  - c. Carry the adjustment(s) into the layout; verify the layout, e.g. DRC & LVS
3. SR Latch; using the 2 input NAND that you created for the previous layout lab, implement an SR latch (synthesized from 2 NAND gates)
  - a. Open the schematic editor; wire the SR latch (also create the symbol)
  - b. Verify the schematic via simulation
  - c. Generate the layout; verify the layout, e.g. DRC & LVS

Note:

- One can find drawings of this latch in chapter 5 of the textbook
- The SR Latch will have the following truth table

| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 1 | 1 | Q | $\bar{Q}$ |
| 0 | 1 | 1 | 0         |
| 1 | 0 | 0 | 1         |
| 0 | 0 | 1 | 1         |

4. Draw a CMOS transmission gate (layout only)

Note:

- Information on transmission gates can be found in section 7.3 of the textbook

## Lab Write-up:

For all components:

- a. Schematic
  - i. Provide an image
  - ii. How many of each type of MOSFET were used in your design?
  - iii. How does the component work?
- b. Simulation
  - i. Provide images
    1. Simulation setup and results
  - ii. Does the output make sense?
    1. Provide a truth table
- c. Layout
  - i. Show an image of your layout
  - ii. Explain how the device is represented in the layout
    1. Where is each component located?
  - iii. Did DRC and LVS pass?
    1. If it failed, what did you have to modify to get them to pass?