


Basics – 4

series/parallel resistance;
voltage/current division


Applying KCL and KVL

Consider:

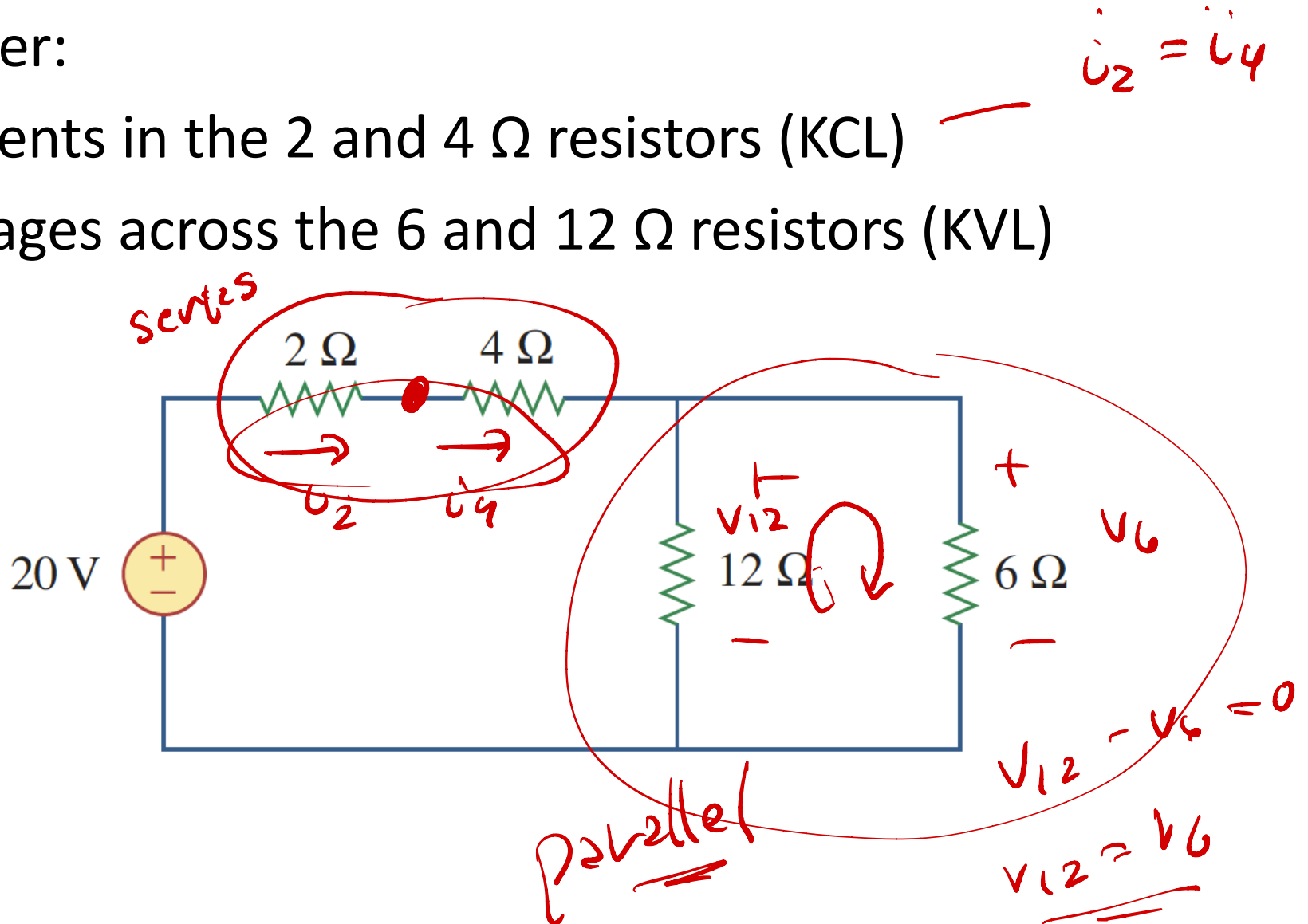- Currents in the 2 Ω and 4 Ω resistors (KCL)
- Voltages across the 6 Ω and 12 Ω resistors (KVL)



Series Resistors & Voltage Division

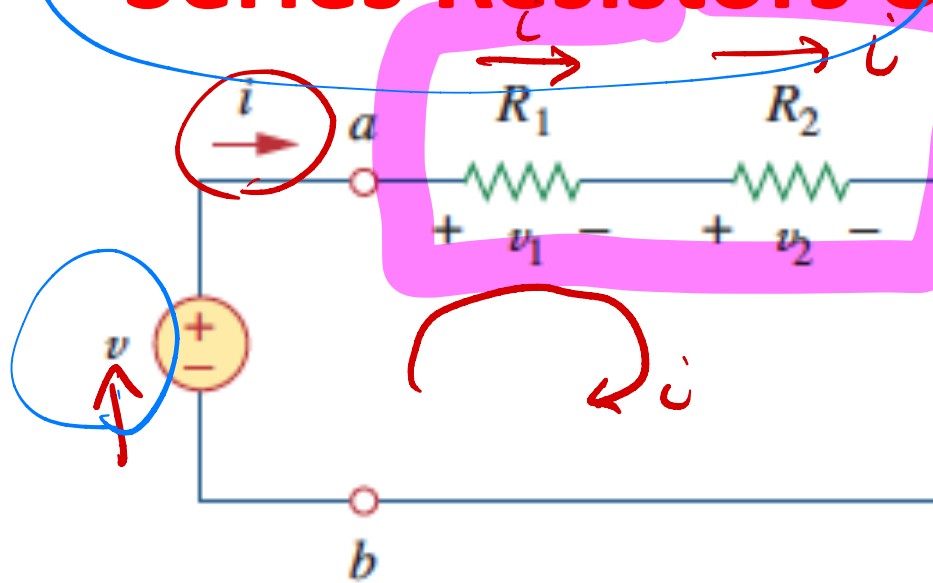

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot v$$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot v$$

$$V_1 = R_1 \cdot i$$
$$V_2 = R_2 \cdot i$$




$$v - v_1 - v_2 = 0$$

$$v - R_1 i - R_2 i = 0$$


$$v = i (R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$



Examples

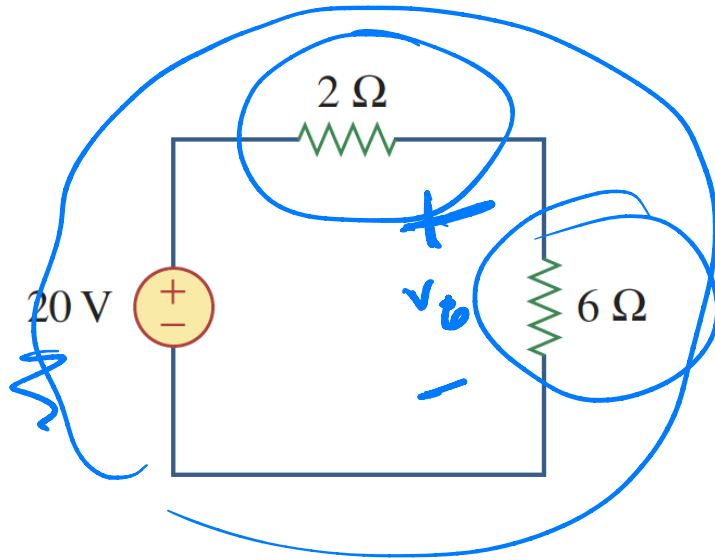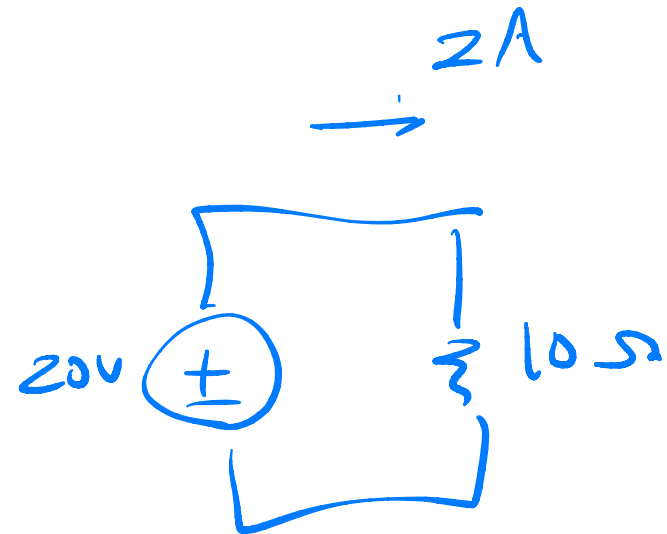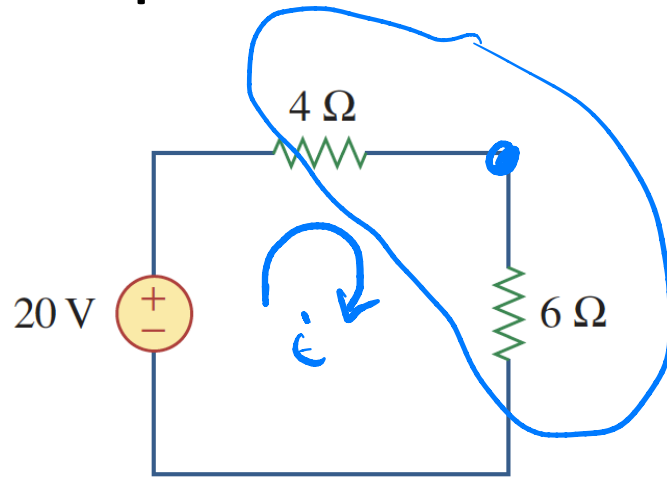
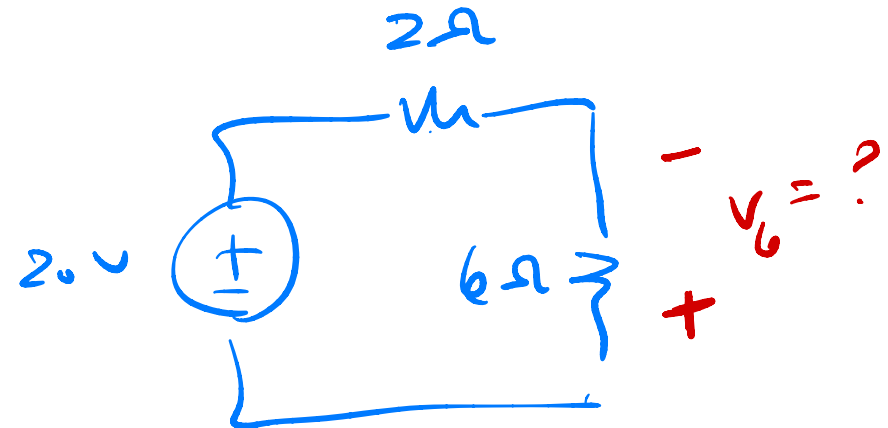
$$V_2 = \frac{6}{6+2} \cdot 20 = 15 \text{ V}$$




Example:

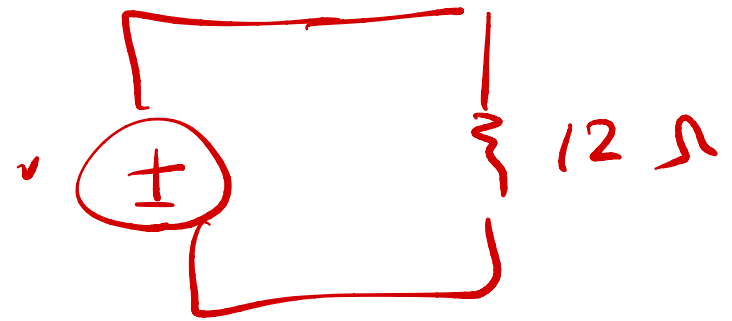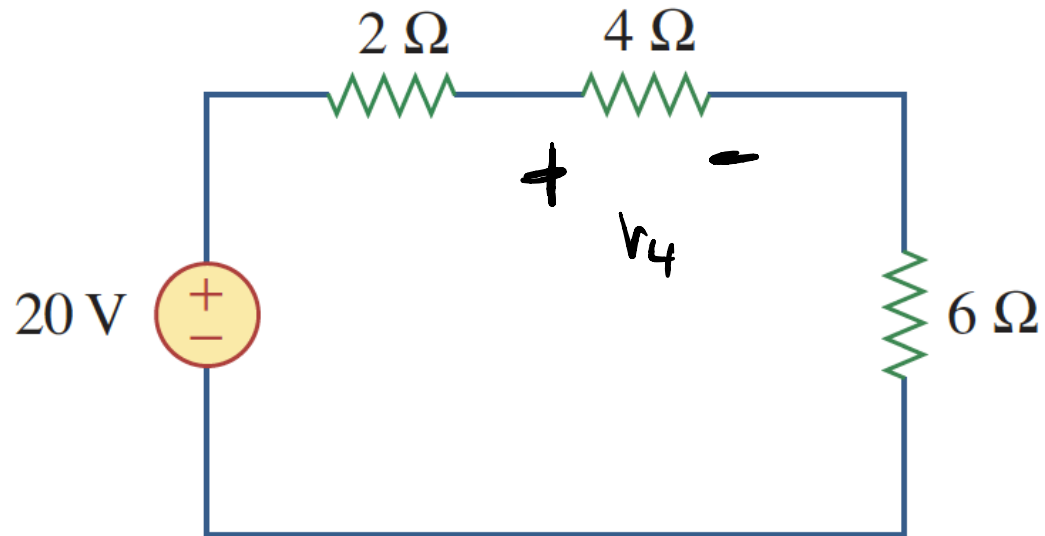

$$v_4 = \frac{4}{2 + 4 + 6} \cdot 20 = \frac{80}{12} \text{ V}$$

Parallel Resistors & Current Division

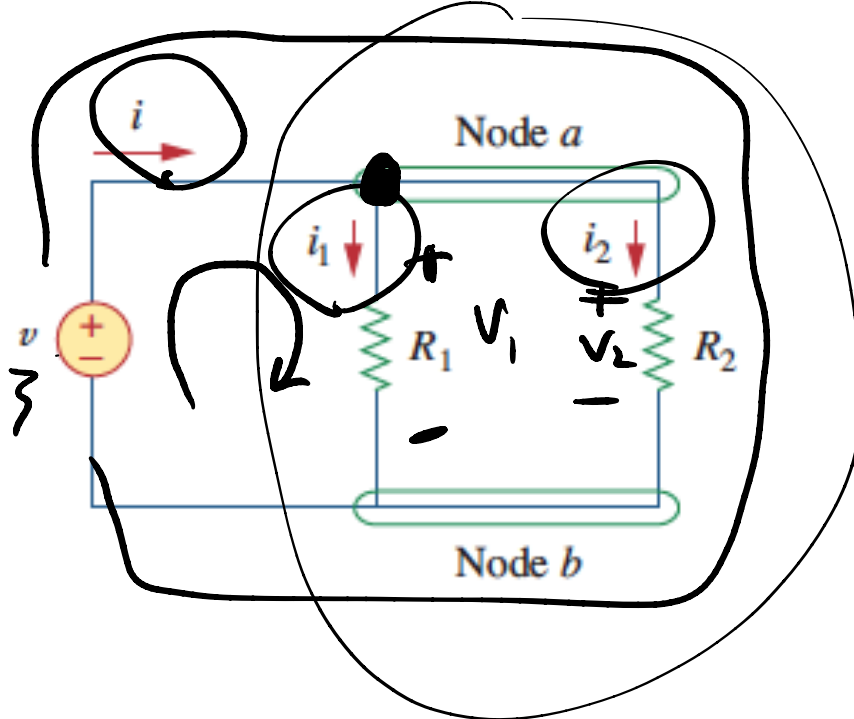

$$KVL = v_1 = v$$

$$v_2 = v$$

$$\text{Ohm} \quad i_1 = \frac{v_1}{R_1} = \frac{v}{R_1}$$

$$i_2 = \frac{v_2}{R_2} = \frac{v}{R_2}$$

$$i = v \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$KCL \quad i = i_1 + i_2$$


$$= v \cdot \frac{R_2 + R_1}{R_1 R_2}$$

$$i = \frac{v}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$= \frac{v}{R_1} + \frac{v}{R_2}$$

$$i = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Examples:

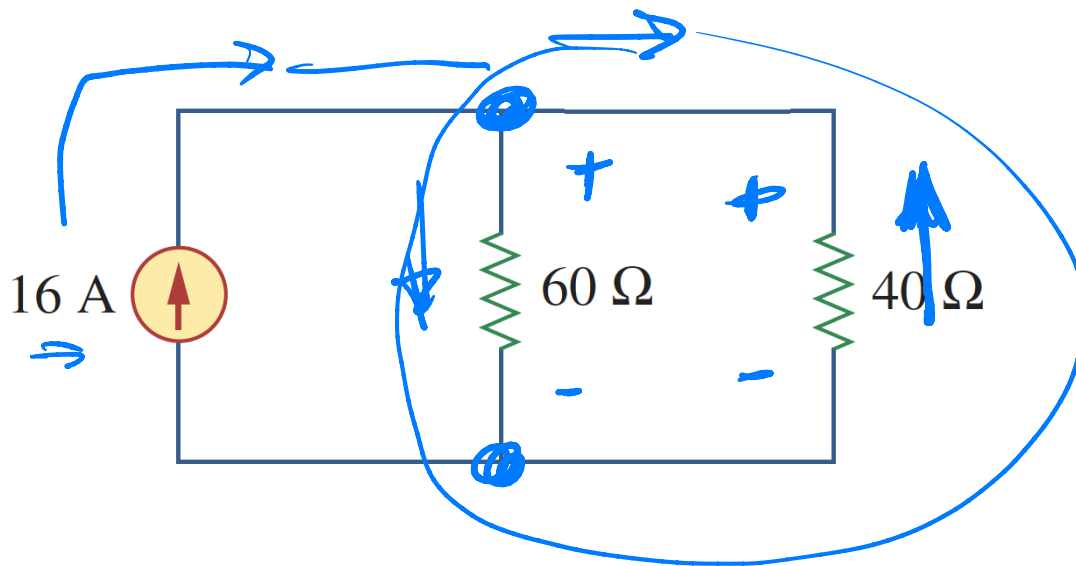


$$R_{eq} = \frac{60 \cdot 40}{60 + 40}$$


$$= \frac{2400}{100} = 24 \Omega$$

$$i_{60} = 16 \cdot \frac{40}{40 + 60}$$

$$i_{40} = 16 \cdot \frac{60}{40 + 60}$$


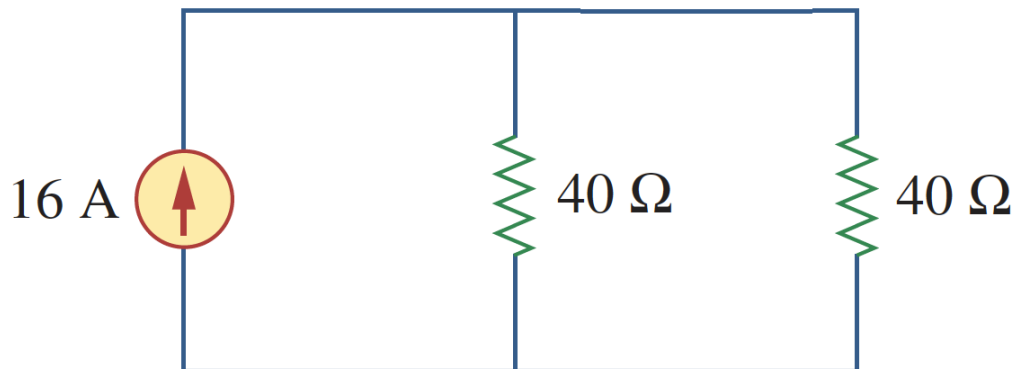


Example:

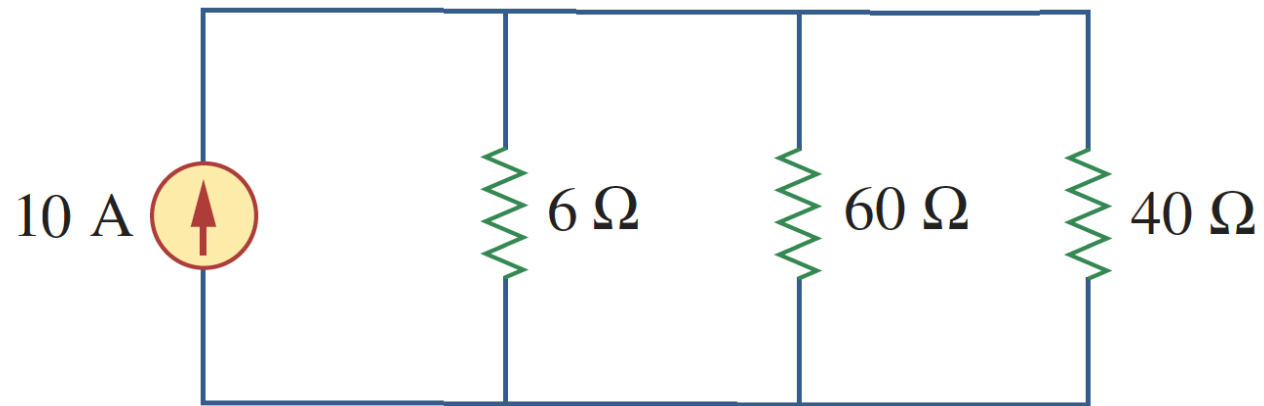


Series/Parallel Summary

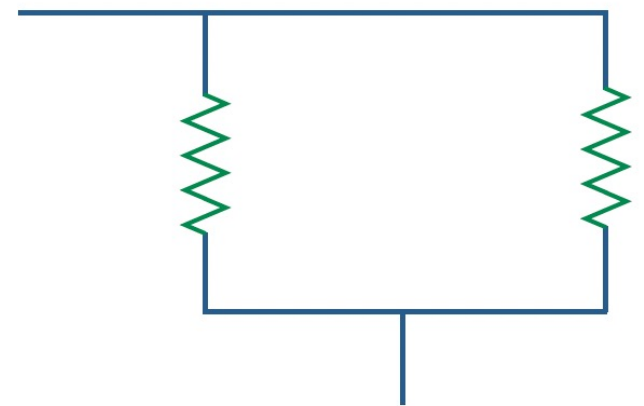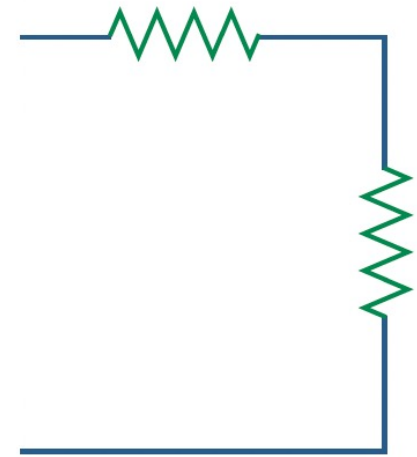- Series: resistances add
 - Nothing connected in the middle
 - **Same current (KCL)**
 - Voltage divides proportionally
- Parallel: resistances add inversely
 - Connected at both ends
 - **Same voltage (KVL)**
 - Current divides proportionally



Example: find v

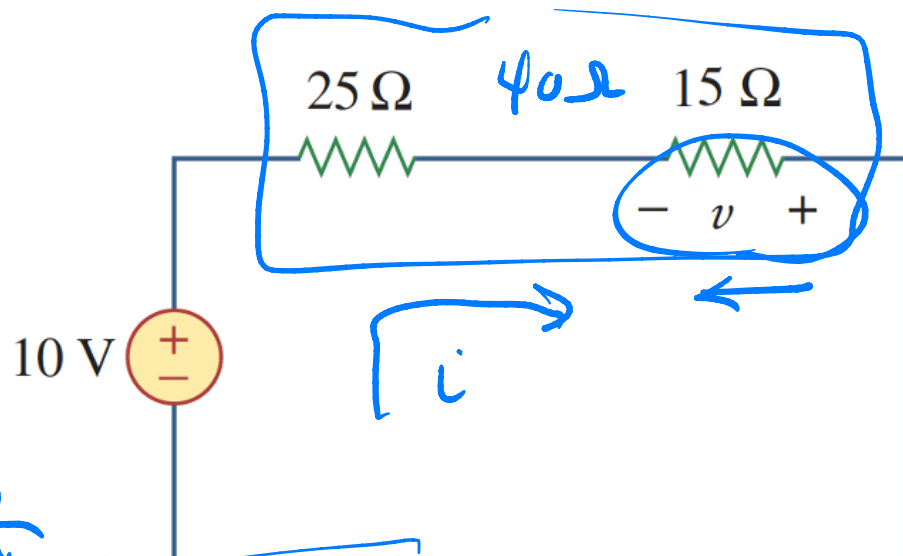

$$i = \frac{10}{40} = \frac{1}{4} \text{ A}$$

$$v_{15} = 15 \cdot (-i)$$
$$= 15 \cdot -\frac{1}{4} = -3.75 \text{ V}$$

Brute Force

$$-3.75 \text{ V}$$

$$v_{15} = 15 \cdot i_{15}$$

$$v_{25} = 25 \cdot i_{25}$$

$$i_{10} = -i_{25}$$


$$i_{15} = -i_{25}$$

$$10 - v_{25} + v_{15} = 0$$

$$v_2 = -\frac{15}{15+25} \cdot 10$$


27 W

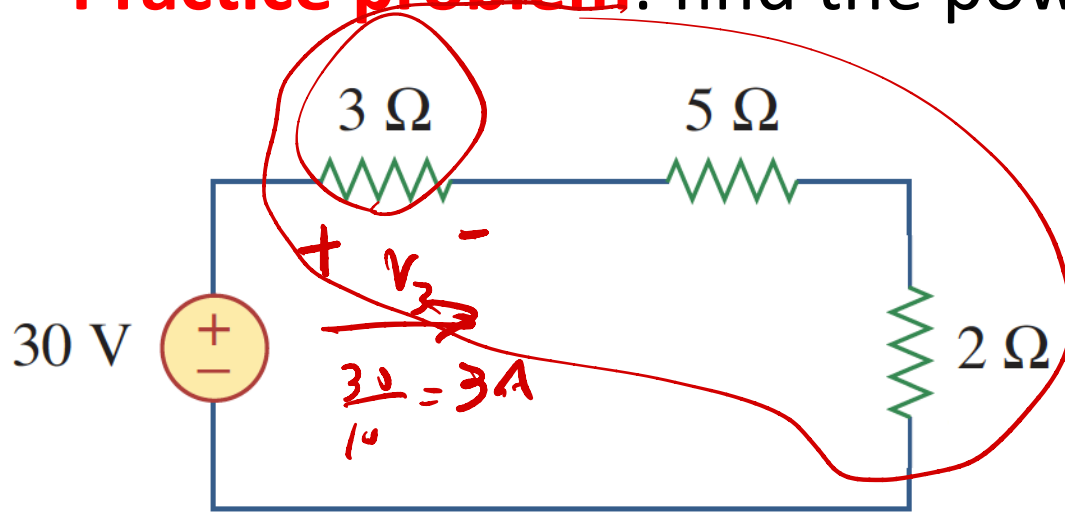Practice problem: find the power in the 3 Ω resistor



$$V_3 = 30 \cdot \frac{3}{10} = 9V$$


$$P = \frac{81}{3} = 27W$$

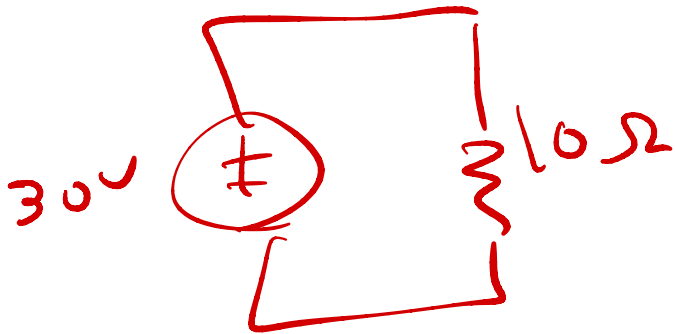

$$P = i^2 R = 3^2 \cdot 3 = 27W$$

20 V

Practice problem: find v

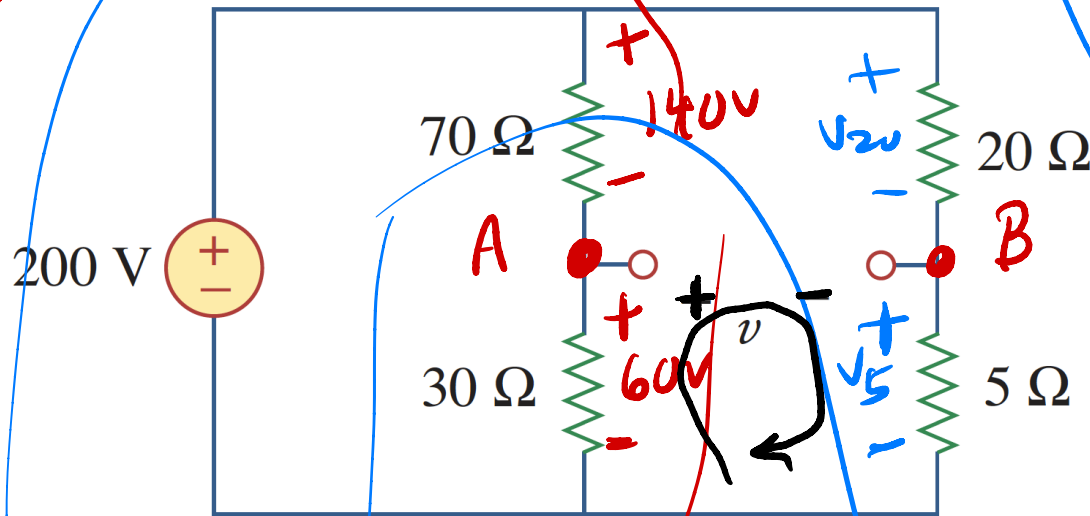

use voltage div.

$$V_{30} = 200 \cdot \frac{30}{100} = 60 \text{ V}$$

$$V_{70} = 200 \cdot \frac{70}{100} = 140 \text{ V}$$

use voltage div
or right

$$V_5 = 40 \text{ V}$$

$$V_{20} = 160 \text{ V}$$

KVL

$$V_{30} - v - V_5 = 0$$

$$v = V_{30} - V_5 = 60 - 40 = 20 \text{ V}$$

3.2 kW

Practice problem: find the power in the 50 Ω resistor

