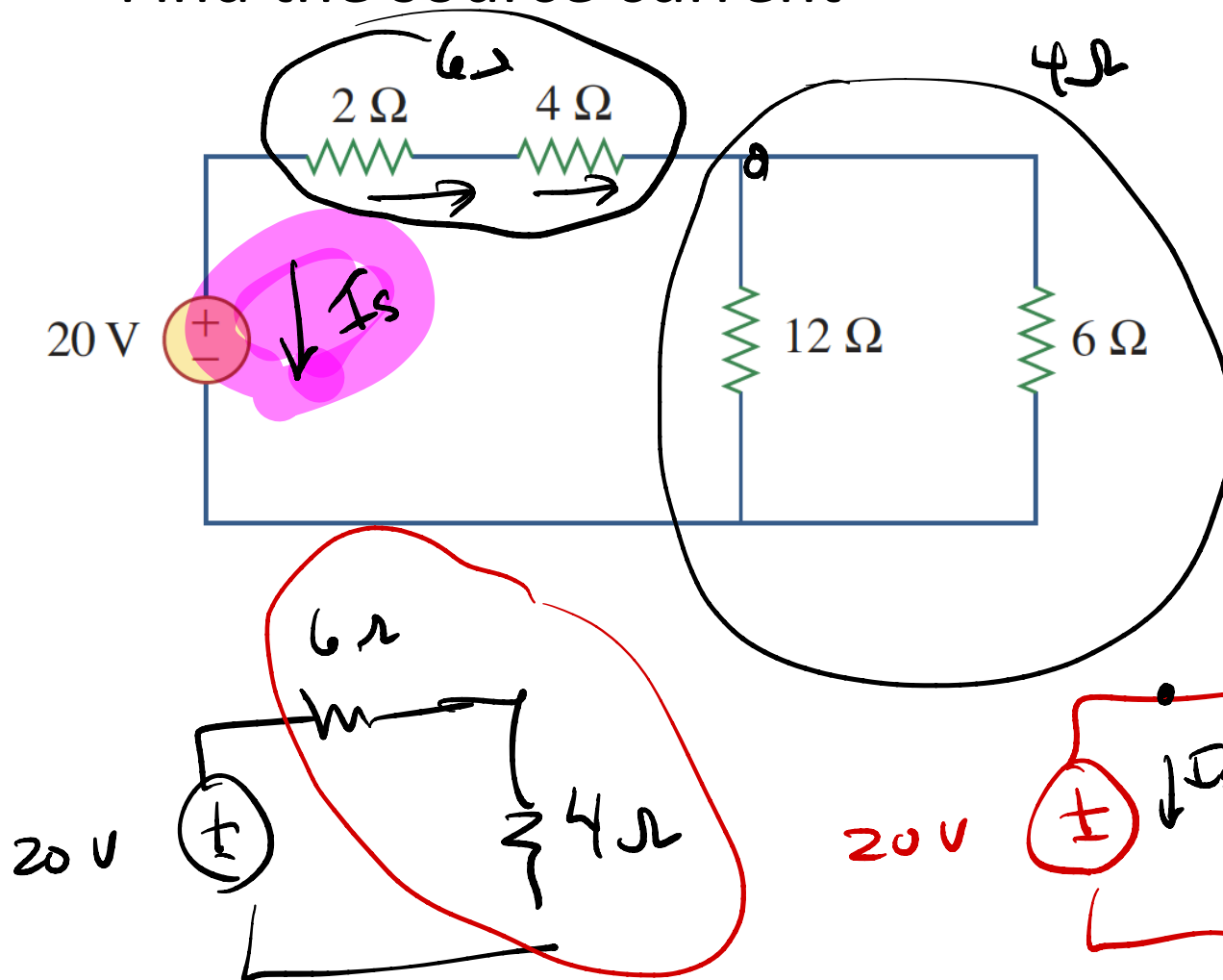


Basics – 5

equivalent resistance

Applying Series/Parallel Ideas

- Find the source current



1- series R

$$2 + 4 = 6 \Omega$$

2- parallel R

$$\frac{12 \cdot 6}{12 + 6} = 4 \Omega$$

3- series R

$$6 + 4 = 10 \Omega$$

4- KVL
 $V_R = 20V$

5- Ohm
 $I_s = 2A$


6- KCL $I_s = -2A$

Example: find the source power

1 - series

2 - parallel


3 - series

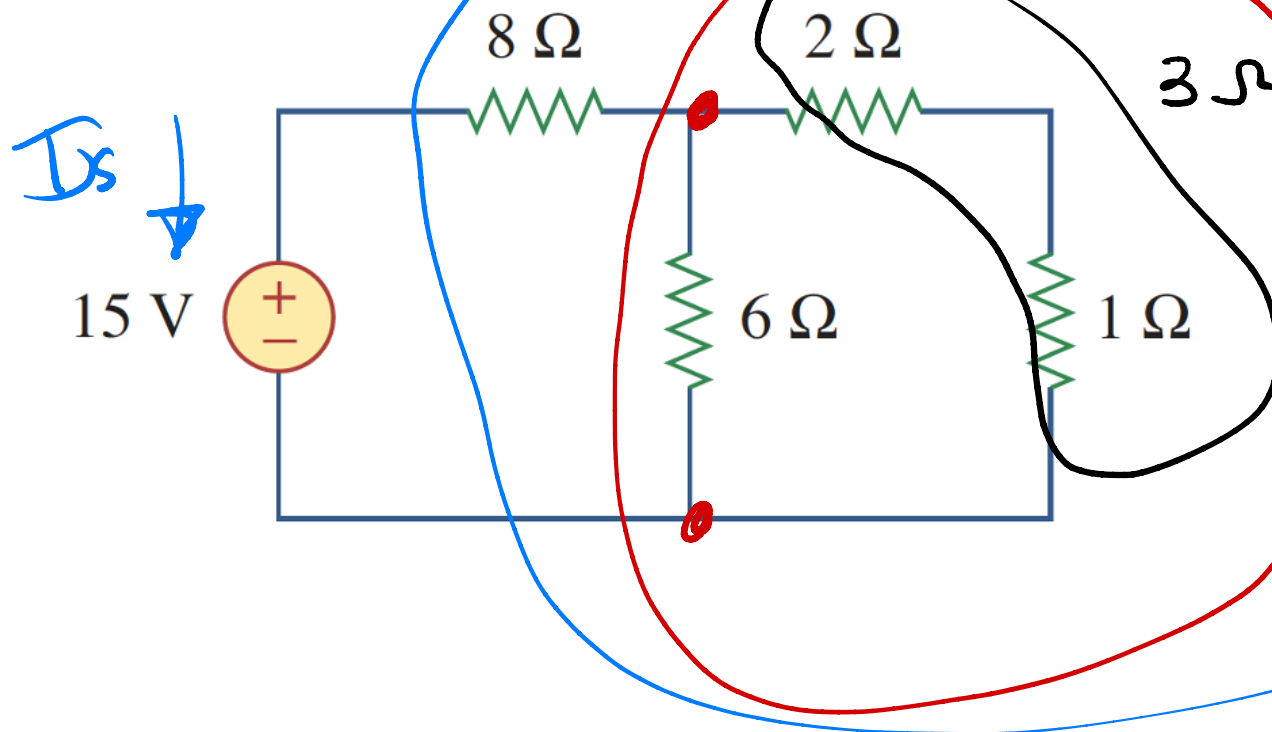

10Ω

2Ω

4 - $I_s = -1.5A$

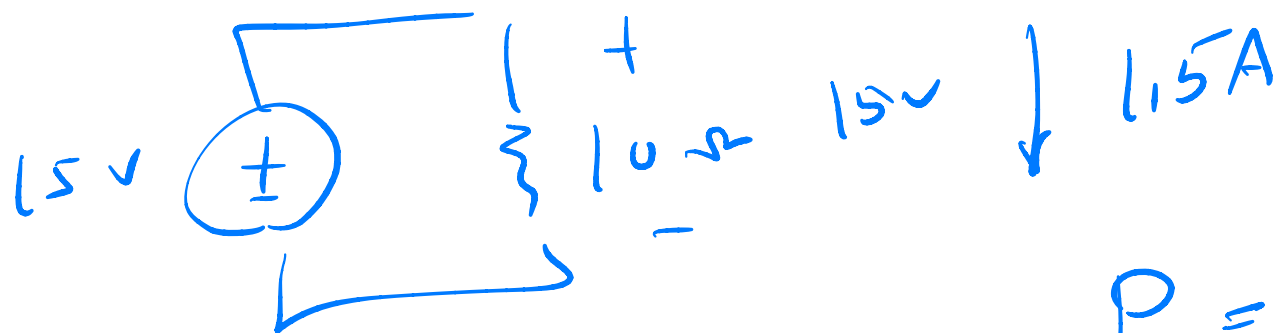


$$P_s = V \cdot I_s$$


$$= 15 \cdot -1.5 = -22.5 \text{ W}$$

Equivalent Resistance

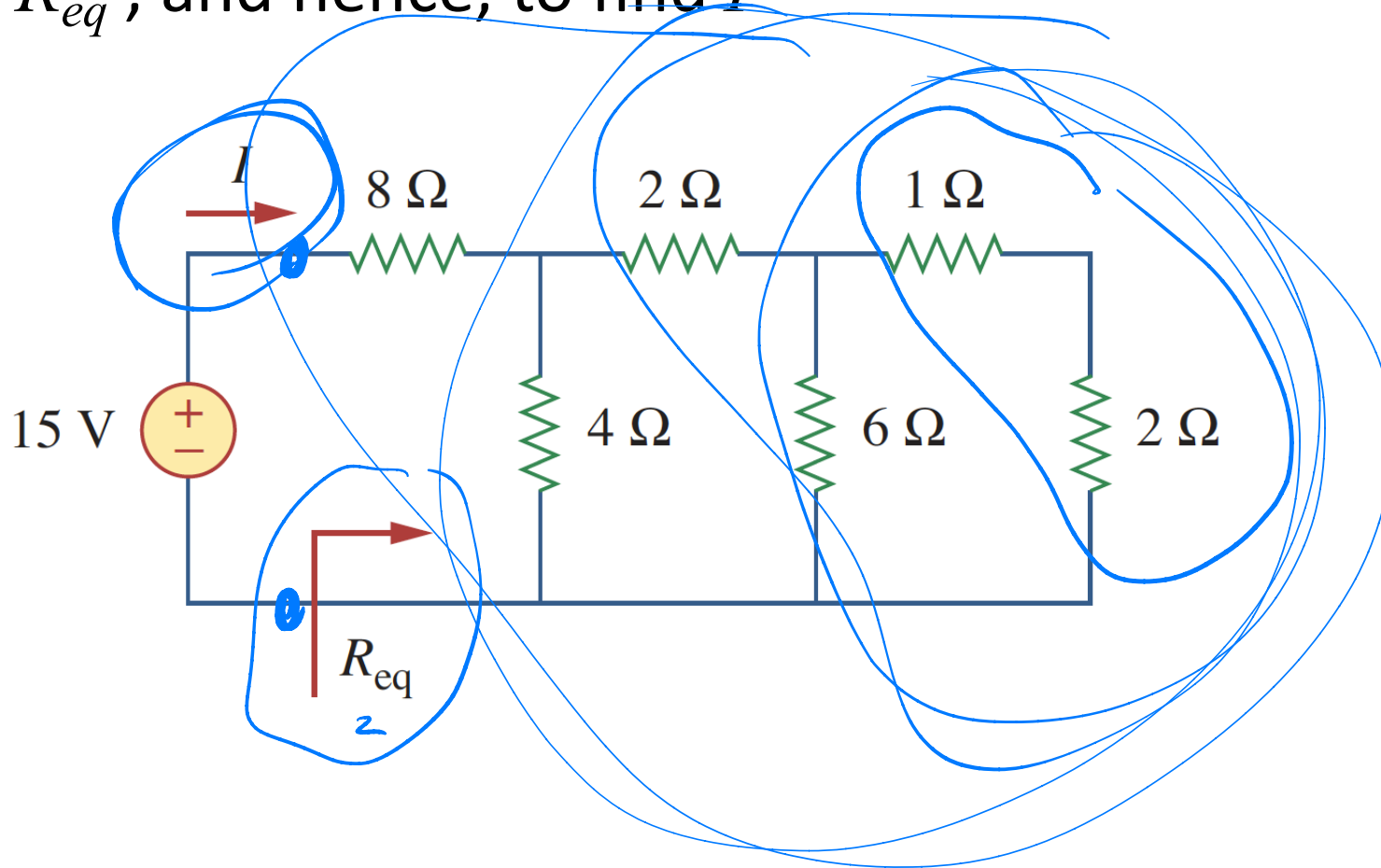
- Concept – use series and parallel combining to find R_{eq} , and hence, to find I






Example:

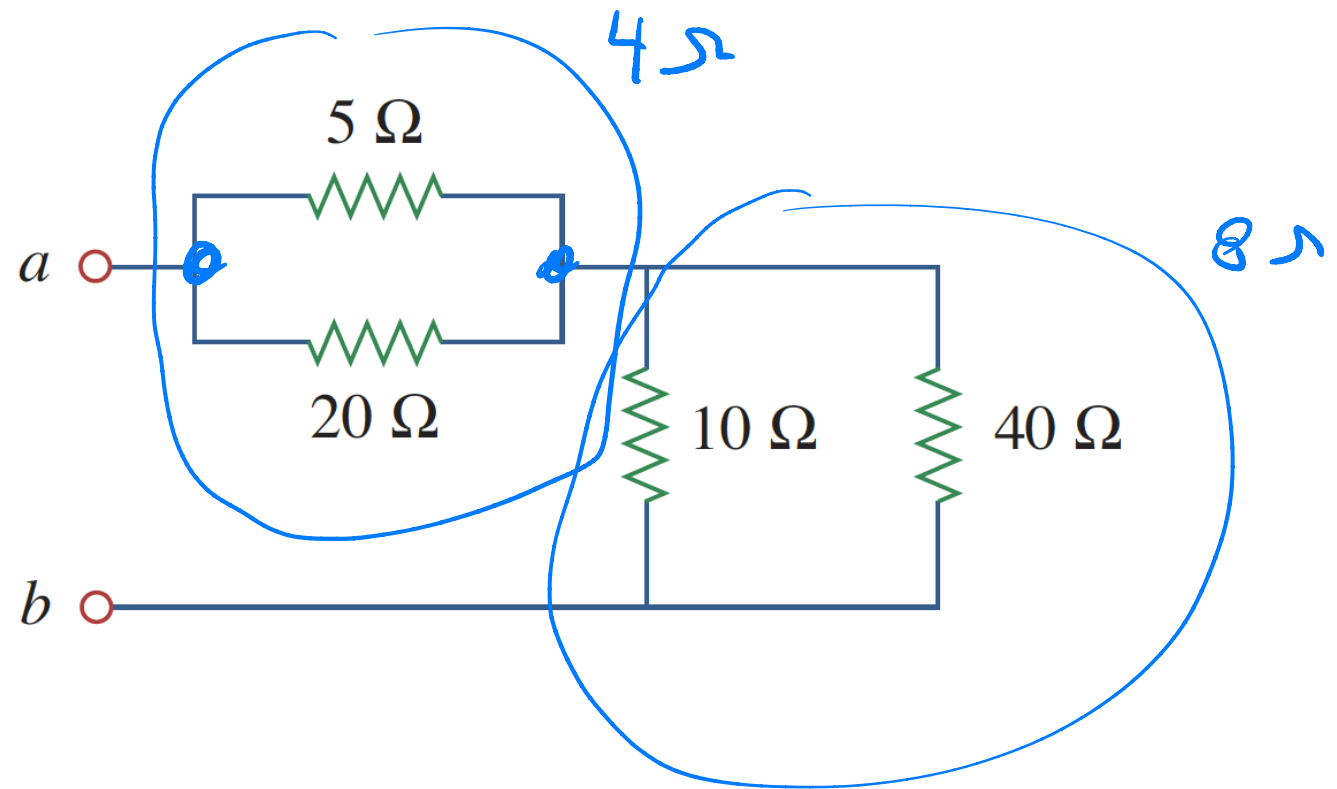

$$R_{eq} = 12\ \Omega$$

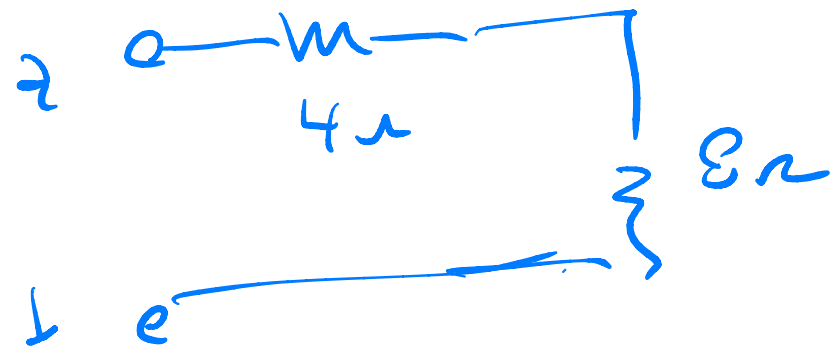

Sometimes the circuit looks strange

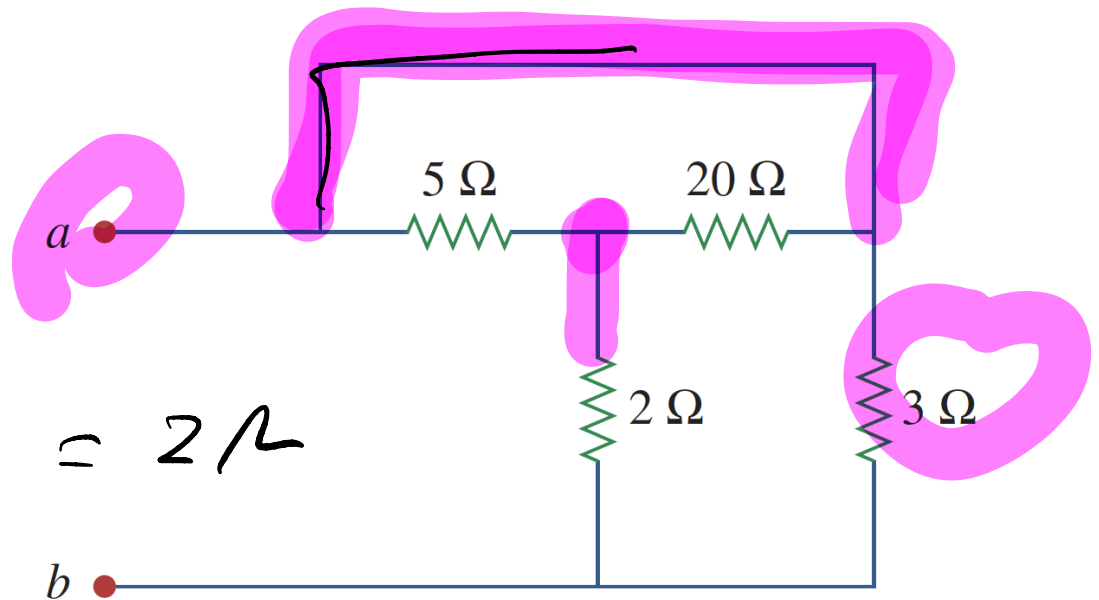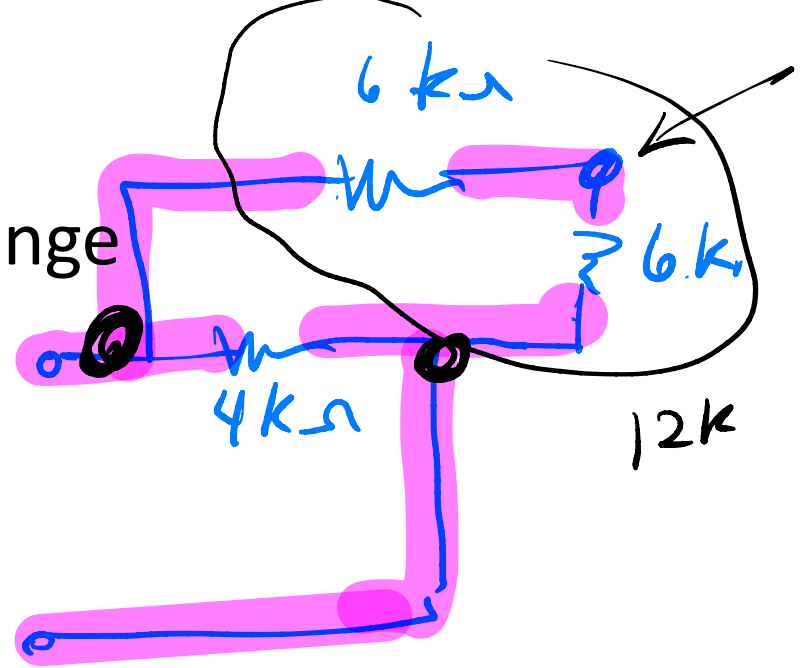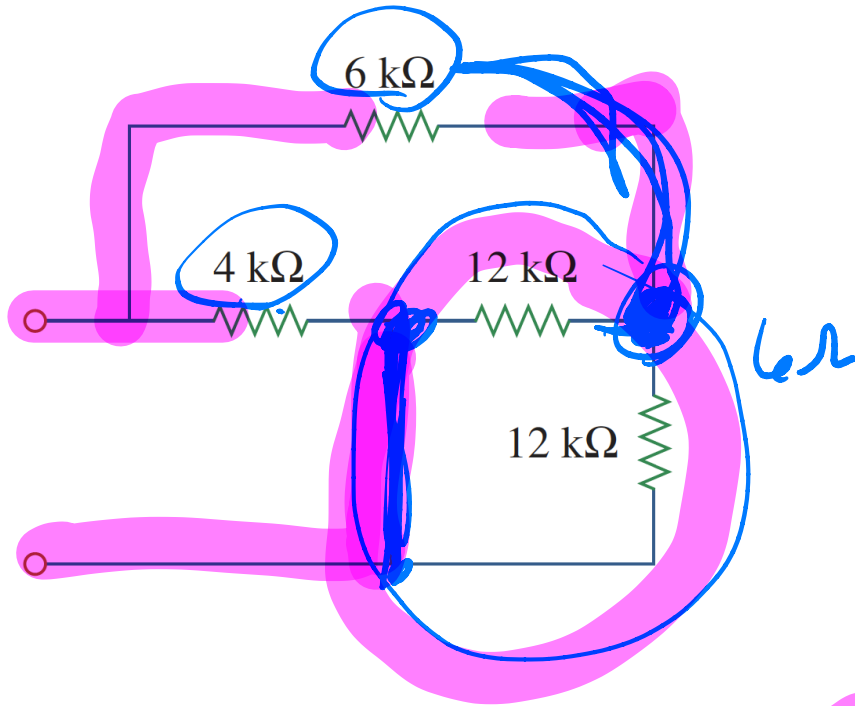


$$= 2\text{ }\Omega$$

$$= \frac{35}{R_{eq}}$$


$$R_{eq} = 10 \Omega$$


Example: find R_{eq} and i_o

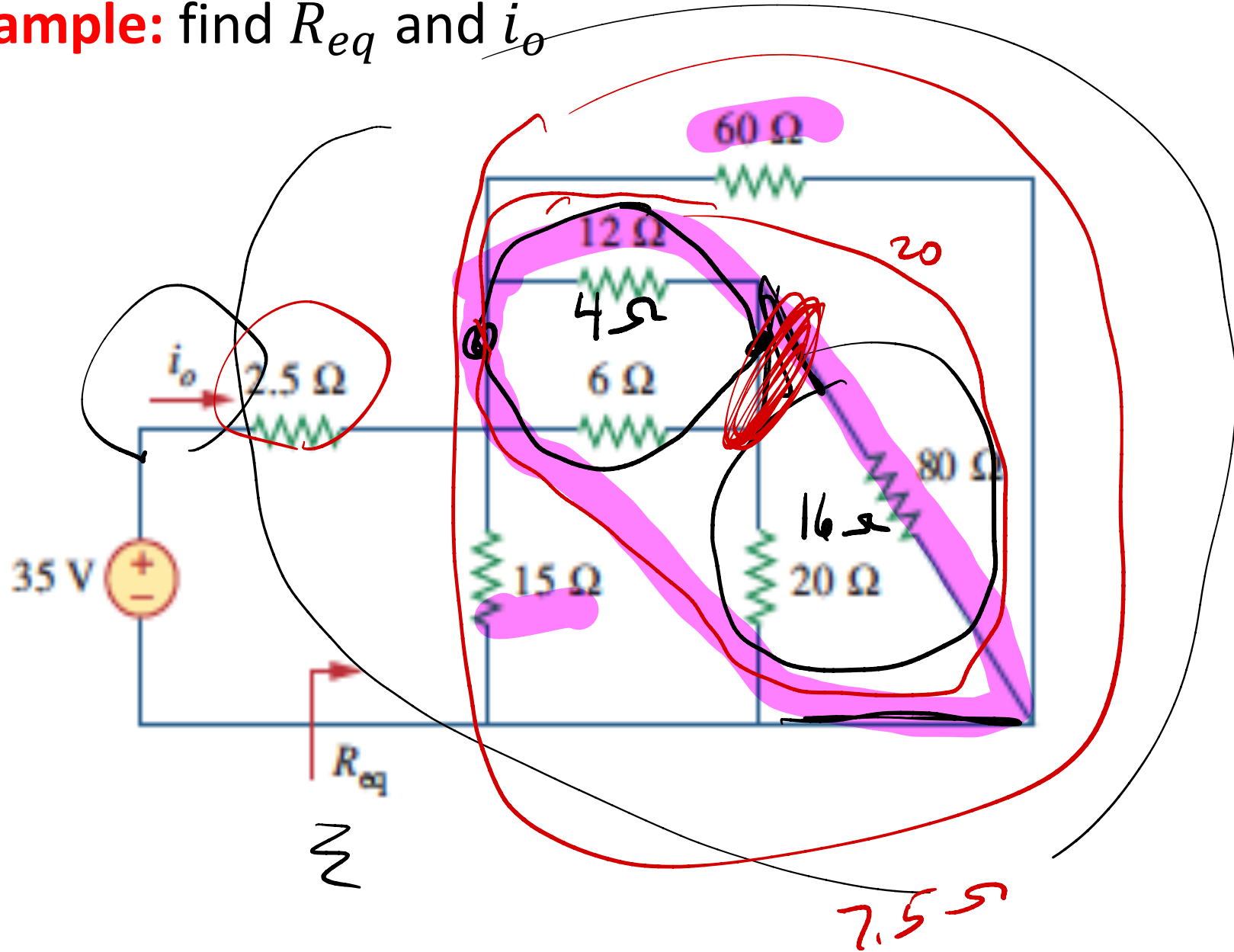


Circuit Analysis

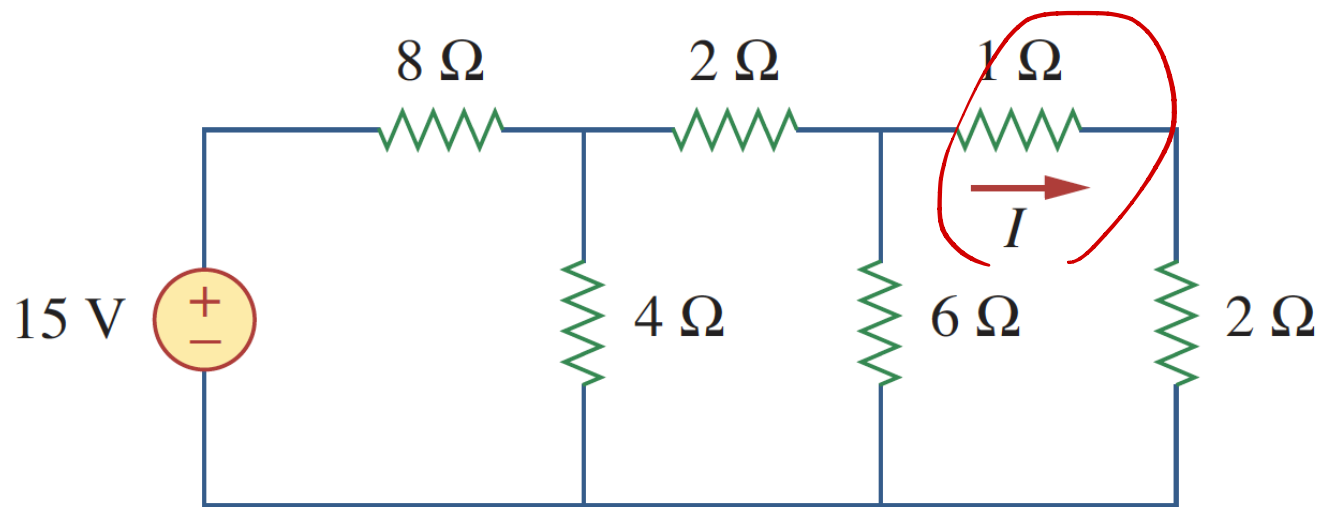- Sometimes we can do a full analysis using just series/parallel combining and voltage/current division
- Example: find I (next slide)




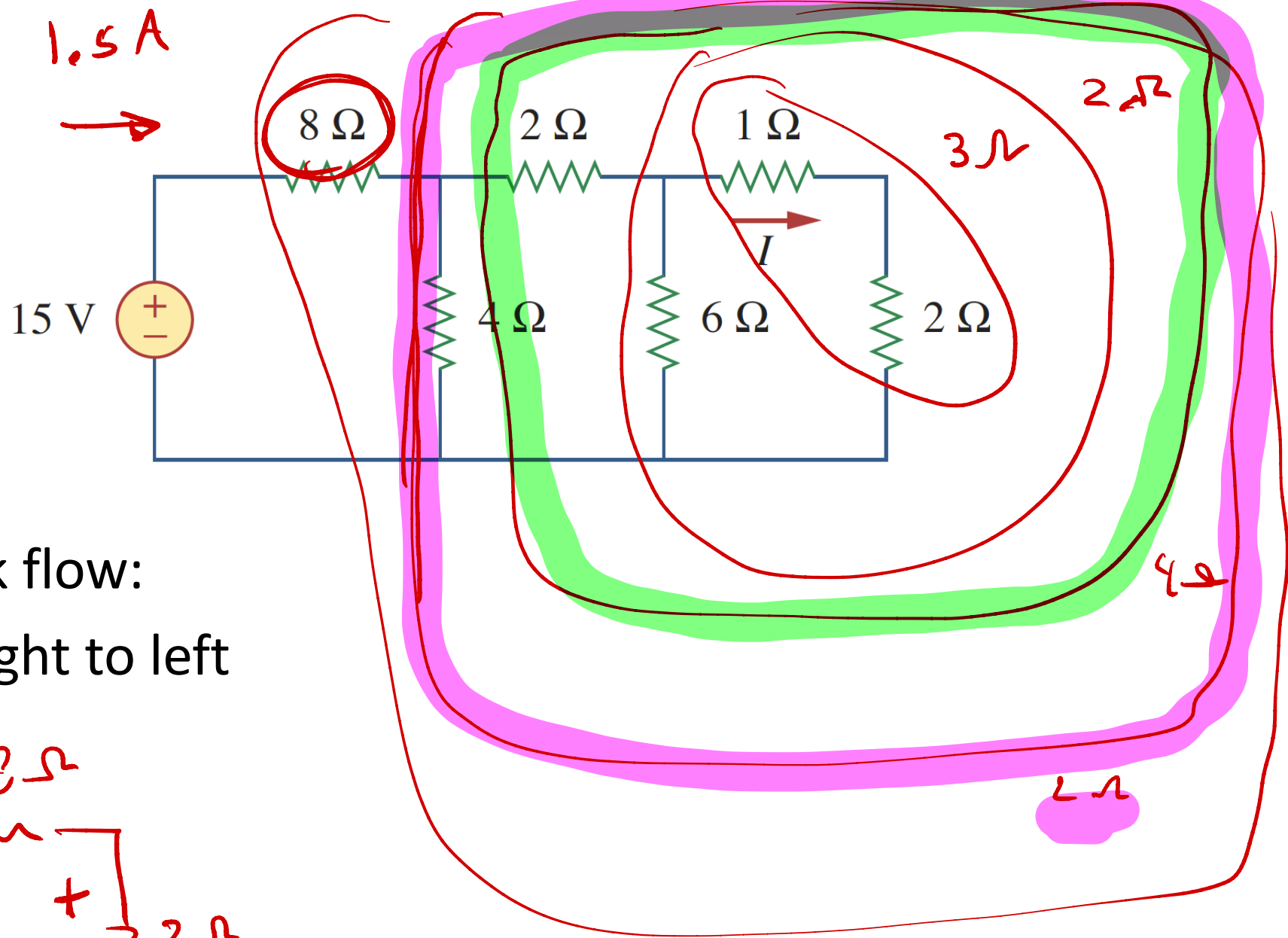

- Work flow:
– Right to left

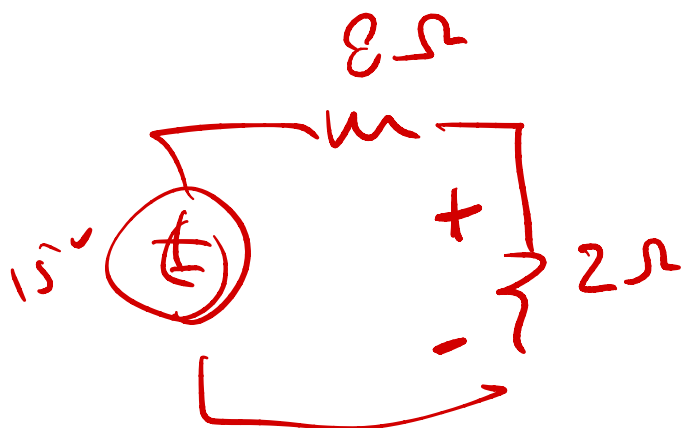

$$R_{eq} = 10\ \Omega$$


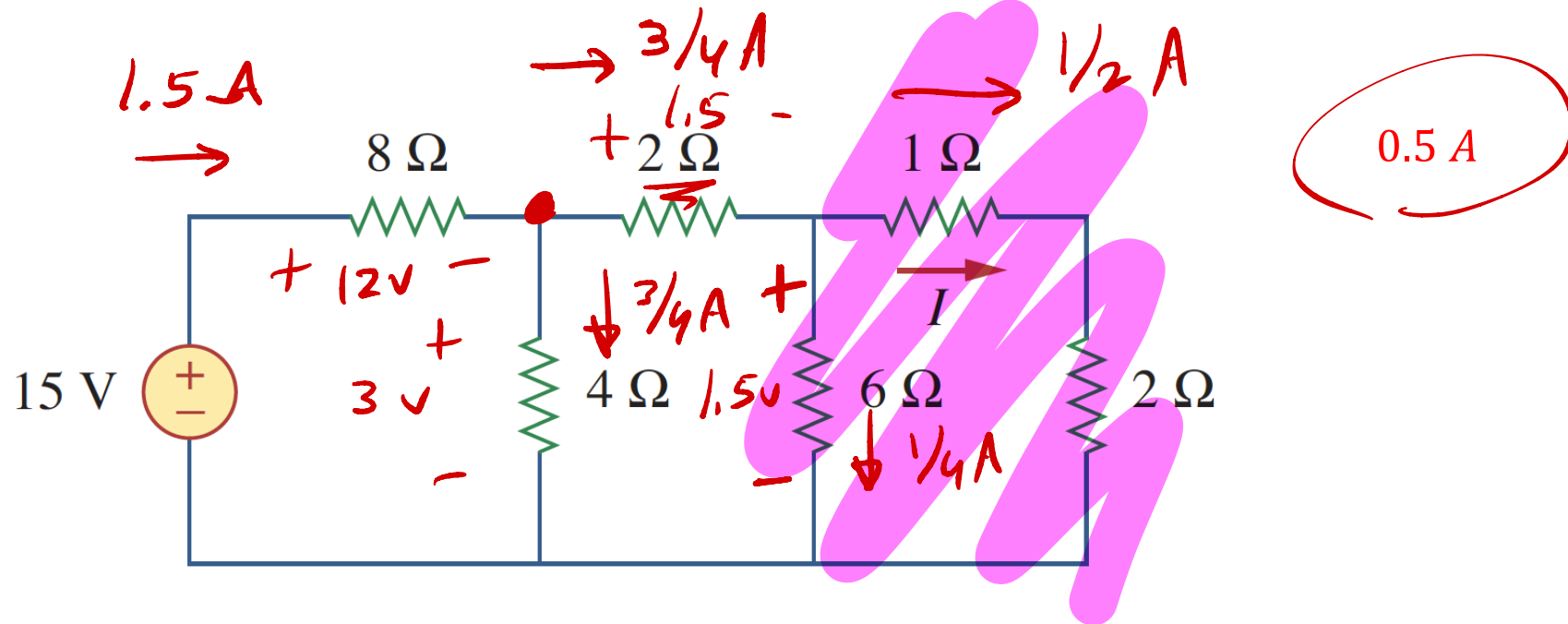


- Work flow:
 - Left to right

~~12 Ω , 15 Ω~~


Practice problems: find the equivalent resistances

16 Ω

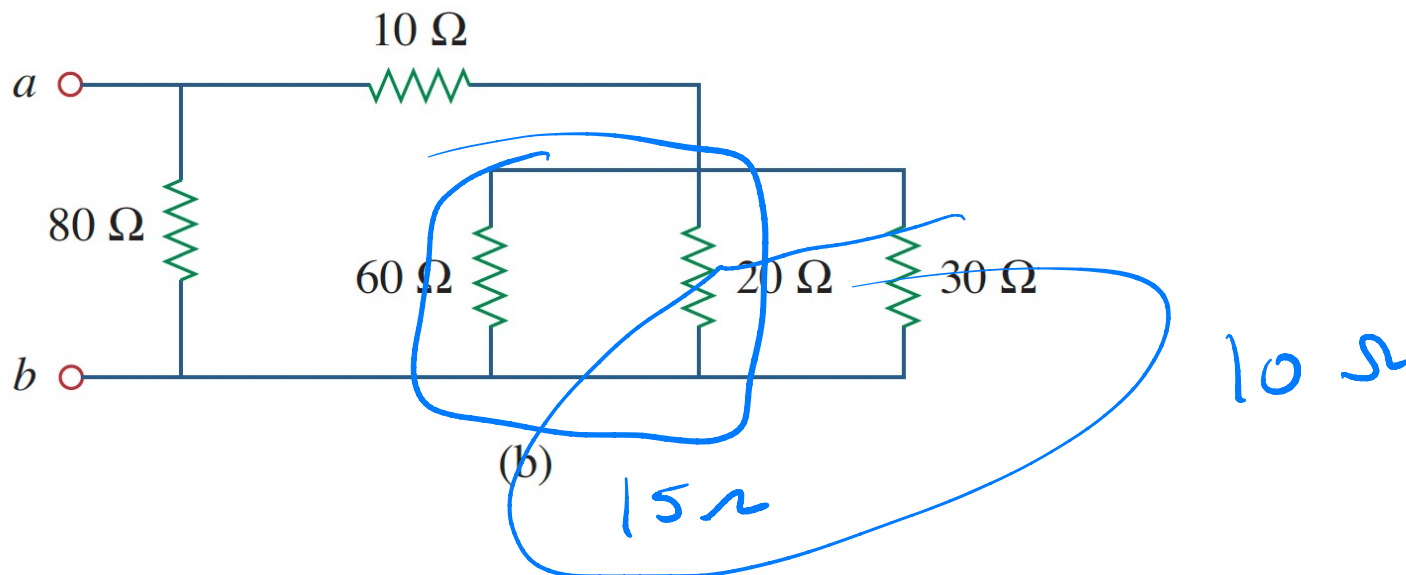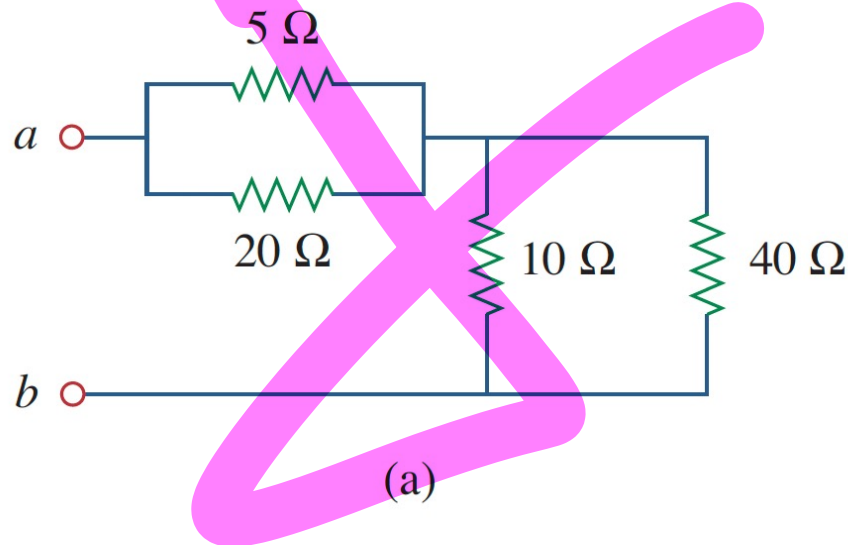


13 Ω

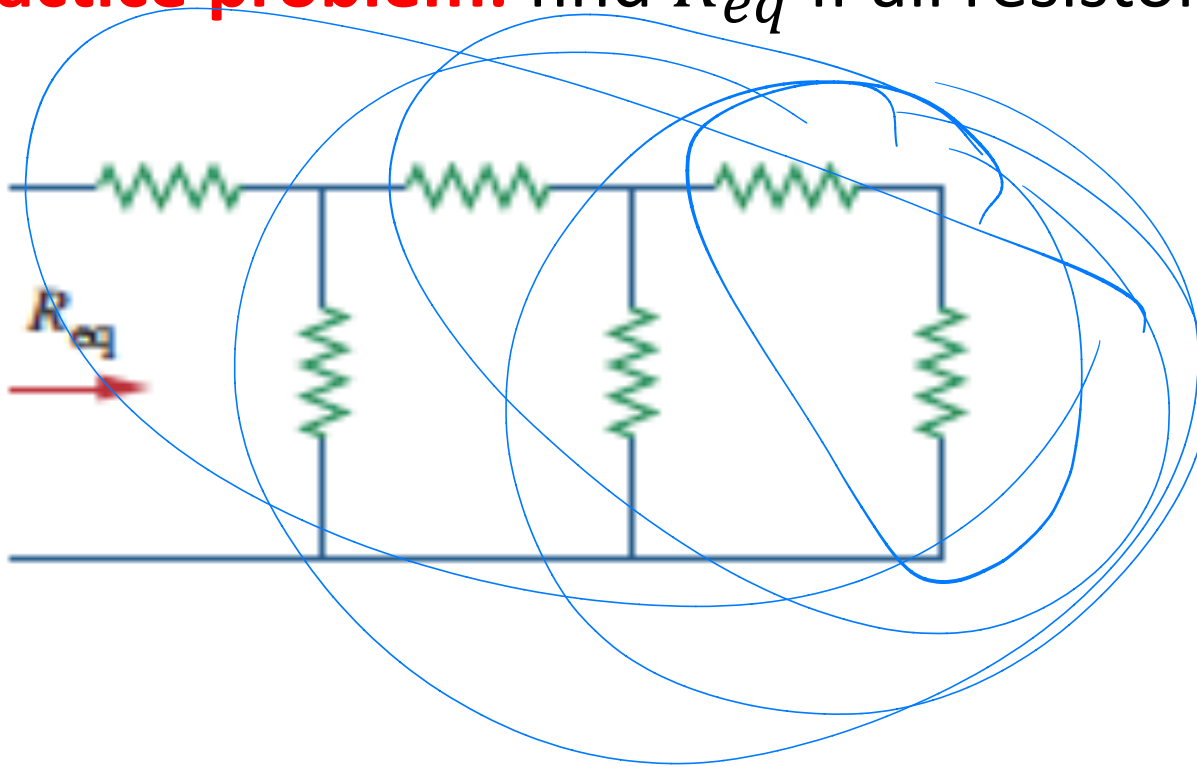Practice problem: find R_{eq} if all resistors are 8 Ω




16 Ω

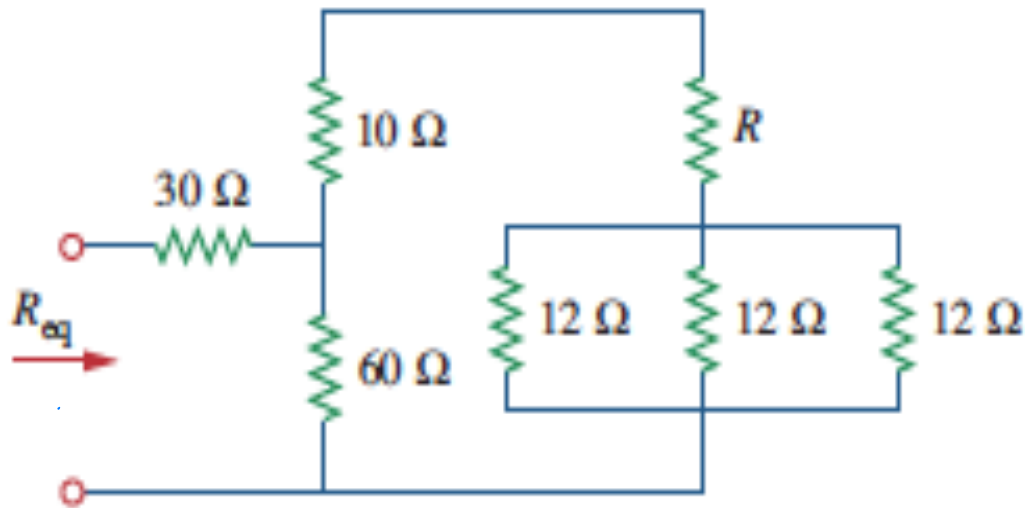Practice problem: if $R_{eq} = 50 \Omega$, find R




2.5 A

Practice problem: find I

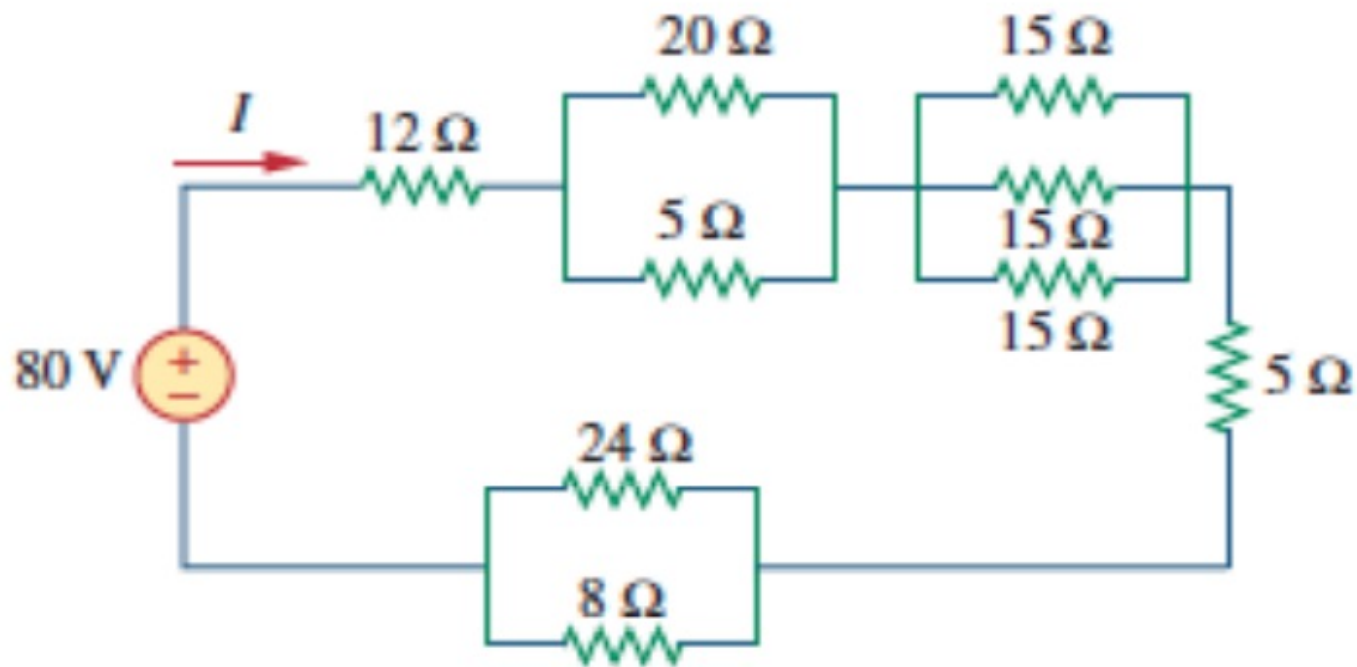


24 Ω

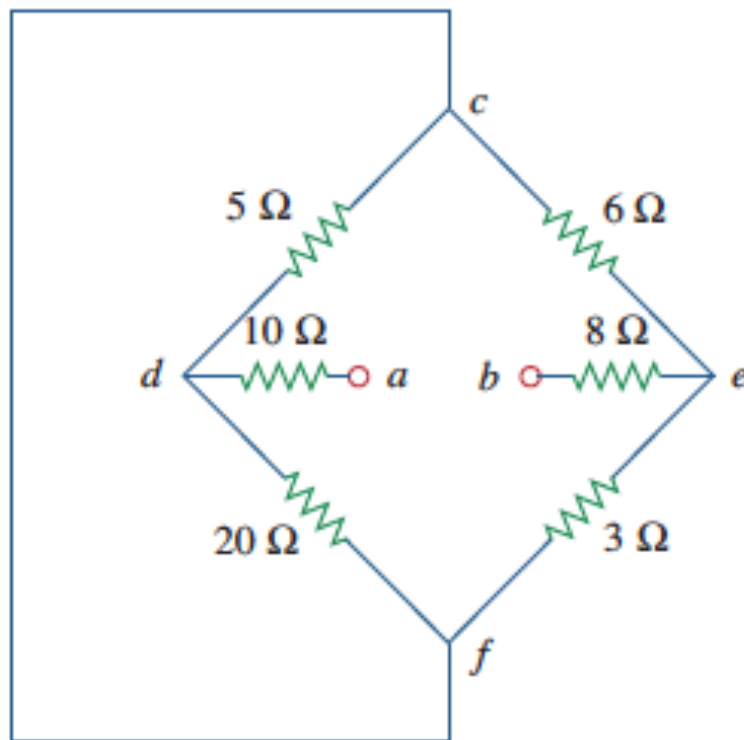Practice problem: find the equivalent resistance at $a-b$



−400 W

Practice problem: find the source power

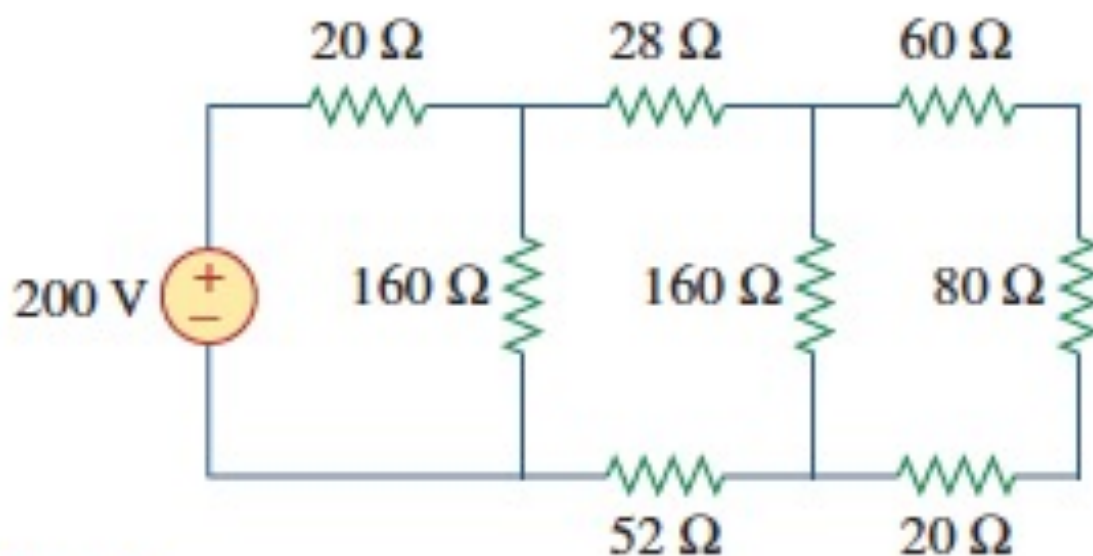

20 V

Practice problem: find v

