
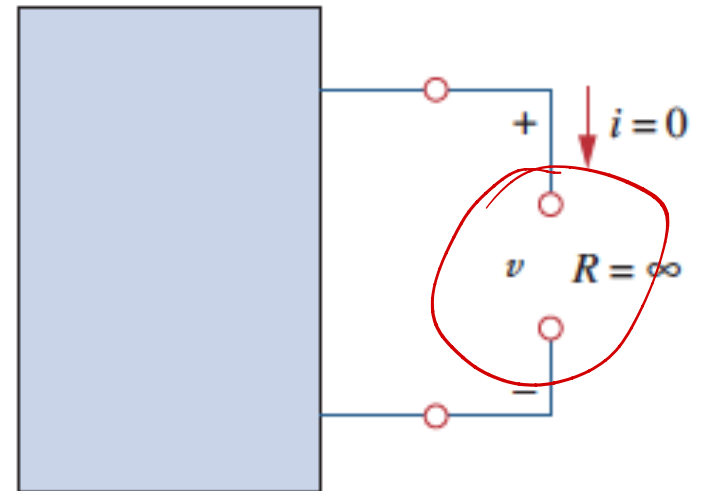


Basics – 7

odds and ends


Special Cases

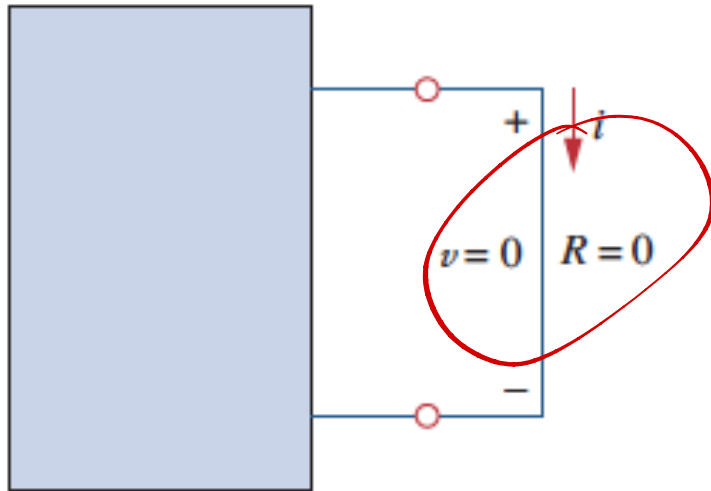- Short circuit ($R = 0$)
- Open circuit ($R = \text{infinity}$)




- Voltage division

$$v_1 = \frac{R_1}{R_1 + R_2} v$$

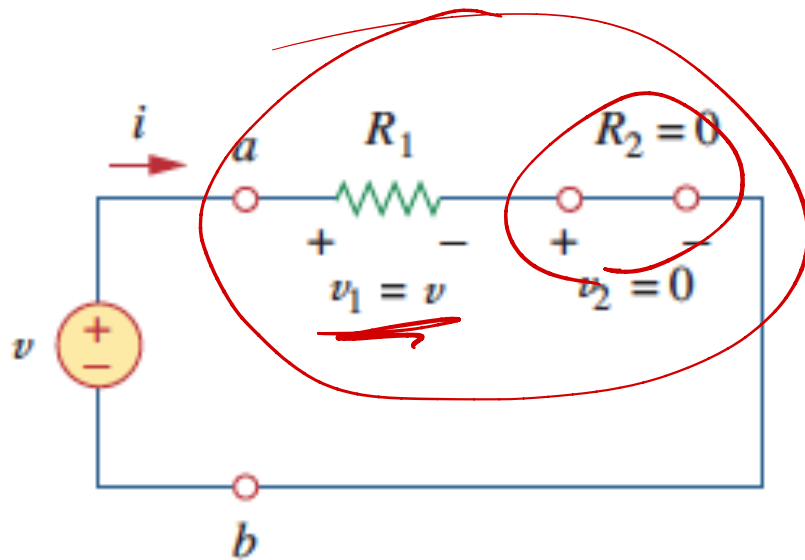



$$v_2 = \frac{R_2}{R_1 + R_2} v$$

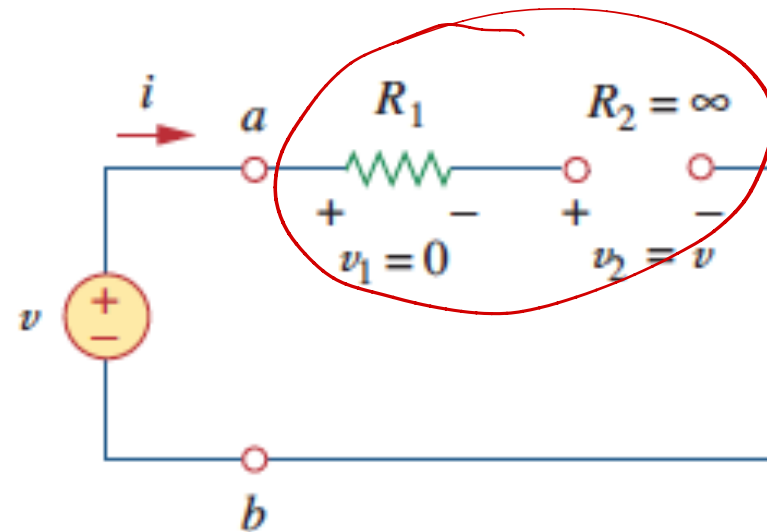


- Current division

$$i_1 = \frac{R_2}{R_1 + R_2} i$$

$$i_2 = \frac{R_1}{R_1 + R_2} i$$

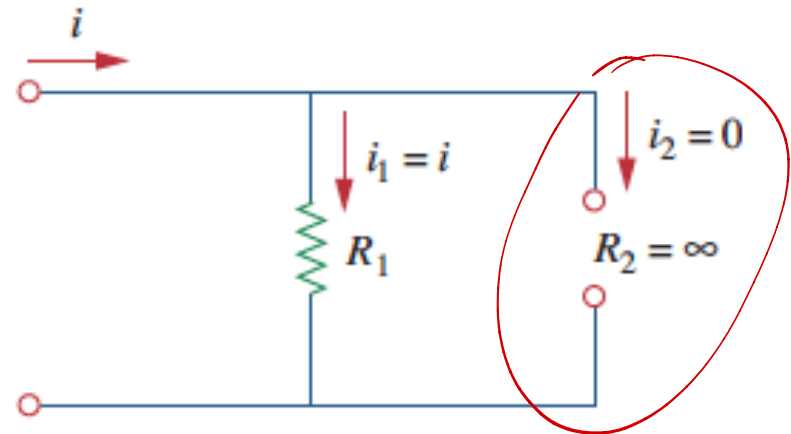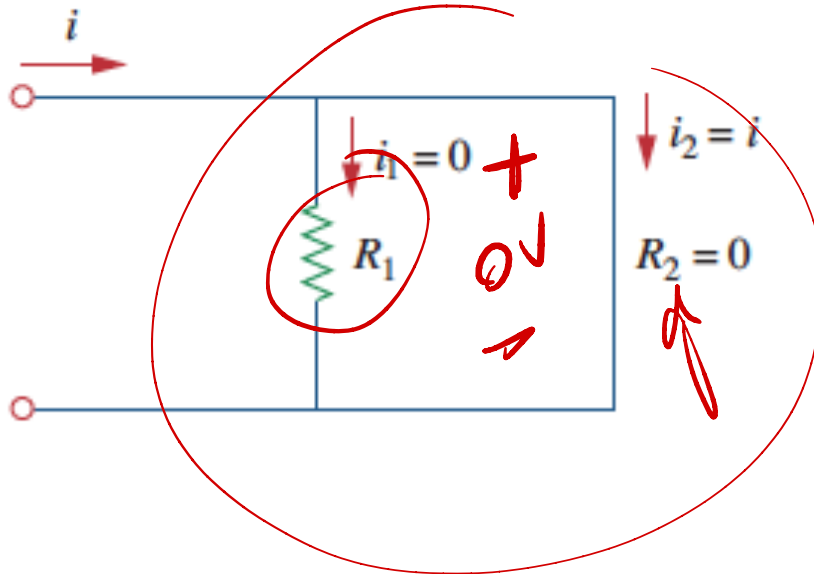

Example:

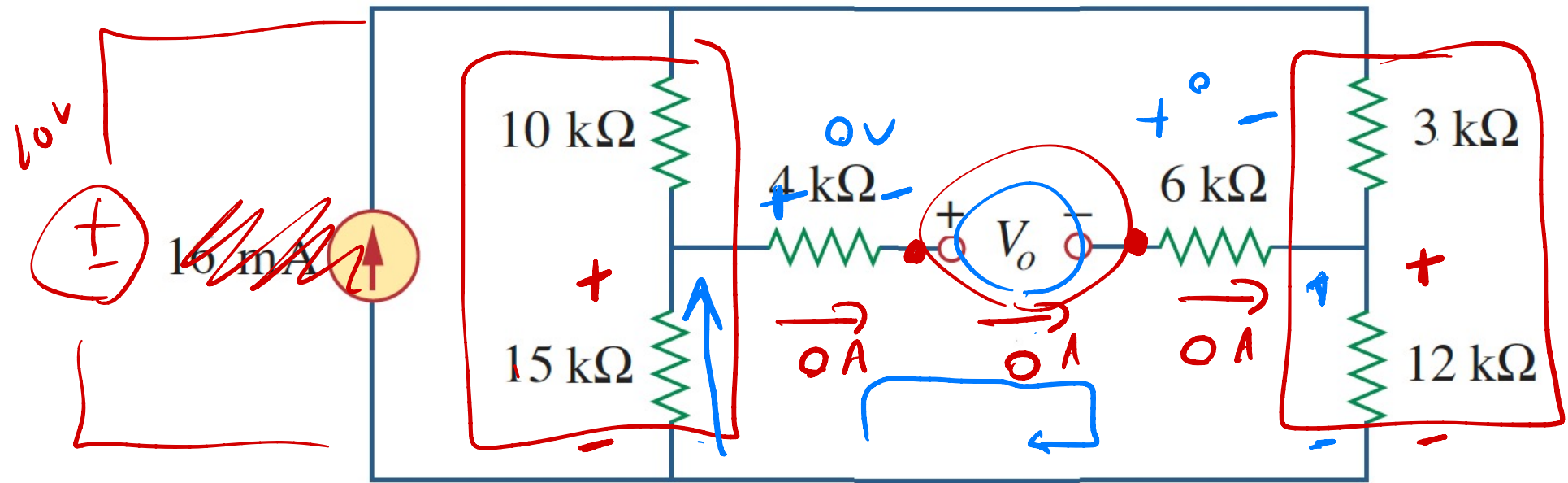

$$\frac{15}{25} \cdot 10 = 6V$$


$$10 \cdot \frac{12}{15} = 8V$$

KVL:

$$6 - 0 - V_o - 0 - 8 = 0$$

$$-2V = V_o$$


Example: find i and v

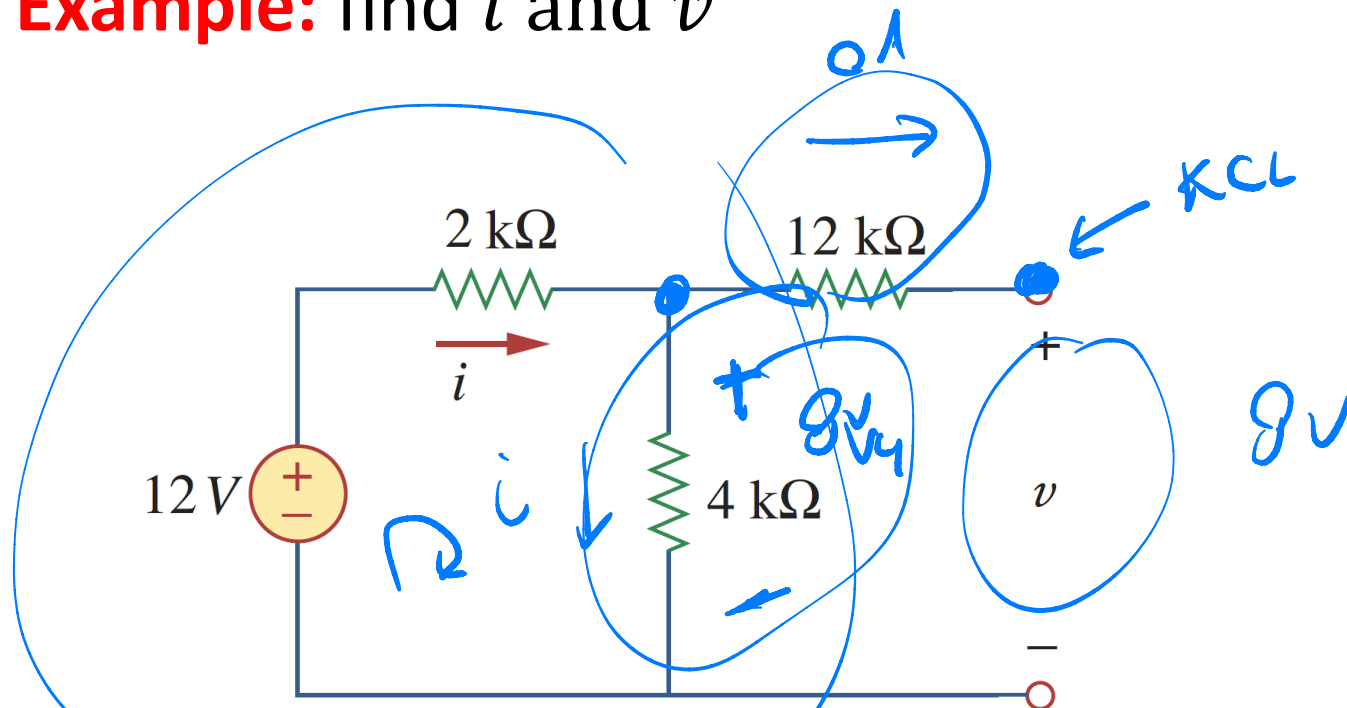




$$12 - 2000i - 4000i = 0$$

$$V_4 = \frac{4000}{2+4} \cdot 12 = 8V$$

Do We Allow Series Sources?


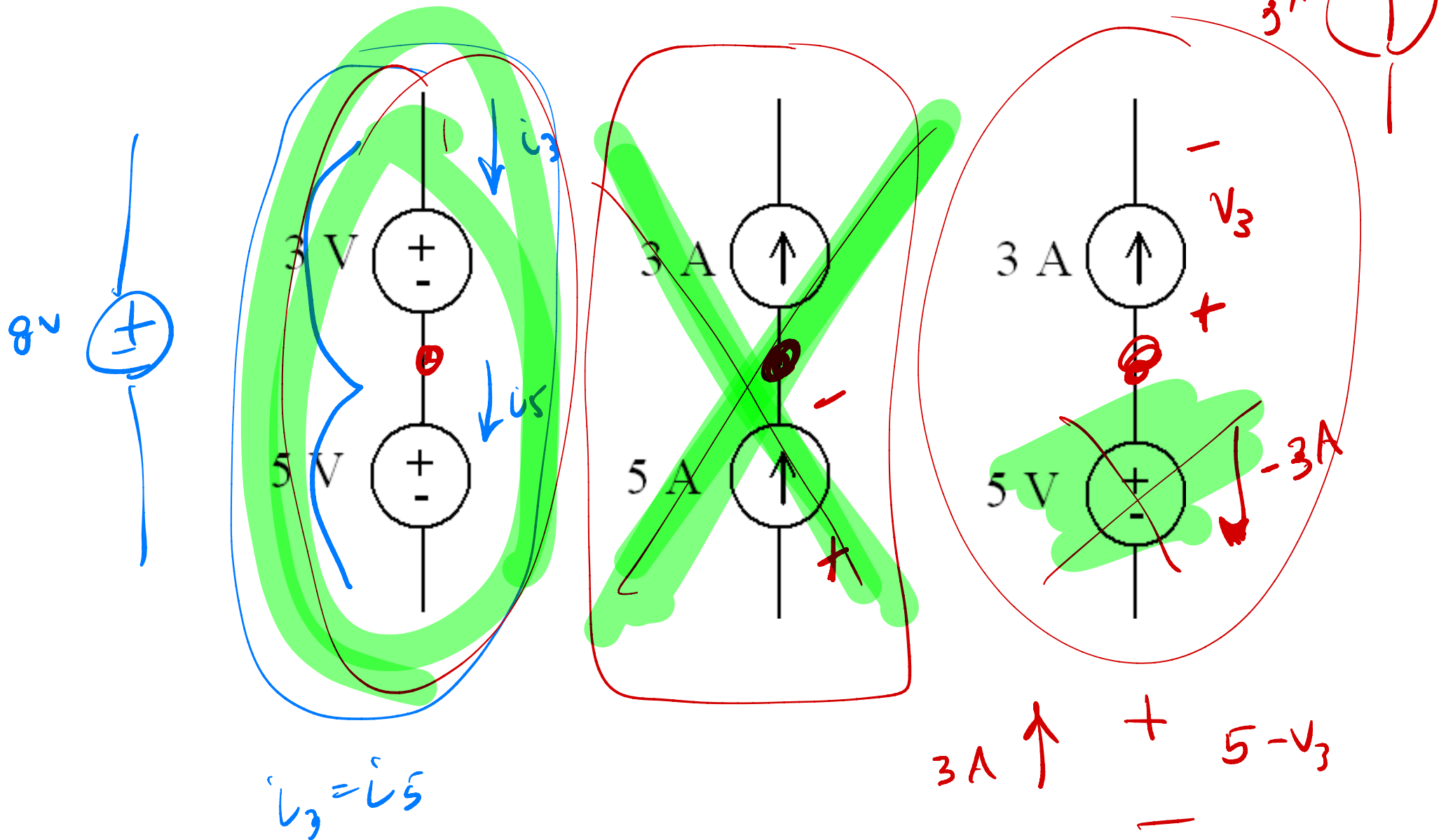


How about parallel sources?

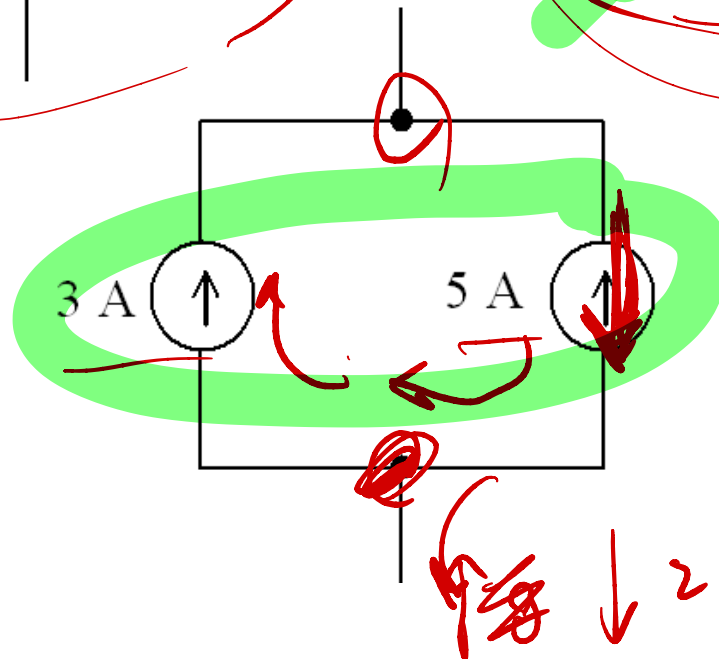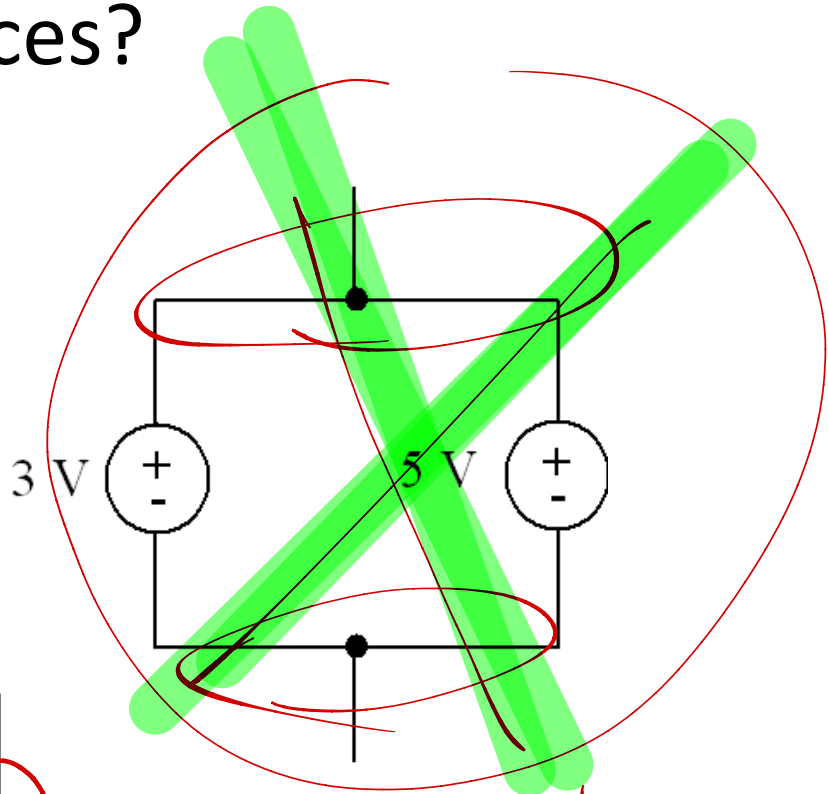
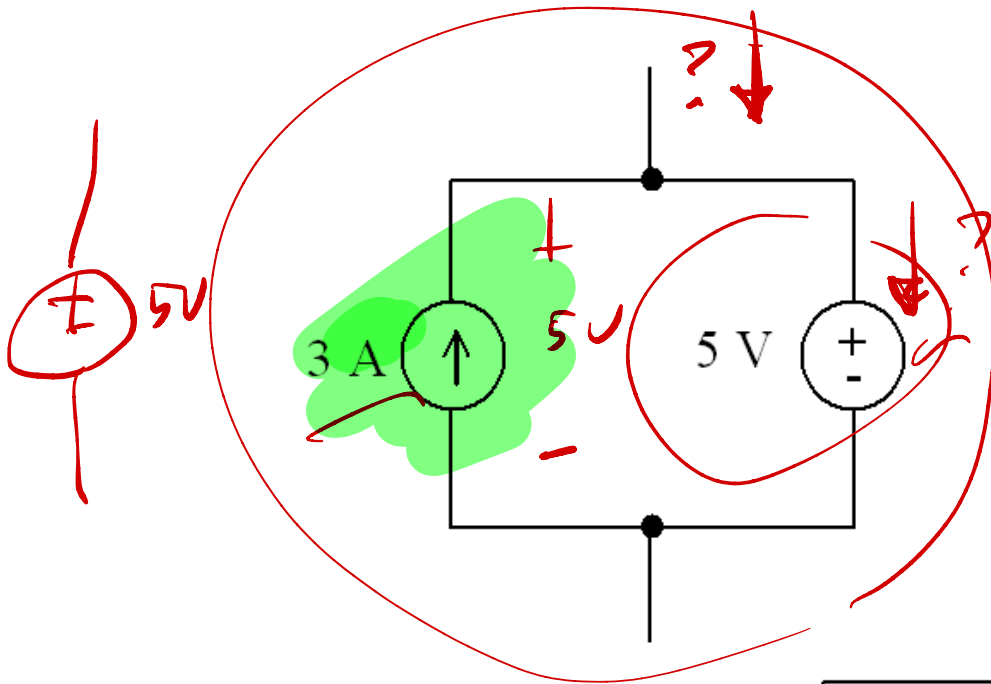


↑ 81



How about resistors and sources?

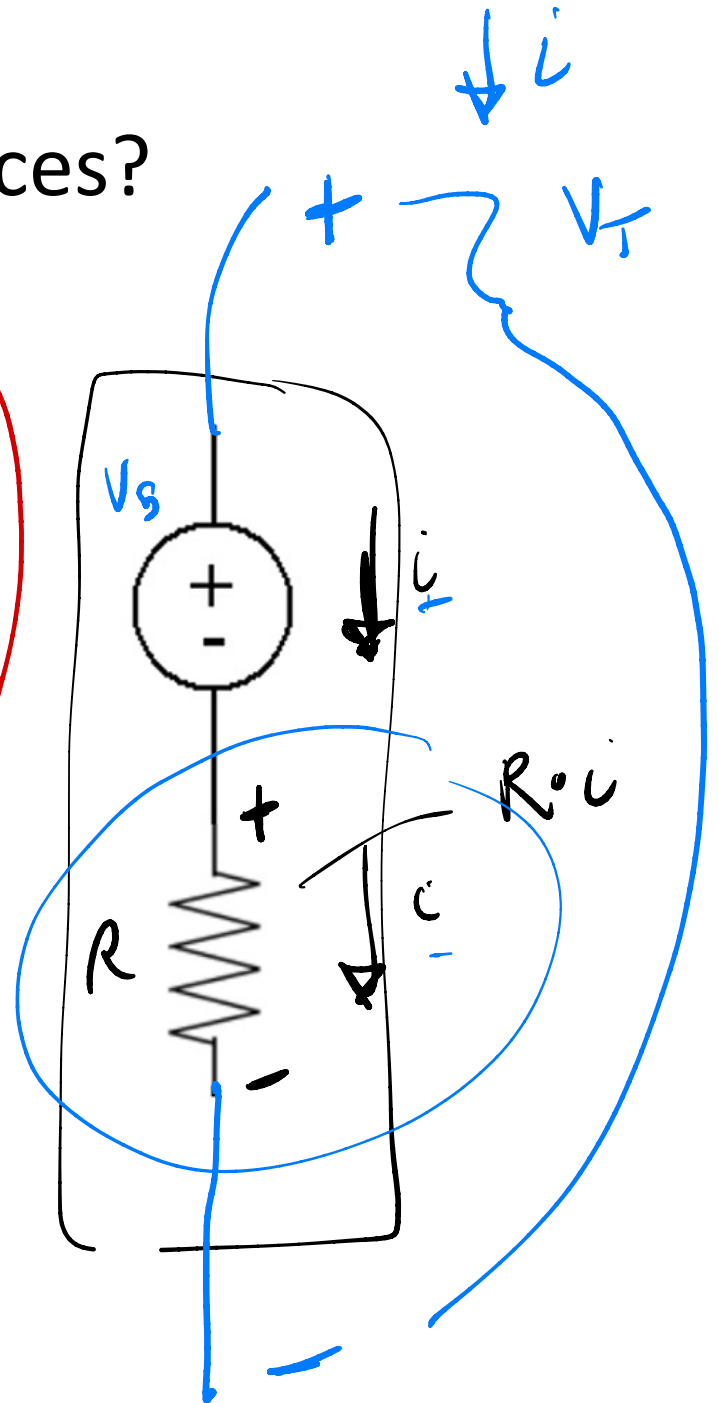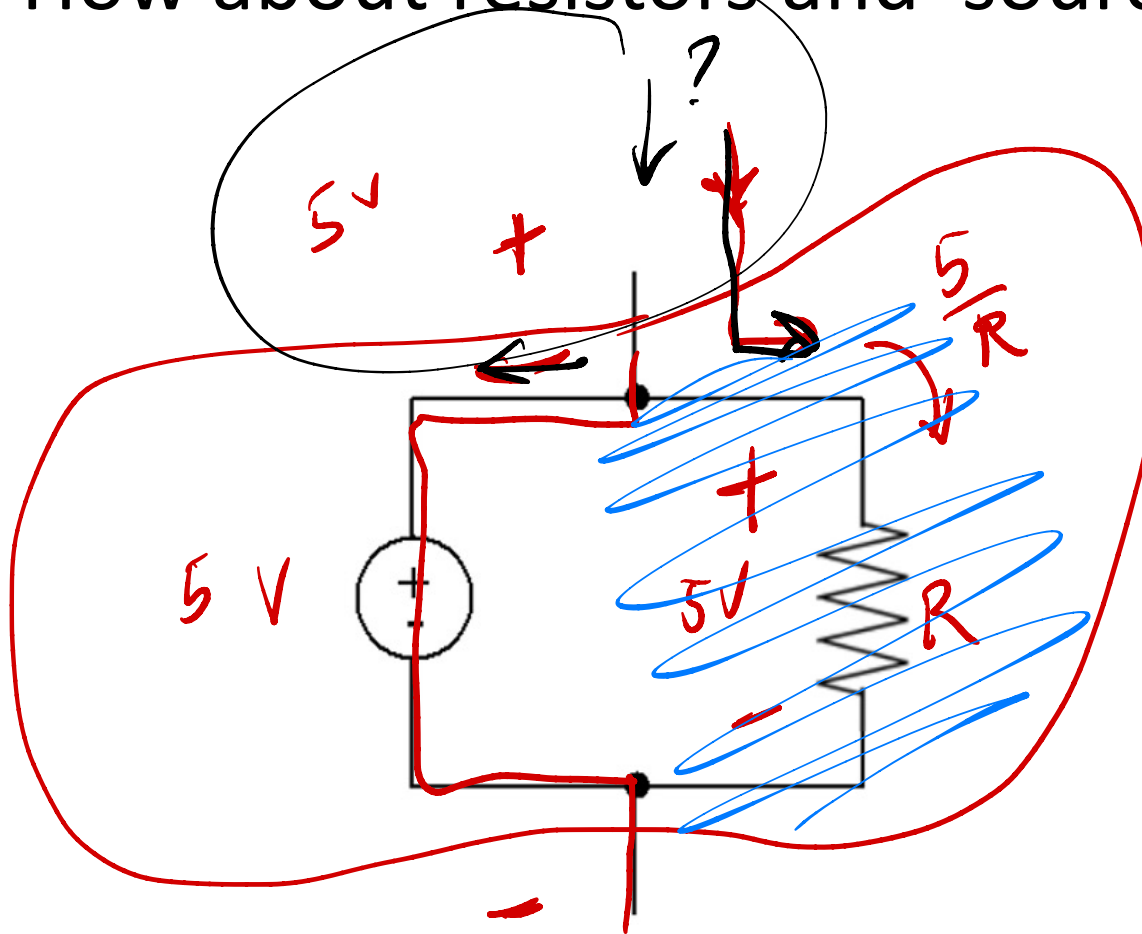

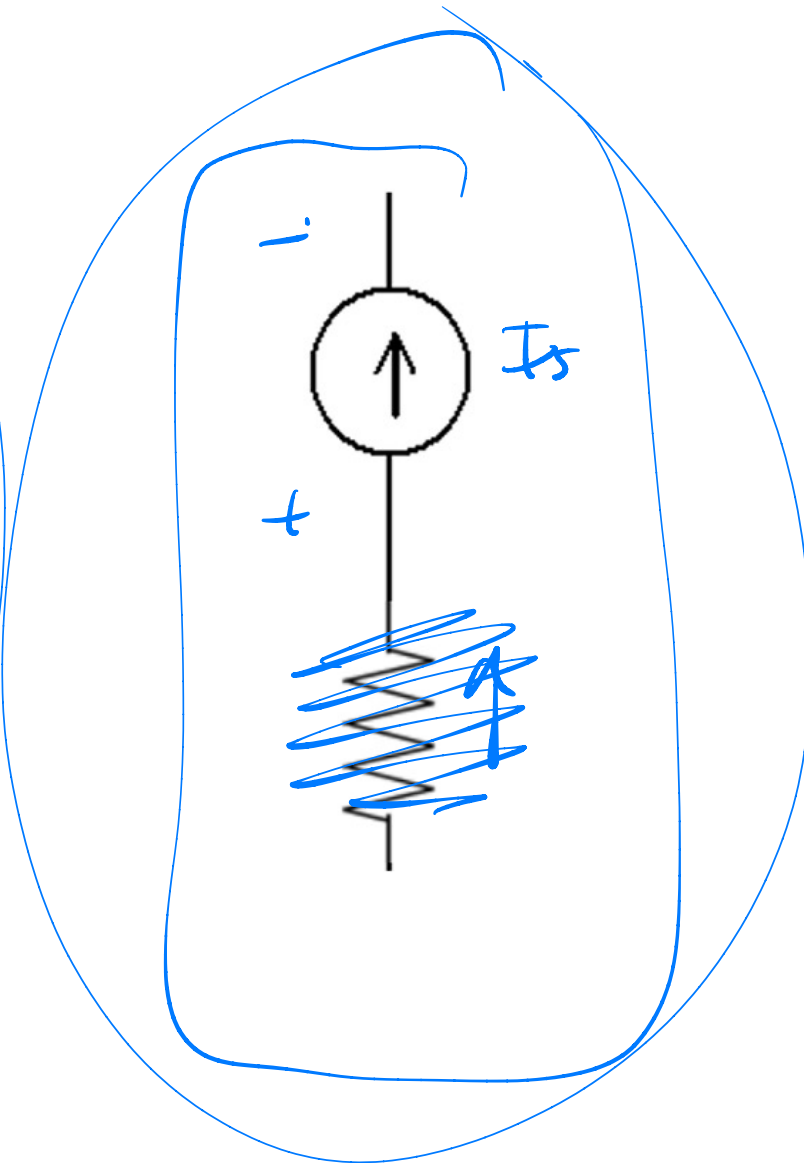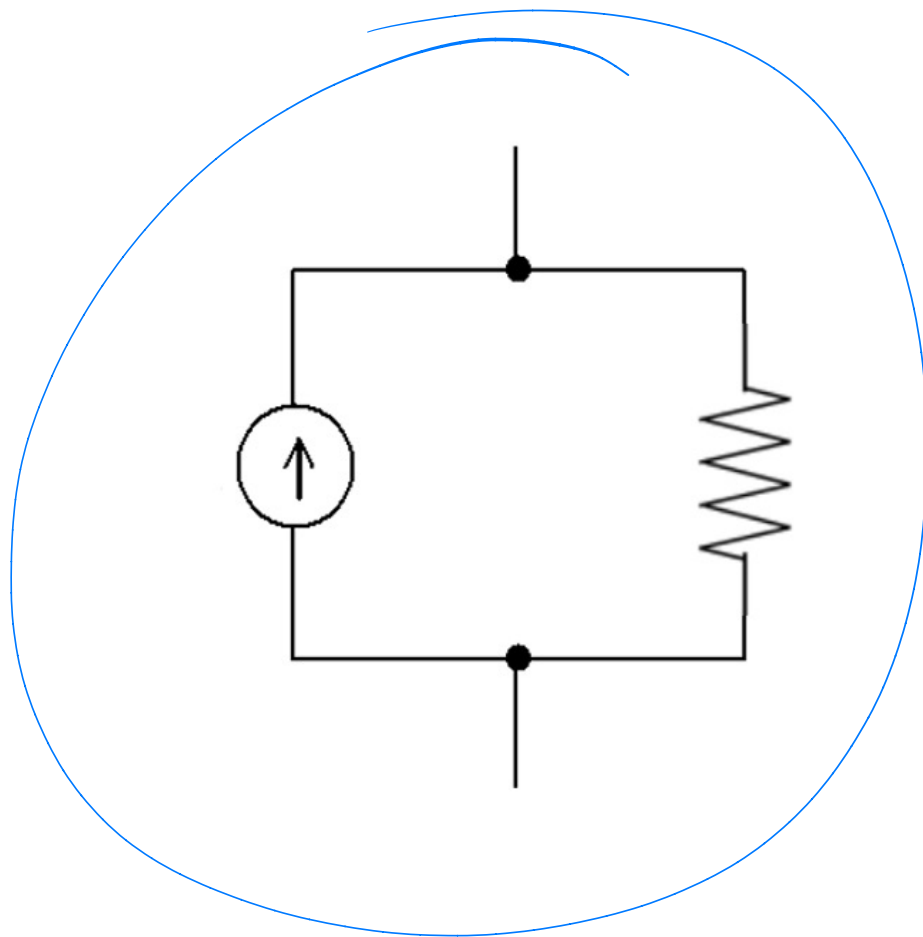
$$V_T = R \dot{I}_+ + V_S$$
$$\dot{I}_+ = \frac{V_T - V_S}{R}$$



Example: find I

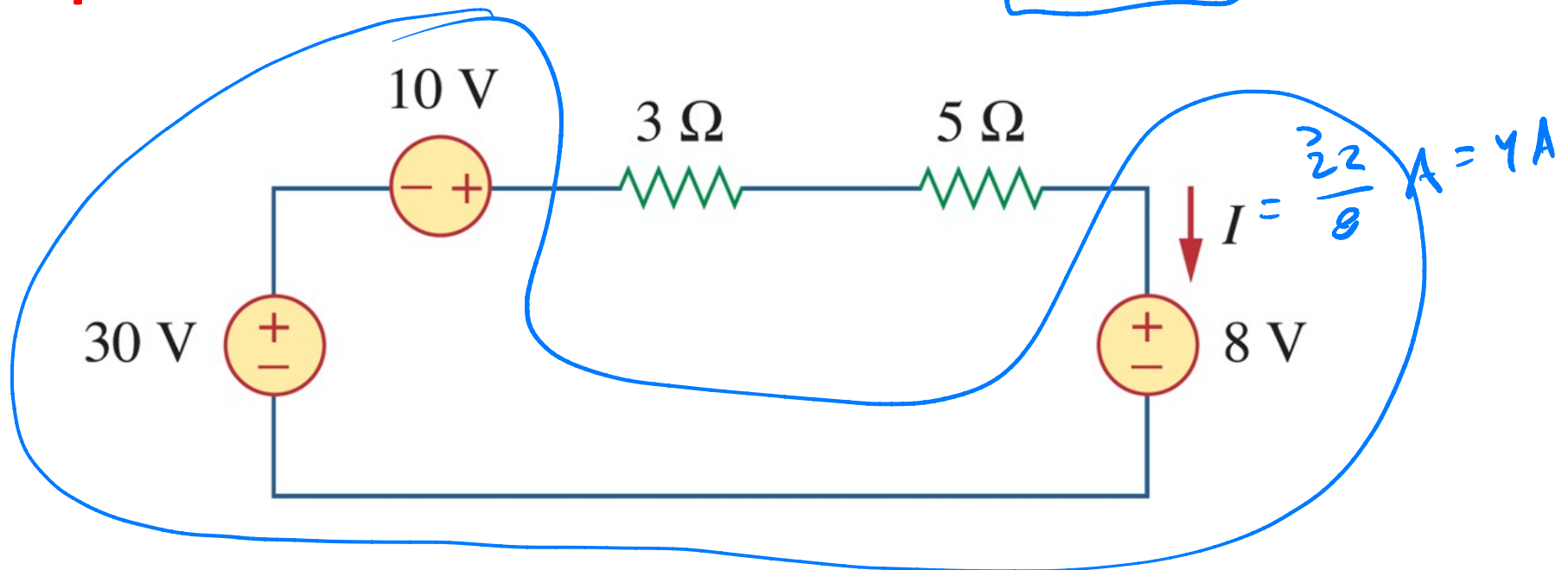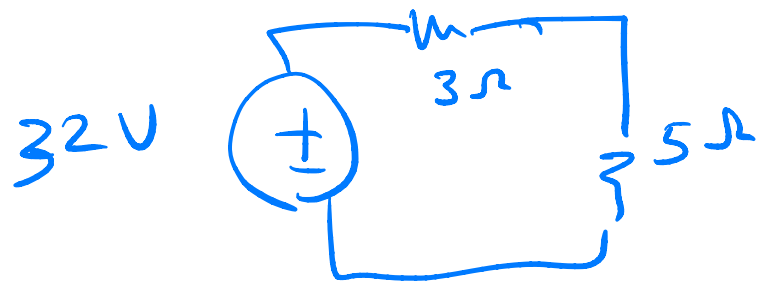

And now?

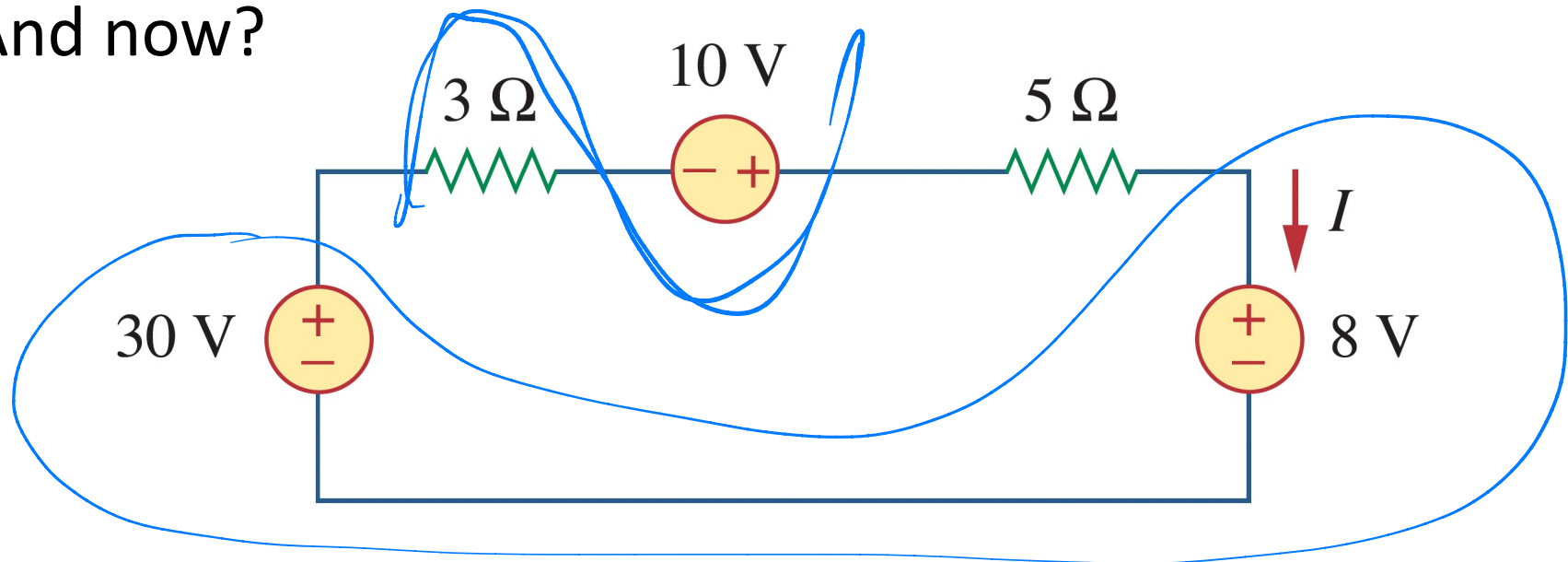

Time Varying Example

- What happens now?

