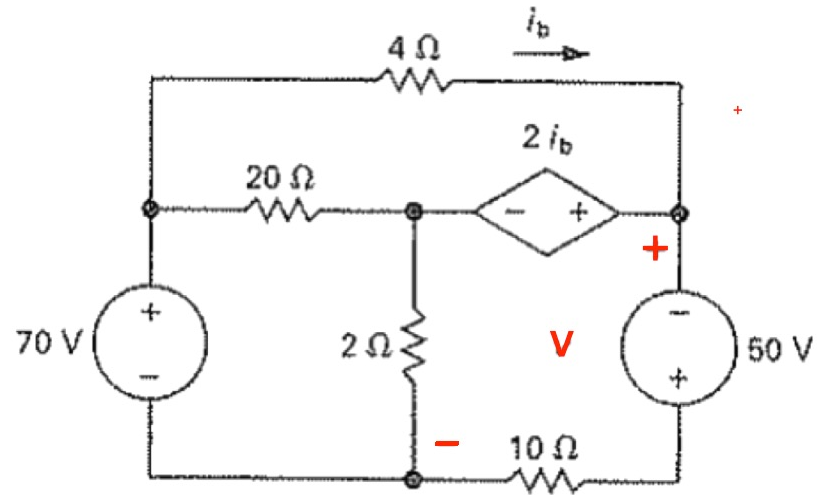


# Node – 1

basic concepts

# General Methods to Analyze Circuits


- What to do first?
  - KVL?
  - KCL?
  - Ohm's Law?




- We need a more direct approach:
  - Nodal analysis (KCL based)
  - Mesh analysis (KVL based, **end of semester**)
- Review appendix A (also online)
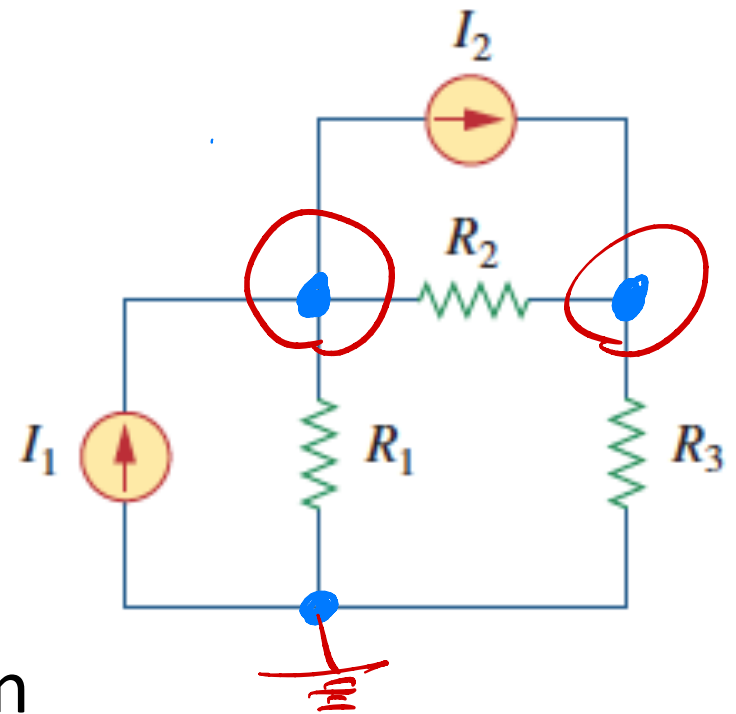
# Node Analysis

- Consider a circuit with current sources and resistors only
- Identify nodes
  - Select one as “ground”
  - Label others
  - Write KCL on these other nodes
  - Use Ohm’s Law for current in the resistive branches
  - Solve resulting equations



Example (details repeated on next slide)

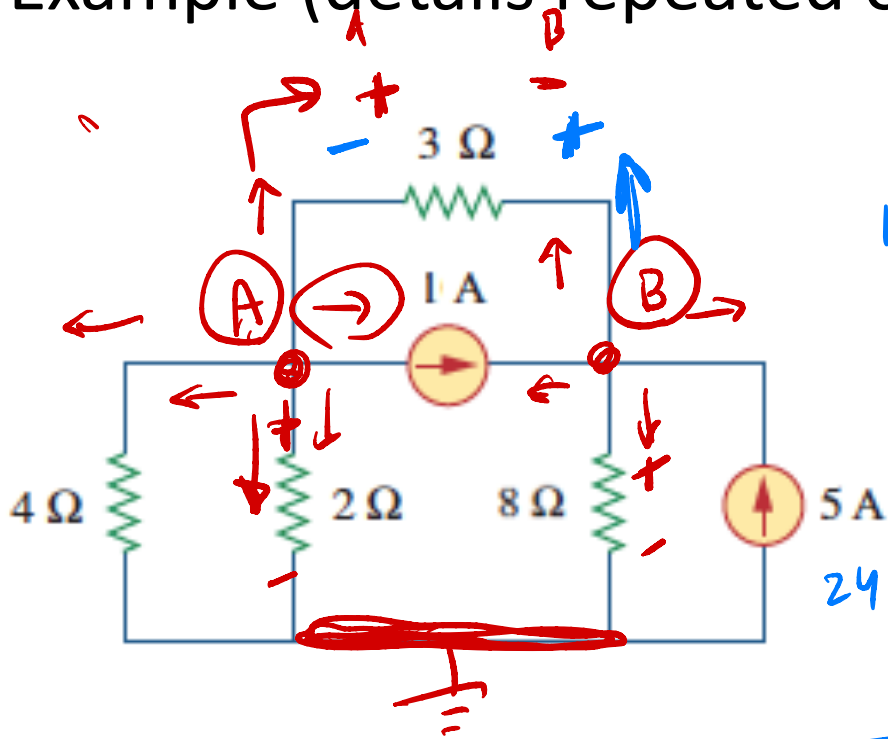

$$12 \left( A: \right. \quad 1 + \frac{A}{2} + \frac{A}{4} + \frac{A-B}{3} = 0$$


$$24 \left( B: \right. \quad -5 + \frac{B}{8} - 1 + \frac{B-A}{3} = 0$$

$$6A + 3A + 4A - 4B = -12$$

$$3B + 8B - 8A = 144$$

$$13A - 4B = -12$$

$$-8A + 11B = 144$$

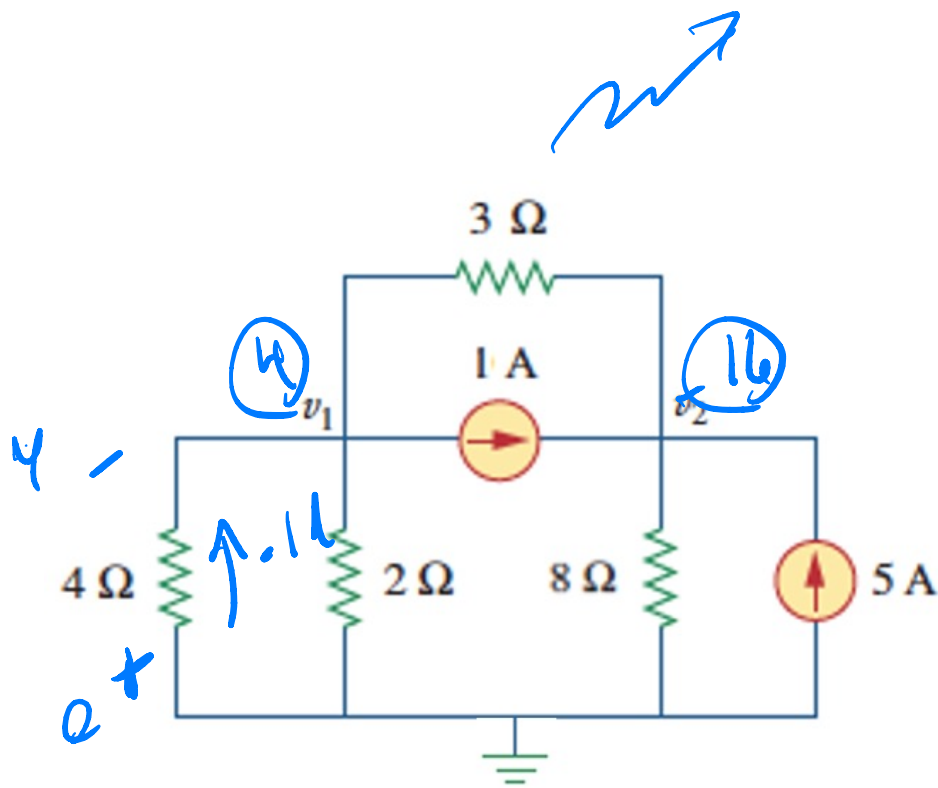

$$\frac{v_1}{2} + \frac{v_1}{4} + \frac{v_1 - v_2}{3} + 1 = 0$$

$$\frac{v_2}{8} + \frac{v_2 - v_1}{3} = 1 + 5$$

---


$$6v_1 + 3v_1 + 4v_1 - 4v_2 = -12$$

$$3v_2 + 8v_2 - 8v_1 = 144$$


---

$$13v_1 - 4v_2 = -12$$


$$-8v_1 + 11v_2 = 144$$


---

$$v_1 = \frac{\begin{vmatrix} -12 & -4 \\ 144 & 11 \end{vmatrix}}{\begin{vmatrix} 13 & -4 \\ -8 & 11 \end{vmatrix}} = \frac{-132 + 576}{143 - 32} = \frac{444}{111} = 4 \text{ volts} \quad = A$$


$$v_2 = \frac{\begin{vmatrix} 13 & -12 \\ -8 & 144 \end{vmatrix}}{\begin{vmatrix} 13 & -4 \\ -8 & 11 \end{vmatrix}} = \frac{1872 - 96}{111} = \frac{1776}{111} = 16 \text{ volts} \quad = B$$

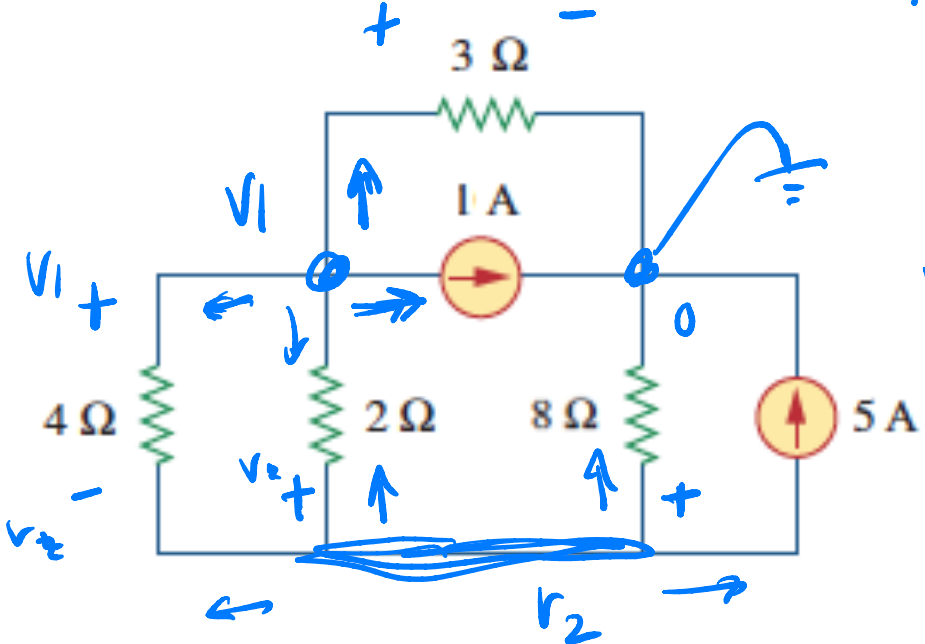Example (same circuit, change ground to top right, details on next slide)



$$V_1: 1 + \frac{V_1}{3} - \frac{V_1 - V_2}{4} + \frac{V_1 - V_2}{2} = 0$$
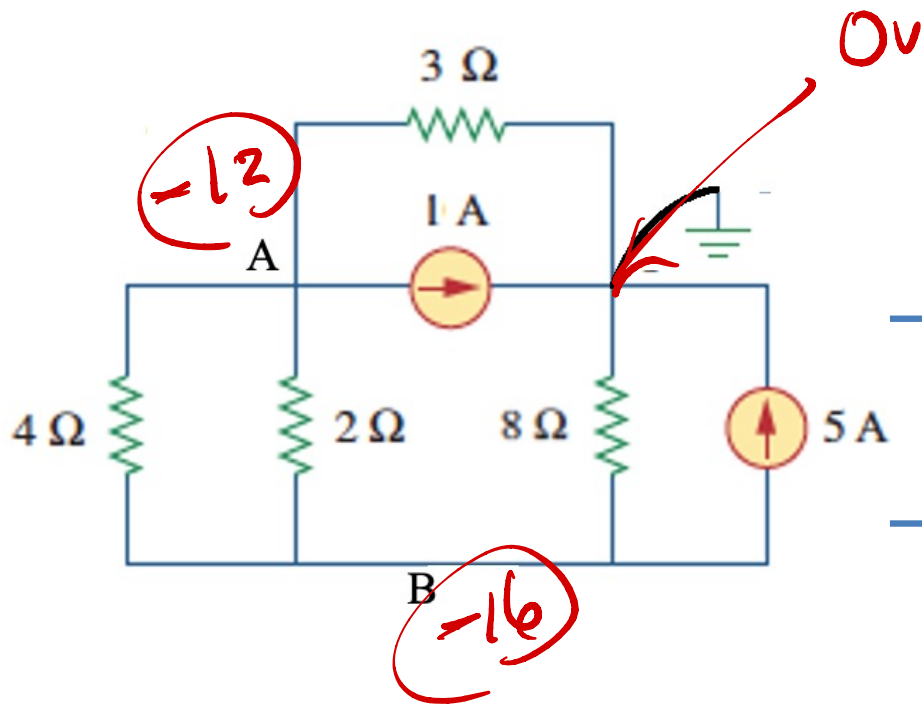
$$V_2: 5 + \frac{V_2}{8} + \frac{V_2 - V_1}{2} + \frac{V_2 - V_1}{4} = 0$$



$$\frac{A - B}{2} + \frac{A - B}{4} + \frac{A}{3} + 1 = 0$$

$$\frac{B - A}{4} + \frac{B - A}{2} + \frac{B}{8} + 5 = 0$$

---


$$6A - 6B + 3A - 3B + 4A = -12$$

$$2B - 2A + 4B - 4A + B = -40$$


---


$$13A - 9B = -12$$

$$-6A + 7B = -40$$

$$A = \frac{\begin{vmatrix} -12 & -9 \\ -40 & 7 \end{vmatrix}}{\begin{vmatrix} 13 & -9 \\ -6 & 7 \end{vmatrix}} = \frac{-84 - 360}{91 - 54} = \frac{-444}{37} = -12 \text{ volts}$$

$$B = \frac{\begin{vmatrix} 13 & -12 \\ -6 & -40 \end{vmatrix}}{\begin{vmatrix} 13 & -9 \\ -6 & 7 \end{vmatrix}} = \frac{-520 - 72}{35} = \frac{-592}{37} = -16 \text{ volts}$$

Example:

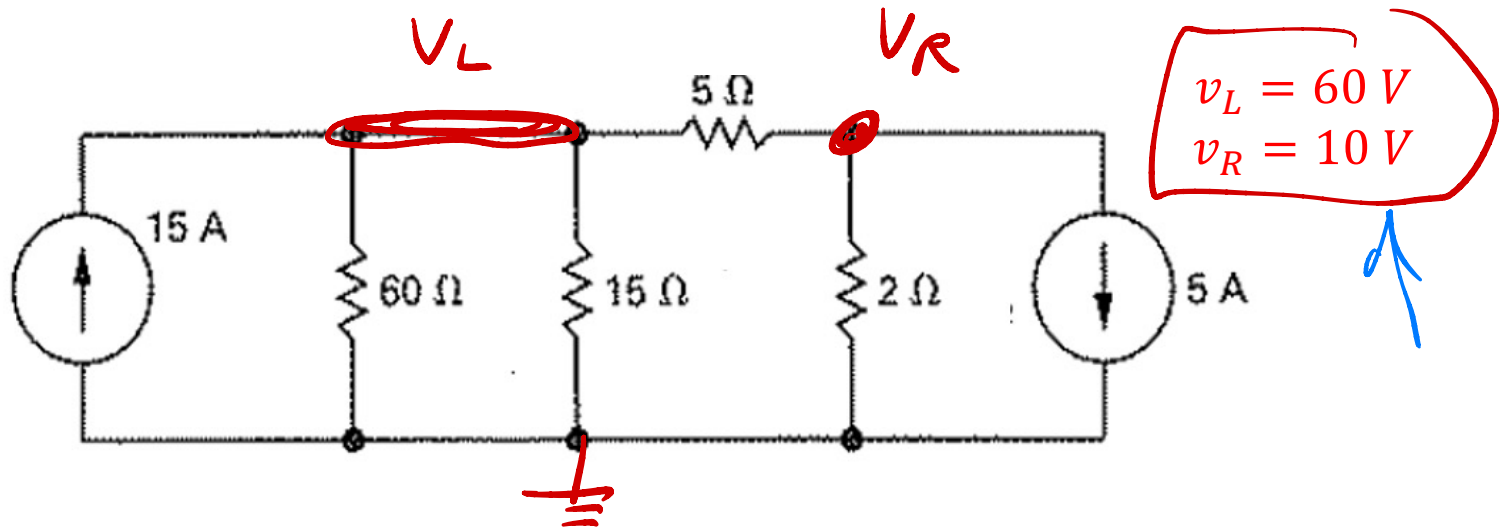

write KCL

$$v_L: 60 \left( -15 + \frac{v_L}{60} + \frac{v_L}{15} + \frac{v_L - v_R}{5} = 0 \right)$$

$$v_R: 10 \left( 5 + \frac{v_R}{2} + \frac{v_R - v_L}{5} = 0 \right)$$

$$16 v_L - 12 v_R = 900$$

$$-2 v_L + 7 v_R = -50$$


$$\begin{bmatrix} 16 & -12 \\ -2 & 7 \end{bmatrix} \begin{bmatrix} v_L \\ v_R \end{bmatrix} = \begin{bmatrix} 900 \\ -50 \end{bmatrix}$$

$$\begin{bmatrix} v_L \\ v_R \end{bmatrix} = \frac{1}{88} \begin{bmatrix} 7 & 12 \\ 2 & 16 \end{bmatrix} \begin{bmatrix} 900 \\ -50 \end{bmatrix}$$




# Extension #1 – a V-only branch

- Consider:

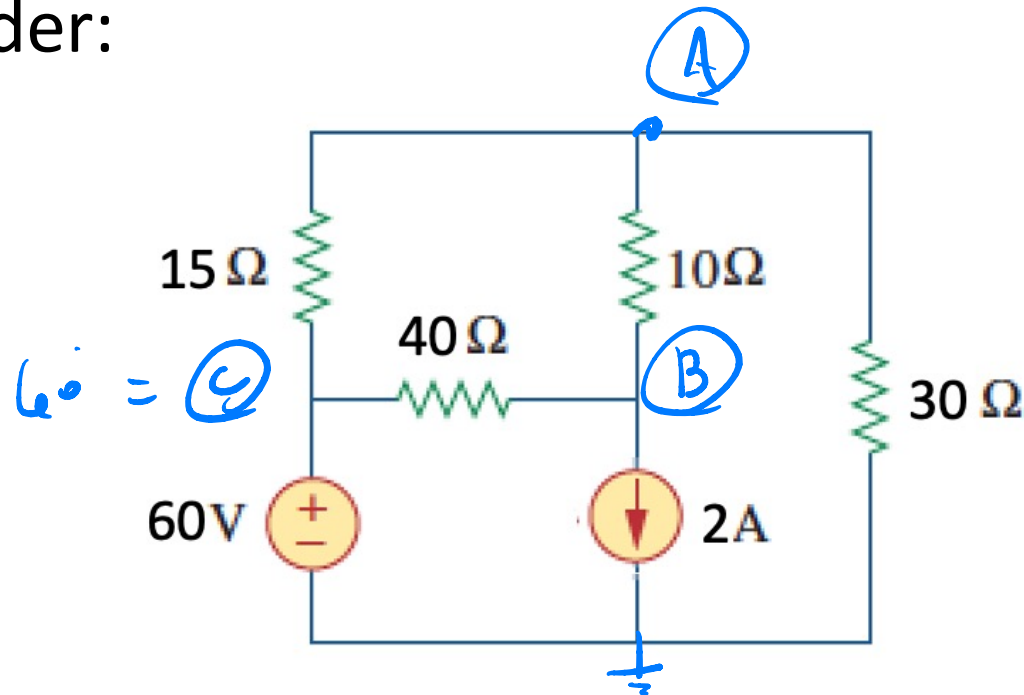

- **IF** connected to ground, it's just one less node voltage to worry about


Example (details on next slide)

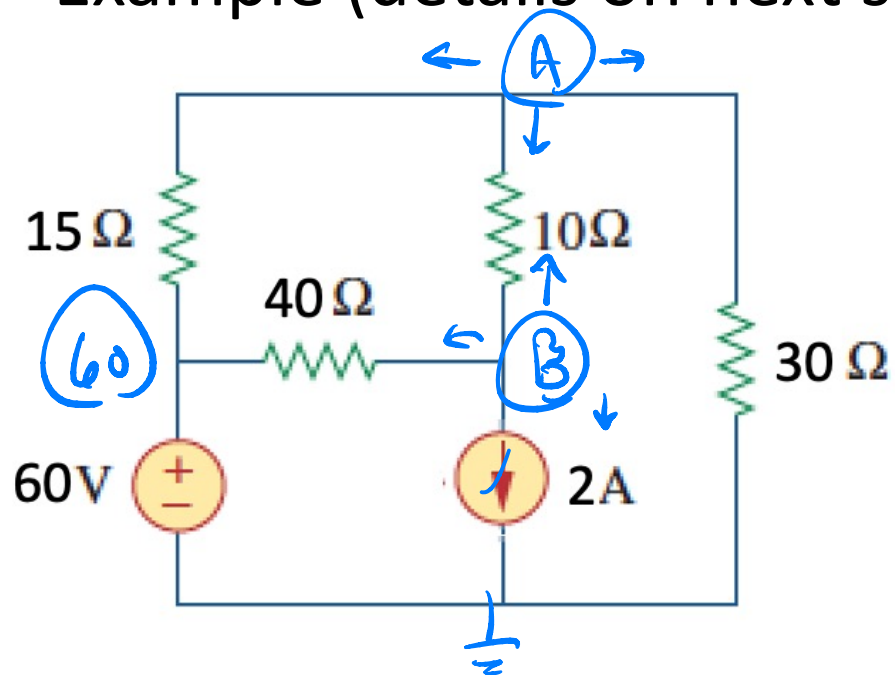

$$A: \frac{A-60}{15} + \frac{A-B}{10} + \frac{A}{30} = 0$$

$$B: 2 + \frac{B-60}{40} + \frac{B-A}{10} = 0$$

---

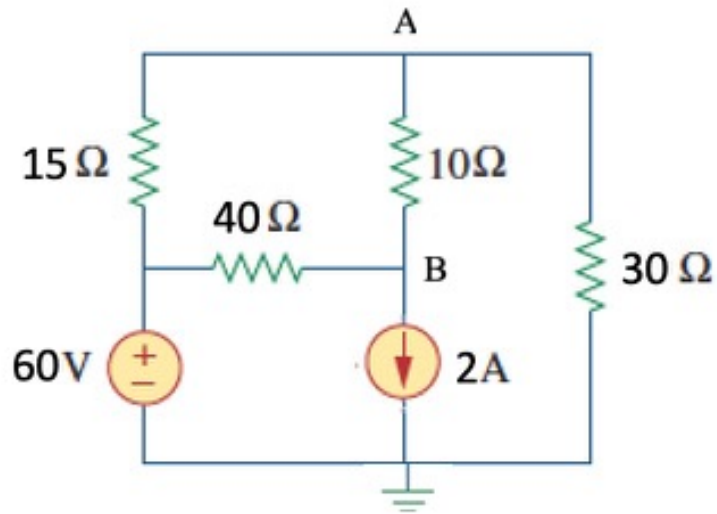

$$\frac{A - 60}{15} + \frac{A - B}{10} + \frac{A}{30} = 0$$

$$\frac{B - 60}{40} + \frac{B - A}{10} + 2 = 0$$

$$6A - 3B = 120$$

$$-4A + 5B = -20$$

$$A = 30 \text{ volts}$$


$$B = 20 \text{ volts}$$

# Example from Delta-Wye transformations

$$v_L = 70.8 \text{ V}$$

$$v_R = 74.8 \text{ V}$$

$$i = 12.5 \text{ A}$$

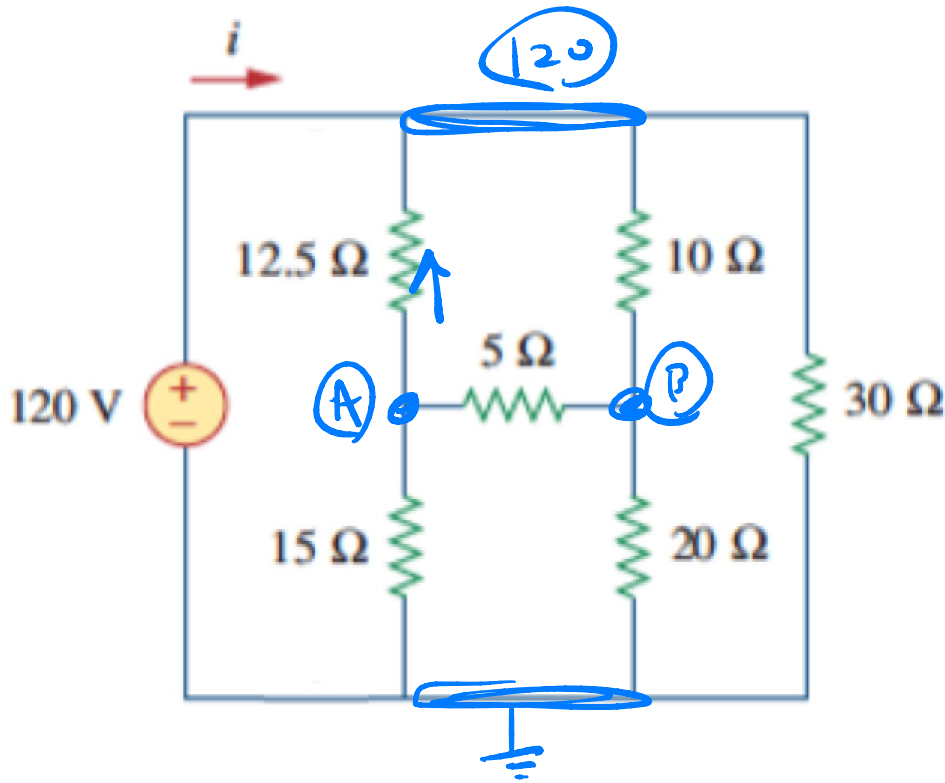


A:


$$\frac{A - 120}{12.5} + \frac{A}{15} + \frac{A - B}{5} = 0$$

B:

$$\frac{B}{20} + \frac{B - 120}{10} + \frac{B - A}{5} = 0$$

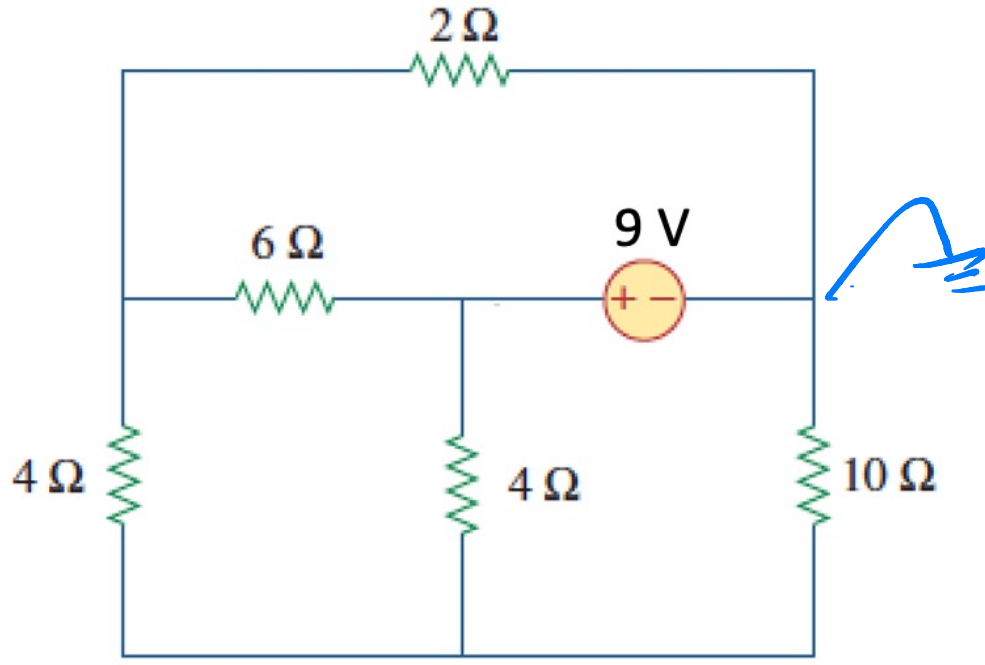**Example:** recall that we can place ground as needed; put it on the right and solve for left and bottom




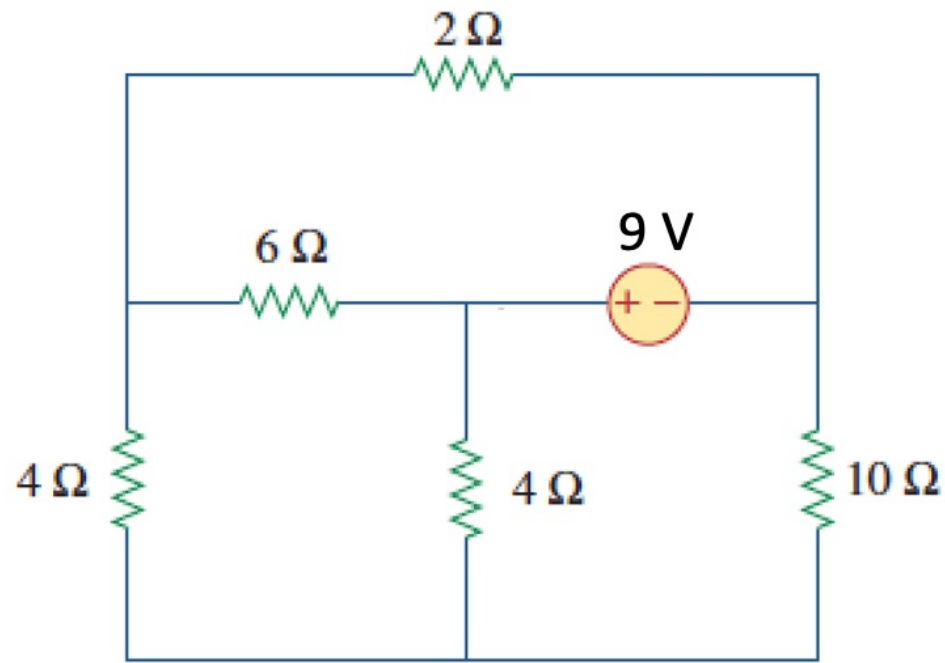

$$v_L = 3 \text{ V}$$
$$v_B = 5 \text{ V}$$


120 V, 96 V

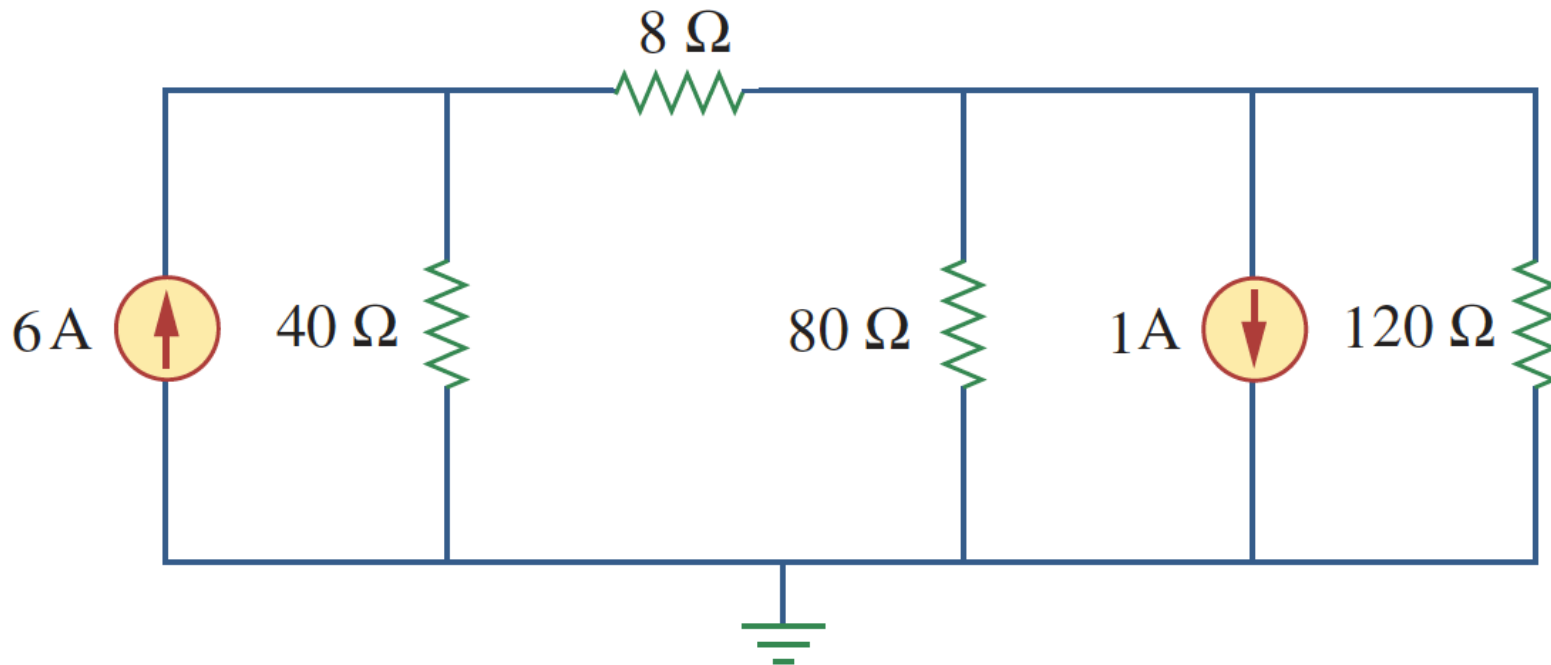**Practice problem:** find the nodes voltages to the left and right of the 8  $\Omega$  resistor



50 V, 36 V

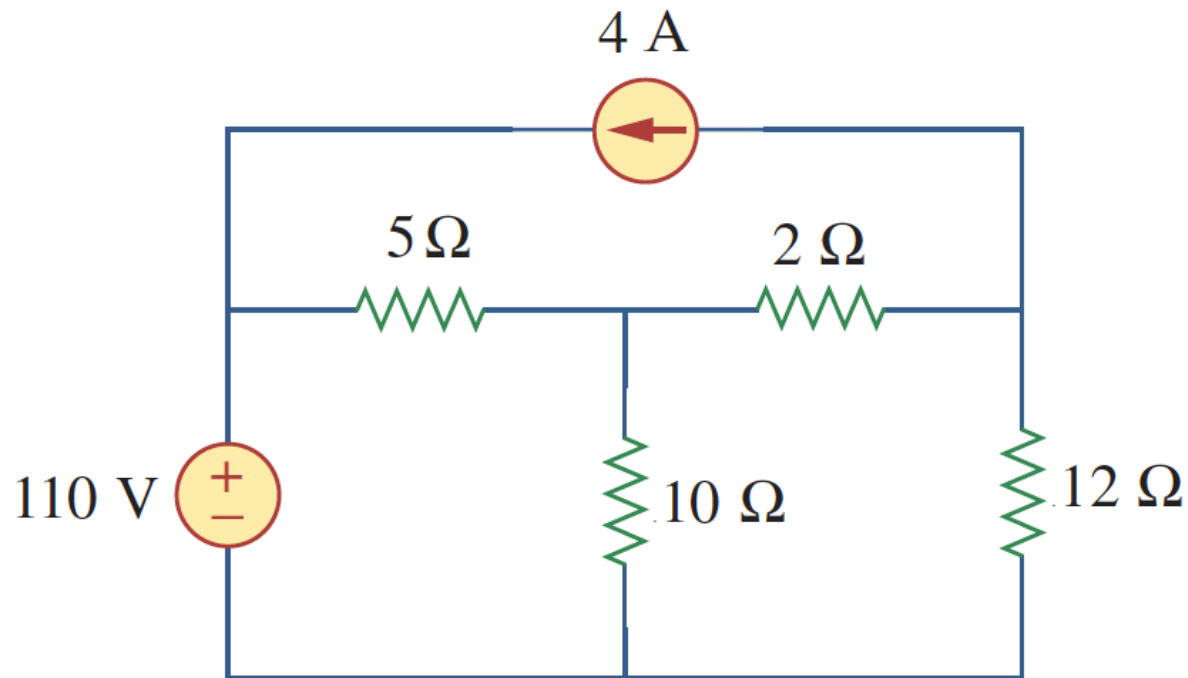**Practice problem:** assuming ground on the bottom, find the nodes voltages to the left and right of the 2  $\Omega$  resistor





70 V, 60 V

**Practice problem:** find the nodes voltages to the left and right of the  $10\text{ k}\Omega$  resistor, ground at the bottom

