


Node – 2

more complex branches

Extension #2 – V + R branches


$$v_6 = A - 30$$

- Consider:

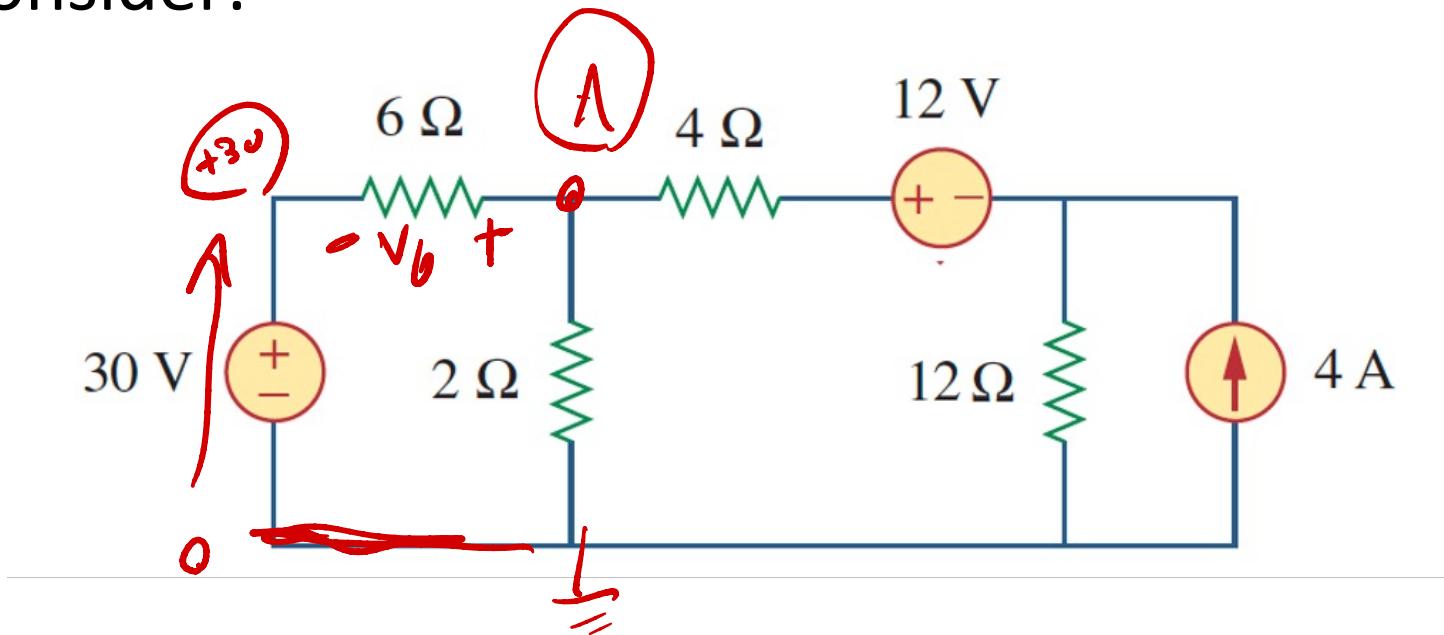


- Solution: Modify the Ohm's Law expression(s) for the individual branch current(s)

Example (solved on next slide)

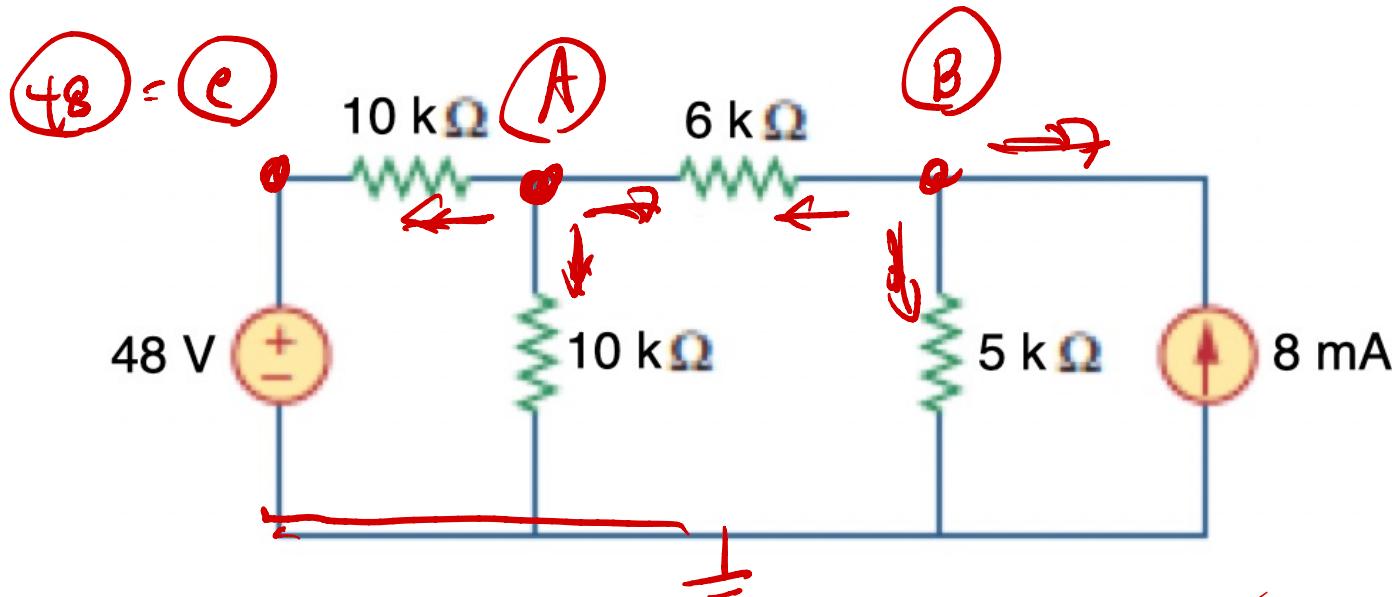

$$B: -\frac{8}{1000} + \frac{B}{5000} + \frac{B-A}{6000} = 0 \quad \checkmark$$
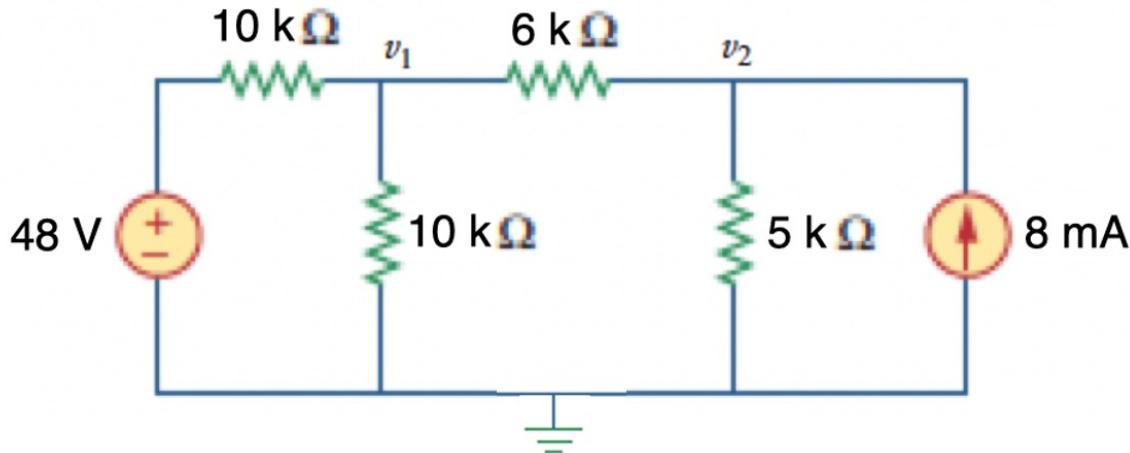
$$A: \frac{A-B}{6000} + \frac{A}{10,000} + \frac{A-48}{10,000} = 0$$



$$\frac{v_1}{10k} + \frac{v_1 - 48}{10k} + \frac{v_1 - v_2}{6k} = 0$$


$$\frac{v_2}{5k} + \frac{v_2 - v_1}{6k} - .008 = 0$$

$$3v_1 + 3v_1 + 5v_1 - 5v_2 = 144$$

$$6v_2 + 5v_2 - 5v_1 = 240$$


$$\begin{aligned} 11v_1 - 5v_2 &= 288 \\ -5v_1 + 11v_2 &= 240 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 29 V \\ v_2 &= 35 V \end{aligned}$$

Example

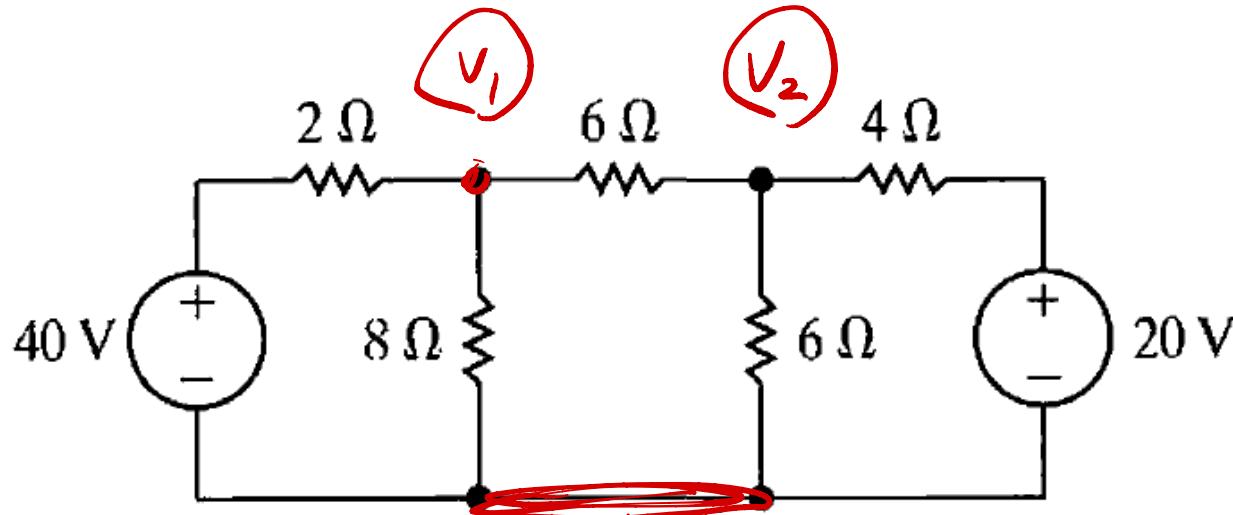


node v_1 : $\frac{v_1}{8} + \frac{v_1 - v_2}{6} + \frac{v_1 - 40}{2} = 0$

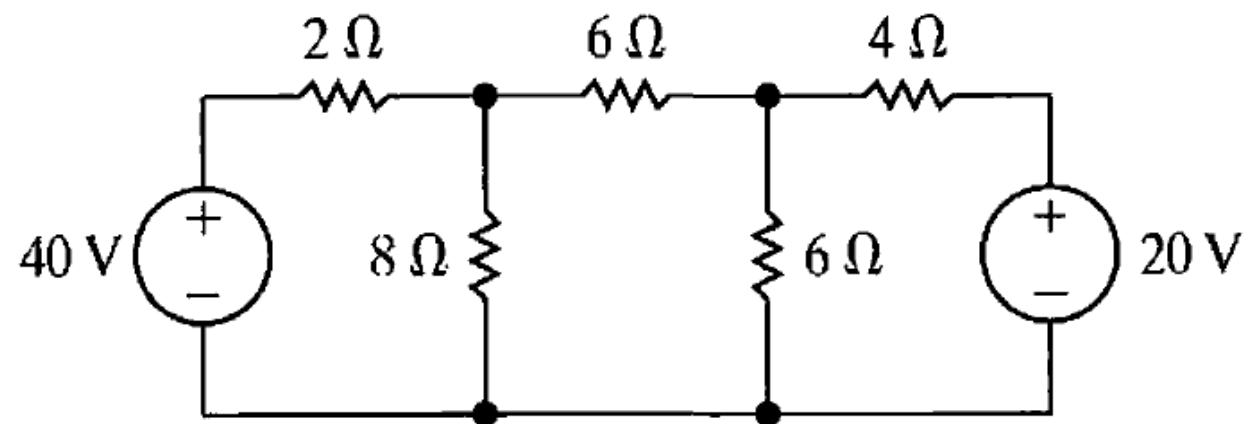node v_2 : $\frac{v_2}{6} + \frac{v_2 - v_1}{6} + \frac{v_2 - 20}{4} = 0$




28 V, 16 V
↗

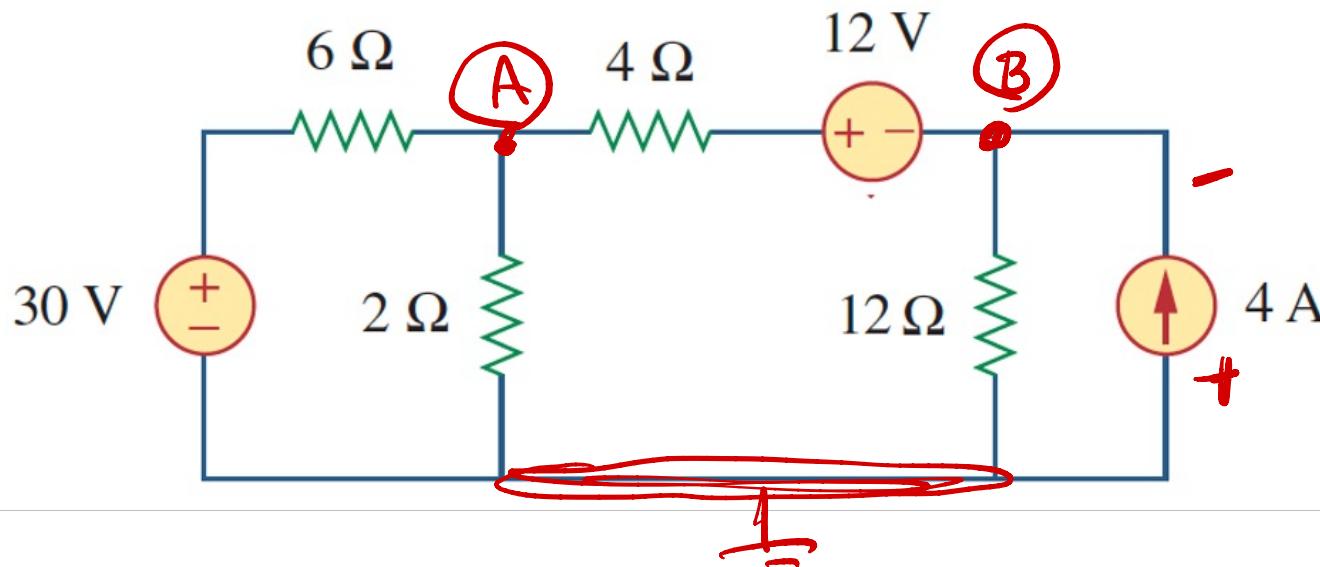Example: find the power of the current source



$$\text{node A: } \frac{A}{2} + \frac{A-30}{6} + \frac{A-(B+12)}{4} = 0$$
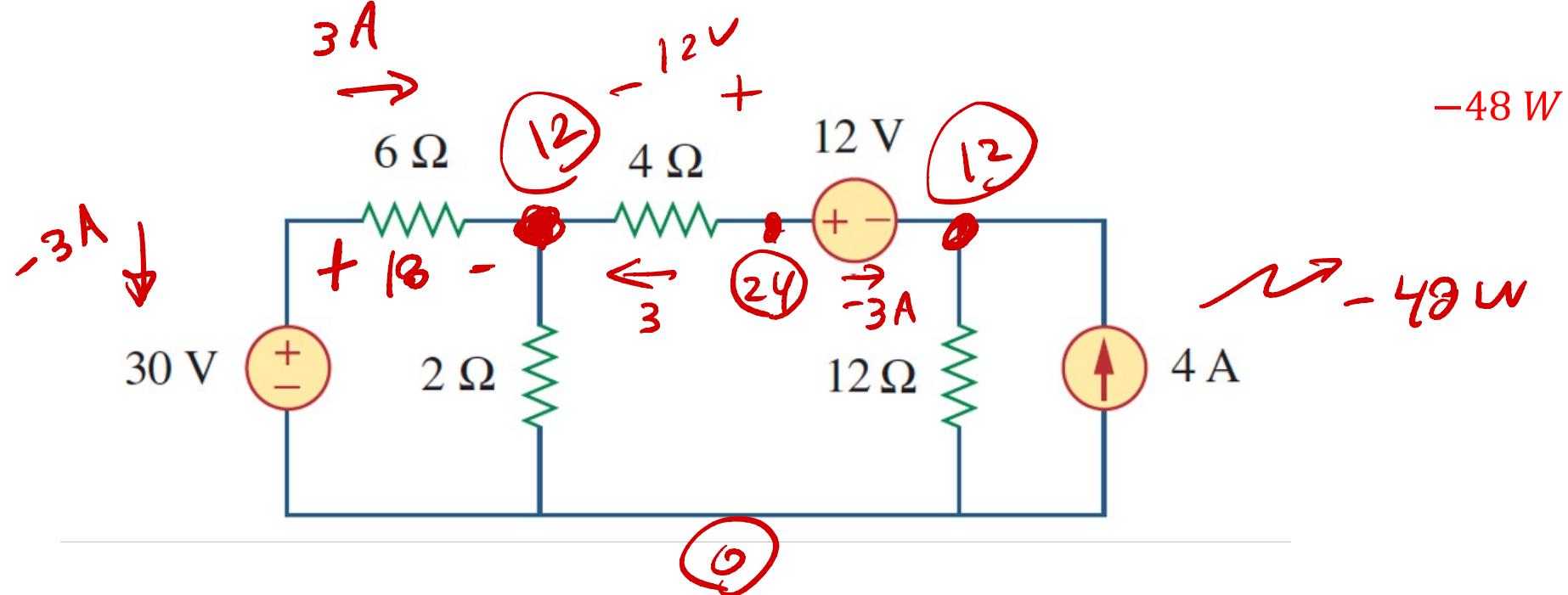
$$\text{node B: } -4 + \frac{B}{12} + \frac{B+12-A}{4} = 0$$



$$P_{30} = ? \quad (-3)(30) = -90 \text{ W}$$


$$P_{12} = (-3)(12) = -36 \text{ W}$$

Example: find v

$$\frac{A-B}{8} =$$

$$\frac{A-B}{4}$$

$$v_i = B + \frac{A-B}{4}$$

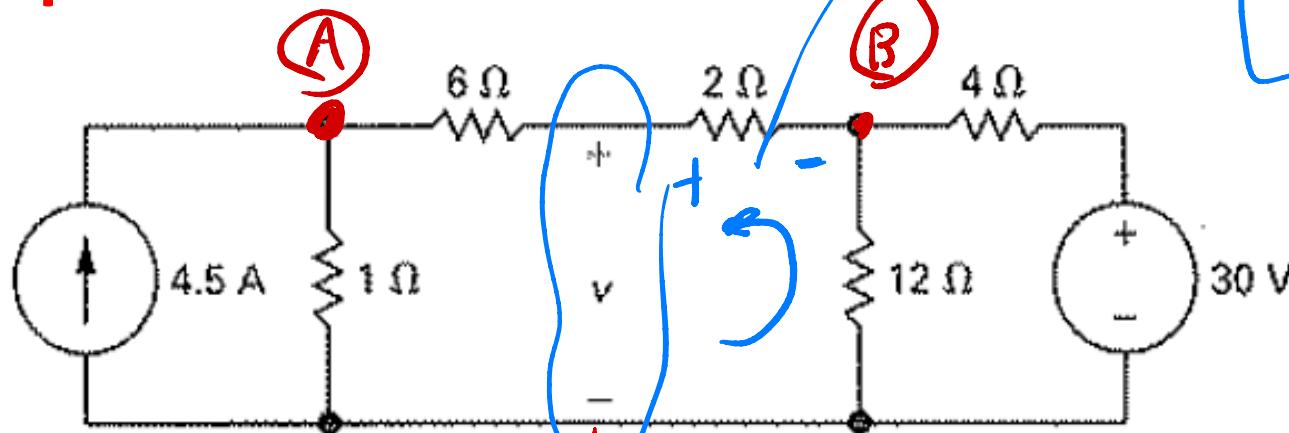

node A: $\frac{8}{4.5 + \frac{1}{1} + \frac{A-B}{8}} = 0$


node B: $\frac{B-30}{4} + \frac{B}{12} + \frac{B-A}{8} = 0$

$$9A - 8B = 36$$

$$-3A + 11B = 180$$

$$A = \begin{vmatrix} 36 & -8 \\ 180 & 11 \end{vmatrix} = \frac{396 + 1440}{99 - 24} = 20$$


$$A = \quad B =$$

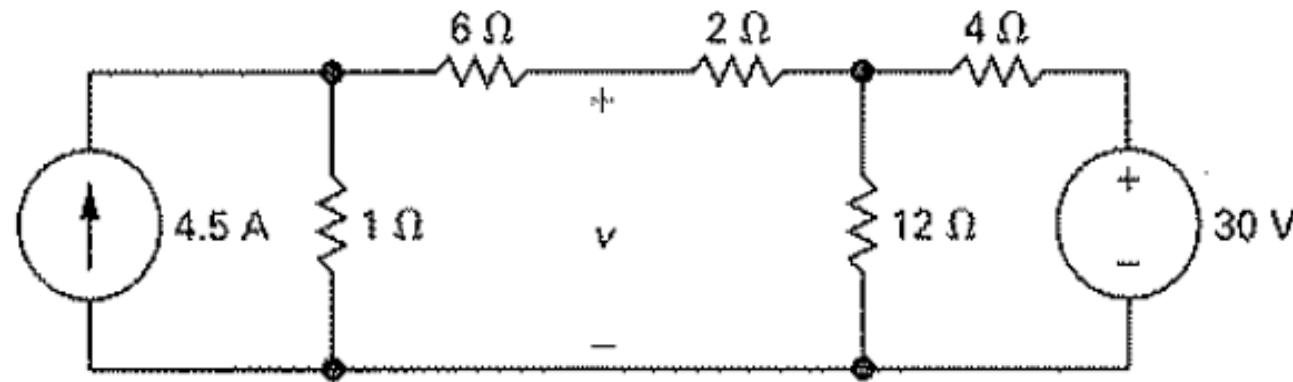

15 V


40 V

Practice problem: find V_o

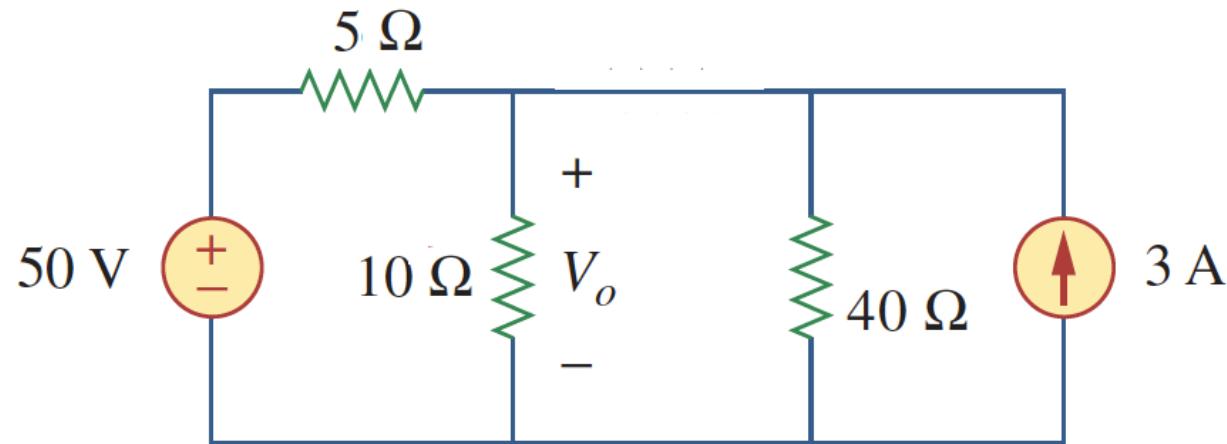

$$v_T = 40 \text{ V}, v_M = 30 \text{ V}$$

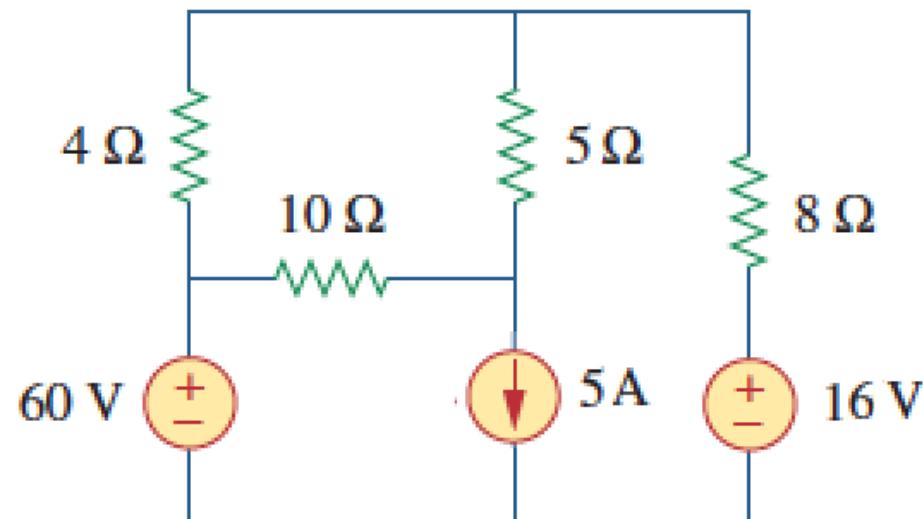Practice problem: find the node voltages to the top and bottom of the 5Ω resistor relative to the bottom



-46 A

Practice problem: find i_o

