


Node – 4

dependent sources

Extension #3 – dependent sources

- Consider:


$$v_o = A \cdot \frac{4}{10}$$

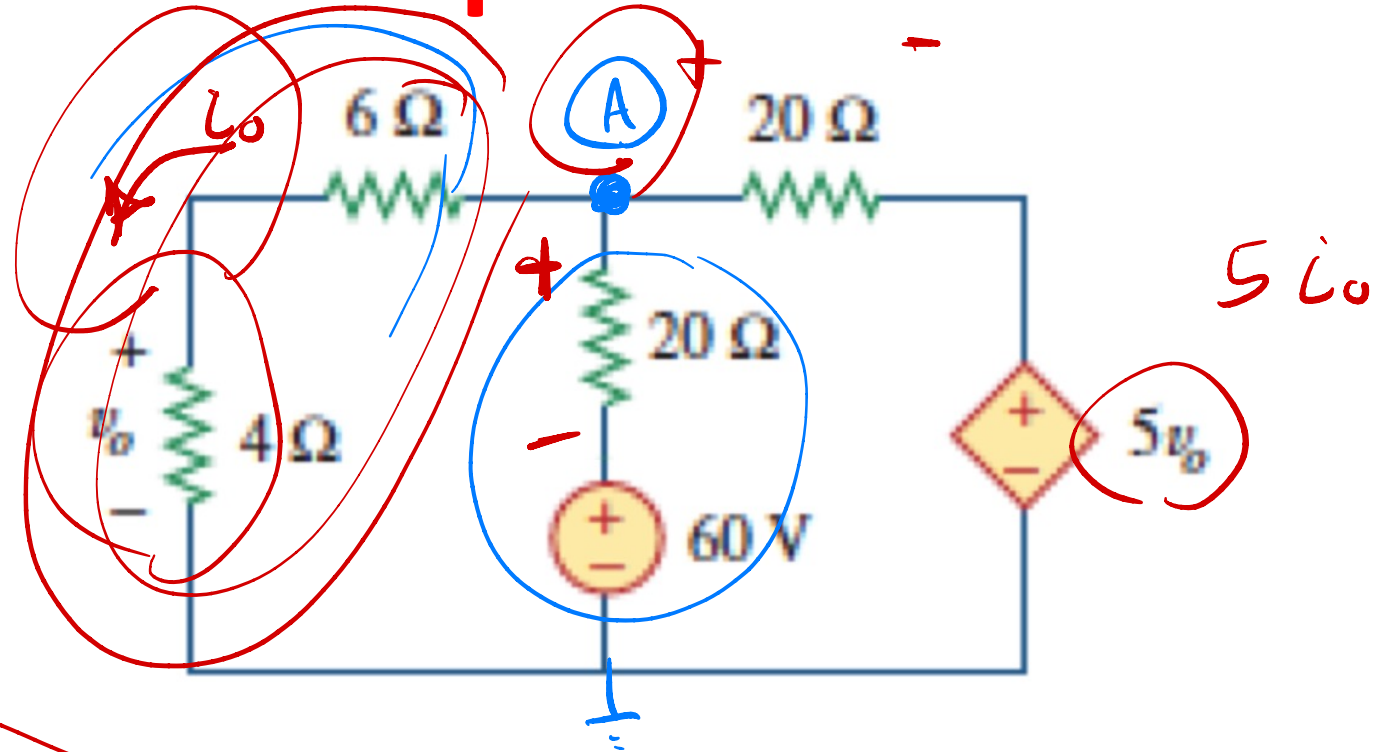


- Write node equations as usual,
- Add an equation “defining” the controlling variable in terms of the node voltages

$$\frac{A}{6+4} + \frac{A-60}{20} + \frac{A-5v_o}{20} = 0$$

Example (solved on next slide)

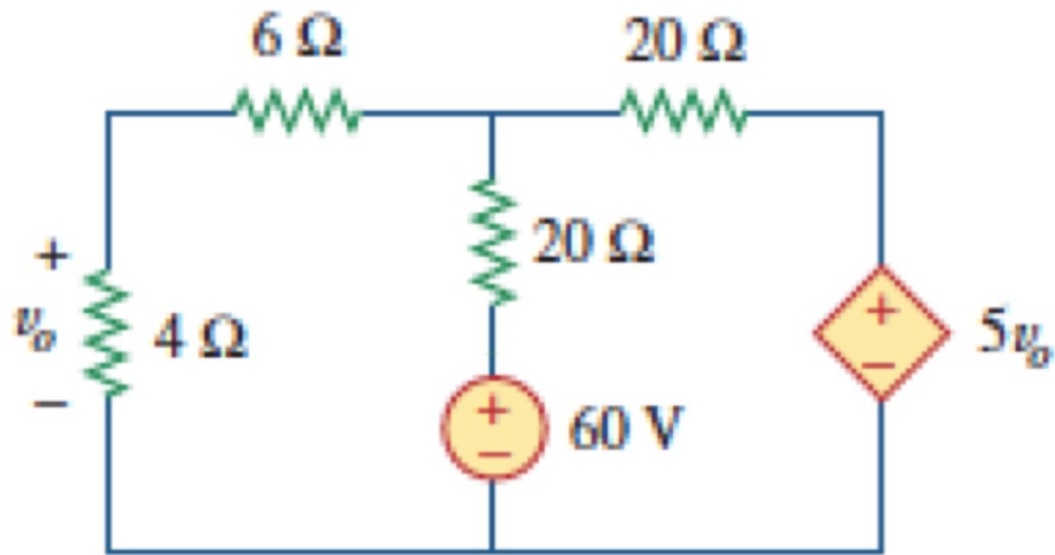

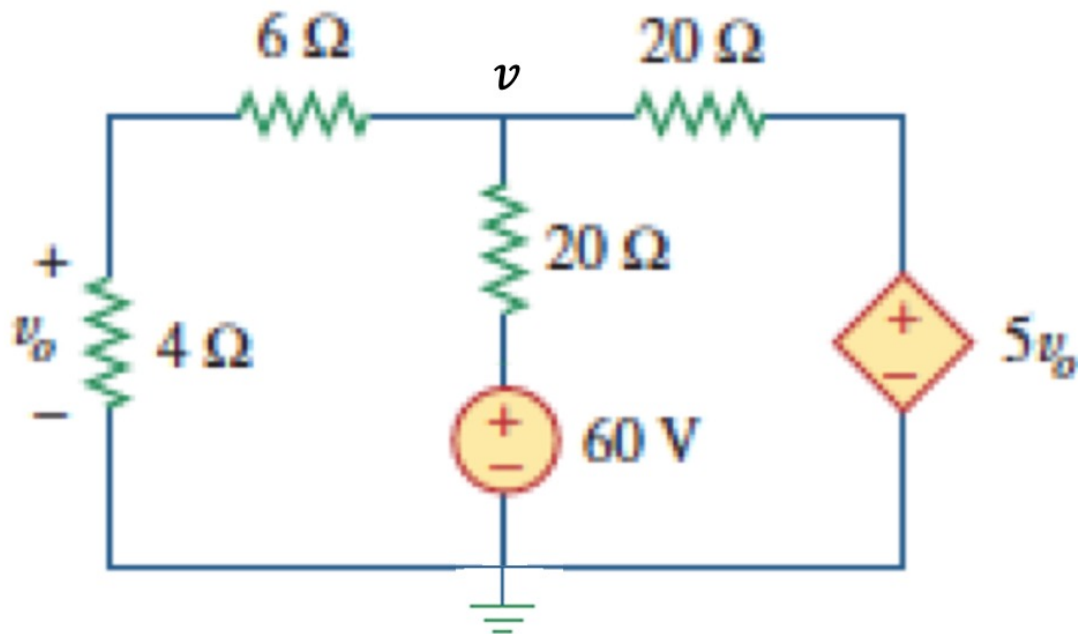

Node equation:

$$\frac{v}{10} + \frac{v - 60}{20} + \frac{v - 5v_o}{20} = 0$$

Relate v_o to the node:


$$v_o = \frac{4}{10}v$$

$$4v - 5v_o = 60$$

$$4v - 5 \frac{4}{10}v = 60$$

$$v = 30 \text{ volts}$$

Example:

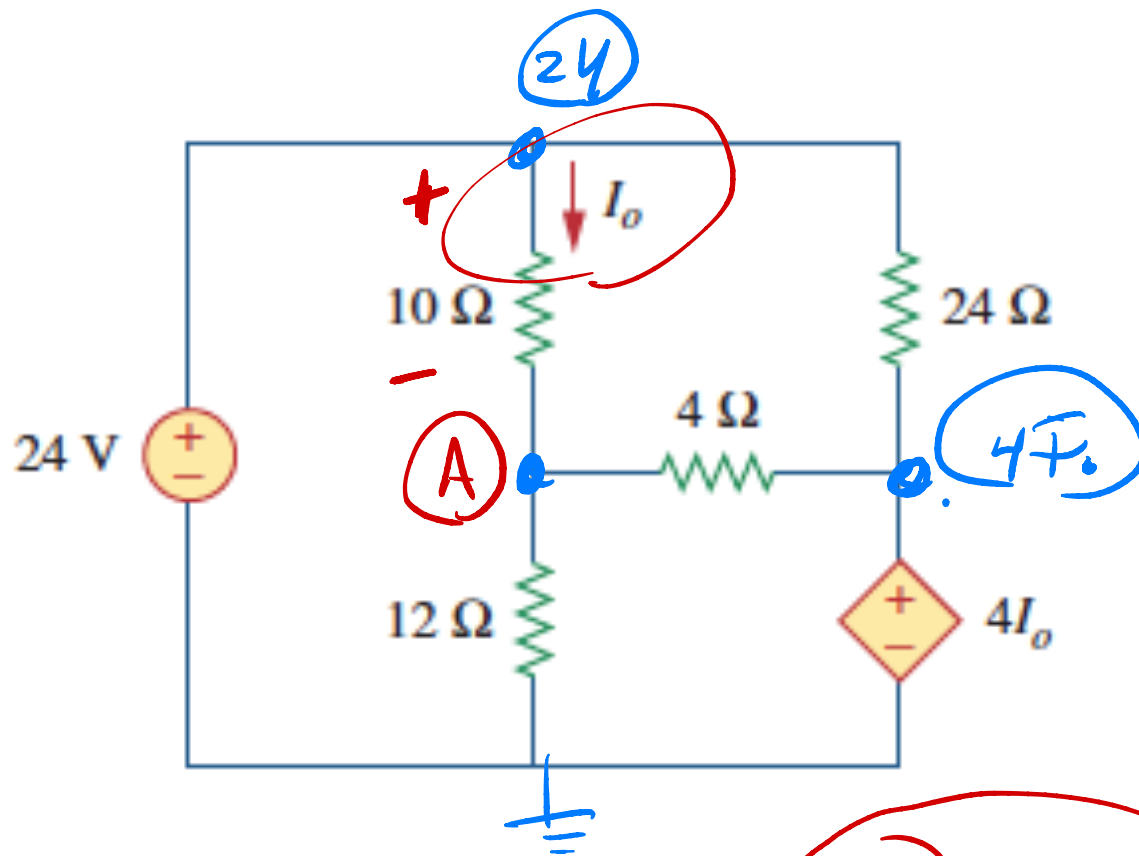


KCL at A:

$$\frac{A}{12} + \frac{A - 24}{10} + \frac{A - 4I_o}{4} = 0$$


$$I_o = \frac{24 - A}{10}$$

$$4I_o = \frac{96 - 4A}{10}$$

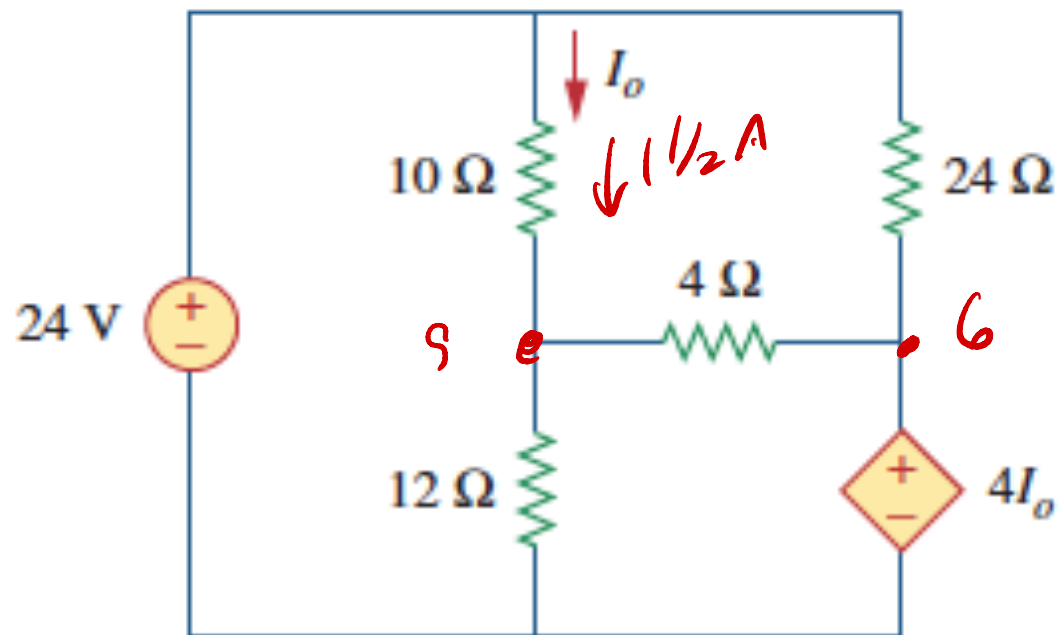

$$\begin{aligned} v_L &= 9\text{ V}, \\ i_0 &= 1.5\text{ A} \\ v_R &= 6\text{ V} \end{aligned}$$

Example:

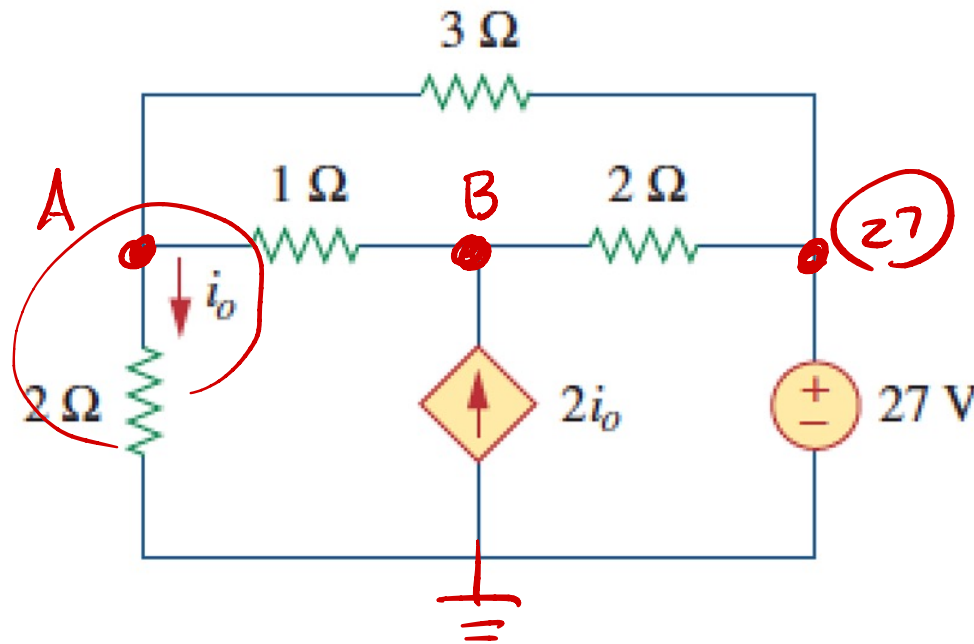

$$i_o = \frac{A}{2}$$

node A :

$$\frac{A}{2} + \frac{A-B}{1} + \frac{A-27}{3} = 0 \quad \text{--- (1)}$$

" B :


$$\frac{B-A}{1} + \frac{B-27}{2} - 2i_o = 0 \quad \text{--- (2)}$$

A

$$3A + 6A - 6B + 2A = 54$$

$$2B - 2A + B - 2A = 27$$
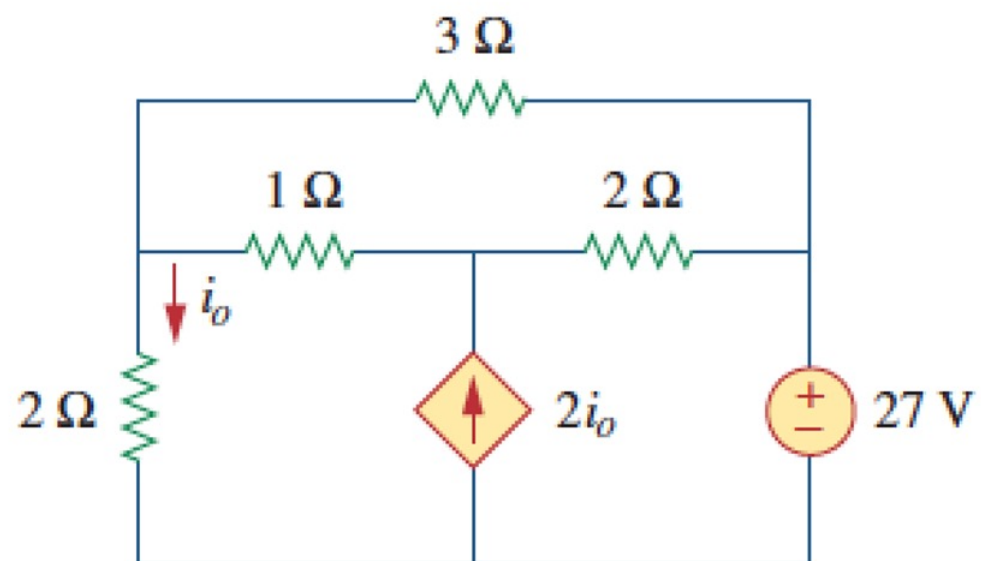
$$\begin{aligned} 11A - 6B &= 54 \\ -4A + 3B &= 27 \end{aligned}$$




$$v_L = 36\text{ V}$$

$$v_R = 57\text{ V}$$

$$V_o = 10 \text{ V}$$

Practice problem: find V_o

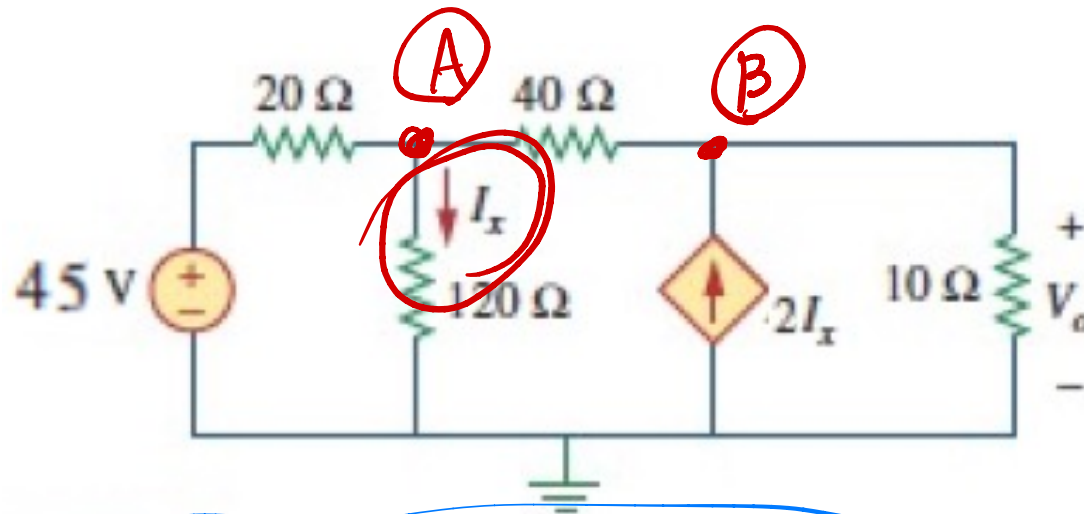

node A :

$$\frac{A - 45}{20} + \frac{A}{120} + \frac{A - B}{40} = 0$$

node B :

$$\frac{B - A}{40} + \frac{B}{10} - \cancel{2I_x} = 0$$

$-\frac{A}{60}$

$$I_x = \frac{A}{120}$$

$$2I_x = \frac{A}{60}$$

$$6A - 270$$

$$+ A + 3A - 3B = 0$$

$$10A - 3B = 270$$


$$3B - 3A + 12B$$

$$-2A = 0$$

$$-3A + 15B = 0$$

$$P = -36 \text{ W}$$

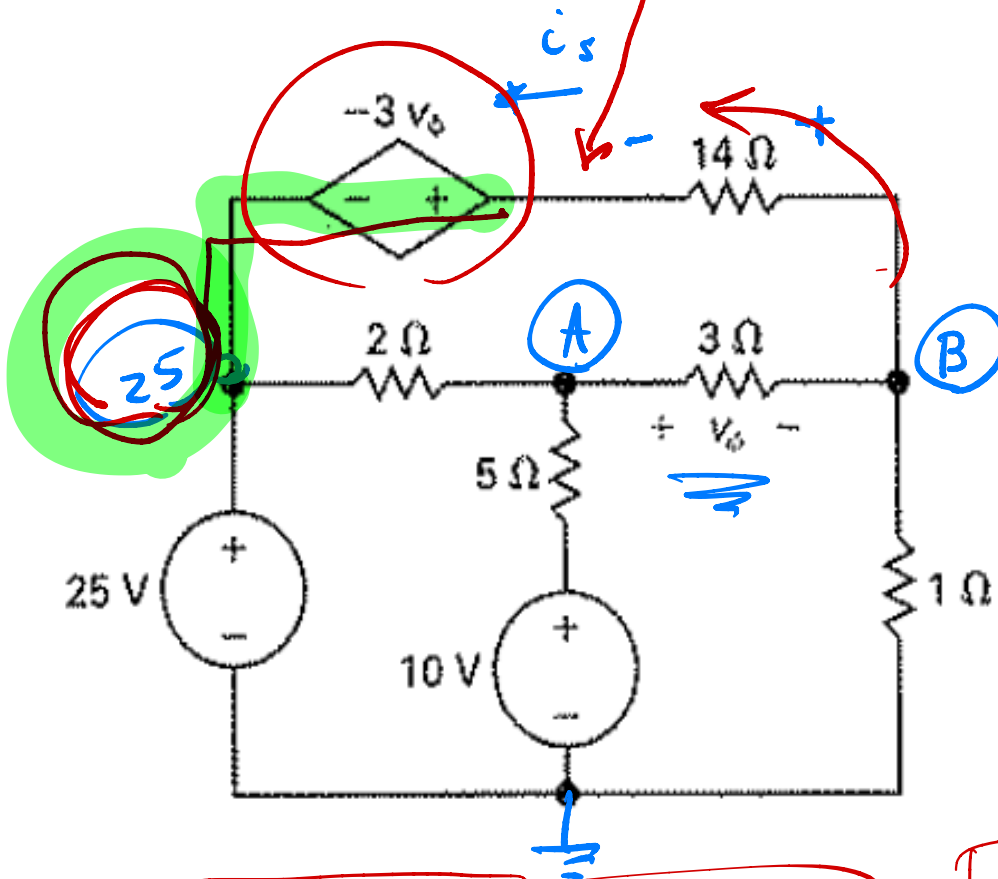Practice problem: find the power of the dependent source



$$25 + (-3V_\phi) = 25 - 3(A-B)$$

$$V_\phi = A - B$$

node A:

$$\frac{A-25}{2} + \frac{A-B}{3} + \frac{A-10}{5} = 0$$

node B:


$$\frac{B}{1} + \frac{B-A}{3} + \frac{B-25+3(A-B)}{14} = 0$$

$$I_s = \frac{B - 25 + 3(A-B)}{14}$$

$$V_s = -3(A-B)$$


$$i_0 = 11.25 \text{ A}$$

Practice problem: find i_0

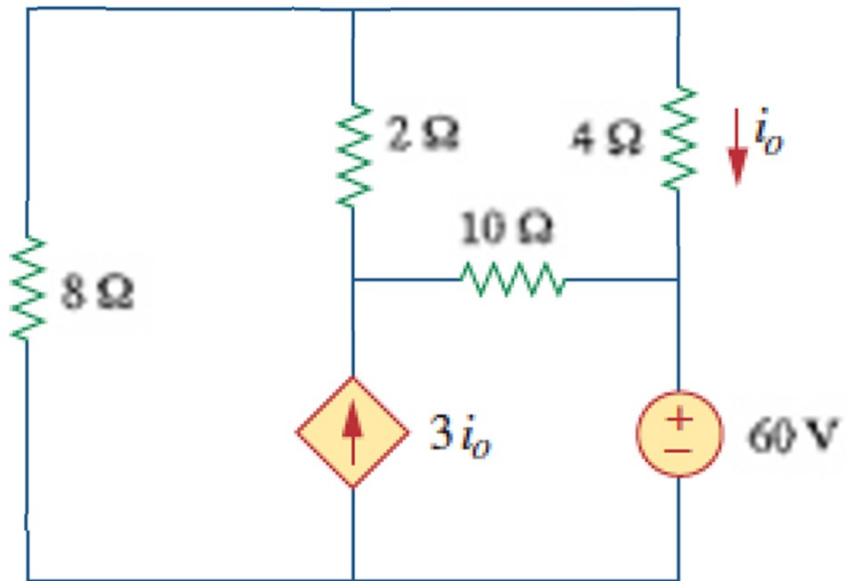


$$I_0 = 7.5 \text{ A}$$

Practice problem: find I_0

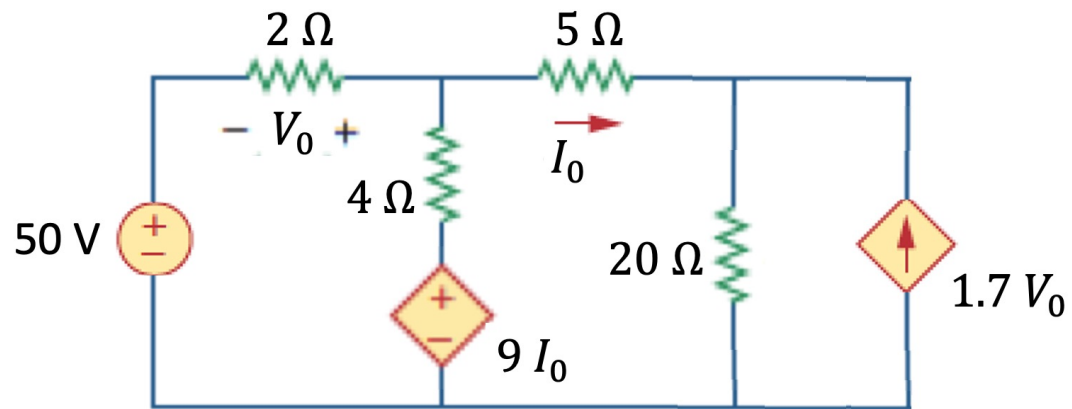

Practice problem: find v_o

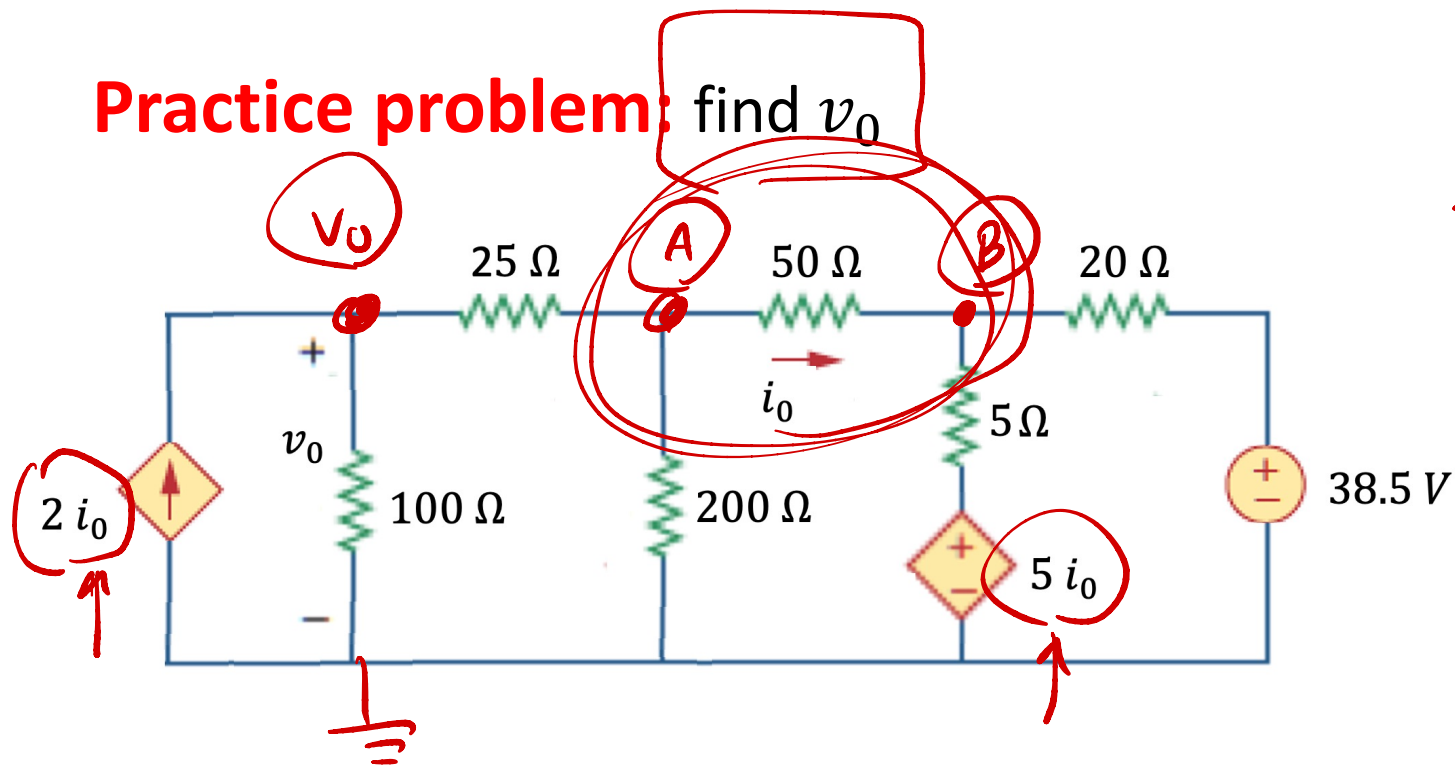

$$v_o = -50 V$$

KCL
3 eqs at
 v_o, A, B

one extra

$$i_o = \frac{A - B}{50}$$