
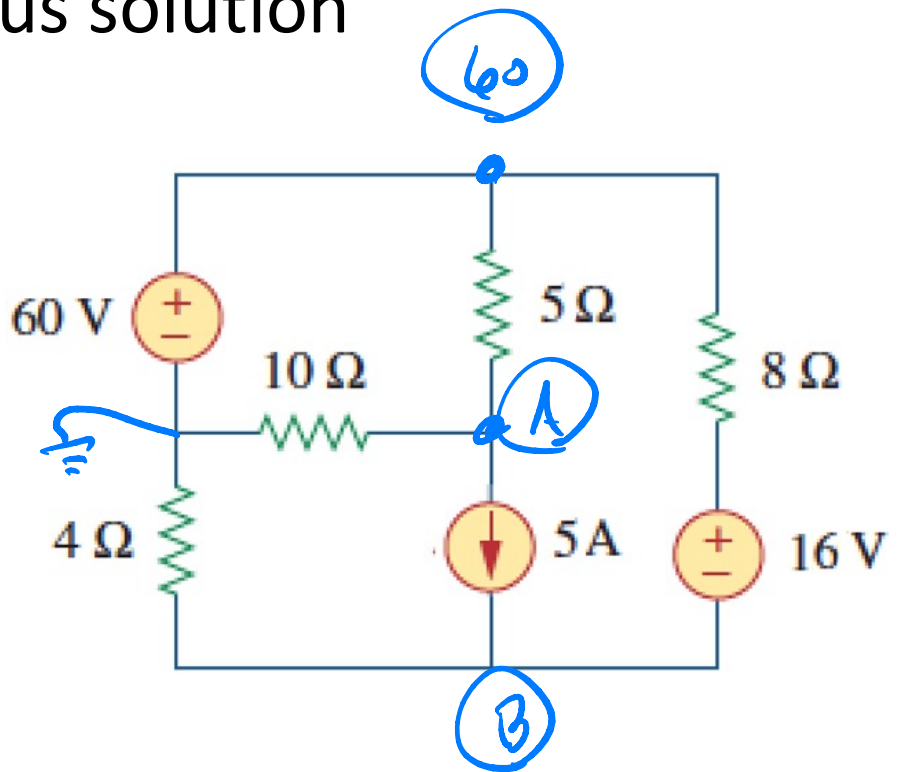


Node – 5


supernodes

Extension #4 – multiple V-only branches


- There might be an obvious solution

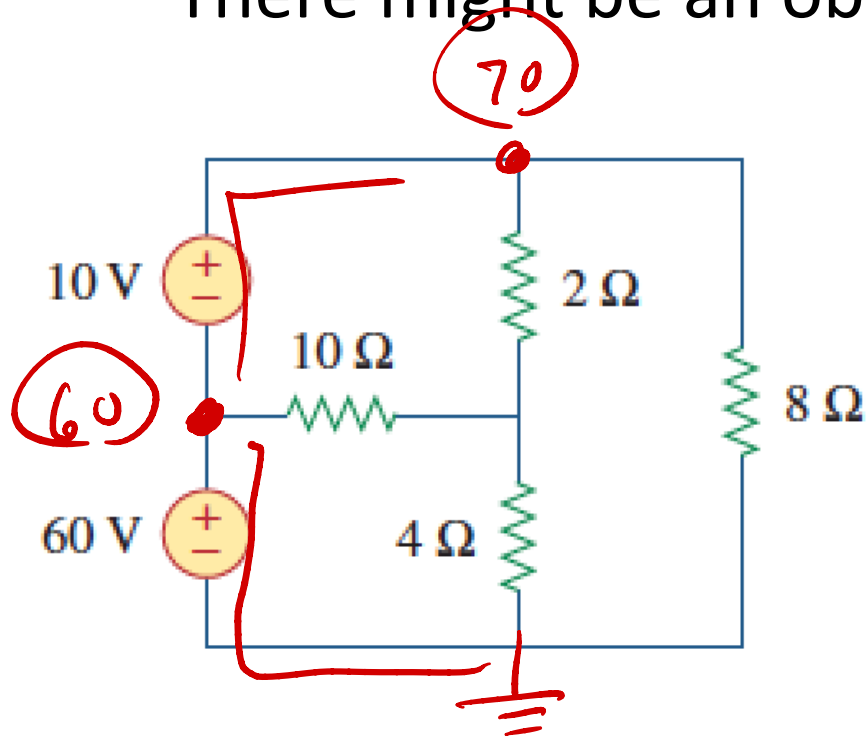


But sometimes ??

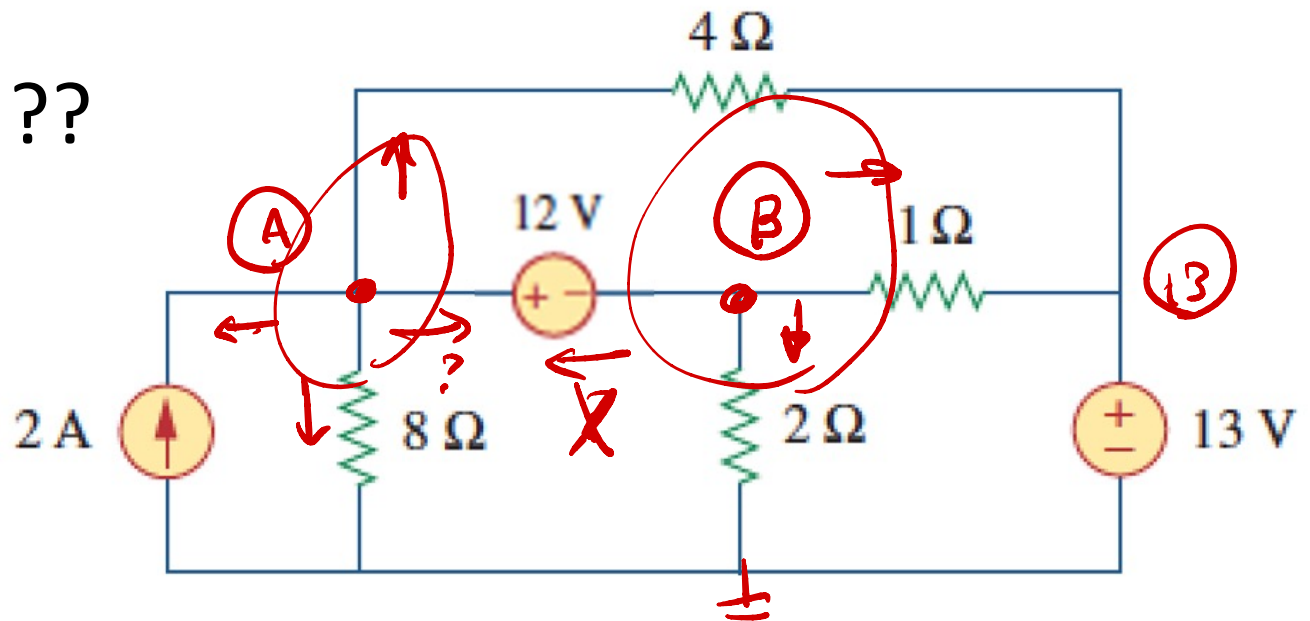

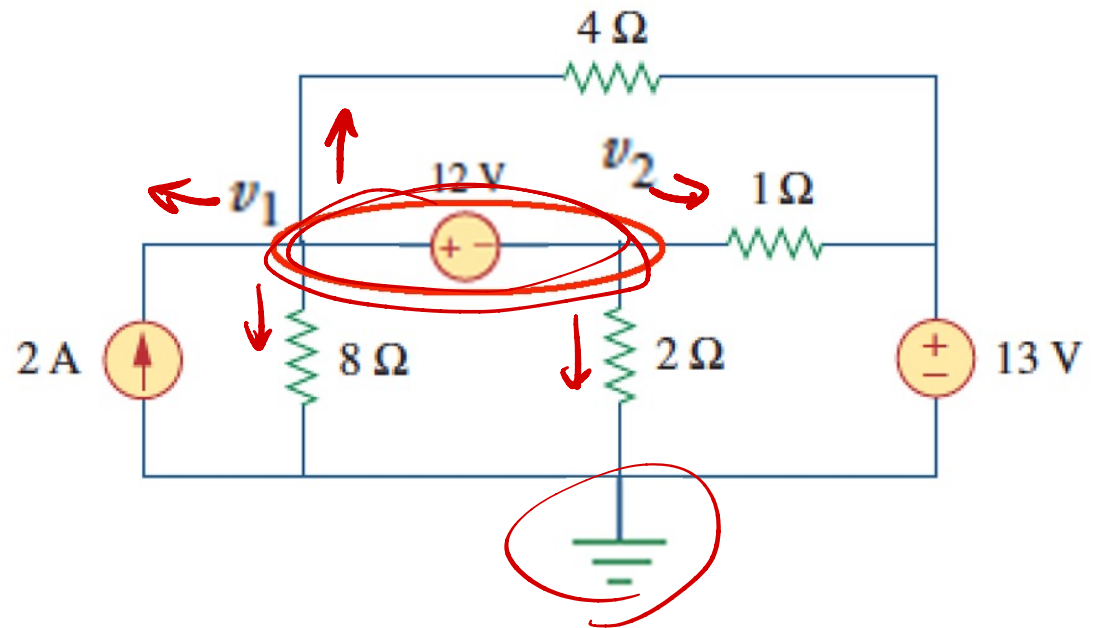- Define a “supernode” (a cutset)
- Apply KCL on it
- Relate the voltages across it




Example (details on next slide)

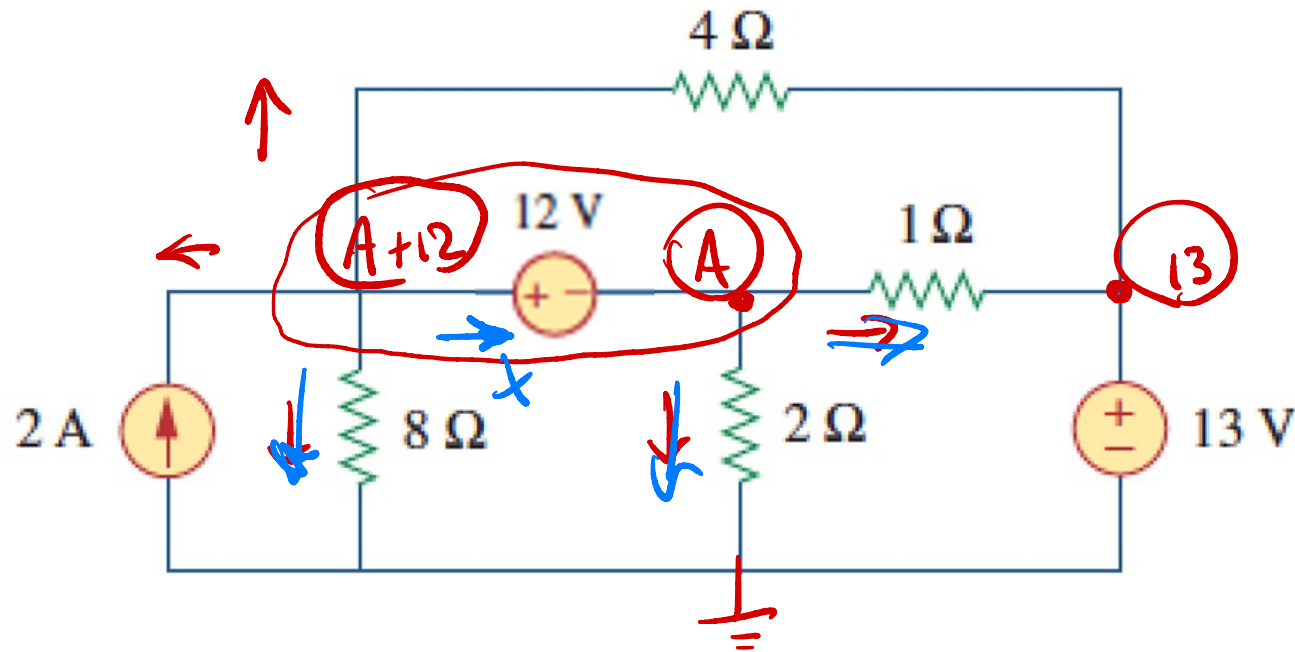

KCL @ supernode:
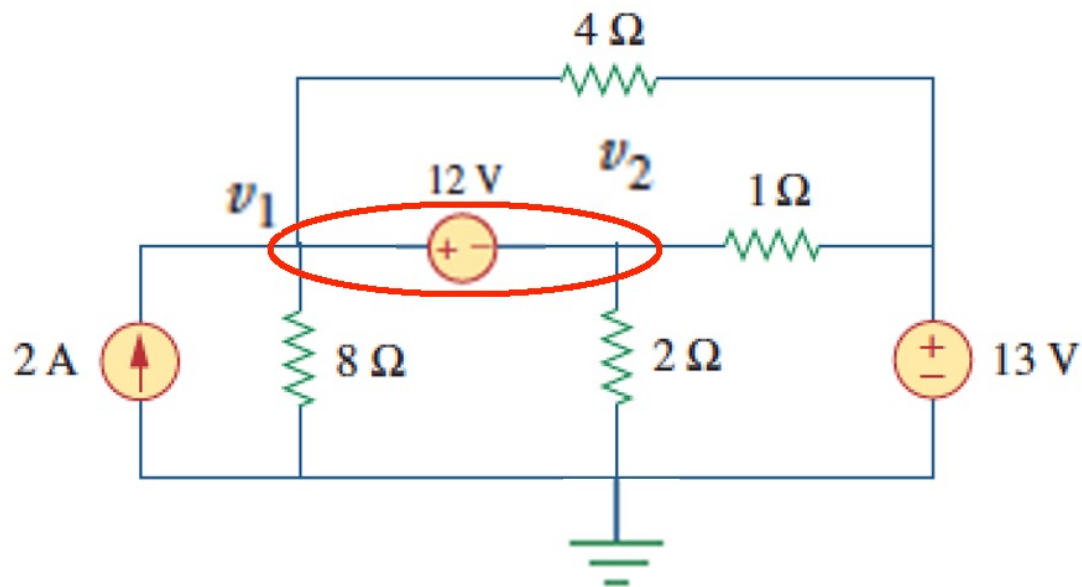
$$\frac{A}{2} + \frac{A-13}{1} + \frac{A+12}{8} - 2 + \frac{A+12-13}{4} = 0$$



Relate nodes:

$$v_2 = v_1 - 12$$

Node equation:

$$\frac{v_1}{8} - 2 + \frac{v_1 - 13}{4} + \frac{v_2 - 13}{1} + \frac{v_2}{2} = 0$$

$$3v_1 + 12(v_1 - 12) = 146$$


$$3v_1 + 12v_2 = 146$$

$$15v_1 = 290$$

$$v_1 = 19\frac{1}{3}$$

$$v_2 = 7\frac{1}{3}$$

Example: find i

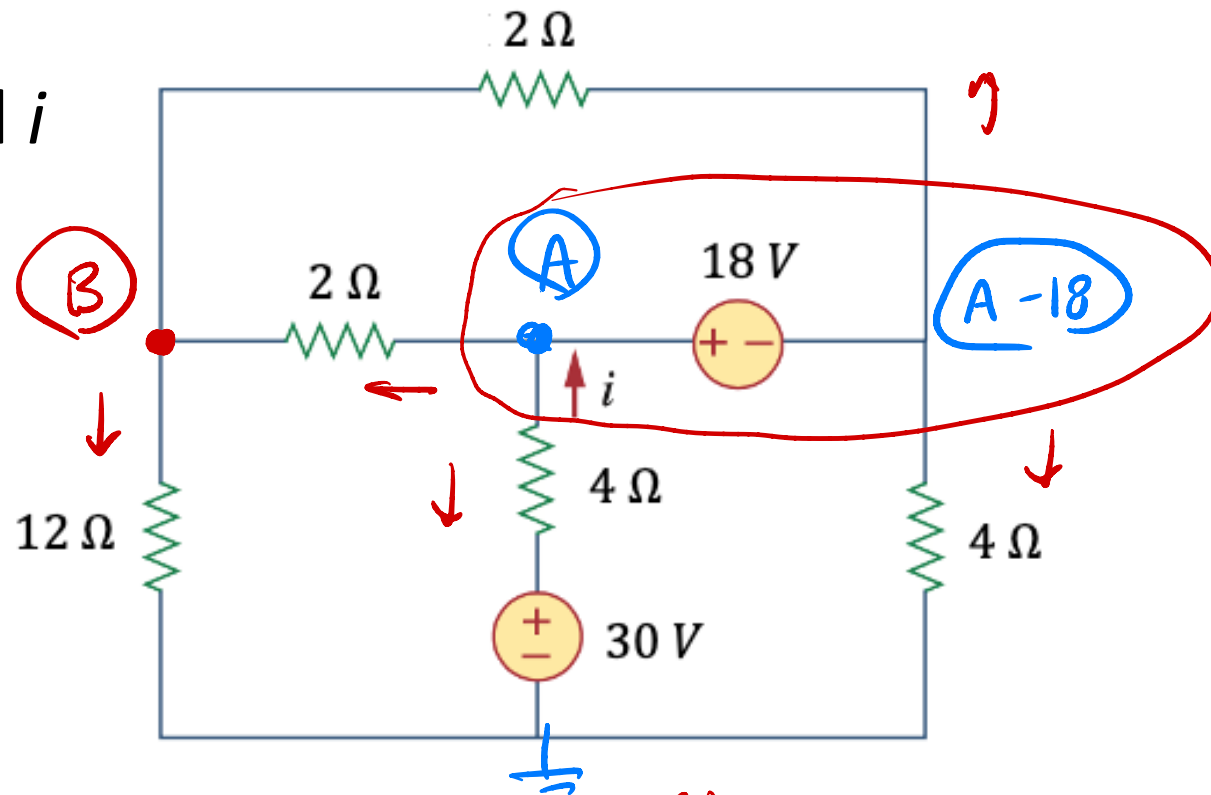


node B :


$$\frac{B}{12} + \frac{B-A}{2} + \frac{B - (A-18)}{2} = 0$$

sup. node :

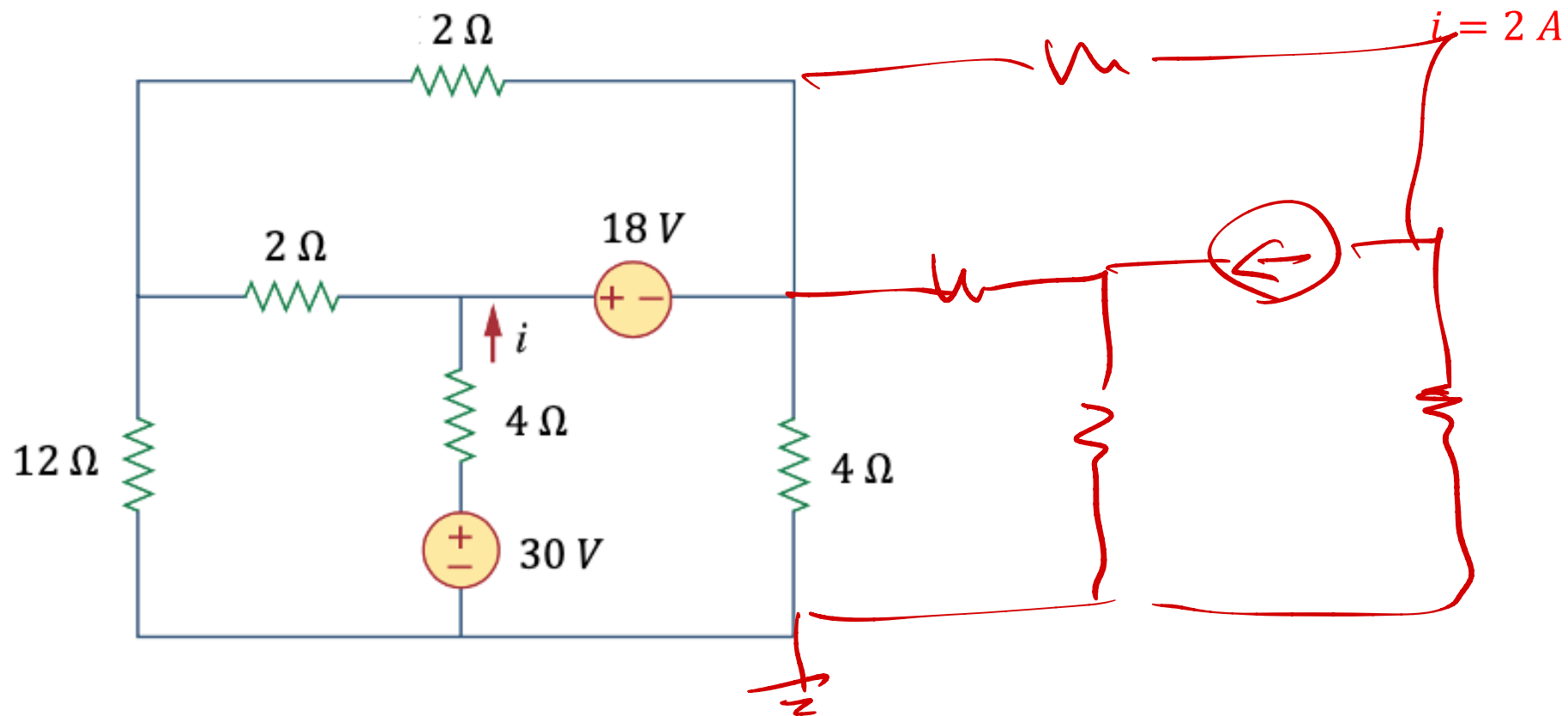
$$\frac{A-B}{2} + \frac{A-30}{4} + \frac{A-18}{4} + \frac{A-18-B}{2} = 0$$



Example: find v

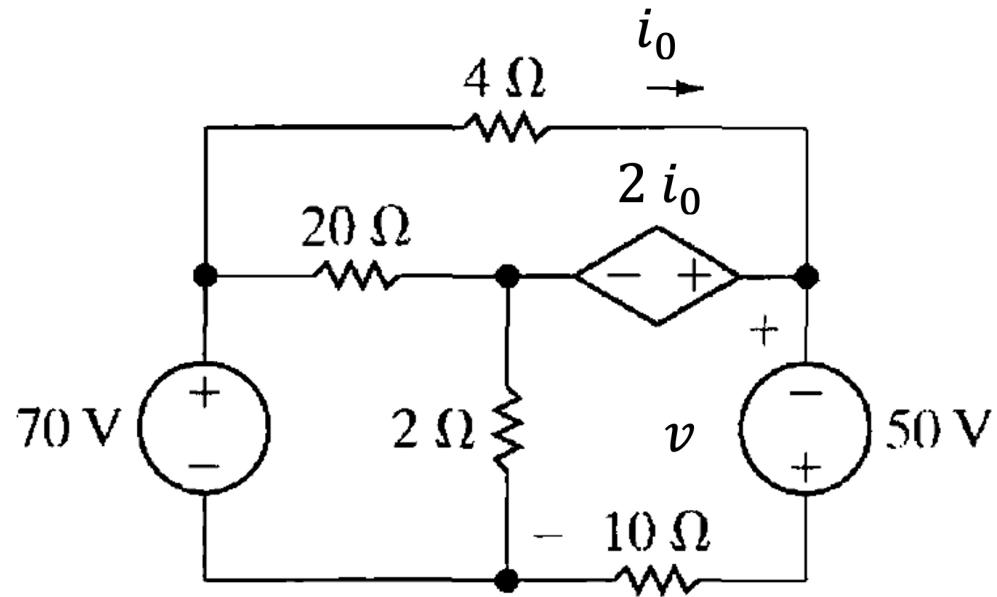


$$v = 30 \text{ V}$$

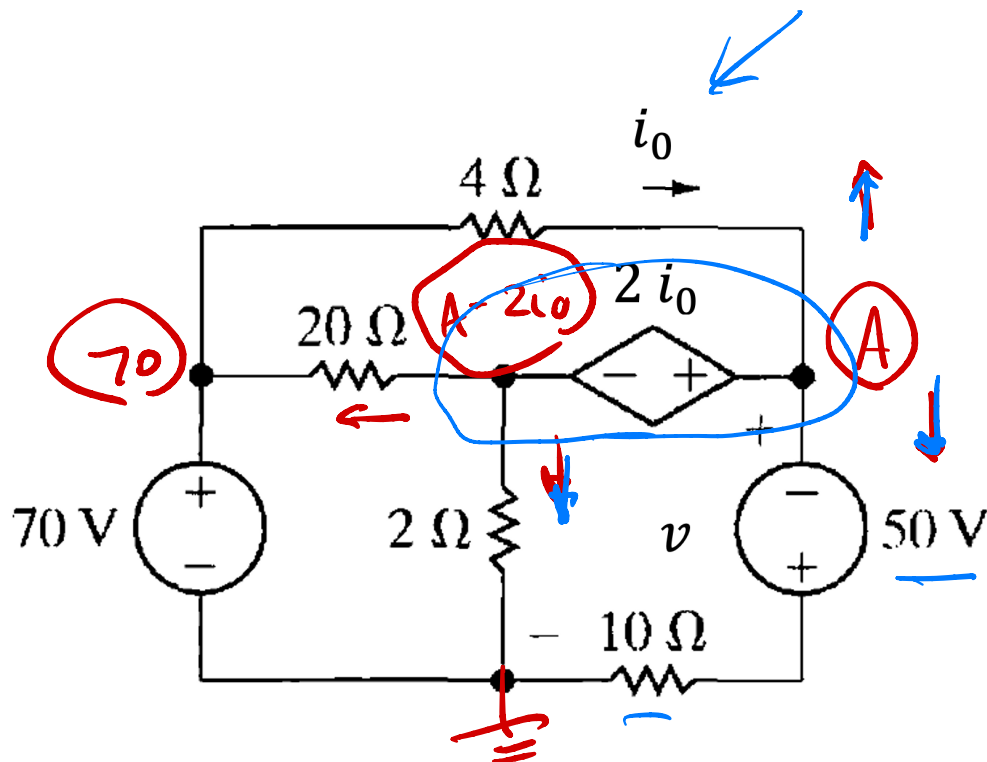

$$\frac{A + 50}{10} + \frac{A - 70}{4} + \frac{A - 2i_0}{2} + \frac{A - 2i_0 - 70}{20} = 0$$

$$i_0 = \frac{70 - A}{4}$$

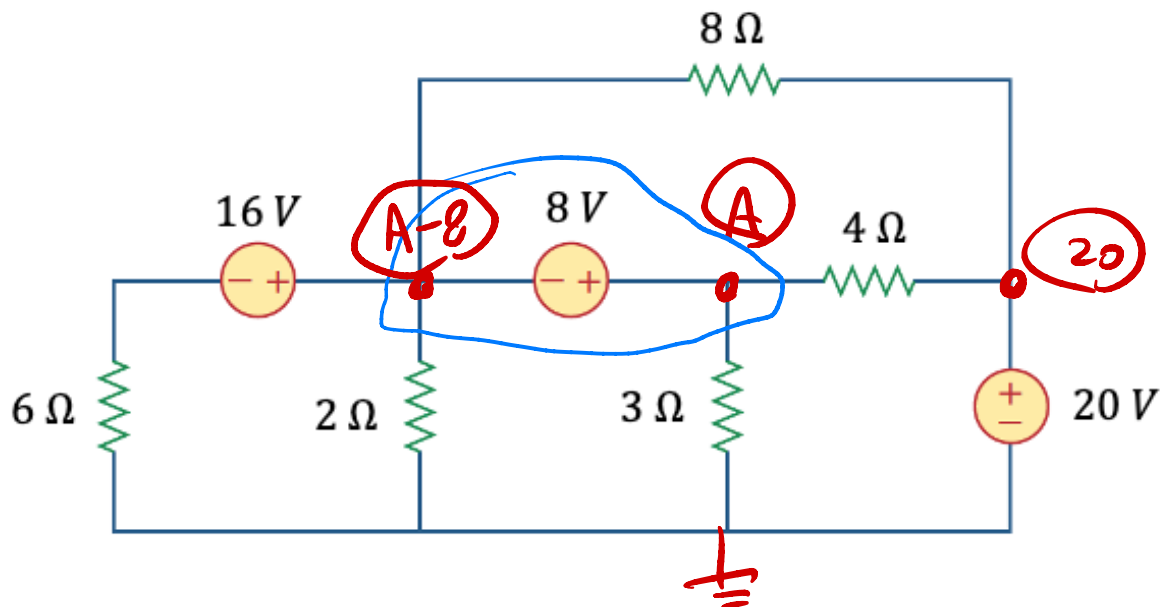
Practice problem: find the power of the 3 Ω resistor



$$\frac{A - 20}{4} + \frac{A}{3} + \frac{A - 8}{2} + \frac{A - 8 - 16}{6} + \frac{A - 8 - 20}{8} = 0$$

$$v_o =$$

Practice problem: find v_o

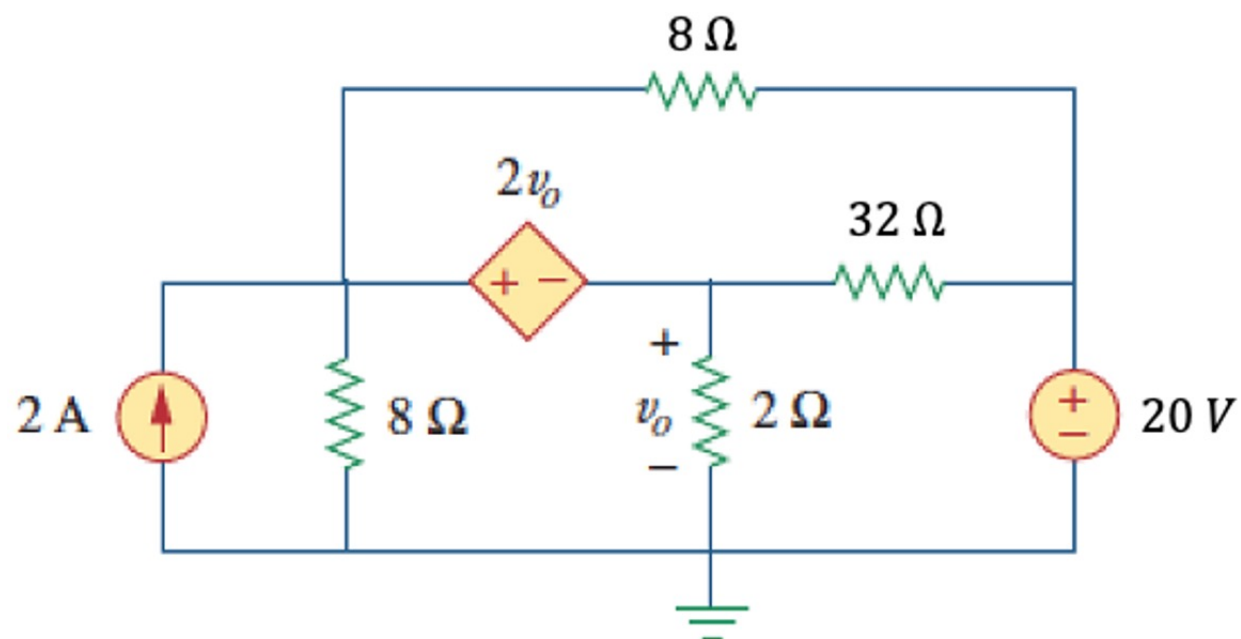

$$v_o =$$

Practice problem : find v_o

