

Node 6

examples

$$v_o = B - 75$$


Example: find v_o

node B:


$$\frac{B-75}{20} + \frac{B}{50} + \frac{B-C}{40} = 0$$

node C:
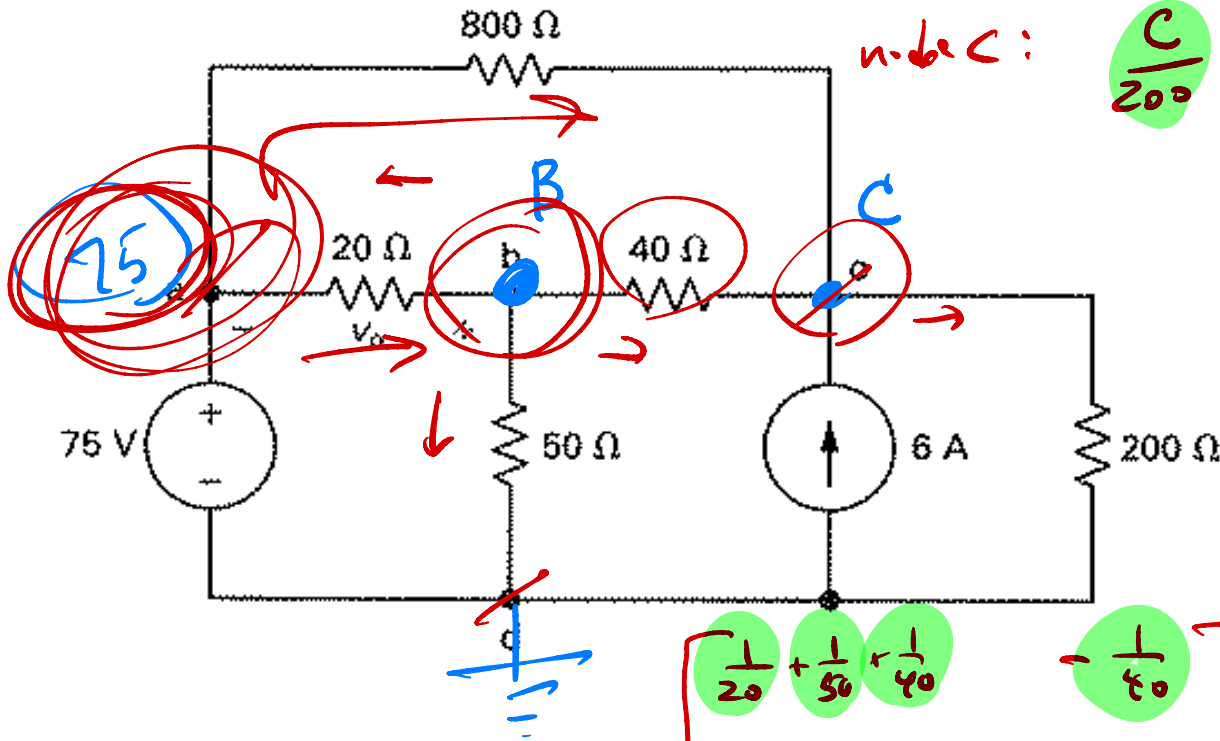
$$\frac{C}{200} - 6 + \frac{C-B}{40} + \frac{C-75}{800} = 0$$



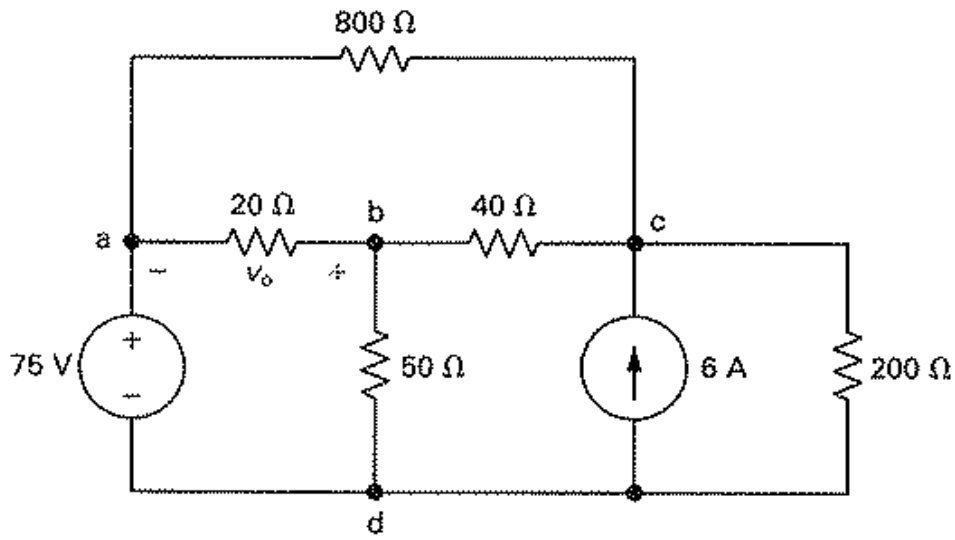
$$\begin{bmatrix} \frac{1}{20} + \frac{1}{50} + \frac{1}{40} & -\frac{1}{40} \\ -\frac{1}{40} & \frac{1}{40} + \frac{1}{200} + \frac{1}{800} \end{bmatrix} \begin{bmatrix} B \\ C \end{bmatrix} = \begin{bmatrix} 75/20 \\ 6 + \frac{75}{800} \end{bmatrix}$$



$v_o = 40 \text{ V}$

Example: find $i_0 = \frac{A-B}{10}$

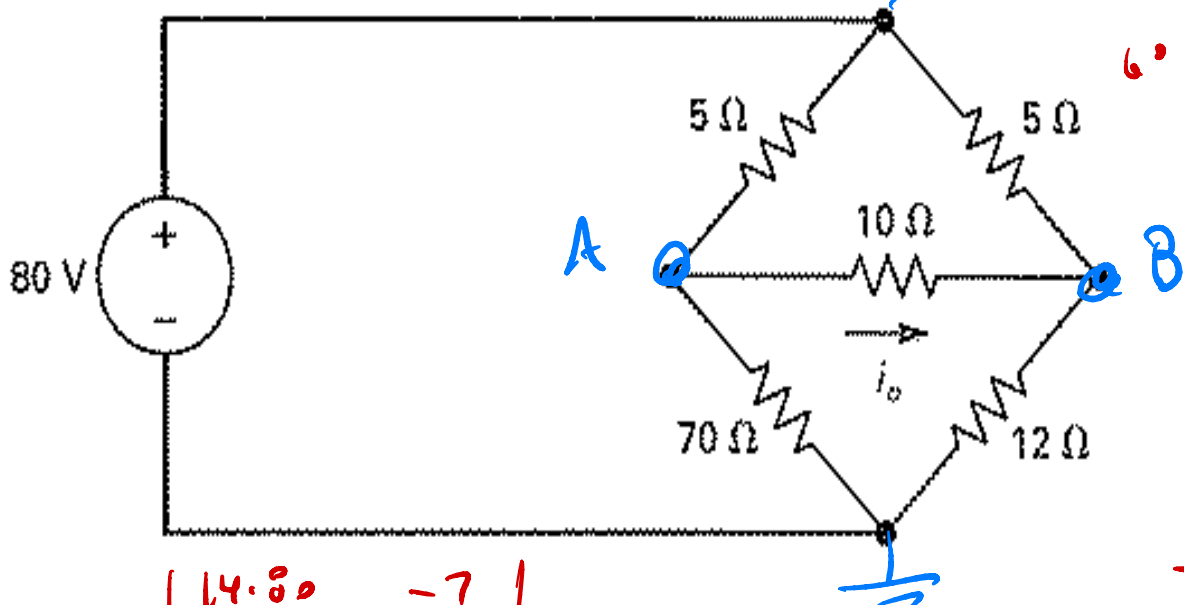

$$70 \left(\frac{A-80}{5} + \frac{A-B}{10} + \frac{A}{70} = 0 \right)$$

$$60 \left(\frac{B-80}{5} + \frac{B-A}{10} + \frac{B}{12} = 0 \right)$$

$$14A + 7A + A - 7B = 14 \cdot 80$$


$$22A - 7B = 14 \cdot 80$$

$$12B + 6B - 6A + 5B = 12 \cdot 80$$

$$-6A + 23B = 12 \cdot 80$$

$$A = \frac{\begin{vmatrix} 14 \cdot 80 & -7 \\ 12 \cdot 80 & 23 \end{vmatrix}}{\begin{vmatrix} 22 & -7 \\ -6 & 23 \end{vmatrix}} = \frac{80(14 \cdot 23 + 7 \cdot 12)}{464}$$

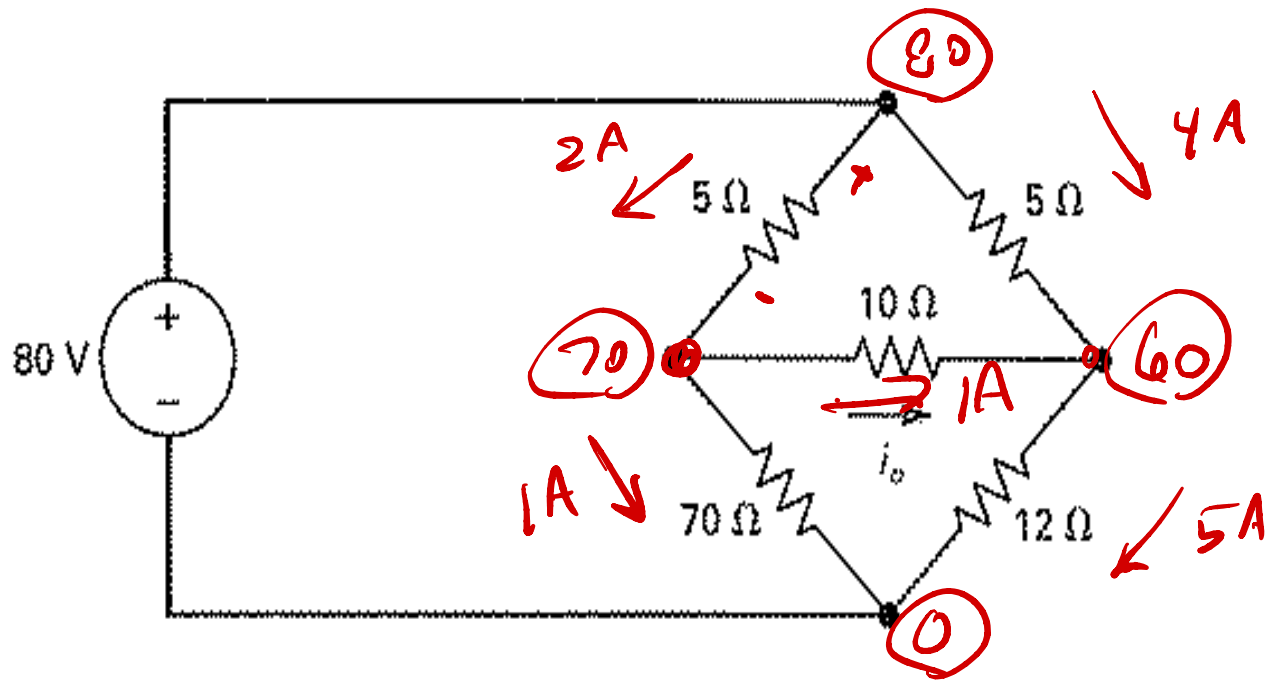
$$= \frac{\quad}{464} = 40 \quad \Rightarrow B = 30$$



$$i_0 = 1A$$


$$P = \frac{(A - B)^2}{10}$$

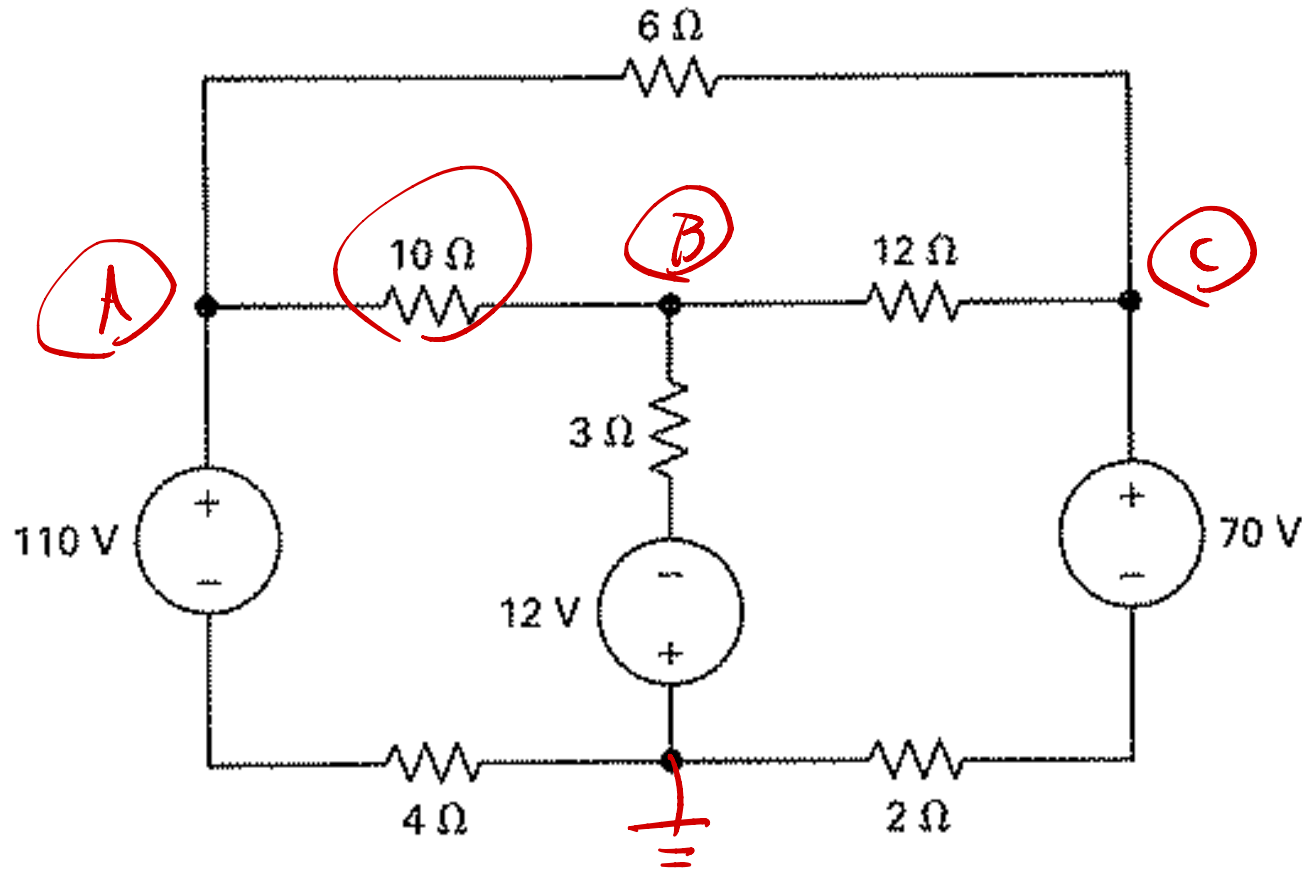Example: find the power of the 10 Ω resistor



$$P = \frac{A^2}{10}$$

$$P = 360 \text{ W}$$

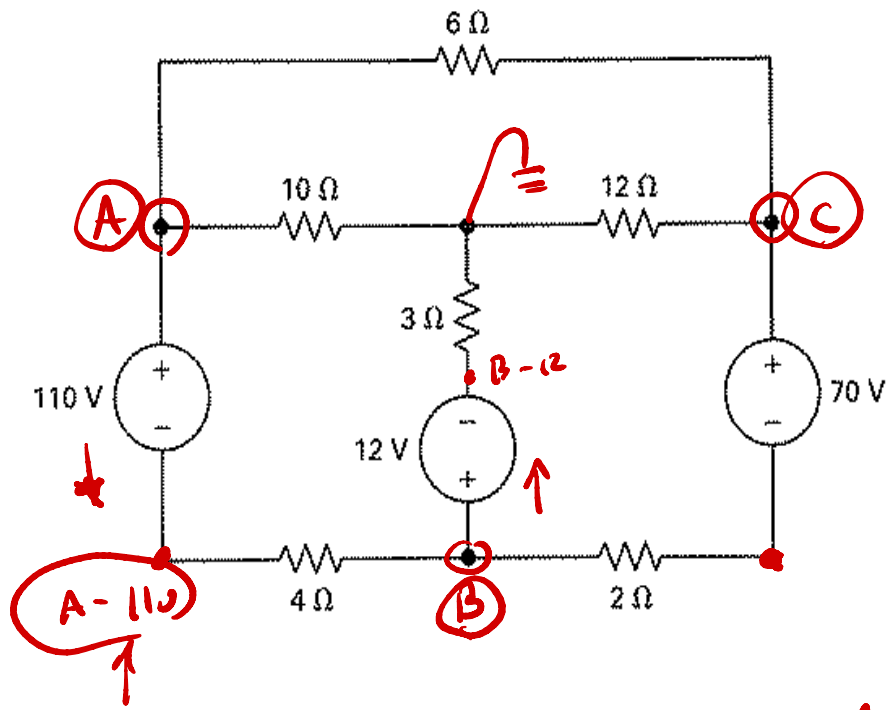

node A:

$$\frac{A-C}{6} + \frac{A}{10} + \frac{A-110-B}{4} = 0$$

node B:


$$\frac{B-(A-110)}{4} + \frac{B-(C-70)}{2} = 0$$


$$\frac{B-12}{3} = 0$$

node C:

$$\frac{C}{12} + \frac{C-A}{6} + \frac{C-70-B}{2} = 0$$


Example: find v

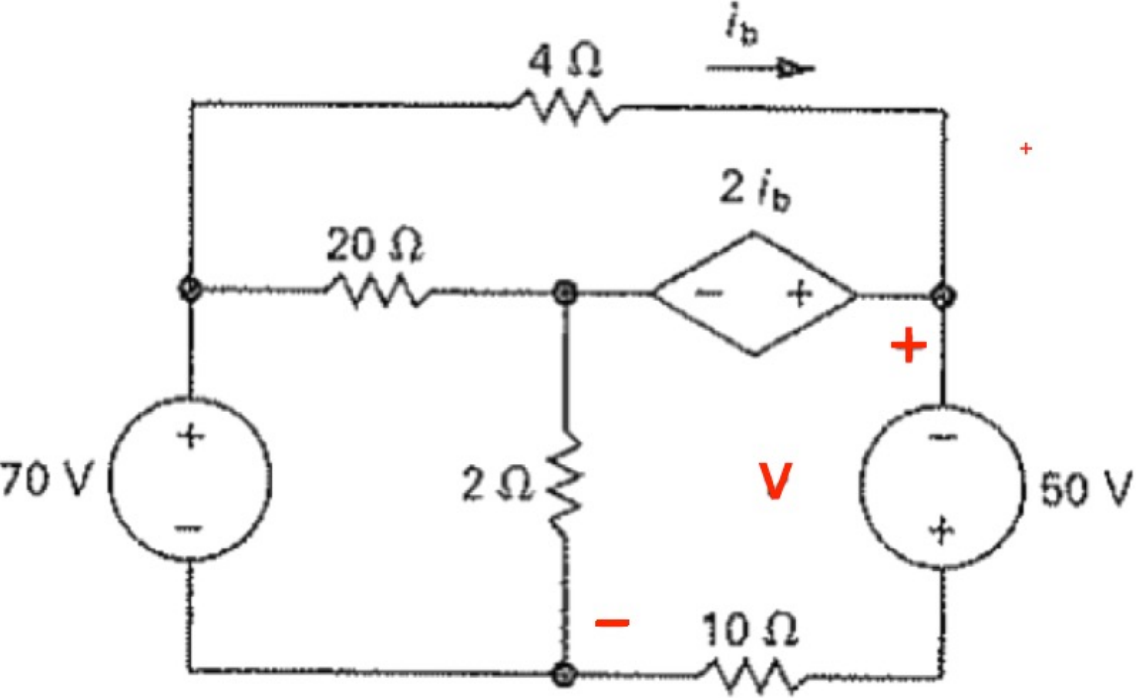


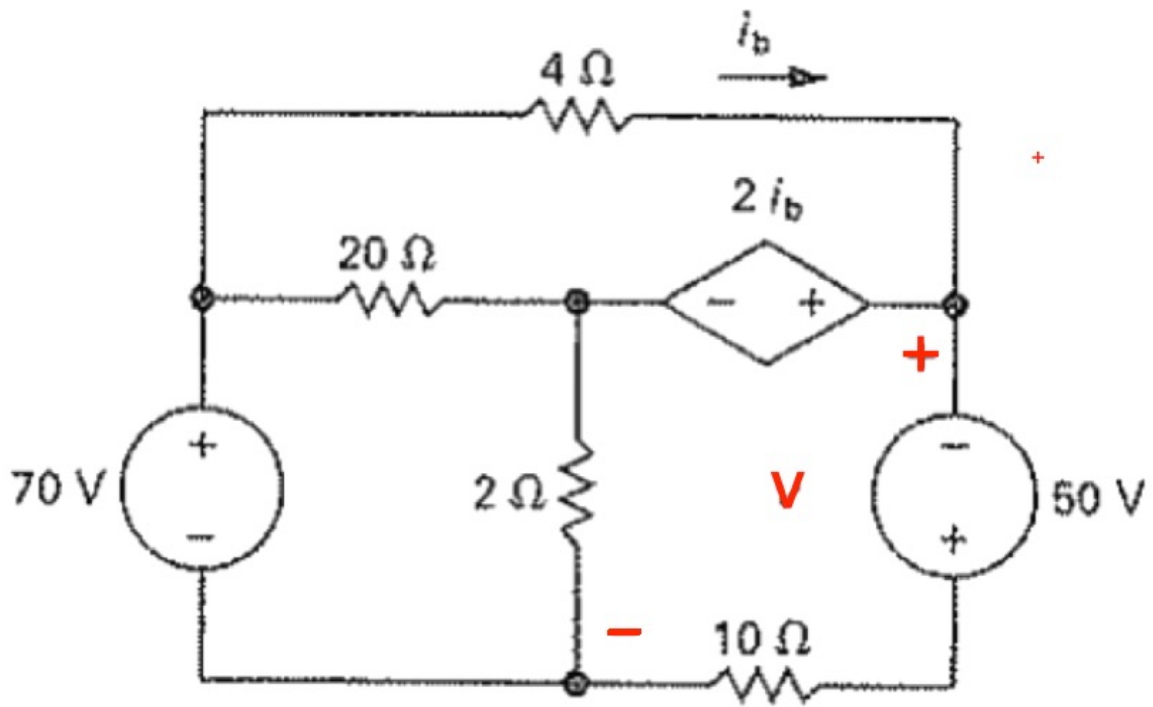

$$v = 30 \text{ V}$$

Example:

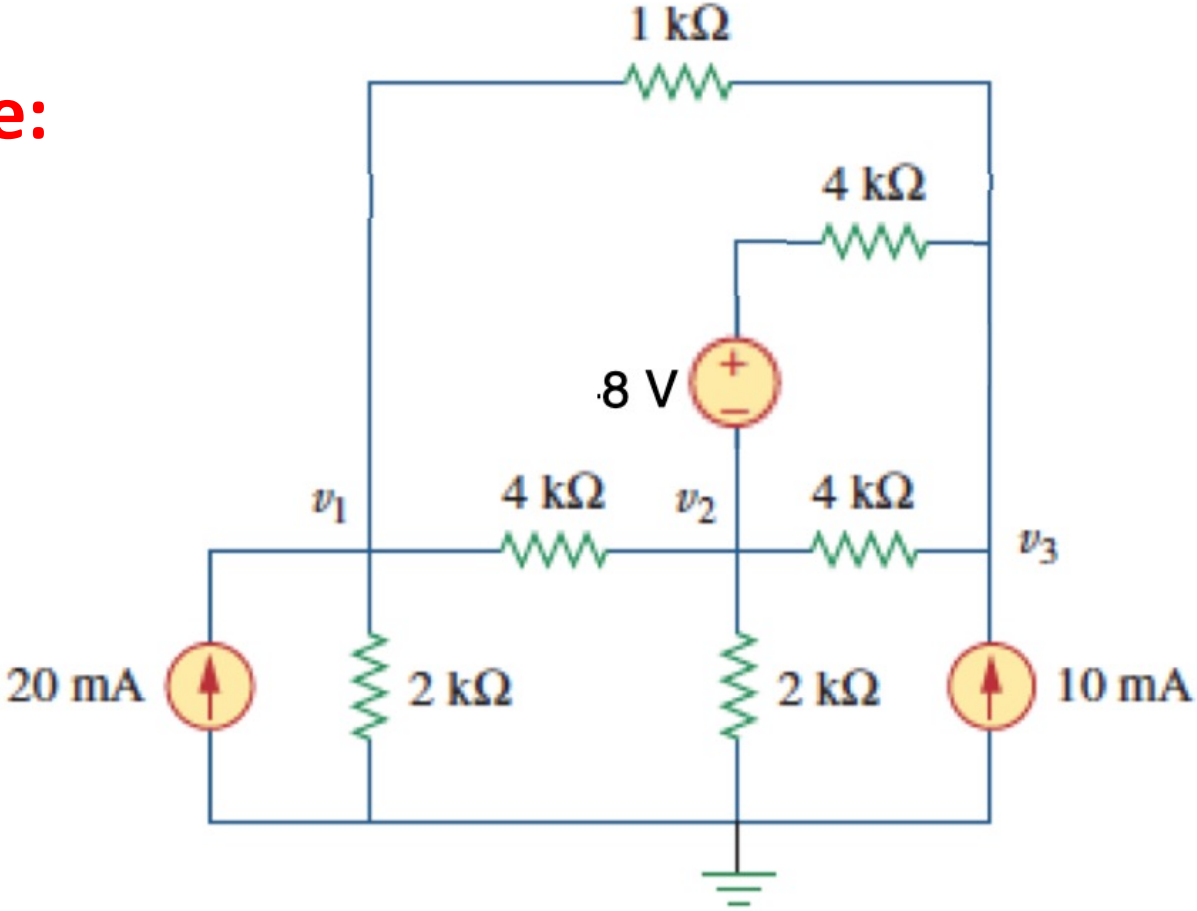

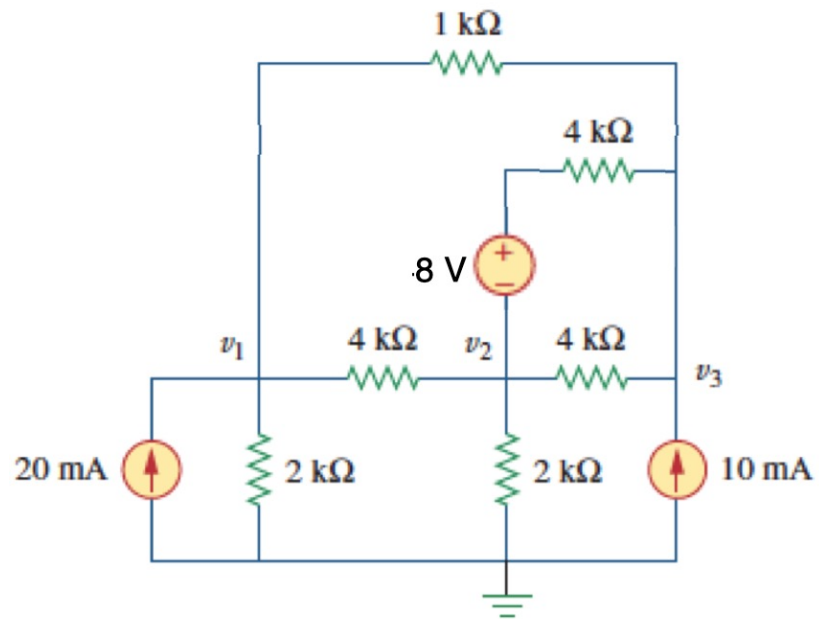


$$v_1 = 37.8 \text{ V}$$

$$v_2 = 22.2 \text{ V}$$

$$v_3 = 40.6 \text{ V}$$

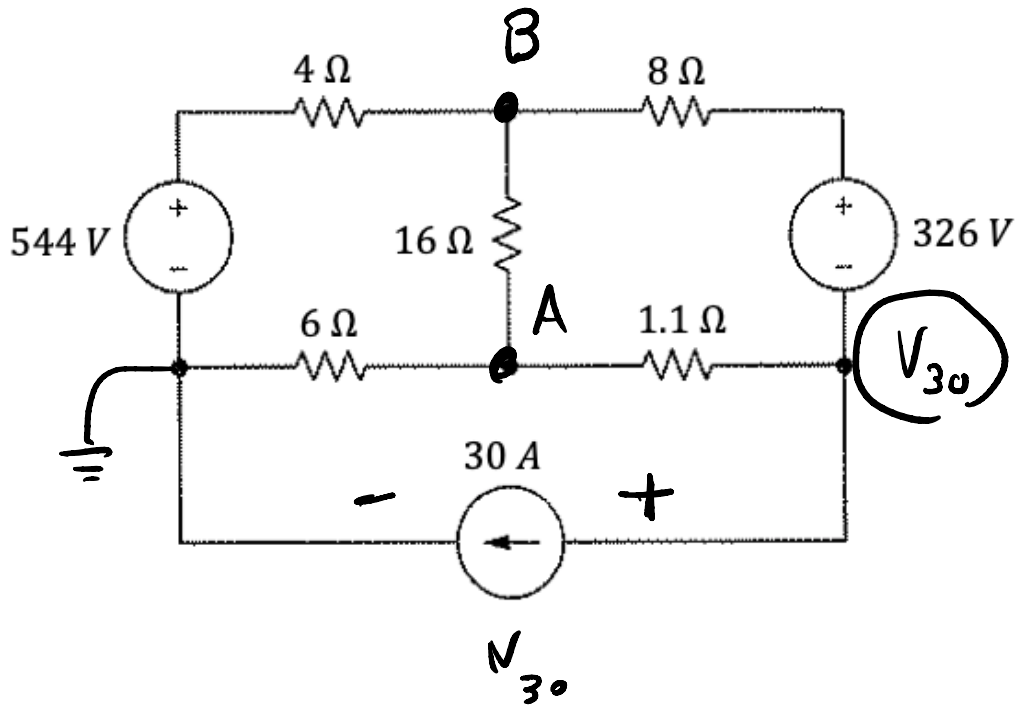Practice problem: find the power of the current source



$$= 30 \cdot V_{30}$$

node A:

$$\frac{A}{6} + \frac{A - V_{30}}{1.1} + \frac{A - B}{16} = 0$$

node B:

$$\frac{B - 544}{4} + \frac{B - A}{16} + \frac{B - (V_{30} + 326)}{8} = 0$$

node V_{30} :

$$30 + \frac{V_{30} - A}{1.1} + \frac{V_{30} + 326 - B}{8} = 0$$

Practice problem: The variable voltage source shown in the circuit below (the source with the diagonal line through it) is adjusted so that the power absorbed by the $5\ \Omega$ resistor is 5 watts. Find the value of v_{DC} .

