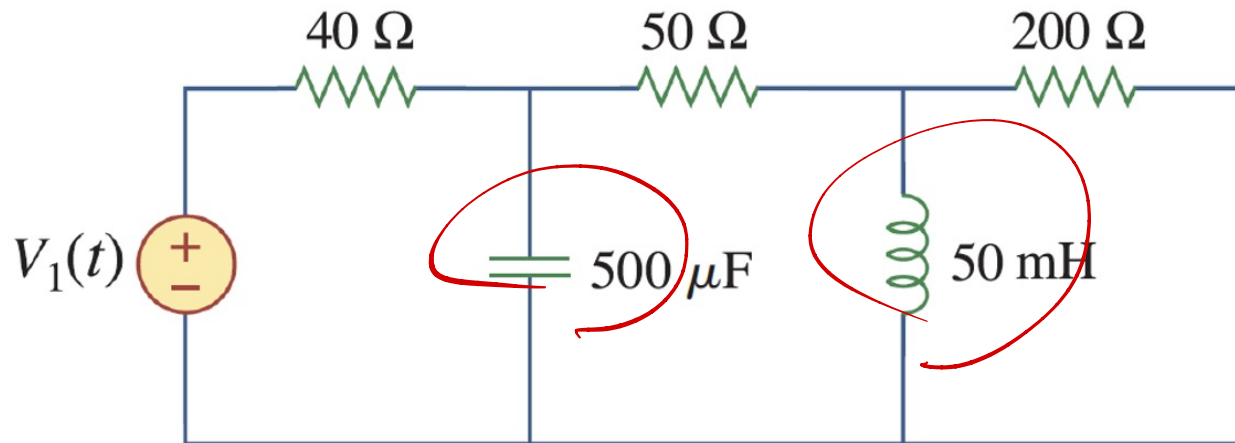


# Phasors – 2

RLC circuits


# RLC Circuits

- How do we analyze this?



- Watch the following (details posted)

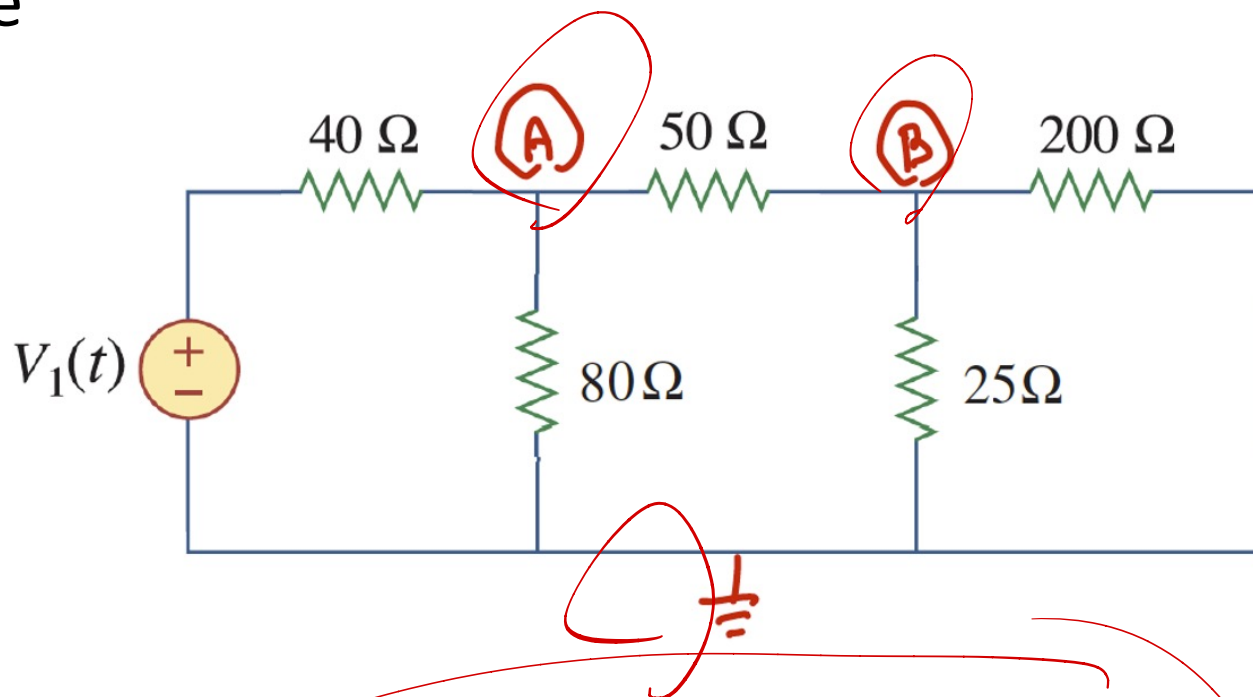
- If only resistors, then node analysis would be the obvious choice



$$\frac{A - V_1(t)}{40} + \frac{A}{80} + \frac{A - B}{50} = 0$$

$$\frac{B}{200} + \frac{B}{25} + \frac{B - A}{50} = 0$$

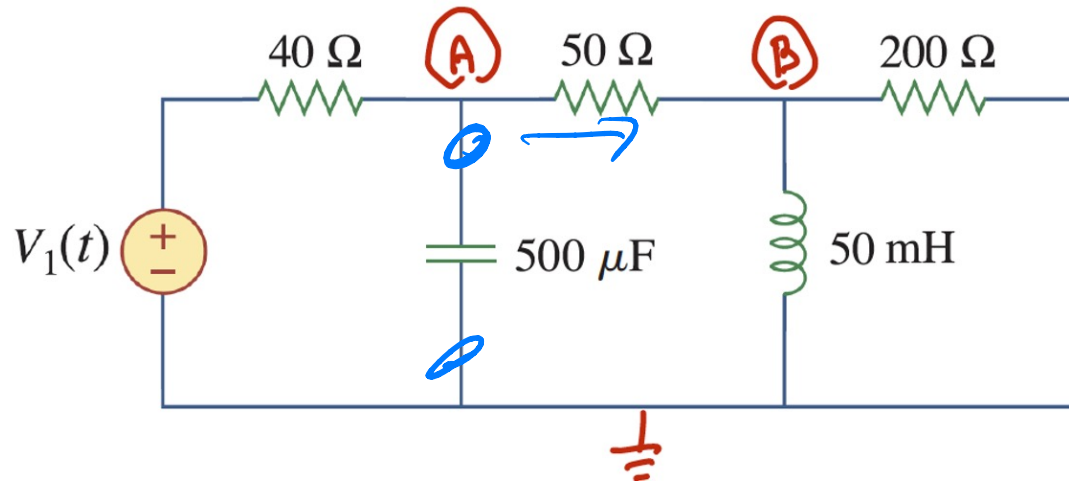- Let's try the same using L & C definitions




- Node A:

$$\frac{A(t) - V_1(t)}{40} + i_C(t) + \frac{A(t) - B(t)}{50} = 0$$

$$0.0005 \frac{dA(t)}{dt}$$
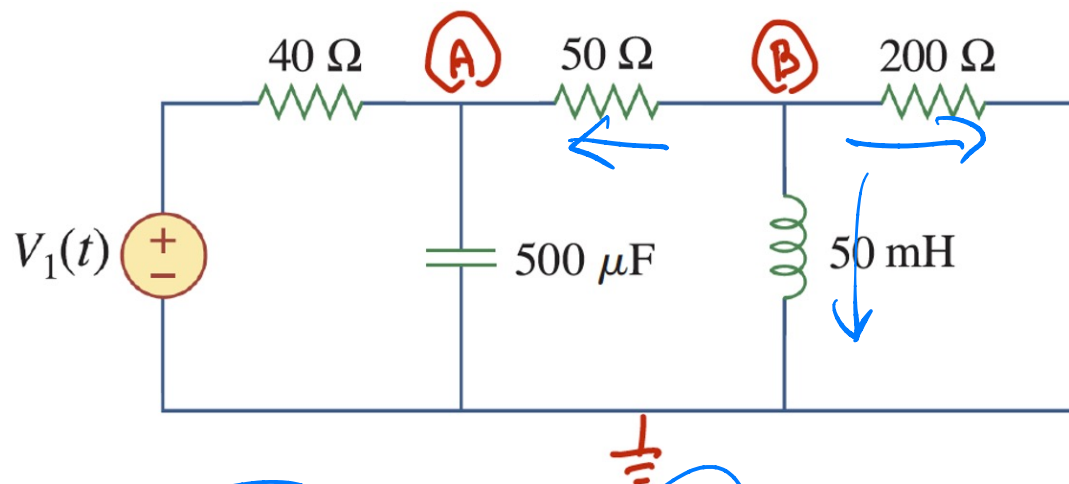
$$\frac{dA(t)}{dt} + 90 A(t) - 40 B(t) = 50 V_1(t)$$



- Node B:

$$\frac{B(t)}{200} + i_L(t) + \frac{B(t) - A(t)}{50} = 0$$

$\frac{1}{L} \int B(s) ds$  and take a time derivative


$$\frac{1}{200} \frac{dB(t)}{dt} + \frac{1}{0.05} B(t) + \frac{1}{50} \frac{dB(t)}{dt} - \frac{1}{50} \frac{dA(t)}{dt} = 0$$

$$\frac{dB(t)}{dt} + 800 B(t) - 0.8 \frac{dA(t)}{dt} = 0$$

- Result is a pair of differential equations

$$\frac{dA(t)}{dt} + 90 A(t) - 40 B(t) = 50 V_1(t)$$
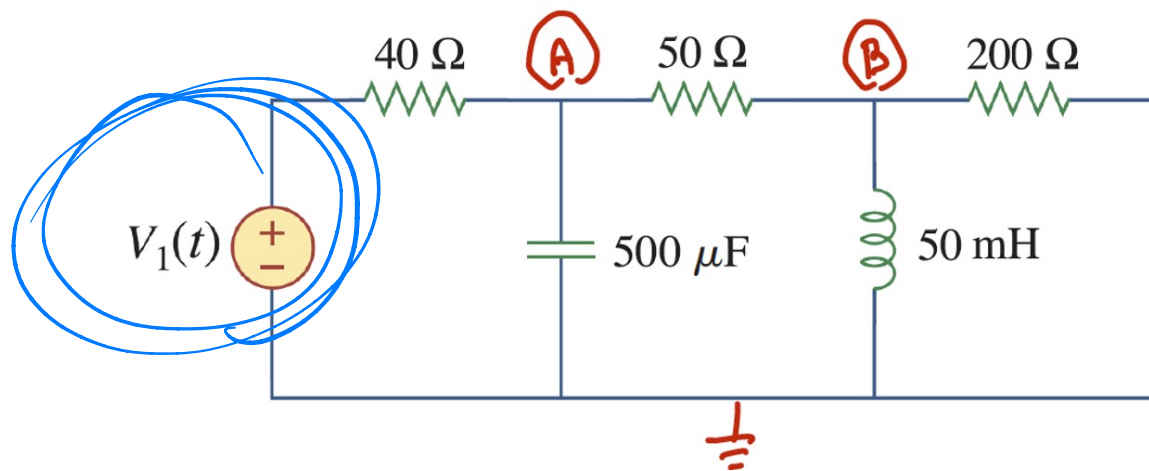
$$\frac{dB(t)}{dt} + 800 B(t) - 0.8 \frac{dA(t)}{dt} = 0$$



- How to solve?

- Linear ✓

- Constant coefficient ✓

- Homogeneous and particular solutions

- Steps:

1. Form a single equation from the pair
2. Find the homogeneous solution
3. Find the particular solution
4. Solve for the unknowns

$$\frac{dA(t)}{dt} + 90A(t) - 40B(t) = 50V_1(t)$$
$$\frac{dB(t)}{dt} + 800B(t) - 0.8\frac{dA(t)}{dt} = 0$$

1. Form a single equation from the pair


– Some magic yields

$$\frac{d^2 A(t)}{dt^2} + 858 \frac{dA(t)}{dt} + 72,000 A(t) = 50 \frac{dV_1(t)}{dt} + 40,000 V_1(t)$$

and

$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 40 \frac{dV_1(t)}{dt}$$

– Continue with  $B(t)$

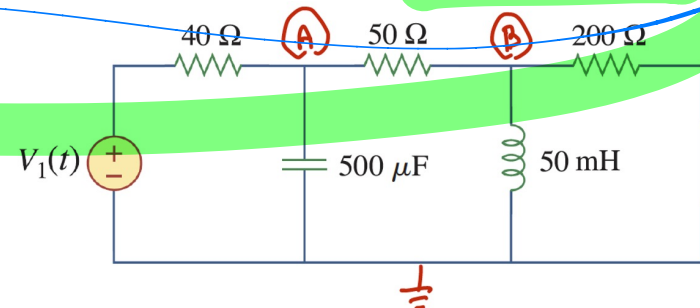



$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 40 \frac{dV_1(t)}{dt}$$

2. Find the homogeneous solution

$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 0$$

– Characteristic polynomial:  $s^2 + 858s + 72,000 = 0$

• Roots,  $s = -94.3, -764$

$$B_{\text{homogeneous}}(t) = a_1 e^{-94.3t} + a_2 e^{-764t}$$

– Since real parts are negative, then

$$\lim_{t \rightarrow \infty} B_{\text{homogeneous}}(t) = 0 \Rightarrow \text{“transient”}$$

3. Find the particular solution – depends upon the rhs  
 – Table lookup:


**Table 2.1** Method of Undetermined Coefficients

Term in $r(x)$	Choice for $y_p(x)$
$ke^{\gamma x}$	$Ce^{\gamma x}$
$kx^n$ ( $n = 0, 1, \dots$ )	$K_n x^n + K_{n-1} x^{n-1} + \dots + K_1 x + K_0$
$k \cos \omega x$	$\left. \begin{aligned} &K \cos \omega x + M \sin \omega x = K \cos(\omega t + \theta) \\ &e^{\alpha x} (K \cos \omega x + M \sin \omega x) \end{aligned} \right\}$
$k \sin \omega x$	
$ke^{\alpha x} \cos \omega x$	$\left. \begin{aligned} &e^{\alpha x} (K \cos \omega x + M \sin \omega x) \end{aligned} \right\}$
$ke^{\alpha x} \sin \omega x$	

- Focus on sinusoidal sources – why? Let

$$V_1(t) = 10 \cos(500t) \text{ volts}$$

4. Find the unknowns  $K$  and  $\theta$

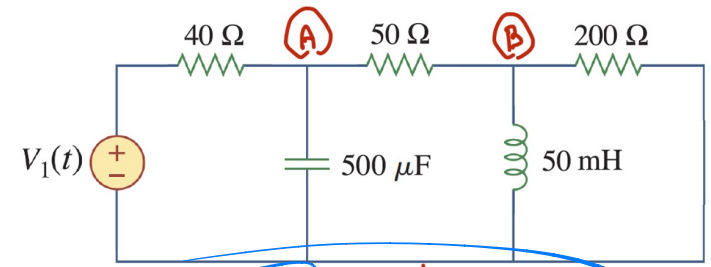

$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = -40,000 \sin 500t$$

$$B(t) = K \cos(500t + \theta)$$

– Grind through calculus, algebra, and trig

$$B_{steady-state}(t) = 431 \cos(500t - 22.5^\circ) \text{ mV}$$

- **Summary** – while it works, the method is tedious and we need want a better approach → the “phasor” method

# The Phasor Concept

Extend a sinusoid with an imaginary part

$$x(t) = A \cos(\omega t + \phi)$$



$$x(t) = A \cos(\omega t + \phi) + jA \sin(\omega t + \phi)$$

$$= A e^{j(\omega t + \phi)}$$



$$= \underbrace{A e^{j\phi}}_{\text{phasor}} \underbrace{e^{j\omega t}}_{\text{rotating part}}$$

**$A$** , the "phasor"  
Rotating part

Euler's identity

Bold for complex

$$A \cos \phi + j A \sin \phi$$

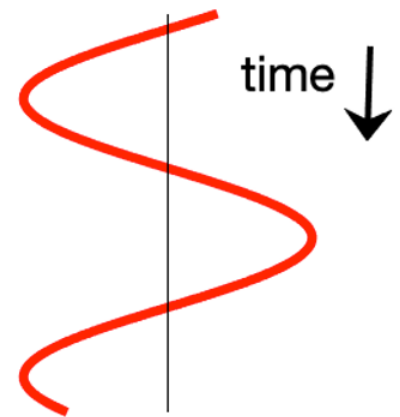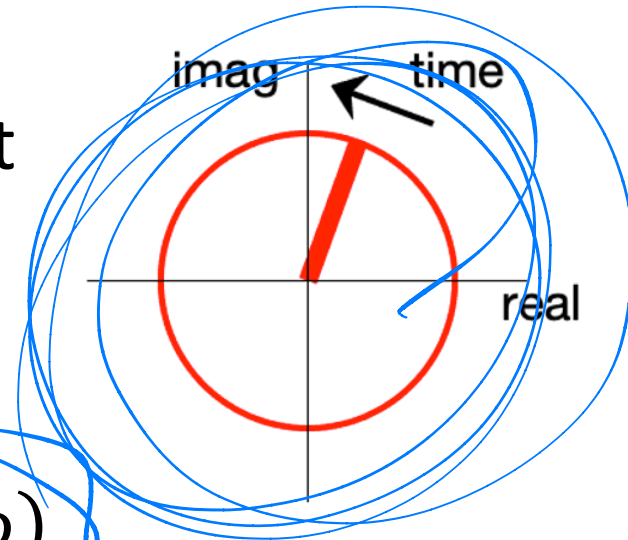

- Time functions to phasors

$$x(t) = 10 \cos \omega t$$

$$\Rightarrow \mathbf{X}e^{j\omega t} = 10 \cos \omega t + j10 \sin \omega t$$

$$= 10(\cos \omega t + j \sin \omega t)$$

$$= 10 e^{j\omega t}$$

$$\text{so } \mathbf{X} = 10 = 10 \angle 0^\circ$$

$$10 + j0$$

$$A \cos \phi + j A \sin \phi$$

- If  $x(t) = 10 \cos(500t + 30^\circ)$  find the phasor

$$\mathbf{X}e^{j\omega t} = 10 \cos(500t + 30^\circ) + j10 \sin(500t + 30^\circ)$$

$$= 10(\cos 500t \cos 30^\circ - \sin 500t \sin 30^\circ) + j10(\cos 500t \sin 30^\circ + \sin 500t \cos 30^\circ)$$

$$= 10 \cos 500t (\cos 30^\circ + j \sin 30^\circ) + j10 \sin 500t (\cos 30^\circ + j \sin 30^\circ)$$

$$= 10(\cos 30^\circ + j \sin 30^\circ)(\cos 500t + j \sin 500t)$$

$$= (8.66 + j5) e^{j500t} = 10 e^{j30\pi/180} e^{j500t}$$

$\mathbf{X}$

Also,  $10 \angle 30^\circ$

$\mathbf{X}$

$10 \cos 30^\circ$   
 $t, 10 \sin 30^\circ$

- If  $x(t) = 4 \cos(\omega t + 45^\circ)$  then


$$\mathbf{X} = 4 \angle 45^\circ$$

$$= 4 \cos 45^\circ + j 4 \sin 45^\circ$$

$$= 2\sqrt{2} + j 2\sqrt{2}$$

$$= 2\sqrt{2} (1 + j)$$

And back again

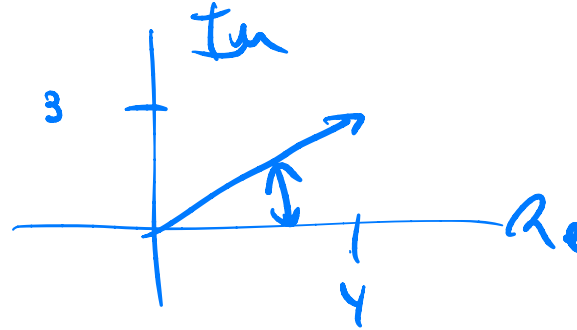


• If  $\mathbf{X} = 4 + j3 = \sqrt{4^2 + 3^2} \angle \tan^{-1} \frac{3}{4} = \underline{5 \angle 36.9^\circ}$

then  $x(t) = 5 \cos(\omega t + 36.9^\circ)$

• If  $\mathbf{X} = -8 - j3 = \sqrt{(-8)^2 + (-3)^2} \angle \tan^{-1} \frac{-3}{-8}$   
 $= \sqrt{73} \angle -162^\circ$

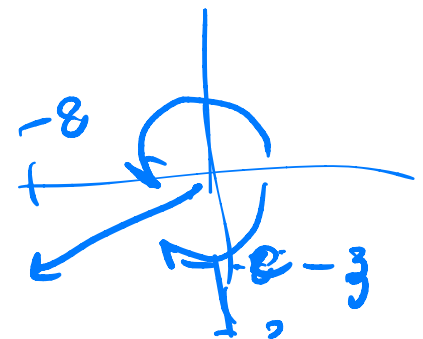then  $x(t) = \sqrt{73} \cos(\omega t - 162^\circ)$





**Practice problem:** If  $x(t) = 100 \cos(100t + 102^\circ)$ ,  
find **X**

$$-20.6 + j97.8$$

**Practice problem:** If  $x(t) = 12 \cos(100t + 12^\circ)$ , find  
**X**

$$11.7 + j2.49$$

**Practice problem:** If  $x(t) = 12 \sin(100t + 12^\circ)$ , find  
**X**

$$2.49 - j211.7$$

**Practice problem:** If  $x(t) = 13 \cos(100t - 202.6^\circ)$ ,  
find **X**

$$-12 + j5$$

**Practice problem:** If  $\mathbf{X} = 4 + j2$ , find  $x(t)$

$$4.47 \cos(\omega t + 26.6^\circ)$$

**Practice problem:** If  $\mathbf{X} = 7.5\angle 31^\circ$ , find  $x(t)$

$$47.5 \cos(\omega t + 31^\circ)$$