

Phasors – 4

using phasors;
variation with frequency

Phasor Review

- Extend sinusoidal voltages/currents to phasors (complex)
- Convert components (R,L,C) to impedances
- Solve the problem using Ohm's Law, KVL/KCL, ...
- Convert back

$$V_s \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_s e^{j\phi}$$

$$I_s \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_s e^{j\phi}$$


$$Z = \begin{cases} R & \text{resistor} \\ j\omega L & \text{inductor} \\ \frac{1}{j\omega C} = -j \frac{1}{\omega C} & \text{capacitor} \end{cases}$$

$$B \angle \theta \Rightarrow B \cos(\omega t + \theta)$$

Common Usage


- Find the voltage $v(t)$
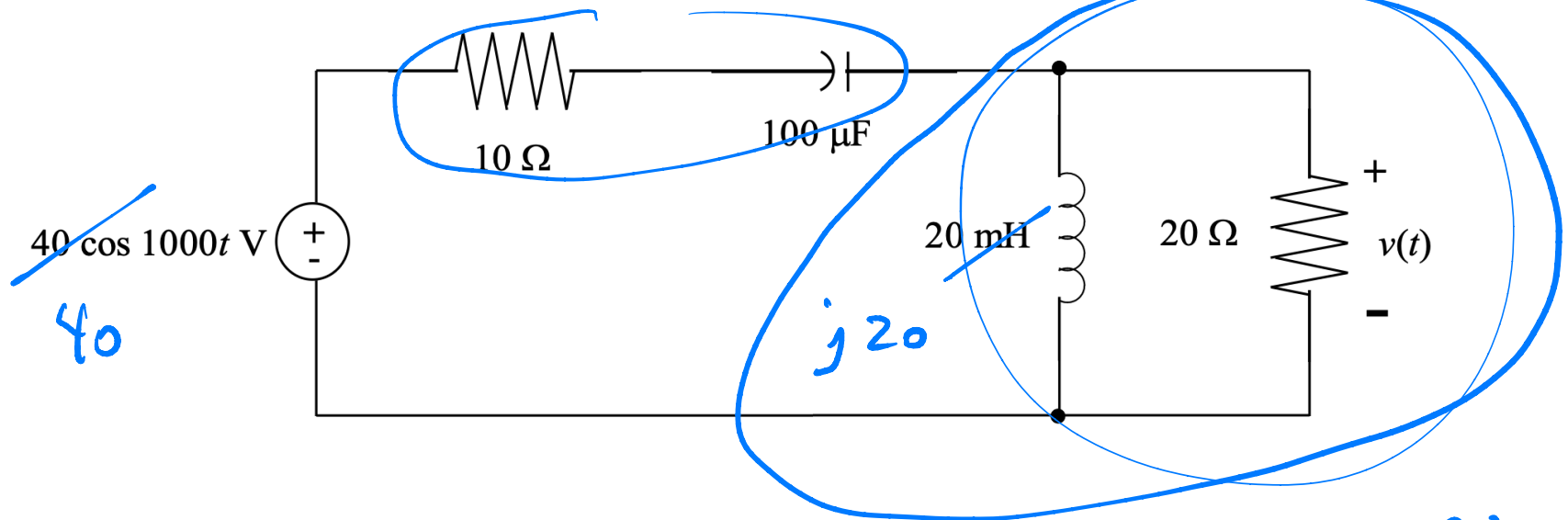
$$-j \frac{10^6}{1000 \cdot 10^6} = -j10$$




$$V = 40 \cdot \frac{2}{2 + 10 - j10}$$

$$\frac{20 \cdot j20}{20 + j20} = 2$$

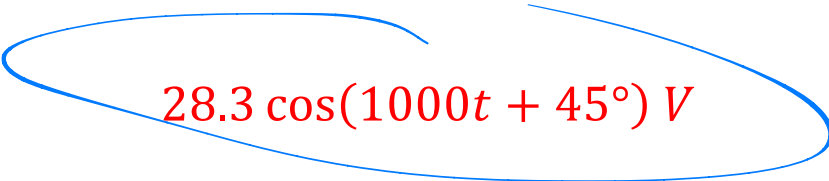
$$28.3 \cos(1000t + 45^\circ) \text{ V}$$

Consider Variation with Frequency

Consider voltage division:

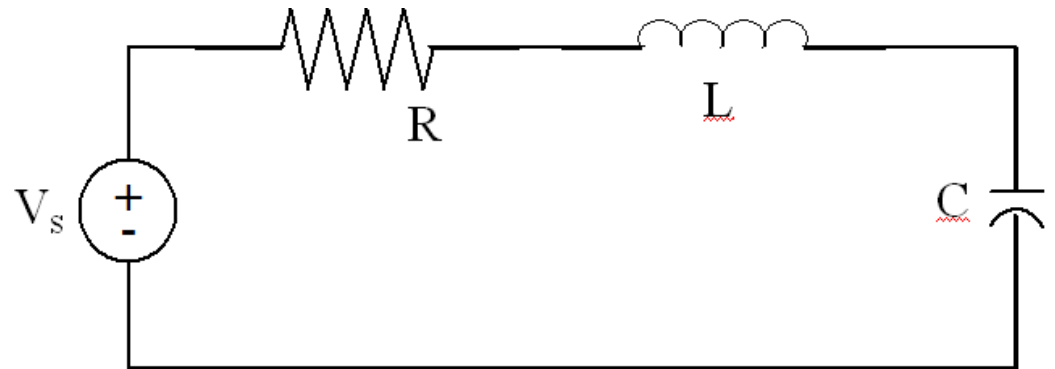




$$V_R = \frac{RV_s}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} V_s$$

Similarly


$$V_L = \frac{-\omega^2 LC}{1 - \omega^2 LC + j\omega RC} V_s$$

$$V_C = \frac{1}{1 - \omega^2 LC + j\omega RC} V_s$$

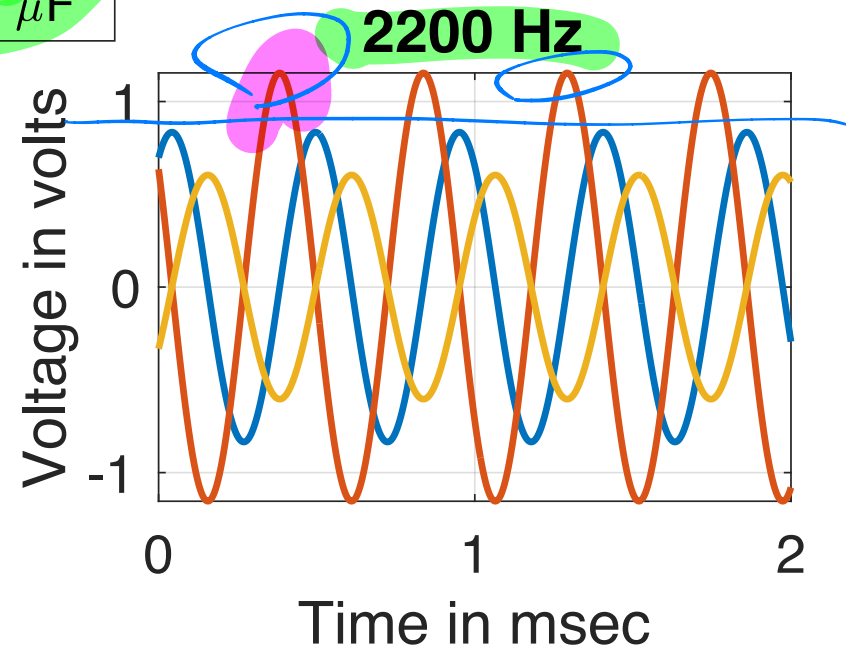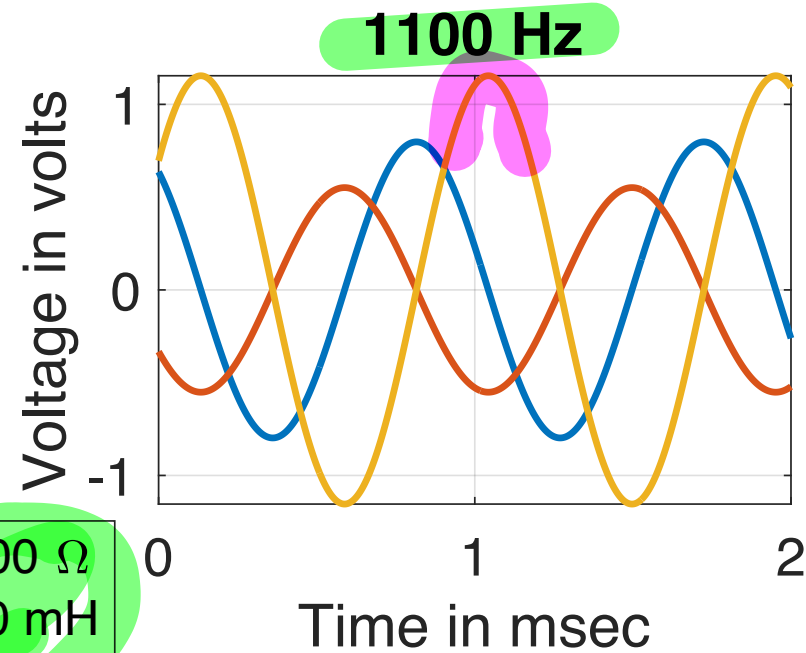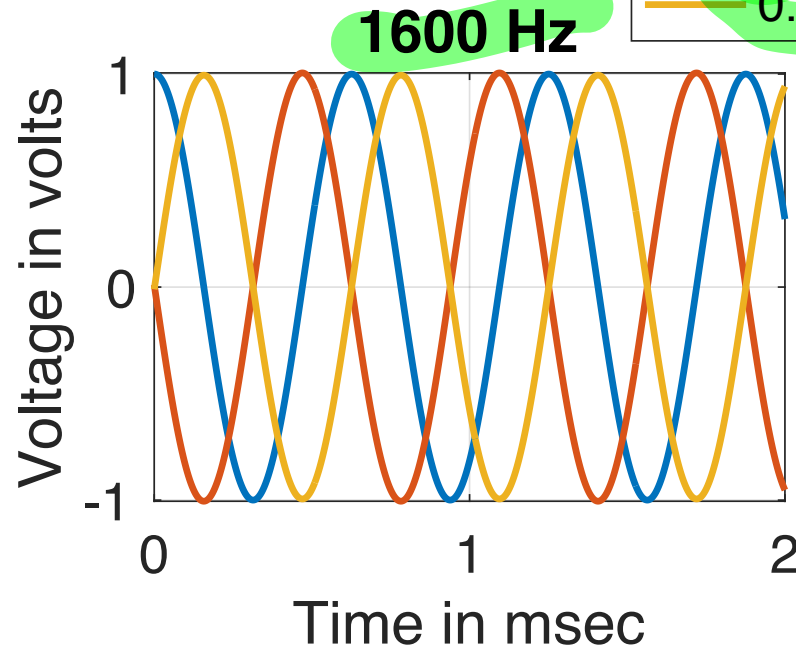- Comparison of the component voltages for different frequencies ($V_s = 1$)



Consider combined impedance variation

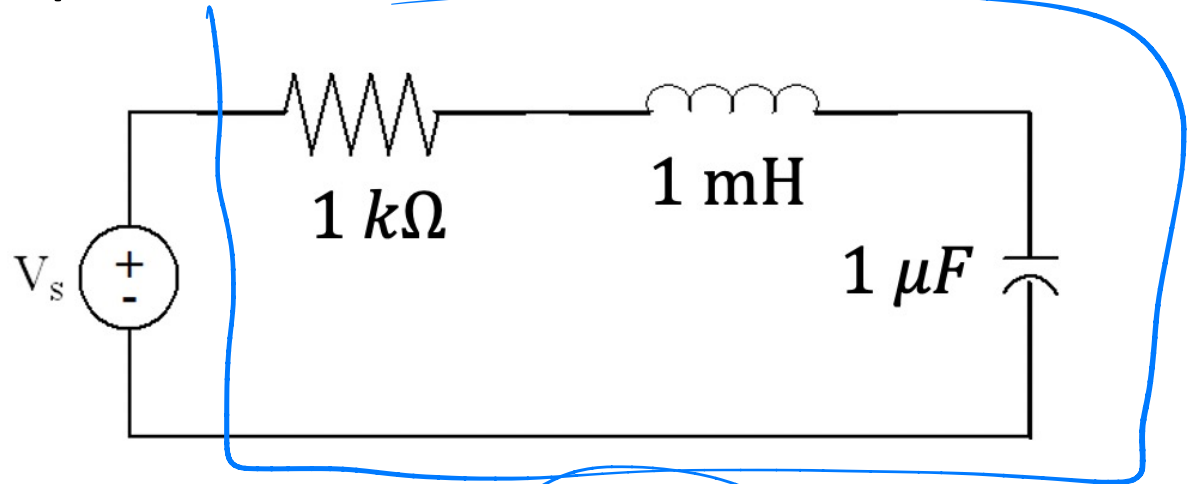


$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$
$$= 1000 + j\left(\frac{\omega}{1000} - \frac{10^6}{\omega}\right) = 0$$

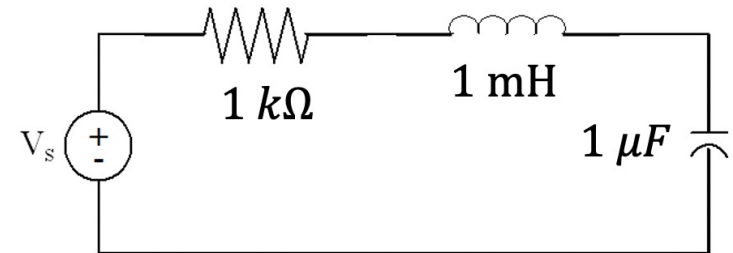Question – at what frequency does this “appear” purely resistive?

How might we graph impedance vs frequency?

$$Z = 1000 + j \left(\frac{\omega}{\underline{1000}} - \frac{10^6}{\omega} \right)$$




- Real/imag vs frequency?
- Real vs imag?

$$\frac{\omega}{1000} = \frac{10^6}{\omega}$$

$\omega = \sqrt{1000}$

$$80 + j40 \Omega$$

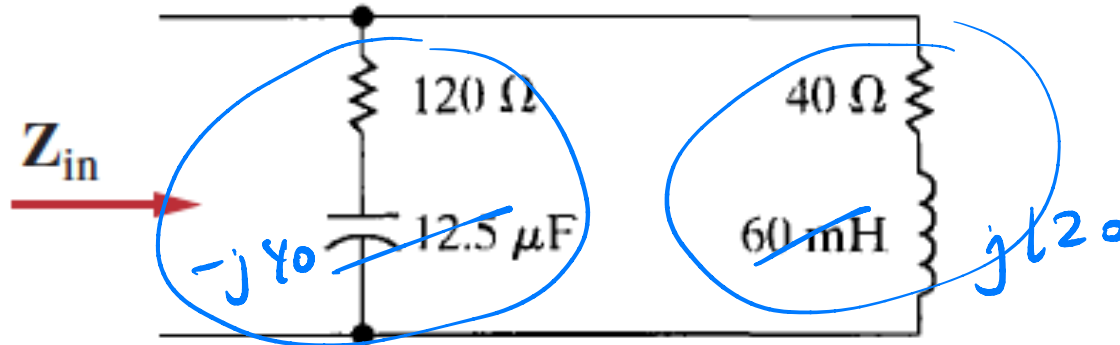Example: find Z_{in} if $\omega = 2000$ rad/sec



$$\text{ind } j\omega L$$

$$= j 2000 \cdot \frac{60}{1000}$$

$$-j \frac{1}{\omega C} = j \frac{10^6}{2000 \cdot 12.5}$$

2500

$$120 - j40$$

$$40 + j120$$


$$= -j40$$

$$Z_{in} = \frac{(120 - j40)(40 + j120)}{120 - j40 + 40 + j120}$$

$$= \frac{40(3 - j)40(1 + 3j)}{160 + j80} =$$

$$\frac{40^2 (6 + 8j)(4 - j2)}{40(4 + j2)4j2}$$

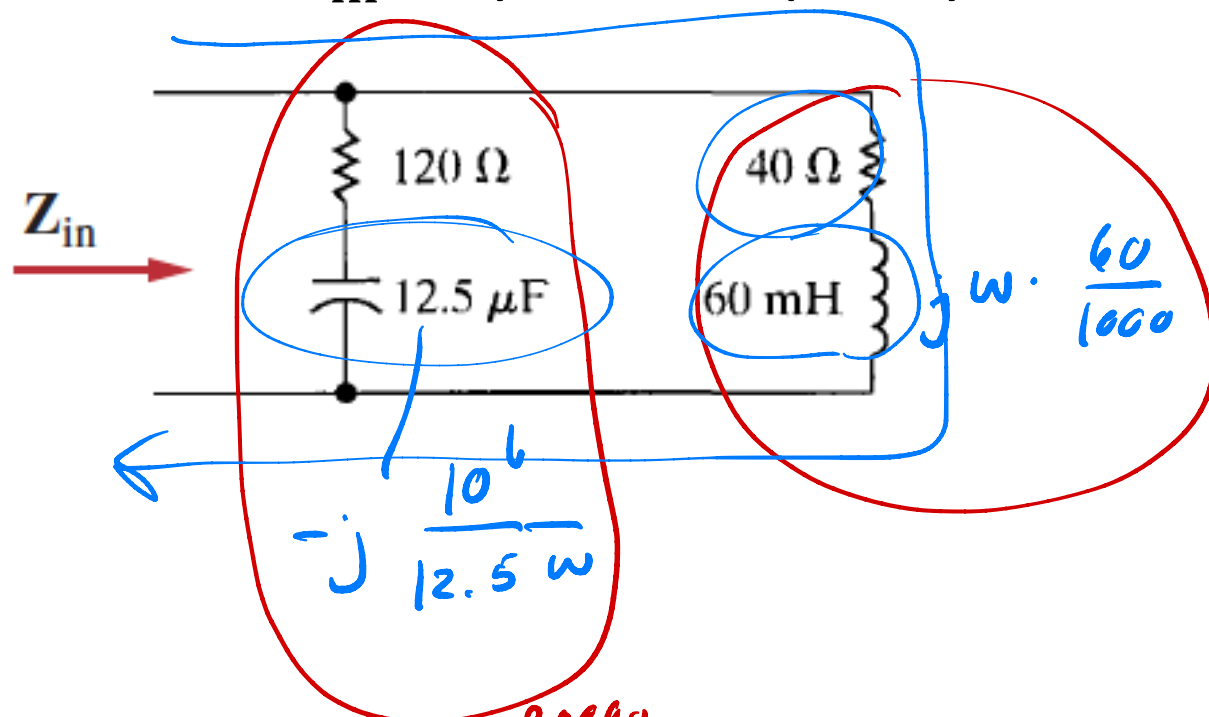How does Z_{in} vary with frequency? Is it ever purely real?



$$40 + j \frac{6\omega}{100}$$

$$120 - j \frac{80,000}{\omega}$$

$$Z_{in} = \frac{(120 - j \frac{80,000}{\omega})(40 + j \frac{6\omega}{100})}{160 + j(\frac{6\omega}{100} - \frac{80000}{\omega})}$$

$$100\ \omega$$

$$\frac{100\ \omega}{100\ \omega}$$

$$\left(120\omega - j \frac{80,000}{\omega}\right) \left(40 + j \frac{6\omega}{100}\right)$$



$$100\omega$$

$$160 + j \left(\frac{6\omega\omega}{100} - \frac{8000\omega^2}{\omega} \right)$$


$$100\omega$$

$$\frac{(120\omega - j 80,000)(40 + j 6\omega)}{1600\omega - j(6\omega^2 - 8 \cdot 10^5)}$$

How do these vary with frequency?

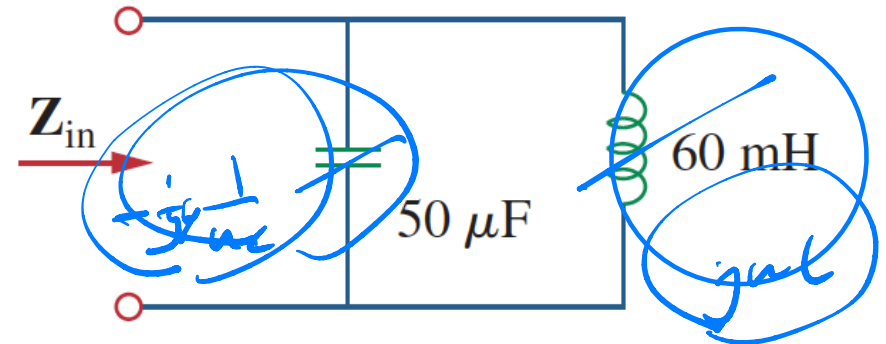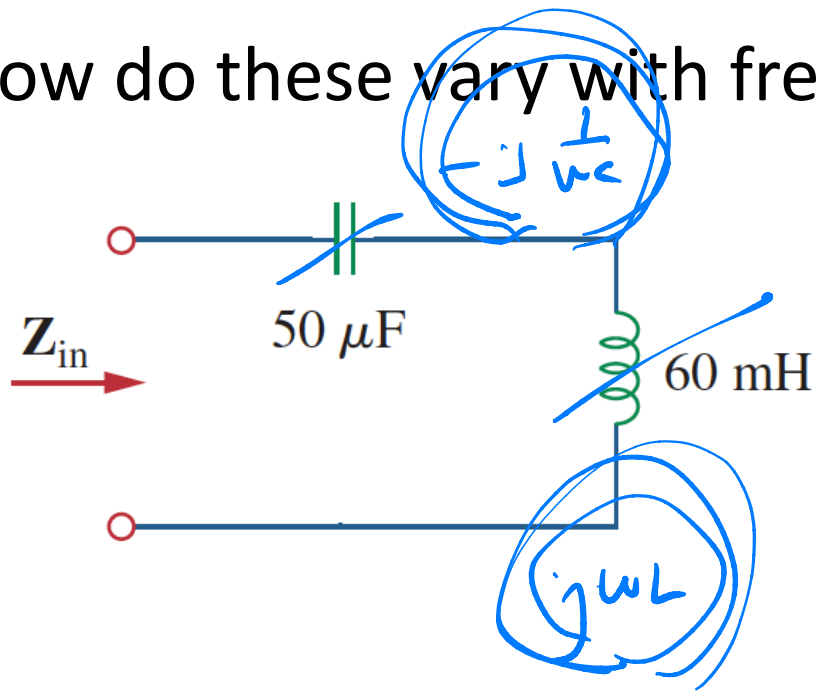


- **Example:** find $i(t)$

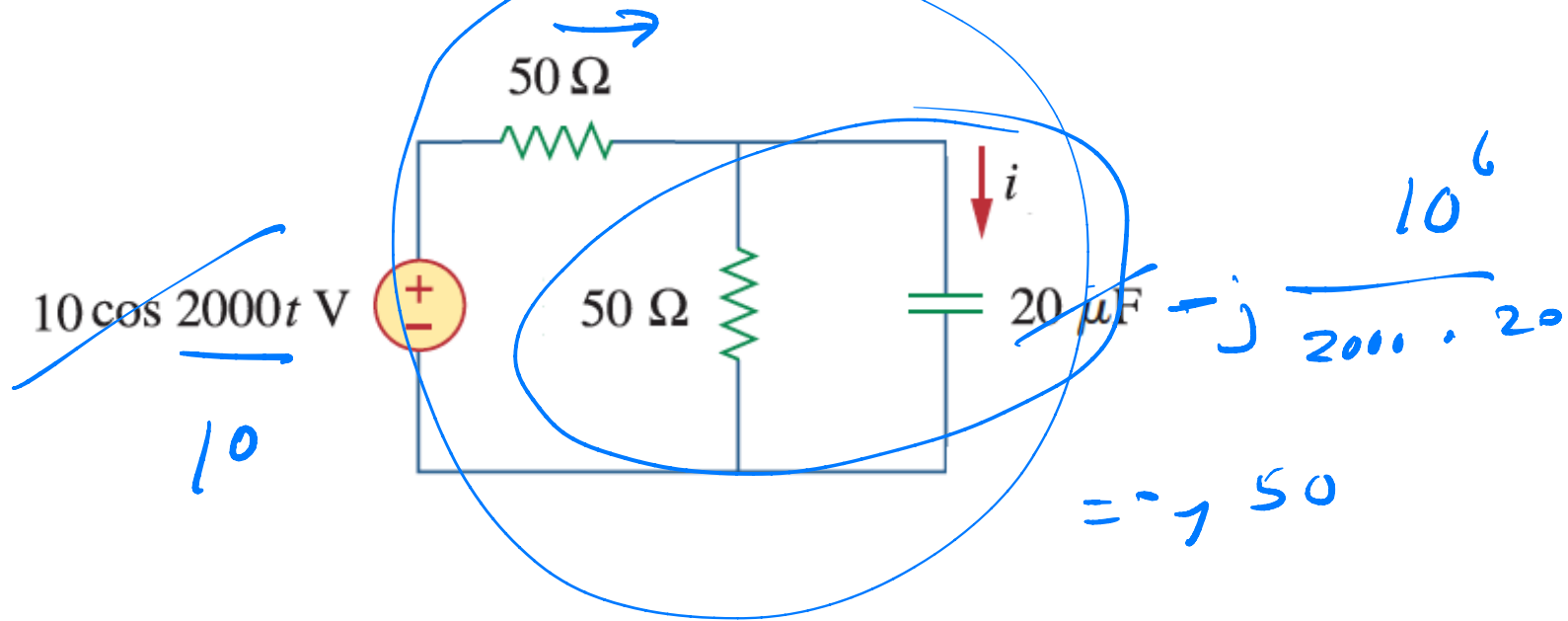

$$141 \cos(2000t + 45^\circ) \text{ mA}$$

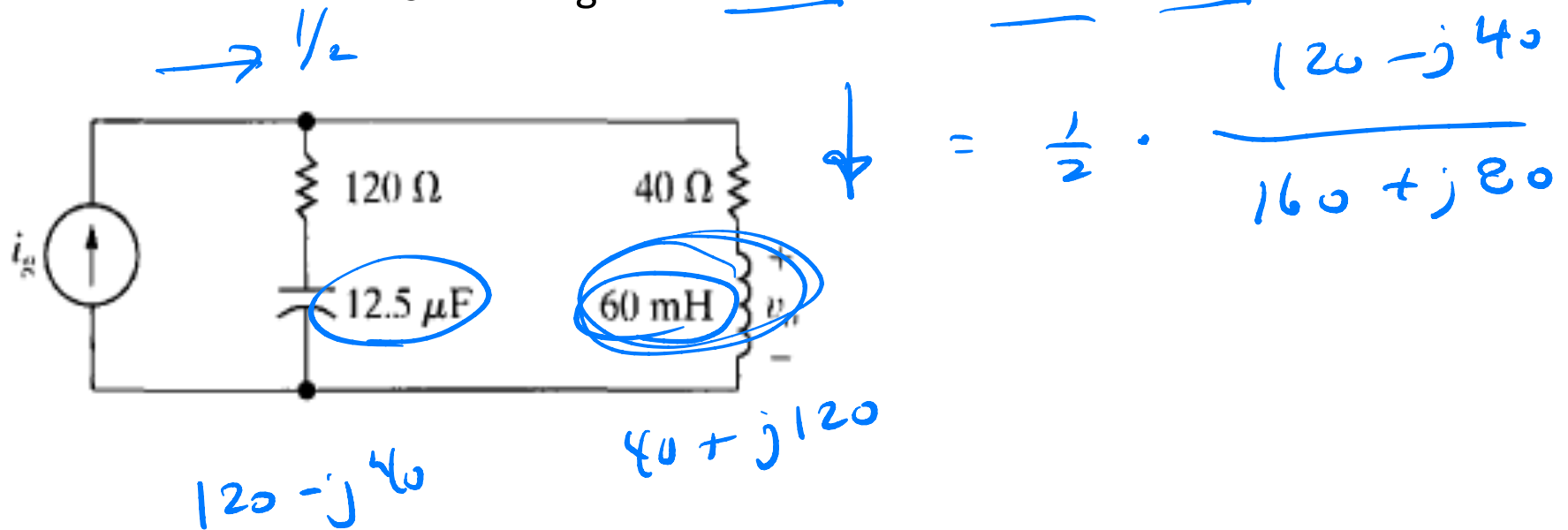
Example: find $v_o(t)$ if $i_g(t) = \underline{500} \cos \underline{2000 t} \text{ mA}$



$$1.59 \cos(2000t - 17.0^\circ) \text{ V}$$

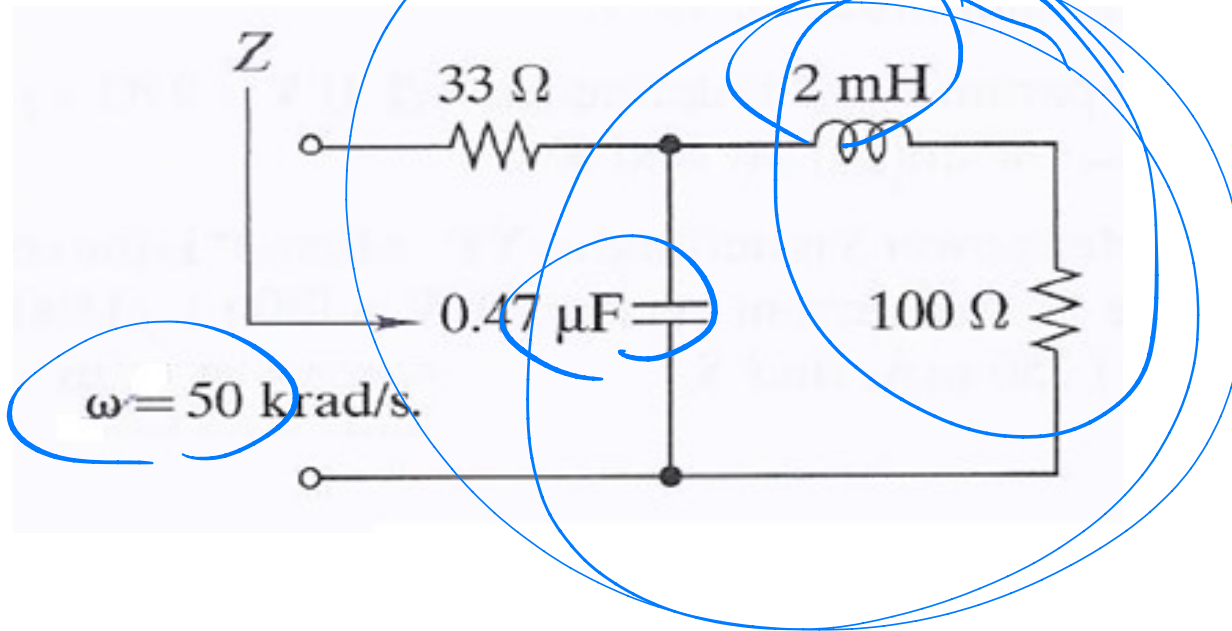
Example: find Z

$$46.4 - j50.4;$$
$$\underline{46.4\ \Omega} \quad \underline{0.397\ \mu F}$$




Practice problem: find Z

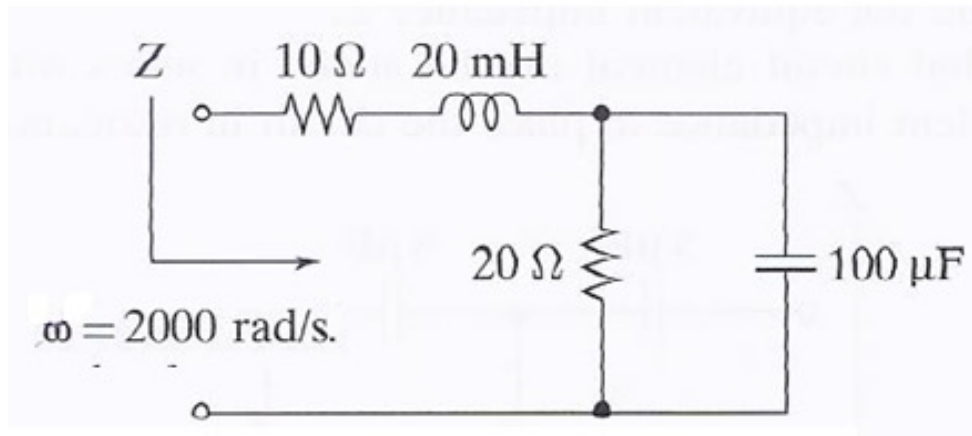$11.2 + j35.3$;
 $11.2\ \Omega\ 17.6\text{ mH}$



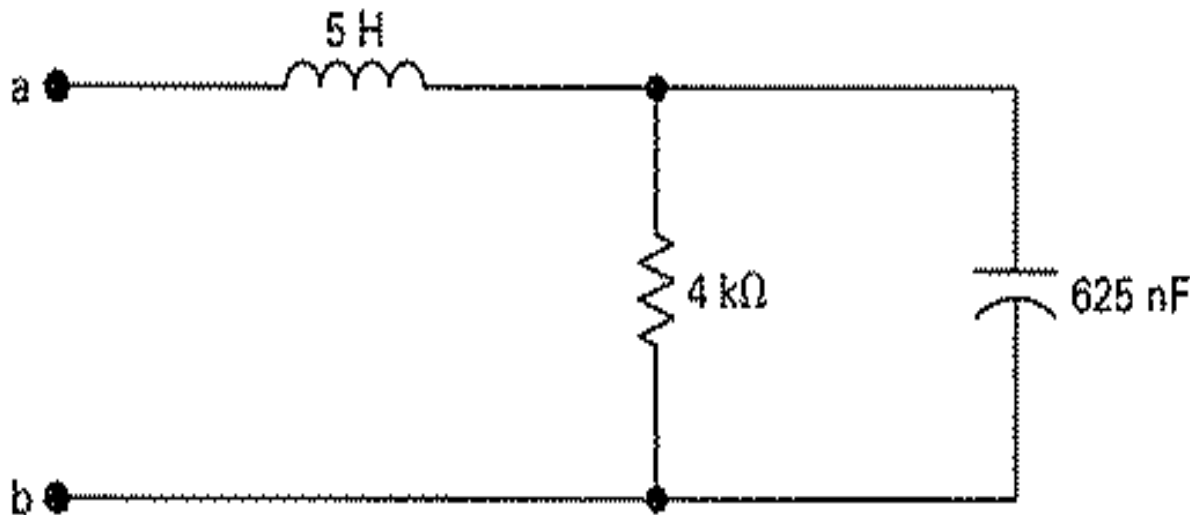Practice problem: at what frequency does this circuit seem purely resistive? What is the resistance?



$$400 \frac{\text{rad}}{\text{sec}}; 2 \text{ k}\Omega$$

- **Practice problem:** consider the parallel connection of a $220\ \Omega$ resistor, a $0.5\ \mu\text{F}$ capacitor, and a $5\ \text{mH}$ inductor.
 - What is the equivalent impedance of this circuit at $1000\ \text{Hz}$?
 - At $5000\ \text{Hz}$?
 - At what frequency is the impedance purely real?

$11.6 + j49.2\ \Omega$; $1.42 - j17.6\ \Omega$; $1.59\ \text{kHz}$

Practice problem: Find the time expression for $v_o(t)$.

Note that $\sin \omega t = \cos(\omega t - 90^\circ)$

$17.1 \cos 200t \text{ V}$

