

Phasors – 5

examples


What Now?

- Have used seen that voltage division, series and parallel impedance, and simple analysis all work with phasors
- Let's practice analysis methods
 - Node analysis
 - Dependent sources
 - Super nodes
 - ...

$$I = \frac{A}{-j5}$$

Example: Find the current $i(t)$.

$$\omega = 2$$

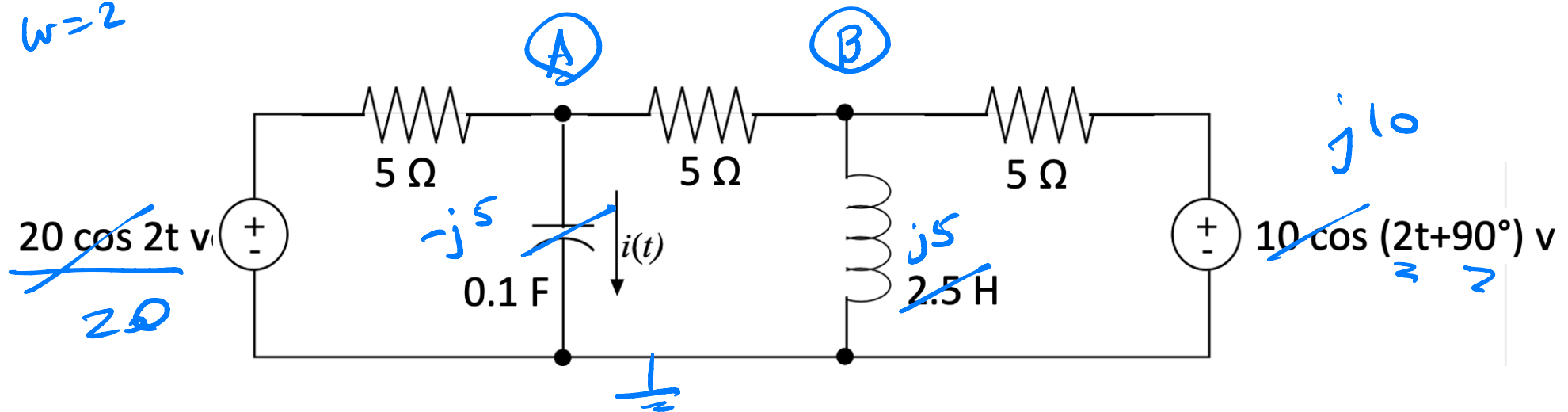

1- convert

2- node analysis

$$\frac{A - 20}{5} + \frac{A - B}{5} + \frac{A}{-j5} = 0$$

$$\frac{B - A}{5} + \frac{B}{j5} + \frac{B - j10}{5} = 0$$

3- solve


$$A = 10 - j2.5$$

$$I = \frac{10 - j2.5}{-j5}$$

$$I = \frac{10 \angle 2.5^\circ}{-j5} = j \left(\frac{10}{5} - j \frac{2.5}{5} \right)$$

$$= 2j + \frac{1}{2} = \frac{1}{2} + j2$$


$$= 2.2 \angle 76^\circ$$

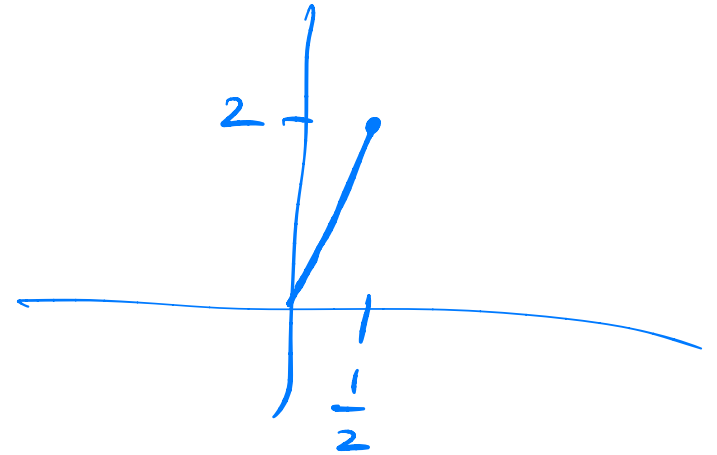

$$2.06 \cos(2t + 76^\circ) \text{ A}$$

~~$$1.12 \cos(2t + 153^\circ) \text{ A}$$~~

Example: Find V

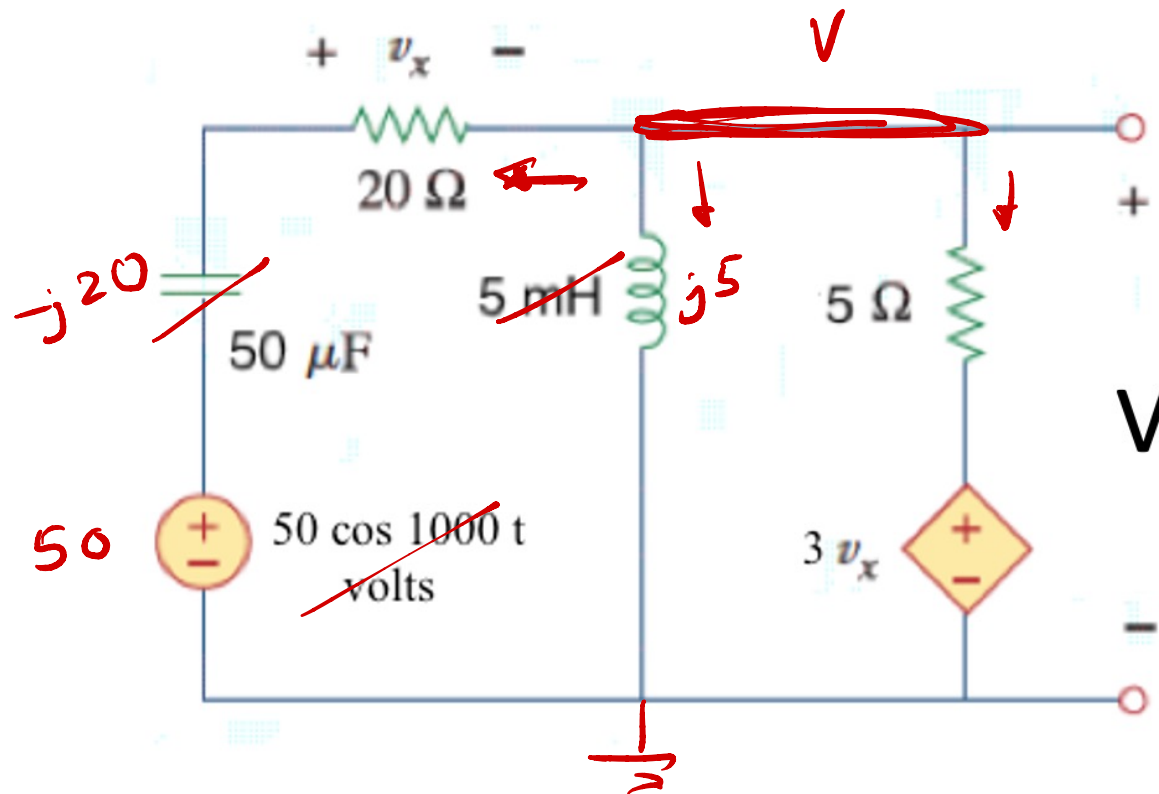

1- convert

$$j\omega L = j \cdot 1000 \cdot \frac{5}{1000}$$

$$\frac{1}{j\omega C} = -j \frac{10^6}{1000} \text{ } \Omega$$

$$= -j \frac{1000}{50}$$

2- node

$$\frac{V - 50}{20 - j20} + \frac{V}{j5} + \frac{V - 3v_x}{5} = 0$$

$$v_x = \frac{50 - V}{20 - j20} \cdot 20$$

$$\frac{V - 50}{20 - j20}$$

$$+ \frac{V}{j5}$$

$$+ \frac{V - 3V_X}{5} = 0$$

$$V_X =$$

$$\frac{50 - V}{20 - j20} \cdot \cancel{20} \frac{(1+j)}{1+j}$$

$$1 - j$$

$$= \frac{50 - V + 50j - jV}{2}$$

$$\frac{V - 50}{20 - j20}$$

$$+ \frac{V}{j5}$$

$$+ \frac{V}{5} - \frac{3}{5}$$

$$\frac{50 - 50j - V(1+j)}{2} = 0$$

$$42.6 \cos(1000t + 31.6^\circ) \text{ V}$$

$$\frac{\cancel{V-50}}{20-j20} + \frac{\cancel{V}}{j5} + \frac{\cancel{V}}{5} - \frac{\cancel{3}}{5} \frac{50-50j \boxed{-V(1+j)}}{2} = 0$$

$$V \left(\frac{1}{20-j20} + \frac{1}{j5} + \frac{1}{5} + \frac{(1+j)^3}{10} \right) = \frac{50}{20-j20} + \frac{3}{5} \cdot \frac{50-50j}{2}$$

$$V = \frac{50}{20-j20} + \frac{3}{5} \cdot \frac{50-50j}{2}$$

$$\frac{20(1-j)}{20(1-j)} = 1$$

$$\cancel{\frac{1}{20-j20}} + \cancel{\frac{1}{j5}} + \cancel{\frac{1}{5}} + \frac{(1+j)^3}{10}$$

$$22.6 \cos(1000t + 31.6^\circ) \text{ V}$$


5.24

300

$$V = \frac{50 + \underbrace{2(1-j)}_{300} \underbrace{3 \cdot 50(1-j)}_{300}}{1 - j \underbrace{4(1-j)}_{300} + \underbrace{4(1-j)}_{300} + \underbrace{2(1-j)^3(1+j)}_{300}}$$

$$= \frac{50 - 600j}{13 - 8j} = \frac{610 \angle -80^\circ}{15 \angle -30^\circ} \quad ?$$

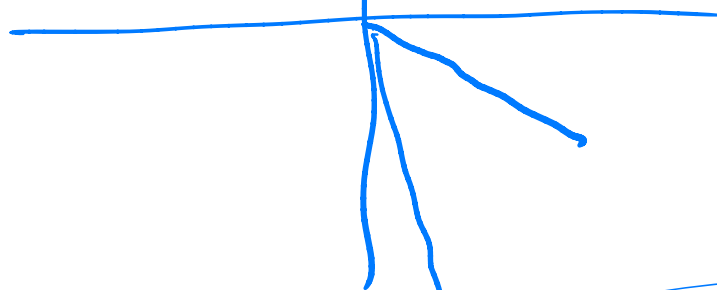
$$\begin{aligned} (1-j)(1-j) &= 1 - j - j + j^2 \\ &= 1 - 2j - 1 \\ &= -2j \end{aligned}$$



~~40.6~~ $40.6 \cos(1000t + 31.6^\circ) \text{ V}$

$$I_o = \frac{A}{100 + j80}$$

Example: Find i_o

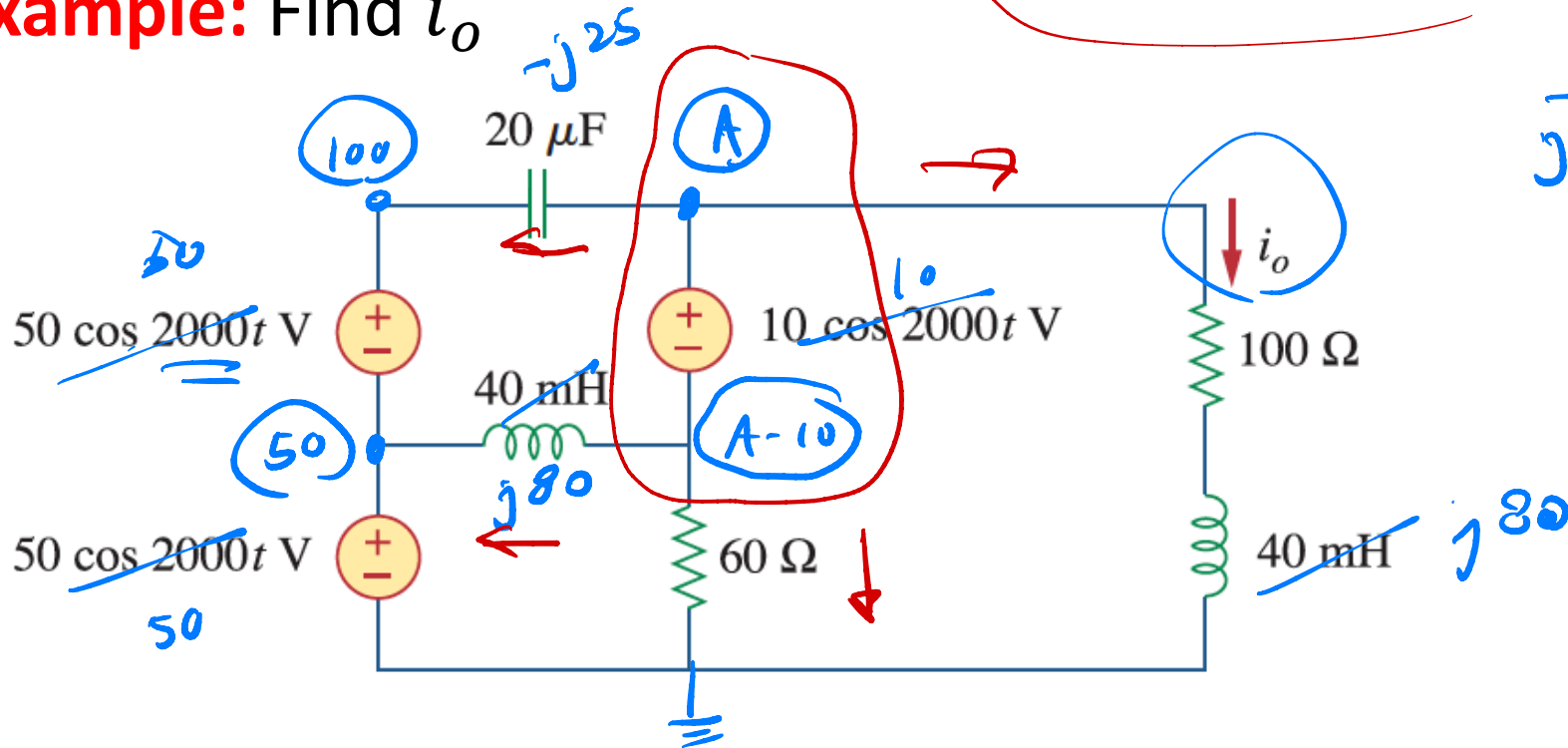


$$\frac{1}{j\omega C} = \frac{-j10^6}{2000} = -j50$$

2- superim. eq:

$$0 = \frac{A - 100}{-j25} + \frac{A - 10 - 50}{j80} + \frac{A - 10}{60} + \frac{A}{100 + j80}$$


3- solve --

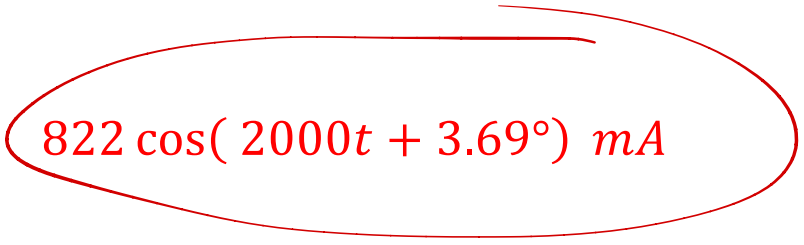
$$822 \cos(2000t + 3.69^\circ) \text{ mA}$$

Example: Find $v(t)$

1. convert

$$-j \frac{1}{100 \cdot 0.002}$$

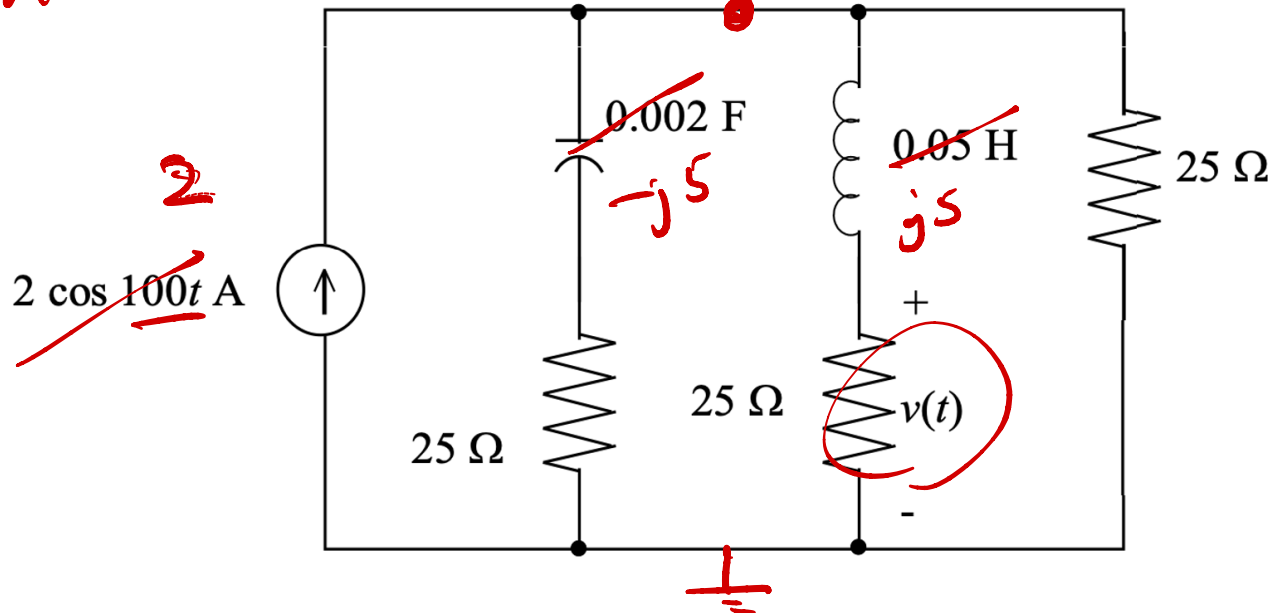

$$V = A \cdot \frac{25}{25 + j5}$$


2. nodal

$$\left(\frac{A}{25 - j5} + \frac{A}{25 + j5} + \frac{A}{25} = 2 \right) 25$$

$$\frac{A}{1 - j} + \frac{A}{1 + j} + A = 50$$


$$16.8 \cos(100t - 11.3^\circ) \text{ V}$$

Example: find $v(t)$ – try node analysis

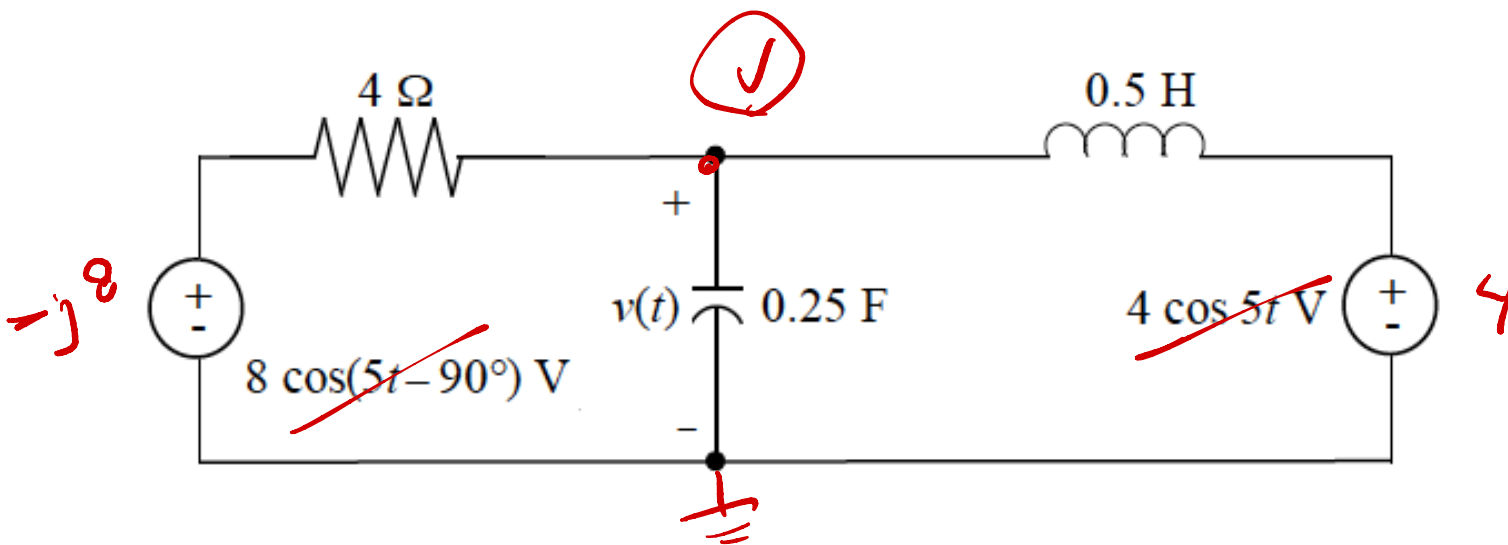

$$4.06 \cos(5t - 164^\circ) \text{ V}$$

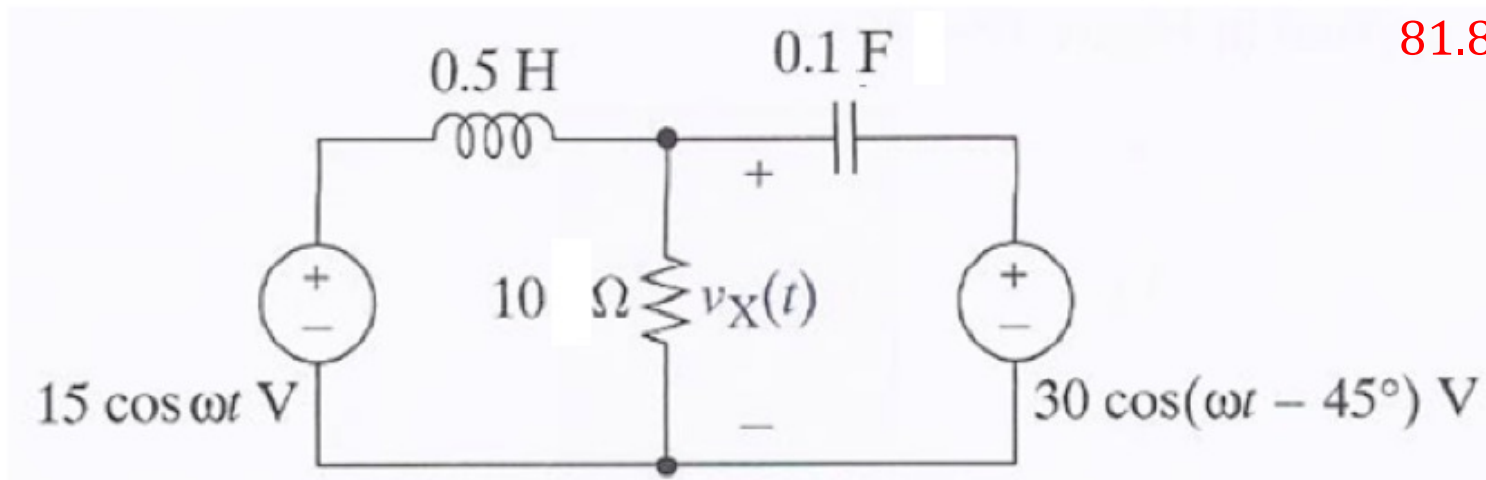
Practice problem: find $v(t)$ with $\omega = 5$ rad/sec



$$81.8 \cos(5t + 112^\circ) \text{ V}$$


Practice problem: find $v_X(t)$
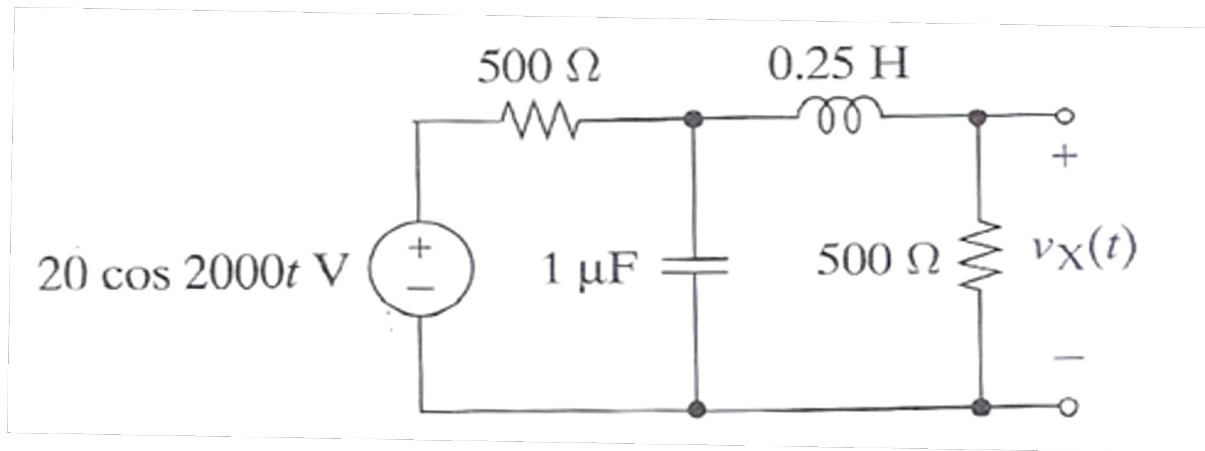
$$6.67 \cos(2000t - 90^\circ) \text{ V}$$




Practice problem: find $v(t)$
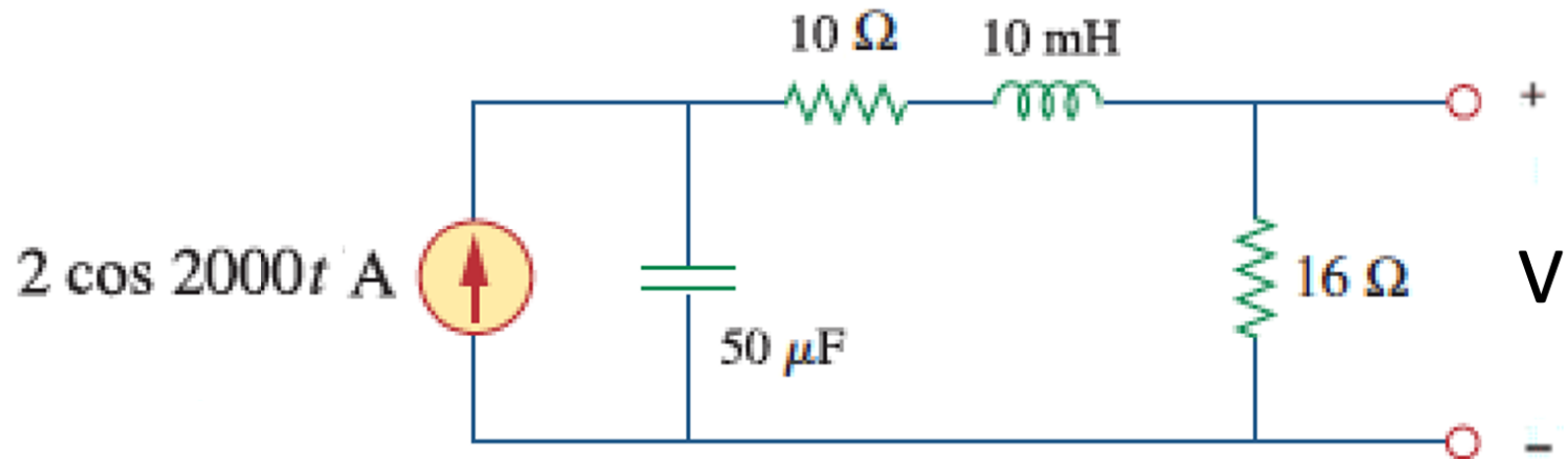
$$13.8 \cos(2000t - 115^\circ) \text{ V}$$




Practice problem: find $v(t)$
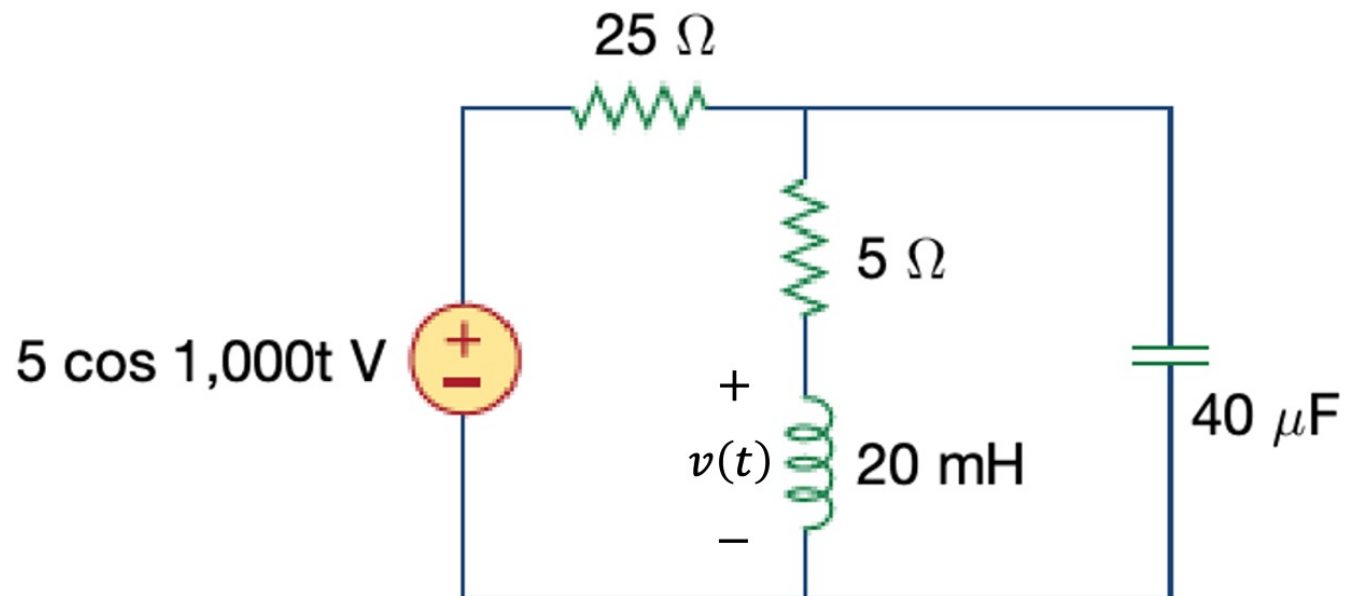
$$3.71 \cos(1000t + 21.8^\circ) \text{ V}$$



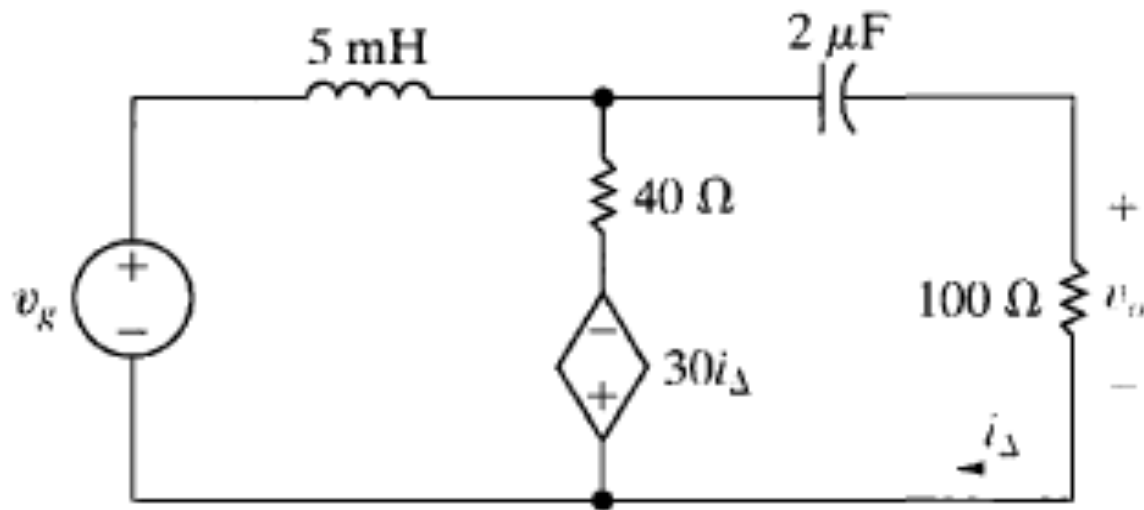Example: find $v(t)$ if $v_g(t) = 130 \cos 10,000 t$ V,
f



$$73.2 \cos(10,000t - 67.5^\circ) \text{ V}$$