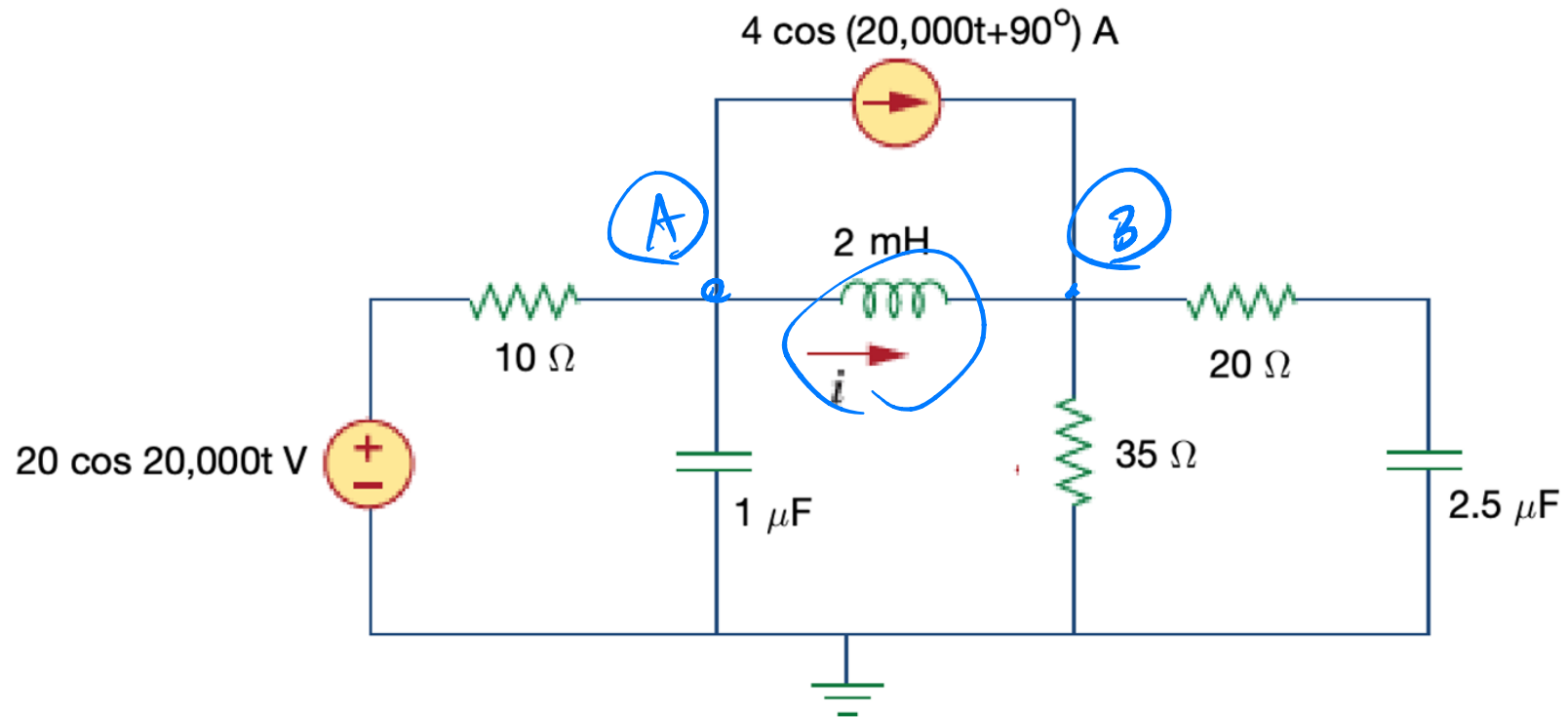


Phasors 6

more examples

Where Are We?


- What we know how to solve: find $i(t)$:



$$1.91 \cos(20,000t - 123^\circ) \text{ A}$$

Other Question Types

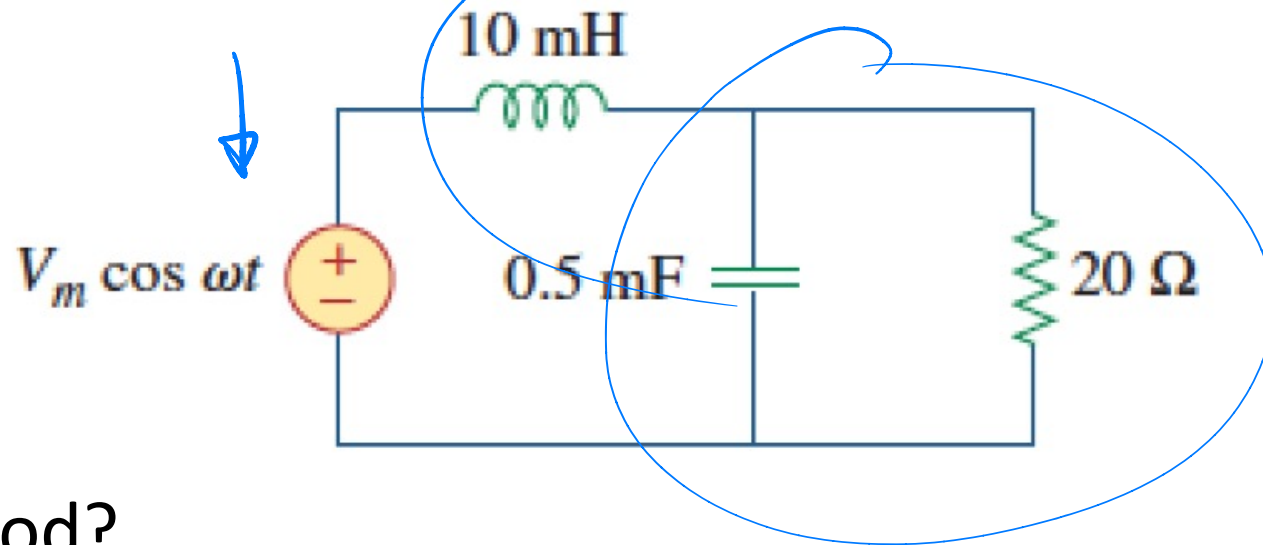
Sample: for what frequency is the source current the largest?



– Method?

- Numerical calculation
- Analysis

$$I = \frac{V_m}{Z}$$

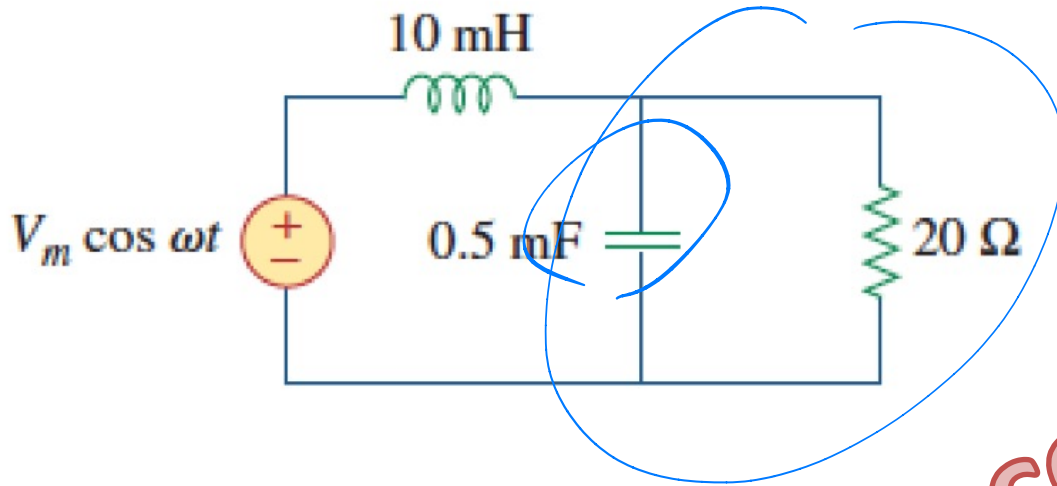


Idea 1 – compute it

```


om = logspace(0,6,500);
ZC = 1./(1j*om*0.5e-3);
ZP = 20*ZC./(20+ZC);
I0 = 1./(1j*om*10e-3+ZP);
semilogx(om,(abs(I0)), 'linewidth', 3)

```

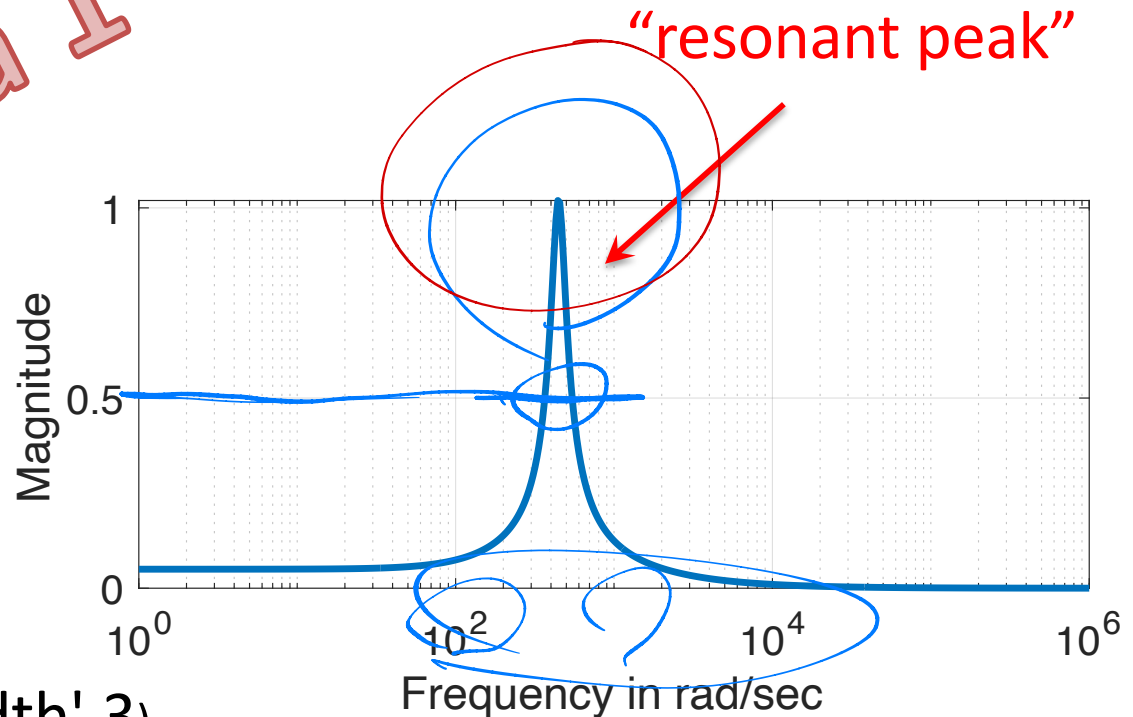

$$j\omega \frac{10}{1000} = j\frac{\omega}{100}$$

$$|I_f| \left| \frac{V_m}{2} \right| = \frac{|V_m|}{|Z|}$$

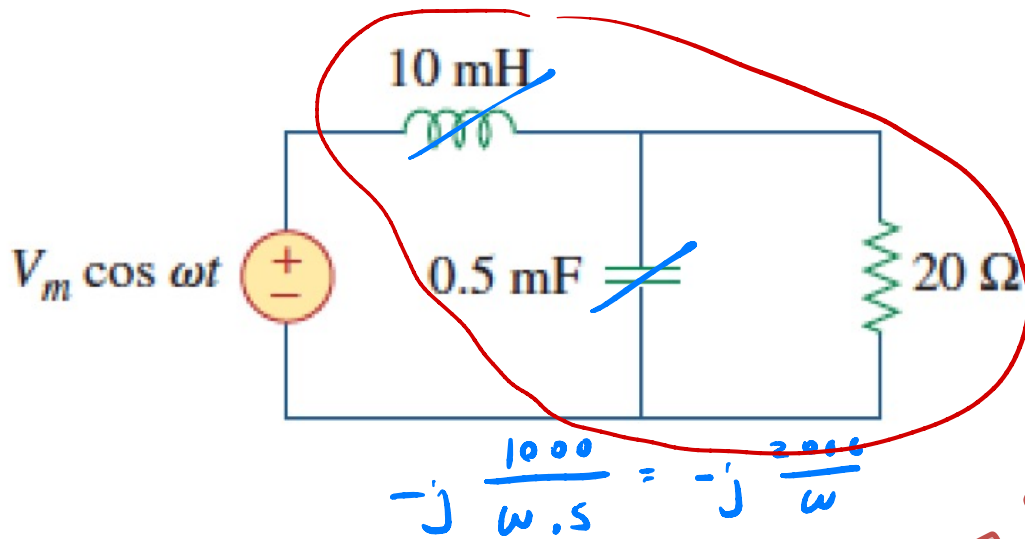

Idea 2 - analyze it

$$Z_p = \frac{(20) \left(-j \frac{2000}{\omega} \right)}{20 - j \frac{2000}{\omega}} \cdot \frac{\omega}{\omega} = \frac{-j 40,000}{20\omega - j 2000} = \frac{-j 2000}{\omega - j 100}$$

$$|Z| = \left| j \frac{\omega}{100} + \frac{-j 2000}{\omega - j 100} \frac{\omega + j 100}{\omega + j 100} \right| = \left| j \frac{\omega}{100} + \frac{2 \cdot 10^5}{\omega^2 + 10^4} + \frac{-j 2000 \omega}{\omega^2 + 10^4} \right|$$

$$= \left| \frac{2 \cdot 10^5}{\omega^2 + 10^4} + j \left(\frac{\omega}{100} - \frac{2000 \omega}{\omega^2 + 10^4} \right) \right|$$

$$\min_w \left| \frac{2 \cdot 10^5}{w^2 + 10^4} + j \left(\frac{w}{100} - \frac{2000w}{w^2 + 10^4} \right) \right|$$

$$\Rightarrow \min_w \sqrt{\left(\frac{2 \cdot 10^5}{w^2 + 10^4} \right)^2 + \left(\frac{w}{100} - \frac{j 6000w}{w^2 + 10^4} \right)^2}$$

$$\Rightarrow \min_w \left(\quad \right)^2 + \left(\quad \right)^2$$

```
>> syms w real
>> zc = 1/(1j*w*5e-4)
```

zc =

$-2000i/w$

```
>> zp = 20*zc/(20+zc)
```


zp =

$40000i/(w*(2000i/w - 20))$

```
>> z = 1j*w*1e-2 + zp
```


z =

$(w*1i)/100 + 40000i/(w*(2000i/w - 20))$

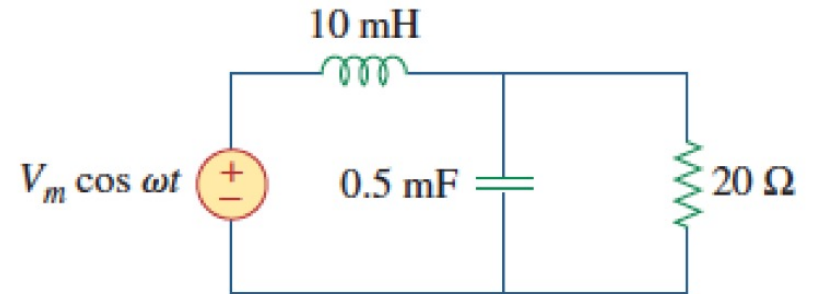

Or use a tool
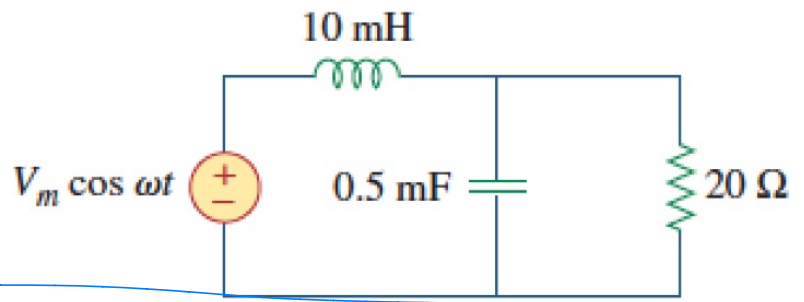
```
>> H = 1/z;
>> aH = sqrt( real(H)^2 + imag(H)^2 );
>> pretty(aH)
```



$$\sqrt{\frac{800000}{100} + \frac{4000000}{w^2} + 400} + \frac{6400000000000000}{4 \sqrt{\frac{4000000}{w^2} + 400}}$$

where

$$\#1 = \frac{6400000000000000}{4 \sqrt{\frac{4000000}{w^2} + 400}} + \frac{800000}{100 \sqrt{\frac{4000000}{w^2} + 400}}$$


```
>> daH = diff(aH,w);  
>> solve(daH,w)
```



ans =

```
(20000*110^(1/2) - 10000)^(1/2)  
-(20000*110^(1/2) - 10000)^(1/2)
```


```
>> eval(ans(1))
```

ans =

```
446.9472
```

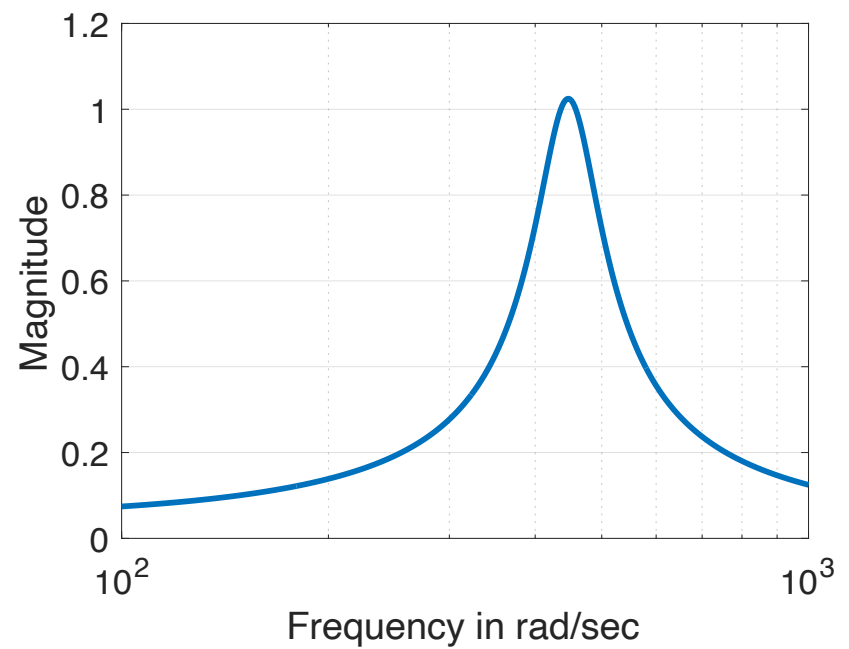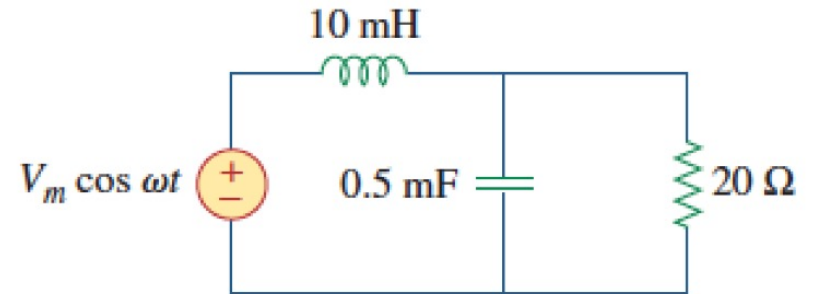

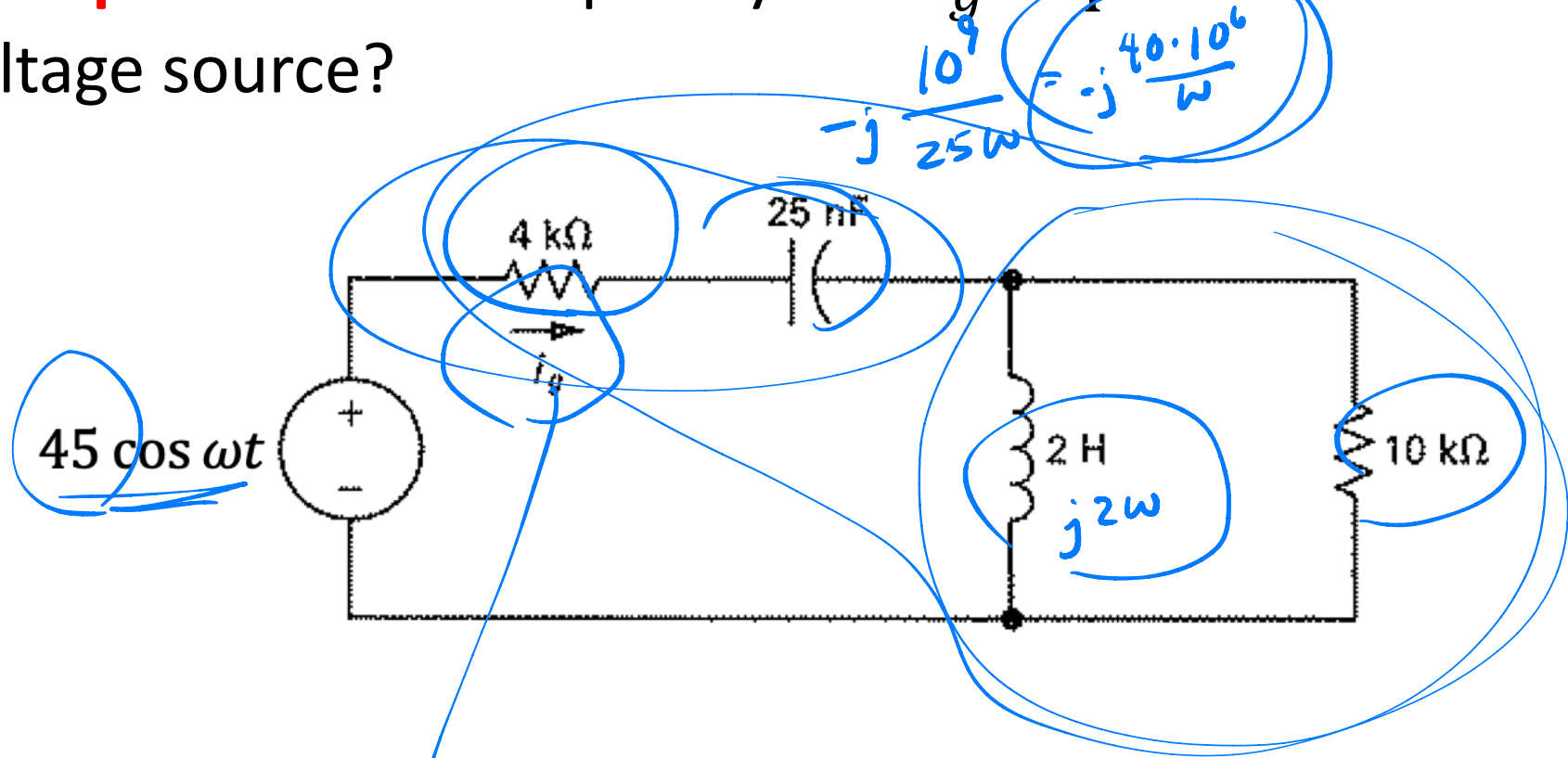Example: At what frequency ω is i_g in phase with the voltage source?



$A \cos \omega t$

$I = \frac{45}{Z}$

$Z = (j\omega L \parallel 10k) + 4k + \frac{1}{j\omega C}$

10^4 rad/sec

$$Z_p = \frac{10^4 \cdot j2\omega}{10^4 + j2\omega}$$

$$Z = \frac{10^4 \cdot j2\omega}{10^4 + j2\omega} + 4000 + j \frac{40 \cdot 10^6}{\omega}$$

10^4 rad/sec

$$I = \frac{45}{Z}$$


$Z \text{ real}$

$$\frac{10^4 j2\omega (10^4 - j2\omega)}{(10^4 + j2\omega)(10^4 - j2\omega)}$$

$$\frac{2 \cdot 10^8 \omega}{10^8 + 4\omega^2} = \frac{40 \cdot 10^6}{\omega}$$

$$2 \cdot 10^8 \omega^2 = 40 \cdot 10^6 (10^8 + 4\omega^2)$$

Example: We model a real inductor as shown with a series parasitic resistance R_L . To measure its parameters, R_L and L , we build the circuit shown (with a 60 Hz source) and use an AC voltmeter to measure the amplitudes of the component voltages. Given $|V_S| = 120\text{ V}$, $|V_R| = 100\text{ V}$, $|V_L| = 30$, find R_L and L .

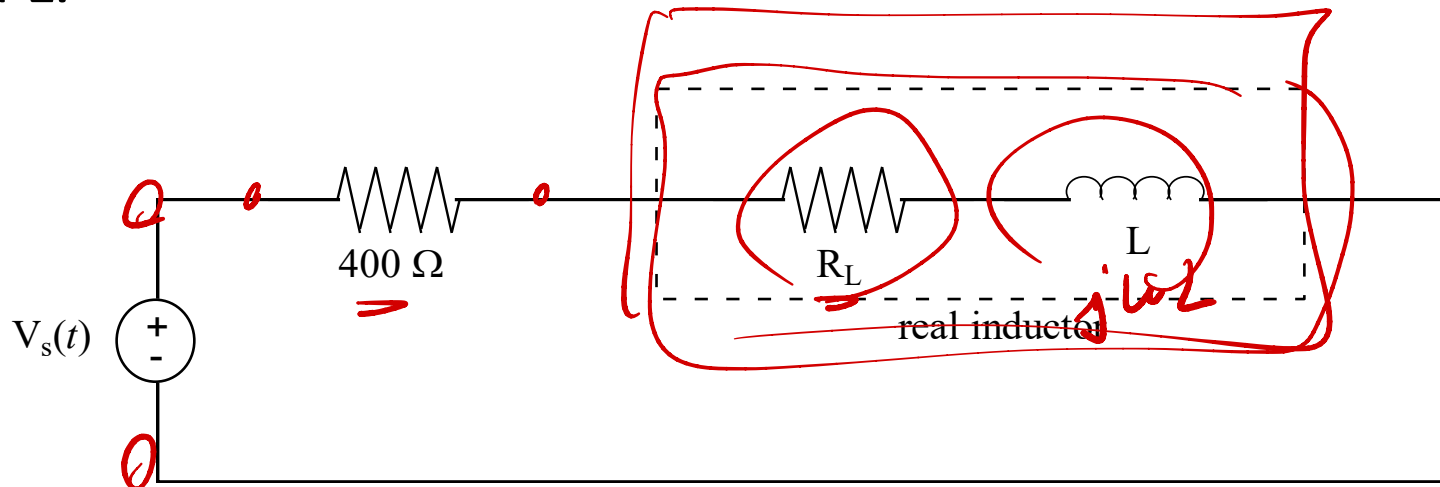

$$|V_R| = \left| \frac{120 \angle \phi \cdot 400}{400 + R_L + j\omega L} \right| = 100$$

$$|V_L| = \left| \frac{120 \angle \phi \cdot (R_L + j\omega L)}{400 + R_L + j\omega L} \right| = 30$$

$$\omega = 2\pi \cdot 60$$

$$\left| \frac{120 \angle \phi \cdot 400}{400 + R_L + j\omega L} \right| = 100$$

$$\left| \frac{120 \angle \phi \cdot (R_L + j\omega L)}{400 + R_L + j\omega L} \right| = 30$$


$$\frac{120 \cdot 400}{\sqrt{(400 + R_L)^2 + \omega^2 L^2}} = 100$$

$$\frac{120 \cdot \sqrt{R_L^2 + \omega^2 L^2}}{\sqrt{(400 + R_L)^2 + \omega^2 L^2}} = 30$$

70 Ω , 259 mH

$$\omega = 2\pi \cdot 60$$

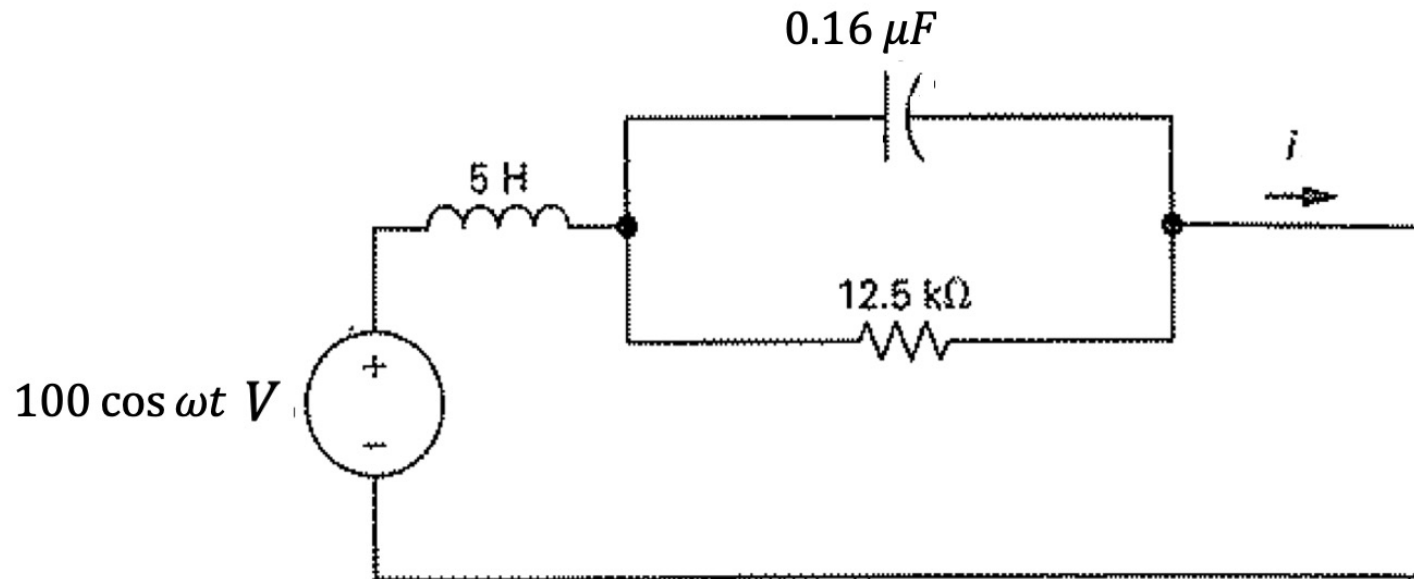Practice problem: At what frequency does the current i have the largest magnitude? What is that magnitude?



$$1120 \frac{\text{rad}}{\text{sec}}; 43.8 \text{ mA}$$