

Phasors – 8

more AC power; start design


Improving AC Power Delivery

- Real average power is

$$P = \frac{VI}{2} \cos \theta = V_{RMS} I_{RMS} \cos \theta$$

- The goal is to get θ close to 0 (equivalently, S close to real
 - Load close to resistive


A Typical Example – Power Distribution

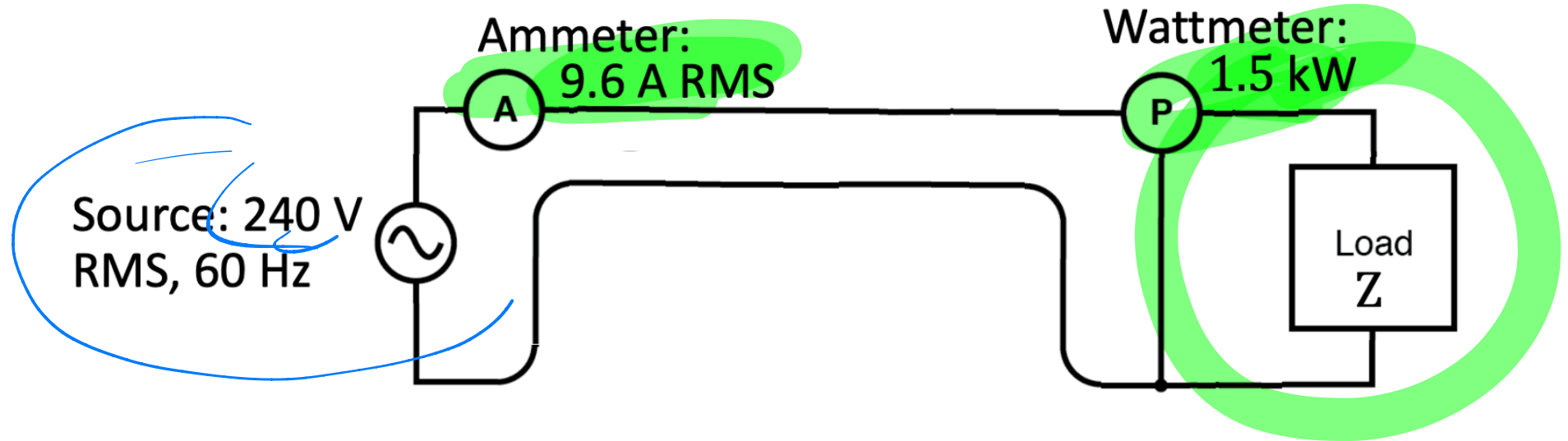

- Load Apparent power is

$$P = V_{RMS} I_{RMS} = 240 * 9.6 = 2.3 \text{ kVA}$$

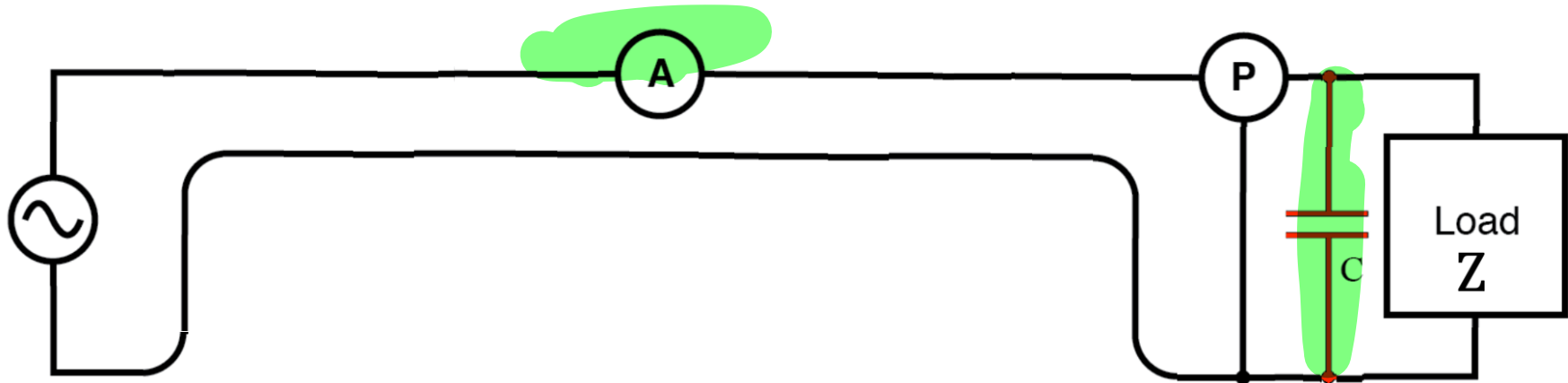- Real power = 1.5 kW, so power factor = $\frac{1.5}{2.3} = 0.65$
- Can we improve this? e.g. get current below 7 amps?




- Since a typical load is inductive, using the power factor value of 0.65 then the model is likely to be:

$$|Z| = \frac{240}{9.6} = 25 \Omega$$

$$Z = R + jX \\ = 16.25 + j19$$

- Try to improve matters with a shunt capacitor, C , so

$$Z_{new} = Z || \frac{1}{j\omega C}$$

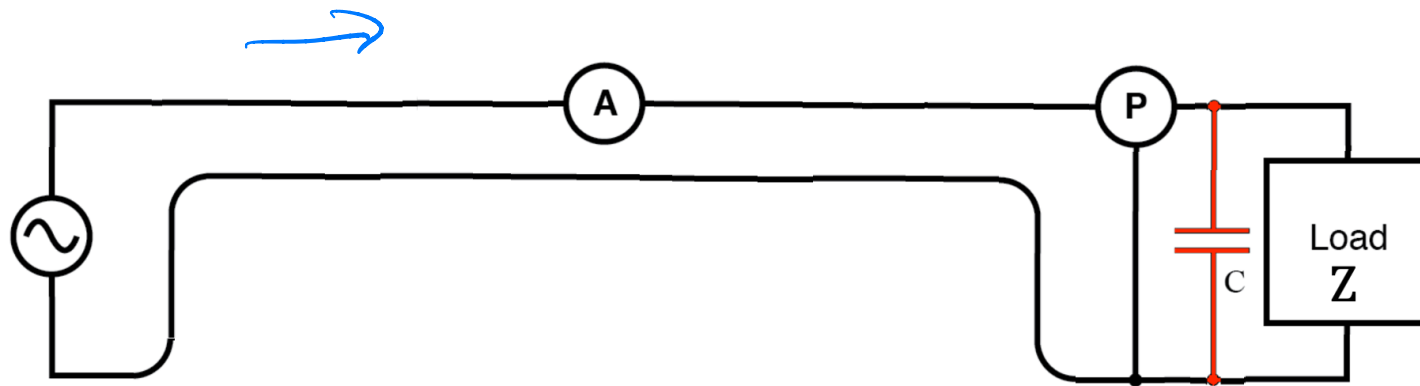


$$Z_{new} = Z \parallel \frac{1}{j\omega C} = \frac{Z \frac{1}{j\omega C}}{Z + \frac{1}{j\omega C}} = \dots$$

$$= \frac{R(1 - \omega CX) + \omega RCX}{(1 - \omega CX)^2 + \omega^2 R^2 C^2} + j \frac{X(1 - \omega CX) - \omega R^2 C}{(1 - \omega CX)^2 + \omega^2 R^2 C^2}$$

- Want Z_{new} to be real for best performance $\rightarrow C = 80.6 \mu F$
- $Z_{new} = 38.46 \Omega$ and now ammeter reads 6.24 A

Why this really matters: line resistance

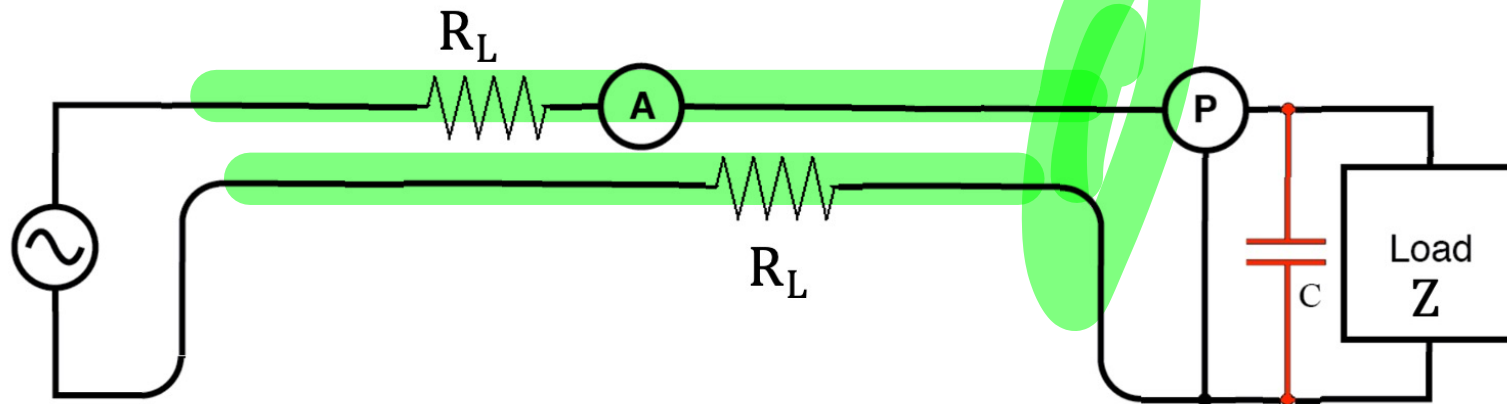


Shunt C yields higher voltage at the load and less heat in the wires

	$R_L = 0$	$R_L = 0.1 \Omega$	$R_L = 0.1 \Omega \ C = 80.6 \mu F$
Z_L	$16.25 + j19 \Omega$	$16.25 + j19 \Omega$	38.46Ω
I_L	9.6 A	9.55 A	6.24 A
V_L	240 V	238 V	239 V
P_{Load}	1500 W	1480 W	1500 W
P_{Line}	0	18.2 W	7.79 W


Analysis vs Design

- Voltage division **analysis** yields

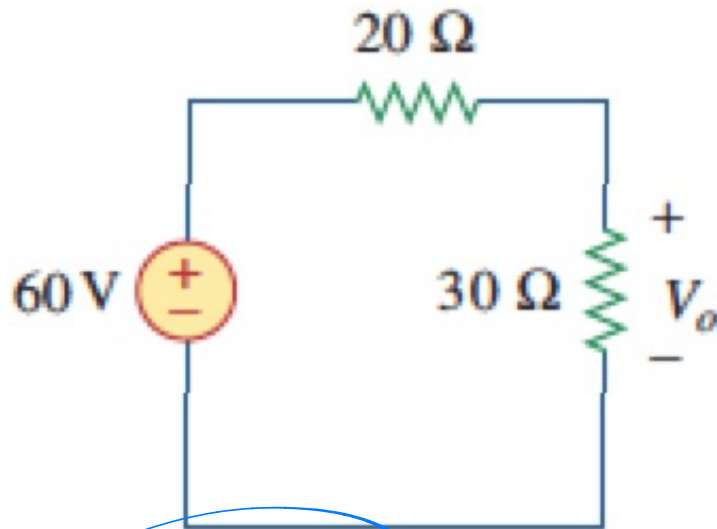

$$V_o = \frac{30}{20+30} 60 = 36 \text{ volts}$$

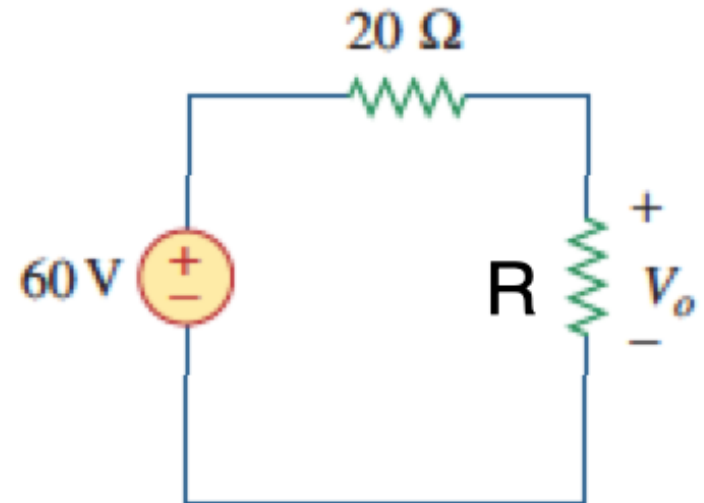- **Design:** How do we choose R for $V_o = 10$ volts? And is this even possible?




$$60 \cdot \frac{R}{R+20} = 10$$

- Solving :

$$V_o = \frac{R}{20 + R} 60 \Rightarrow R = \frac{20V_o}{60 - V_o}$$

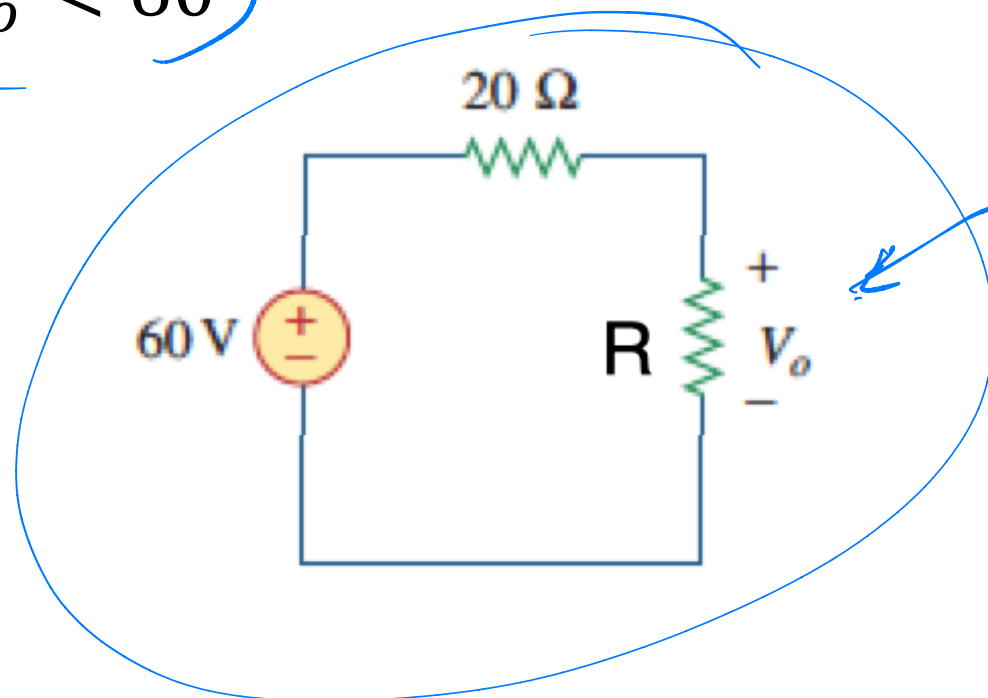
- One solution if $0 < V_o < 60$
- None otherwise



Phasor Circuit Design


$$i(t) = I \cos(5000t + \phi) \text{ A}$$

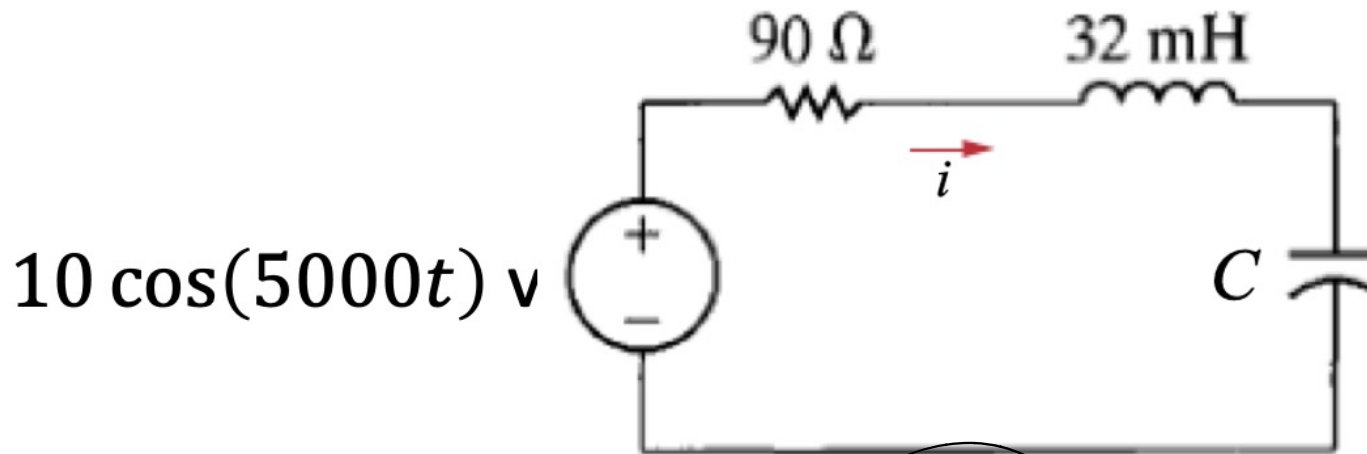- Choose components to achieve a certain goal.
- Example:



- Can you choose a capacitor C so that the steady state current i has a phase angle of -45° relative to the source? If so, what is the current's amplitude?

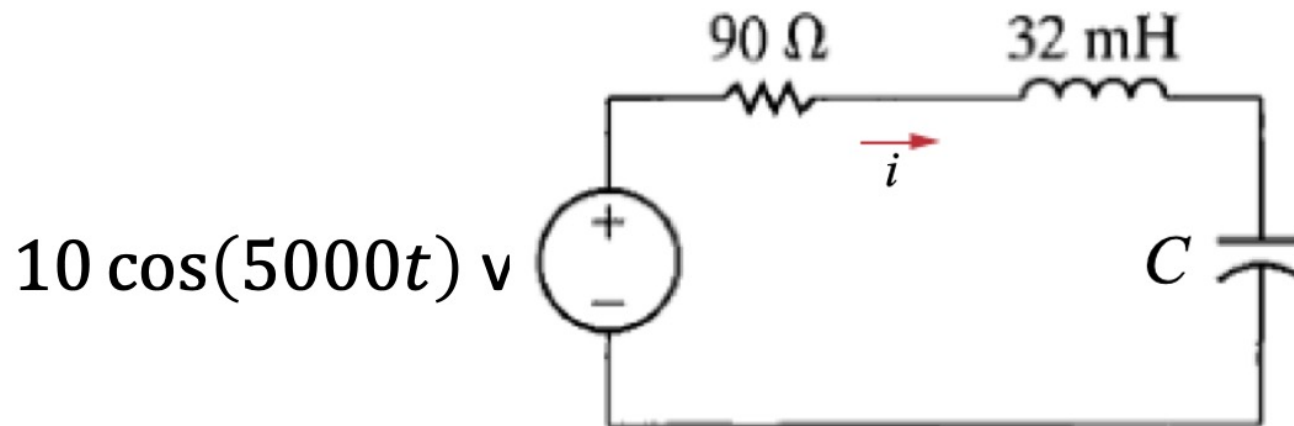- Considerations:
 - Is the request even possible? How many degrees of freedom do you have versus the number of quantitative goals? Is more than one solution possible?
 - For our example, what range of angles is even possible?



```
om = 5000;
```

```
R = 90;
```

```
L = 32e-3;
```


```
ZL = 1j*om*L;
```

```
C = logspace(-9,-1,1000);
```

```
ZC = 1./(1j*om*C);
```

```
I = 10./(R+ZL+ZC);
```

$10 \cos(5000t) \text{ V}$

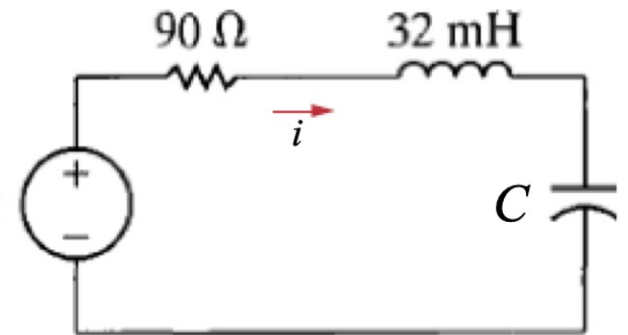

```
subplot(211)
```

```
semilogx(C, 20*log10(abs(I)), 'linewidth', 3)
```

```
xlabel('Capitance in Farads')
```

```
ylabel('Magnitude in dB')
```

```
set(gca, 'fontsize', 16)
```

```
grid on
```

```
subplot(212)
```



```
semilogx(C, 180/pi*angle(I), 'linewidth', 3)
```

```
xlabel('Capitance in Farads')
```


```
ylabel('Phase in degrees')
```

```
set(gca, 'fontsize', 16)
```

```
grid on
```

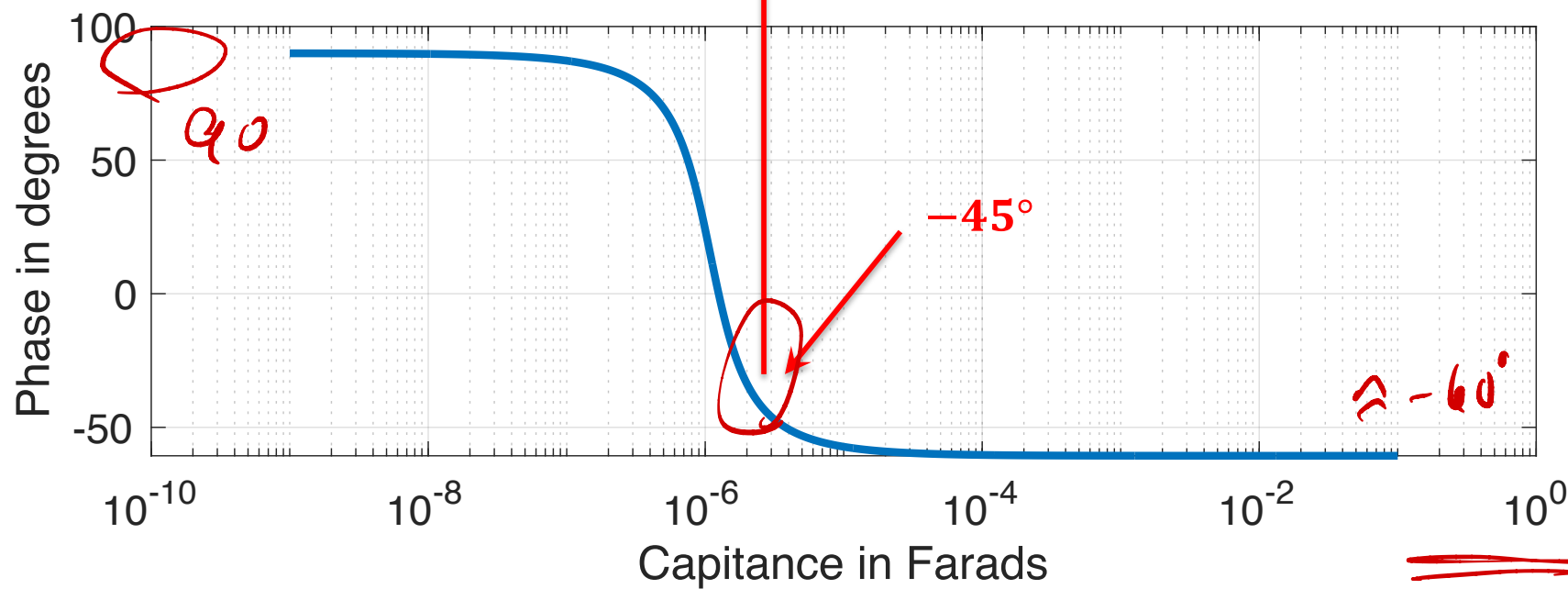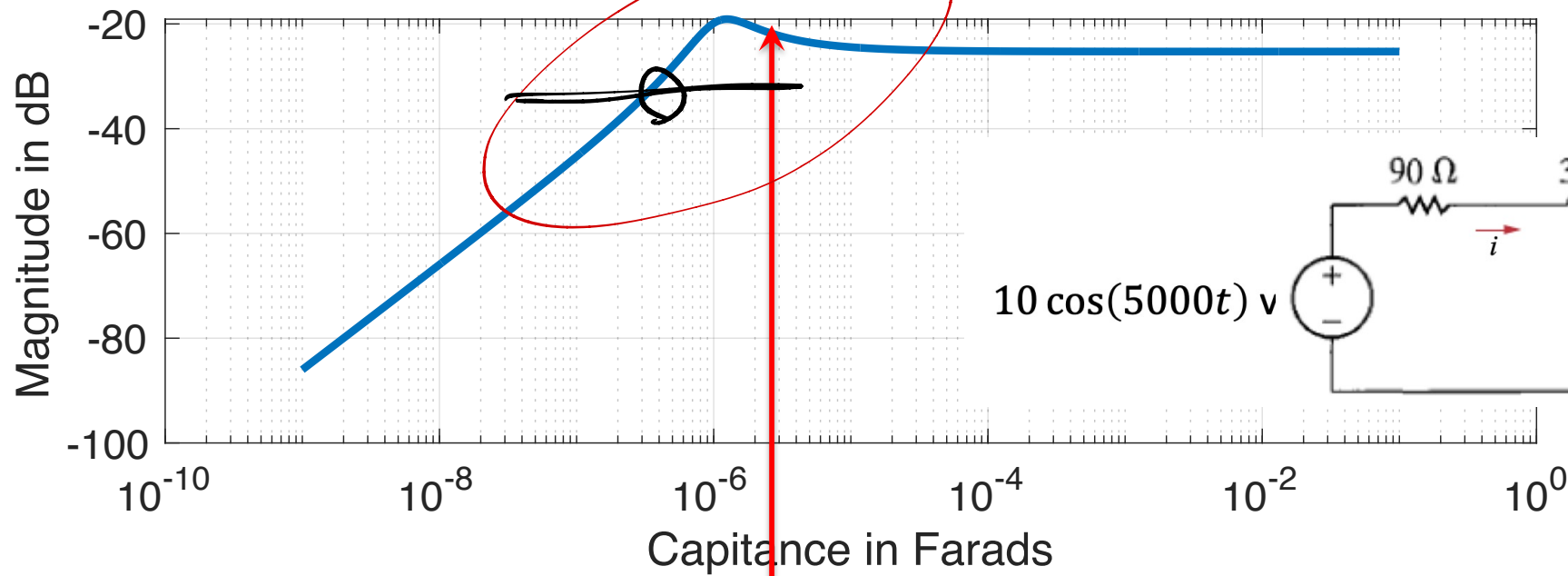

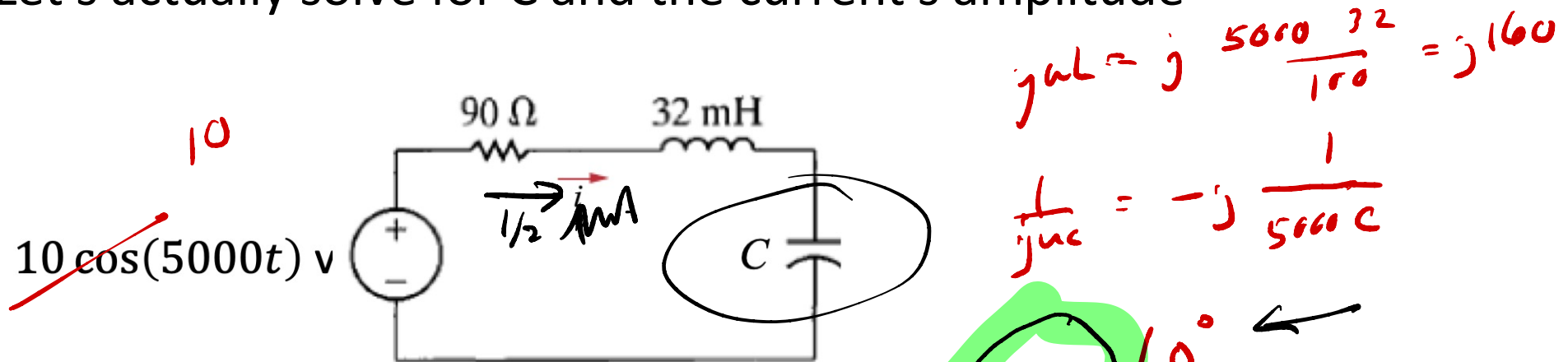Let's actually solve for C and the current's amplitude




$$j\omega L = j \frac{5000 \cdot 32}{100} = j160$$

$$\frac{1}{j\omega C} = -j \frac{1}{5000 C}$$

$$I = \frac{10}{90 + j160 - j \frac{1}{5000 C}}$$
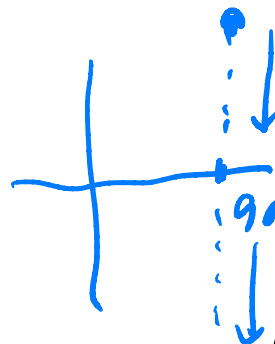
$$= \frac{10 \angle 0^\circ}{\sqrt{90^2 + \left(160 - \frac{1}{5000 C}\right)^2}} \angle$$



$$\angle I = \theta = \tan^{-1} \left(\frac{160 - \frac{1}{5000 C}}{90} \right) = -45^\circ$$

$$\tan^{-1} \left(\frac{160 - \frac{1}{5000 C}}{90} \right)$$

$$-\tan^{-1} \left(\frac{160 - \frac{1}{5000s}}{90} \right) = -45^\circ$$

need


$$160 - \frac{1}{5000s} = 90$$

$$+ \frac{1}{5000s} = +70$$

$$5000s = \frac{1}{70}$$


$$C = \frac{1}{70 \cdot 5000}$$

2.86 μF ; 78.6 mA

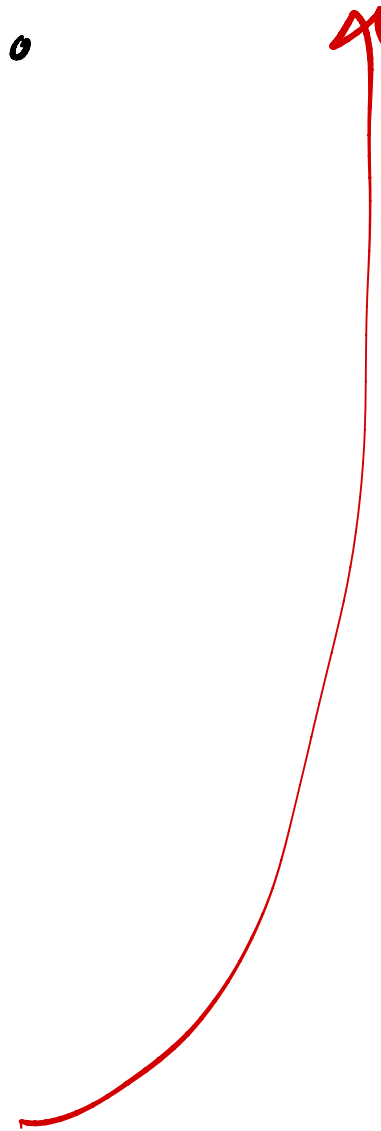


Practice problem:

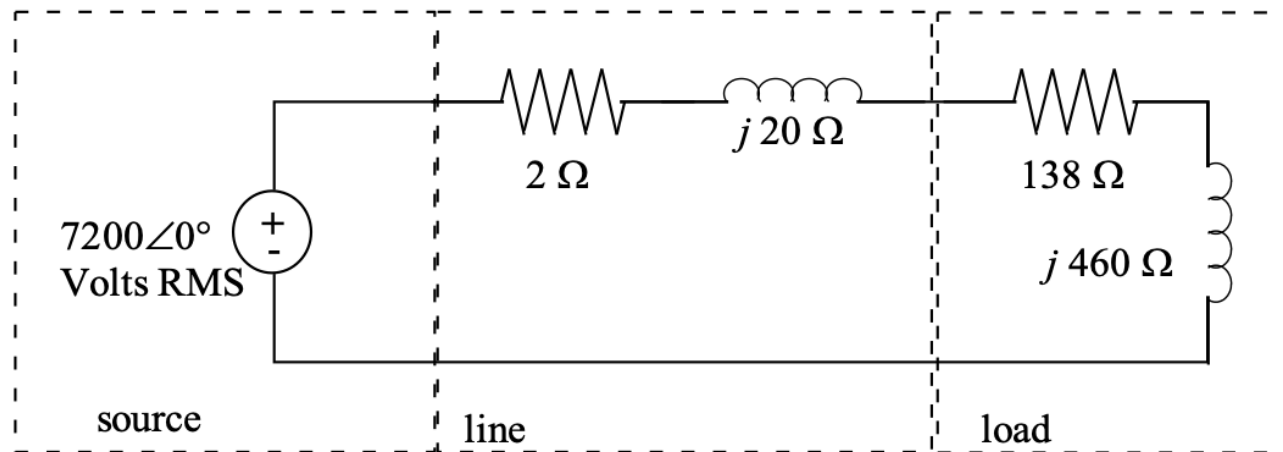- Find the average power dissipated by the line
- Find the shunt capacitance to make the load appear purely resistive
- Find the load resistance resulting from this shunt capacitance
- Find the average power dissipated by the line with the shunt capacitor installed



$207\ W$; $-501\ \Omega$; $1.67\ k\Omega$; $18.6\ W$

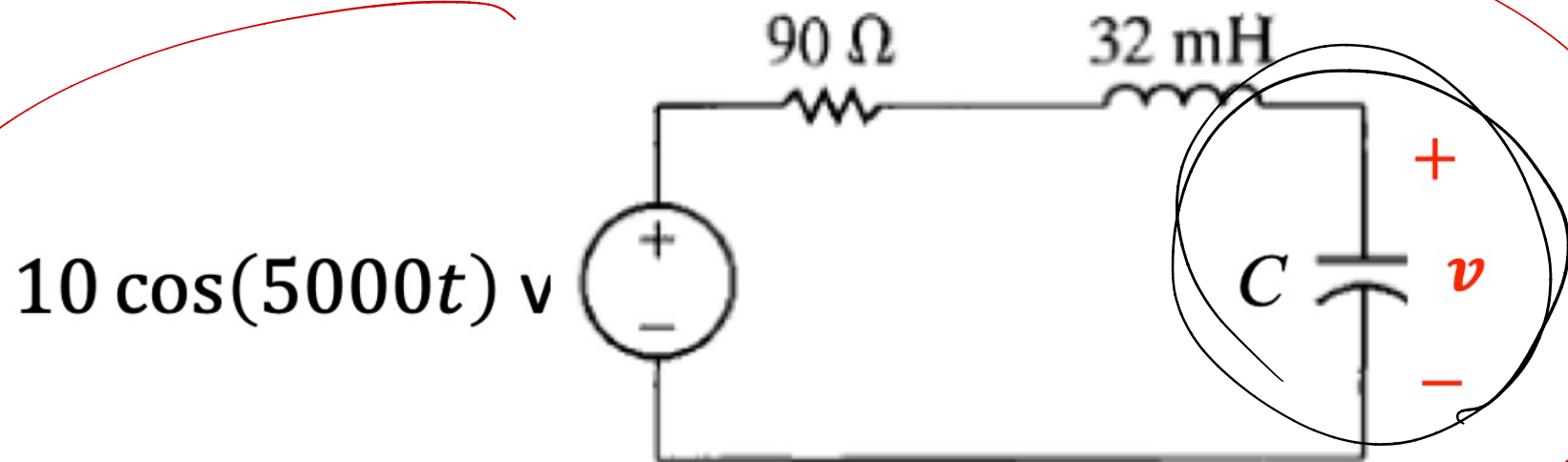Practice problem: for the same circuit, Can you choose a capacitor C so that its steady state voltage v has a phase angle of -45° relative to the source?



$$\angle V. = \angle 10 \cdot \frac{\angle 1}{\angle 90 + j160 - j \frac{1}{5000C}}$$

$$-90 - \tan^{-1} \left(\frac{1}{5000C} \right)$$

$$0.118 \text{ nF}$$