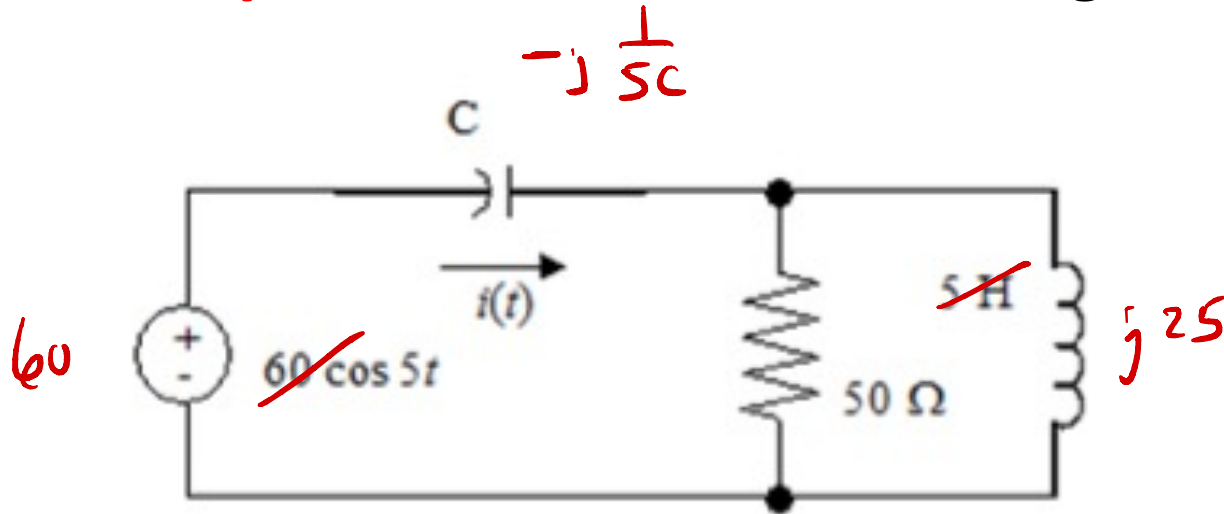


Phasors 9

design examples

Example: Find C so that the magnitude of $i(t)$ is 4 amps.



$$\frac{(50)(j25)}{50 + j25}$$

$$= \frac{j50}{2+j} \cdot \frac{2-j}{2-j} = \underline{10 + j20}$$

$$Z = -j \frac{1}{sC} + 10 + j20$$


$$|10 + j(20 - \frac{1}{sC})| = 15$$

$$I = \frac{60}{Z} = \frac{60}{10 + j(20 - \frac{1}{sC})}$$



```

om = 5;
R = 50;
L = 5;
ZL = 1j*om*L;
C = logspace(-9,0,1000);
ZC = 1./(1j*om*C);
Z = ZC + 50*ZL/(50+ZL);
I = 60./Z;


```

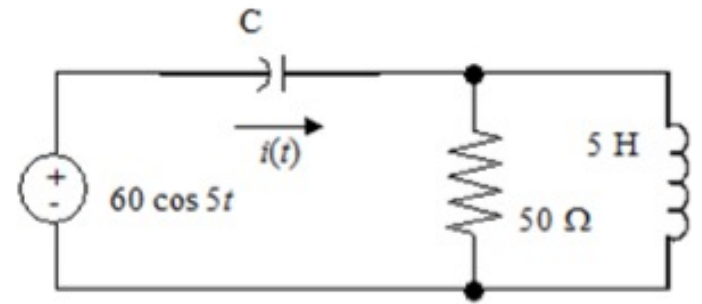

$|I| = 4$ occurs in two spots !!

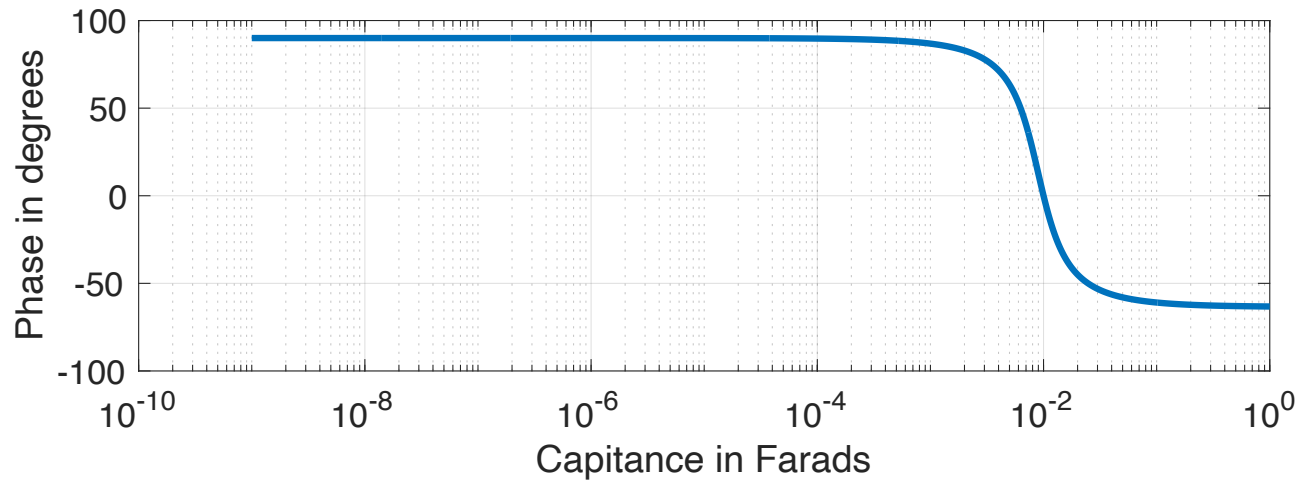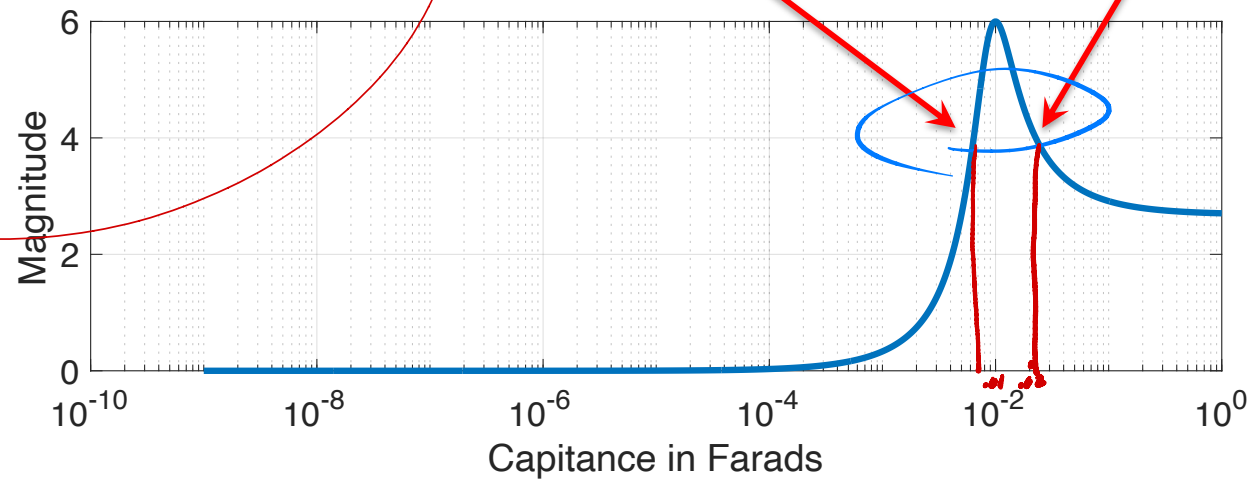

Let's actually solve for C

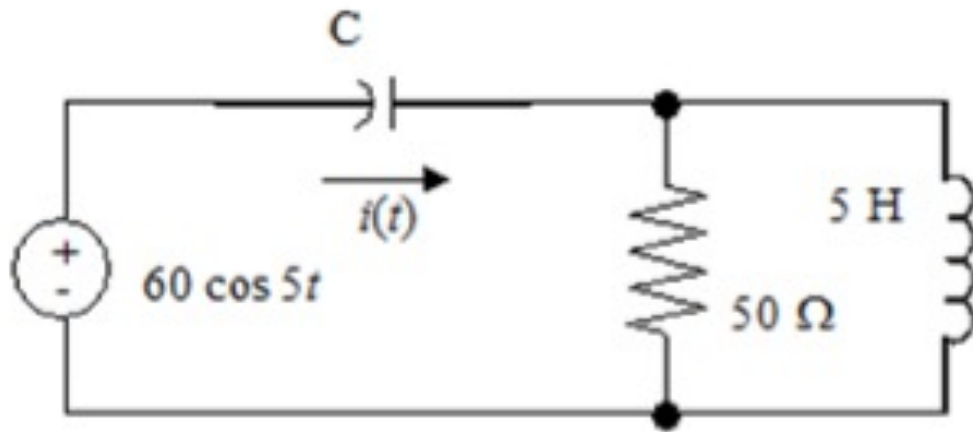

$$|10 + j\left(20 - \frac{1}{5C}\right)| = 15$$

$$\sqrt{100 + \left(20 - \frac{1}{5C}\right)^2} = 15$$

$$100 + \left(20 - \frac{1}{5C}\right)^2 = 225$$

$$10 + j\left(20 - \frac{1}{5C}\right)$$

$$|2 + bj| = \sqrt{a^2 + b^2}$$

$$\left(20 - \frac{1}{5C}\right)^2 = 125$$

$$20 - \frac{1}{5C} = \pm \underbrace{\sqrt{125}}_{11.1}$$

$$20 \mp 11.1 = \left(\frac{1}{5C}\right)$$


~~11.1~~ ?

$$\frac{1}{5C} \approx 31$$


$$C = \frac{1}{5 \cdot 31} \approx \frac{1}{155}$$

$$\frac{1}{5C} \approx 2.7 \text{ ?}$$

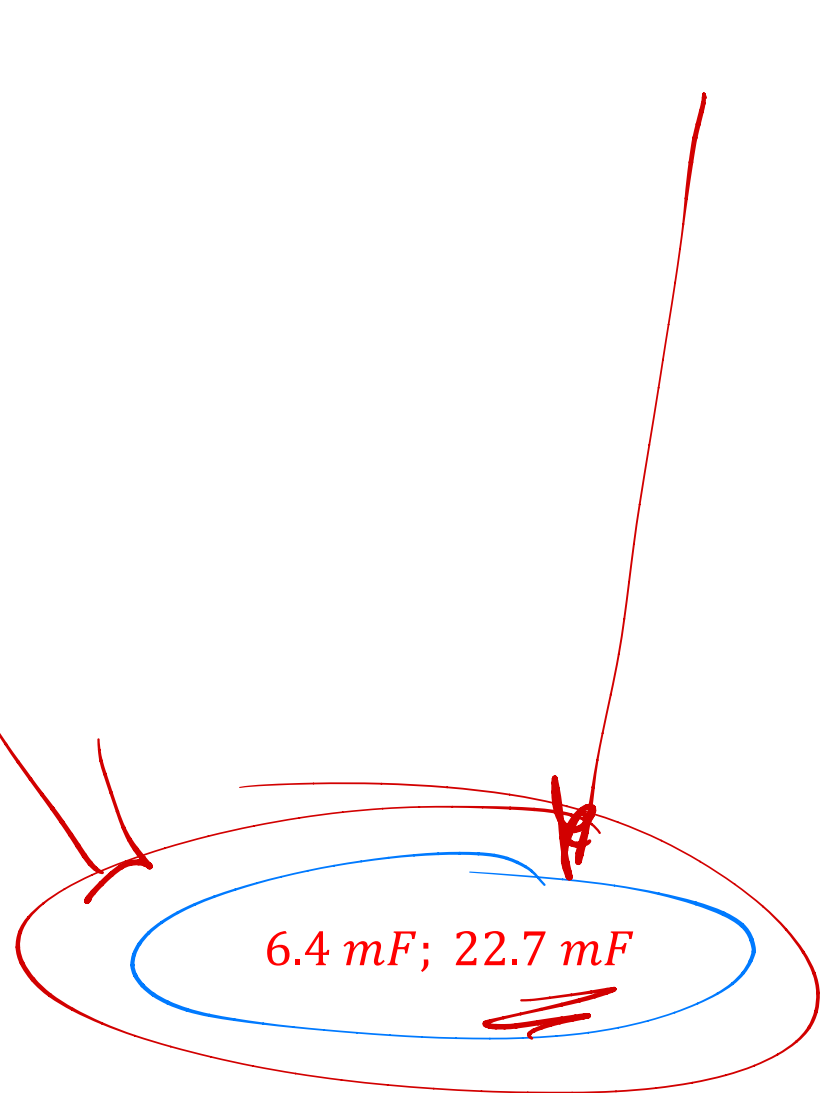
$$C \approx \frac{1}{5 \cdot 2.7} = \frac{1}{13.5}$$



Example: The circuit shown is a low pass filter meaning that it passes lower frequency sinusoids and attenuates higher frequency sinusoids. Find a value for the capacitor C so that all sinusoids above 1000 Hz in frequency are attenuated by at least 90% (i.e. their amplitude scaling, $|V_o/V_s|$, is at most 0.1). Using your result what happens to a 60 Hz signal? How is its amplitude changed? How is its phase angle changed?

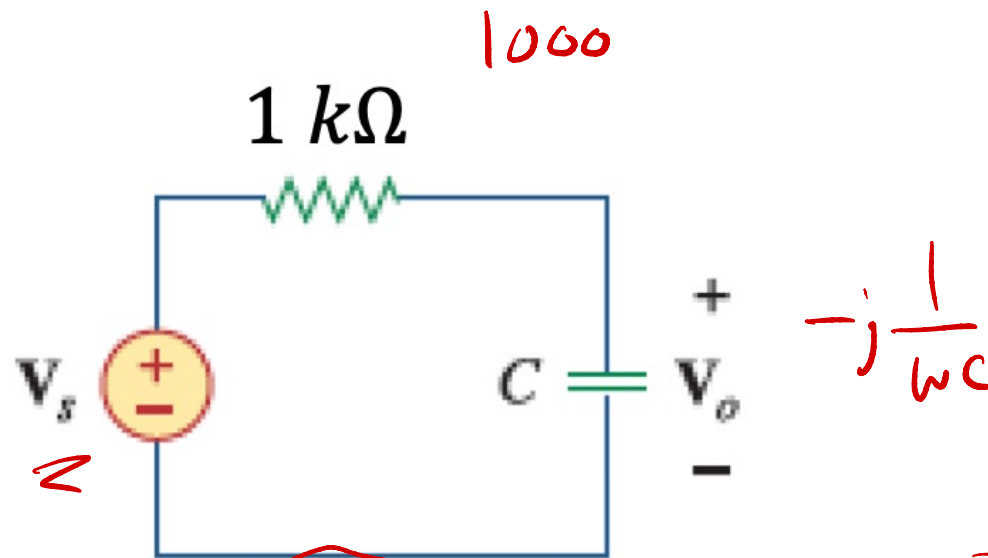
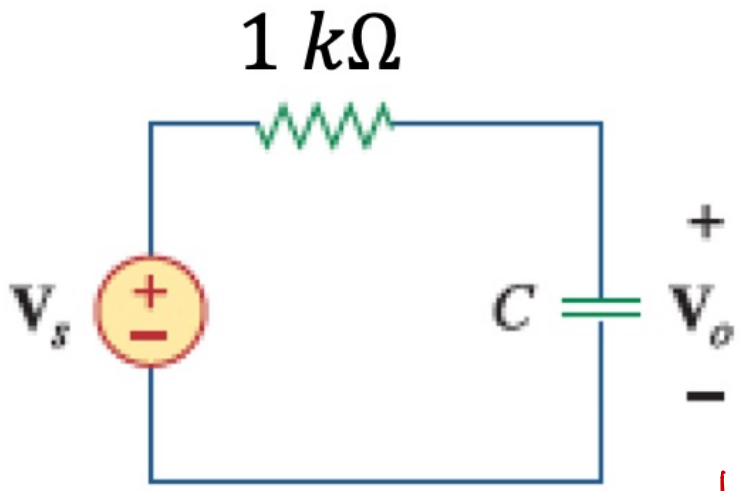
$$\frac{V_o}{V_s} = \frac{-j}{1000\omega C - j} = \boxed{\frac{1}{1 - j1000\omega C}} \quad \frac{V_o}{V_s} = \frac{-j/\omega C}{1000 - j\omega C}$$



$$\frac{V_o}{V_s} = \frac{1}{1 + j 1000 \omega C}$$

$\omega = 1000$ $\left| \frac{V_o}{V_s} \right| < .1$

$$\left| \frac{1}{1 + j 10^6 \cdot C} \right| = .1$$

$$\frac{1}{\sqrt{1 + 10^{12} C^2}} = .1$$

$$1 = 10^{-2} + 10^{10} C^2$$

$$10^{10} C^2 + 10^{-2} - 1 = 0$$


$$\frac{1}{1 + 10^{12} C^2} = 10^{-2}$$

$$10^{10} C^2 = 1 - 10^{-2} = .99$$

$$C^2 = .99 \cdot 10^{-10}$$

1.58 μF ; 85.9 %; -20.8°

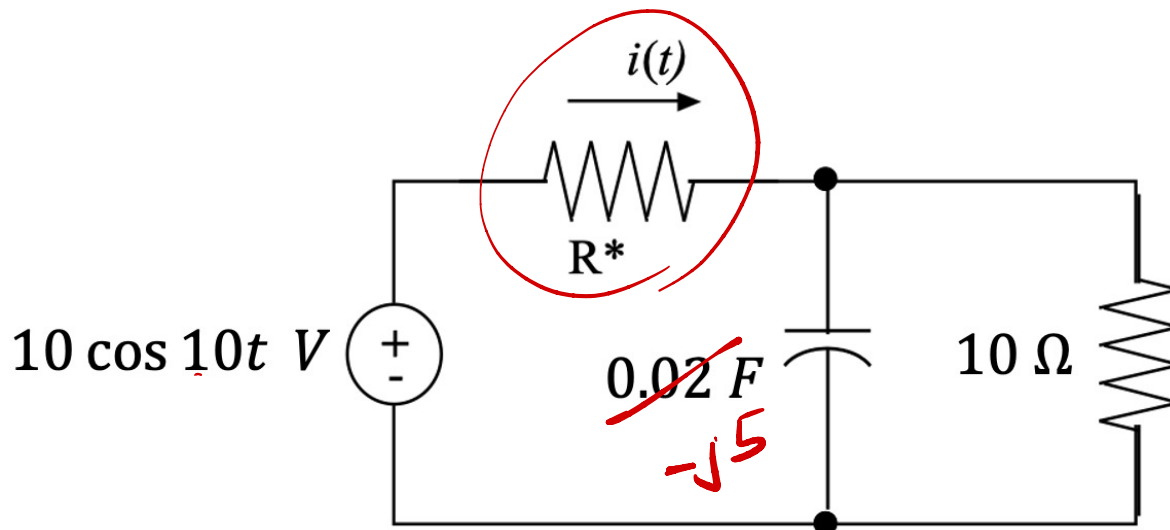Example: Find the resistor R^* so that the magnitude of the current $i(t)$ is 1 A.



$$\frac{(10)(-j5)}{10 - j5} = \frac{-j10}{2-j} \cdot \frac{2+j}{2+j} = 2 - j4$$

$$Z = R^* + 2 - j4$$

$$I = \frac{10}{R^* + 2 - j4} \approx \frac{10}{9 - j4}$$

$$I = \frac{10}{R^* + 2 - j4}$$

97.9 Ω

$$|I| = \frac{10}{\sqrt{(R^* + 2)^2 + 16}} = 1$$

$$\sqrt{\quad} = 10$$

$$(R^* + 2)^2 + 16 = 100$$


$$(R^* + 2)^2 = 84$$

$$R^* + 2 = \pm \sqrt{84} = \pm 9.1$$

$$R^* = -2 \pm 9.1$$


$$R^* = 7 \Omega$$

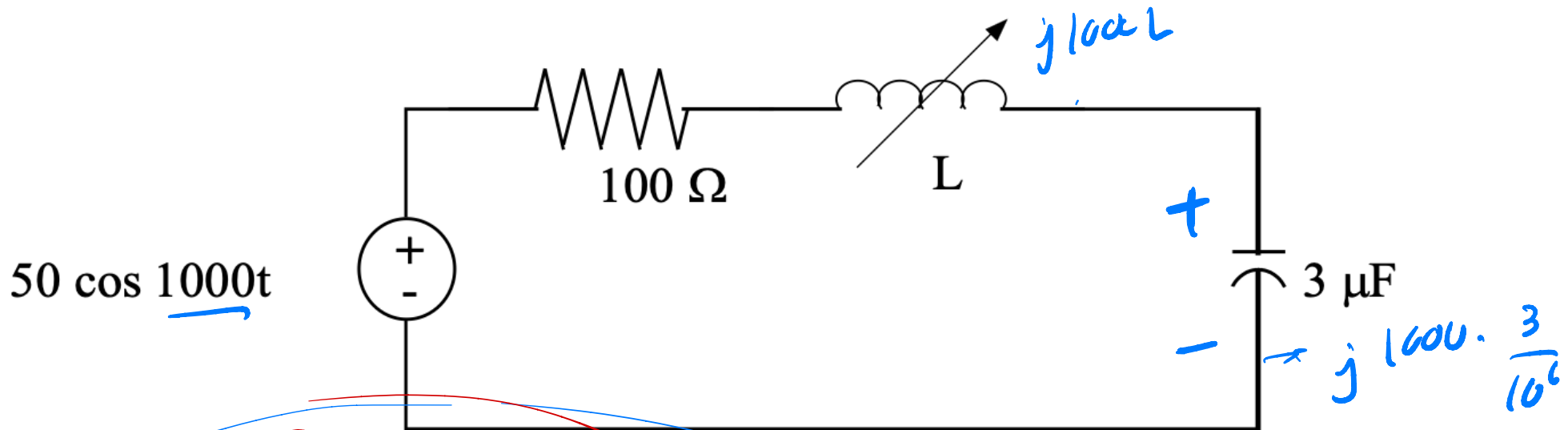Example: Find the inductor value to maximize the magnitude of the voltage appearing across the capacitor. What is that magnitude?




$$V_C = \frac{50 \cdot \left(-j \frac{3}{1000}\right)}{1000 + j1000L - j \frac{3}{1000}}$$

$$-j \frac{3}{1000}$$

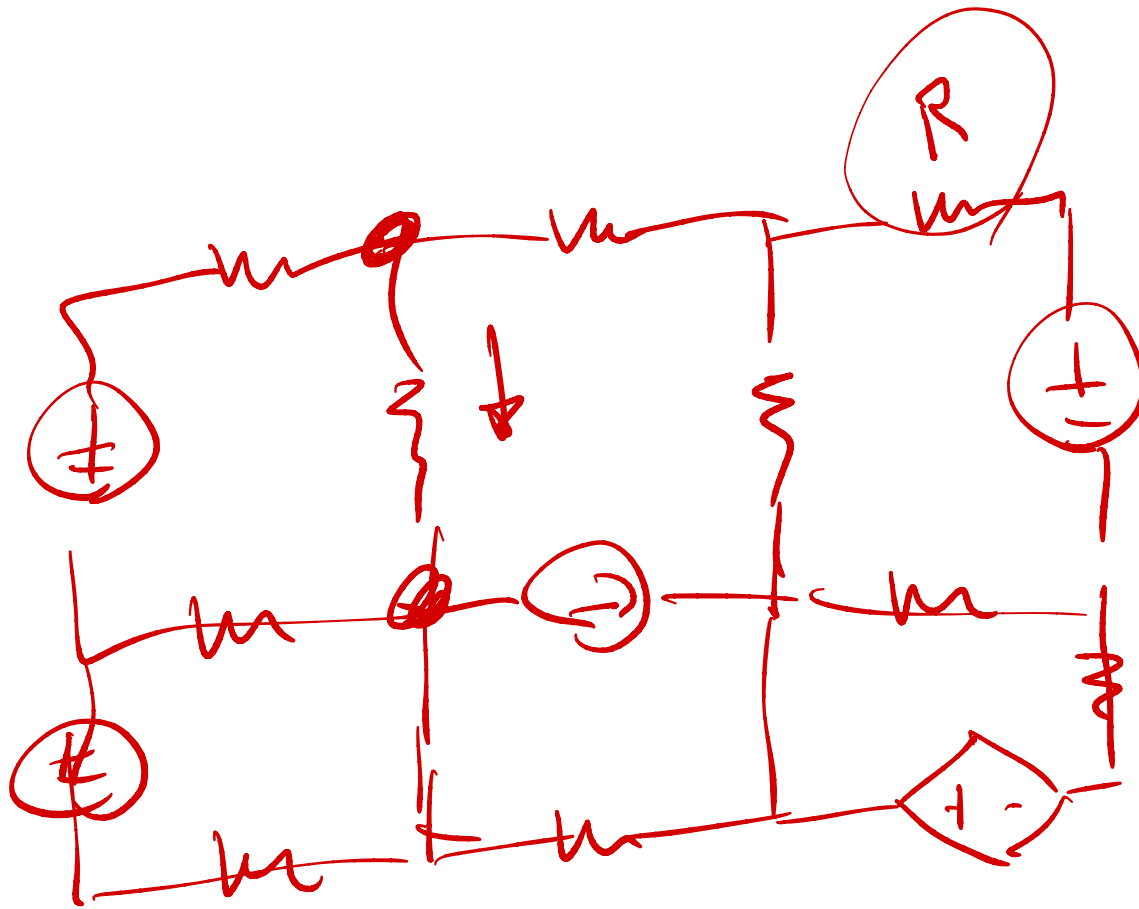

$$\frac{1}{3} A, \frac{10}{3} V$$

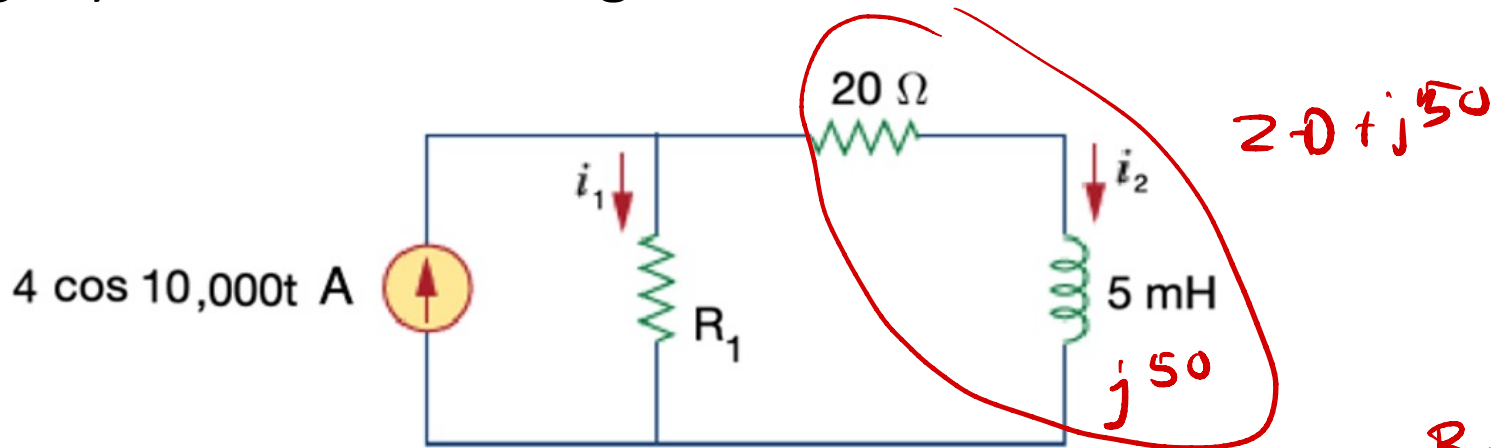Example: what value for resistor R_1 results in the two currents, i_1 and i_2 , having the same magnitude (but might be different phase angles)? What is that magnitude?



$$I_1 = \frac{4 \cdot (20 + j50)}{20 + R_1 + j50} \quad \sqrt{2900}$$

$$|I_1| = \frac{4 \cdot |20 + j50|}{|20 + R_1 + j50|}$$


$$I_2 = \frac{4 \cdot R_1}{20 + R_1 + j50}$$

$$|I_2| = \frac{4 R_1}{|20 + R_1 + j50|}$$

53.9 Ω ; 2.42 A

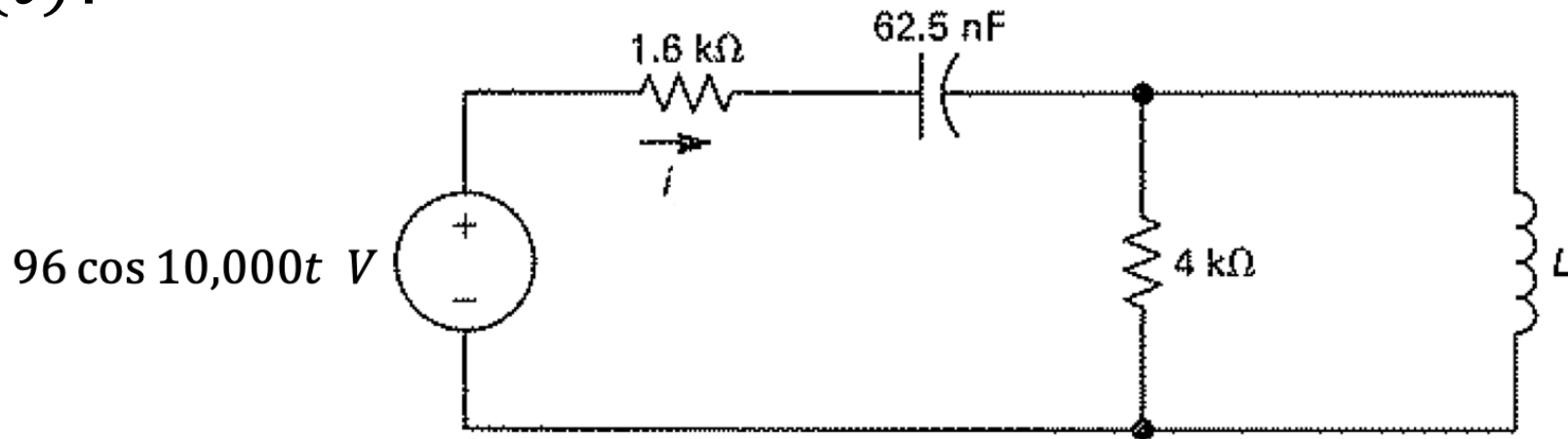
53.9 Ω ; 2.42 A

Practice problem: find the inductor value so that the current i is “in phase” with the voltage source. What is $i(t)$?




$0.8 \text{ H}, 20 \cos(10,000t) \text{ mA}; 0.2 \text{ H}, 405 \cos(10,000t) \text{ mA}$

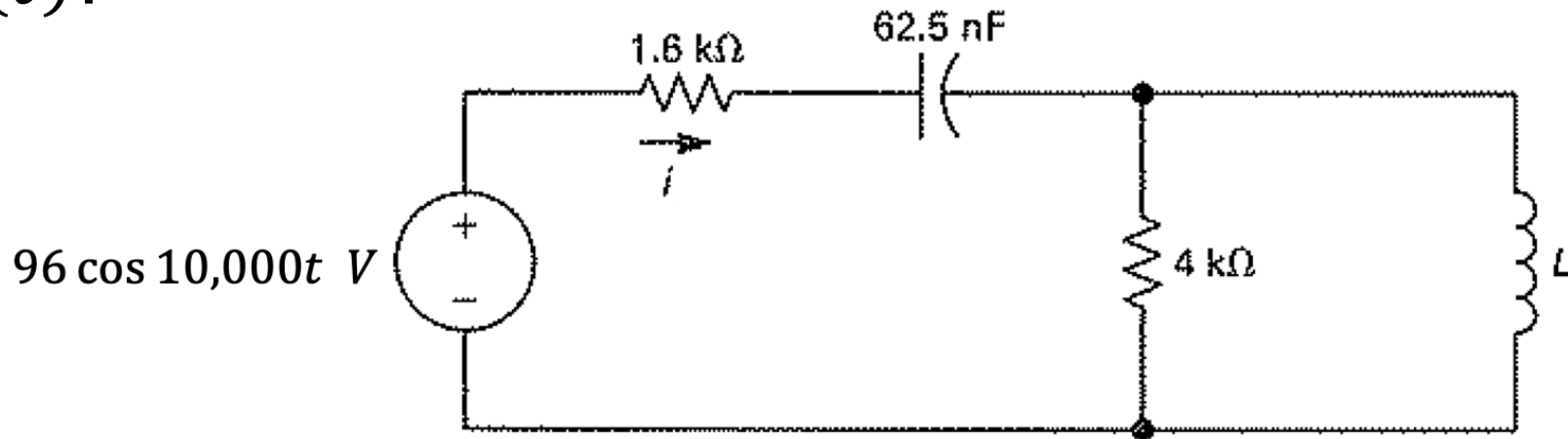Practice problem: find the inductor value so that the current i is “in phase” with the voltage source. What is $i(t)$?



$0.8 \text{ H}, 20 \cos(10,000t) \text{ mA}; 0.2 \text{ H}, 405 \cos(10,000t) \text{ mA}$

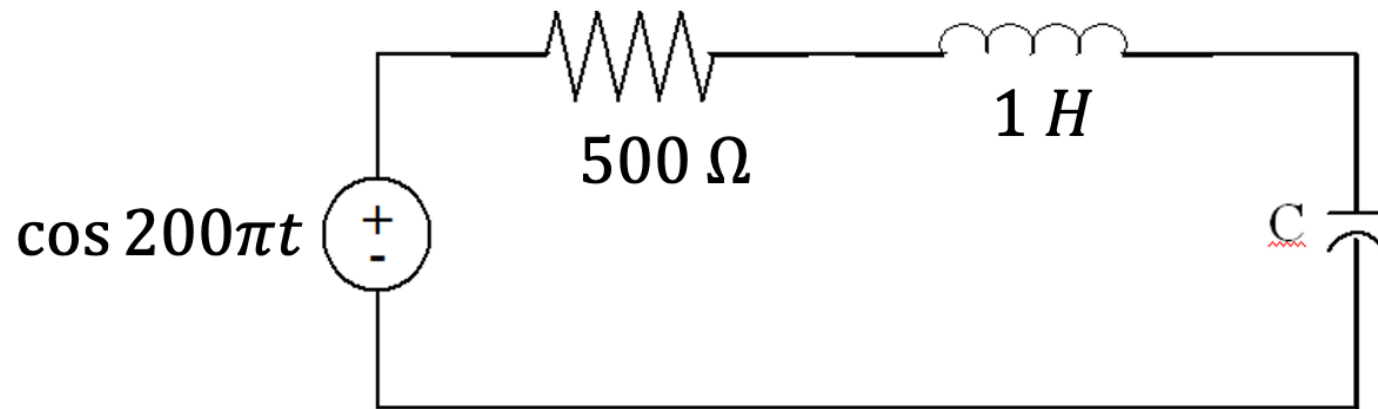Practice problem: find the capacitor value to maximize the magnitude of the voltage appearing across the capacitor. What is that magnitude?



$1.55 \mu F, 1.61 V$