

# Theorems – 1


linearity & superposition;  
transformations

# Linearity & Superposition


- Linearity: for a single “input” (voltage or current), the “output” (voltage or current) is proportional to that input

$$v_o = k v_s$$

- What about multiple “input” sources?

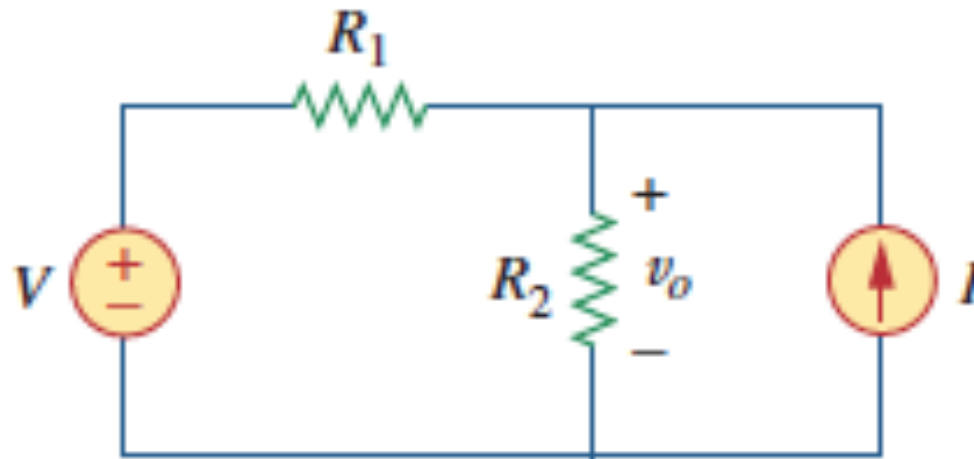

- Analyzing

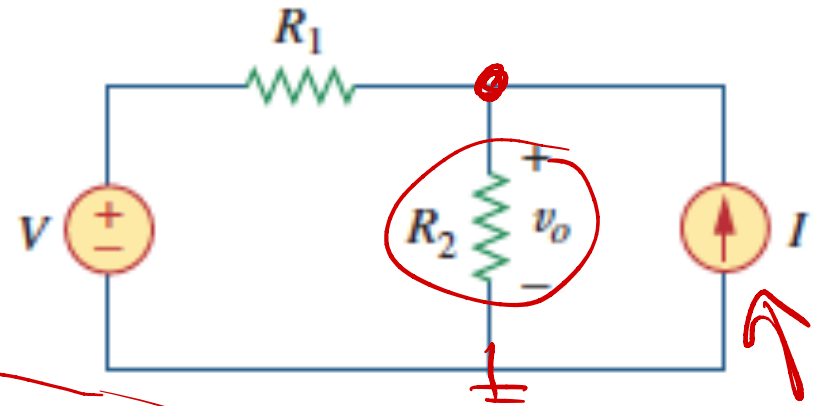

$$\frac{v_o - V}{R_1} + \frac{v_o}{R_2} - I = 0$$

or

$$v_o = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V$$

- And the idea extends to multiple “input” sources


$$v_o = k_1 v_{s1} + k_2 v_{s2}$$

**“Superposition”**

- We can exploit this idea to decompose problems:



– Example:
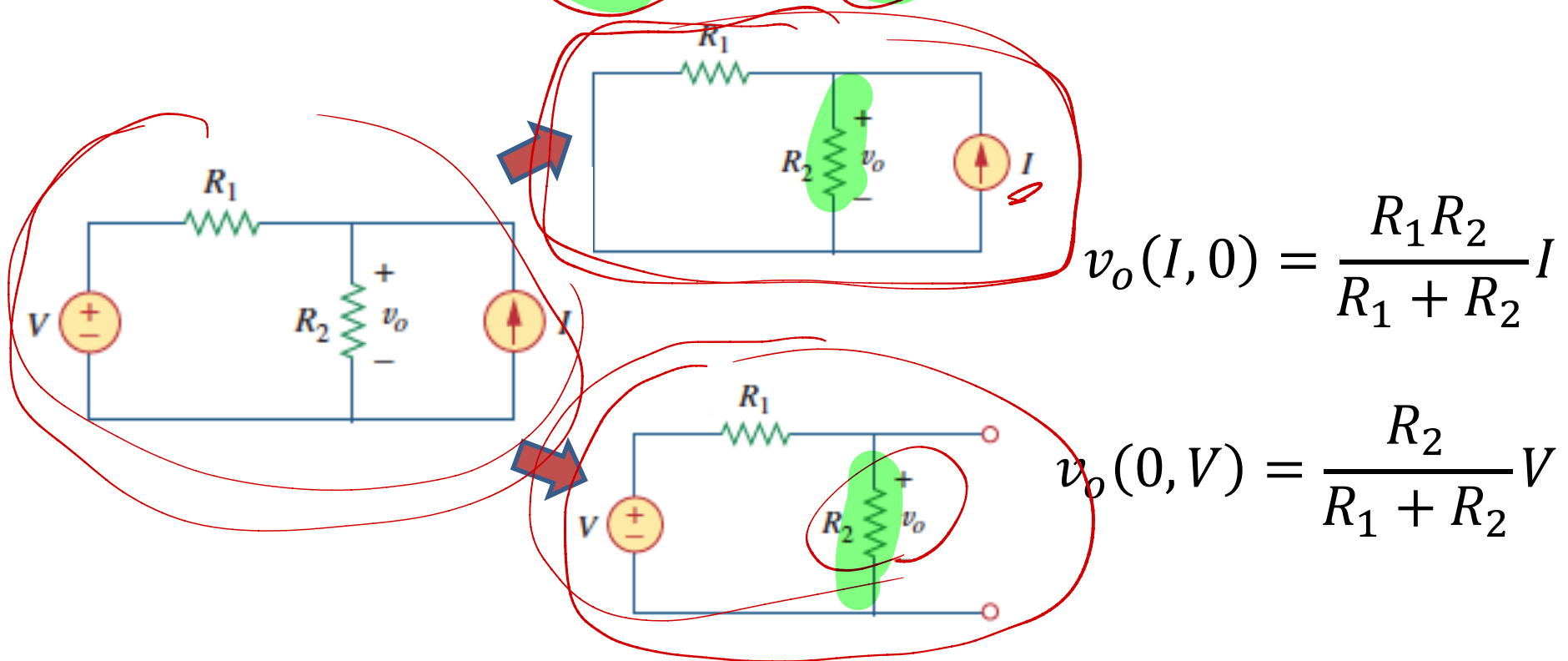
$$v_o(I, V) = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V = \underline{v_o(I, 0)} + \underline{v_o(0, V)}$$




**Example:** find  $i$

$$i = \frac{B}{4}$$

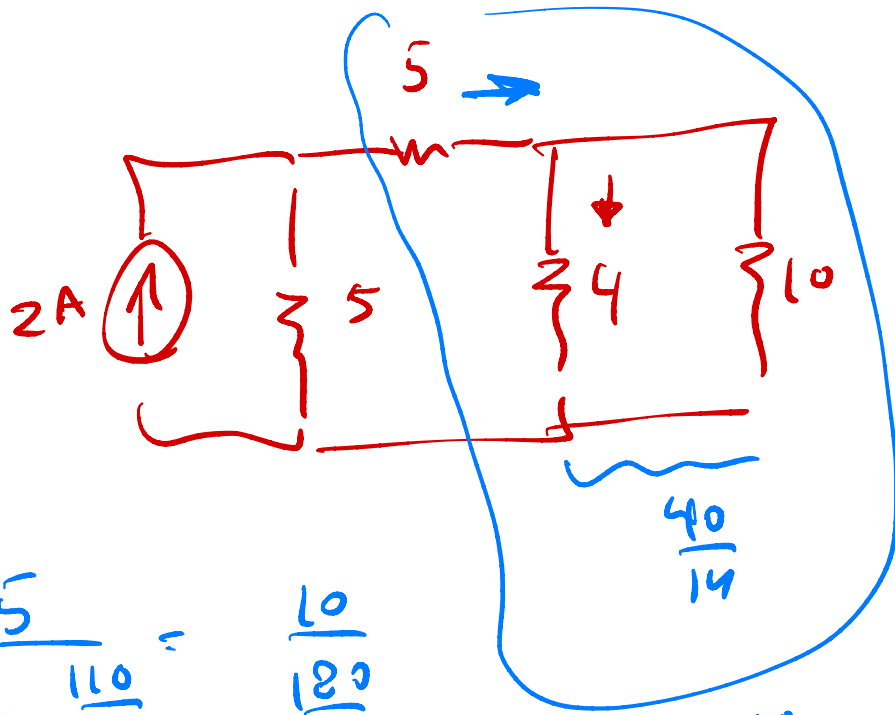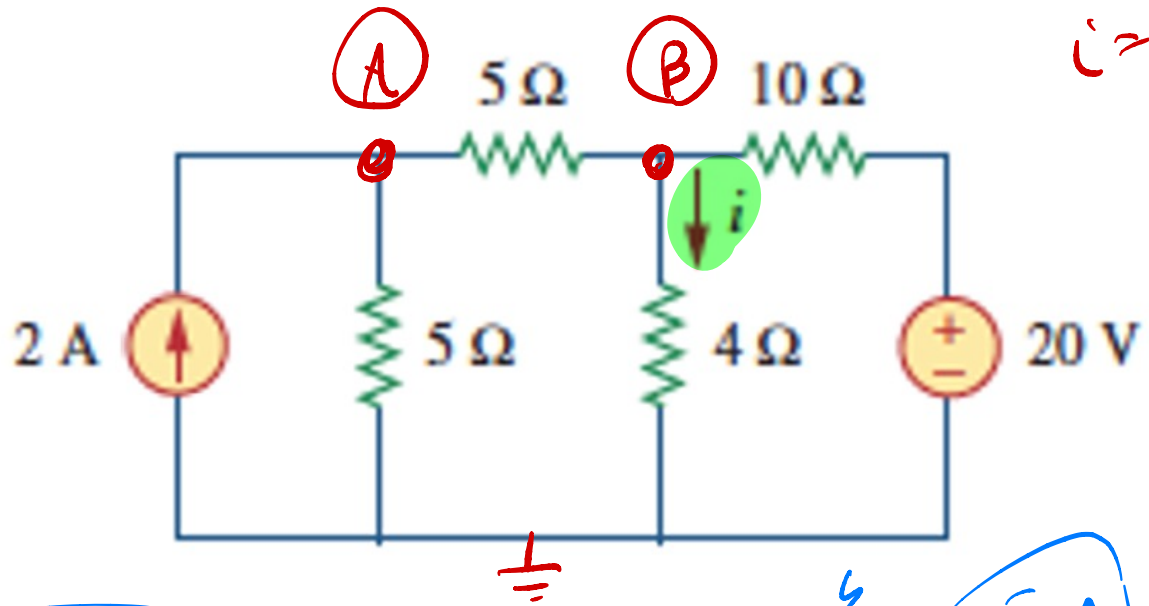

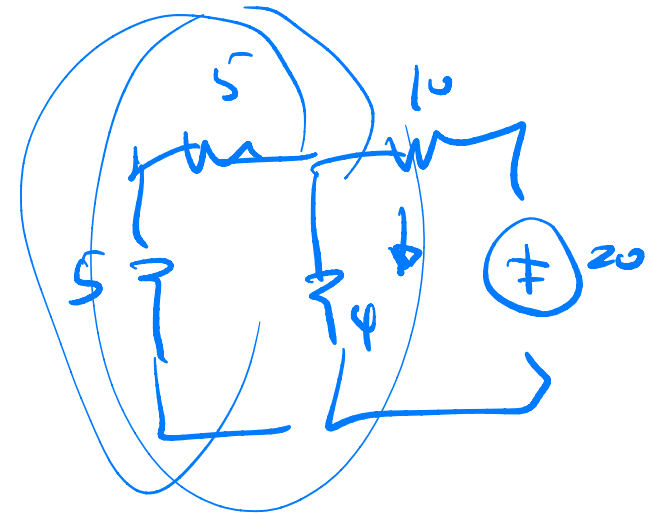Max.  $\frac{10}{5} = \frac{5}{1} = 5 \text{ A}$





$$2. \quad 5 + \frac{5}{14} = \frac{10}{14}$$

$$5 + \frac{10}{14} = \frac{110}{14}$$


$$= \frac{140}{180} = \frac{7}{9} \text{ A}$$

$$i = 1.67 \text{ A}$$

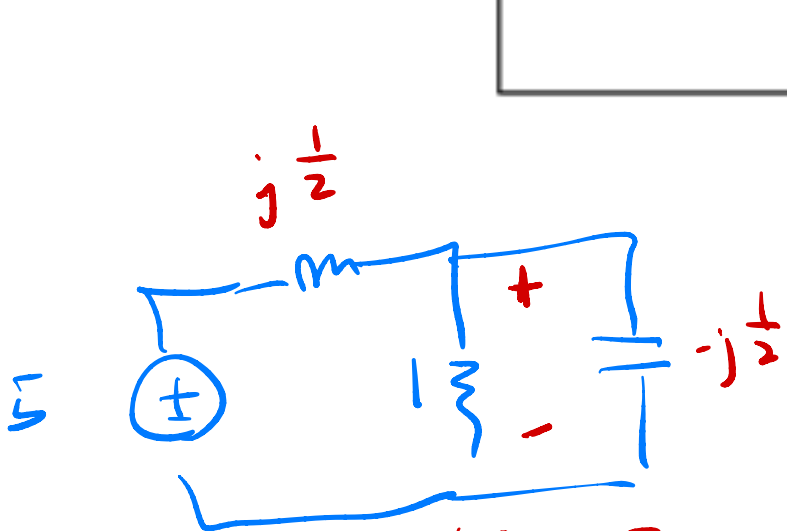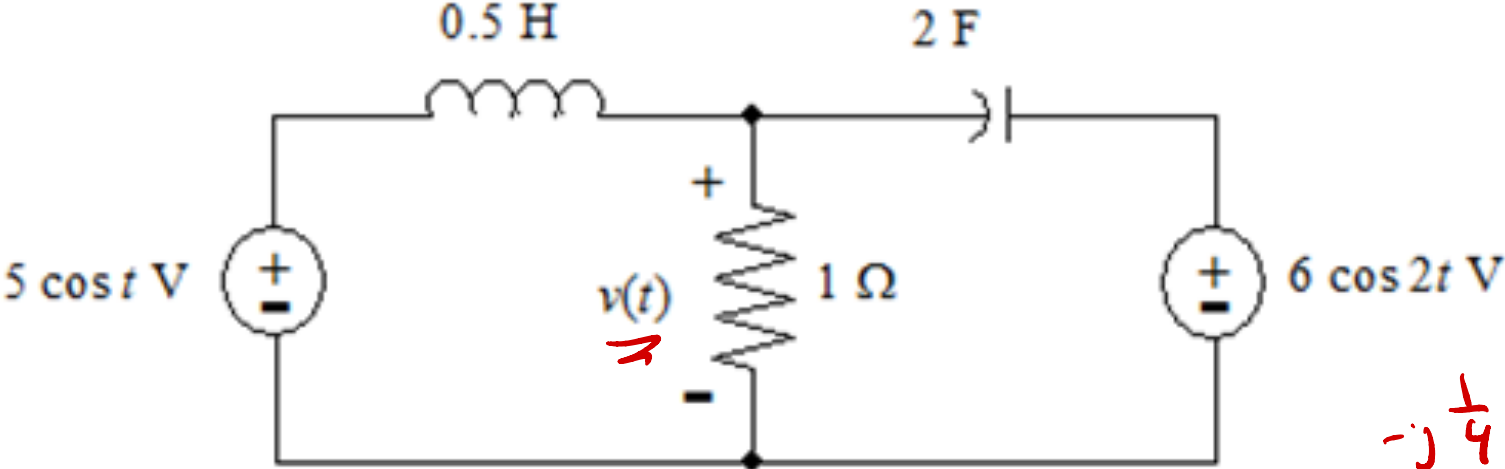
**Phasor example:** note different frequencies


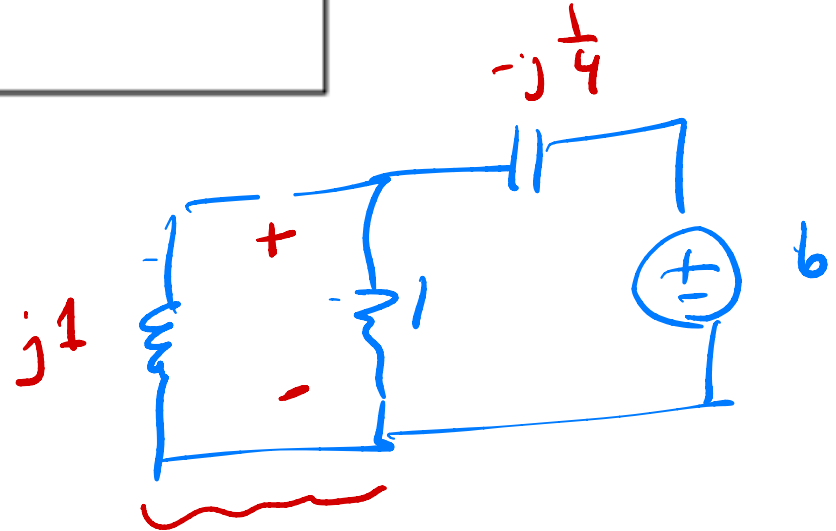
$$\frac{-j \frac{1}{2}}{1 - j \frac{1}{2}} \cdot \frac{1}{2} = \frac{-j}{2 - j}$$



$$\frac{j}{1 + j}$$

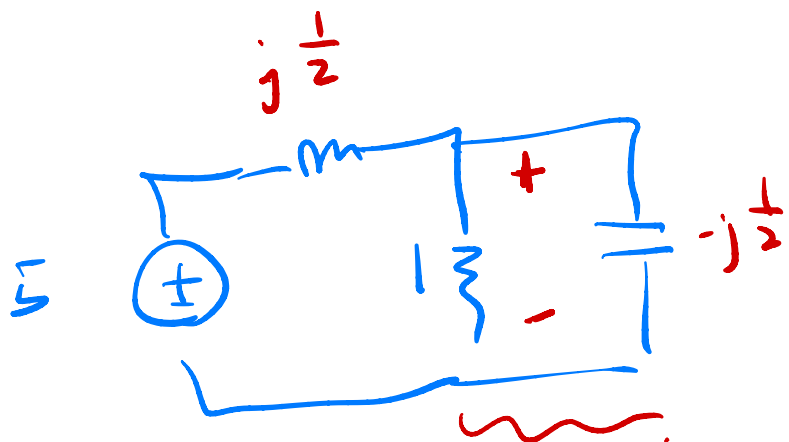


$$\frac{-j \frac{1}{2}}{1 - j \frac{1}{2}} \cdot 2 \angle 120^\circ = \frac{-j}{2 \angle 71.5^\circ}$$

$$v = 5 \cdot \frac{-j}{2 \angle 71.5^\circ} \cdot \frac{2 \angle 120^\circ}{2 \angle 71.5^\circ}$$

$$\frac{1}{2} - \frac{1}{2j}$$

$$= \frac{-10j}{j(2j) - 2j} = \frac{-10j}{1}$$

$$j^2 + (-j)^2 = 1$$

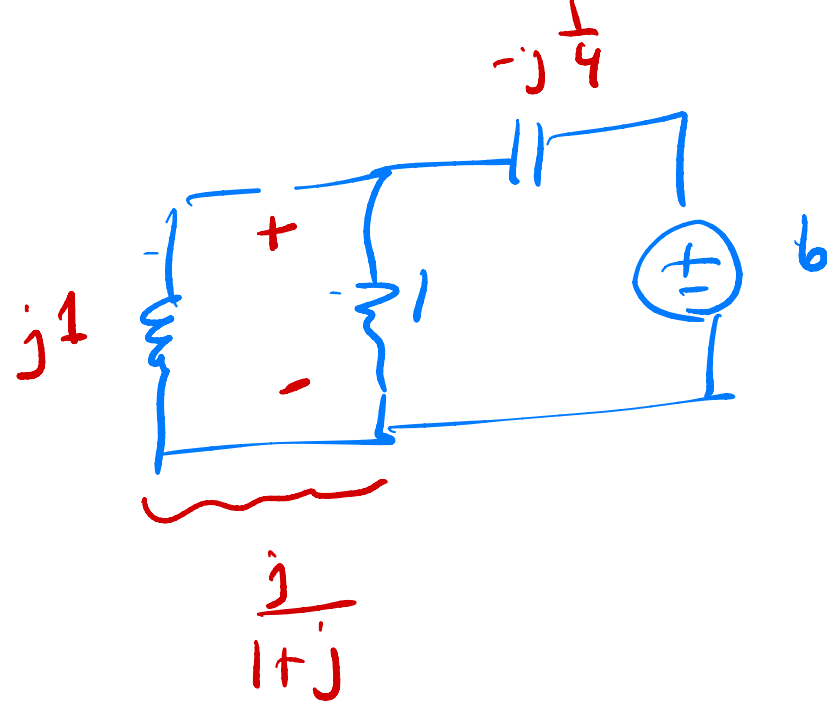


$$v = 6 \cdot \frac{\frac{1}{1+j}}{-\frac{j}{4} + \frac{j}{1+j}} \cdot \frac{4 \angle 180^\circ}{4 \angle 0^\circ}$$

$$= \frac{j 24}{-j(1+j) + 4j} = \frac{j 24}{-j + 1 + 4j} = \frac{j 24}{1 + 3j}$$

$$v(t) = 10 \cos(t - 90^\circ) + 1.2 \cos(2t + 127^\circ) \text{ V}$$




# Source Transformations

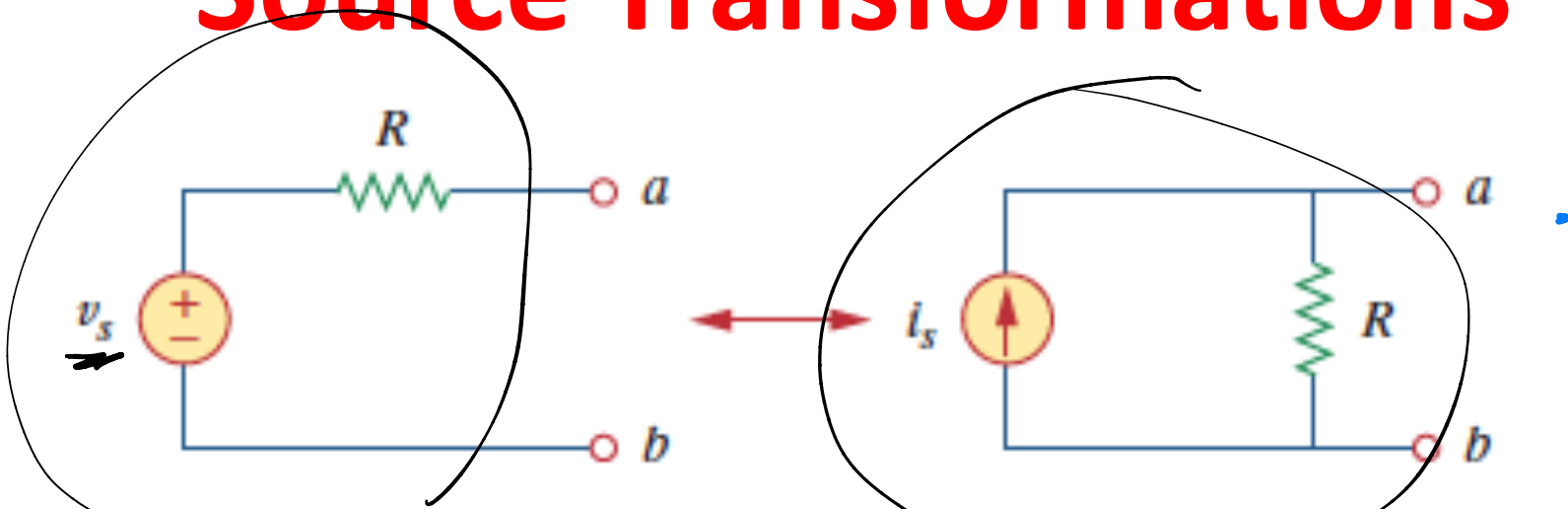

– These two sub-circuits are equivalent *at the terminals a, b*



**iff**  $v_s = R I_s$

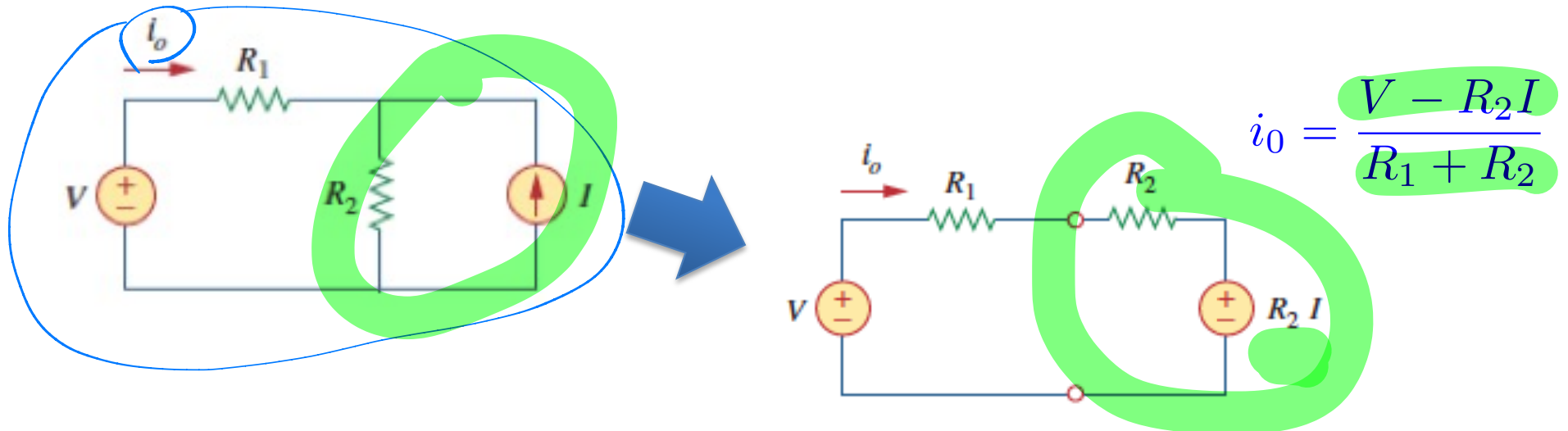– Utility: ~~simplify~~ simplify circuit for quick analysis



$$i_o = \frac{V - R_2 I}{R_1 + R_2}$$

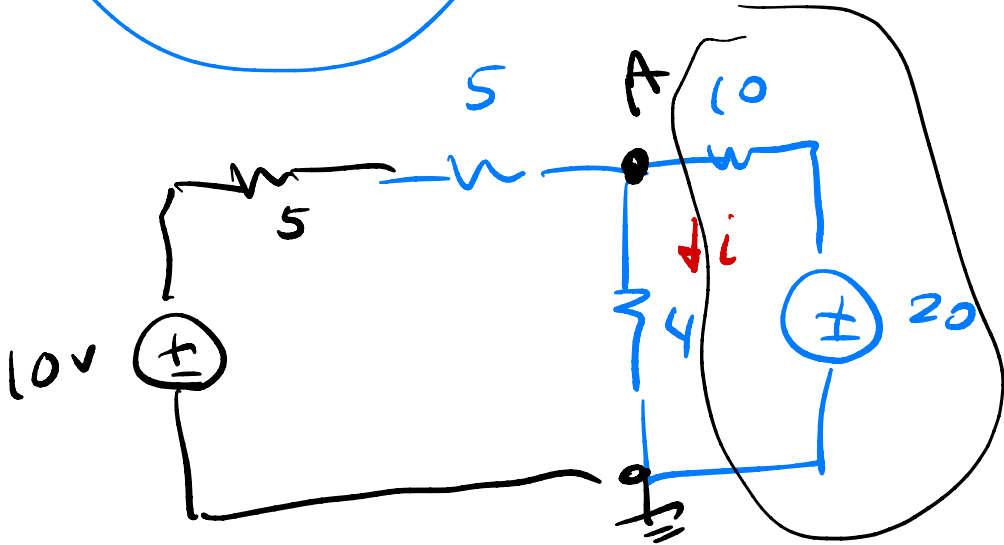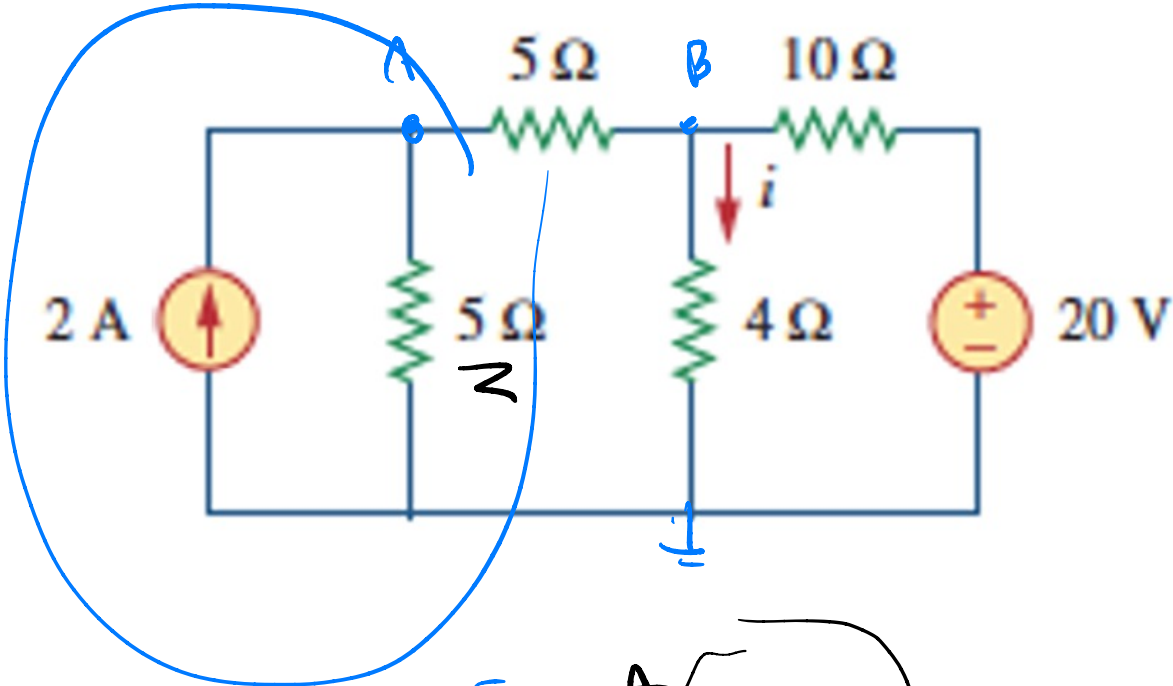
**Example:** find  $i$  (convert to just one node)



$$\frac{A}{9} + \frac{A - 20}{10} = 0$$

1.67 A


**Example:** find  $i_x(t)$

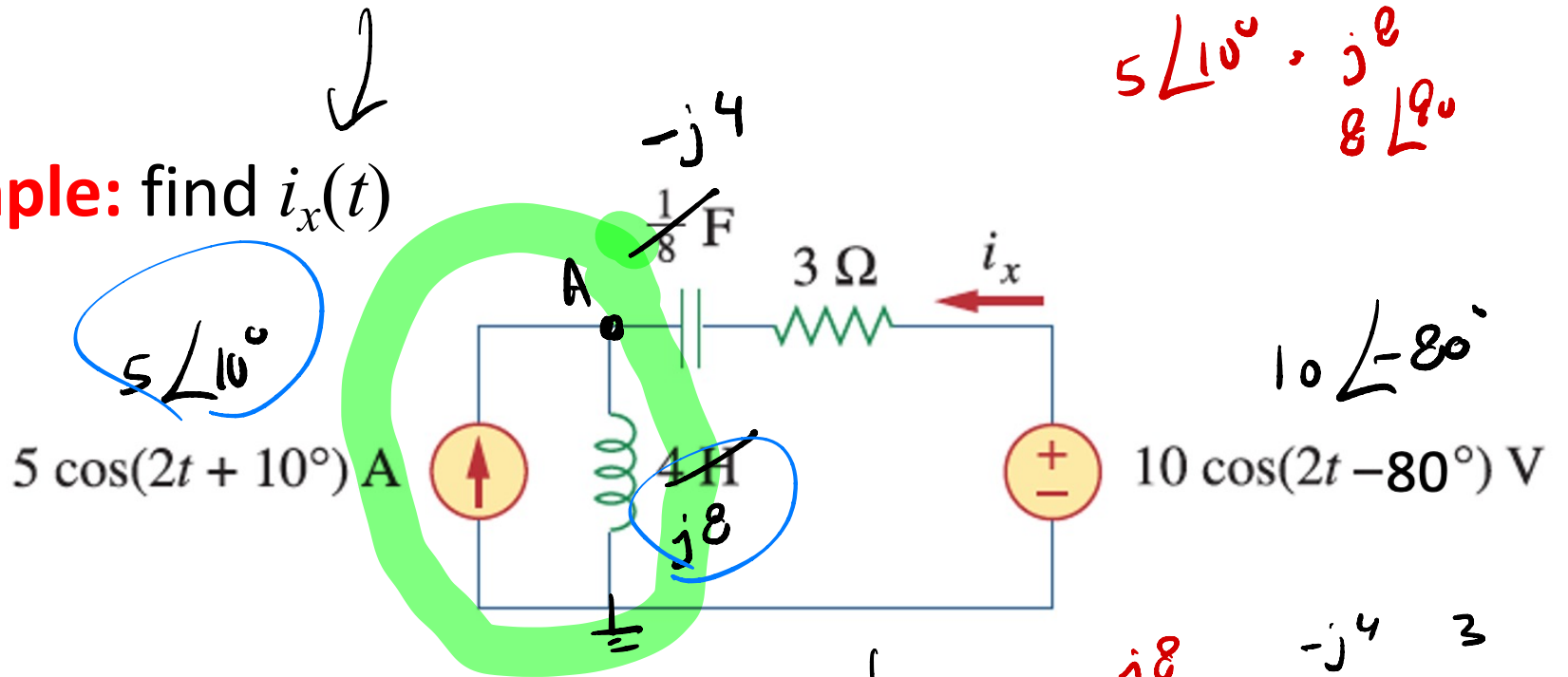

$$\frac{A}{j8} + \frac{A - 10\angle 80}{3 - j4} - 5\angle 10 = 0$$


$$A = \dots$$

$$I = \frac{10\angle -80 - A}{3 - j4}$$

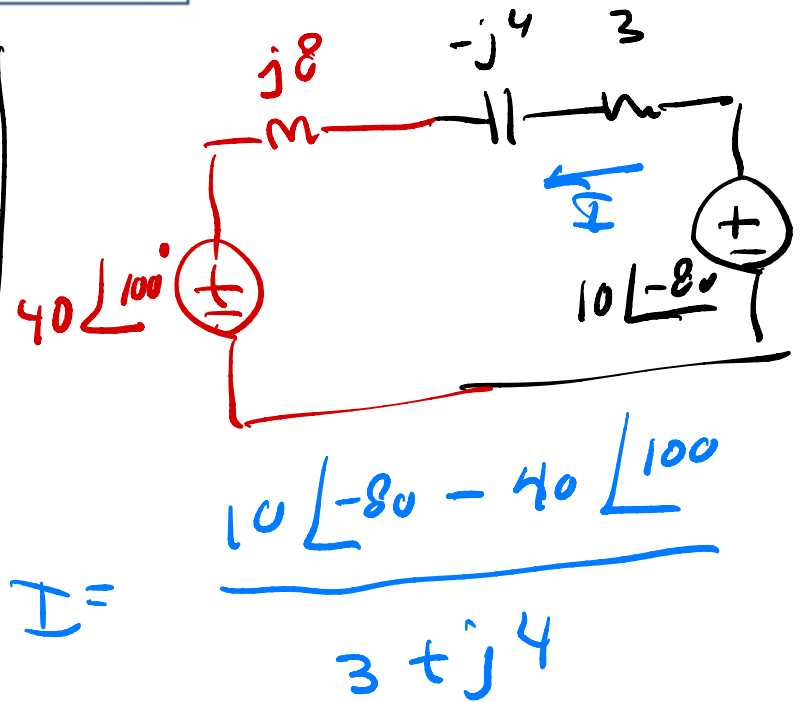


$$i_x(t) = 10 \cos(2t + 174^\circ) \text{ V}$$



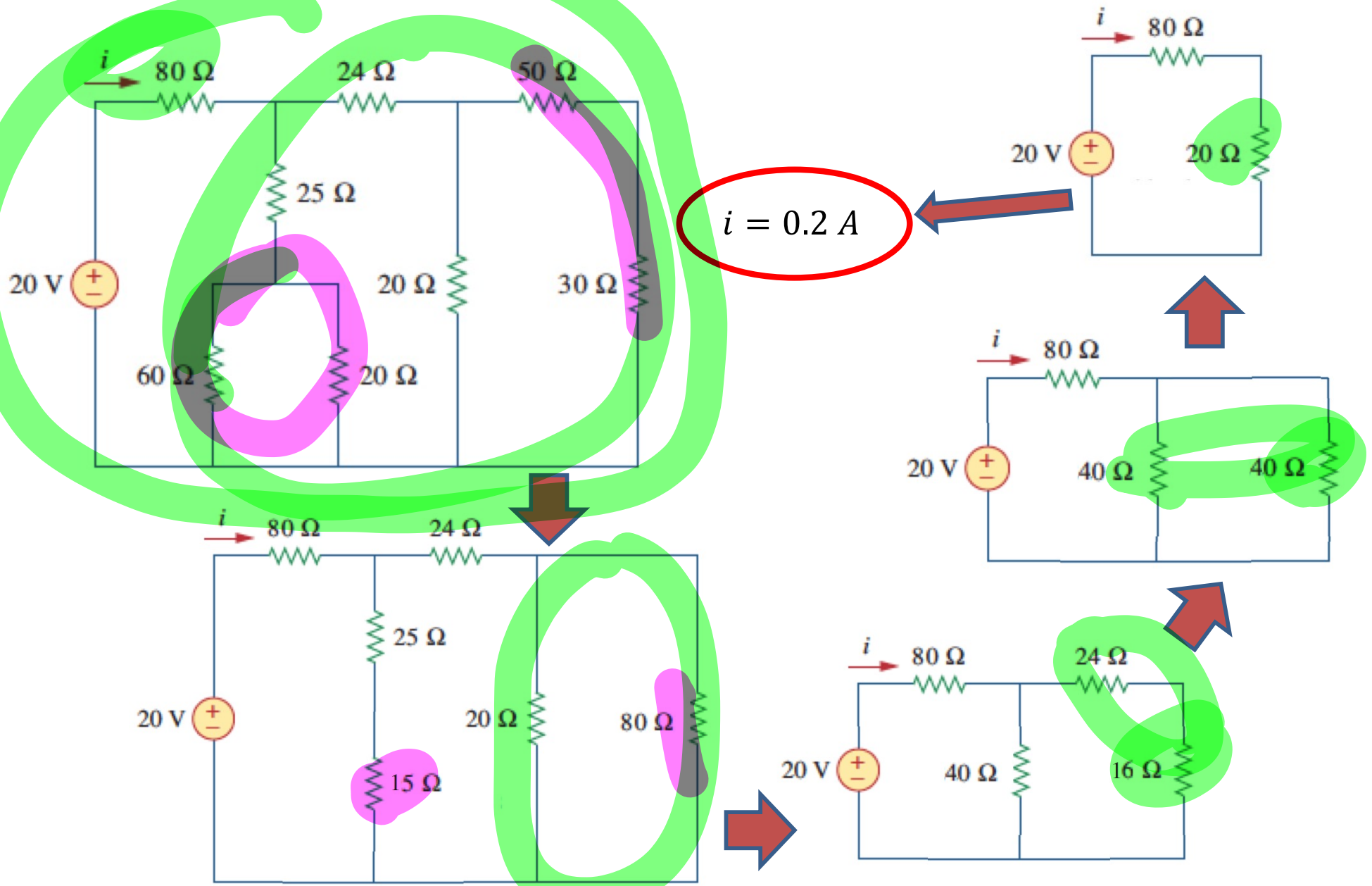
- To find  $i$ , recall series/parallel combining:






- What if there was a source present?


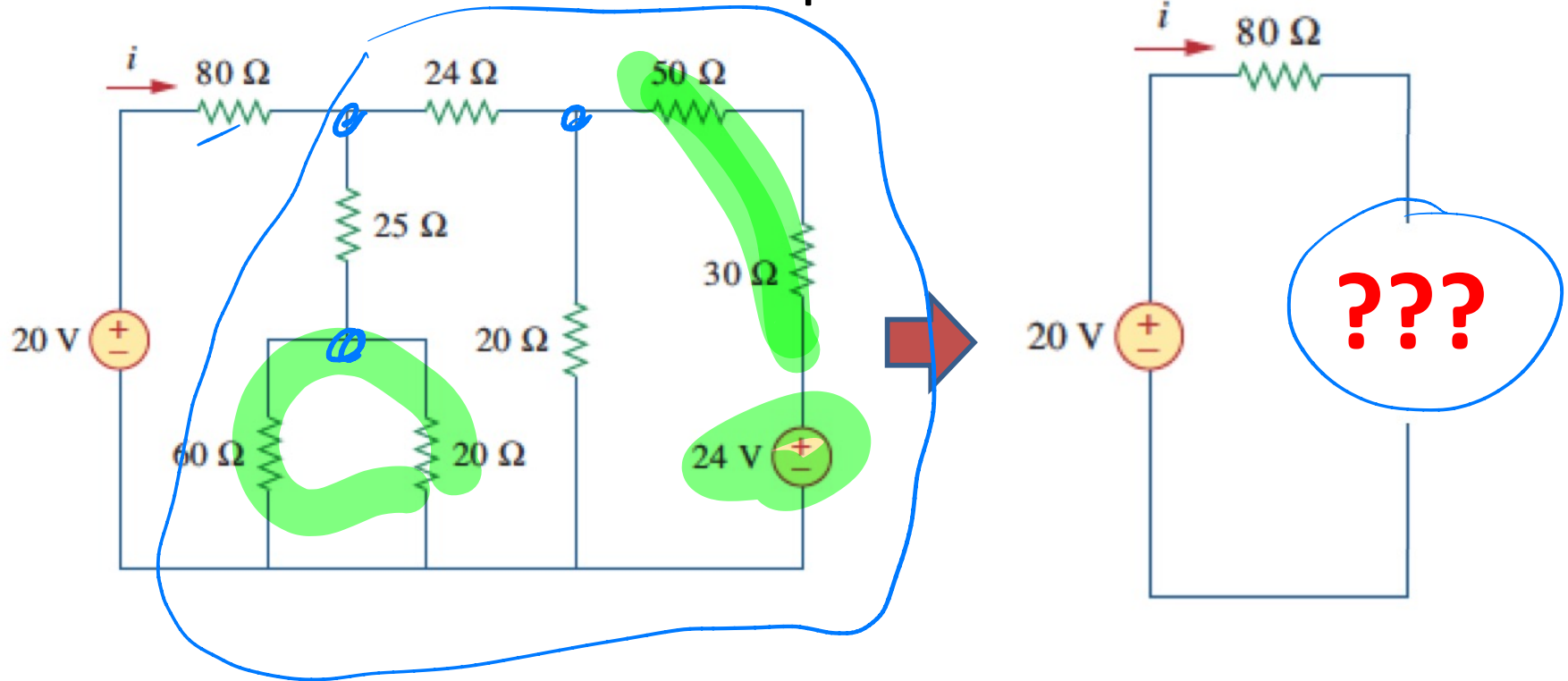


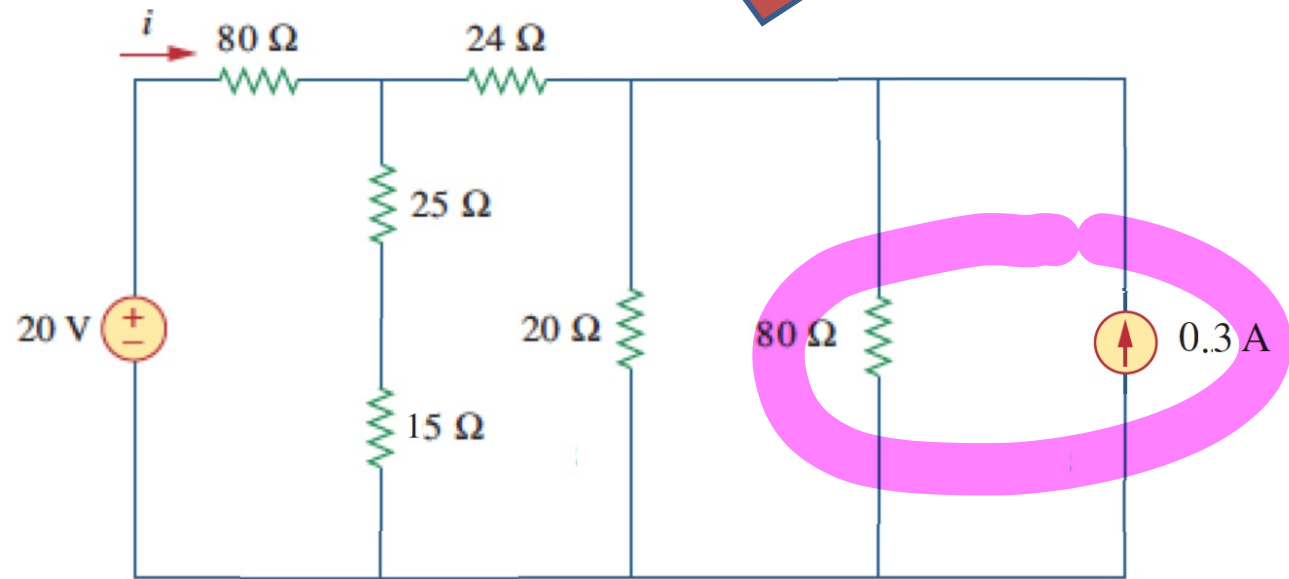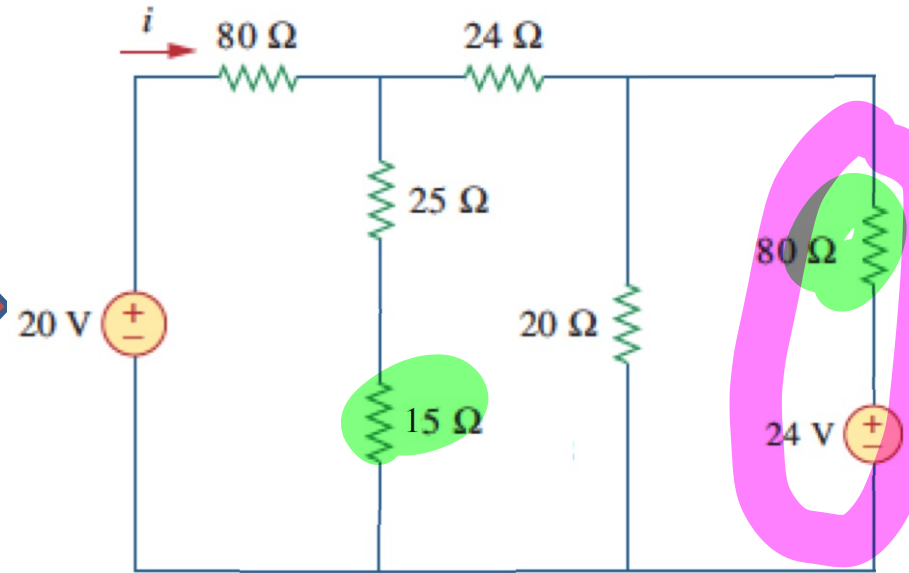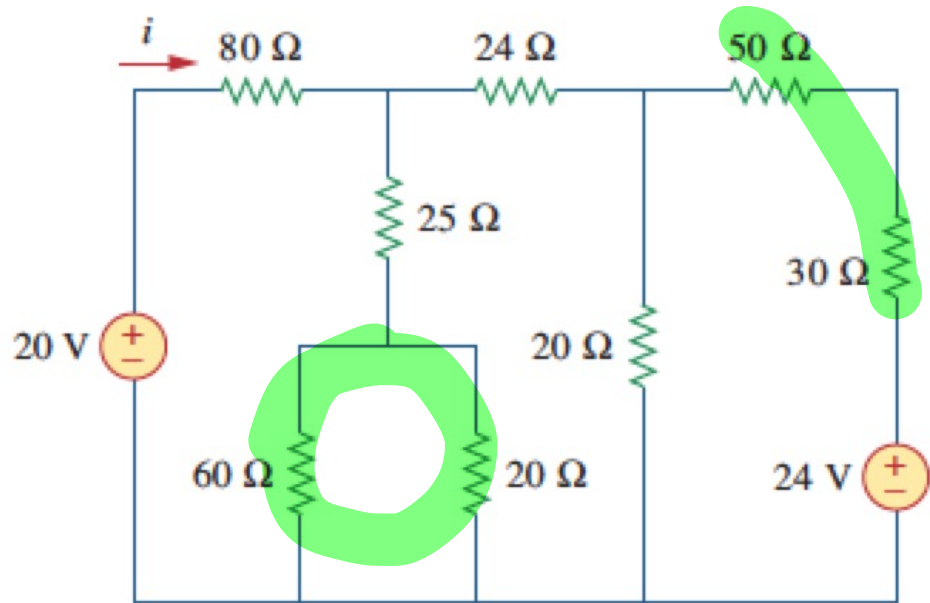- Can combine transformations with series/parallel combining








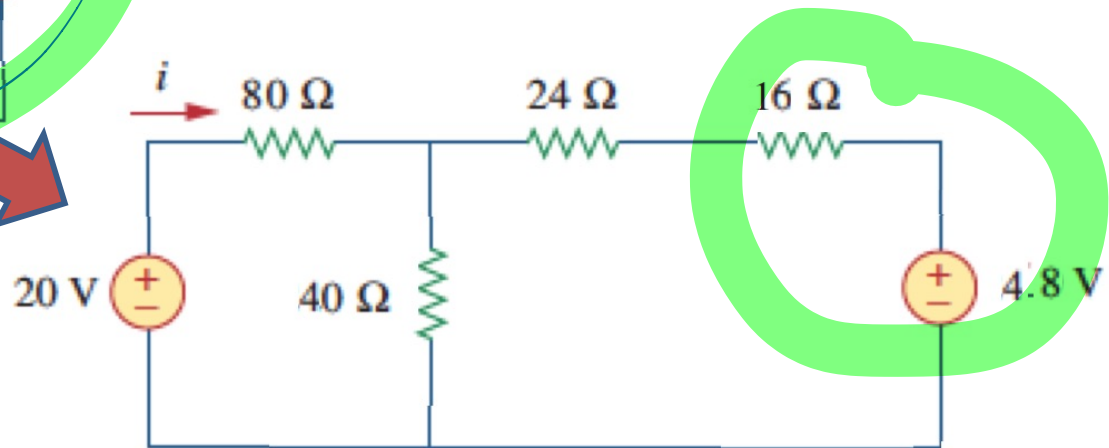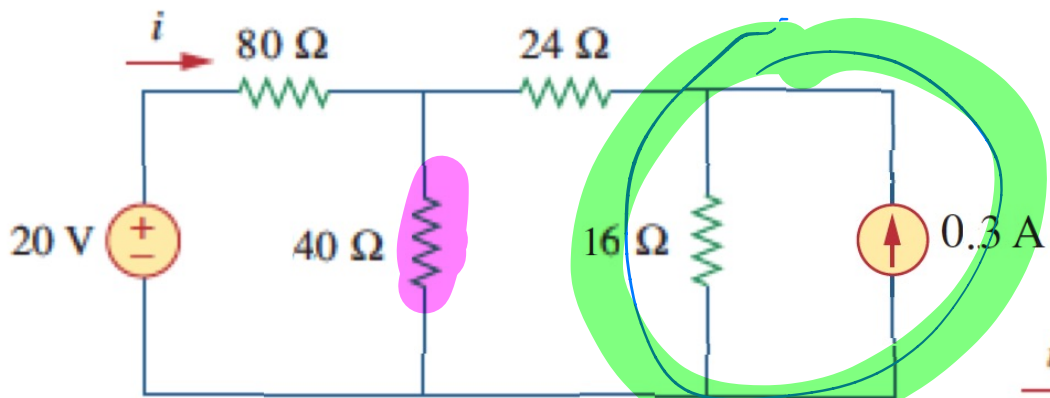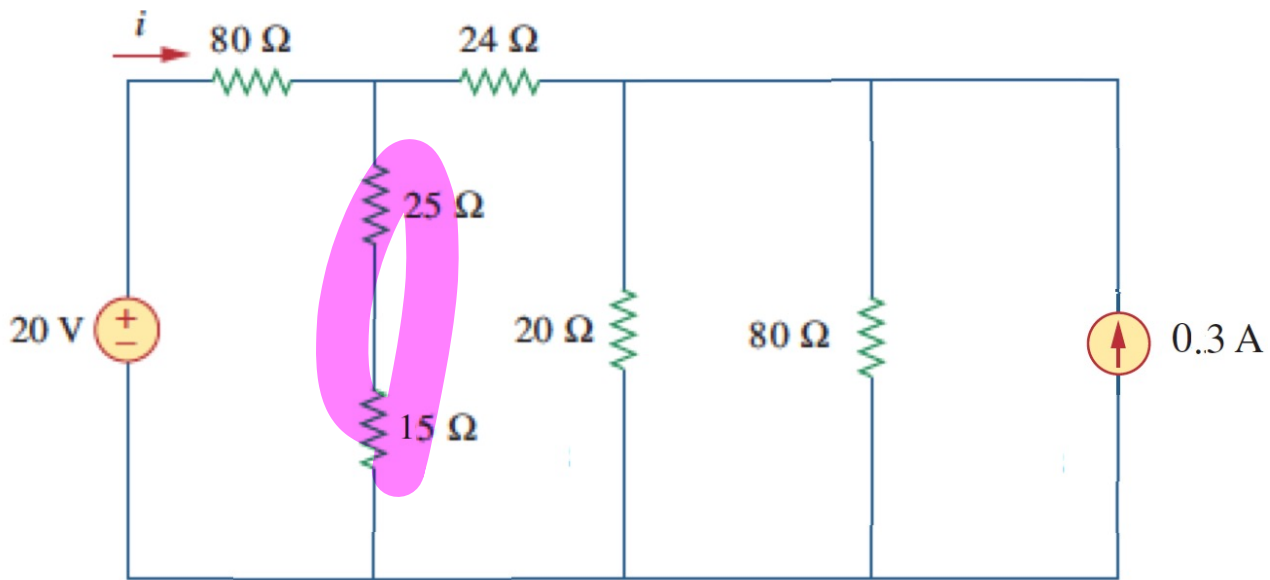


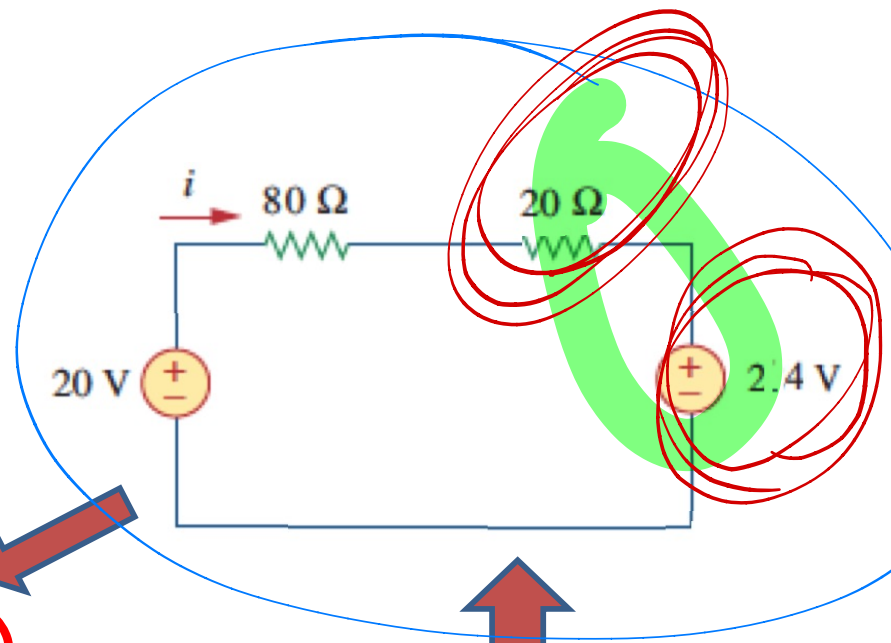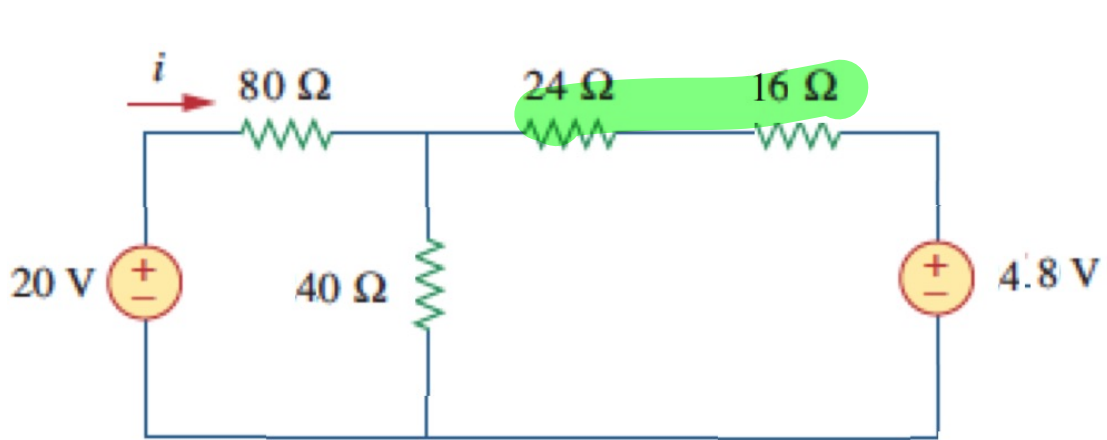

$i = 0.176\ \text{A}$

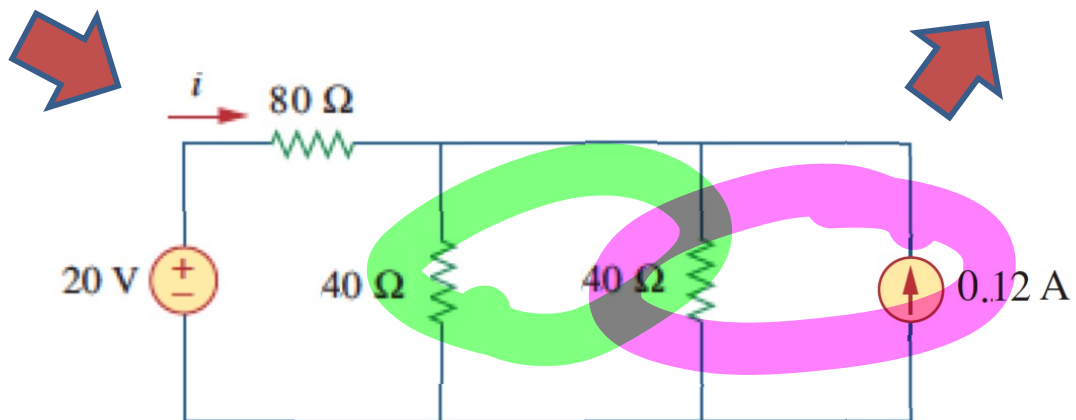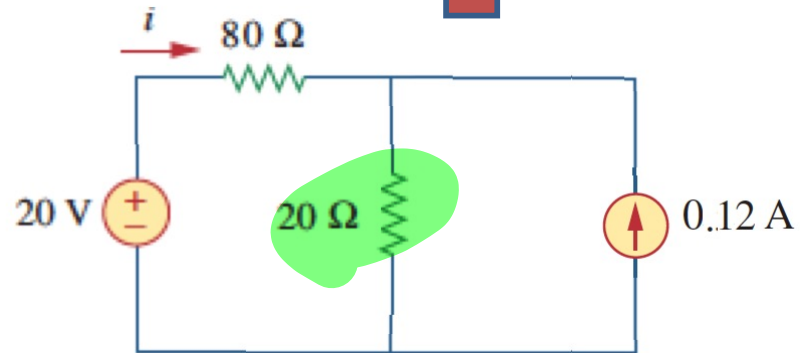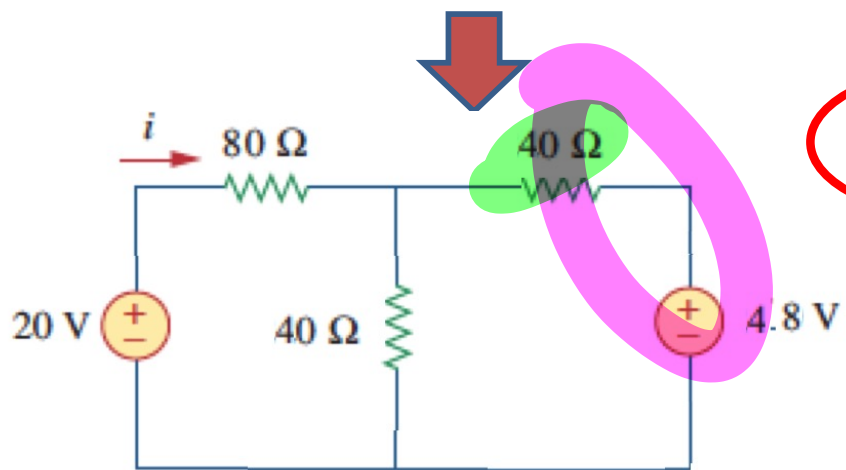


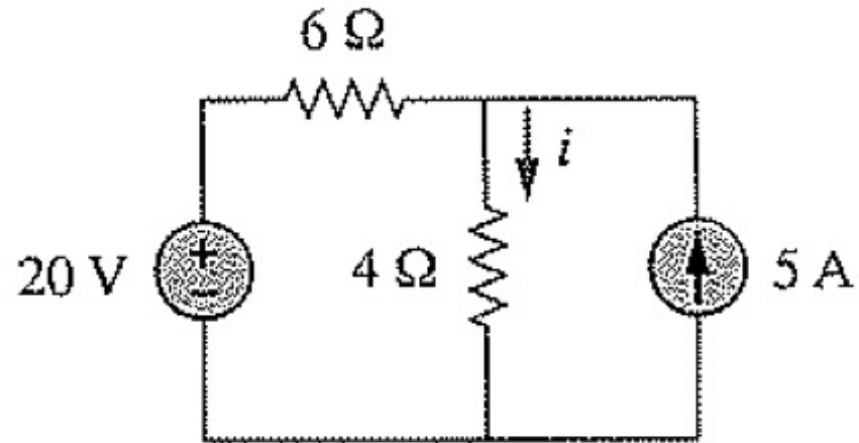**Example:** find  $i$  (convert to parallel current sources and then current division)




$$i = 5 A$$

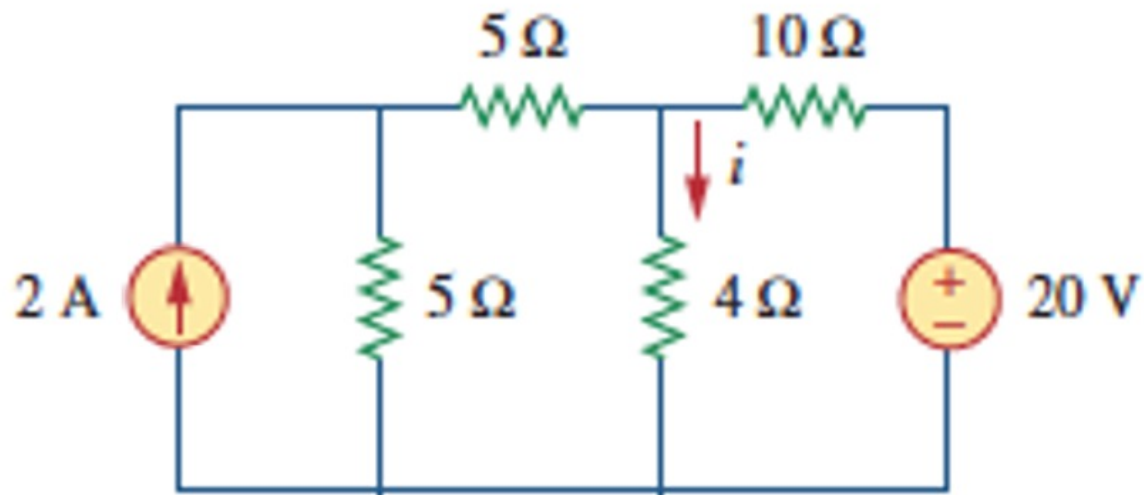**Example from above:** find  $i$  (use current division)







**Example:** find  $i_{\Delta}$

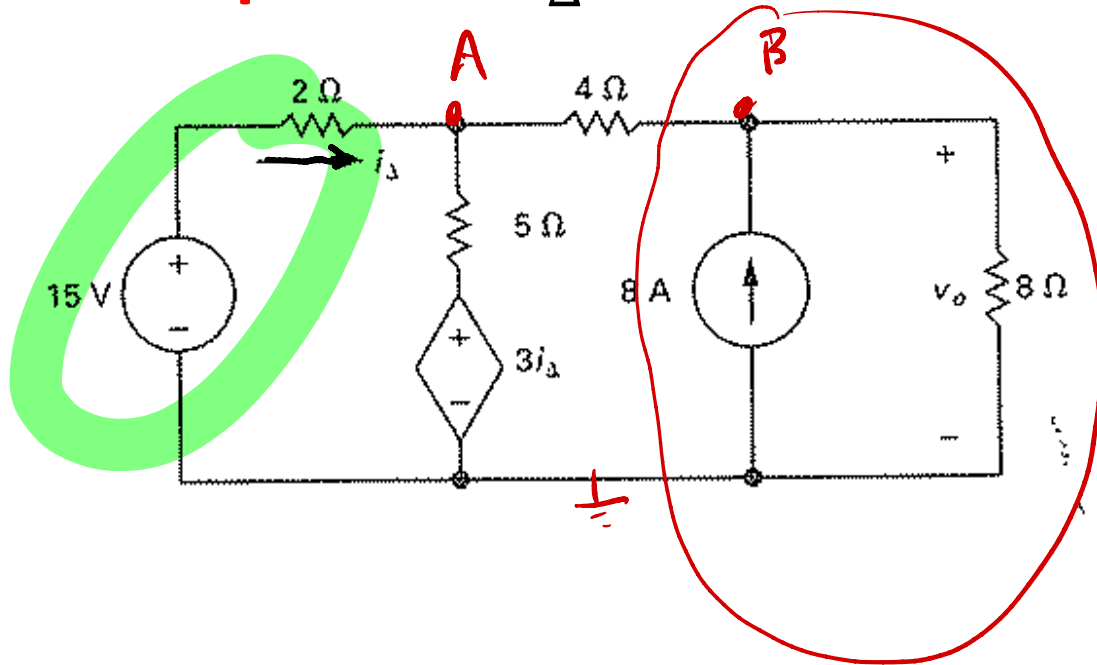


$$\frac{A-15}{2} + \frac{A-B}{4} + \frac{A-3i_{\Delta}}{5} = 0$$

$$\frac{B-A}{4} + \frac{B}{8} - 8 = 0$$

$$i_{\Delta} = \frac{15-A}{2}$$

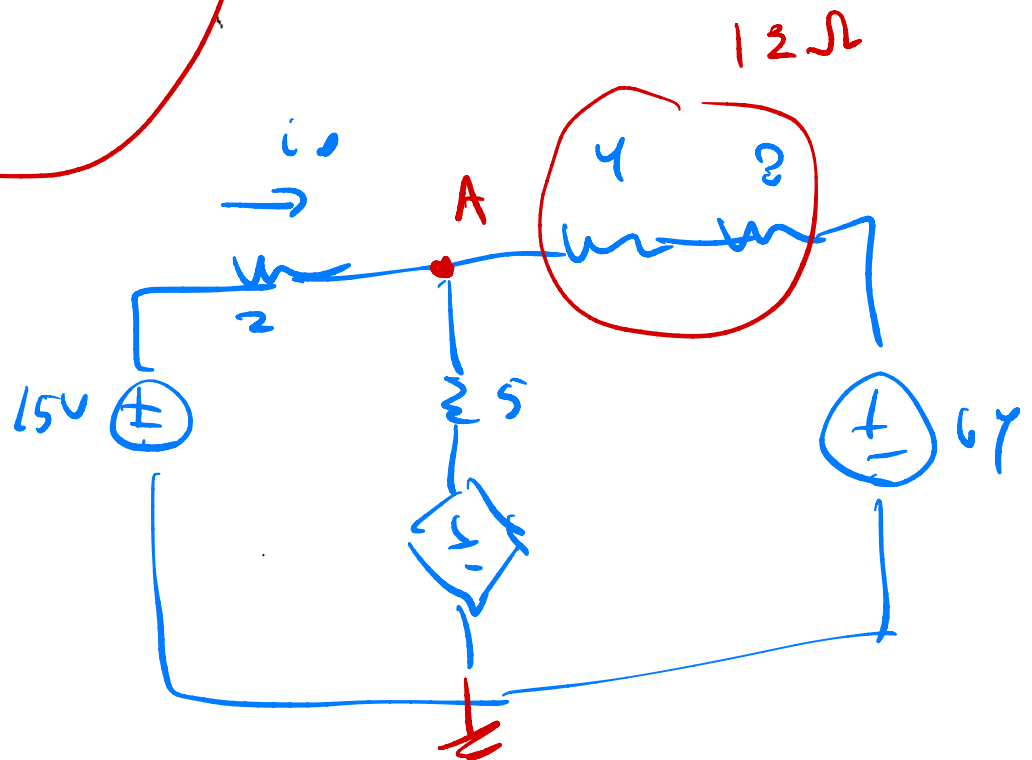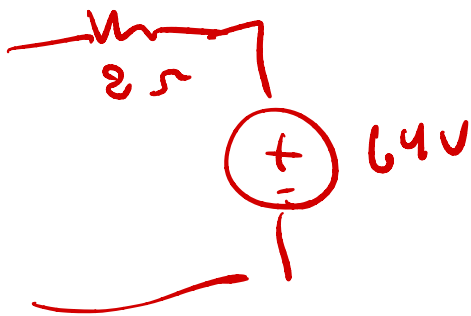


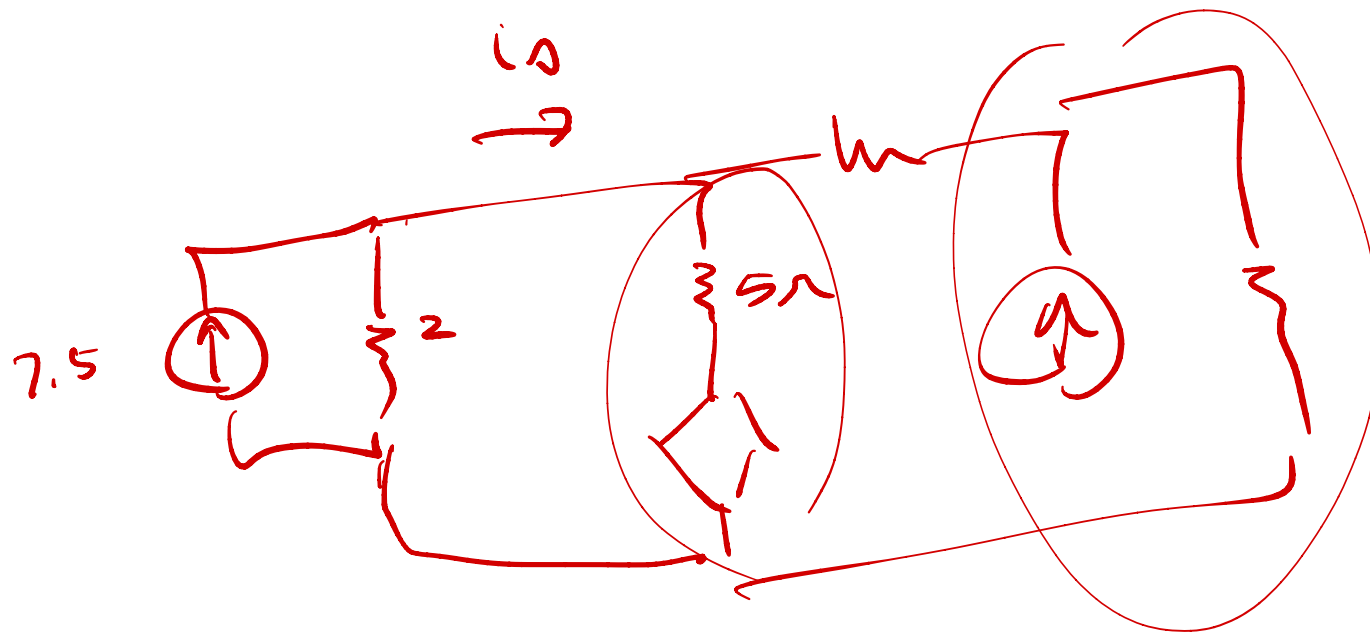

$$i_{\Delta} = \frac{223}{130} A$$

$$I = \frac{40 \angle 30^\circ}{5 + 3 + j\omega L + \frac{1}{j\omega C}}$$

**Example:** find  $i$

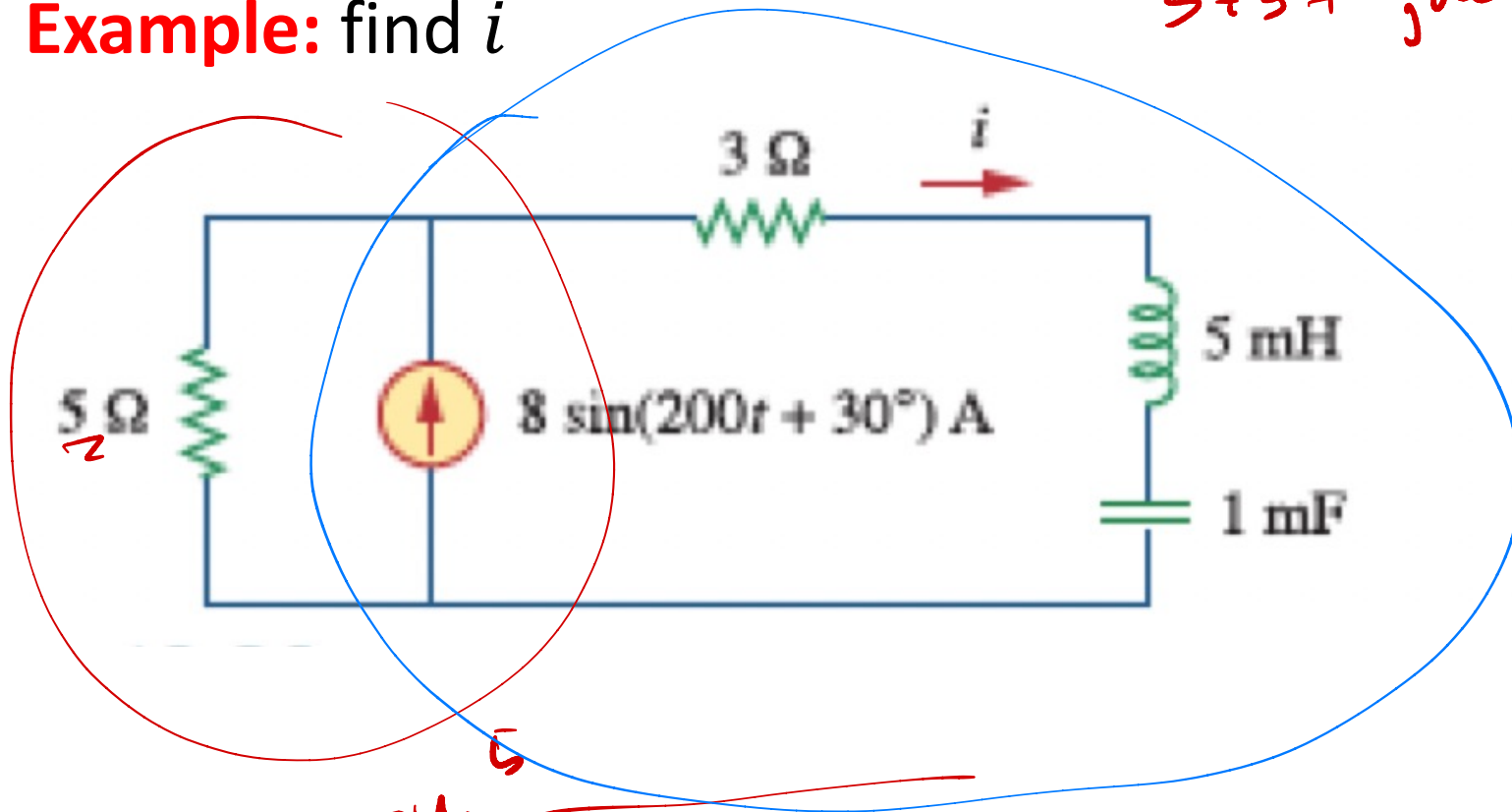


$\oplus$   $40 \cos(200t + 30^\circ) \text{ V}$



$$i(t) = 8.94 \cos(200t + 56.6^\circ) \text{ A}$$


**Practice problem:** find  $v_o$  and  $i_o$
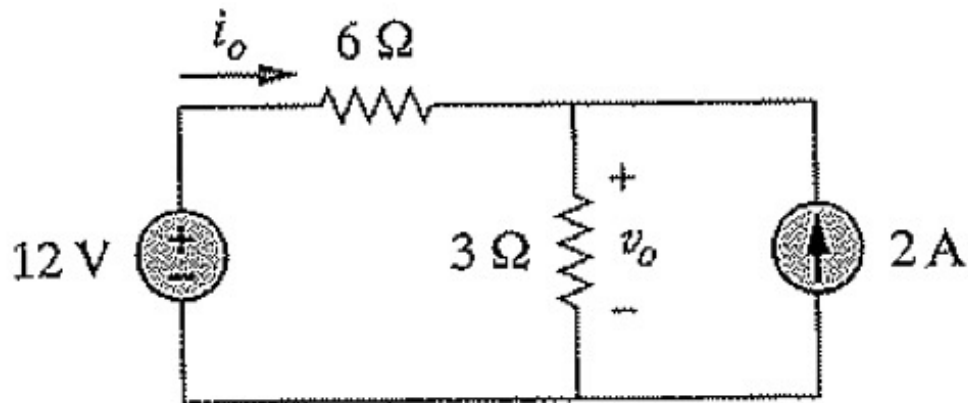
$$v_o = 8\text{ V}, \quad i_o = \frac{2}{3}\text{ A}$$




**Practice problem:** find  $i_o$

$$i_o = \frac{14}{3} \text{ A}$$

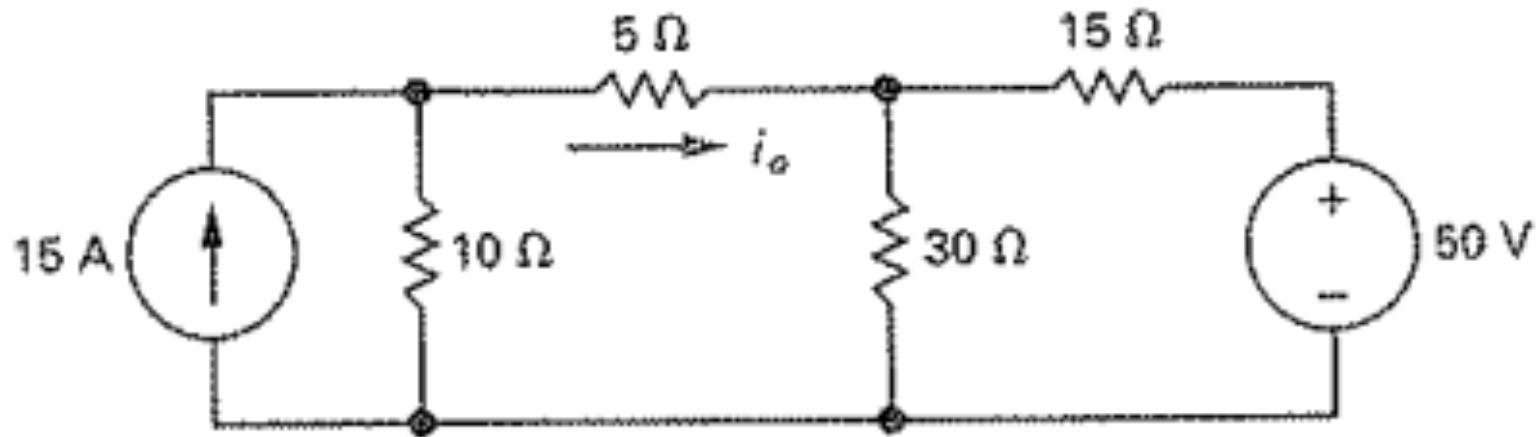


$$i_o = 1.79 \text{ A}$$

**Practice problem:** find  $i_o$

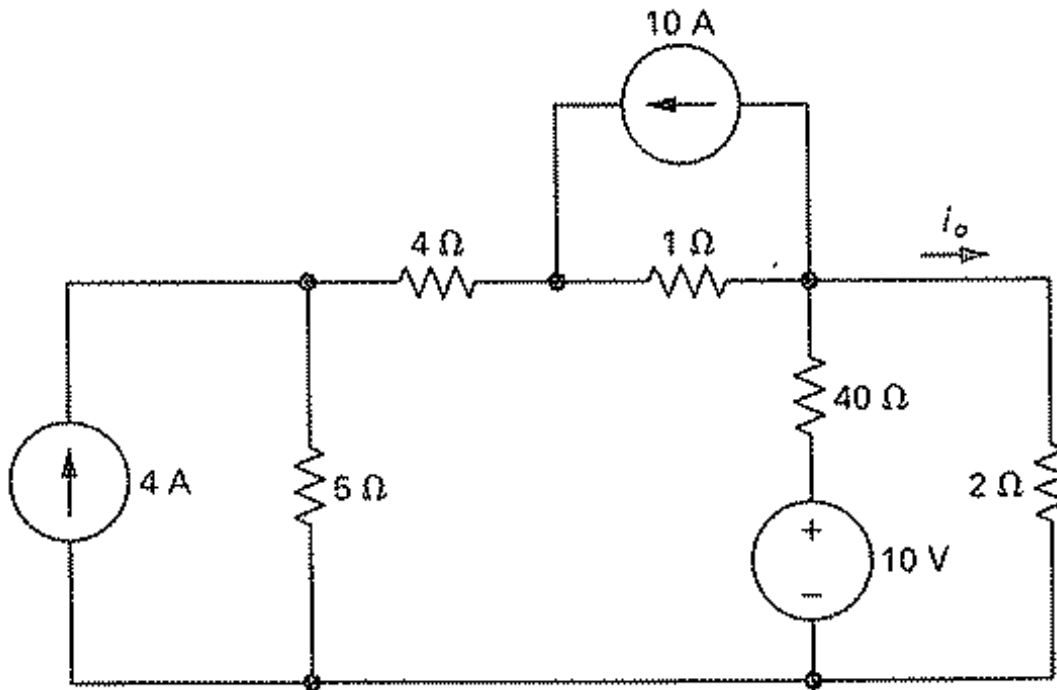

**Practice problem:** find  $v_o$

$$v_o = -11 V$$

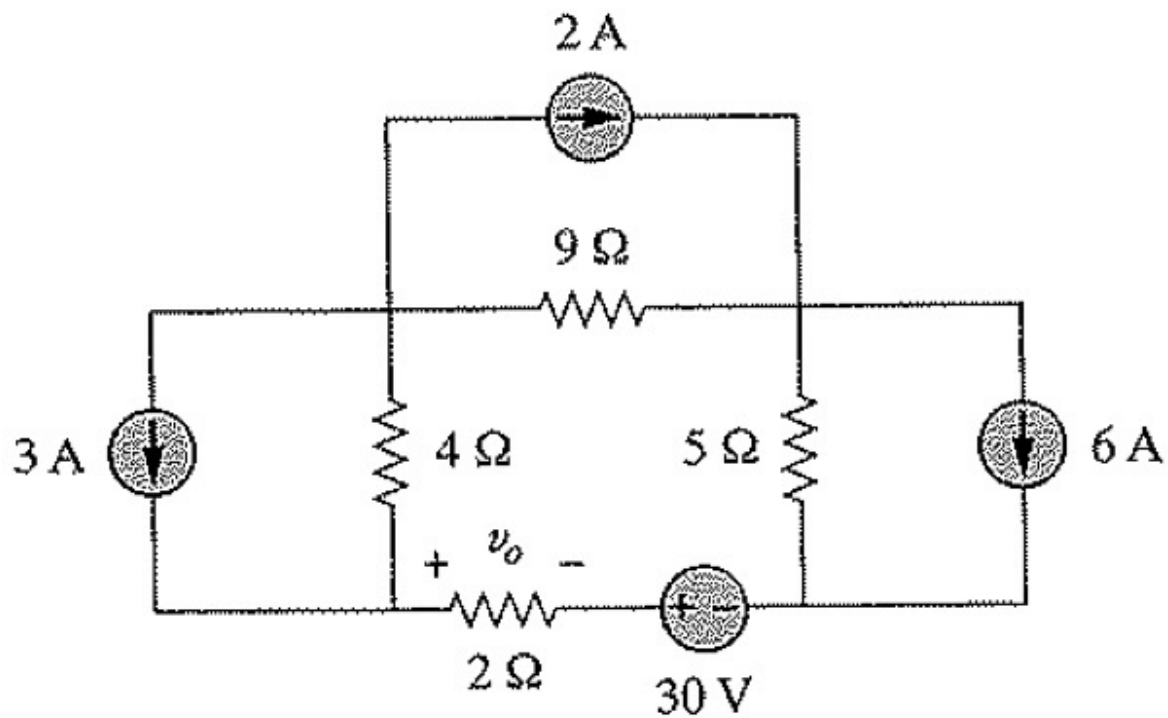

**Practice problem:** find  $v_x$  if  
 $= v_s(t) = 50 \cos(2t + 90^\circ) \text{ V}$   
and  $i_s(t) = 12 \cos(2t + 10^\circ) \text{ A}$

$$v_x(t) = 129 \cos(2t + 28.76^\circ) \text{ V}$$

