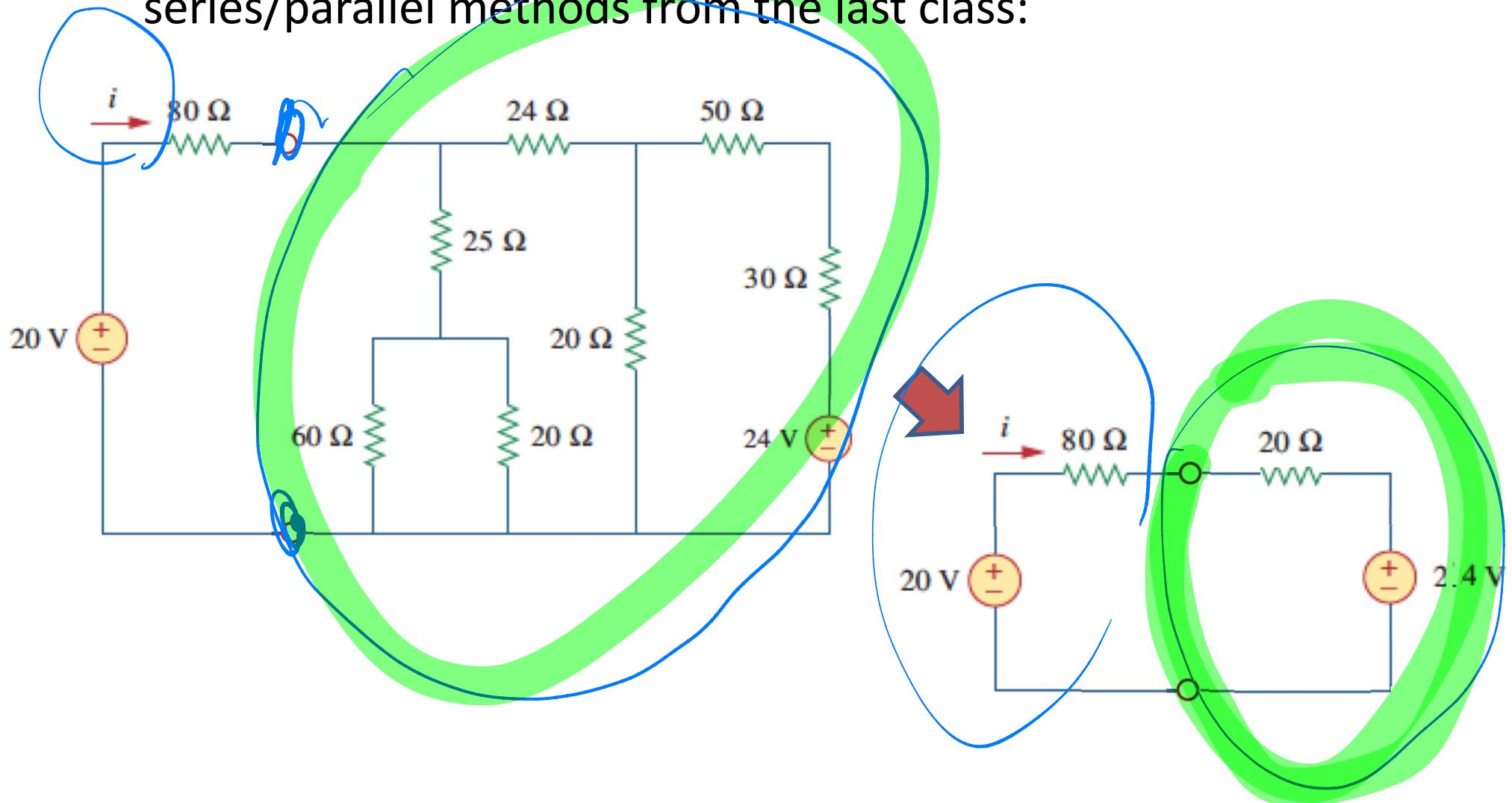


Theorems – 2

Thévenin

Thévenin Models



- Application – recall combining transformations and series/parallel methods from the last class:





Thévenin equivalent circuit \equiv electrical equivalence at any pair of terminals

- 2 parameters:

- V_{Th}
 - R_{Th}

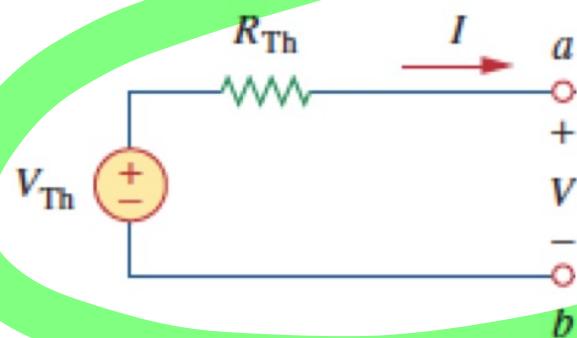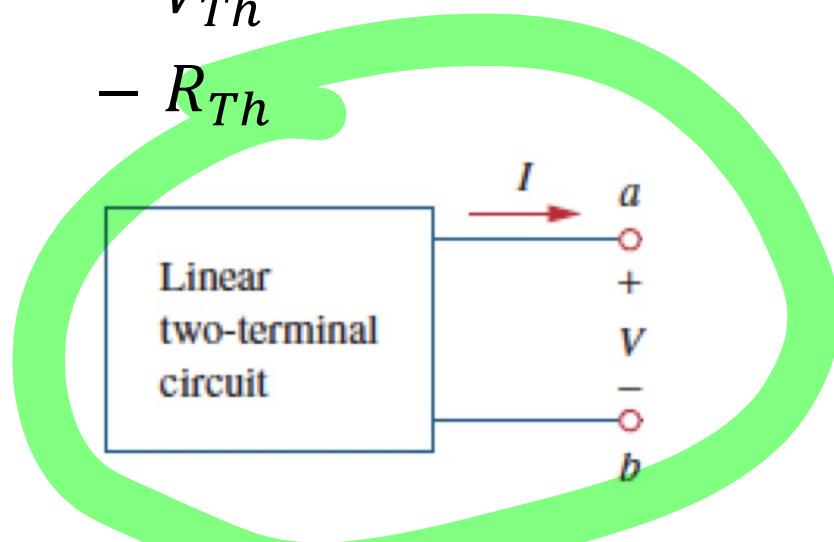


- Example:

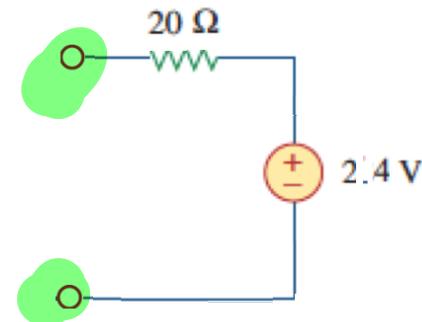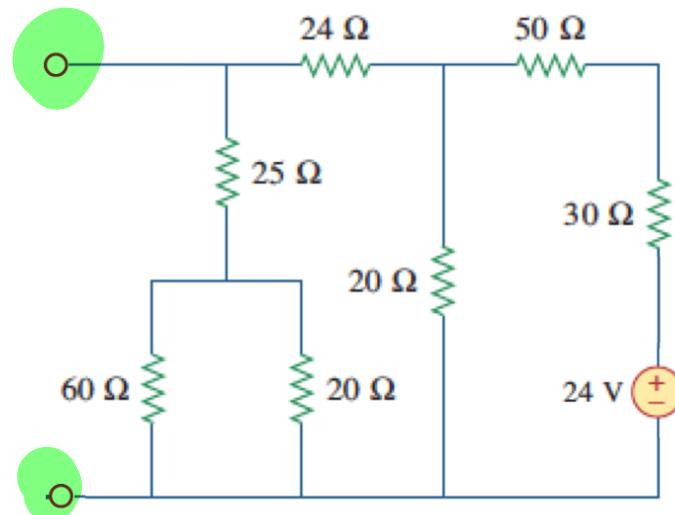


How to find V_{Th} and R_{Th} ?

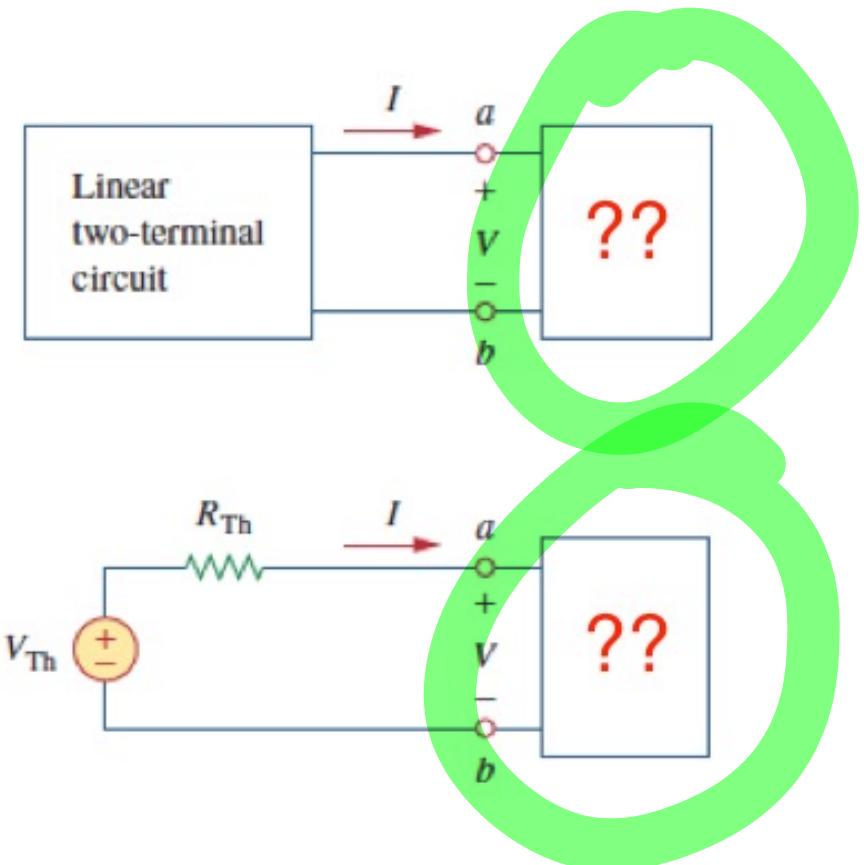- Concept: both the circuit and the model should behave the same way **no matter what** is connected at $a-b$
 - With only 2 variables in the model, we need only check **2** load situations
 - Need only match one of the V or I variables in each




Thevenin: Most Common Approach

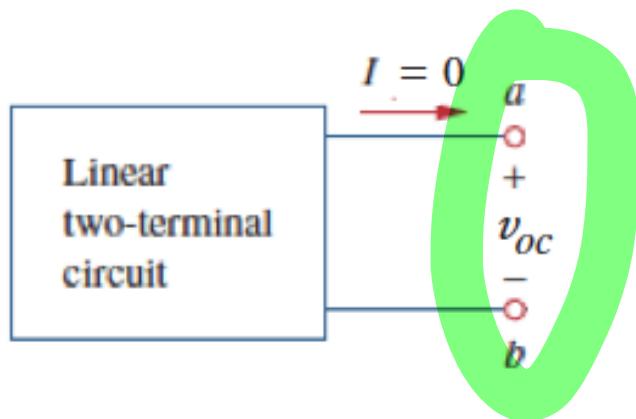- Connect nothing – “open circuit” test
 - Just need a voltmeter




Clearly

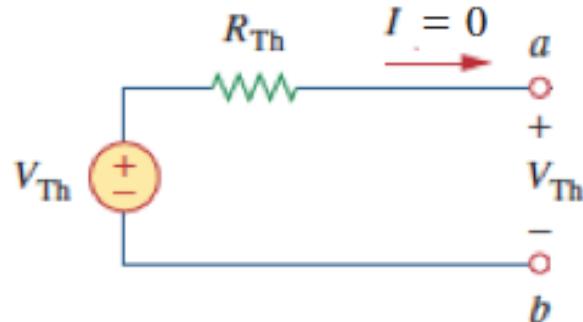

$$V_{Th} = V_{oc}$$


Another popular approach

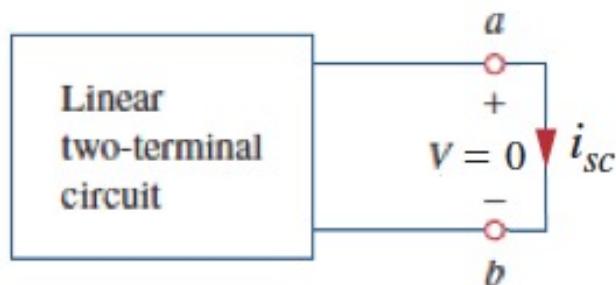- Connect a wire – “short circuit” test
 - Popular for paper analysis



$$i_{SC} = \frac{V_{Th}}{R_{Th}}$$

So

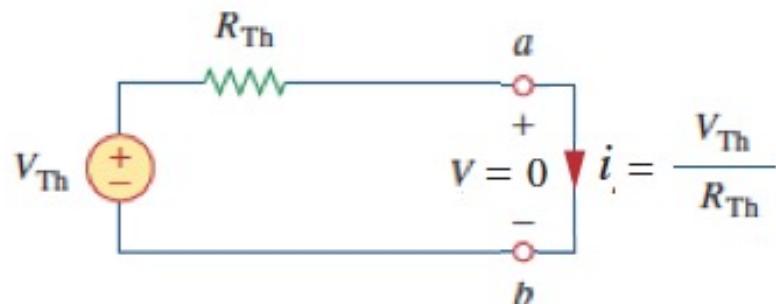


$$R_{Th} = \frac{V_{Th}}{i_{SC}} = \frac{V_{OC}}{i_{SC}}$$

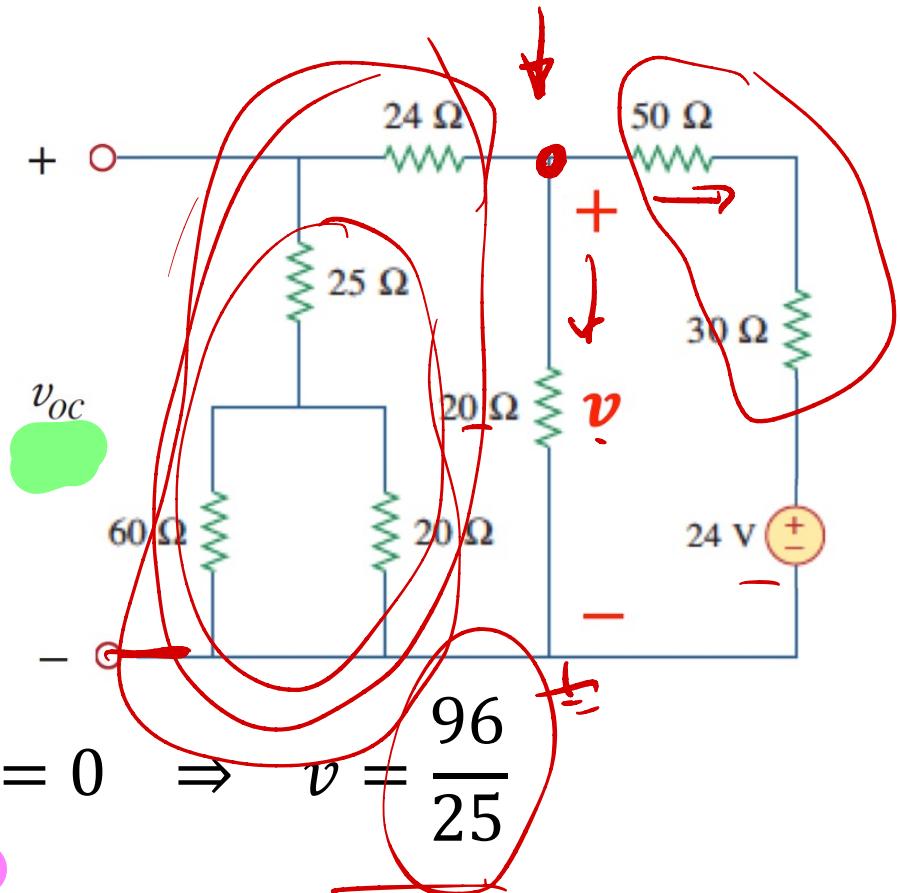Example:

- Use node analysis:

$$\frac{v}{20} + \frac{v - 24}{80} + \frac{v}{64} = 0$$




- Then voltage division:

$$v_{oc} = \frac{40}{64}v \Rightarrow V_{Th} = v_{oc} = 2.4 \text{ volts}$$

Note how the short changes the circuit

- Use node analysis:


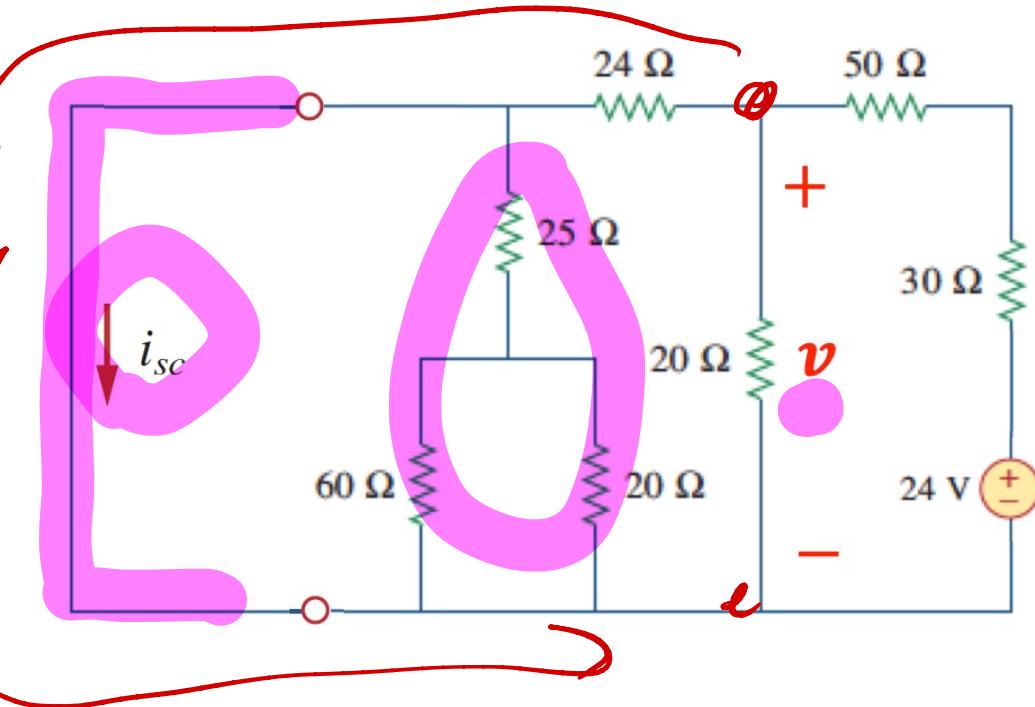


$$\frac{v}{20} + \frac{v - 24}{80} + \frac{v}{24} = 0 \Rightarrow v = \frac{72}{25}$$



- Then Ohm's Law:

$$i_{sc} = \frac{v}{24} = 0.12 \Rightarrow R_{Th} = \frac{v_{oc}}{i_{sc}} = \frac{2.4}{0.12} = 20 \Omega$$

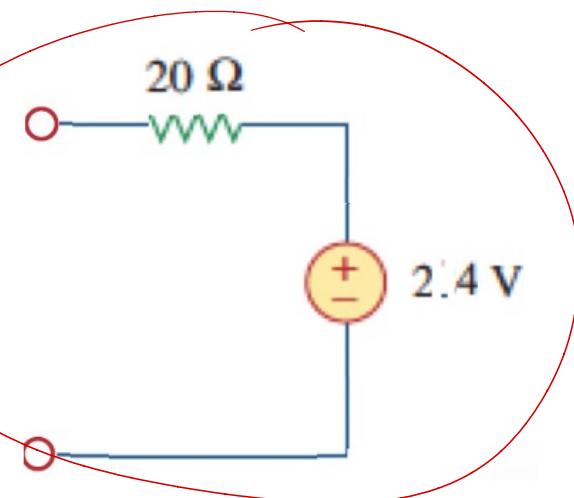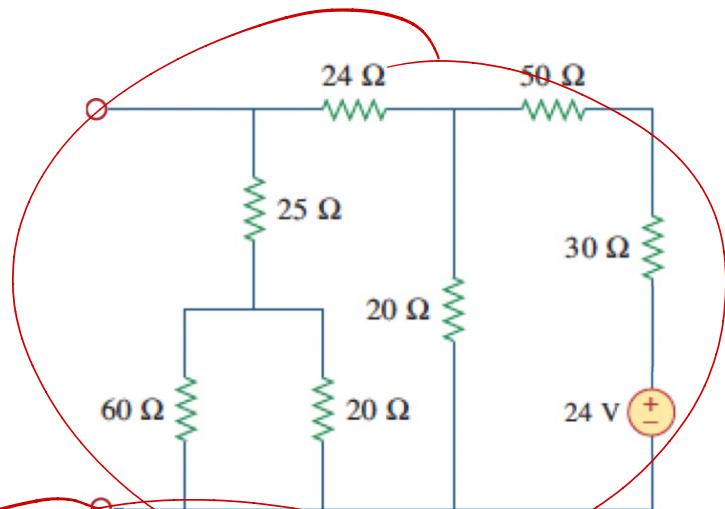So $V_{Th} = 2.4$ volts and $R_{Th} = 20 \Omega$




and

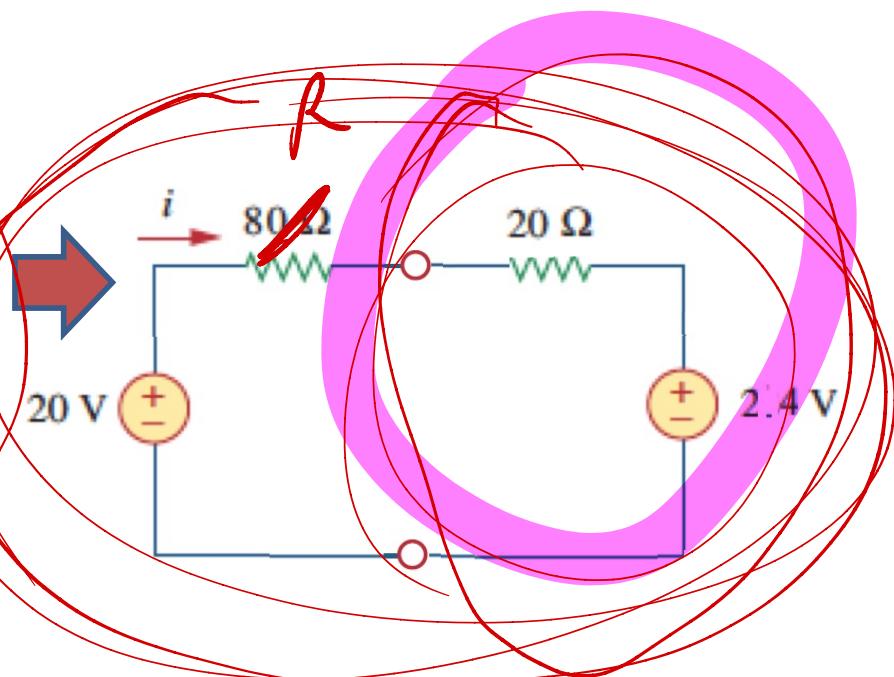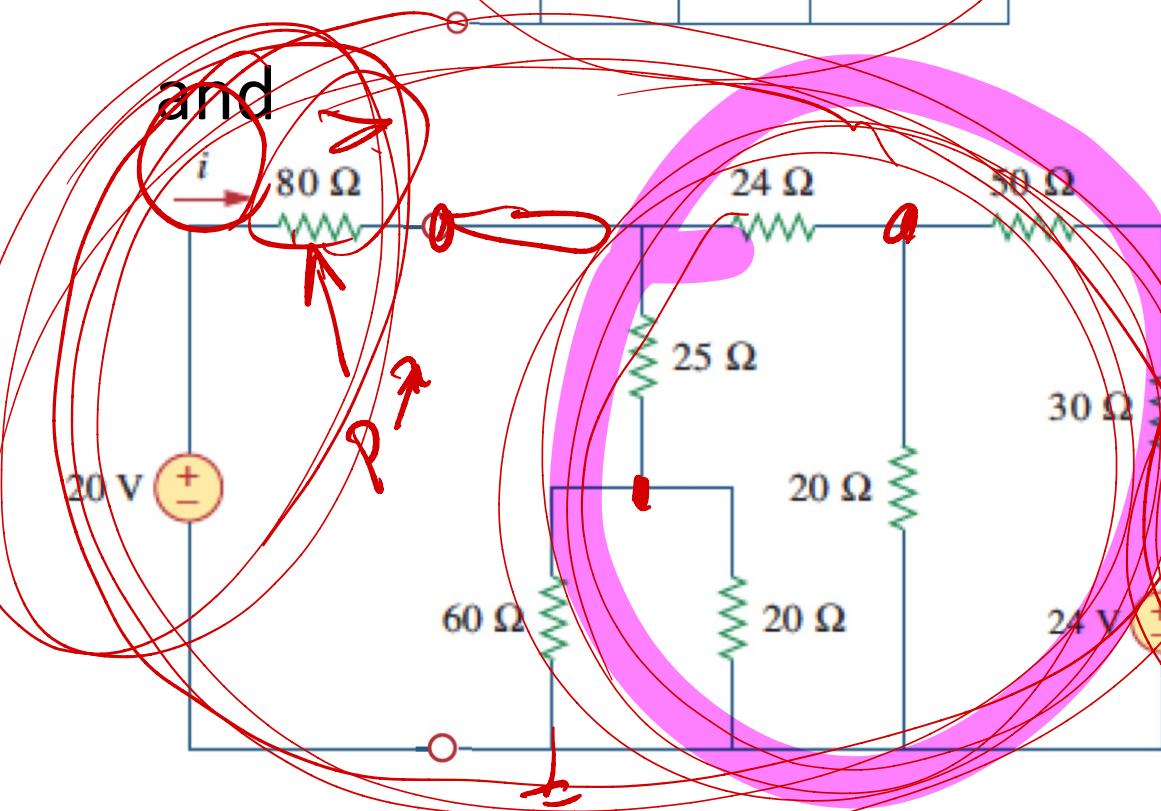

Example: find V_{th} and R_{Th}

$$V_{Th} = v_{OC}$$

$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$

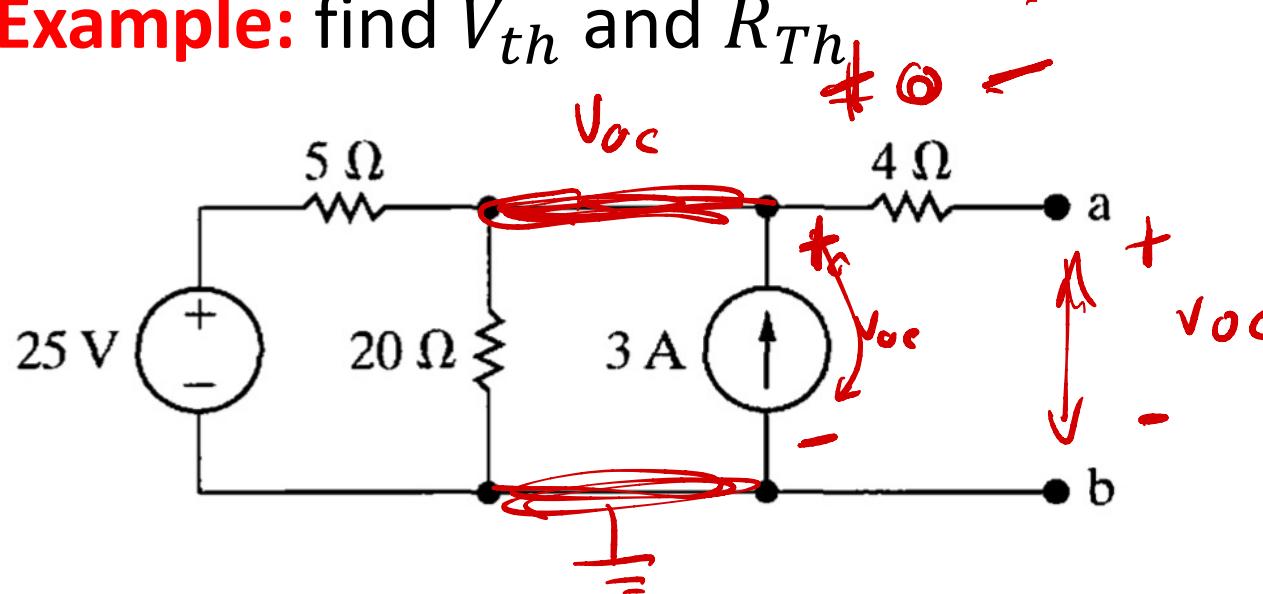


$$V_{Th} = 32V$$


$$25 \left(\frac{V_{OC}}{20} + \frac{V_{OC} - 25}{5} - 3 = 0 \right)$$

$$V_{OC} + 4V_{OC} - 100 - 60 = 0$$

$$5V_{OC} = 160$$

$$V_{OC} = 32V$$

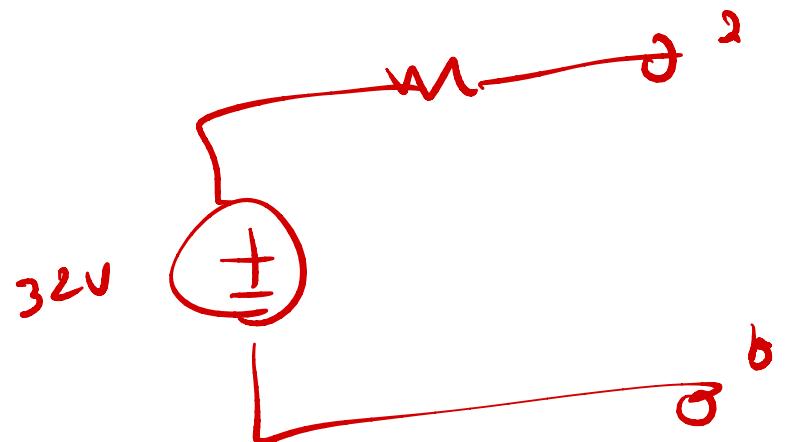

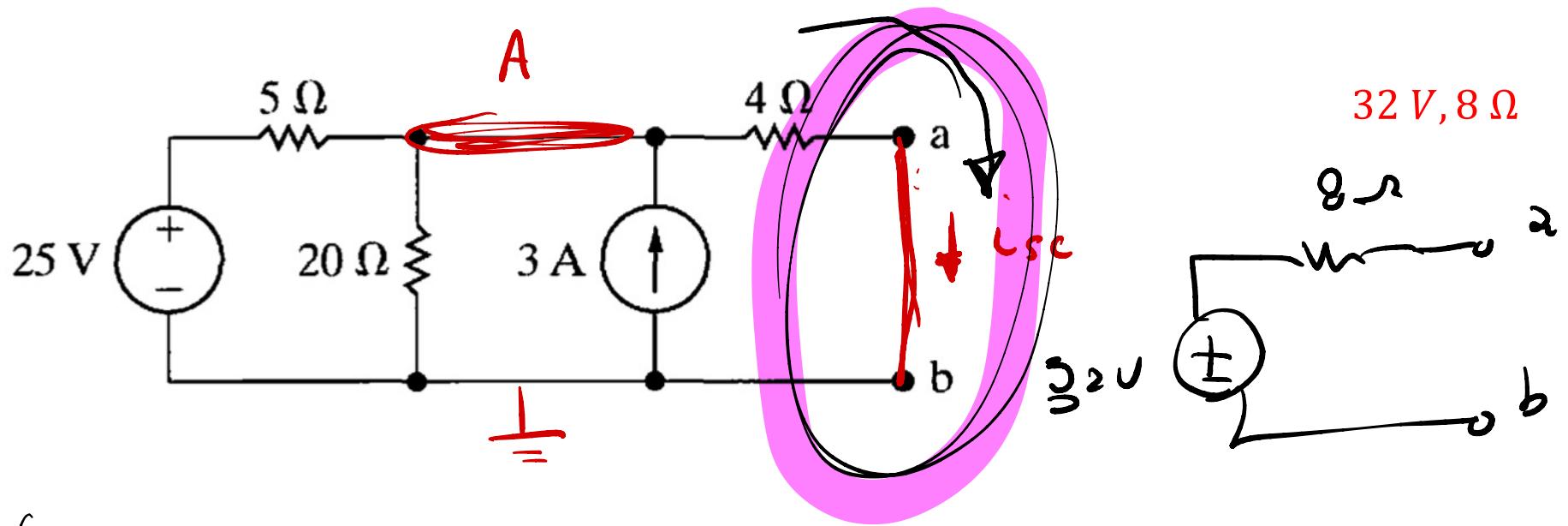

$$25 \left(\frac{A - 25}{5} + \frac{A}{20} - 3 + \frac{A}{4} \right) = 0$$

$$4A - 100 + 4A - 60 + 5A = 0$$

$$10A = 160$$

$$A = 16 \text{ A}$$

$$I_{SC} = \frac{16 \text{ V}}{8\Omega} = 4 \text{ A}$$



$$H = \frac{32}{R_{TH}}$$


$$R_{TH} = 8\Omega$$

Example: find V_{th} and R_{Th}


$$V_{Th} = v_{OC}$$

$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$

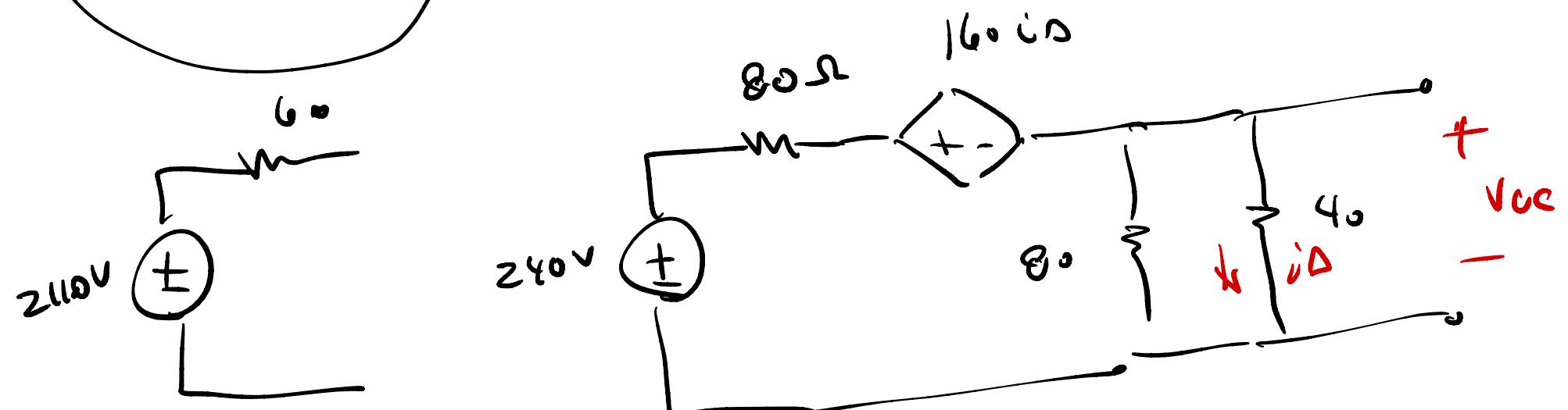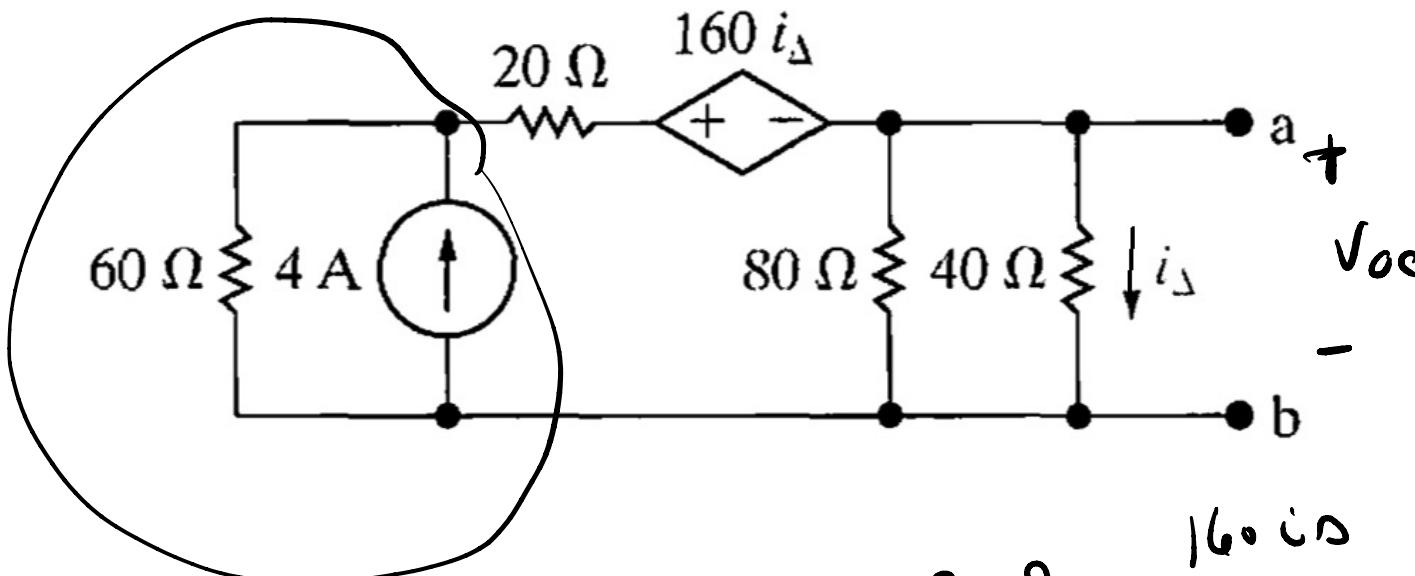

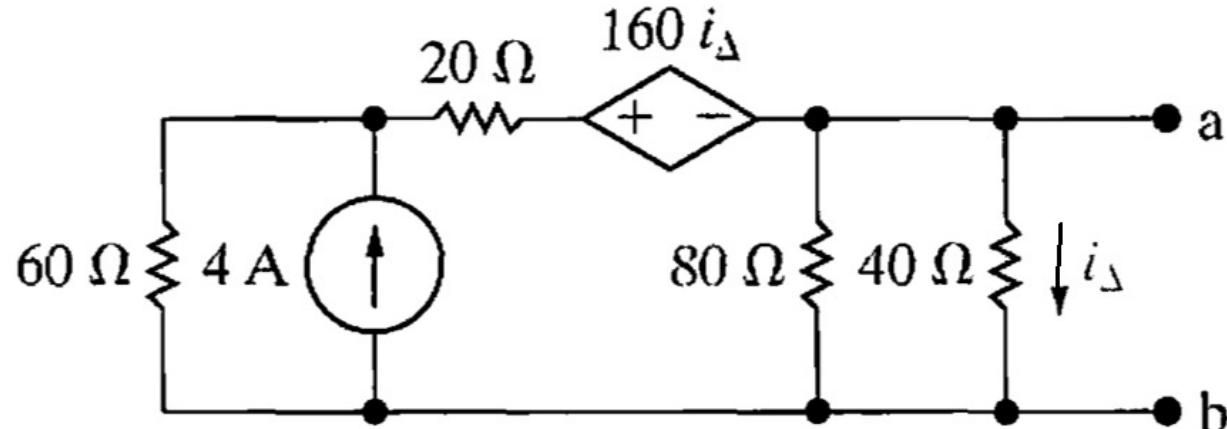

$30 \text{ V}, 10 \Omega$

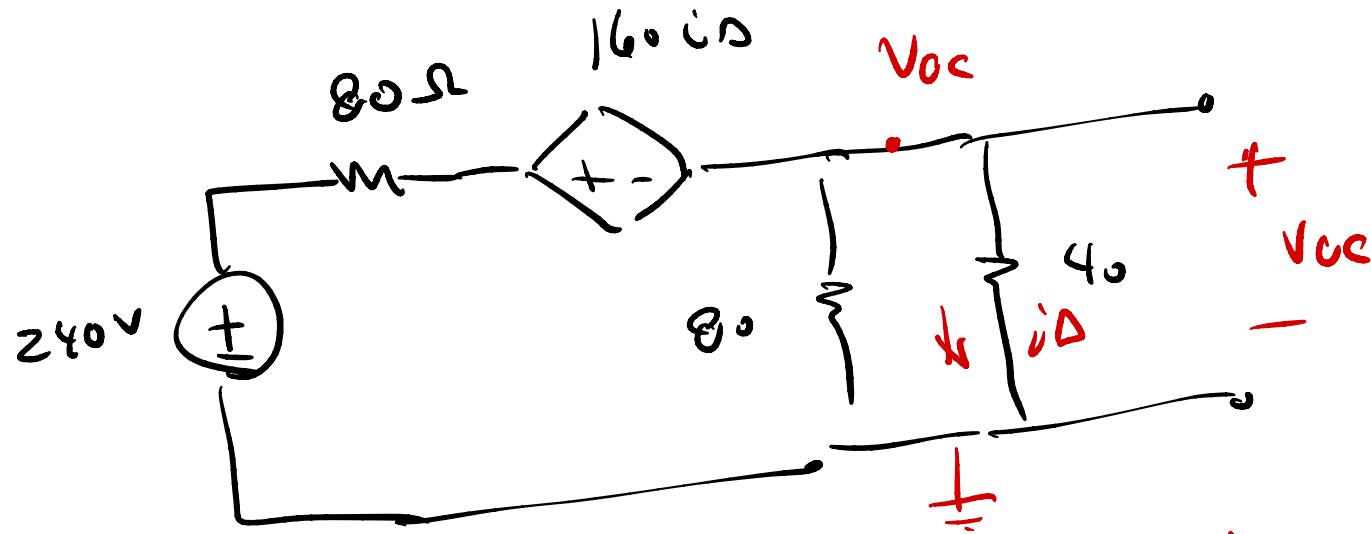 $V_{oc} = V_{+H}$


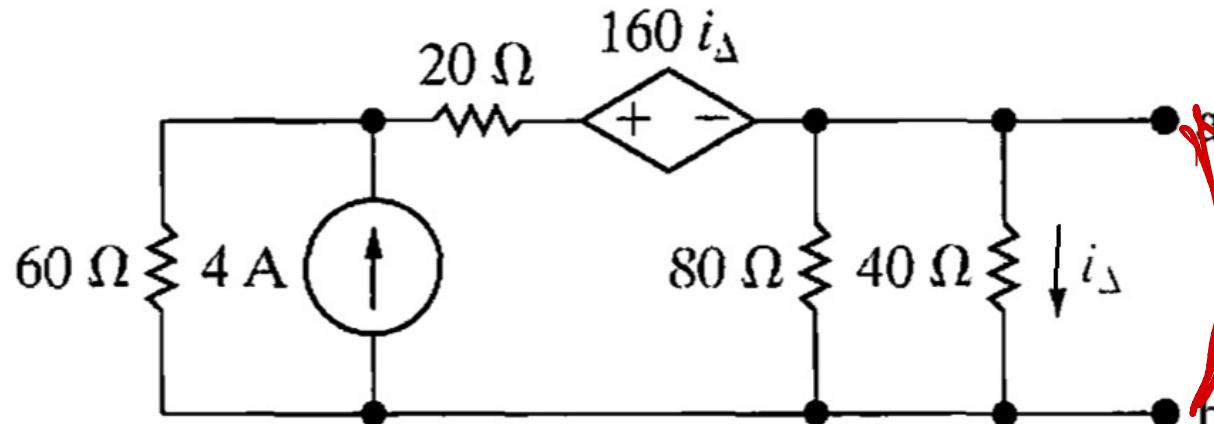
$$\frac{V_{oc}}{80} + \frac{V_{oc}}{80} + \frac{V_{oc} - 240 + 160 i\Delta}{80} = 0$$

$$i\Delta = \frac{V_{oc}}{40}$$

Example: find V_{Th} and R_{Th}

$$V_{Th} = v_{OC}$$

$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$





$v_{OC} = 30 \text{ V}$

$i_{SC} = 3 \text{ A}$

$R_{Th} = 10 \Omega$


$i_{SC} = 3 \text{ A}$

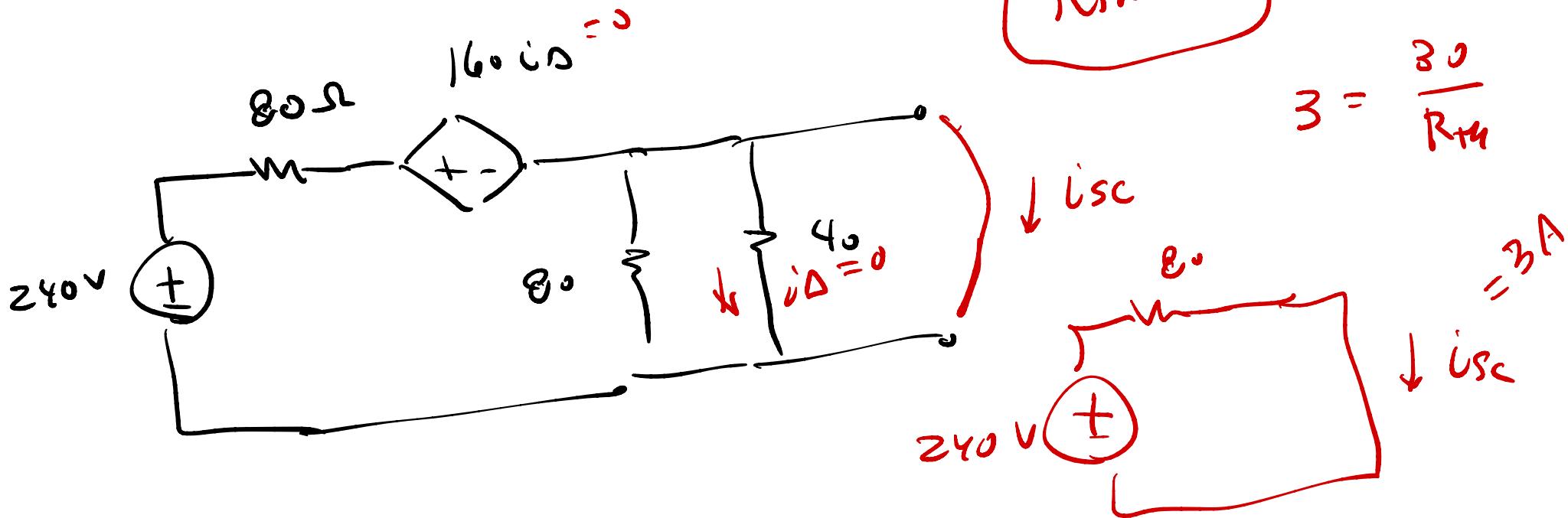

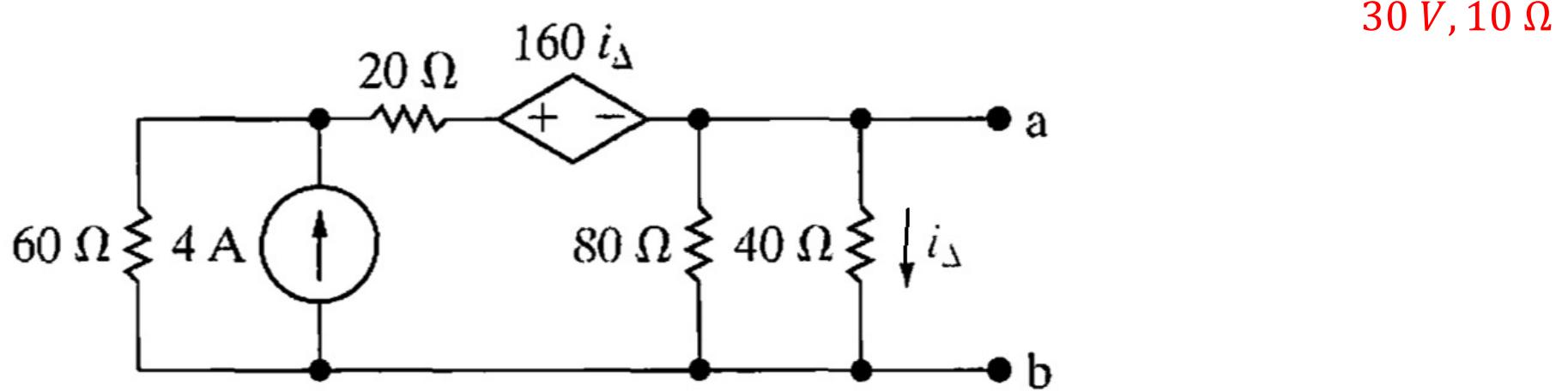


$$\frac{9}{4} V, 30 \Omega$$

Practice problem: find V_{th} and R_{Th}

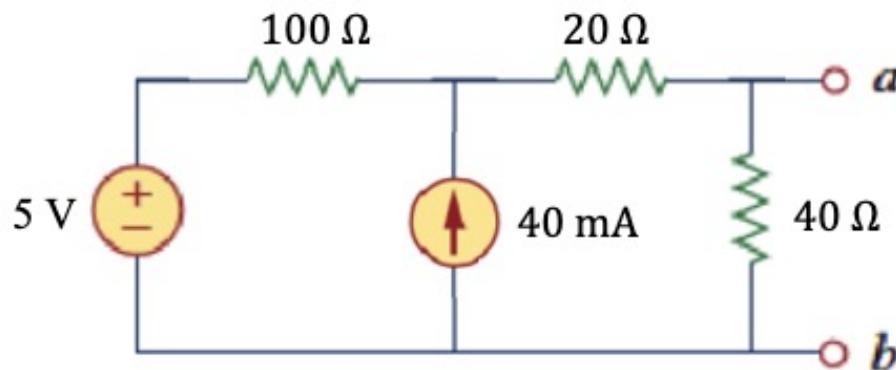


Practice problem: find V_{th} and R_{Th}

23.0 V, 44.6 Ω

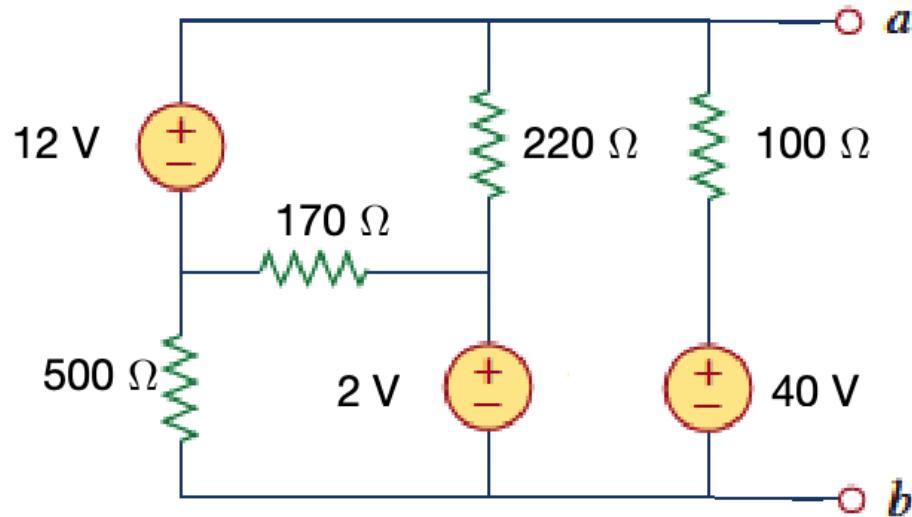

Practice problem: find V_{th} and R_{Th}

200 V, 14,3 k Ω

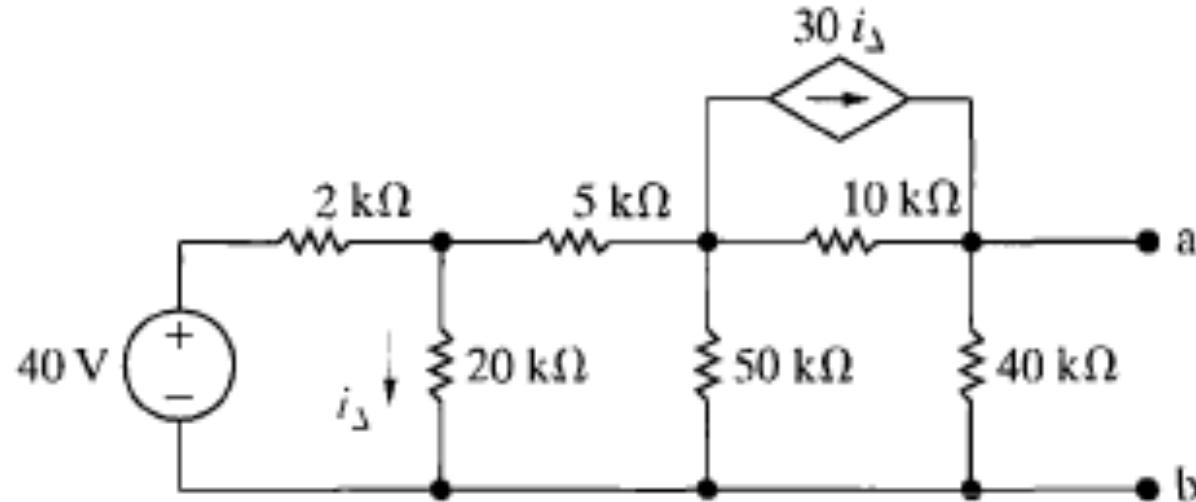

Practice problem: find V_{th} and R_{Th}

$$\frac{500}{3} V, 10 \Omega$$

