
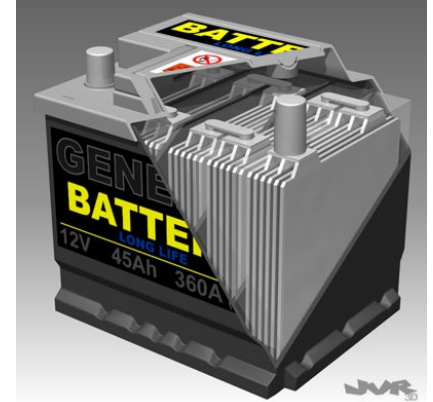


Theorems – 3

more Thevenin; Norton

Everyday Example

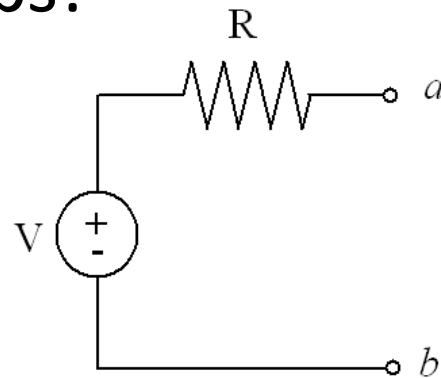- Car battery – 12.6 volts
- Can provide 100-200 amps!
- Thévenin model:
 - 12.6 volt source
 - 0.05-0.2 Ω resistance



- “Dead” when resistance increases (age/cold)
- Short circuit measurement ? (!)
 - How to test?

Alternative Method – Known Load



- Connect a known resistance across the terminals

$$V = \frac{R}{R_{TH} + R} V_{TH}$$

- Original relationships

$$V_{OC} = V_{TH}$$

$$V_{TH} = I_{SC} R_{TH}$$

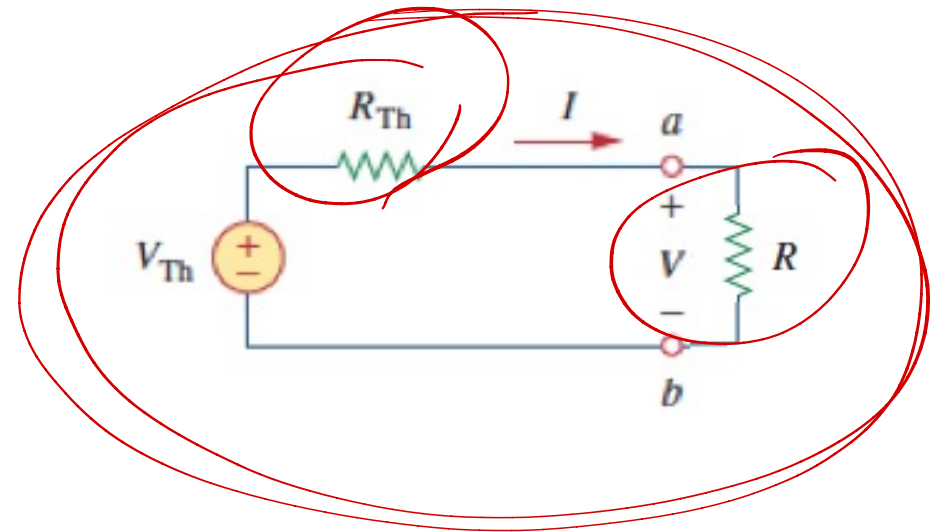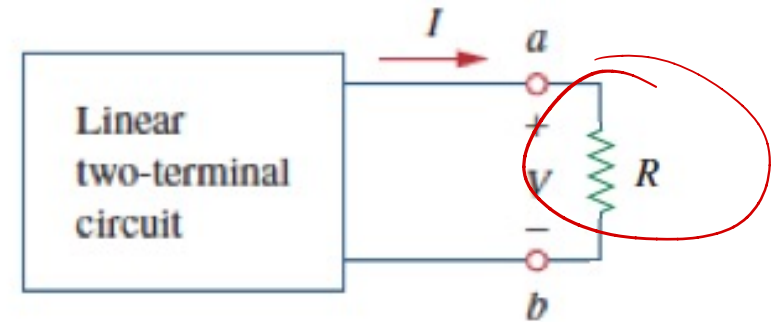

Car battery problem – version 1:

- Open circuit test: 12.6 volts across the terminals
- 10 Ω precision resistor load: 12.46 volts

Solution 1:

- Open circuit test: 12.6 volts across the terminals

$$V_{Th} = V_{oc} = 12.8 \text{ volts}$$

- 10 Ω precision resistor load: 12.46 volts

$\approx$

$$V = \frac{R}{R_{TH} + R} V_{TH}$$

$$12.46 = \frac{10}{R_{TH} + 10} 12.6$$

$$\underline{R_{TH} = 0.112 \Omega}$$

Car battery problem – version 2:

- 100 Ω precision resistor load: 12.45 volts
- 10 Ω precision resistor load: 12.2 volts

Solution 2:

- 100 Ω precision resistor load: 12.45 volts
- 10 Ω precision resistor load: 12.2 volts

$$12.45 = \frac{100}{R_{TH} + 100} V_{TH} \Rightarrow 100 V_{TH} - 12.45 R_{TH} = 1245$$


$$12.2 = \frac{10}{R_{TH} + 10} V_{TH} \Rightarrow 10 V_{TH} - 12.2 R_{TH} = 122$$

Solving

$$V_{TH} = 12.48 \text{ volts} \quad R_{TH} = 0.228 \Omega$$

“Ohmmeter” Test for R_{Th}

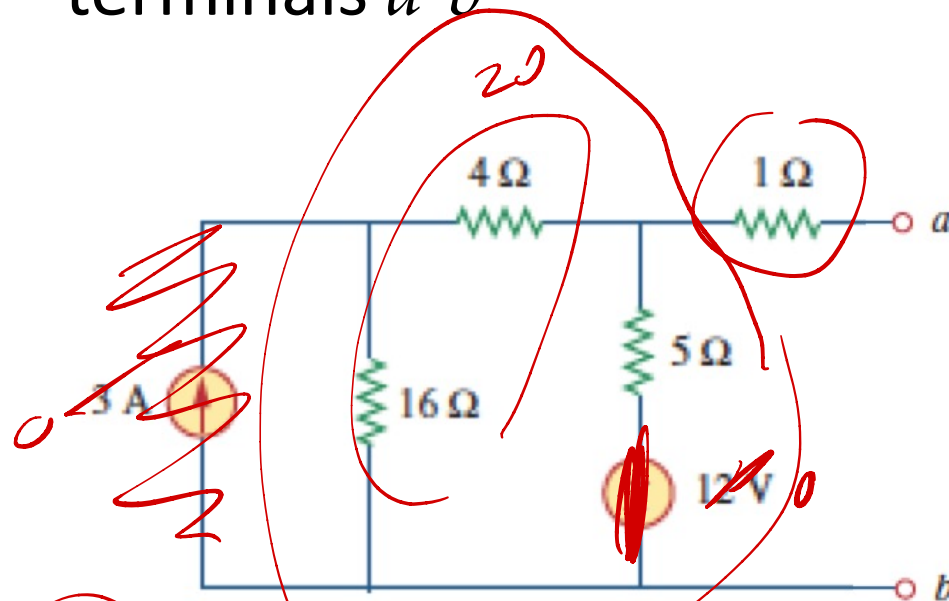
- If no dependent sources, then
 - Turn off independent sources
 - Compute equivalent resistance looking into terminals a - b



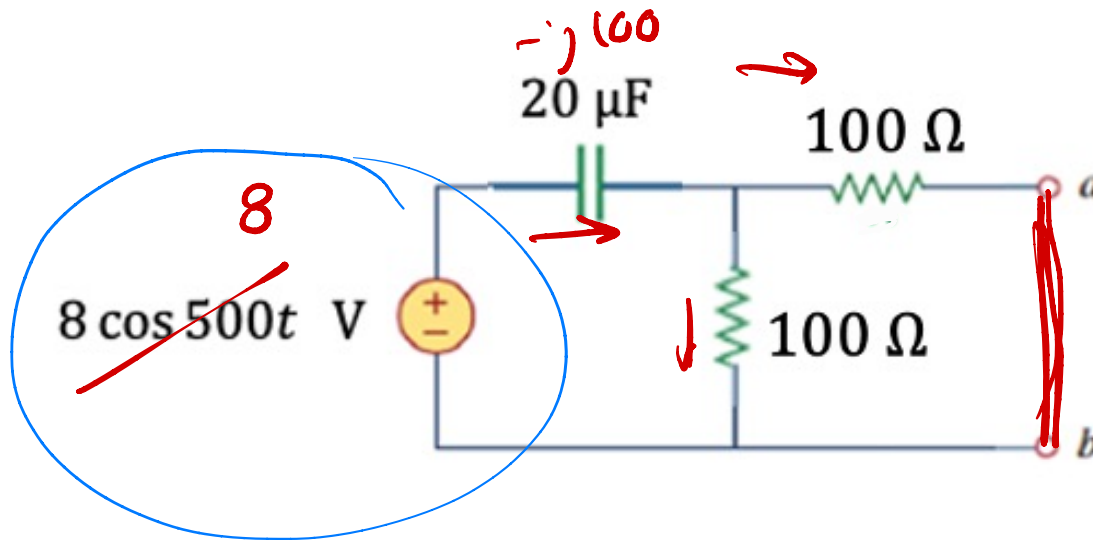19.2 V, $5\ \Omega$

Thévenin and Phasors


$$\frac{1}{j\omega C} = -j \frac{1}{500} \frac{10^6}{20} = -j100$$




$$V_{oc} = 8 \cdot \frac{100}{100 - j100} = \frac{8}{1 - j} = 4(1 + j)$$

$$I_{sc} = \frac{1}{2} \frac{8}{50 - j100}$$

$$= \frac{4}{50 - j100}$$

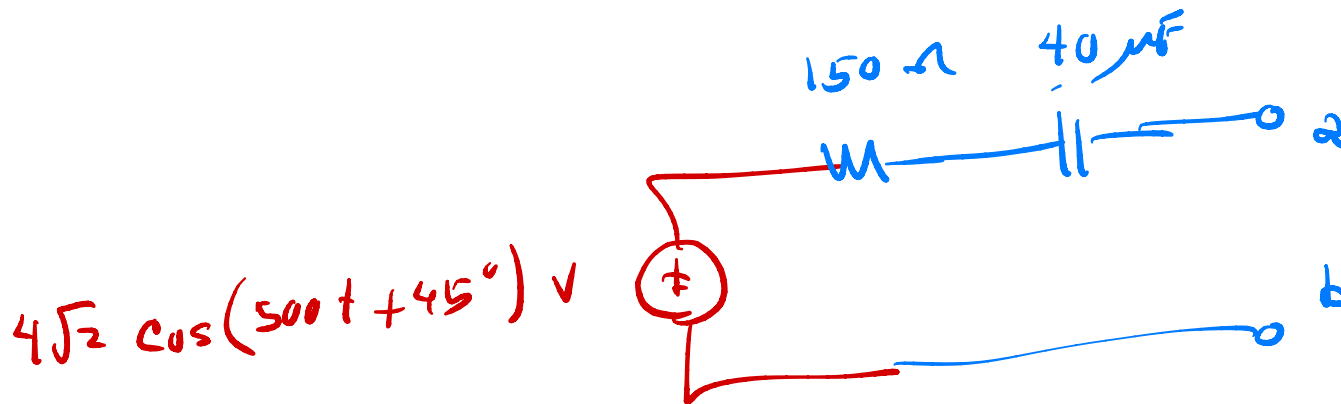

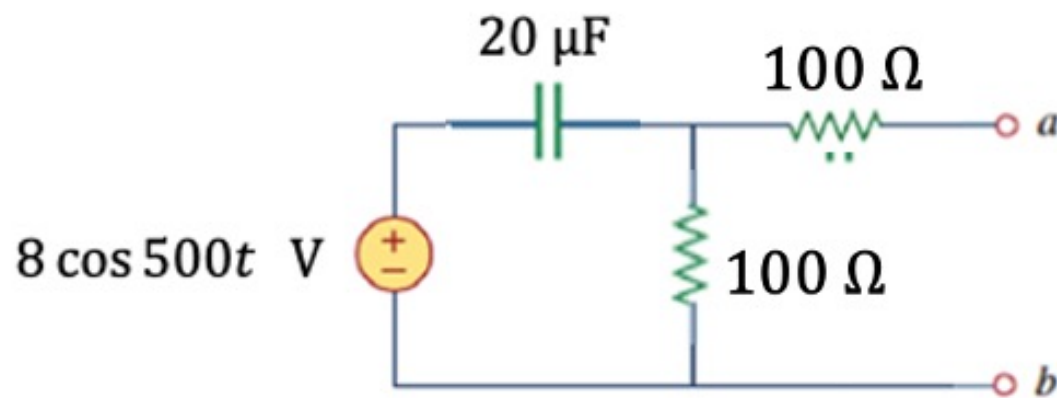

$$Z_{th} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{4(1+j)}{\frac{4}{50-j100}}$$

$$\begin{aligned} Z_{th} &= (1+j)(50-j100) \\ &= 50 + j50 - j100 + 100 \\ &= 150 - j50 \\ &= -j \boxed{50} - j \frac{1}{5000} = -j \boxed{\frac{1}{5000}} \end{aligned}$$

$$50 = \frac{1}{5000C}$$


$$C = \frac{1}{50 \cdot 5000}$$

$$4\sqrt{2} \cos(500t + 45^\circ) \text{ V},$$


$150 \Omega, 40 \mu\text{F}$

Norton Equivalent


- Recall source transformations, then

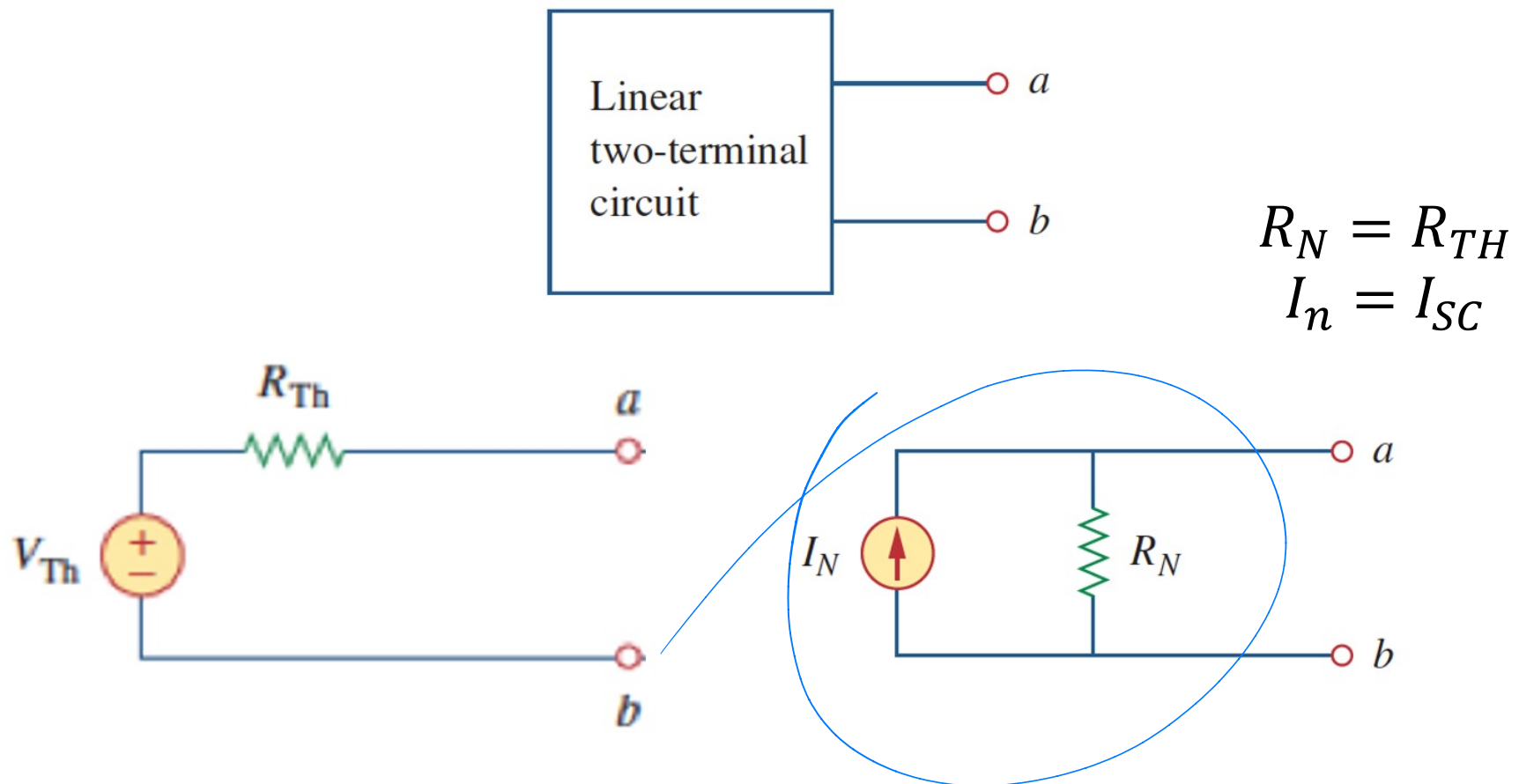


Example: which 2 are equivalent

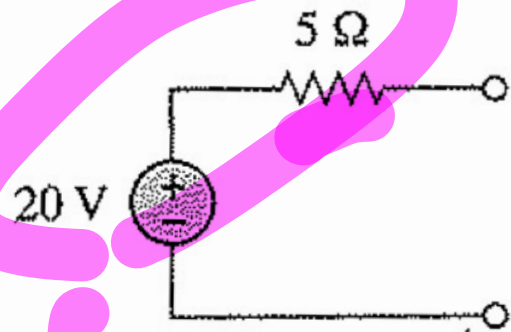


(a)

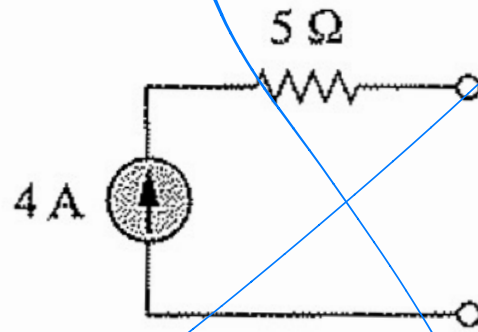

(b)

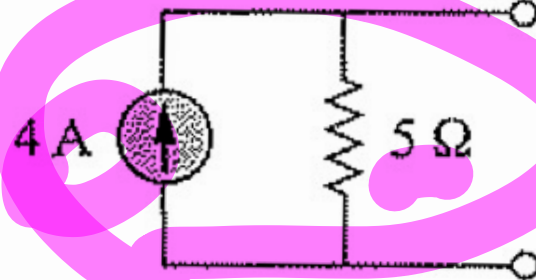



(c)

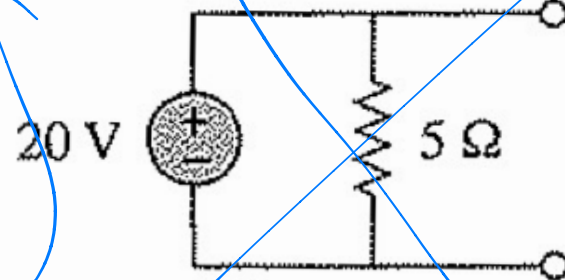

(d)

Example: Find I_N and R_N

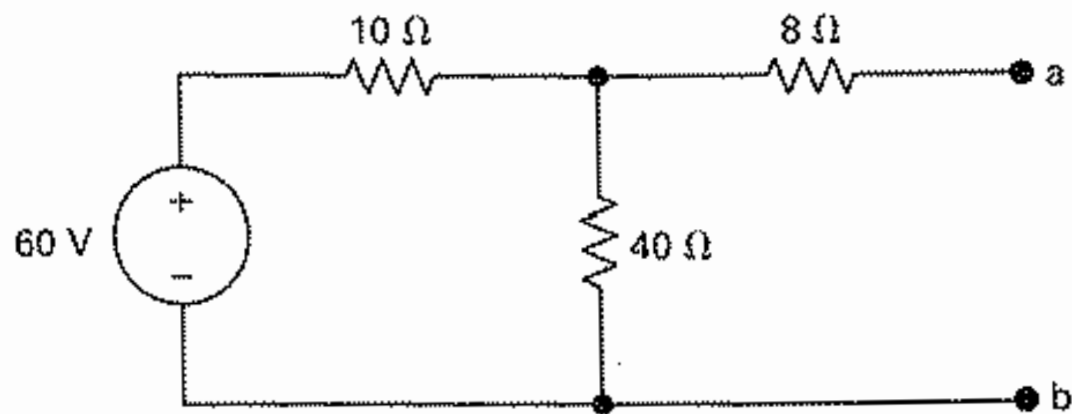

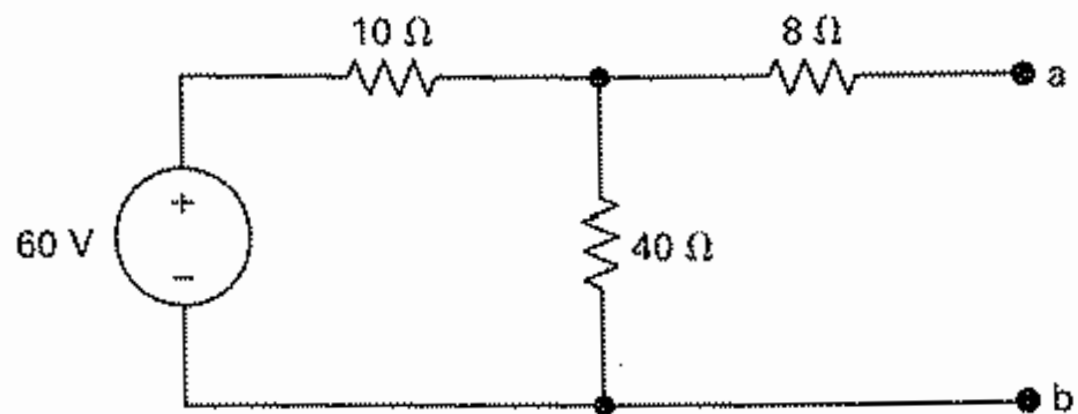


$$I_N = 3 \text{ A}, R_N = 16 \text{ } \Omega$$


$$V_{Th} = V_{oc}$$

$$Z_{Th} = \frac{V_{oc}}{I_{sc}}$$

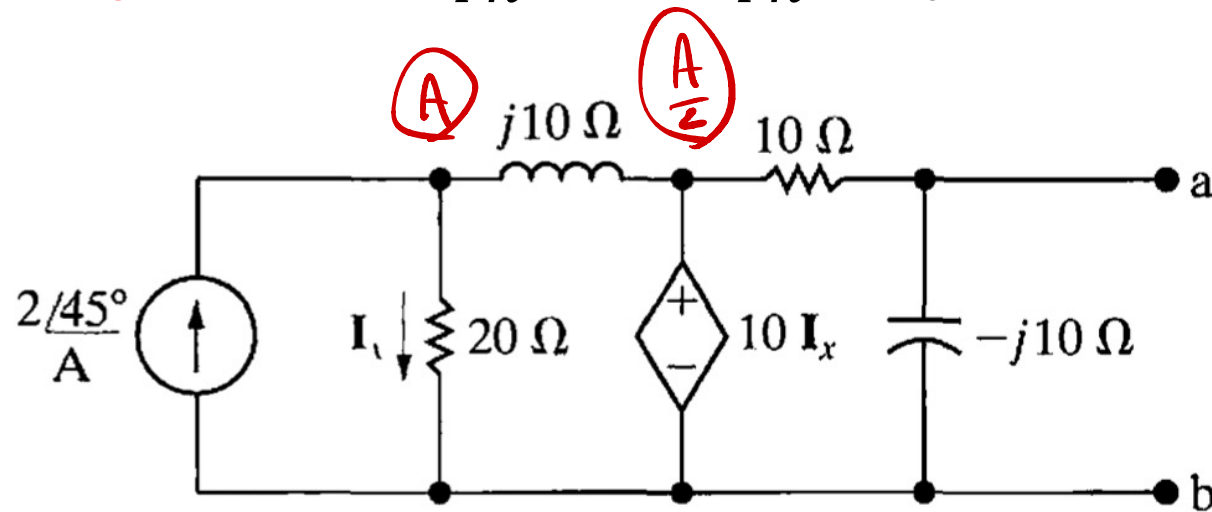Example: Find V_{Th} and Z_{Th} in phasor form




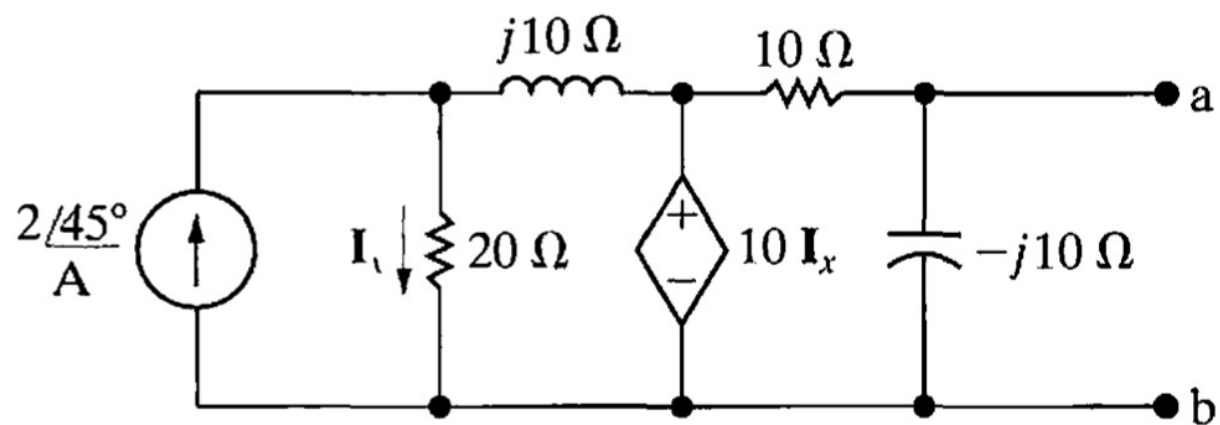$10 \angle 45^\circ \text{ V}, 5 - 5j \Omega$




50 V, 20 Ω , 2.5 A

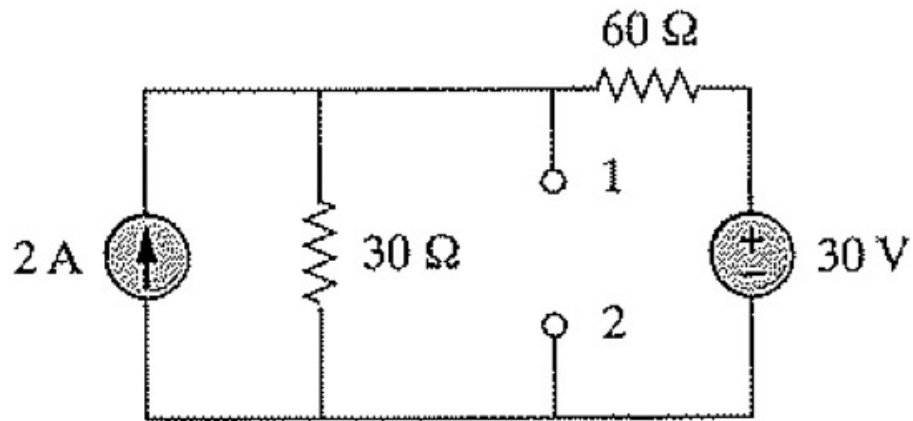
Practice problem: find Thevenin and Norton



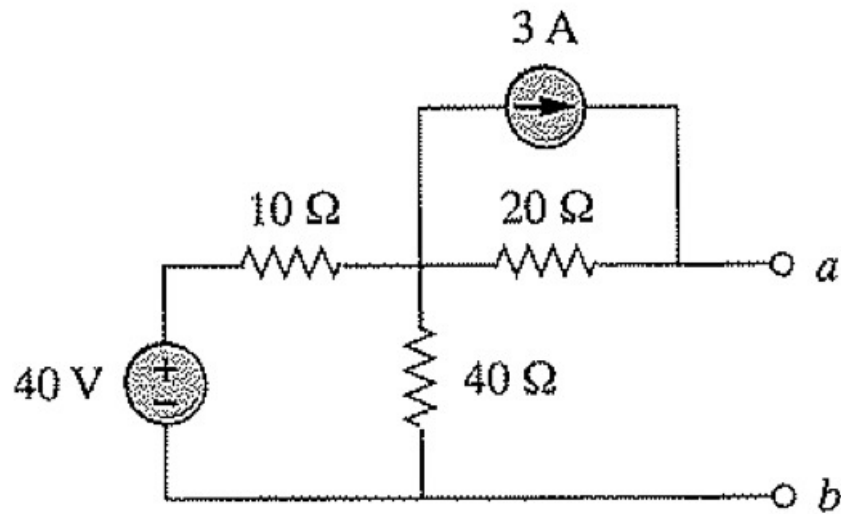Practice problem: find Thevenin and Norton 92 V, 28 Ω , 3.29 A




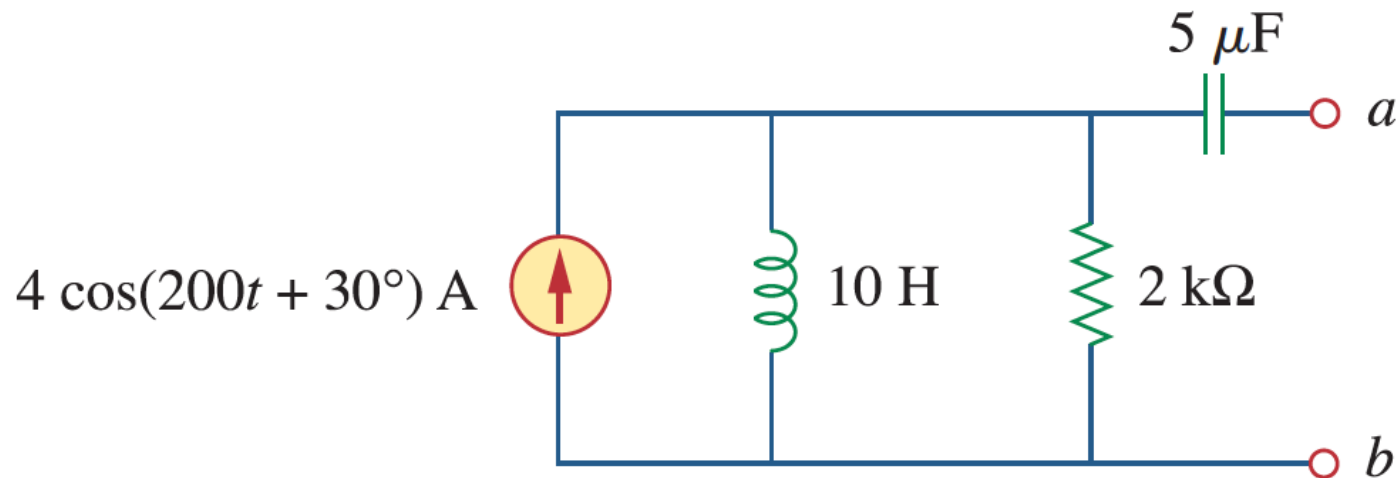Practice problem: find the Thevenin and Norton models




$$\begin{aligned} &4000\sqrt{2} \cos(200t + 75^\circ) \text{ V}, \\ &1000 \Omega, \\ &4\sqrt{2} \cos(200t + 75^\circ) \text{ A} \end{aligned}$$

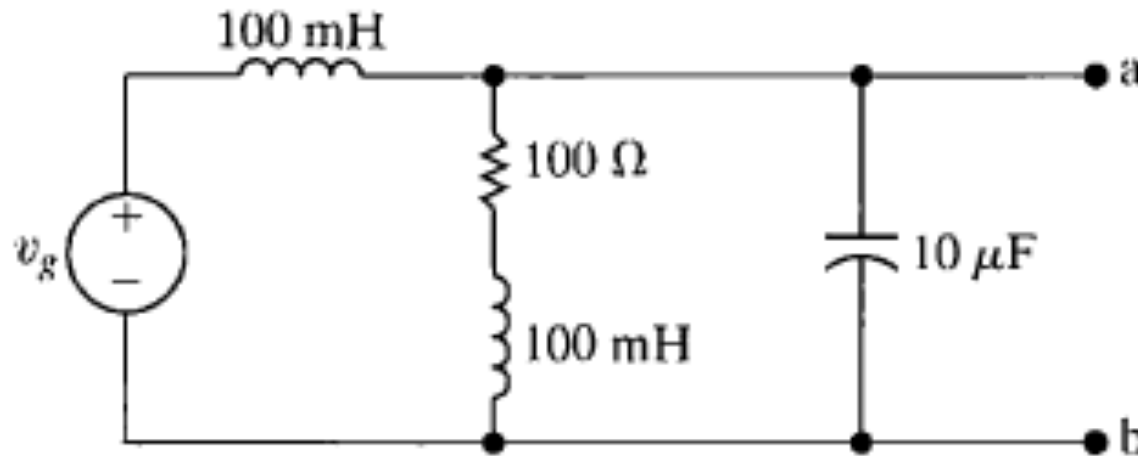Practice problem: find the Thevenin and Norton models if $v_g(t) = 247.49 \cos(1000t + 45^\circ) \text{ V}$



$350 \cos 1000t \text{ V},$
 $100 \Omega, 100 \text{ mH},$
 $2.475 \cos(1000t - 45^\circ) \text{ A}$

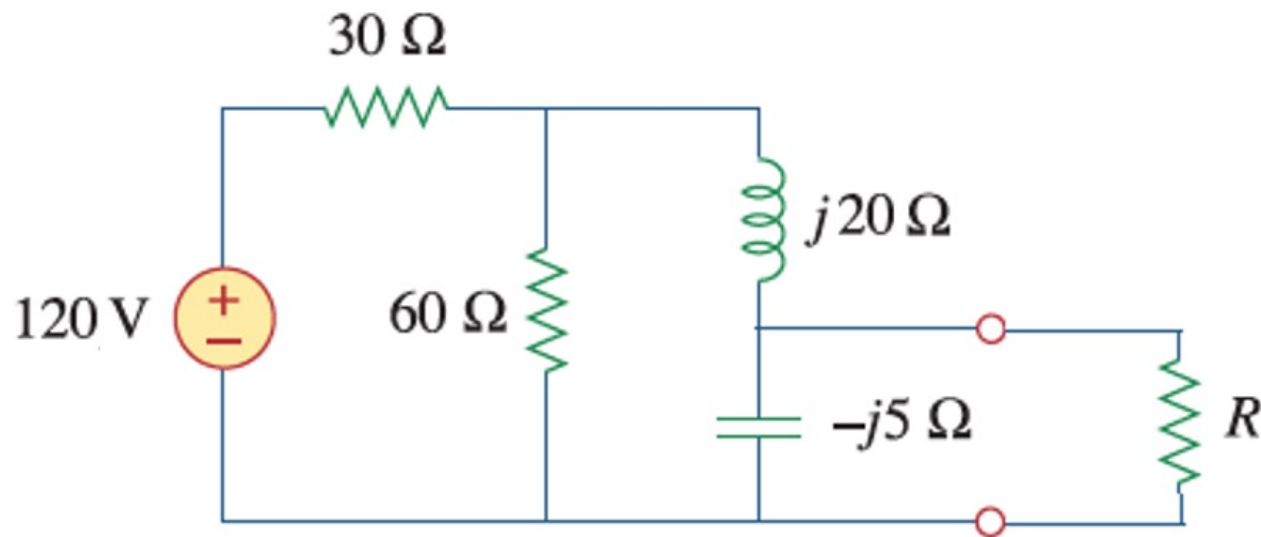Practice problem: find the magnitude of the current through R as a function of R – hint: first find the Thevenin equivalent



$$\frac{16}{\sqrt{(R + 0.8)^2 + 5.6^2}}$$