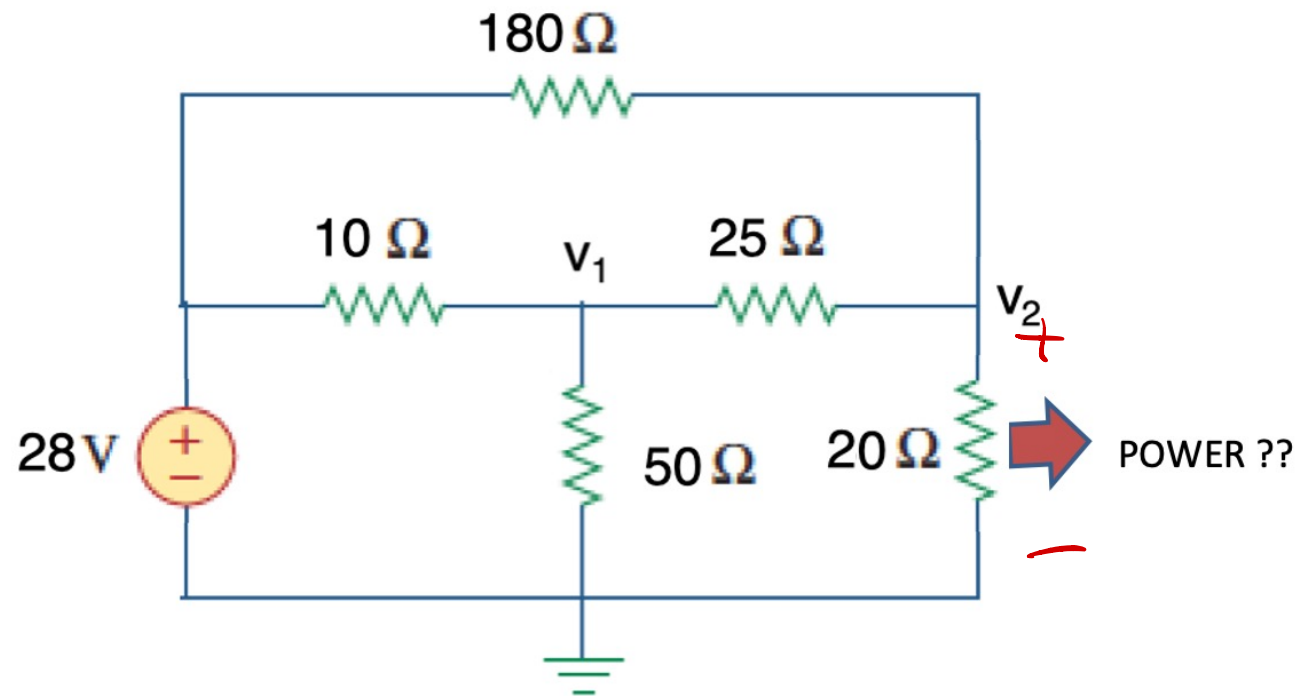


Theorems – 4


maximum power transfer

Power Transfer




- How much power is dissipated in the 20 Ω resistor?
 - Method: node analysis $\rightarrow v_2 = 10 \text{ V}$
 - Power calculation $P = \frac{v_2^2}{20} = \frac{10^2}{20} = 5 \text{ W}$
- Handwritten notes: 10, 5, 20*

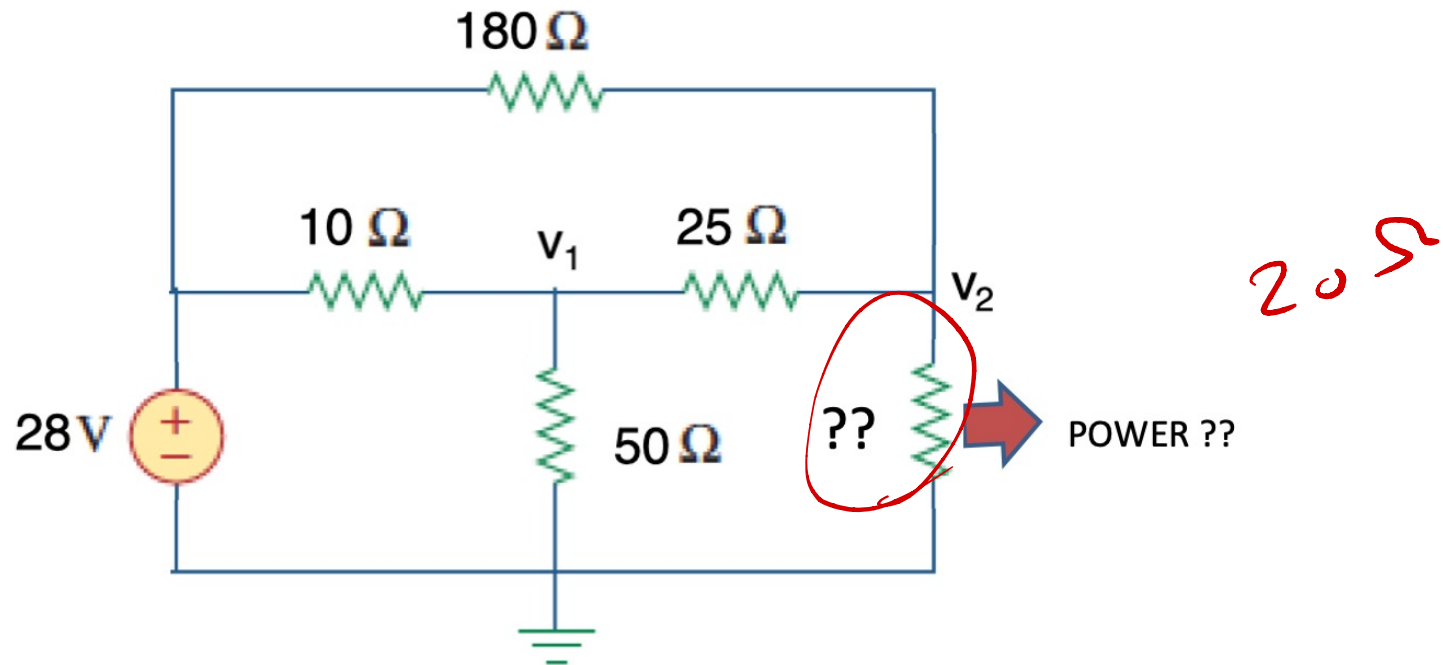- Question – if the resistance was larger/smaller than $20\ \Omega$ could it take more power from the circuit?



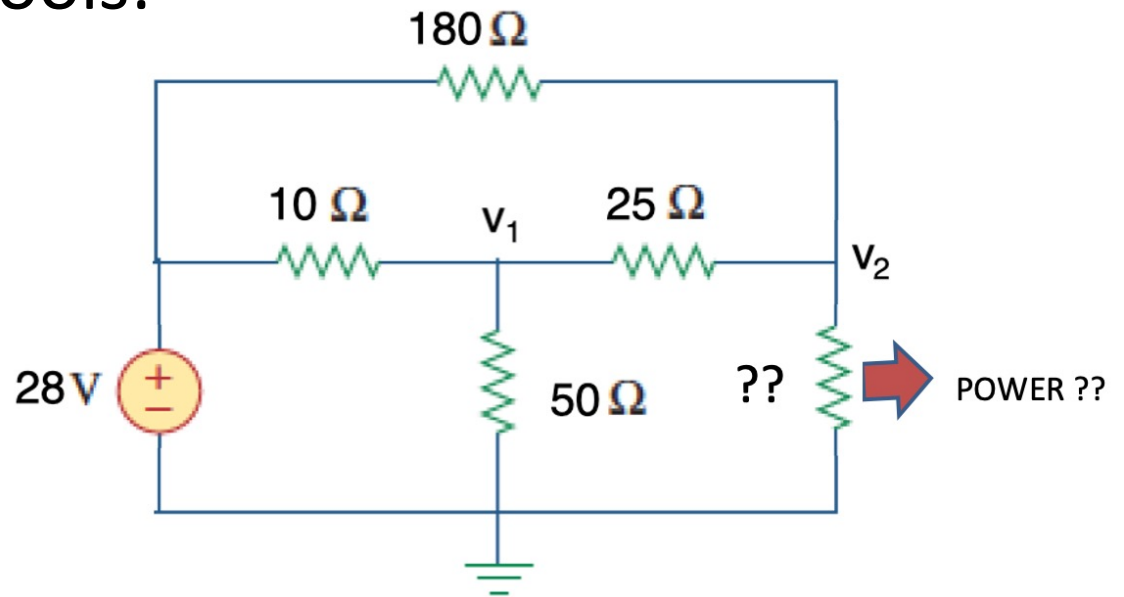- Approach 1 – solve for power in terms of R
 - MatLab symbolic tools:



%% setup problem

syms v_1 v_2 R

$[s1,s2] = \text{solve}(v_1/50+(v_1-28)/10+(v_1-v_2)/25==0, \dots$
 $v_2/R+(v_2-v_1)/25+(v_2-28)/180==0,v_1,v_2)$

$\text{pow} = s2^2/R;$

%% check for R = 20 ohms

$\text{subs}(s2,R,20)$

$\text{subs}(\text{pow},R,20)$

$\text{ans} =$
 10
 $\text{ans} =$
 5


- Optimize

% optimize over R

dpow = diff(pow,R);

Rstar = solve(dpow)

eval(subs(pow,R,Rstar))

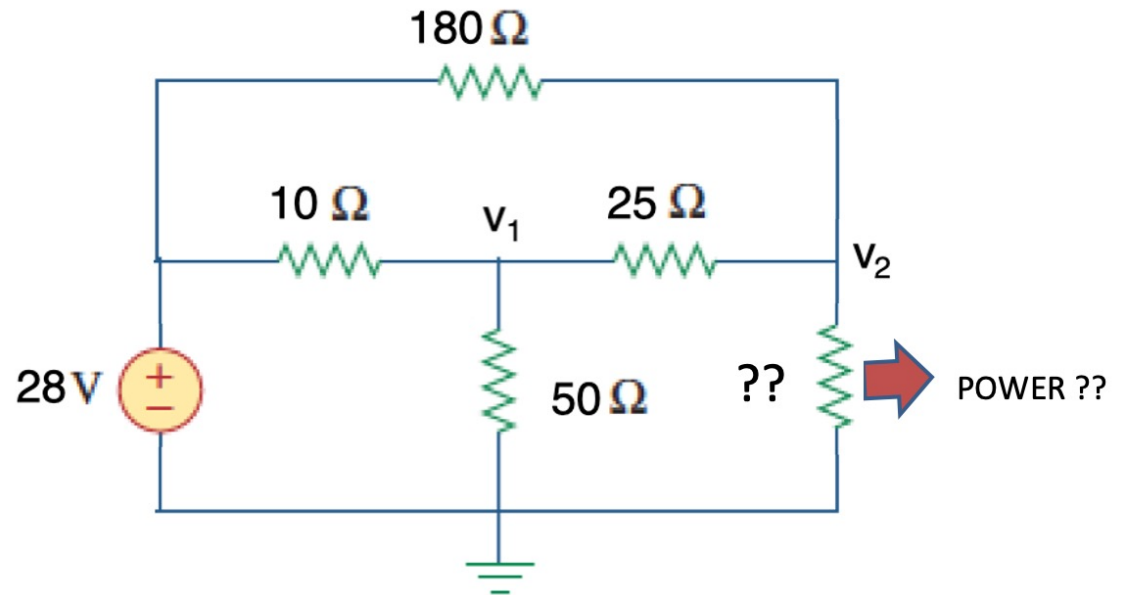

Rstar =

225/8

ans =



5.1467e+00

$$R^* = \frac{225}{8} = 28.1 \Omega$$

$$P_{max} = 5.15 W$$

- What's going on?


$$P = \frac{148225 R}{4 (8R + 225)^2}$$

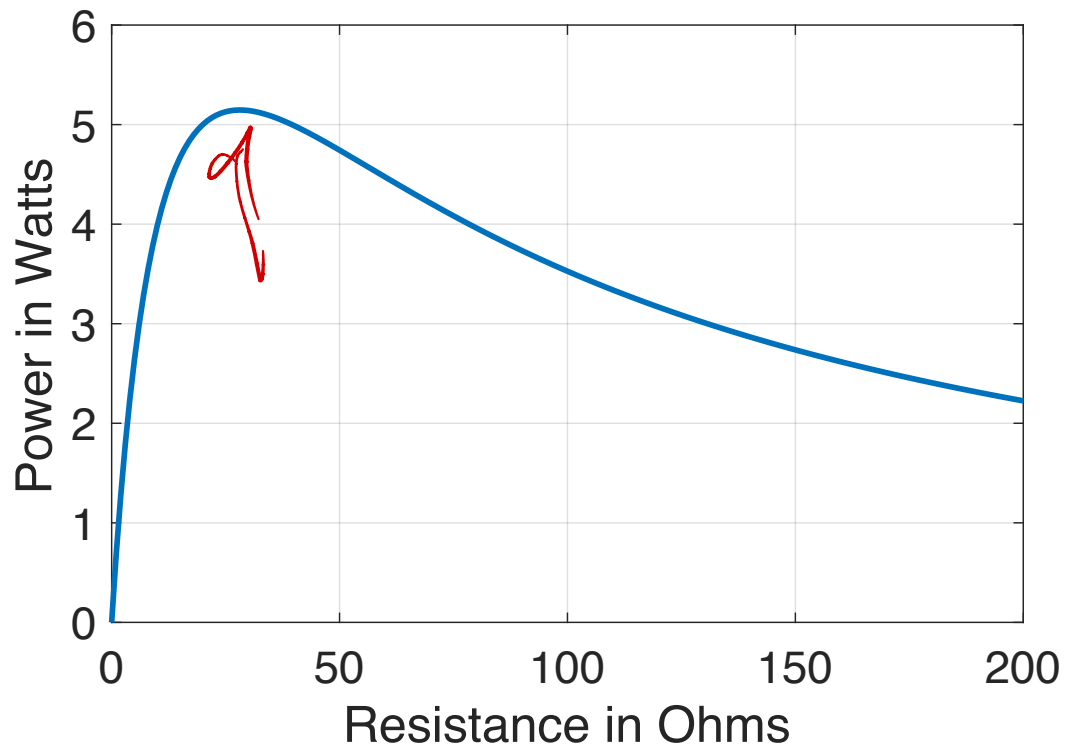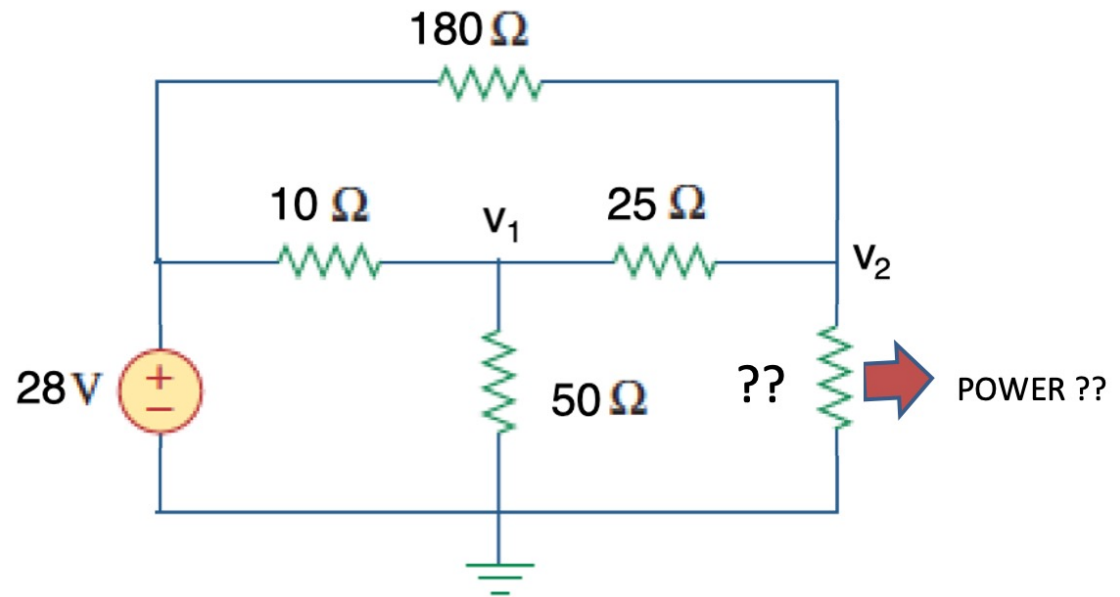



```
Rv = 0:200;
Pv = subs(pow,Rv);
plot(Rv,Pv)
```

Maximum Power Transfer

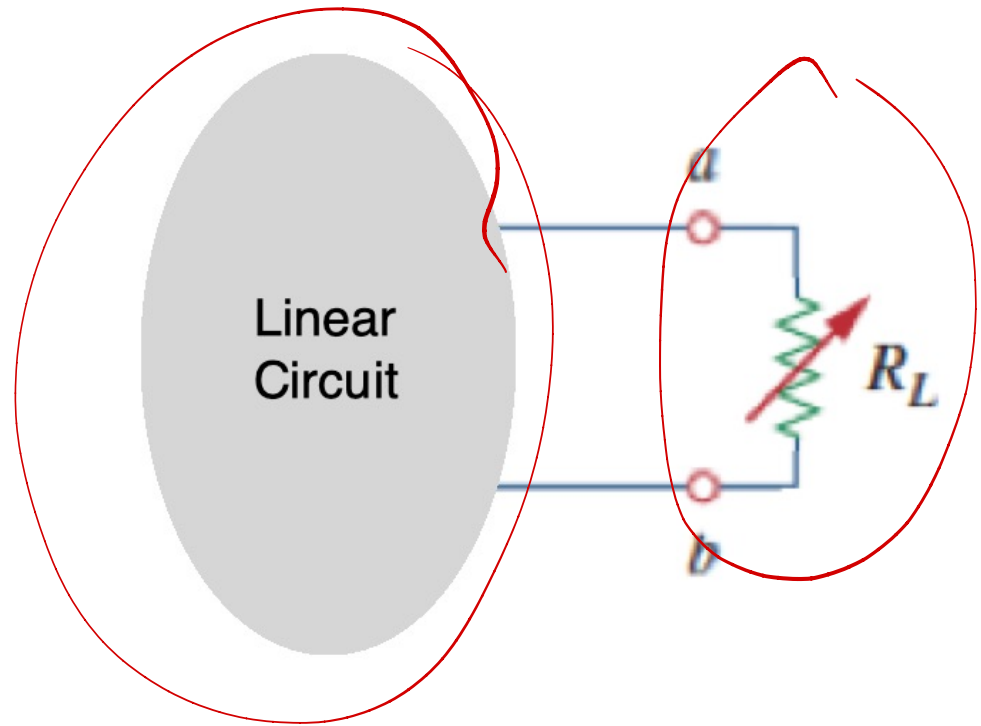- Consider connecting a “load” resistance, R_L , across two points of a circuit
- What happens as it varies?
 - Current
 - Voltage
 - Power



- Use the Thevenin model

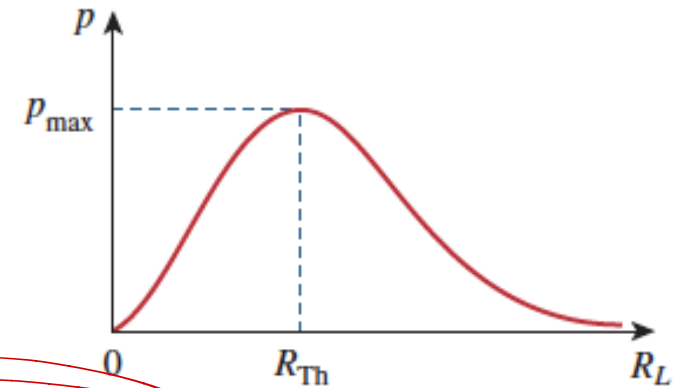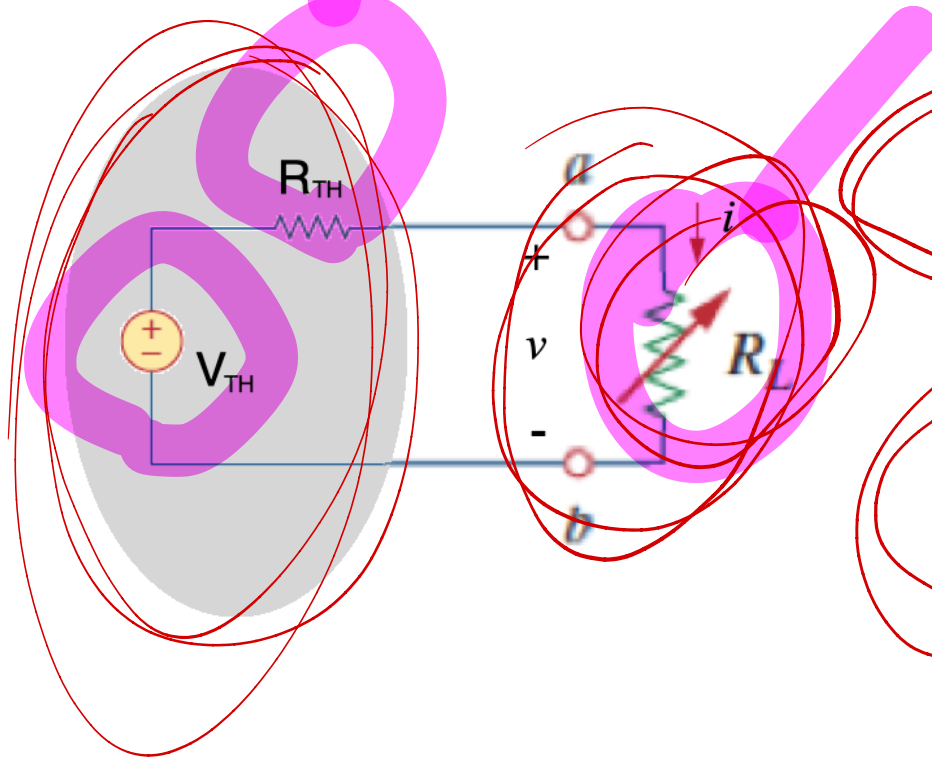


$$v = \frac{R_L}{R_L + R_{th}} v_{th}$$

$$p = \frac{v^2}{R_L} = \frac{R_L}{(R_L + R_{th})^2} v_{th}^2$$

- $\frac{\partial p}{\partial R_L} = 0$ yields a max of $P_{max} = \frac{V_{th}^2}{4R_{th}}$ when $R_L = R_{th}$

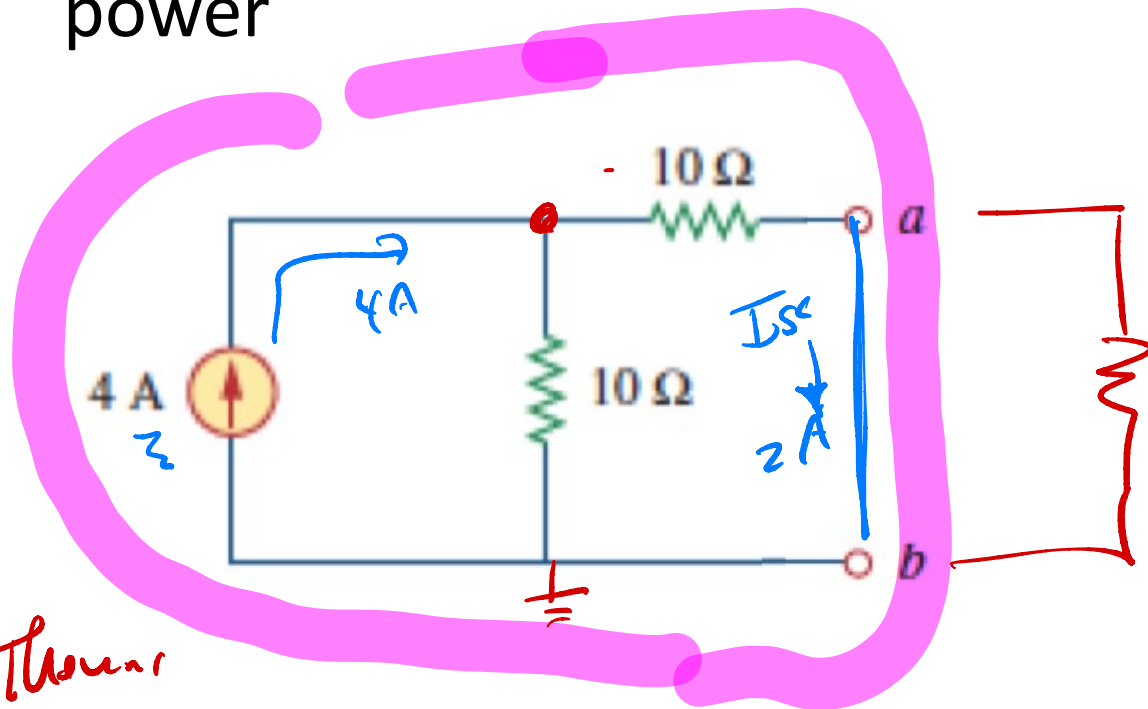Example: find a load resistance to dissipate maximum power



20 Ω, 20 W




P
 $R_L = 20 \Omega$

$$P = \frac{40^2}{4 \cdot 20}$$


Thoum:

oc: $\frac{A}{10} - 4 = 0 \Rightarrow A = 40$
 $V_{oc} = 40 \text{ V}$

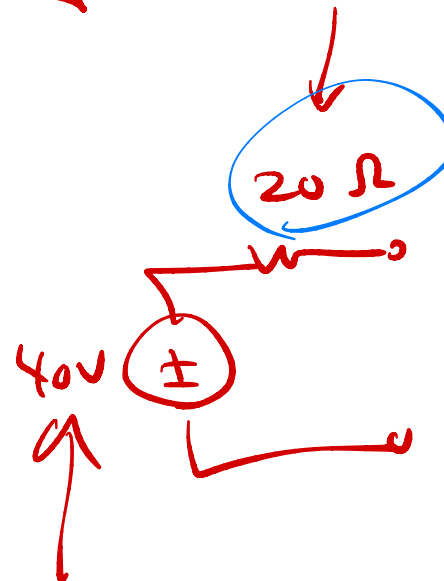sc: $I_{sc} = 2 \text{ A}$
 $R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{40}{2} = 20$



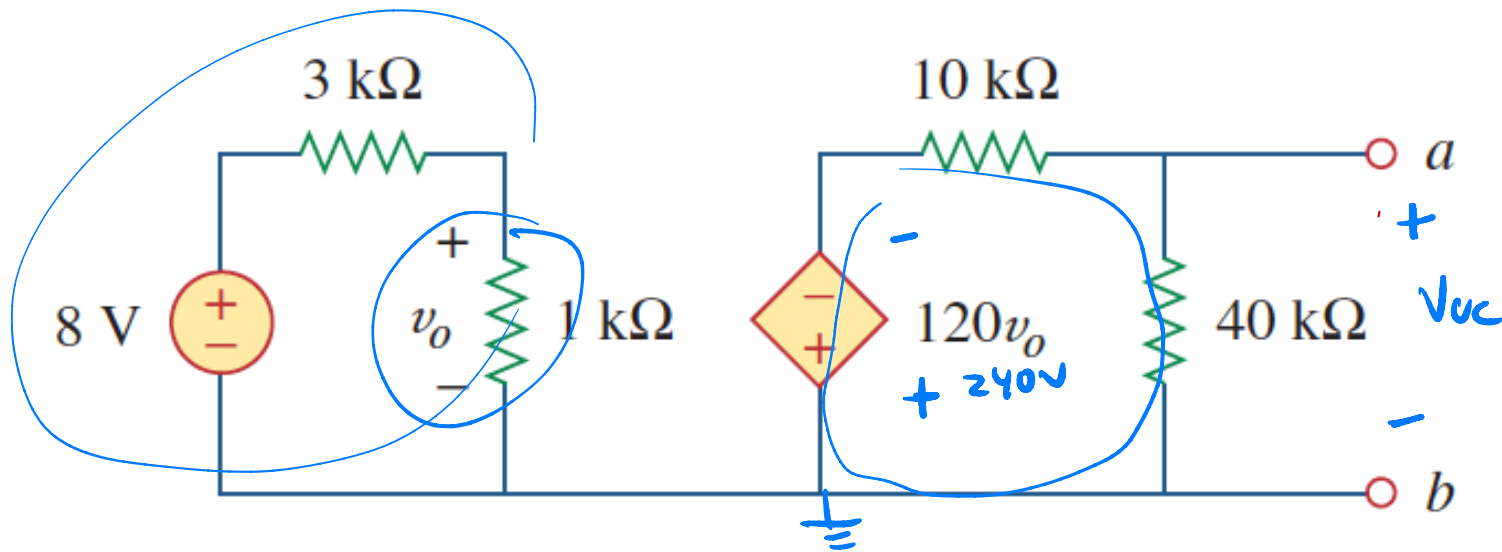
Example: find the load that dissipates maximum power



$$V_{oc}: \quad v_o = \frac{1}{4} \cdot 8 = 2\text{V}$$

$$V_{oc} = -240 \cdot \frac{40}{50} = -192\text{V}$$

$$I_{sc}$$

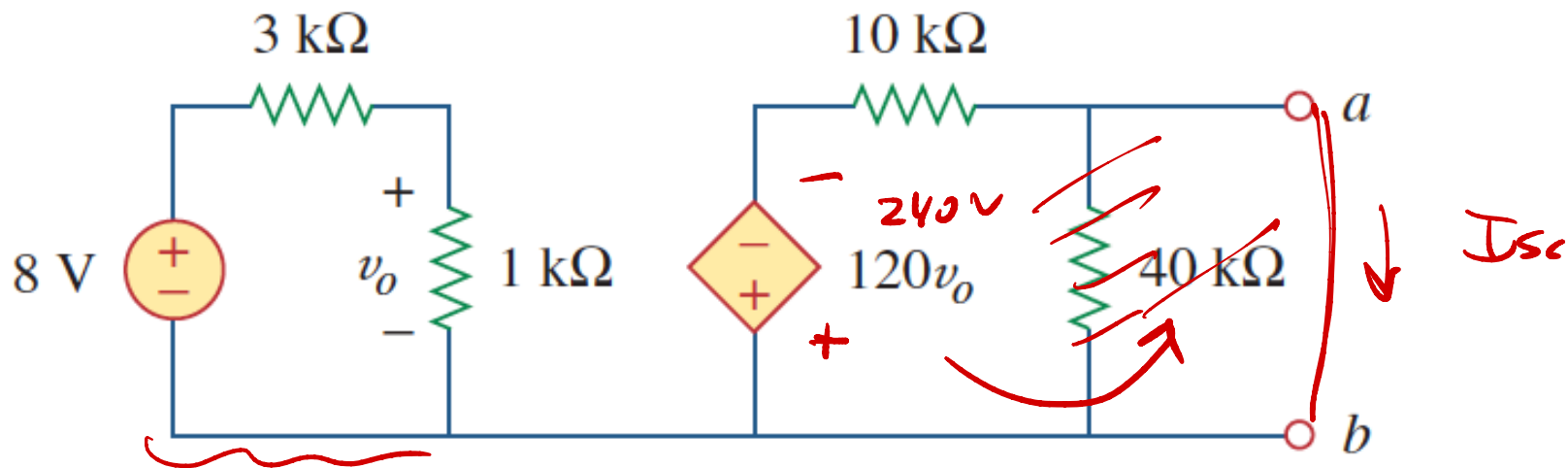


$$I_{sc}: \quad v_o = 2V \quad I_{sc} = -\frac{240}{10000} = -24 \text{ mA}$$

$$R_{Th} = \frac{-192V}{-24 \text{ mA}} =$$

$$P = \frac{(192)^2}{4 \cdot 8000} \text{ W}$$


8 kΩ

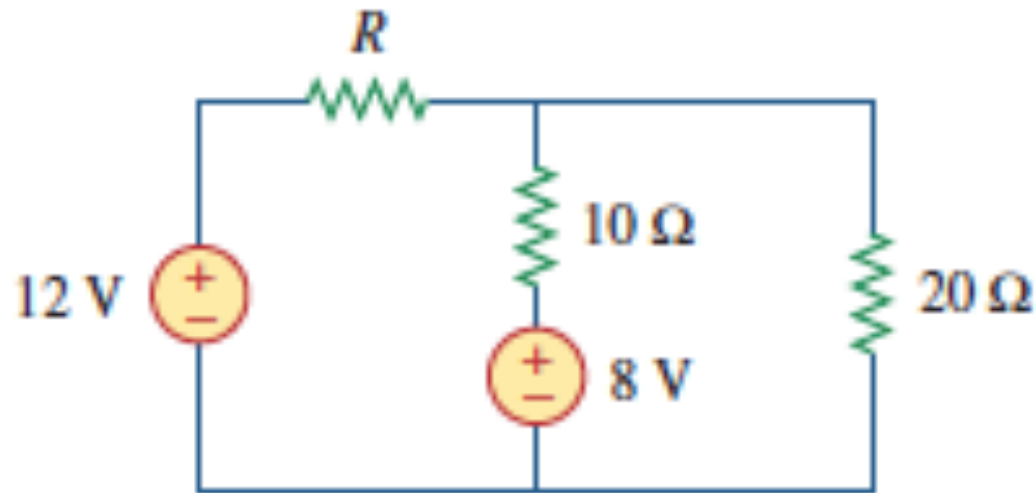Example (trick): find R to maximum the power delivered to the $10\ \Omega$ resistor



Maximum AC Power

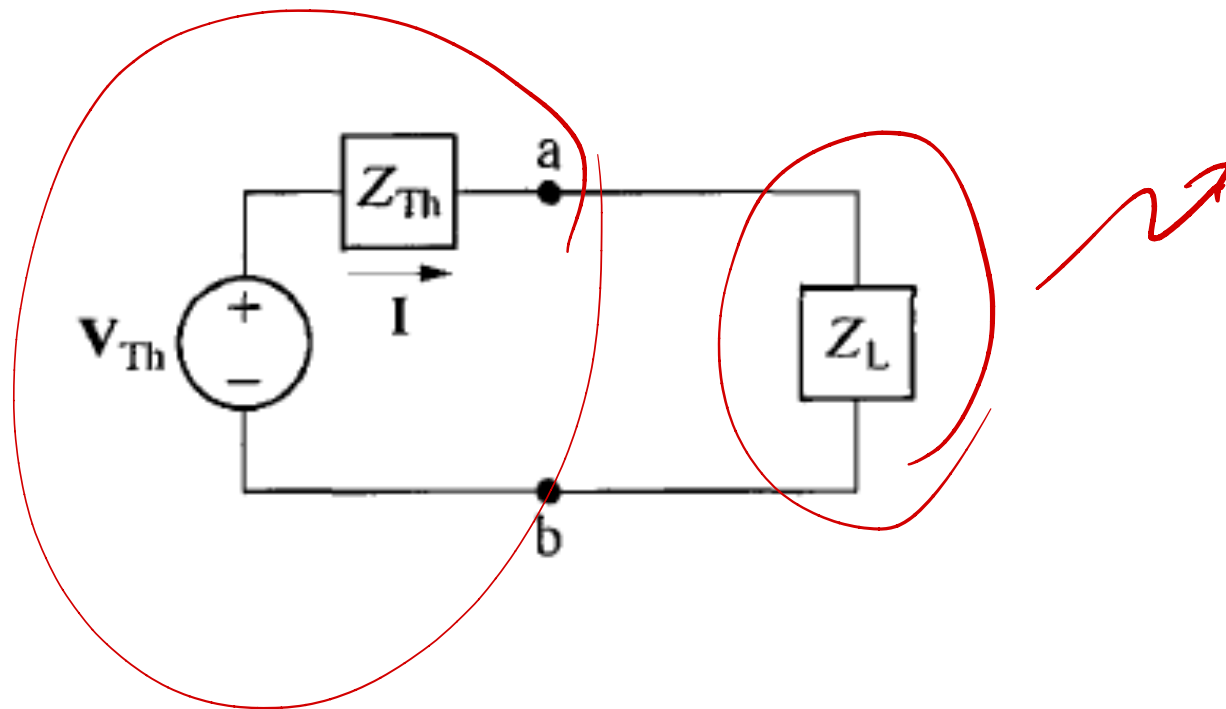- Given a phasor Thevenin model, how do we get maximum power to Z_L ?




- For sinusoidal sources and RLC circuits, power is


$$S = \frac{|\mathbf{I}|^2}{2} Z_L$$

$$P = \frac{|\mathbf{I}|^2}{2} R_L$$

- For our problem

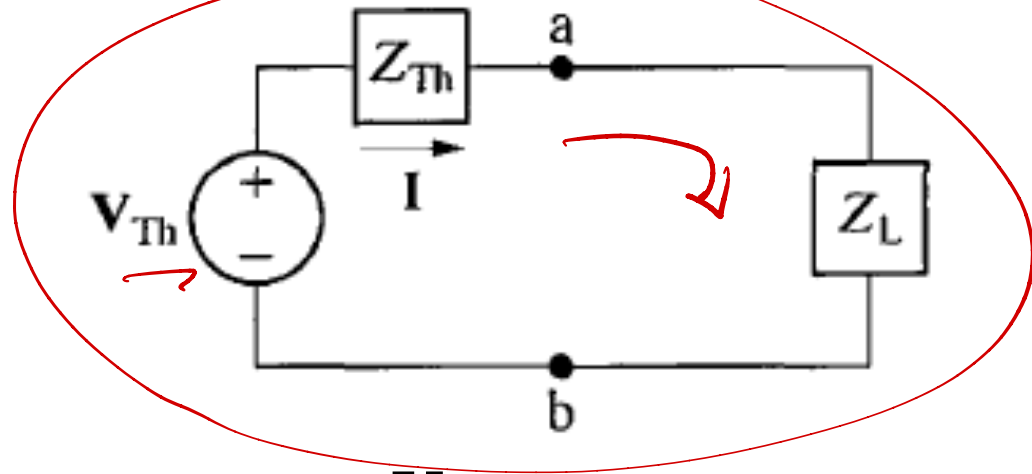
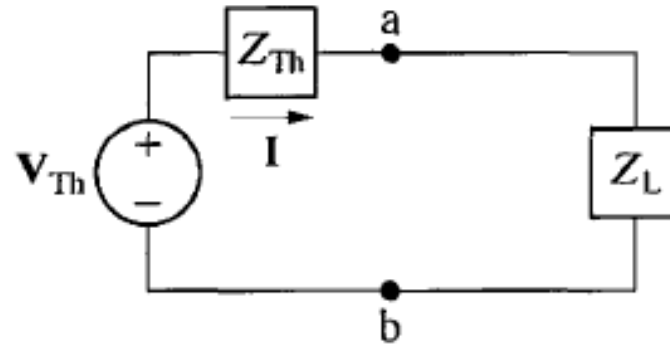
$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{Z_{Th} + Z_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$$



- So

$$P = \frac{|I|^2}{2} R_L = \frac{1}{2} \frac{|V_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- We can optimize this using calculus
- How depends upon which parameters we can change

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Example 1 (unusual): both R_L and X_L are free to choose

$$\frac{\partial P}{\partial X_L} = 0 \quad \frac{\partial P}{\partial R_L} = 0$$

$$Z_L = Z_{Th}^*$$

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Example 2 (more common): X_L is fixed, but R_L is free to choose

$$\frac{\partial P}{\partial R_L} = 0$$


$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$

$$P_{max} = \dots$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Other scenarios:
 - Fixed angle on Z_L
 - Limits on R_L and X_L

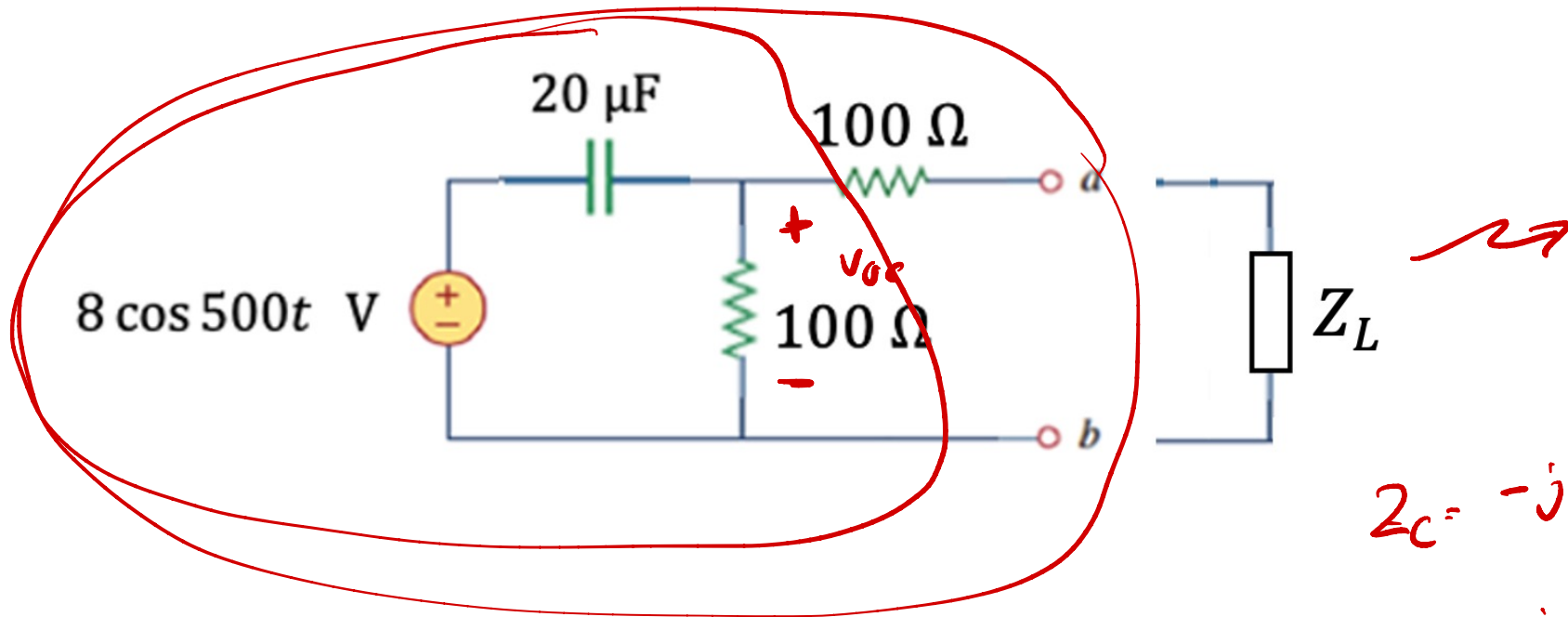Example: find Z_L to maximize the power transfer



$$V_{oc} = \frac{100}{100 - j100} \cdot 8$$


$$= \frac{8}{1-j} \cdot \frac{1+j}{1+j} =$$

$$= 4\sqrt{2} \angle 45^\circ$$

$$4(1+j)$$

$$\begin{aligned} Z_C &= -j \frac{1}{\omega C} \\ &= -j \frac{10^6}{500 \cdot 20} \\ &= -j100 \end{aligned}$$

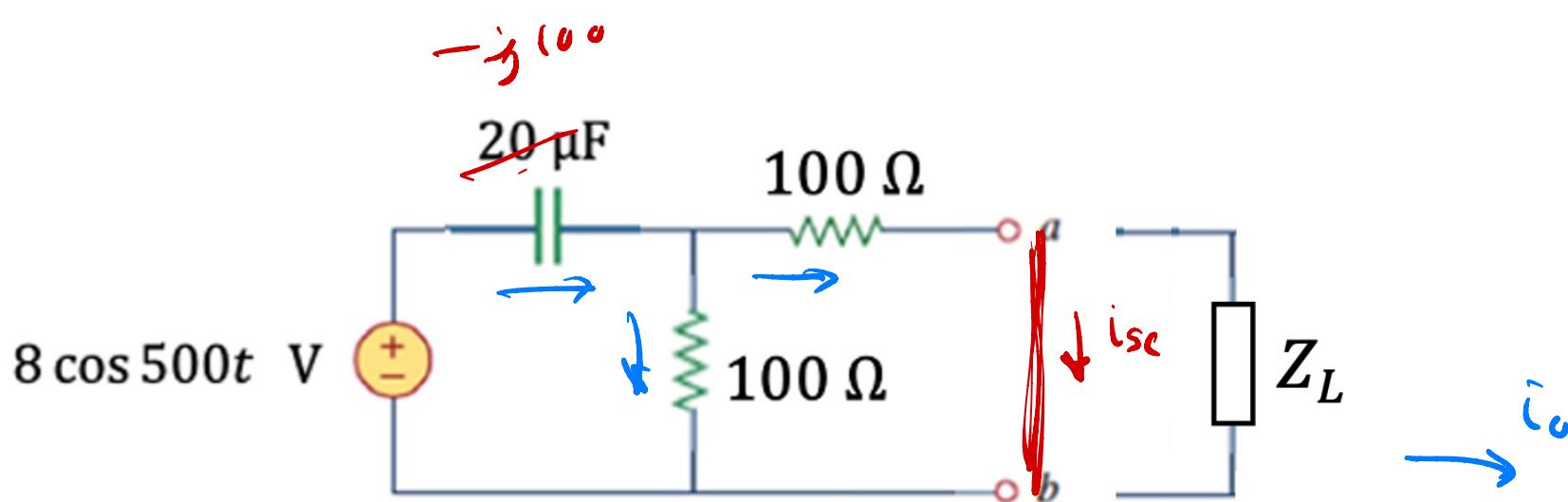
$$V_{Th} = 4\sqrt{2} \cos(500t + 45^\circ) \text{ V}$$



i_{sc} :

$$I_0 = \frac{8}{50 - j100}$$

$$I_{sc} = \frac{4}{50 - j100}$$

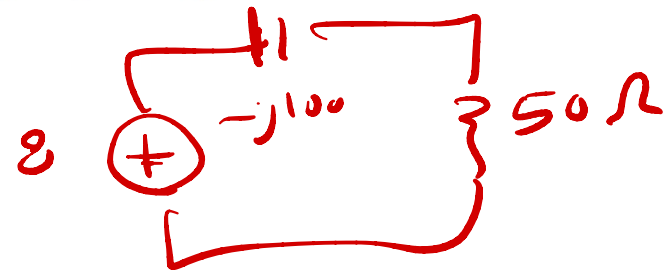

$$Z_{th} = \frac{4(1+j)}{4} = (1+j)(50 - j100)$$



$$= 50 + j50 - j100 + 100$$

$$= (50 - j50)$$


Since $V_{Th} = 4\sqrt{2} \cos(500t + 45^\circ) \text{ V}$ and $Z_{Th} = 150 - j50 \Omega$,
 then $Z_L = 150 + j50 \Omega = 150 \Omega, 0.1 \text{ H}$, and $P = 26.7 \text{ mW}$

$$1.6 \, \Omega, \frac{5}{8} \, W$$

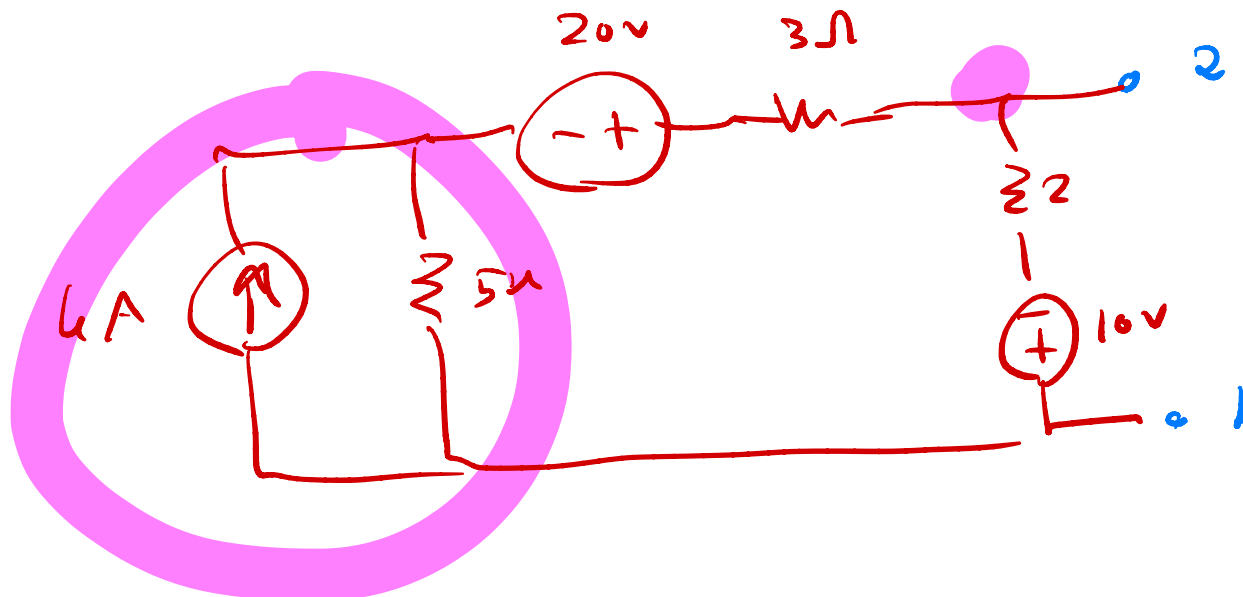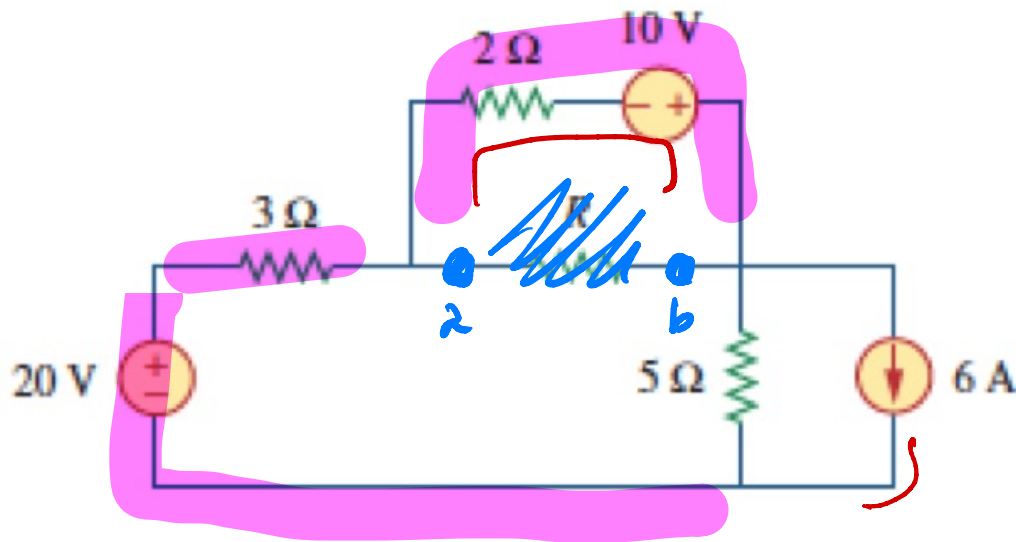Practice problem: maximize the power to R



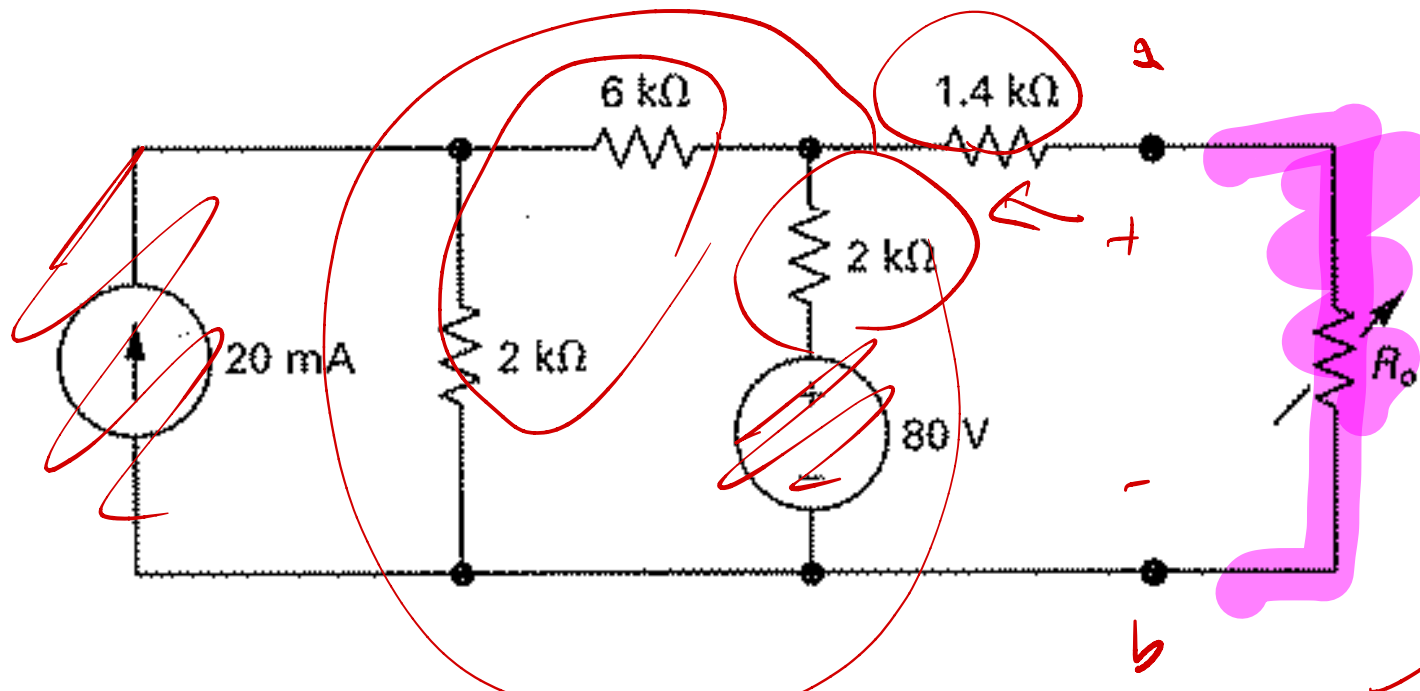Practice problem: maximize the power to R_o




$3\text{ k}\Omega, 468\text{ mW}$

$$1.4 + 1.4 = 3\text{ k} = R_{th}$$

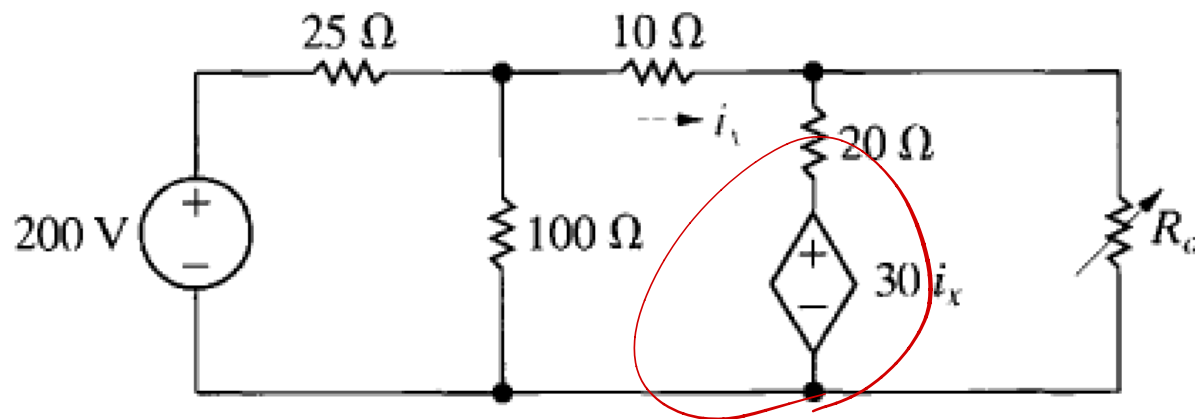
7.5 Ω , 333 W

Practice problem: maximize the power to R_o



$3\ \Omega, 1.2\ \text{kW}$

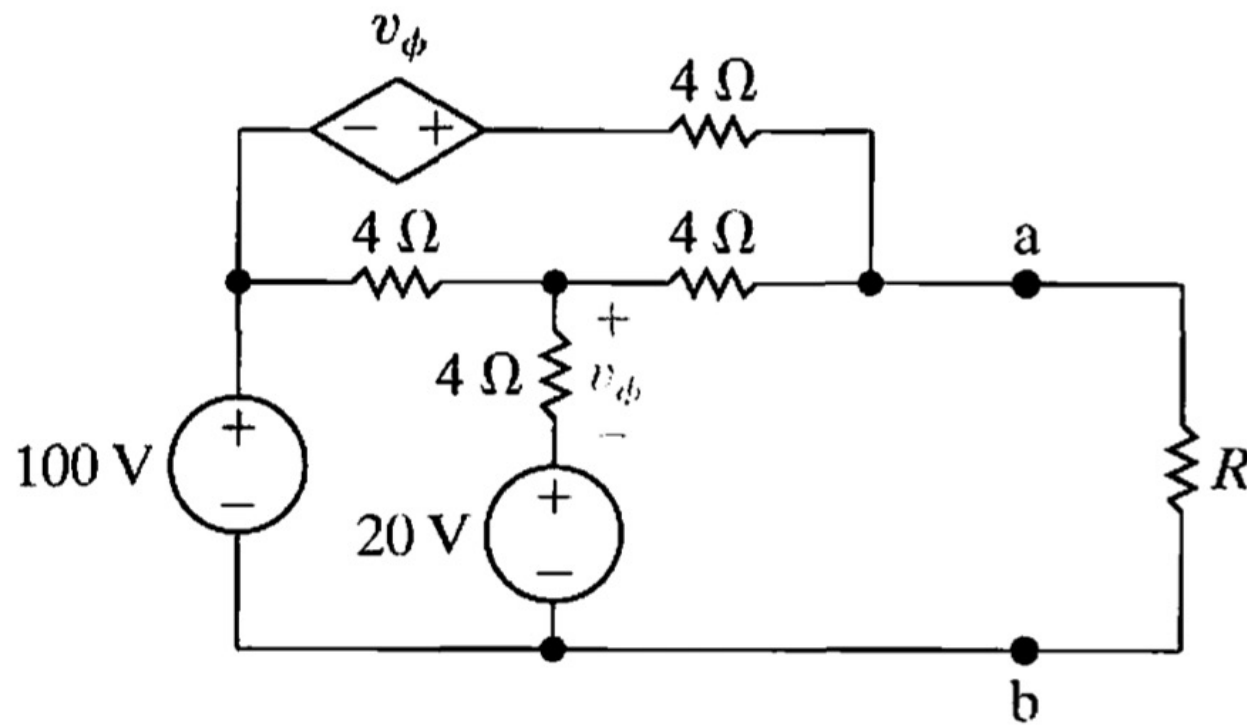Practice problem: maximize the power to R



$4\text{ k}\Omega, 9\text{ mW}$

Practice problem: maximize the power to R_L

