
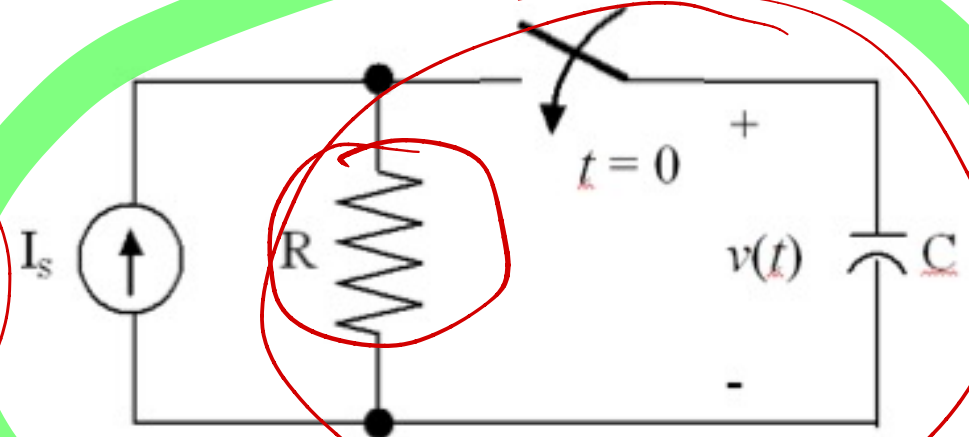


1st Order Transients – 2

general solution

First Order RC Case

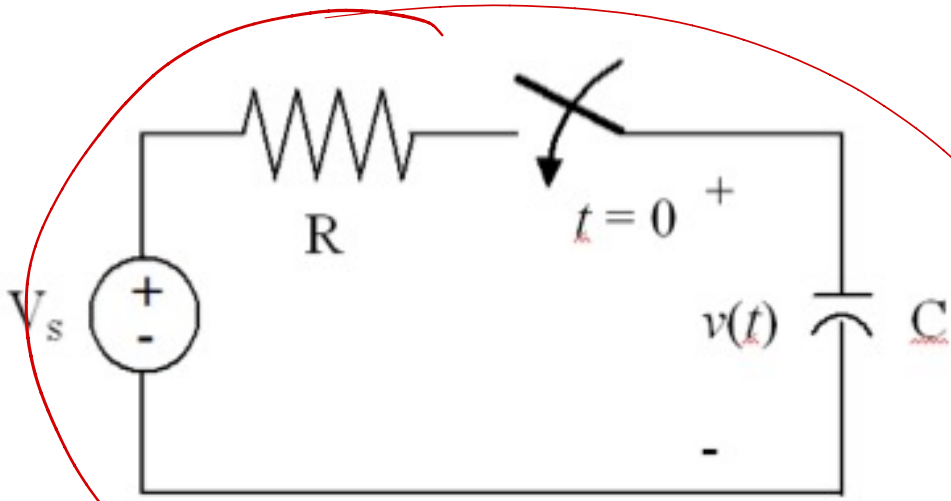


- Thevenin/Norton equivalents

- Solution


$$v(t) = (v_0 - v_\infty) e^{-t/RC} + v_\infty$$

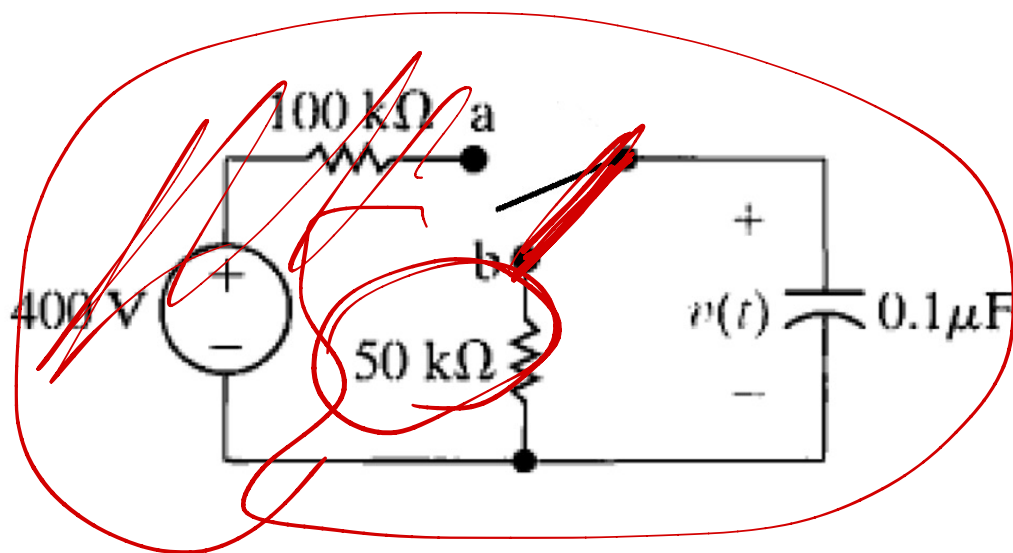Example: switch changes $a \rightarrow b$ at $t = 0$




$$V_0 = 400 \checkmark$$


$$V_\infty = 0$$

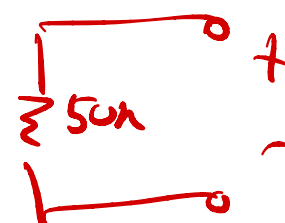
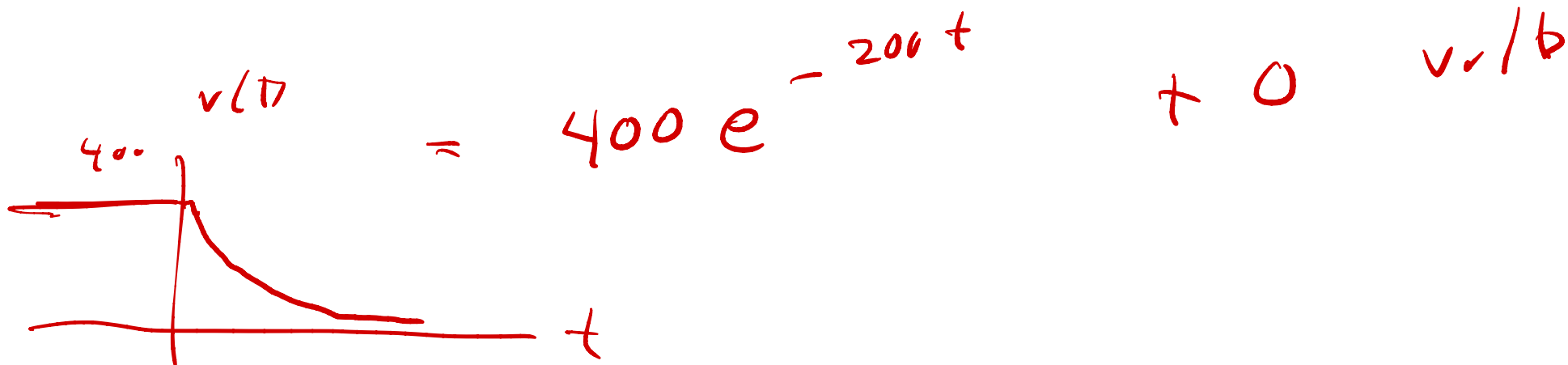
$$v(t) = [V_0 - V_\infty] e^{-t/\tau} + V_\infty$$



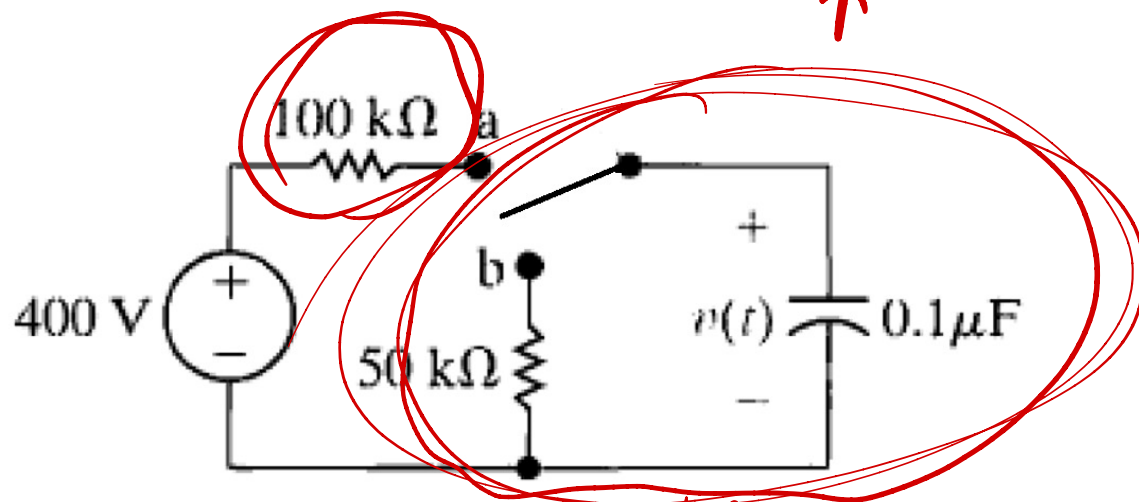Example: switch changes $b \rightarrow a$ at $t = 0$



$$v_C = 0$$

$$v_{\infty} = 400 \text{ V}$$

$$RC = 100 \text{ k} \cdot 0.1 \mu\text{F}$$


$$= 10^5 \cdot 10^{-7}$$

$$= 10^{-2}$$



$$v(t) = [v_C - v_a] e^{-t/\tau} + v_{\infty}$$

$$b \rightarrow a \quad -400 e^{-100t} + 400 \text{ V}$$
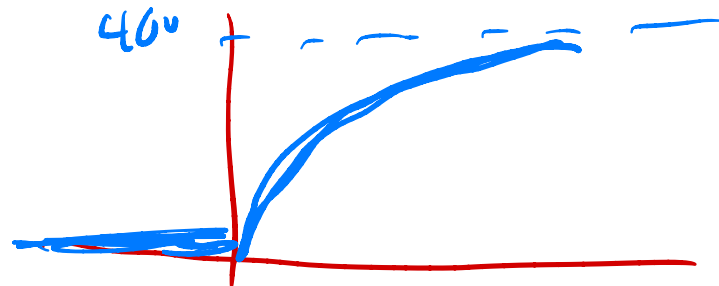
$$a \rightarrow b \quad 400 e^{-200t} \text{ V}$$




First Order RL Case

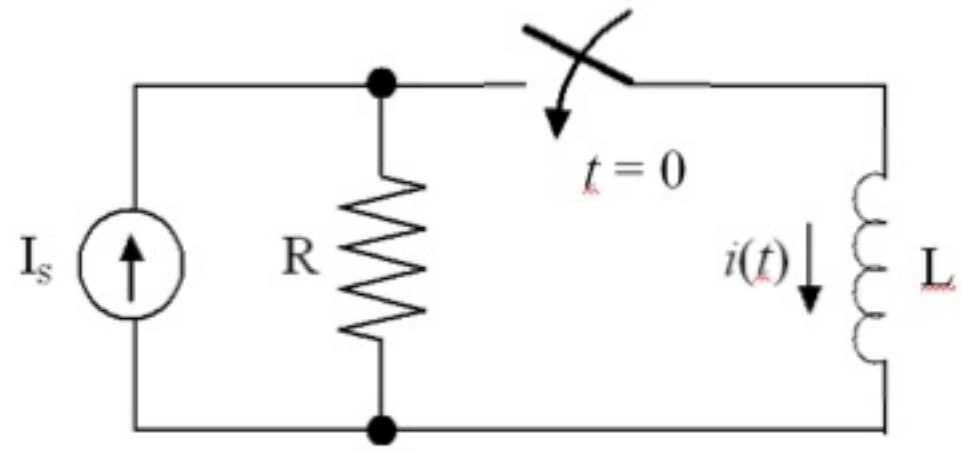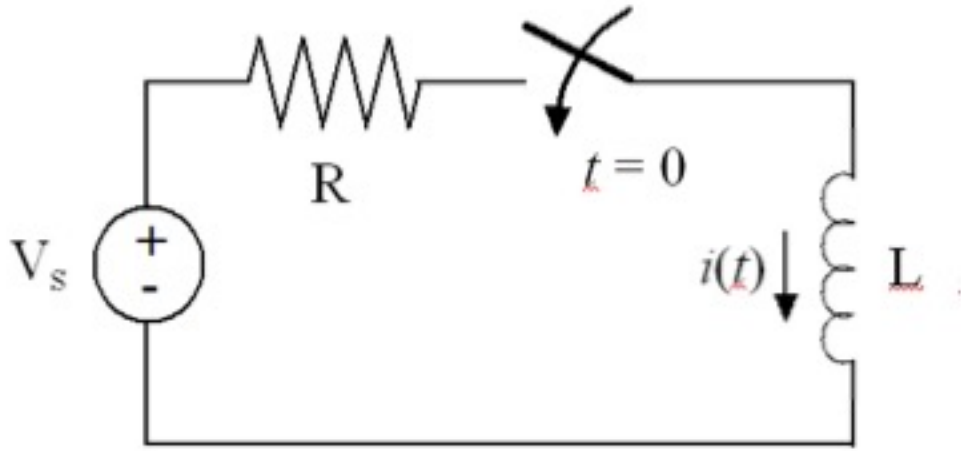

- Loop KVL equation: $\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{1}{R} V_s$


- Solution: $i(t) = \underline{(i_0 - i_\infty)} e^{-\frac{R}{L} t} + \underline{i_\infty}$

Example: switch opens at $t = 0$

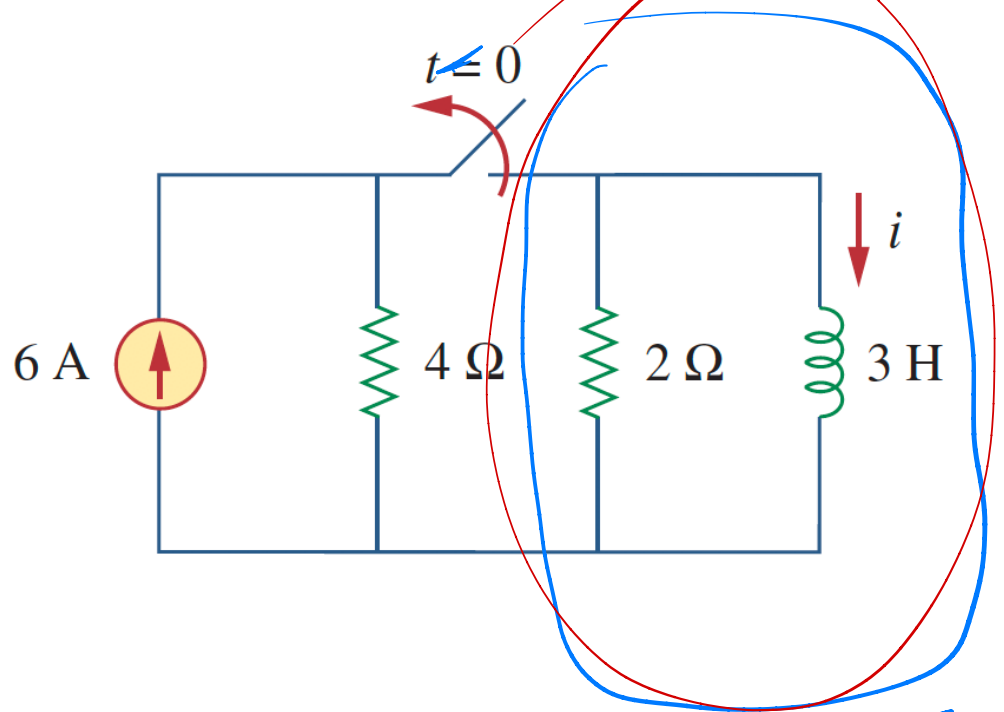

$$i_0 = 6 \text{ A}$$

$$i_\infty = 0 \text{ A}$$

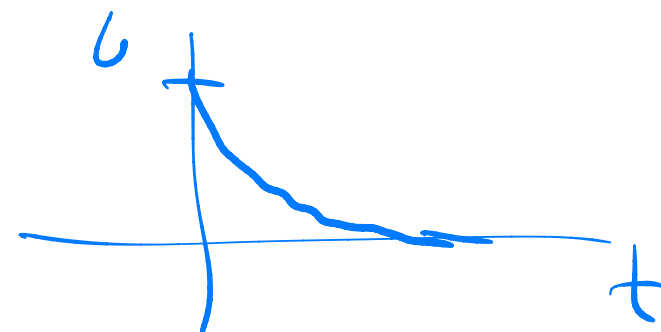


$$i(t) = [i_0 - i_\infty] e^{-\frac{R}{L}t}$$

$$= 6 e^{-\frac{2}{3}t} + 0 \text{ A}$$


$$v_o(t) = \left[\cancel{v(0^-)} - \cancel{v(\infty)} \right] e^{-t/\tau_c} + \cancel{v(\infty)}$$

Example: switch closes at $t = 0$

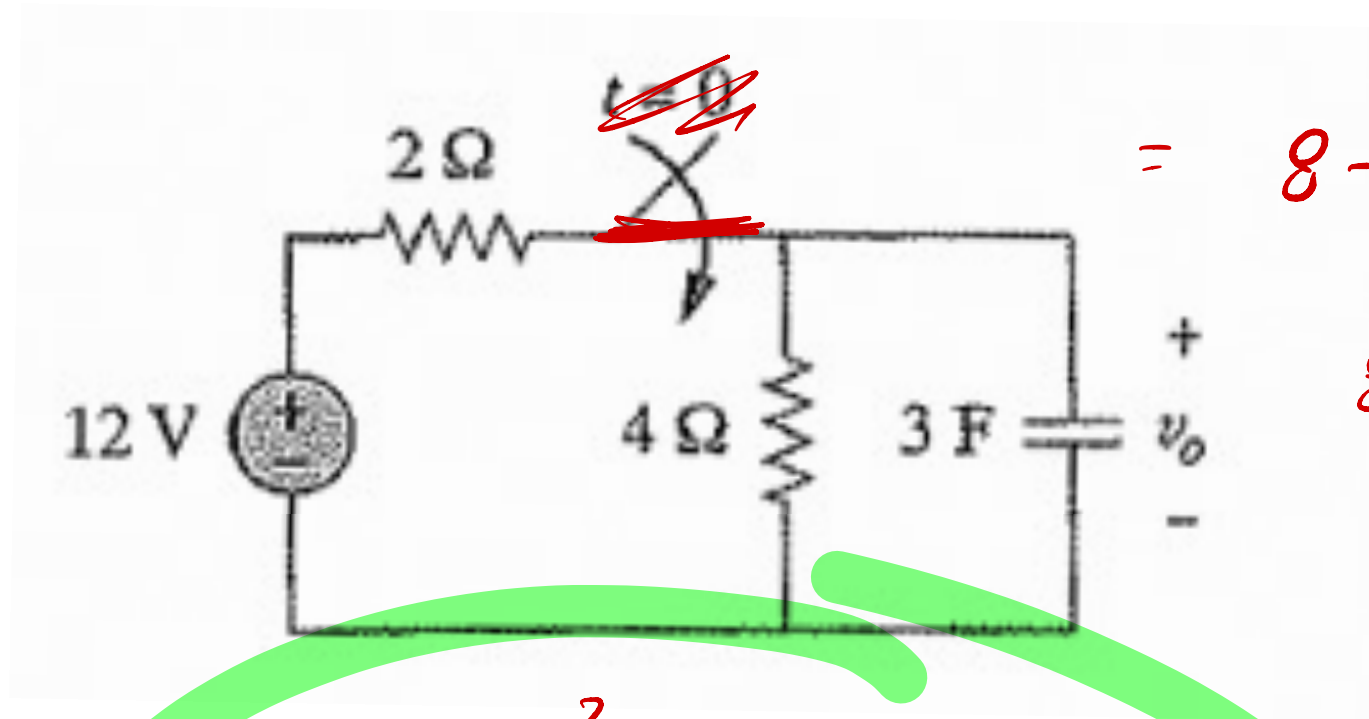


$$= 8 - 8e^{-t/\tau_c} \quad v_o(t)$$
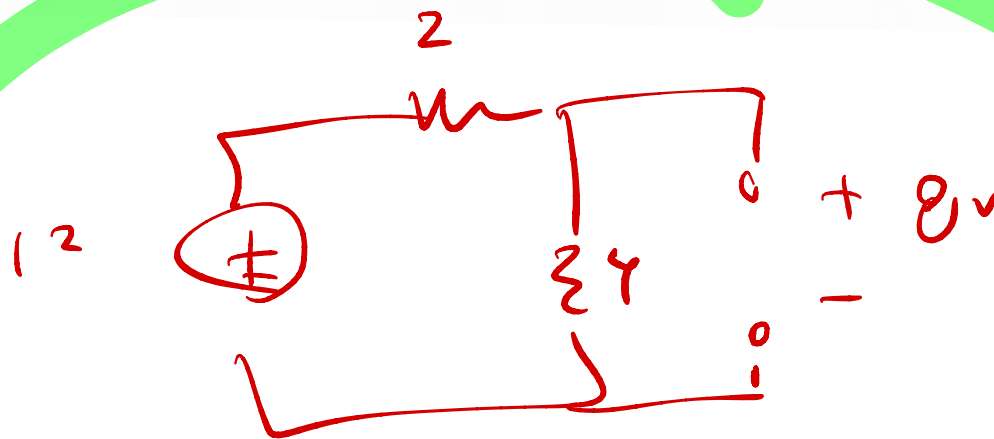
$$\underline{\underline{8 - 8e^{-t/4} \quad v_o(t)}}$$



General Result – 1st Order

- Inductor current or capacitor voltage, $x(t)$ for $t > 0$

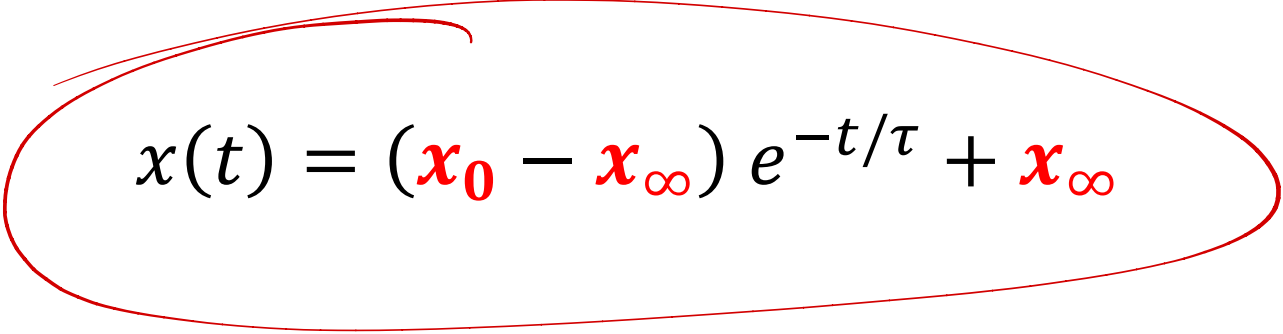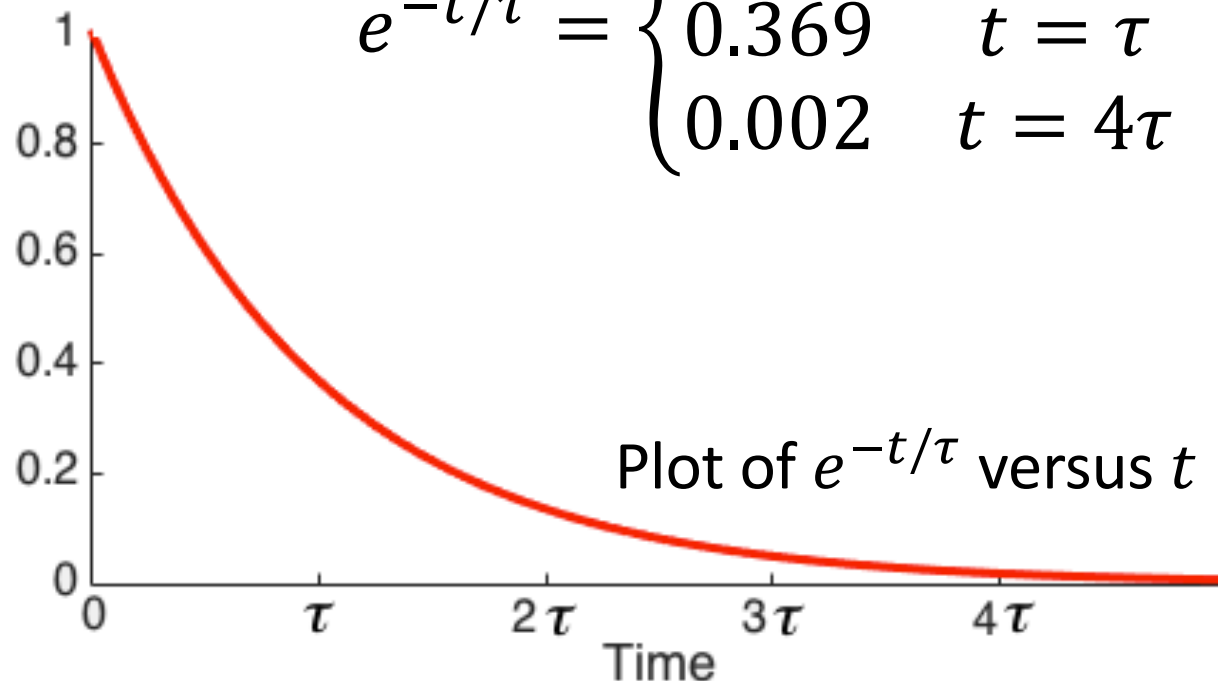

$$x(t) = (\mathbf{x_0} - \mathbf{x_\infty}) e^{-t/\tau} + \mathbf{x_\infty}$$

- Final and initial values, $\mathbf{x_\infty}$ and $\mathbf{x_0}$:
 - From a DC analysis based on “open” or “short” models for C and L
 - Initial value exploits the continuity of capacitor voltages and inductor currents at $t = 0$


$$x(t) = (x_0 - x_\infty) e^{-t/\tau} + x_\infty$$

- Time constant τ ($= L/R$ or RC)
- Why this form?

$$e^{-t/\tau} = \begin{cases} 1 & t = 0 \\ 0.369 & t = \tau \\ 0.002 & t = 4\tau \end{cases}$$




What if the Circuit is more Complex?

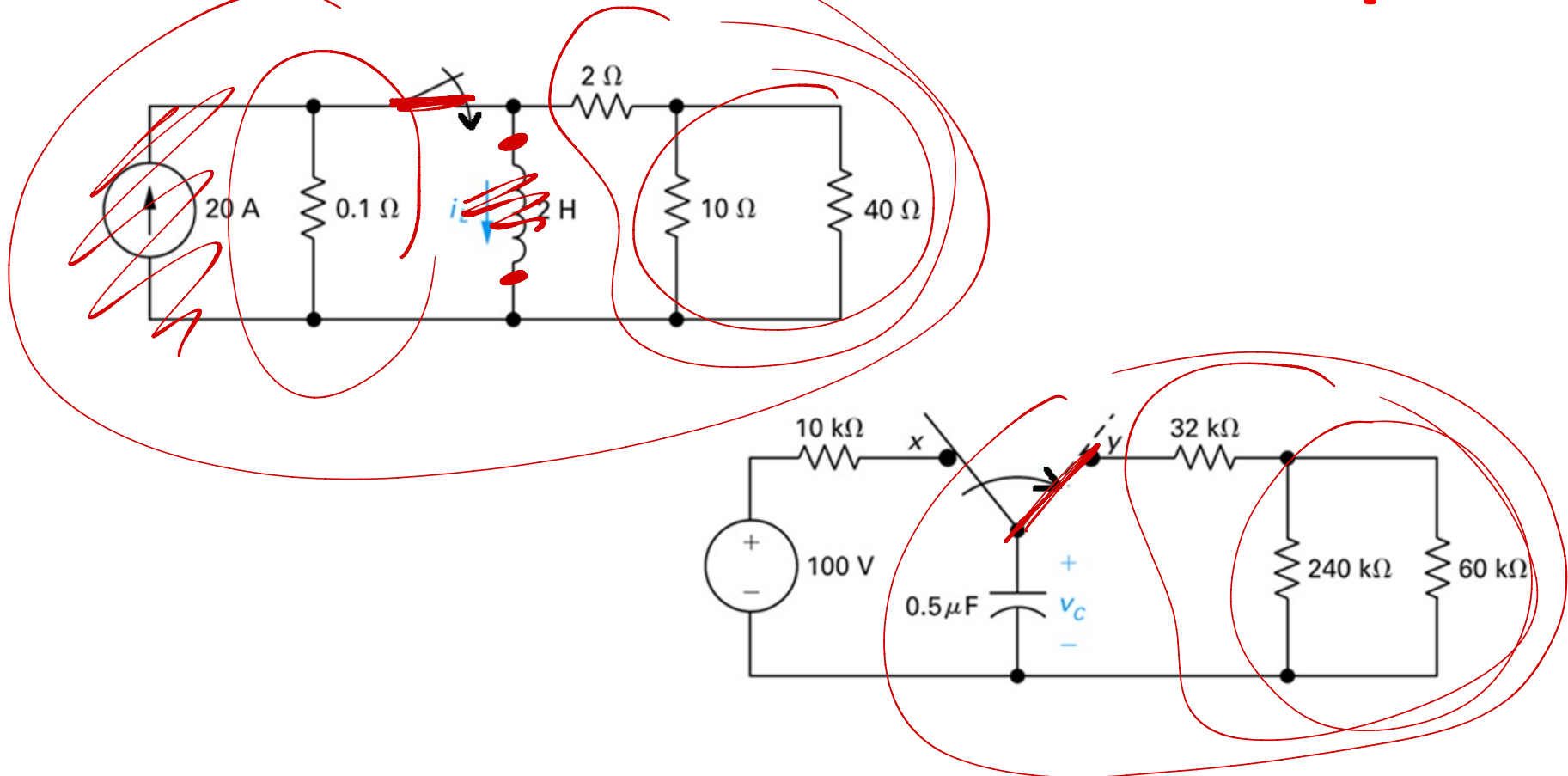

- Use the Thevenin equivalent circuit seen by L or C
 - Time constant $\tau = L/R_{Th}$ or $R_{Th}C$

Worked example

– find $i(t)$

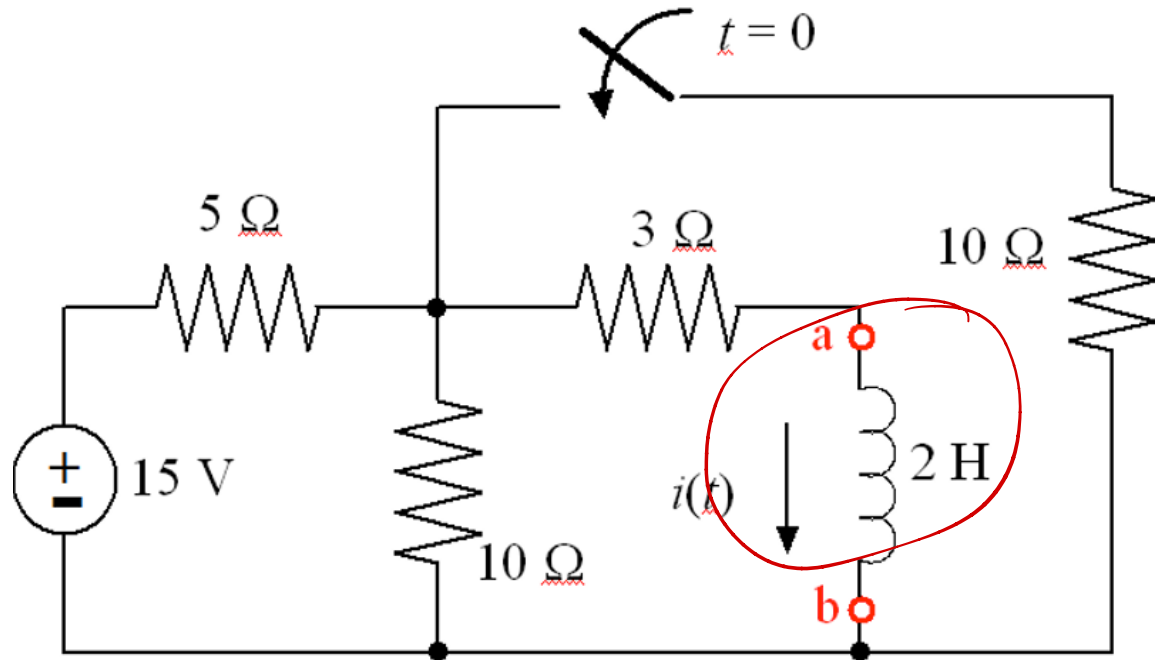


$$i(t) = (i_0 - i_\infty) e^{-t/\tau} + i_\infty$$

- Need: τ , i_∞ , and i_0



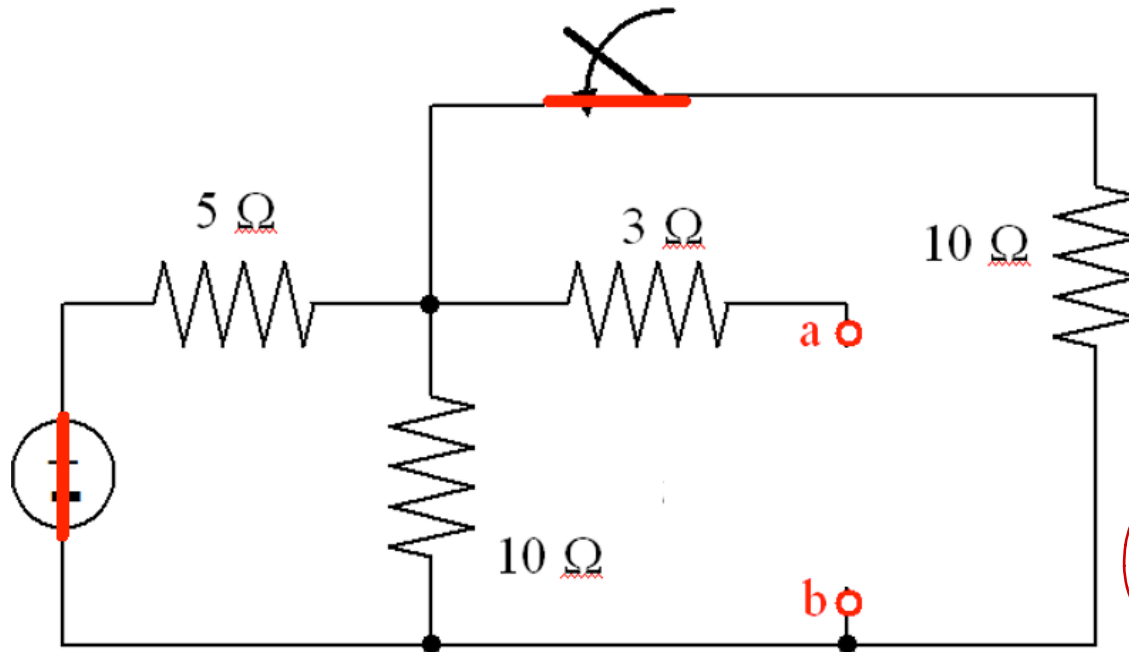
Step 1 – time constant $\tau = \frac{L}{R_{Th}}$



$$\begin{aligned} R_{Th} &= 3 + 5 || 10 || 10 \\ &= 3 + 5 || 5 \\ &= 5.5\ \Omega \end{aligned}$$

$$\tau = \frac{2}{5.5} = \frac{1}{2.75} \text{ sec}$$

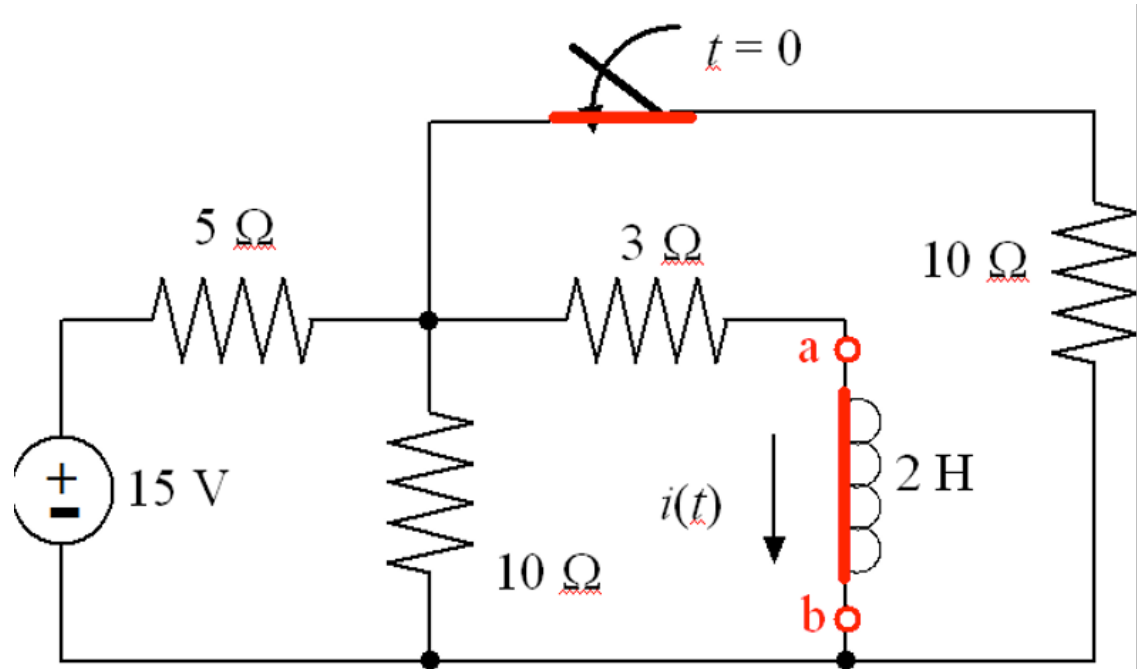
Step 2 – final value i_{∞} ; as $t \rightarrow \infty$



$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} + \frac{v}{10} = 0 \Rightarrow v = \frac{45}{11}$$

$$i_{\infty} = \frac{v}{3} = \frac{15}{11} = 1.36 \text{ amps}$$


Step 3 – initial value i_0

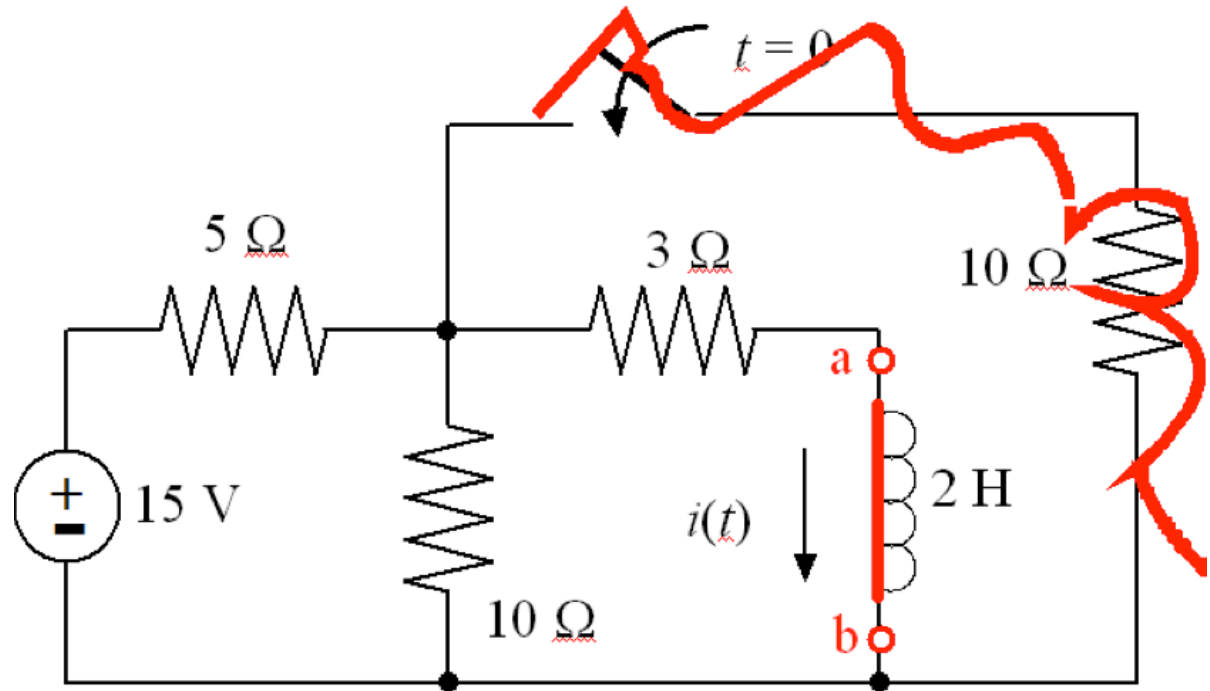


$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} = 0 \Rightarrow v = \frac{90}{19}$$

$$i_0 = \frac{v}{3} = \frac{30}{19} = 1.58 \text{ amps}$$


Combining

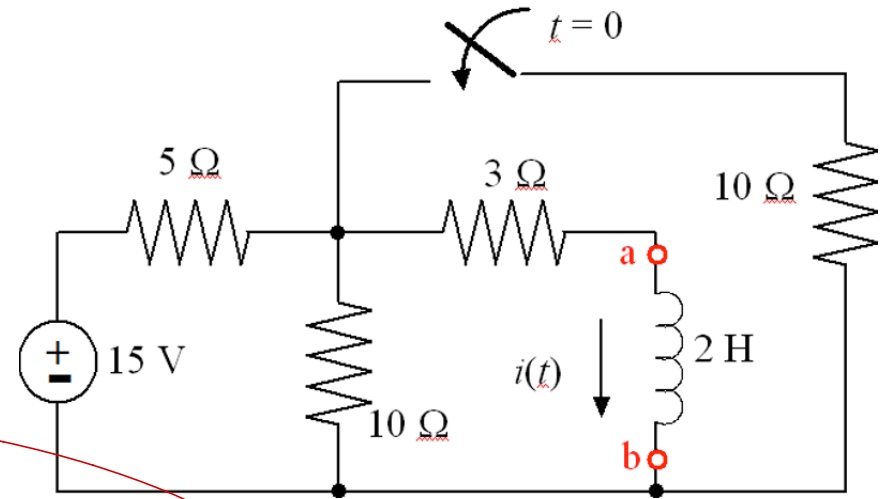

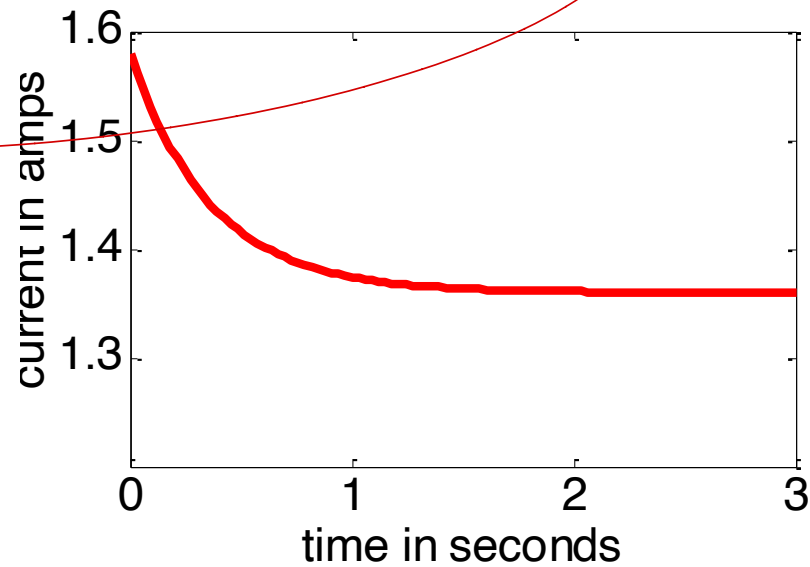
$$i(t) = (i_0 - i_\infty) e^{-2.75 t} + i_\infty$$
$$= 0.22 e^{-2.75 t} + 1.36 \text{ amps}$$



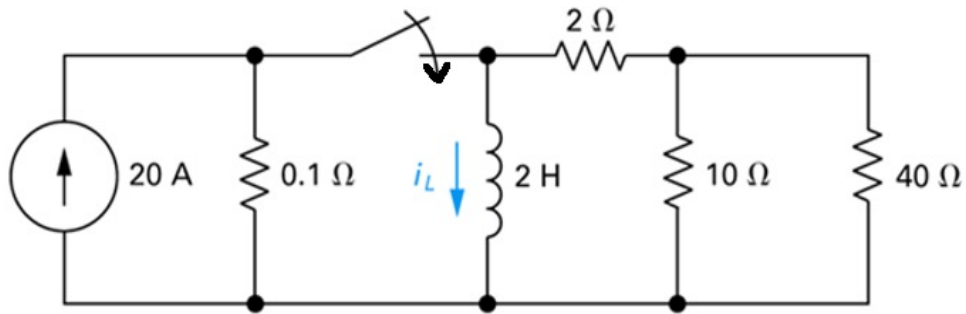
Practice problem: find the inductor current




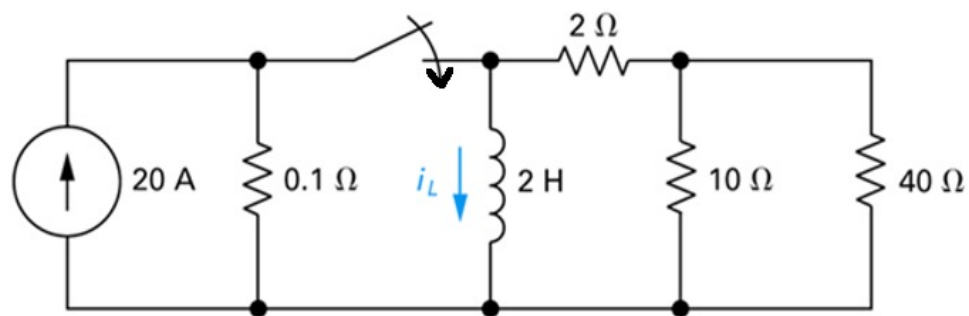

$$\begin{aligned}
 i(0^+) &= 0\text{ A} \\
 i(\infty) &= 20\text{ A} \\
 R_{Th} &= 0.0990\ \Omega
 \end{aligned}$$

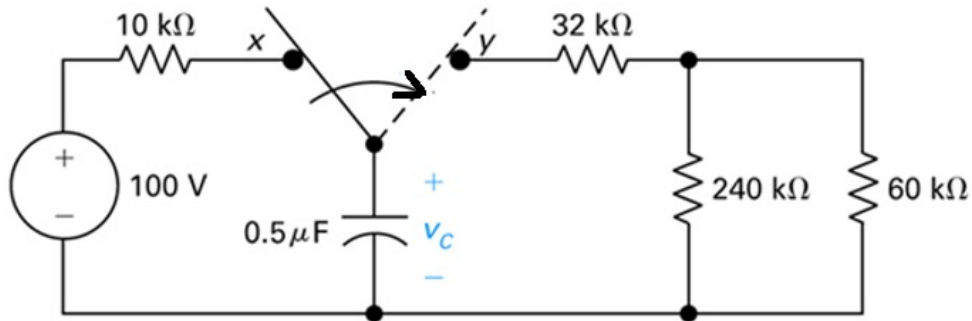Practice problem: find the capacitor voltage



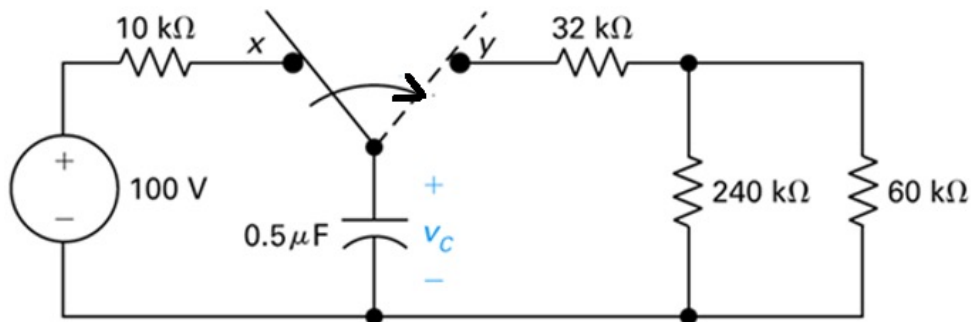

$$v(0^+) = 100 \text{ V}$$

$$v(\infty) = 0 \text{ V}$$

$$R_{Th} = 80 \text{ k}\Omega$$