


# Basics – 4

series/parallel resistance;  
voltage/current division

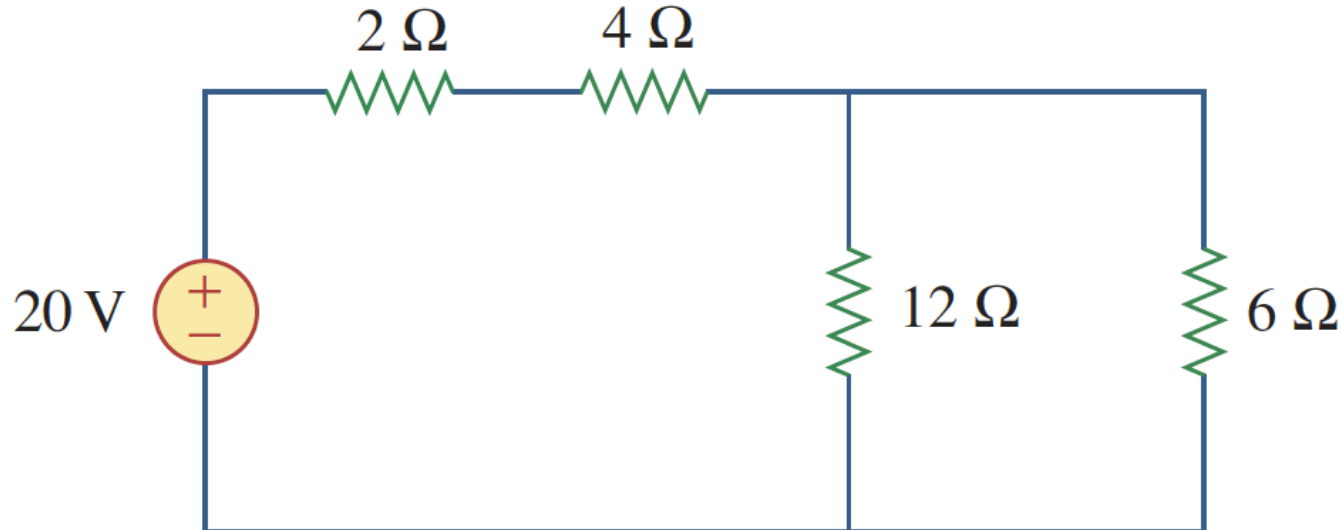
# Applying KCL and KVL

Consider:



- Currents in the 2  $\Omega$  and 4  $\Omega$  resistors (KCL)
- Voltages across the 6 and 12  $\Omega$  resistors (KVL)




# Series Resistors & Voltage Division

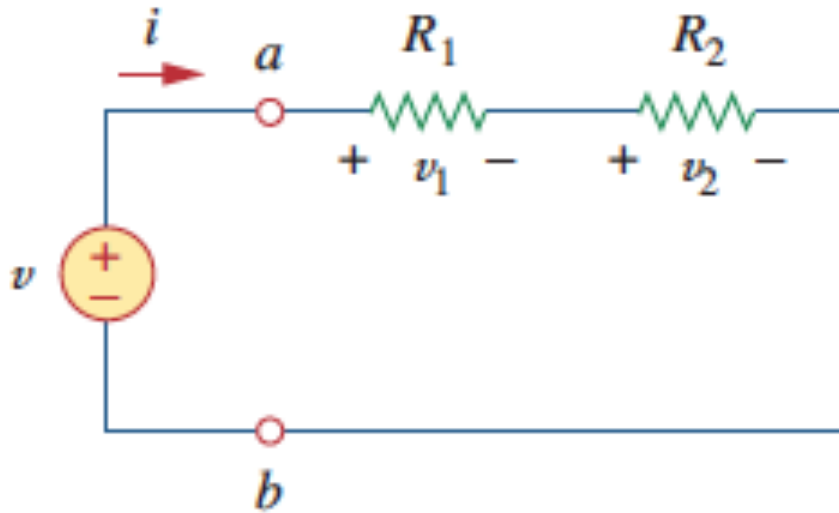


# Examples

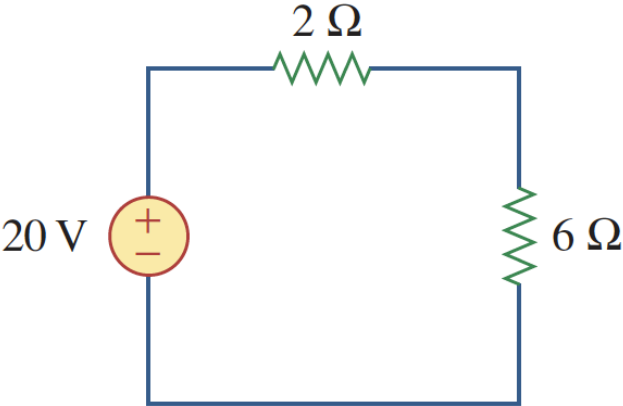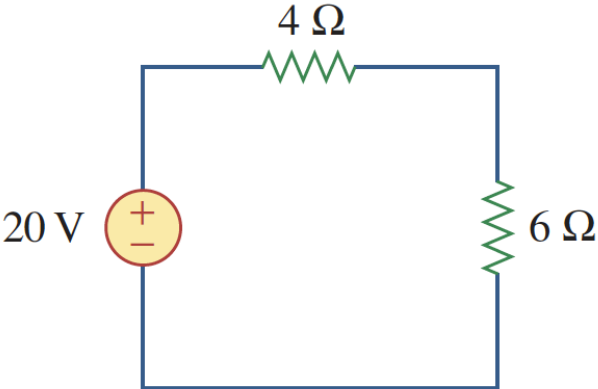



Example:

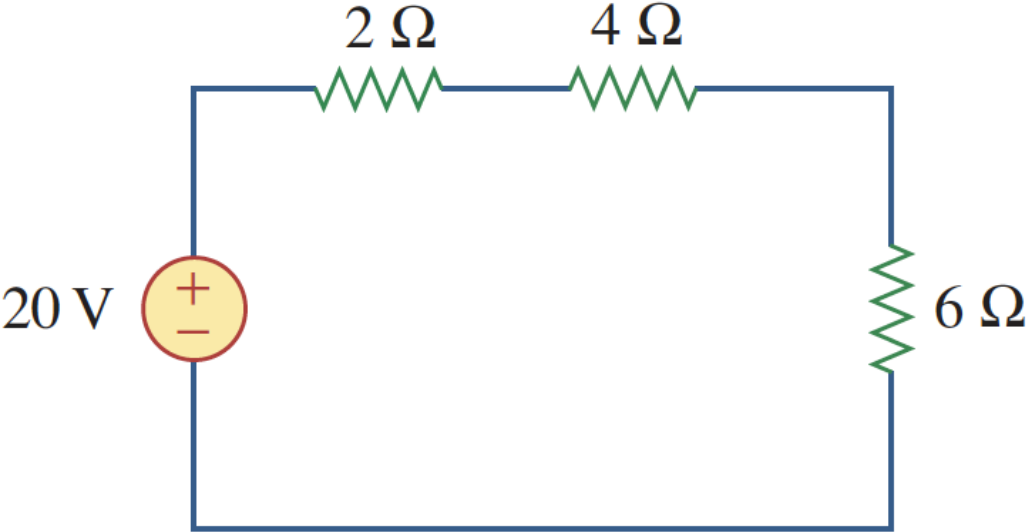


# Parallel Resistors & Current Division

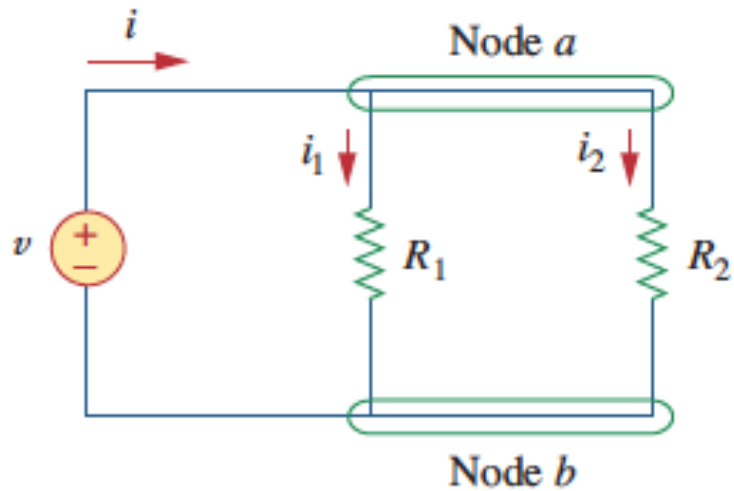

# Examples:

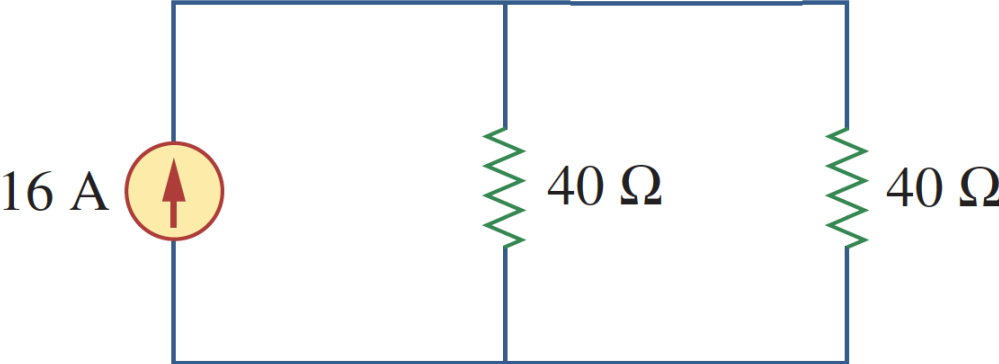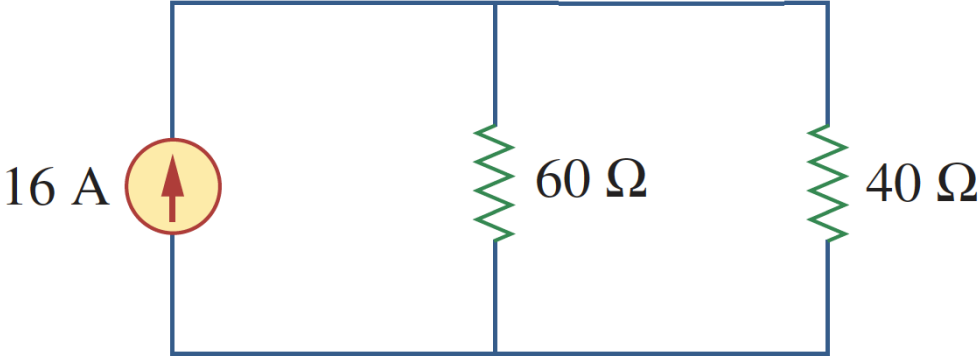



Example:

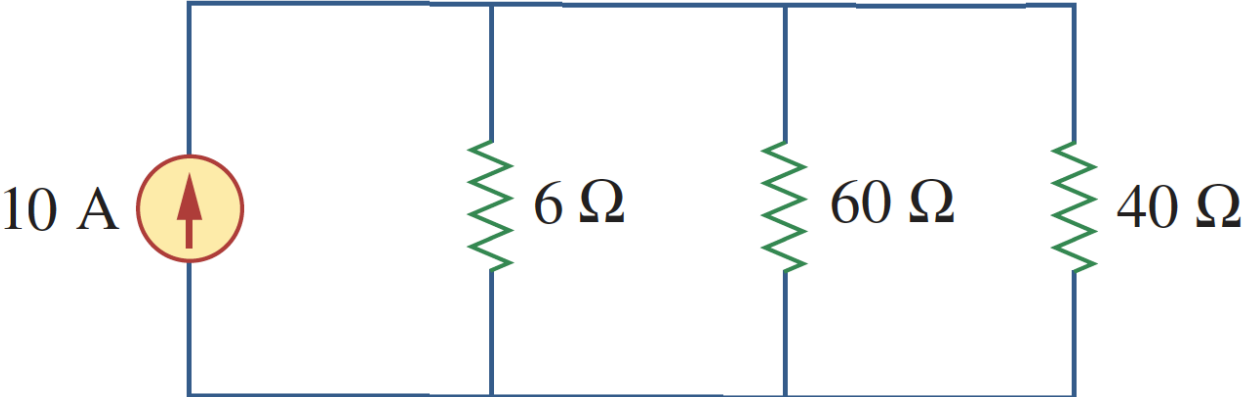



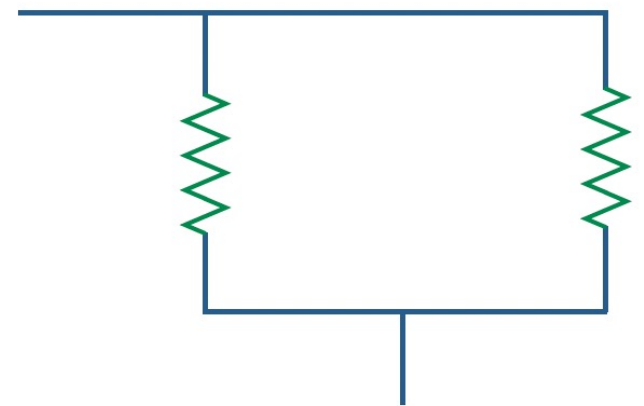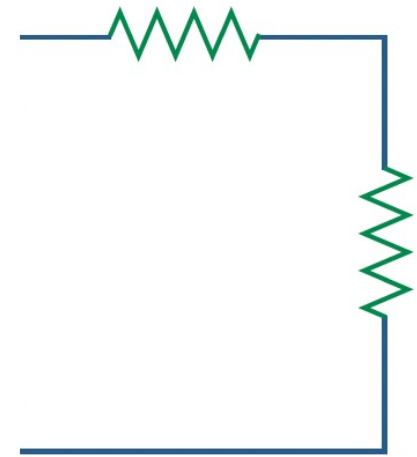
# Series/Parallel Summary

- Series: resistances add
  - Nothing connected in the middle
  - **Same current (KCL)**
  - Voltage divides proportionally
- Parallel: resistances add inversely
  - Connected at both ends
  - **Same voltage (KVL)**
  - Current divides proportionally




$-3.75\text{ V}$


**Example:** find  $v$

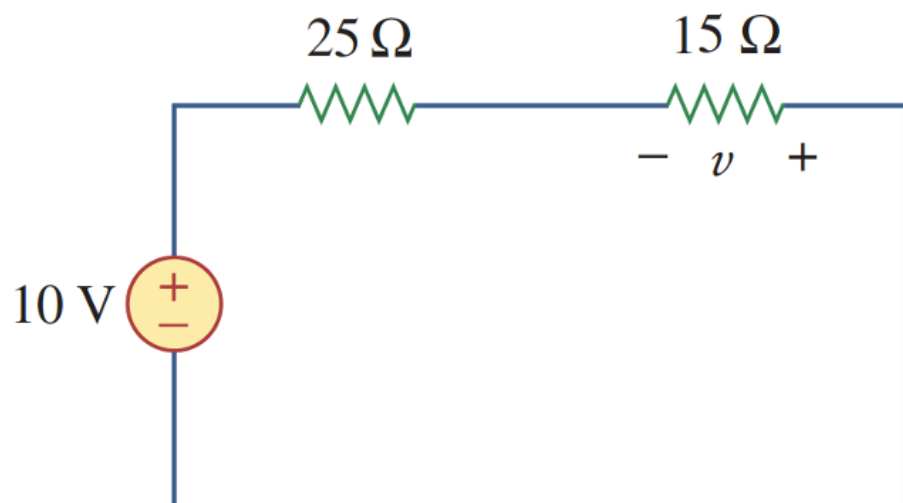

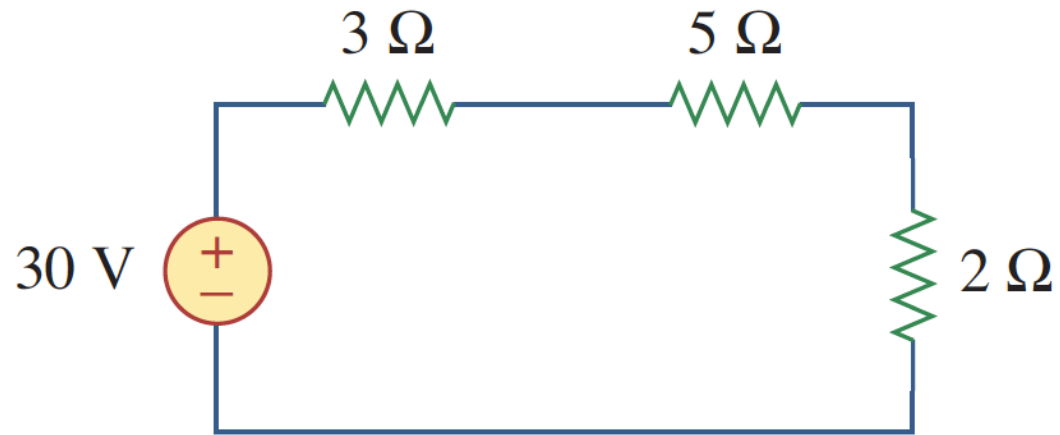**Practice problem:** find the power in the 3  $\Omega$  resistor



**Practice problem:** find  $v$

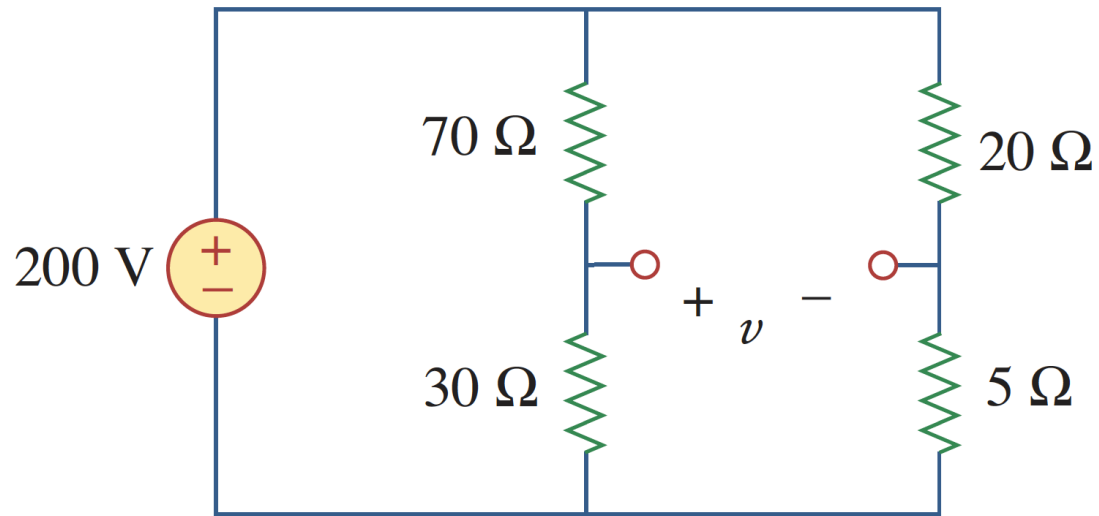

3.2 kW

**Practice problem:** find the power in the 50  $\Omega$  resistor

