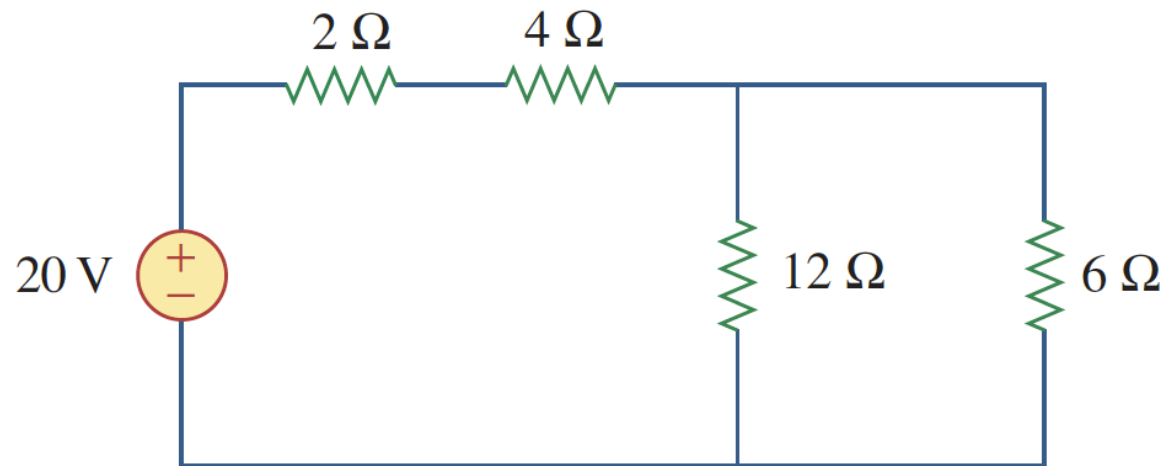


# Basics – 5


equivalent resistance

# Applying Series/Parallel Ideas

- Find the source current




Example: find the source power

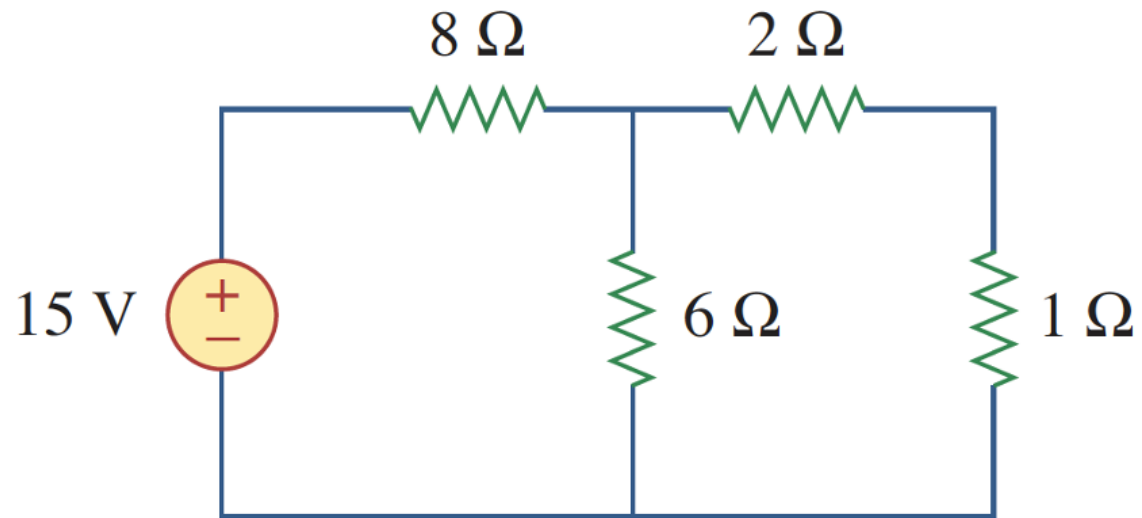

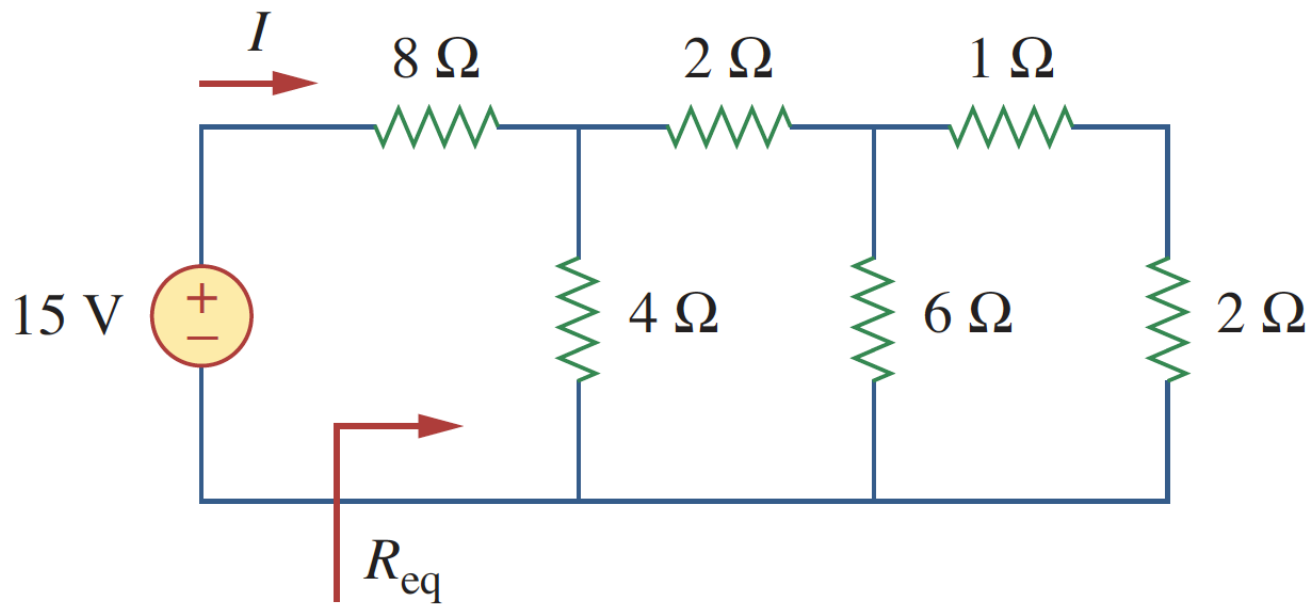
# Equivalent Resistance



- Concept – use series and parallel combining to find  $R_{eq}$ , and hence, to find  $I$




**Example:**

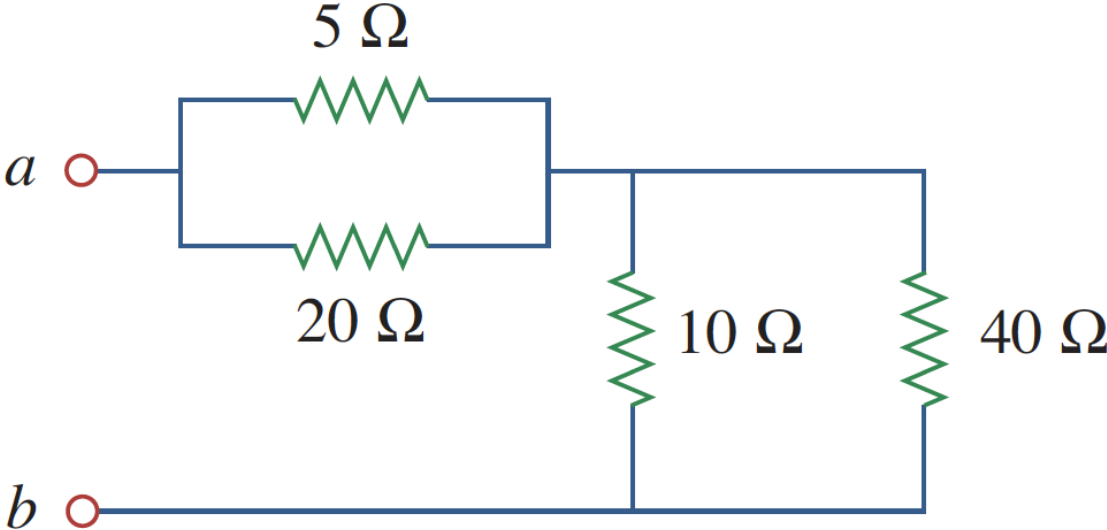

Sometimes the circuit looks strange

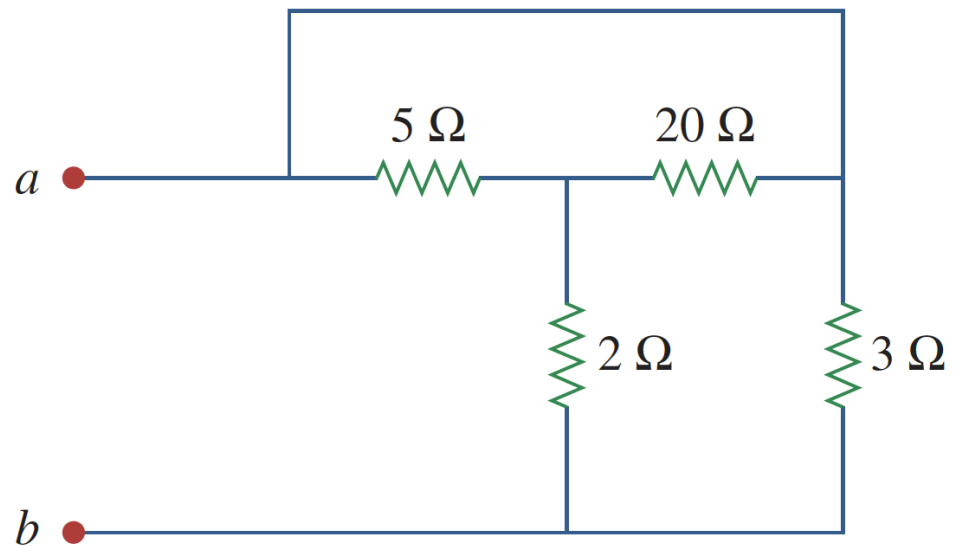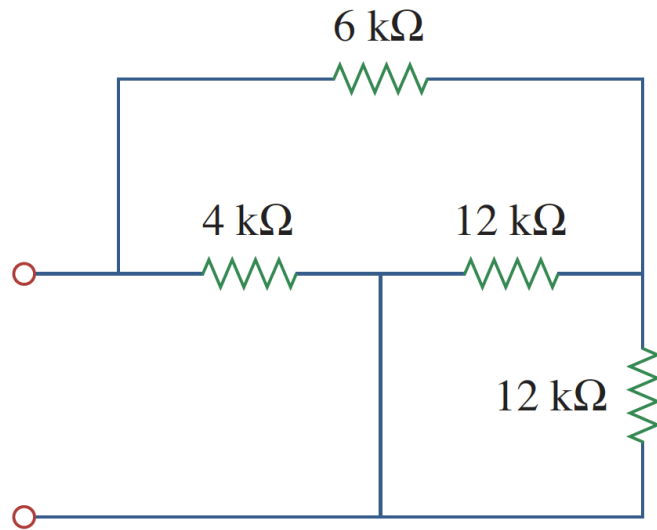


**Example:** find  $R_{eq}$  and  $i_o$

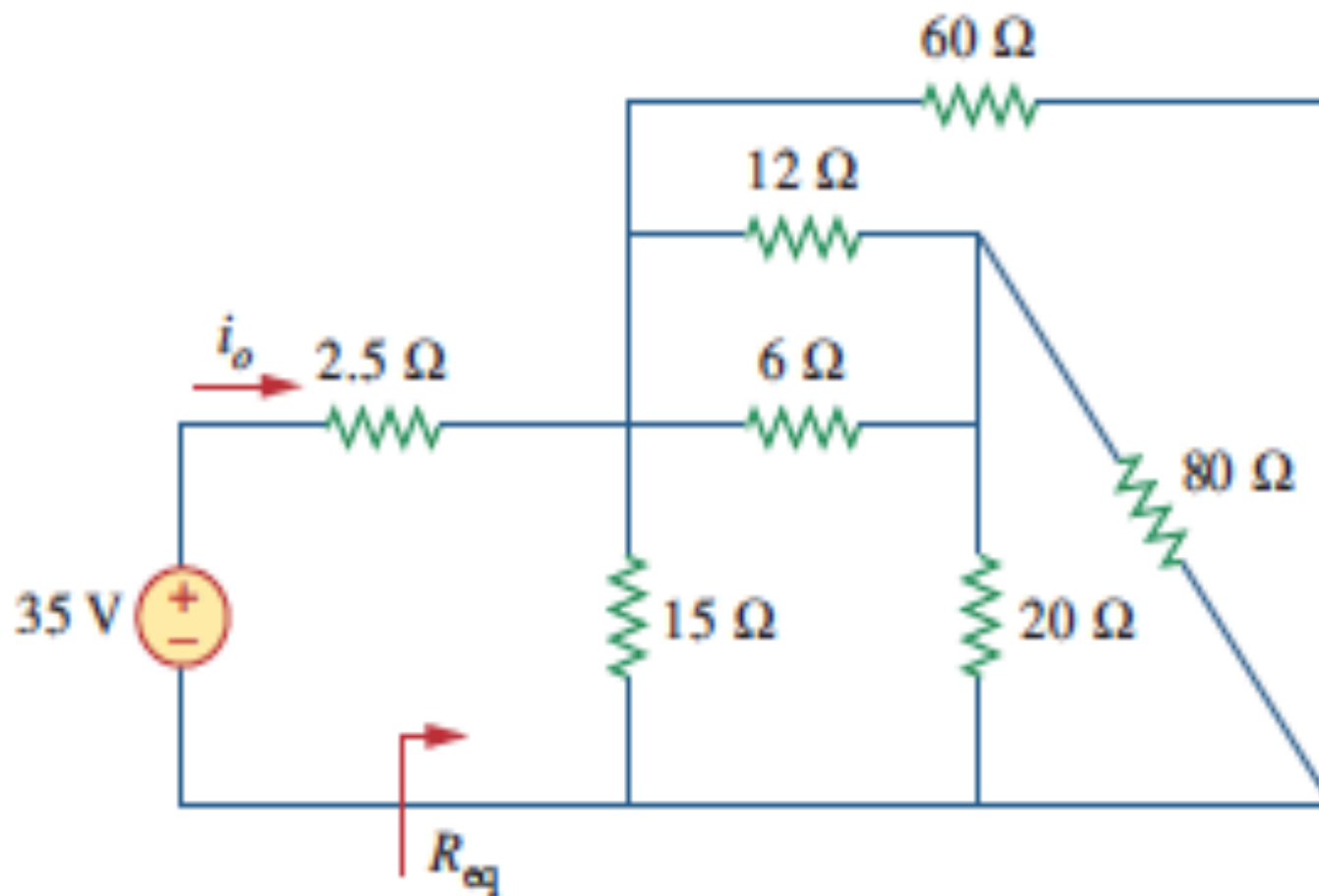

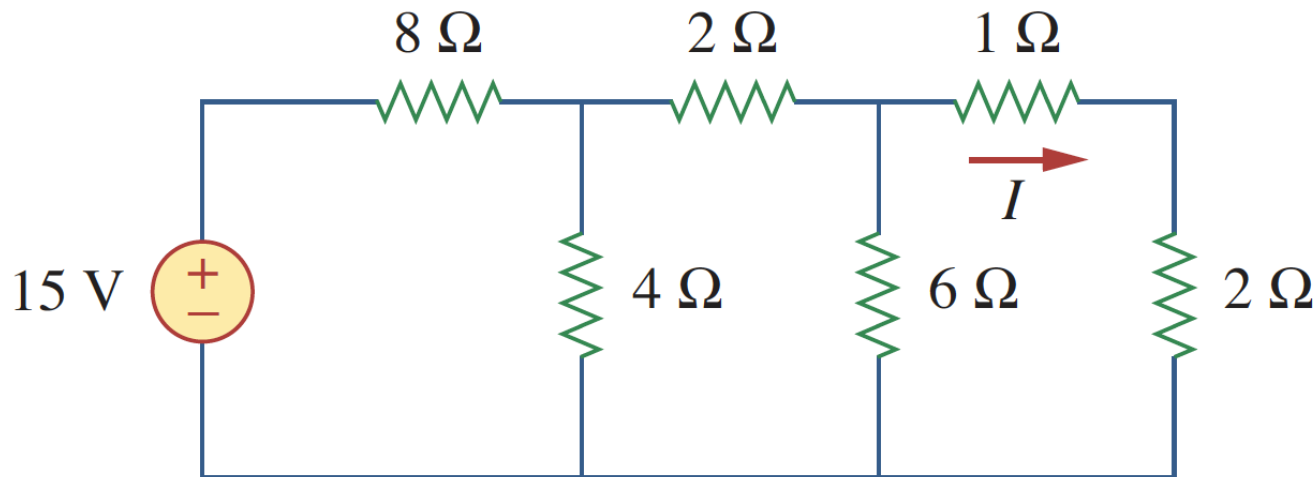
# Circuit Analysis


- Sometimes we can do a full analysis using just series/parallel combining and voltage/current division
- Example: find  $I$  (next slide)





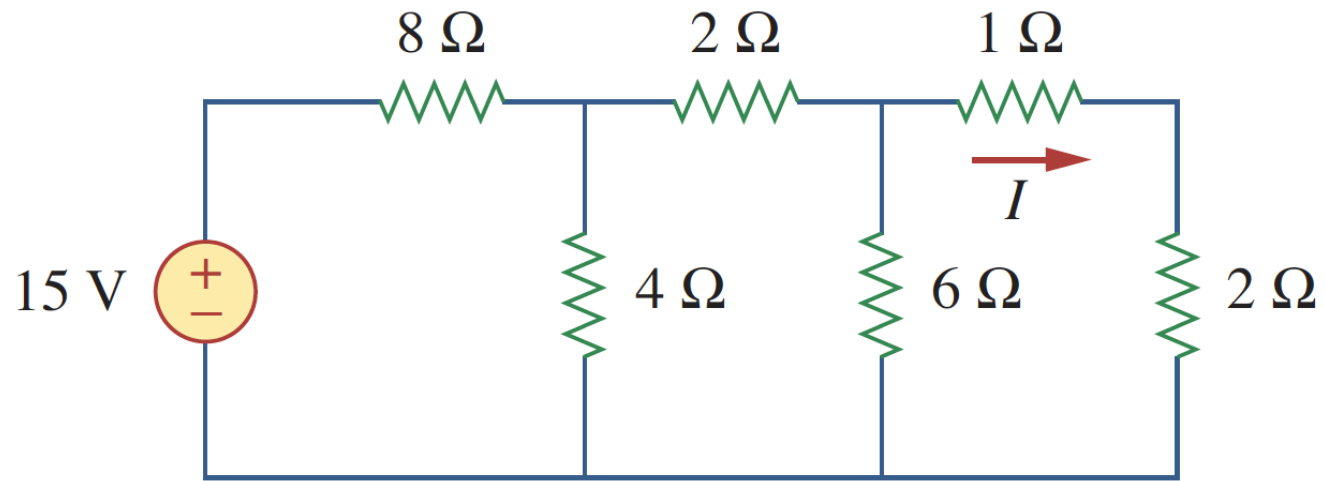

- Work flow:
  - Right to left

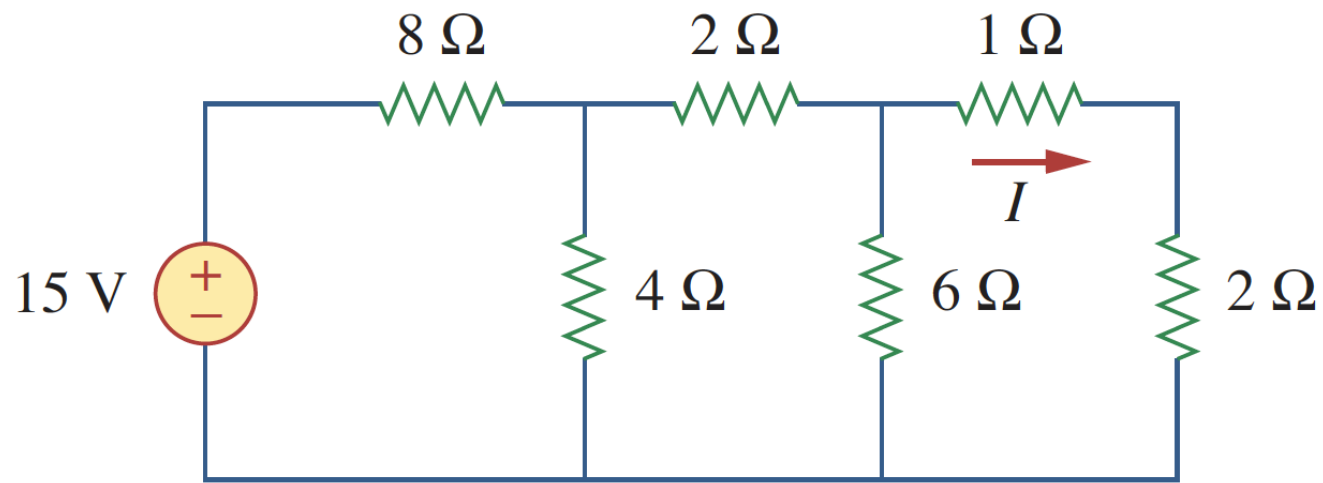


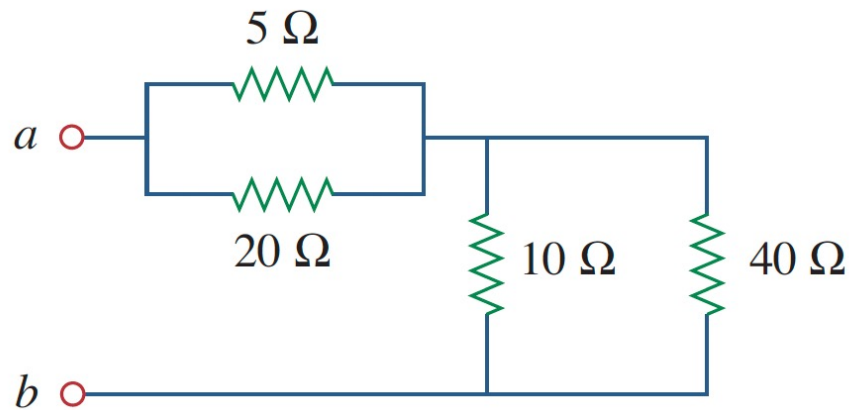0.5 A


- Work flow:
  - Left to right



**Practice problems:** find the equivalent resistances




(a)

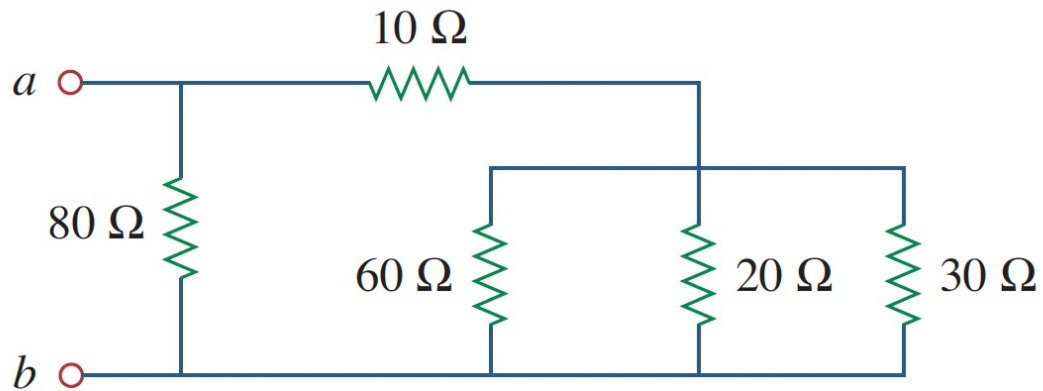


(b)

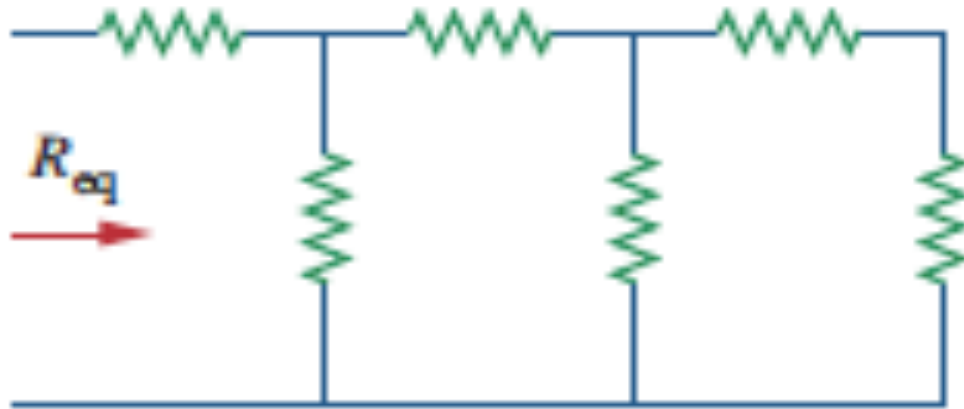**Practice problem:** find  $R_{eq}$  if all resistors are  $8 \Omega$




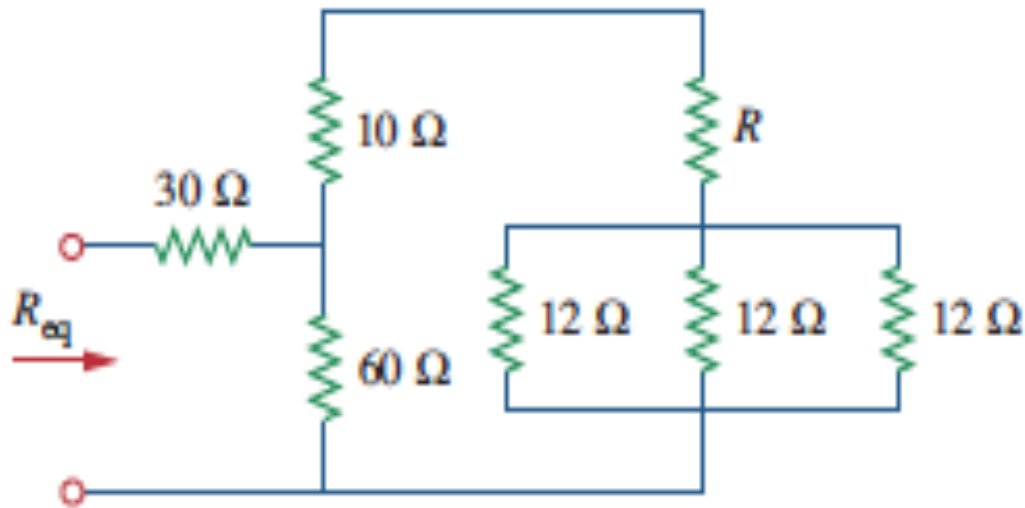**Practice problem:** if  $R_{eq} = 50 \Omega$ , find  $R$




2.5 A

**Practice problem:** find  $I$

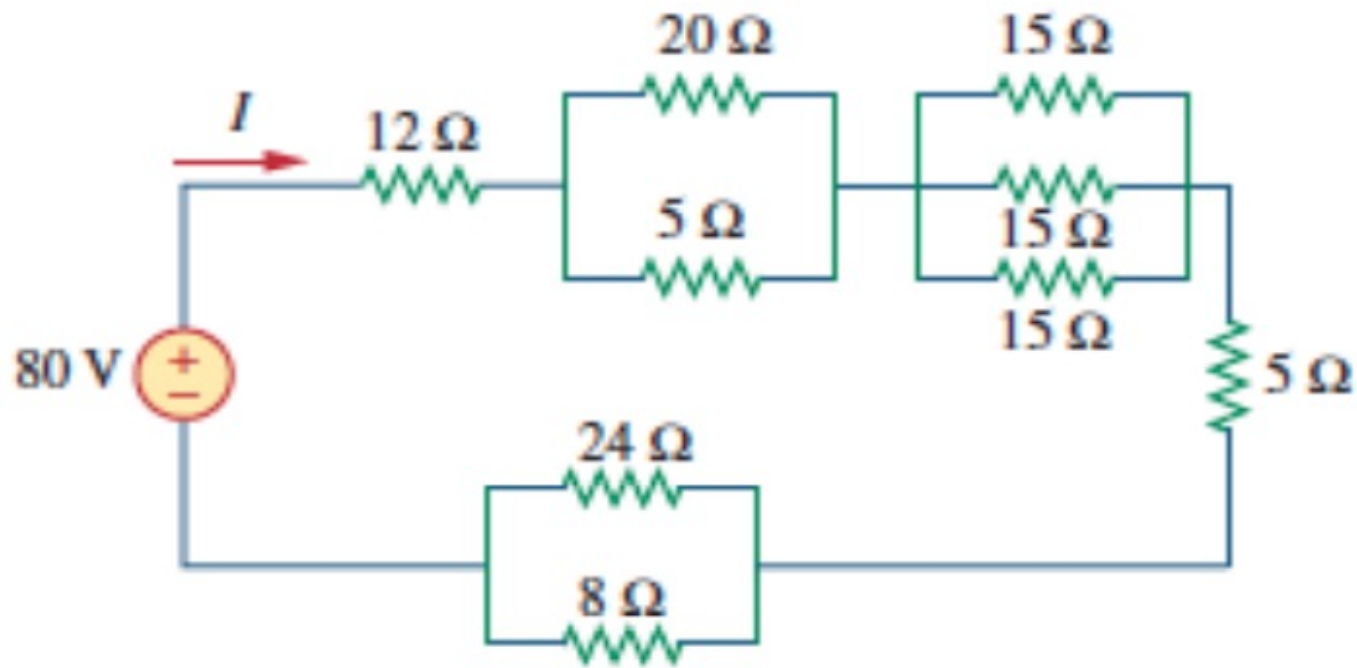

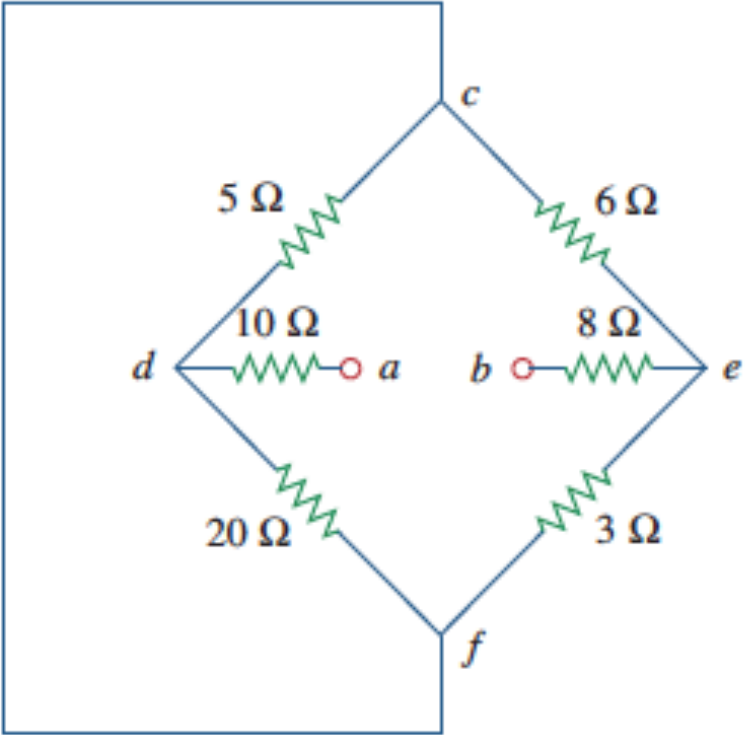
**Practice problem:** find the equivalent resistance at *a-b*





-400 W

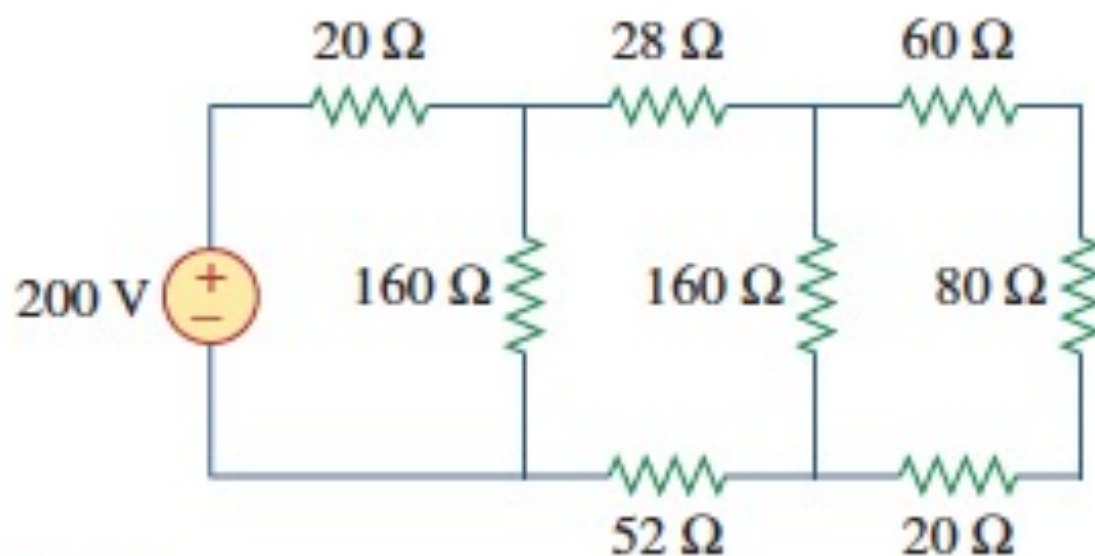**Practice problem:** find the source power



**Practice problem:** find  $v$

