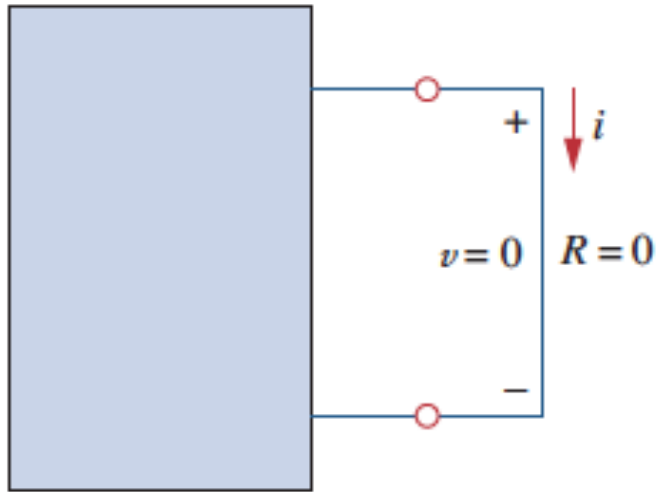


Basics – 7


odds and ends

Special Cases

- Short circuit ($R = 0$)





- Open circuit ($R = \text{infinity}$)

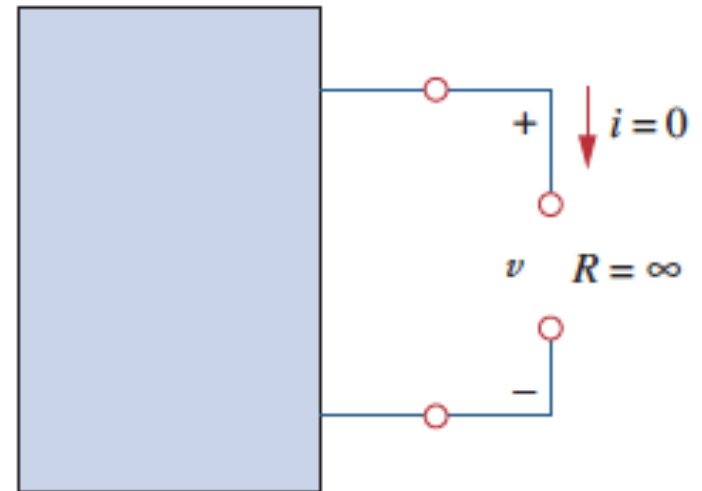

- Voltage division

$$v_1 = \frac{R_1}{R_1 + R_2} v$$



$$v_2 = \frac{R_2}{R_1 + R_2} v$$

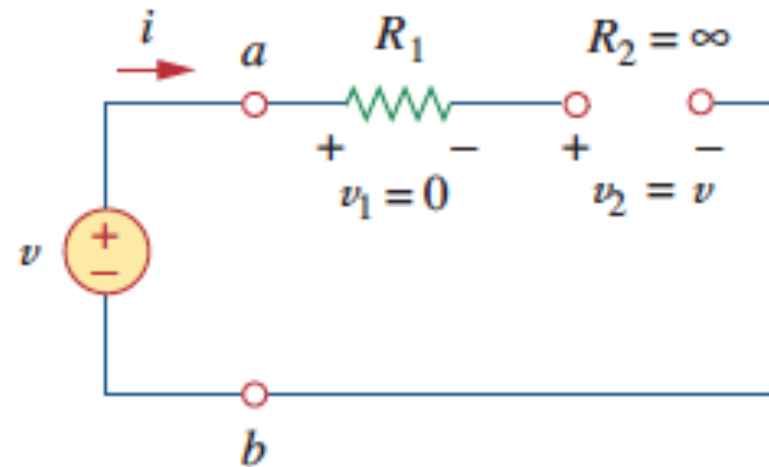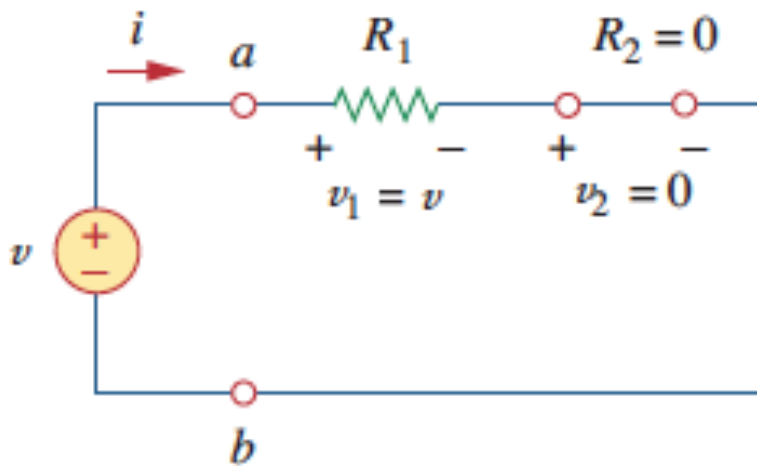


- Current division

$$i_1 = \frac{R_2}{R_1 + R_2} i$$


$$i_2 = \frac{R_1}{R_1 + R_2} i$$

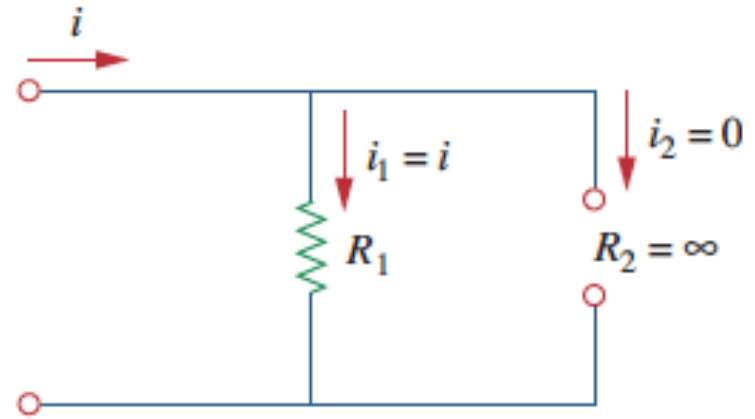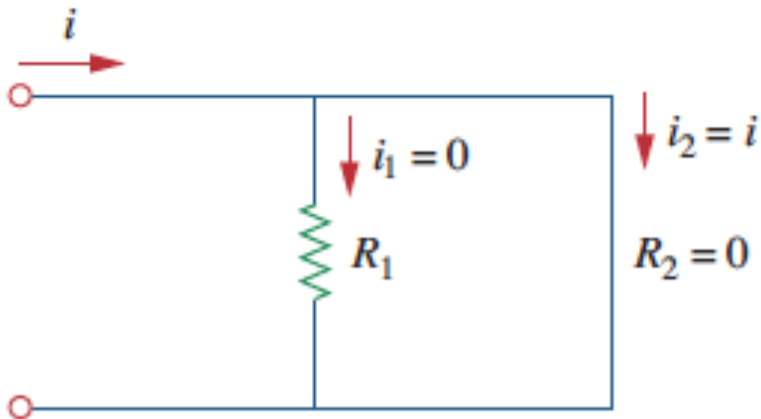


Example:

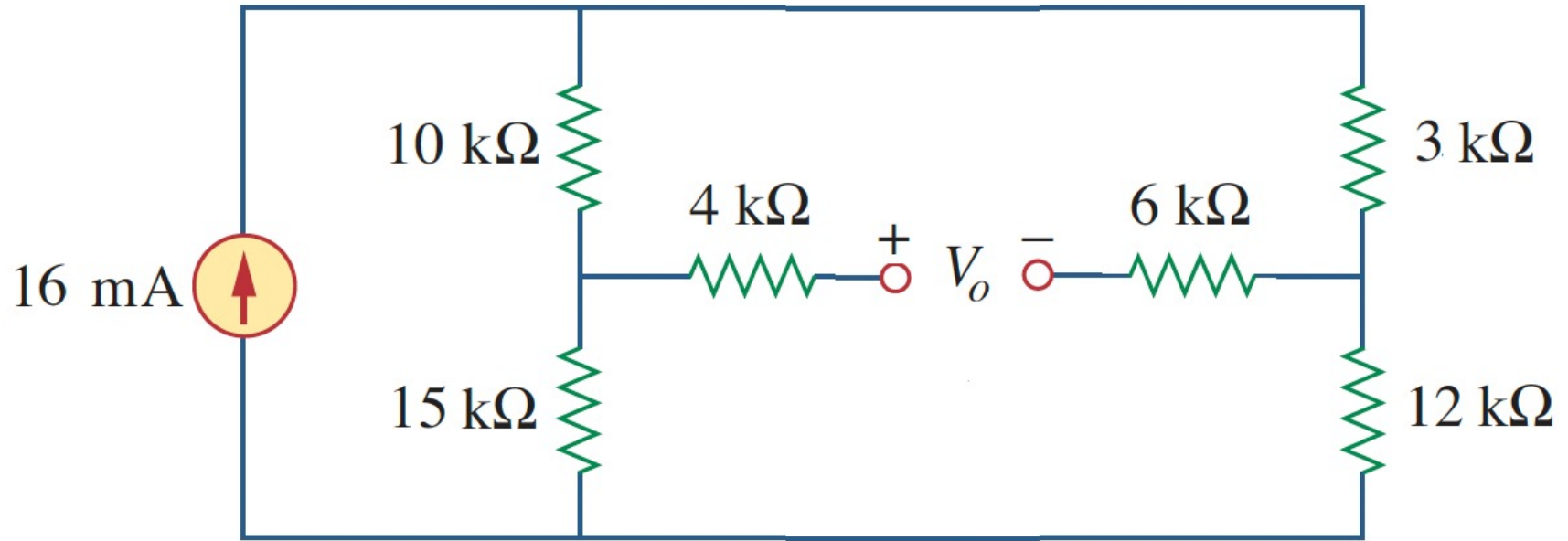


Example: find i and v

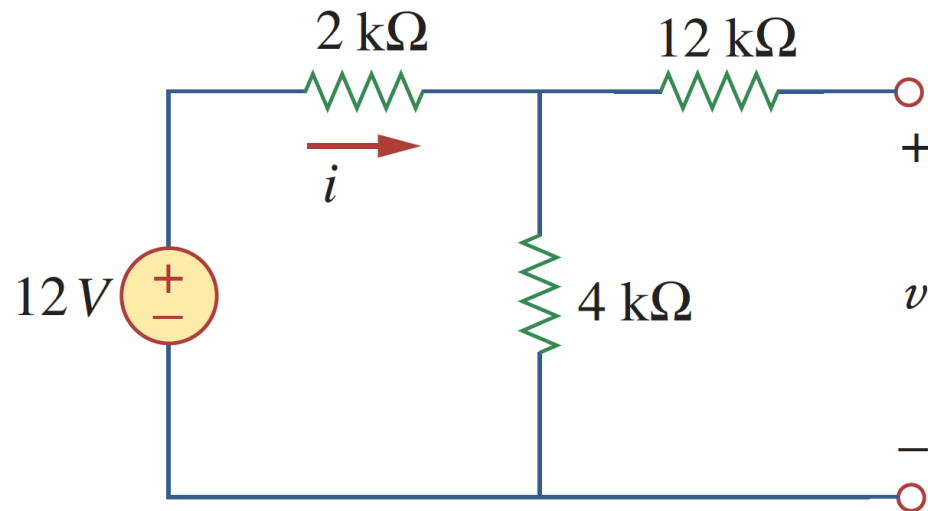


Do We Allow Series Sources?

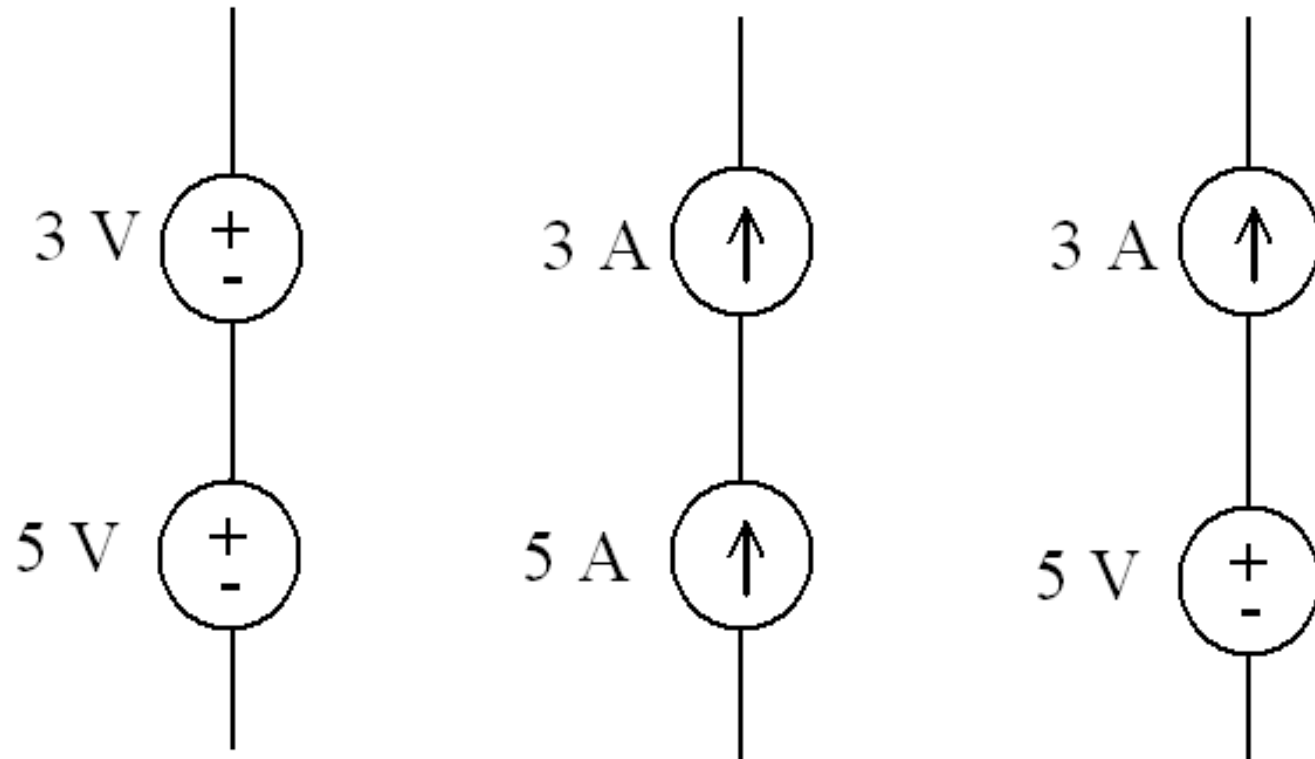


How about parallel sources?

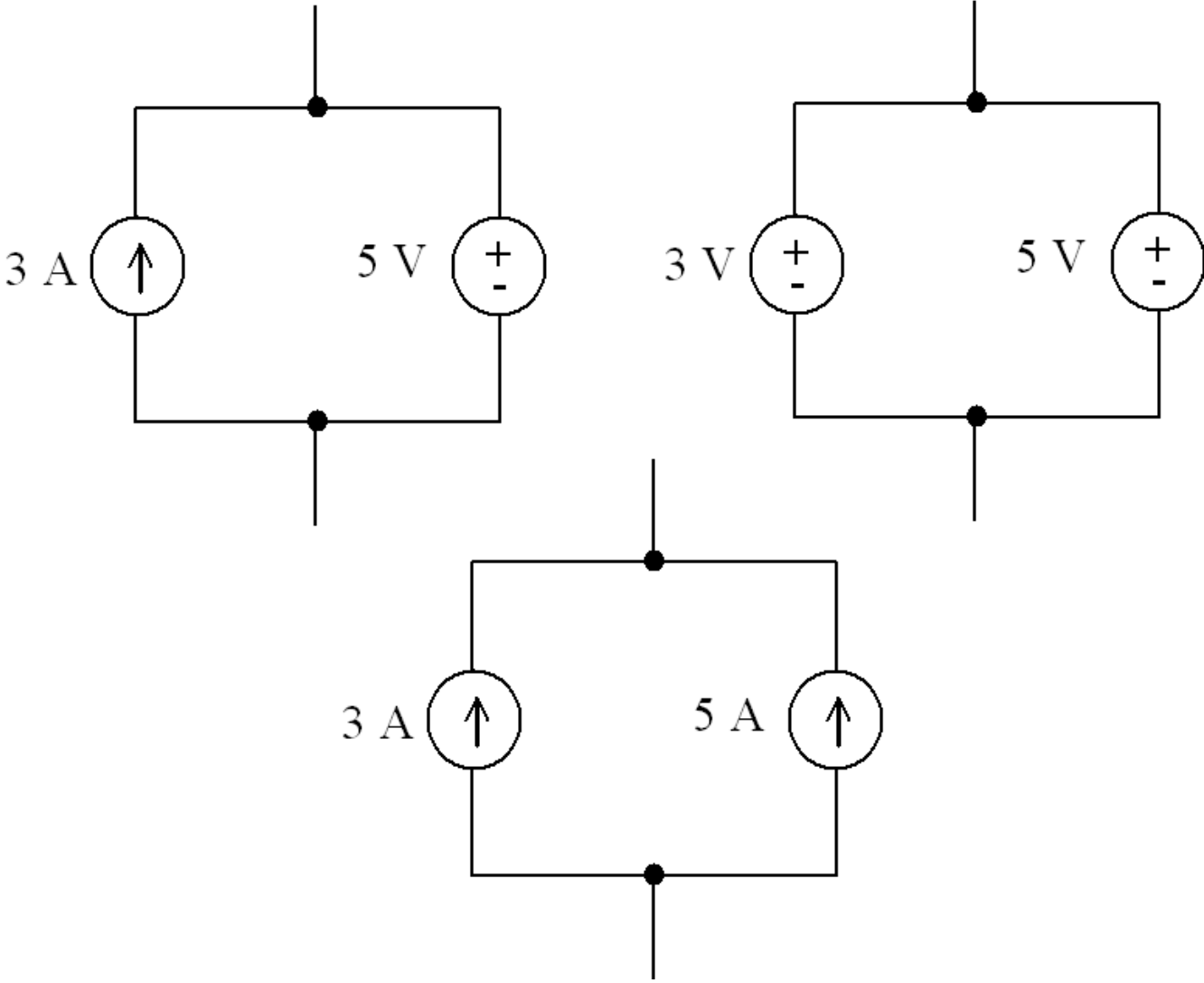


How about resistors and sources?

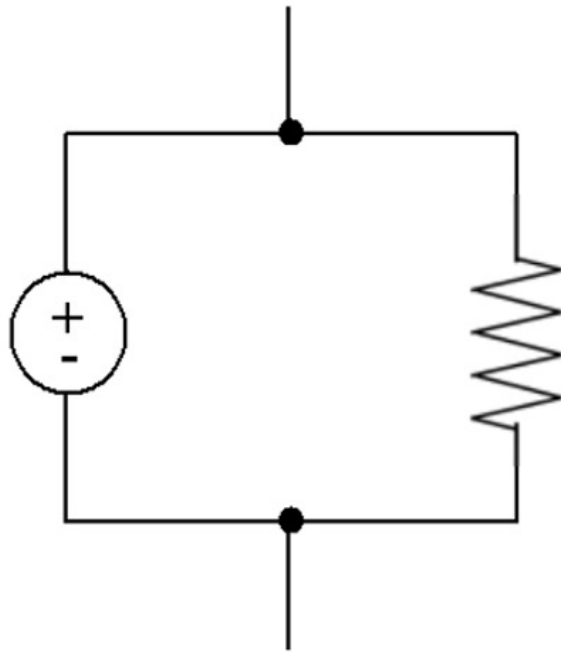


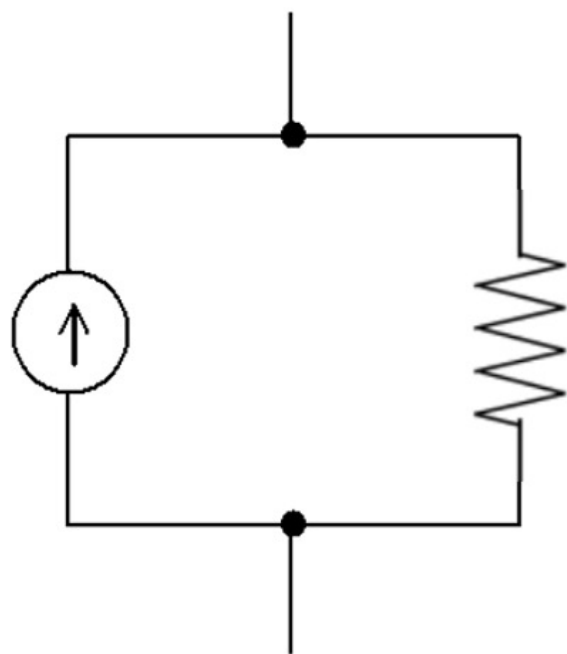

Example: find I

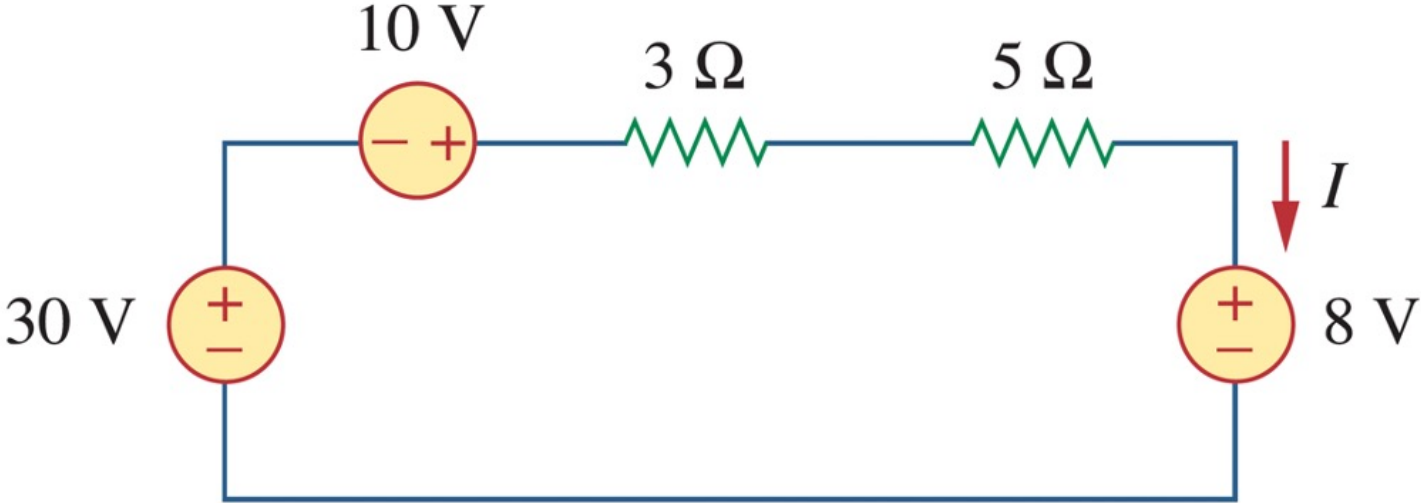

And now?

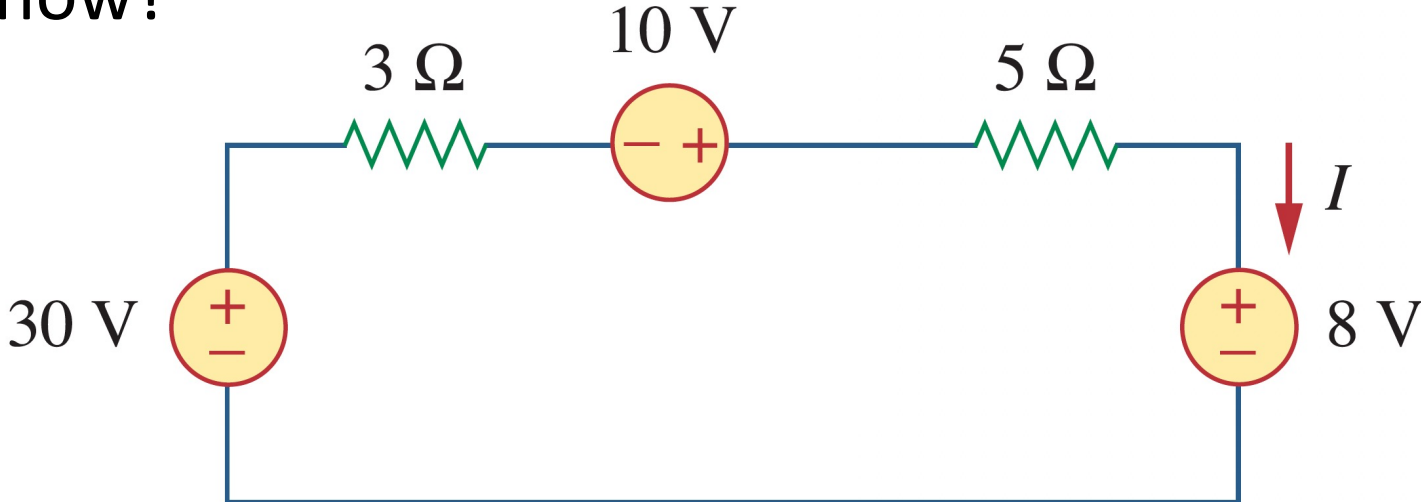

Time Varying Example

- What happens now?

