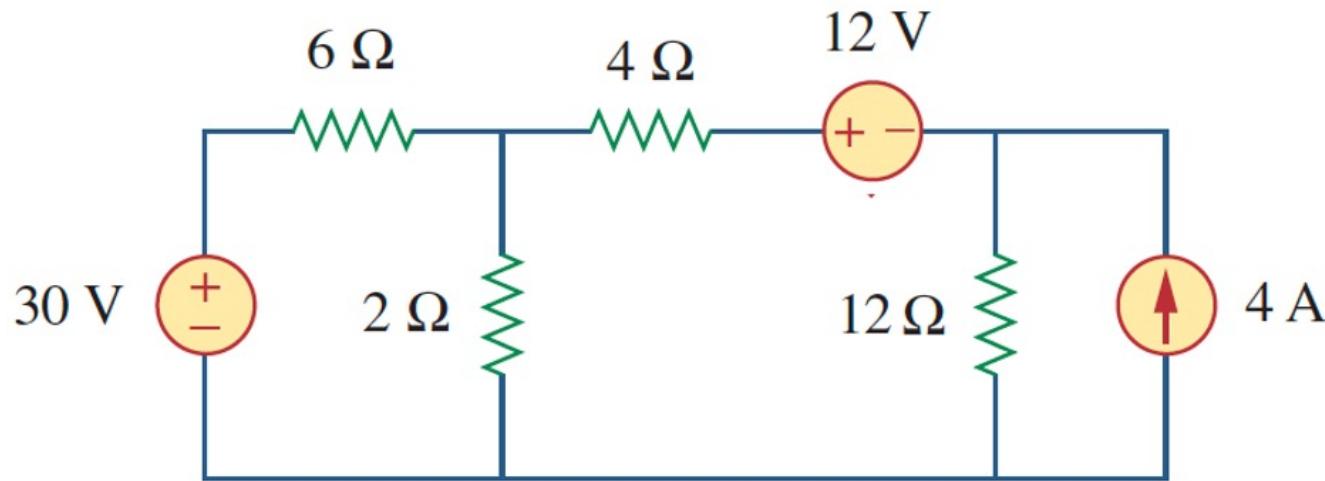


Node – 2

more complex branches


Extension #2 – V + R branches


- Consider:



- Solution: Modify the Ohm's Law expression(s) for the individual branch current(s)

Example (solved on next slide)

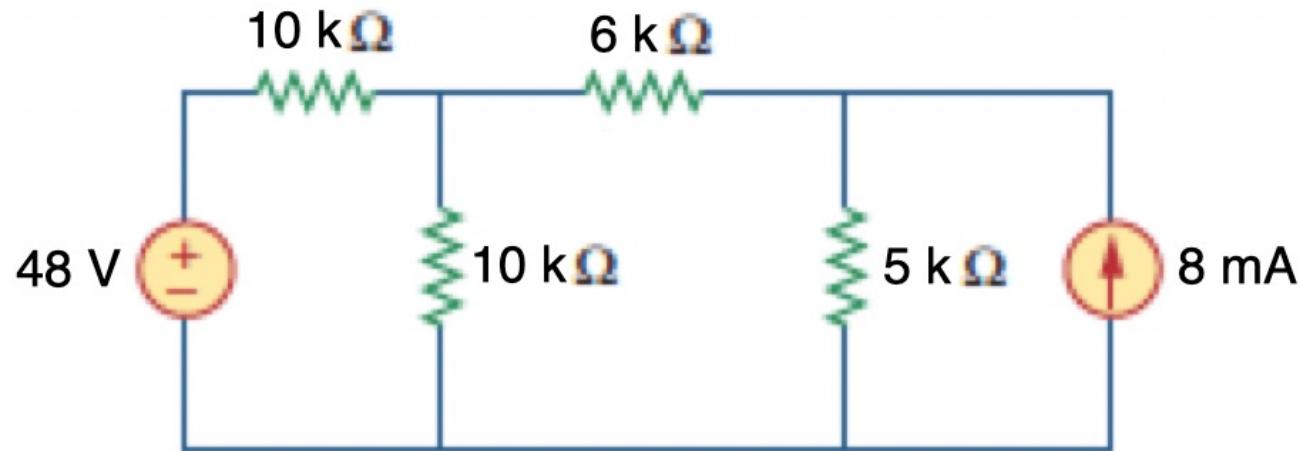

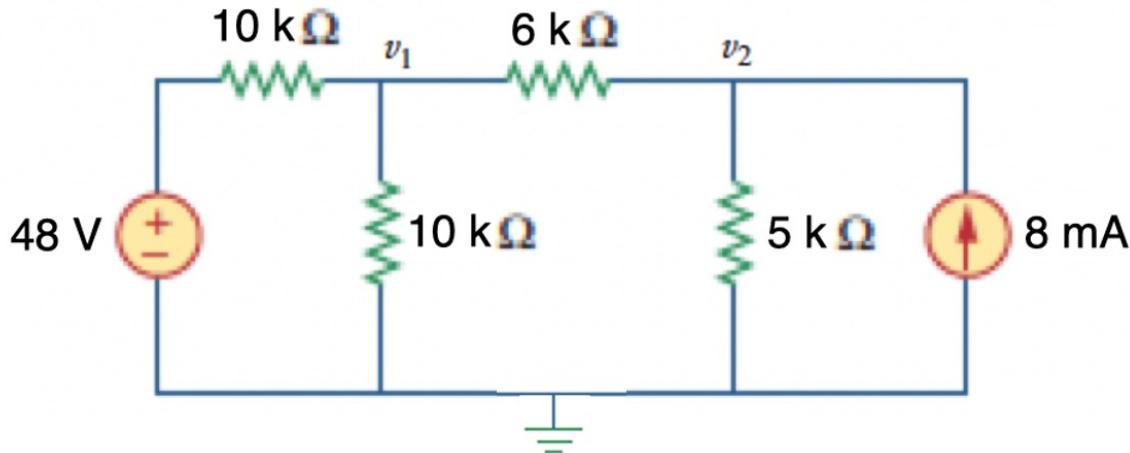

$$\frac{v_1}{10k} + \frac{v_1 - 48}{10k} + \frac{v_1 - v_2}{6k} = 0$$


$$\frac{v_2}{5k} + \frac{v_2 - v_1}{6k} - .008 = 0$$


$$3v_1 + 3v_1 + 5v_1 - 5v_2 = 144$$

$$6v_2 + 5v_2 - 5v_1 = 240$$


$$\begin{aligned} 11v_1 - 5v_2 &= 288 \\ -5v_1 + 11v_2 &= 240 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 29 V \\ v_2 &= 35 V \end{aligned}$$


Example

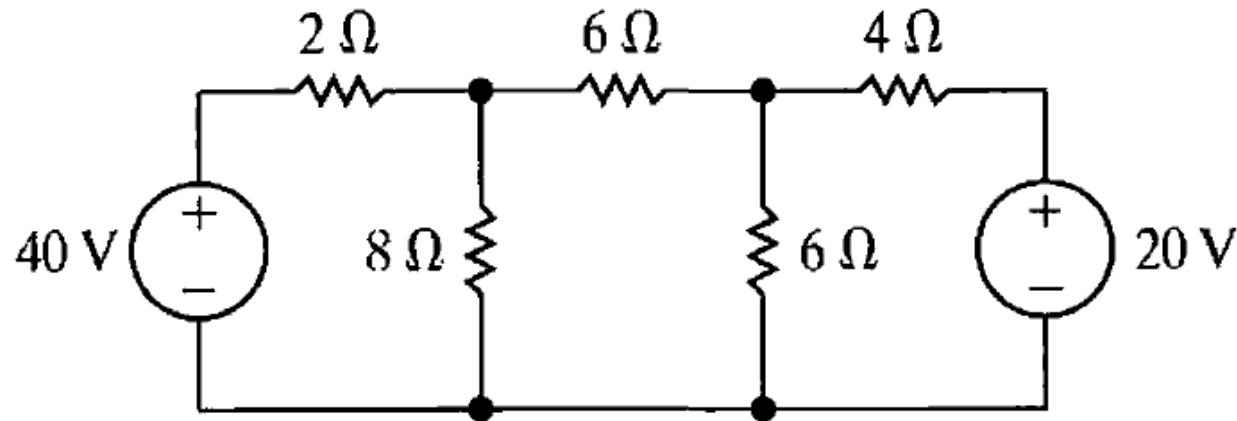

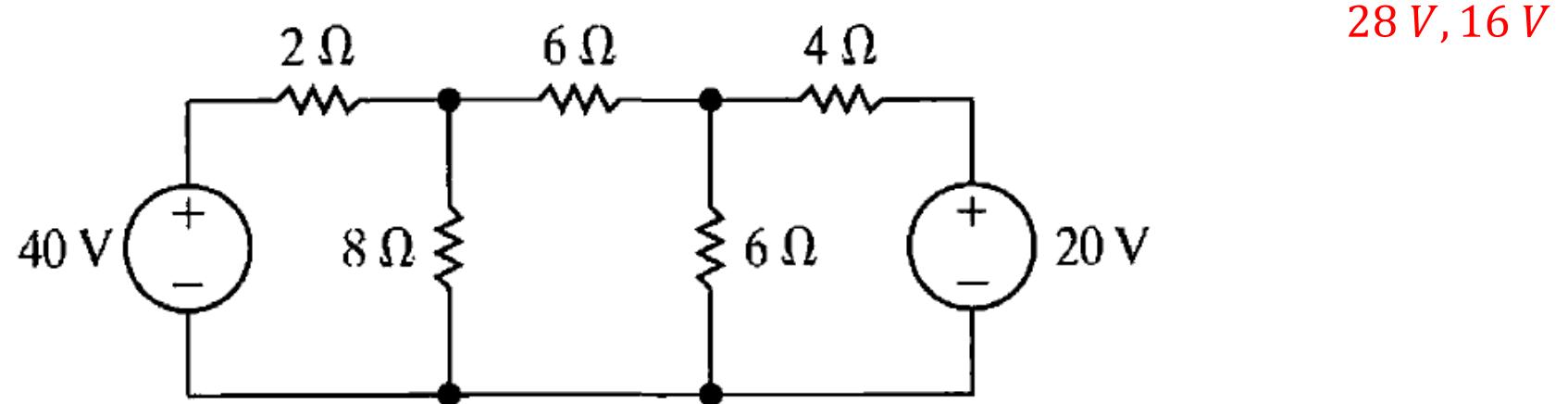

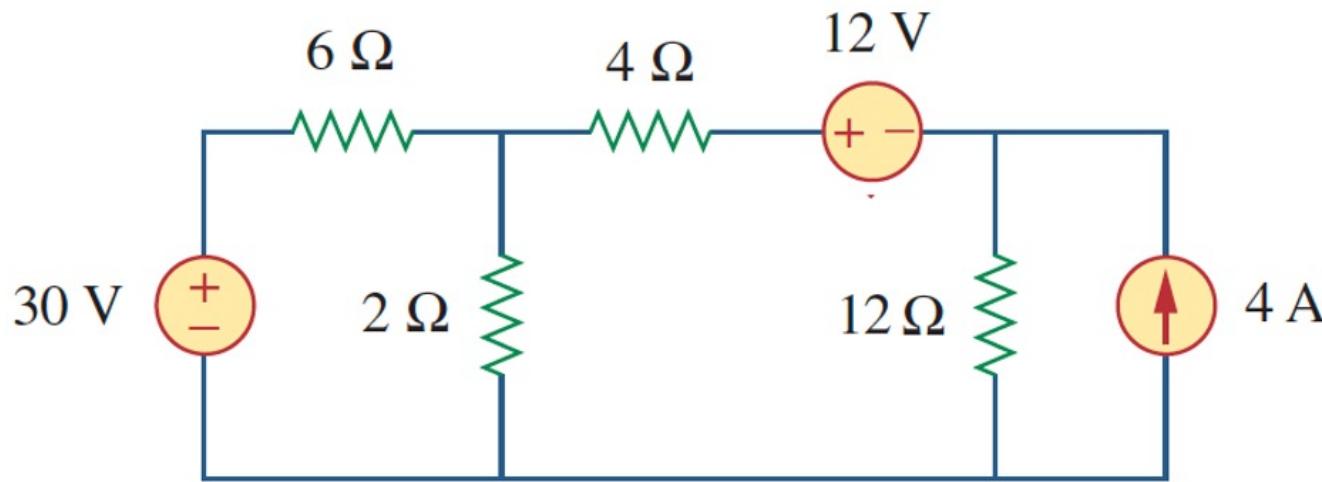
Example: find the power of the current source



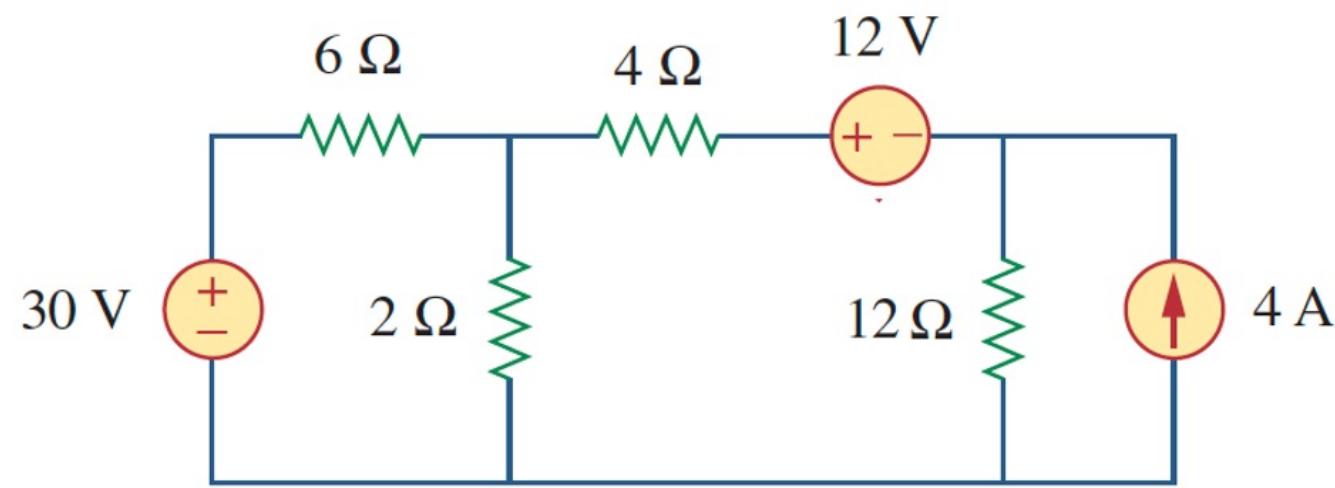


-48 W

Example: find v

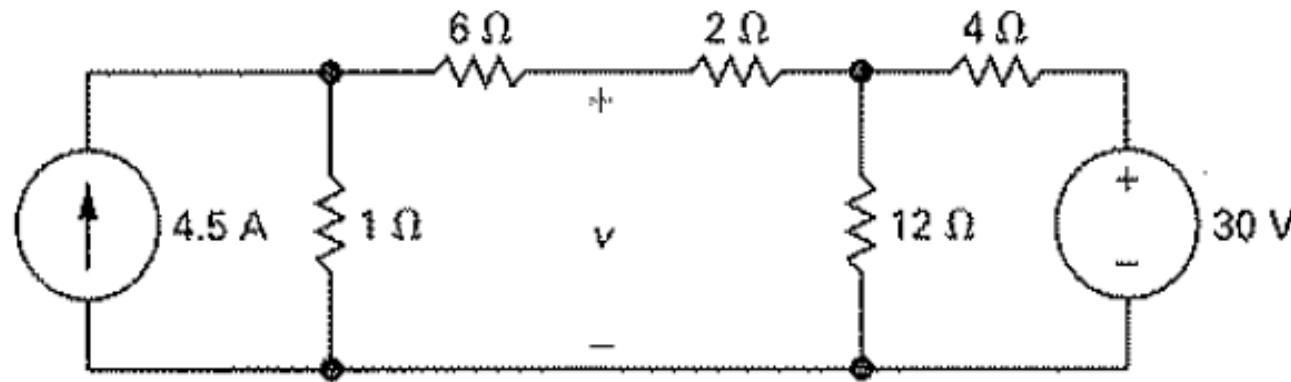


15 V

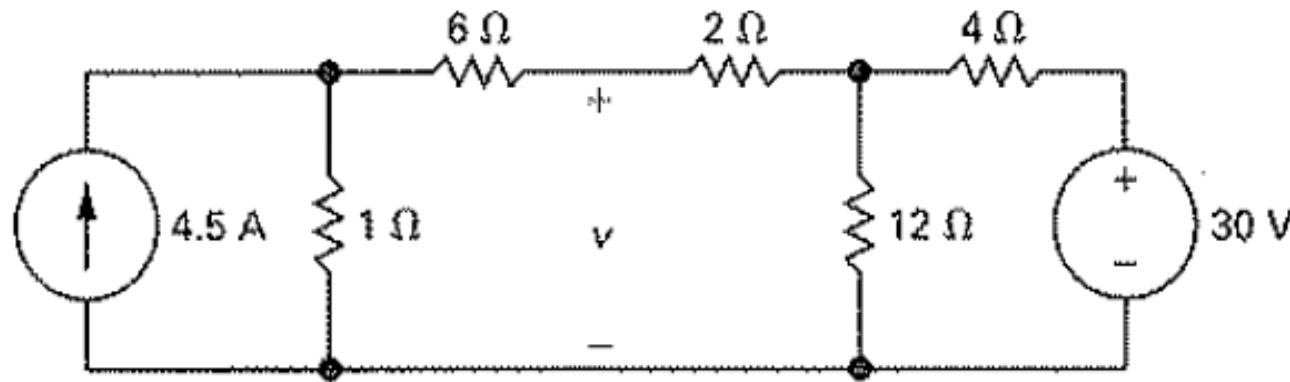


40 V

Practice problem: find V_o

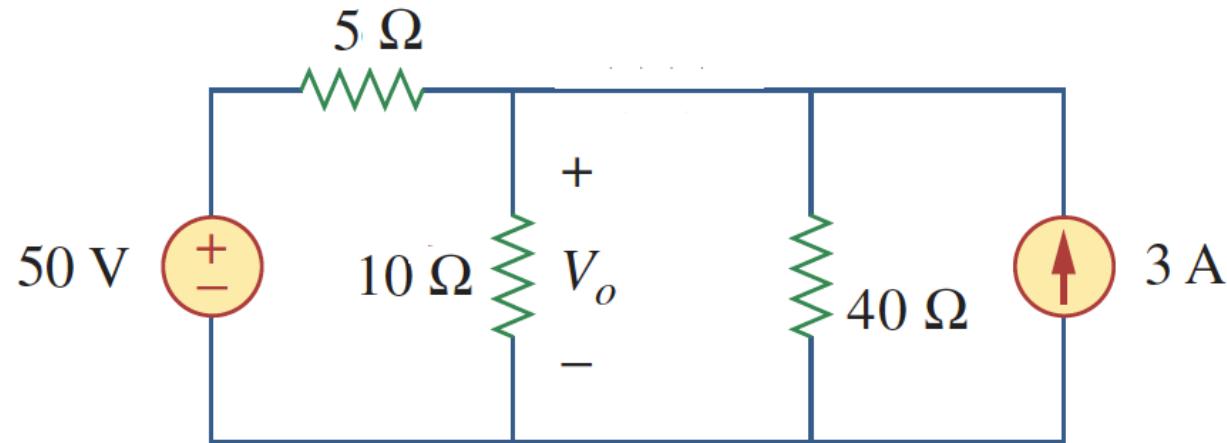

$$v_T = 40 \text{ V}, v_M = 30 \text{ V}$$

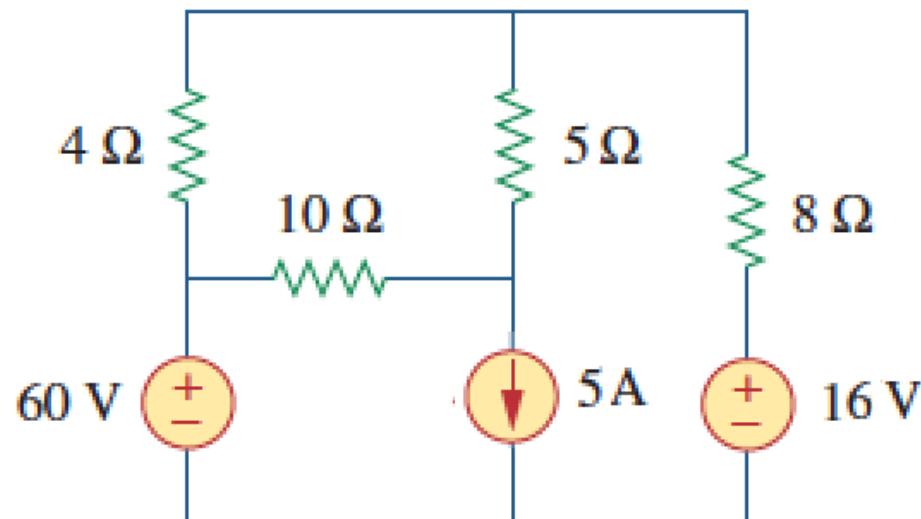Practice problem: find the node voltages to the top and bottom of the 5Ω resistor relative to the bottom



$$-46 \text{ A}$$

Practice problem: find i_o

