


Phasors – 1

introducing L & C

So Far – Resistive DC Circuits


- Circuit variables
 - Voltage, current, and power
- 2-terminal components
 - Passive sign convention
 - Independent and dependent sources
 - Resistors
- Basic tools:
 - KVL, KCL, Ohm's Law
 - Extensions:
 - Series/parallel R
 - Voltage/current division
- Powerful analysis tool
 - Node method

What's Coming

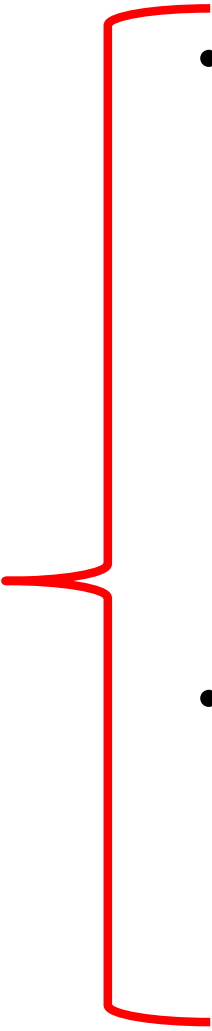
- Two new devices :
 - Inductors (L)
 - Capacitors (C)
 - Time varying voltages and currents
 - Steady-state analysis:
 - Assumes all voltages and currents are sinusoidal
 - Direct extension of methods to date using complex numbers
 - Transient analysis:
 - Voltages and currents that disappear with time
 - Exponential forms
- 



Inductor

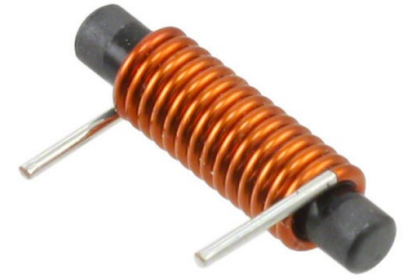

- L (unit is Henries, H)
- V-I rules:

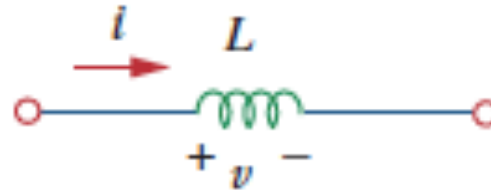

$$v(t) = L \frac{di(t)}{dt} \quad i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0)$$


- Notes:
 - If $i(t)$ jumps then $v(t)$ would be infinite $\rightarrow i(t)$ cannot jump, it is continuous
 - If $i(t) =$ a constant then $v(t) = 0 \rightarrow$ inductor acts like a short circuit



Capacitor




- C (unit is Farads, F)
- V-I rules:

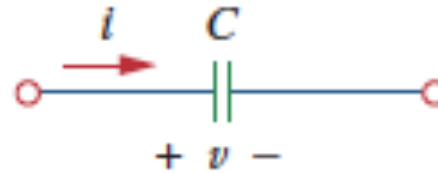

$$i(t) = C \frac{dv(t)}{dt} \quad v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

- Notes:
 - If $v(t)$ jumps then $i(t)$ would be infinite $\rightarrow v(t)$ cannot jump, it is continuous
 - If $v(t)$ a constant then $i(t) = 0 \rightarrow$ inductor acts like an open circuit

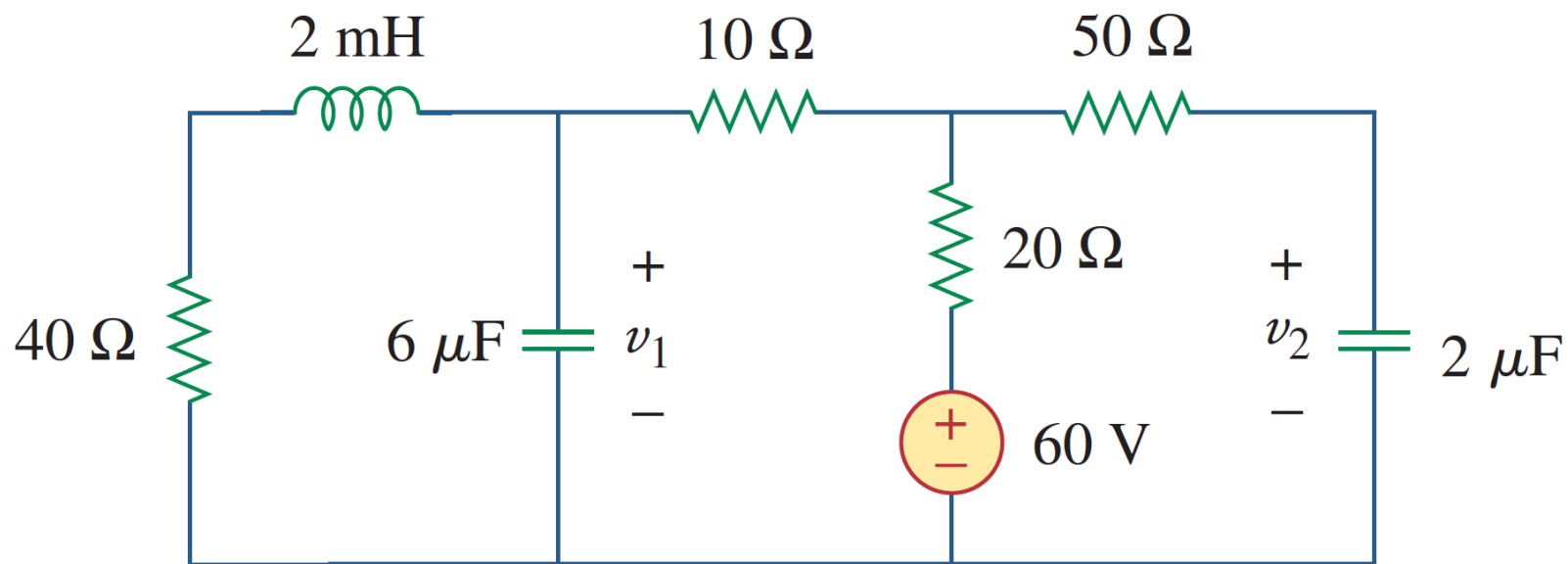Example: Find the voltages v_1 and v_2 for this circuit assuming constant voltage/current conditions.



$$v_1 = \frac{40}{70} 60 = 34.3\ \text{V}, v_2 = \frac{50}{70} 60 = 42.9\ \text{V}$$

Power/Energy for L & C


- Power

$$p(t) = v(t) i(t)$$

- Example:

$10 \mu F$ capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

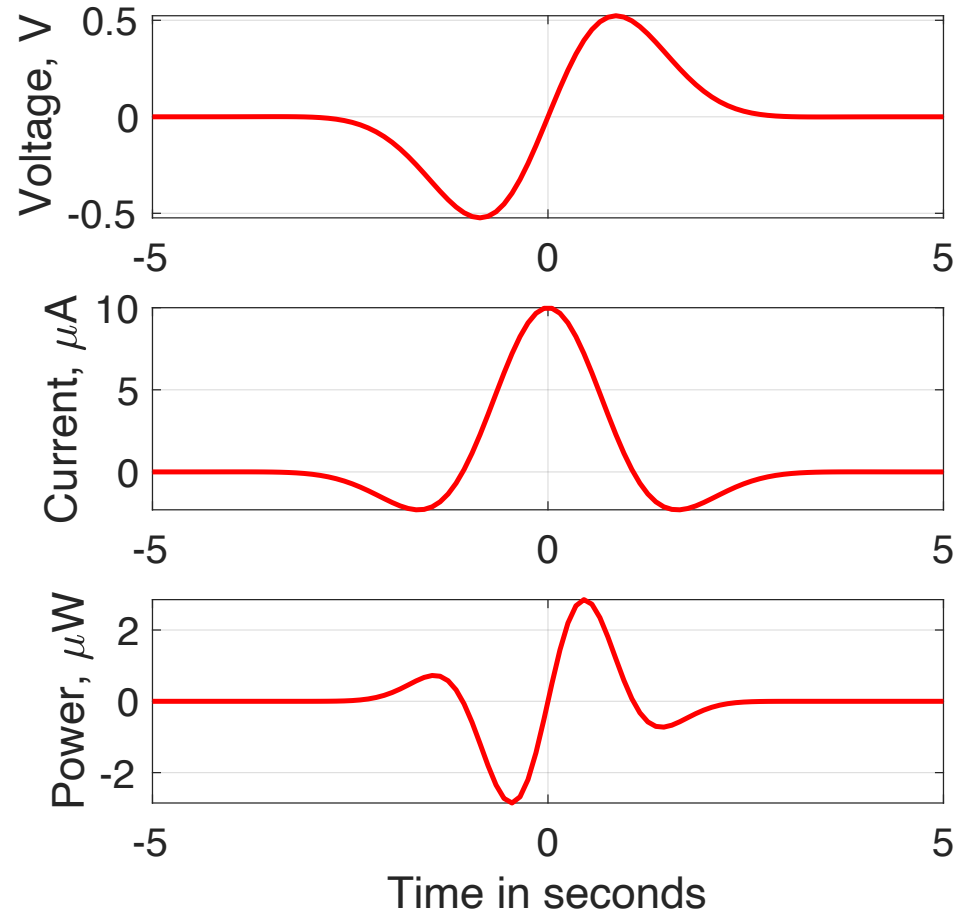

- Energy

$$w(t) = \int p(s) ds = \int v(s) i(s) ds$$

– Inductor:

$$w(t) = \int L \frac{di(s)}{ds} i(s) ds = L \int i(s) di(s) = \frac{L i^2(t)}{2}$$


– Capacitor:

$$w(t) = \int v(s) C \frac{dv(s)}{ds} ds = C \int v(s) dv(s) = \frac{C v^2(t)}{2}$$


Series/Parallel Combining

- Inductors – just like resistors

$$L_{series} = L_1 + L_2$$

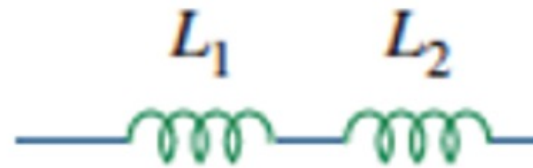
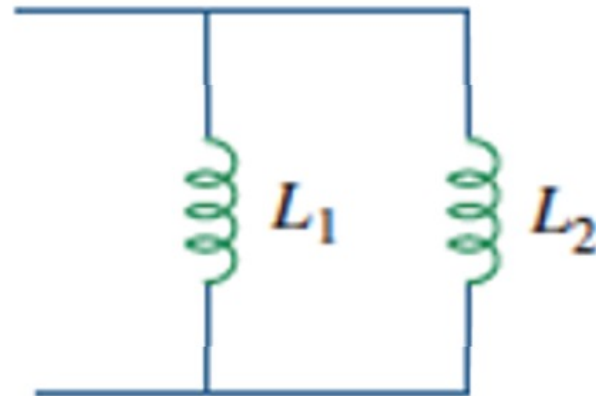
$$L_{parallel} = \frac{L_1 L_2}{L_1 + L_2}$$




- Capacitors – just the opposite of resistors


$$C_{series} = \frac{C_1 C_2}{C_1 + C_2}$$




$$C_{parallel} = C_1 + C_2$$

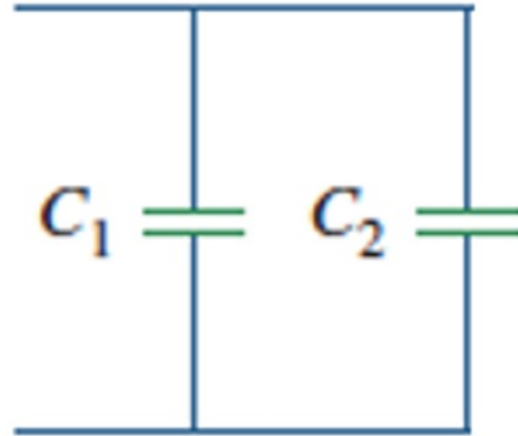

Example: find the equivalent inductance

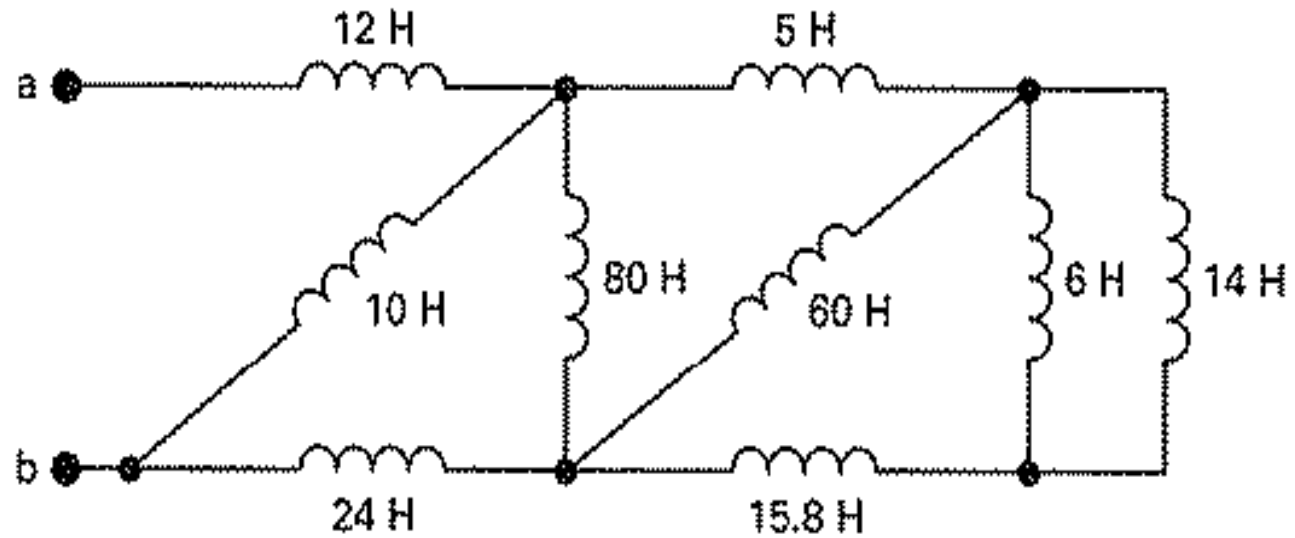


Example: find the equivalent capacitance

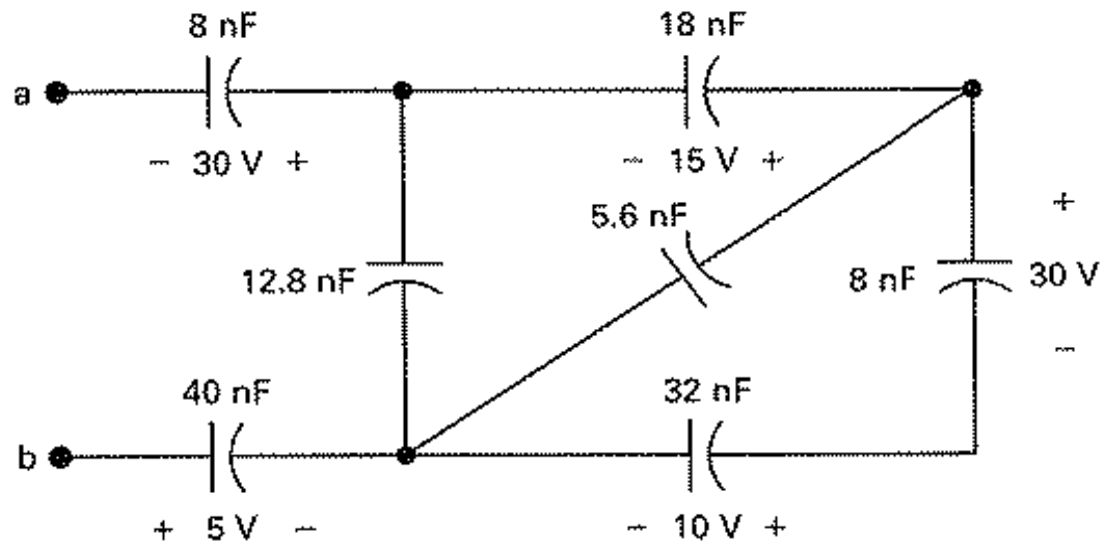

More Realistic Device Models

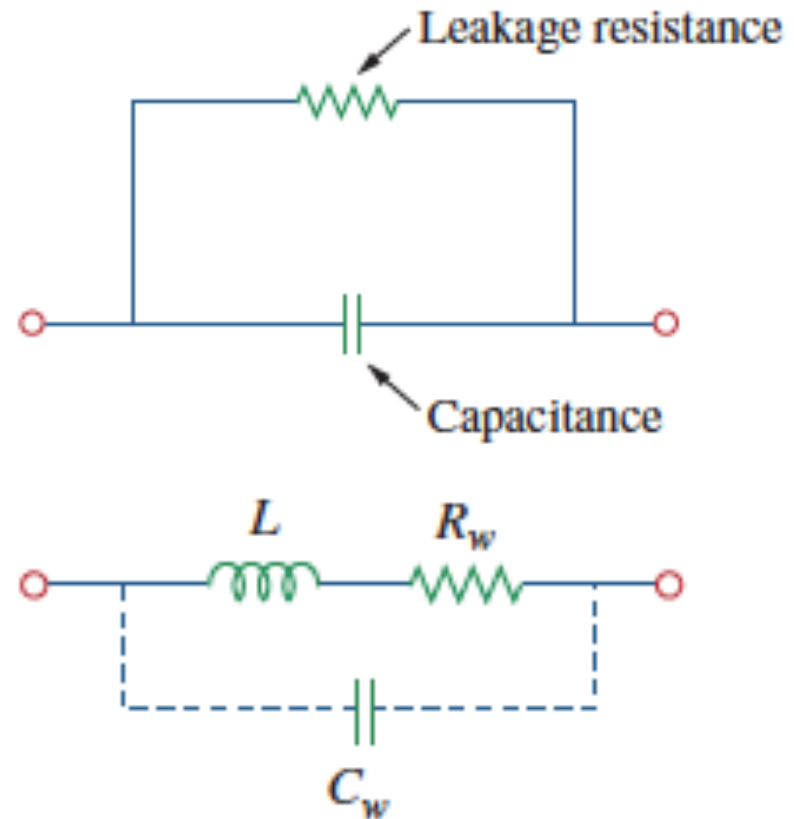- C:
 - Leakage resistance (large)
- L:
 - Winding resistance (small)
 - Winding capacitance (small)
- Will consider more in ELE 215



Practice problem: If a $10 \mu F$ capacitor's voltage is $v(t) = 5(1 - e^{-10t})$ V consider its power as a function of time. When is the power a maximum? What is that maximum? How much energy has been stored in the capacitor at this point?

0.693 sec, 625 μW , 12.5 μJ

Practice problem: A voltage of $20(1 - e^{-500t})$ volts appears across the parallel combination of a $100 \mu F$ capacitor and a 10 ohm resistor. What is the total power absorbed the the parallel combination as a function of time?

$$40 - 60e^{-500t} + 20e^{-1000t} \text{ W}$$

Practice problem: Find the inductor current and capacitor voltage assuming constant voltage/current conditions.

$\frac{1}{3}$ A, 4 V

