

Phasors – 4

using phasors;
variation with frequency

Phasor Review

- Extend sinusoidal voltages/currents to phasors (complex)

$$V_s \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_s e^{j\phi}$$

$$I_s \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_s e^{j\phi}$$

- Convert components (R,L,C) to impedances

$$Z = \begin{cases} R & \text{resistor} \\ j\omega L & \text{inductor} \\ \frac{1}{j\omega C} = -j \frac{1}{\omega C} & \text{capacitor} \end{cases}$$


- Solve the problem using Ohm's Law, KVL/KCL, ...

- Convert back

$$B \angle \theta \Rightarrow B \cos(\omega t + \theta)$$

Common Usage


- Find the voltage $v(t)$

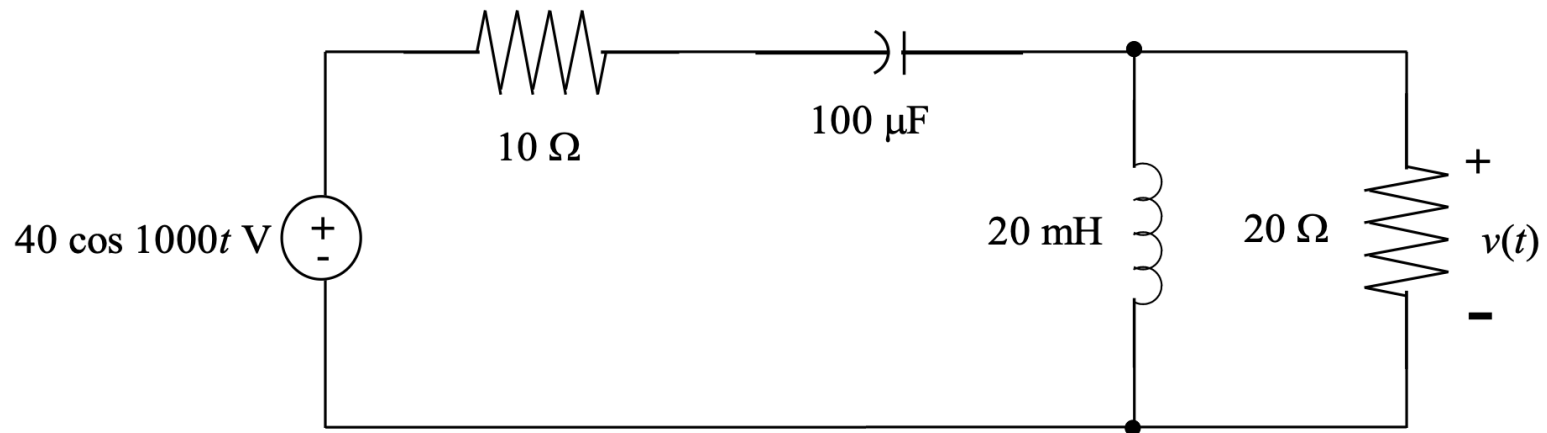

$$28.3 \cos(1000t + 45^\circ) \text{ V}$$

Consider Variation with Frequency

Consider voltage division:

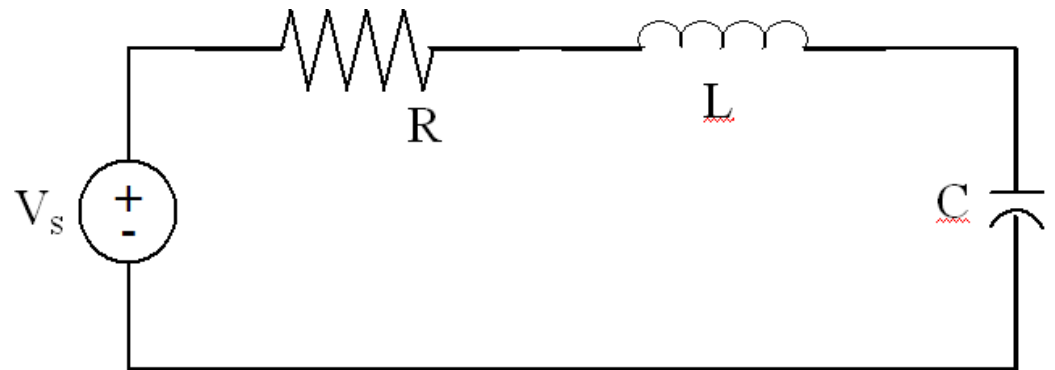





$$V_R = \frac{RV_s}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} V_s$$

Similarly


$$V_L = \frac{-\omega^2 LC}{1 - \omega^2 LC + j\omega RC} V_s$$

$$V_C = \frac{1}{1 - \omega^2 LC + j\omega RC} V_s$$

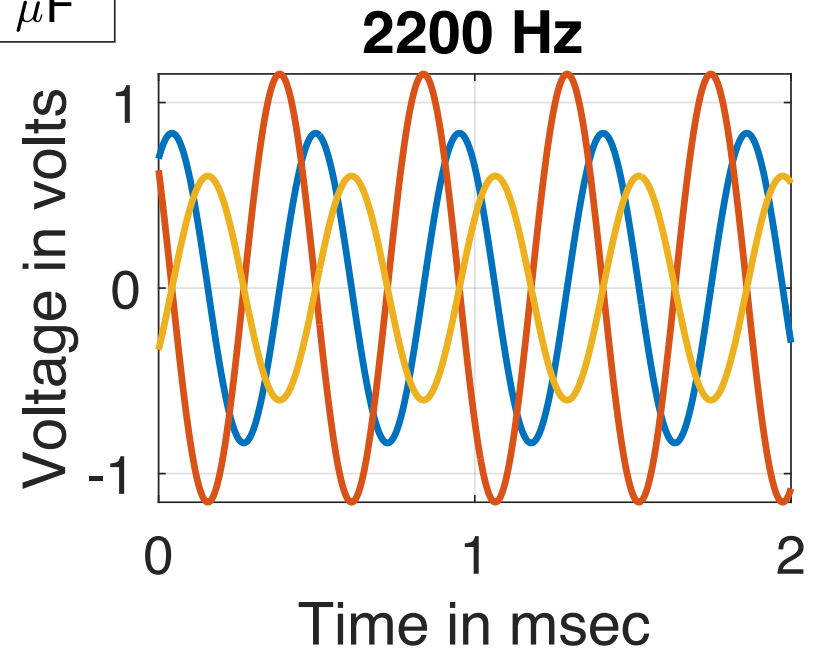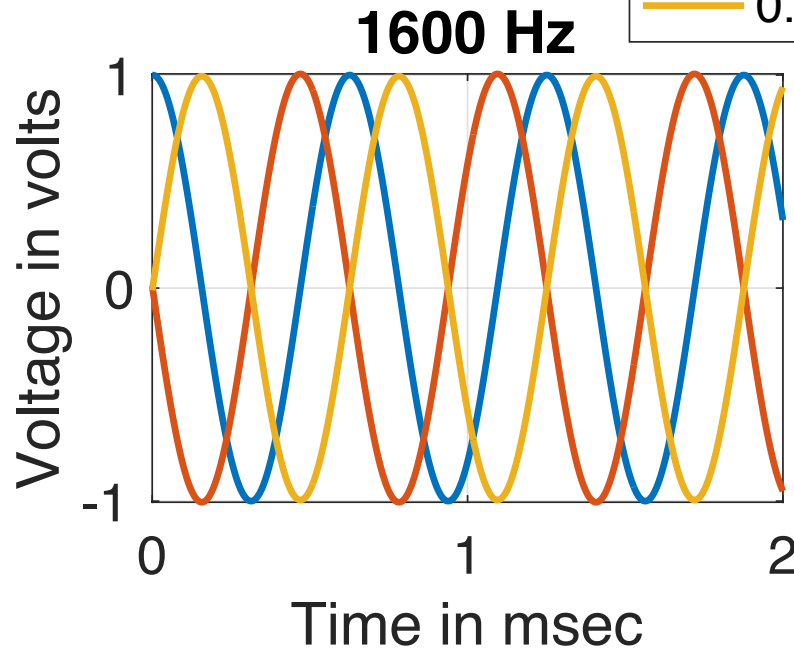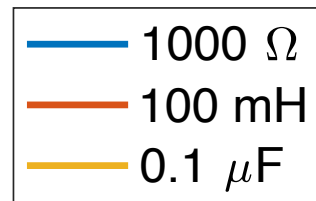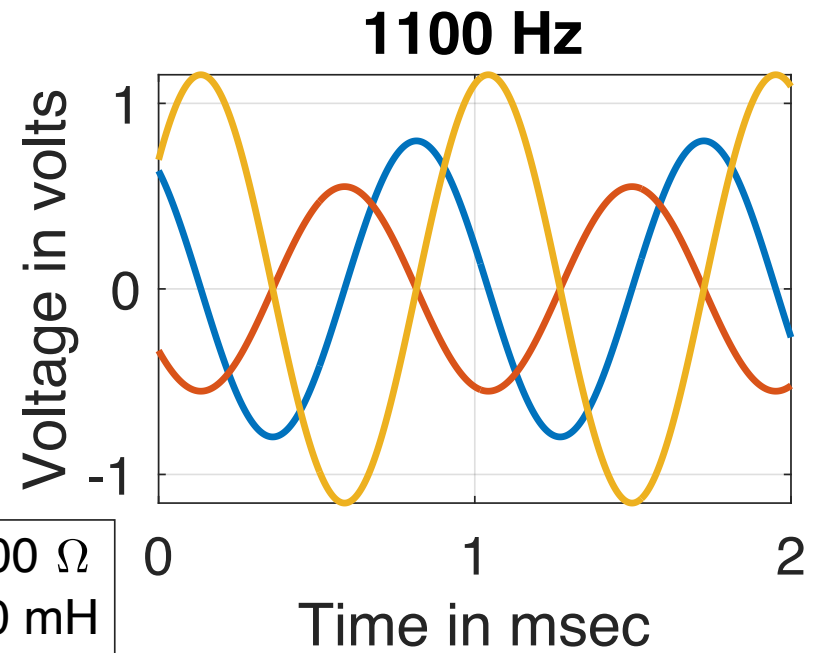- Comparison of the component voltages for different frequencies ($V_s = 1$)



Consider combined impedance variation

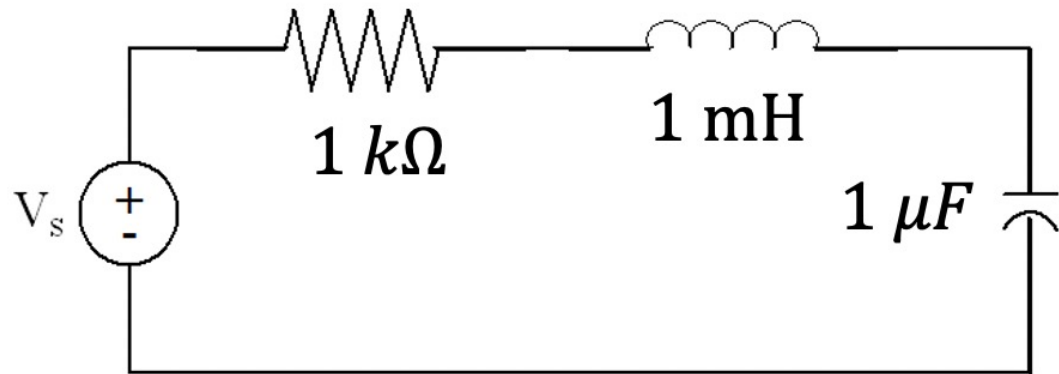


$$\begin{aligned} Z &= R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right) \\ &= 1000 + j\left(\frac{\omega}{100} - \frac{10^6}{\omega}\right) \end{aligned}$$

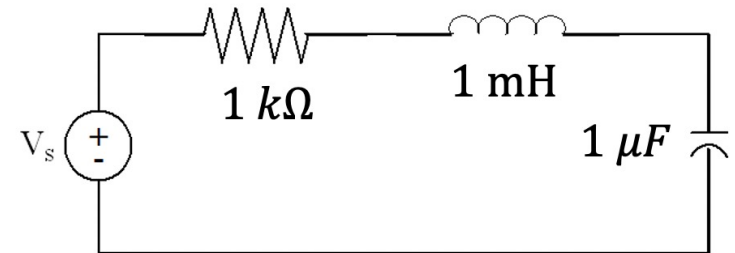Question – at what frequency does this “appear” purely resistive?

How might we graph impedance vs frequency?


$$Z = 1000 + j \left(\frac{\omega}{100} - \frac{10^6}{\omega} \right)$$




- Real/imag vs frequency?
- Real vs imag?

$$80 + j40 \Omega$$


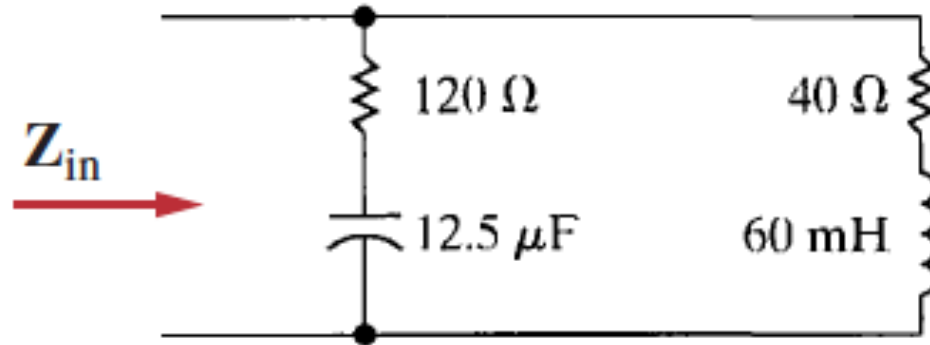
Example: find Z_{in} if $\omega = 2000$ rad/sec



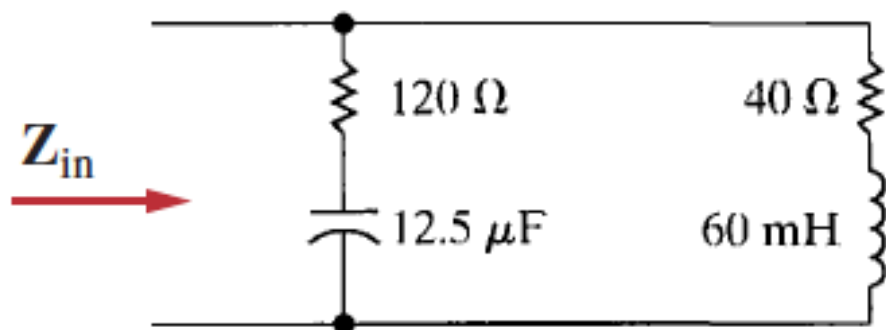
How does Z_{in} vary with frequency? Is it ever purely real?



How do these vary with frequency?

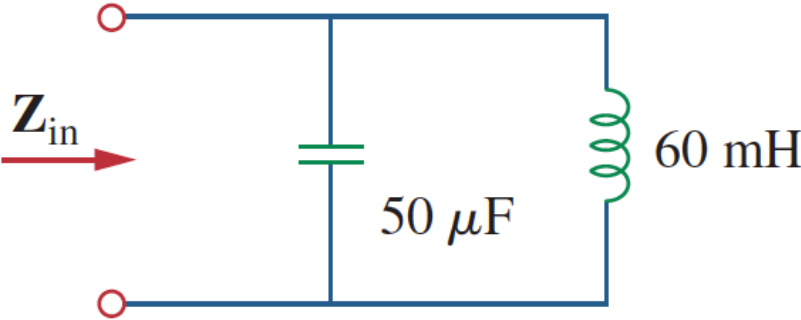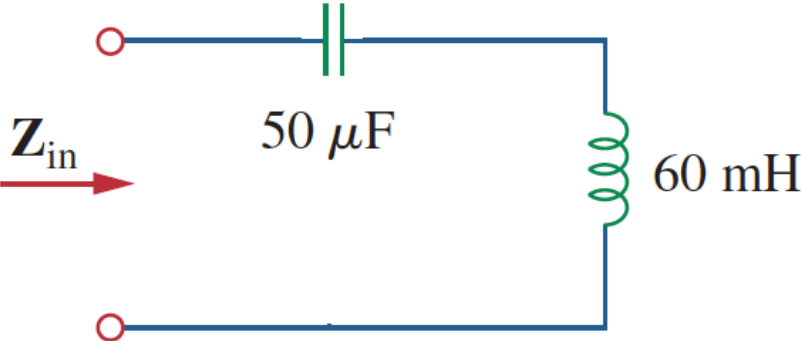


- **Example:** find $i(t)$

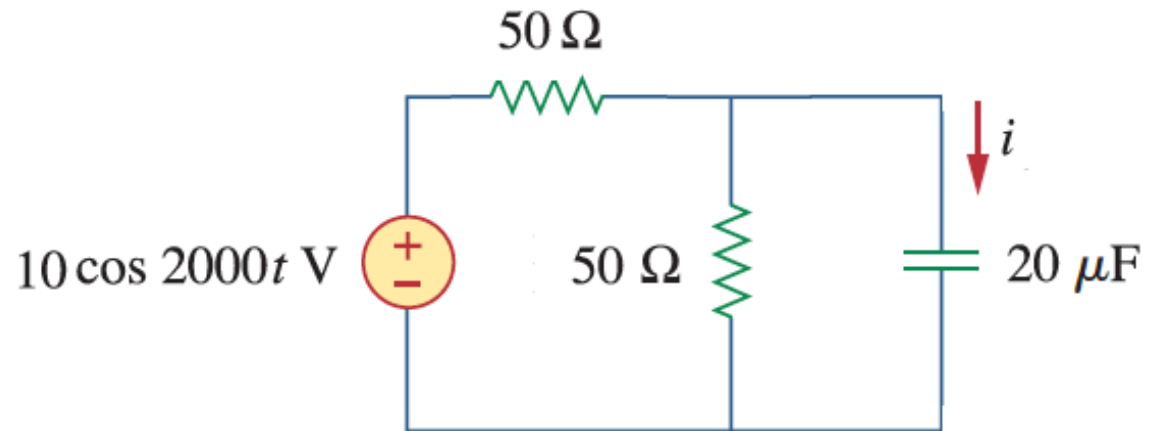

$$141 \cos(2000t + 45^\circ) \text{ mA}$$

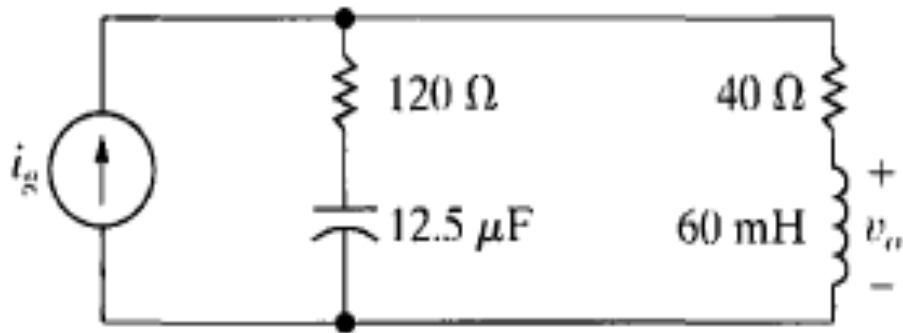
Example: find $v_o(t)$ if $i_g(t) = 500 \cos 2000 t$ mA



$$1.59 \cos(2000t - 17.0^\circ) \text{ V}$$


Example: find Z

$46.4 - j50.4$;
 46.4Ω $0.397 \mu F$

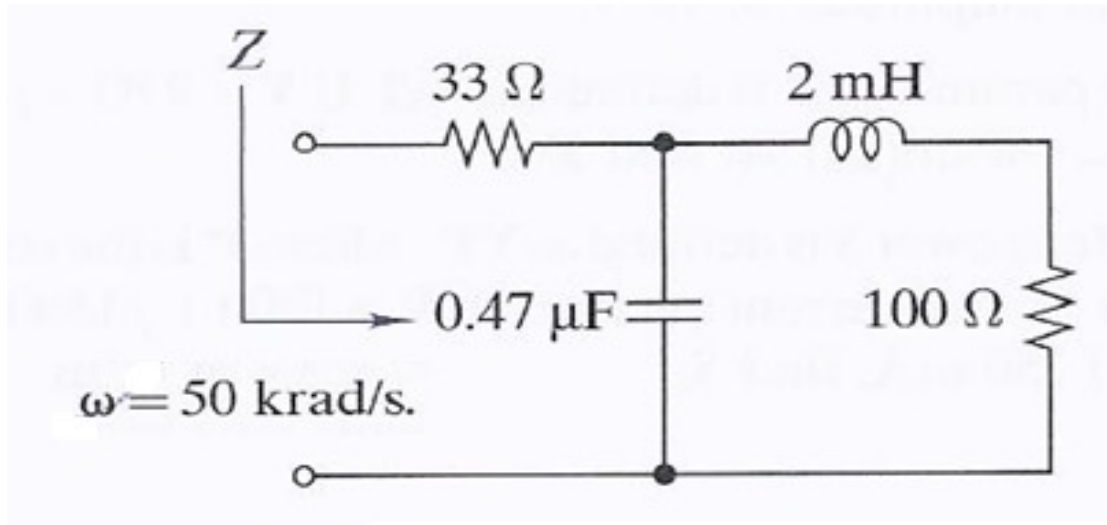


Practice problem: find Z

$11.2 + j35.3$;
 11.2Ω 17.6 mH

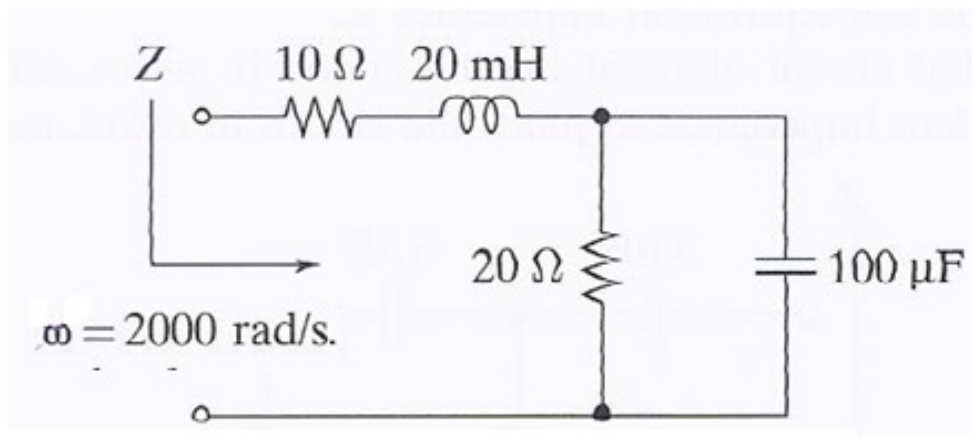

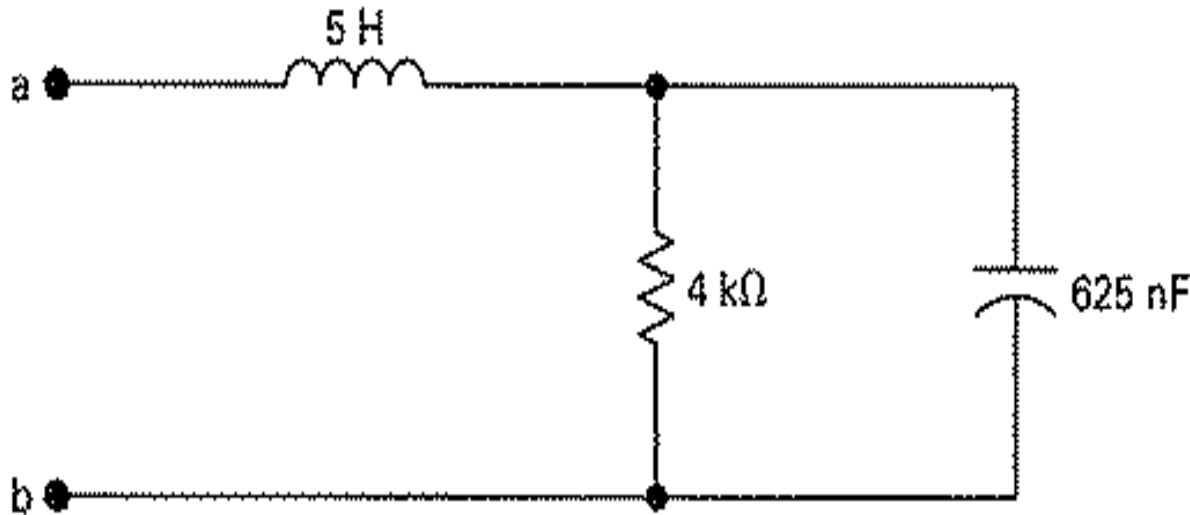Practice problem: at what frequency does this circuit seem purely resistive? What is the resistance?



$$400 \frac{\text{rad}}{\text{sec}}; 2 \text{ k}\Omega$$

- **Practice problem:** consider the parallel connection of a $220\ \Omega$ resistor, a $0.5\ \mu\text{F}$ capacitor, and a $5\ \text{mH}$ inductor.
 - What is the equivalent impedance of this circuit at $1000\ \text{Hz}$?
 - At $5000\ \text{Hz}$?
 - At what frequency is the impedance purely real?

$11.6 + j49.2\ \Omega; 1.42 - j17.6\ \Omega; 1.59\ \text{kHz}$

Practice problem: Find the time expression for $v_o(t)$.

Note that $\sin \omega t = \cos(\omega t - 90^\circ)$

$17.1 \cos 200t \text{ V}$

