


Phasors – 5

examples

What Now?


- Have used seen that voltage division, series and parallel impedance, and simple analysis all work with phasors
- Let's practice analysis methods
 - Node analysis
 - Dependent sources
 - Super nodes
 - ...

Example: Find the current $i(t)$.

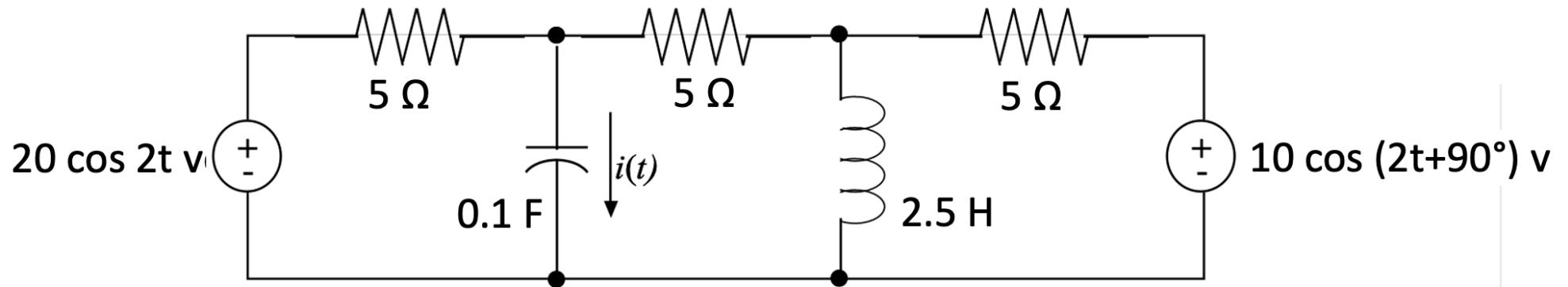


$$1.12 \cos(2t + 153^\circ) A$$

Example: Find V

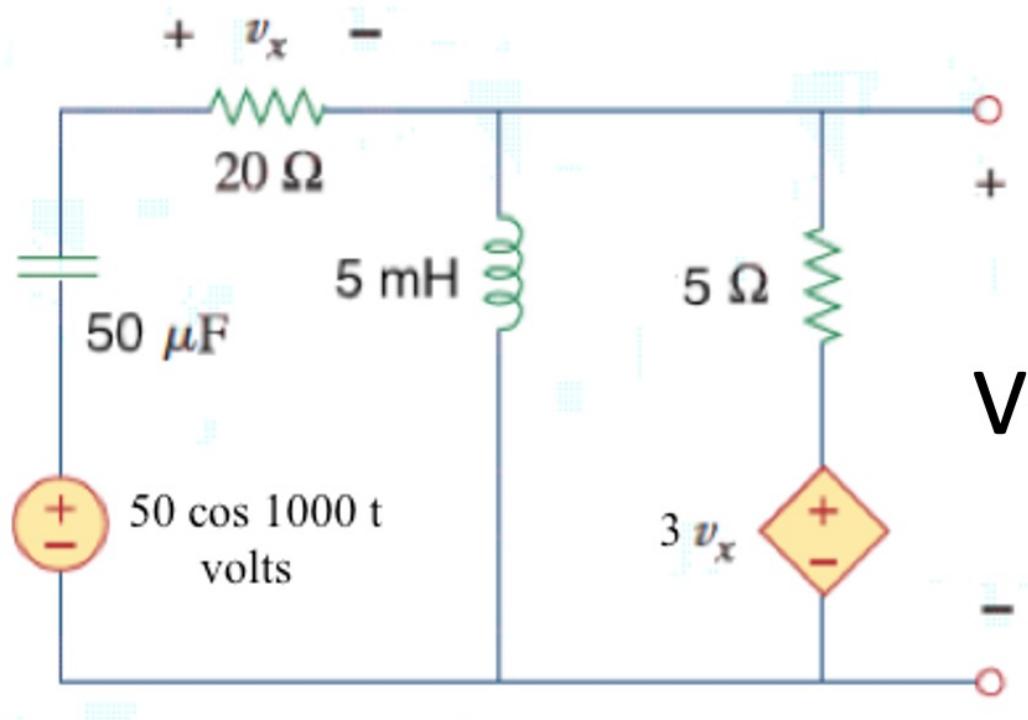


$$42.6 \cos(1000t + 31.6^\circ) \text{ V}$$

Example: Find i_o

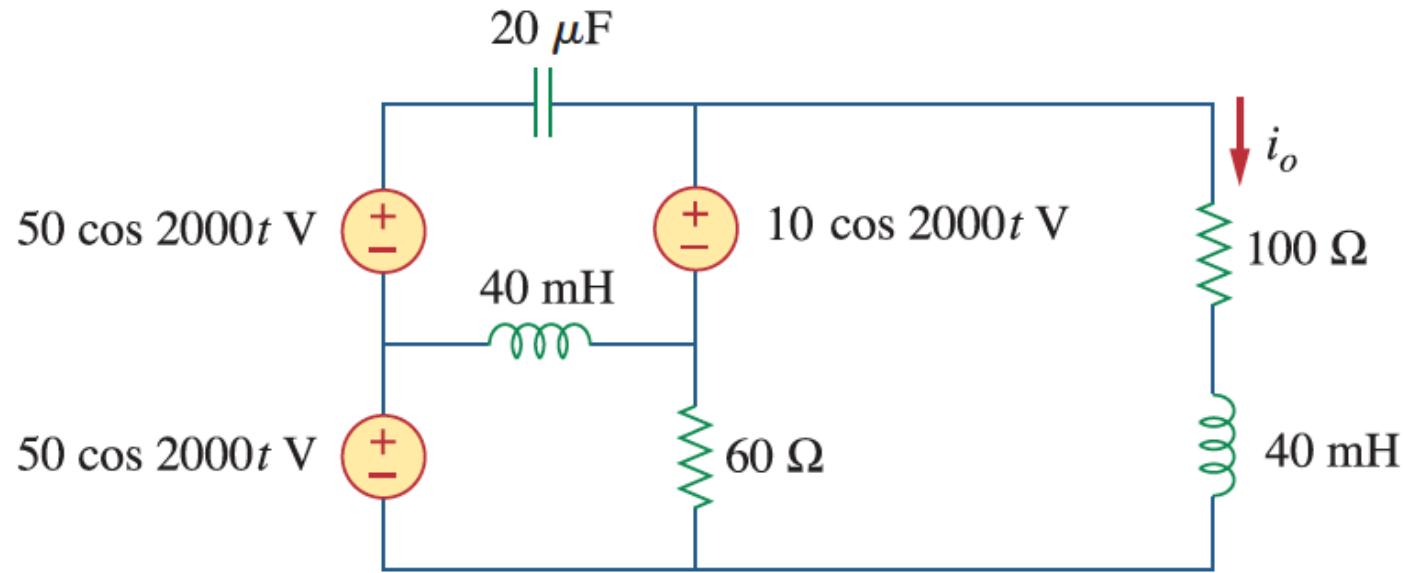


$$822 \cos(2000t + 3.69^\circ) \text{ mA}$$

Example: Find $v(t)$

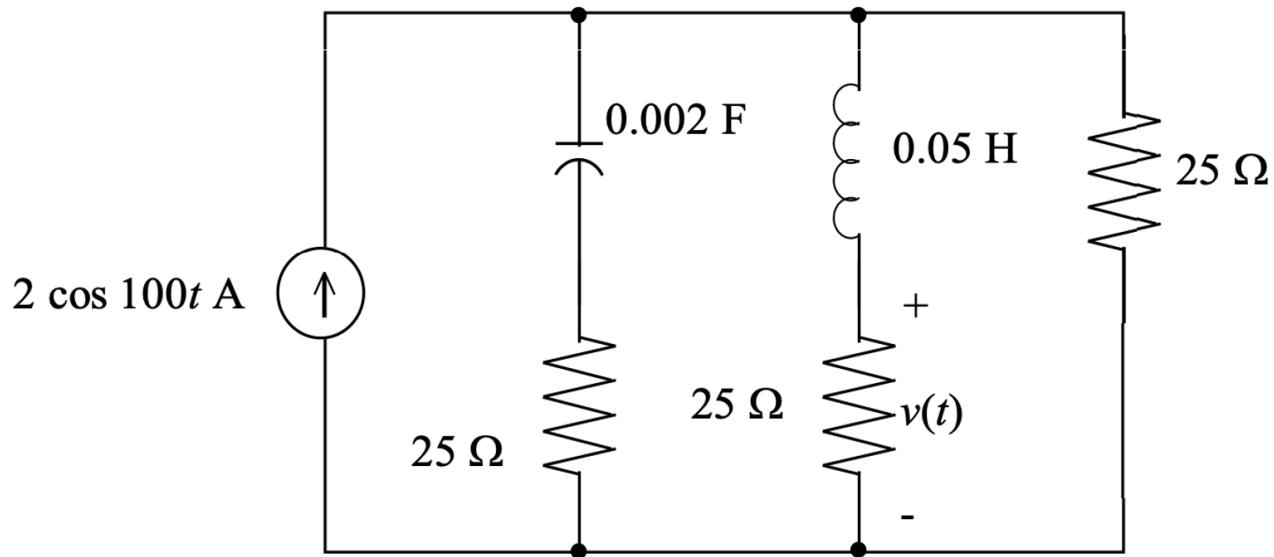


$$16.8 \cos(100t - 11.3^\circ) \text{ V}$$

Example: find $v(t)$ – try node analysis

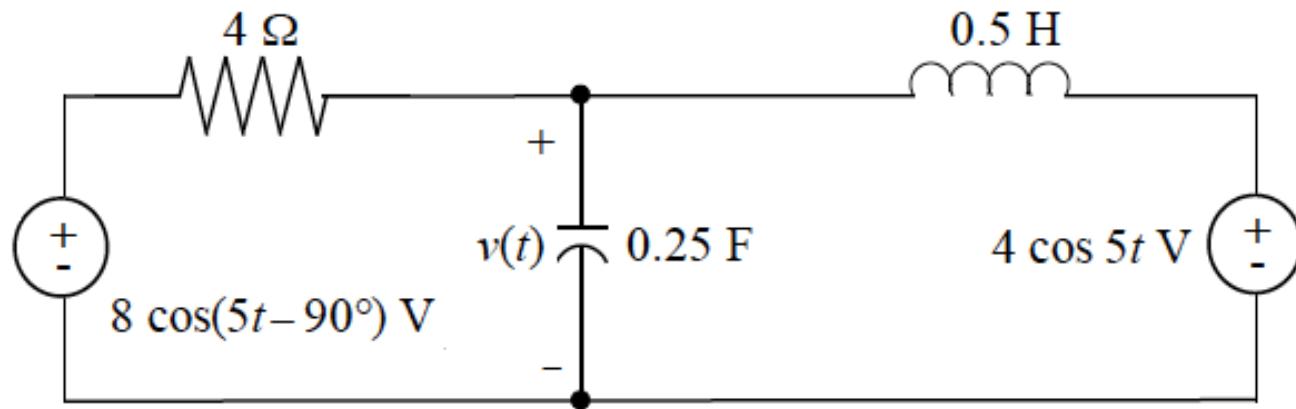


$$4.06 \cos(5t - 164^\circ)~V$$

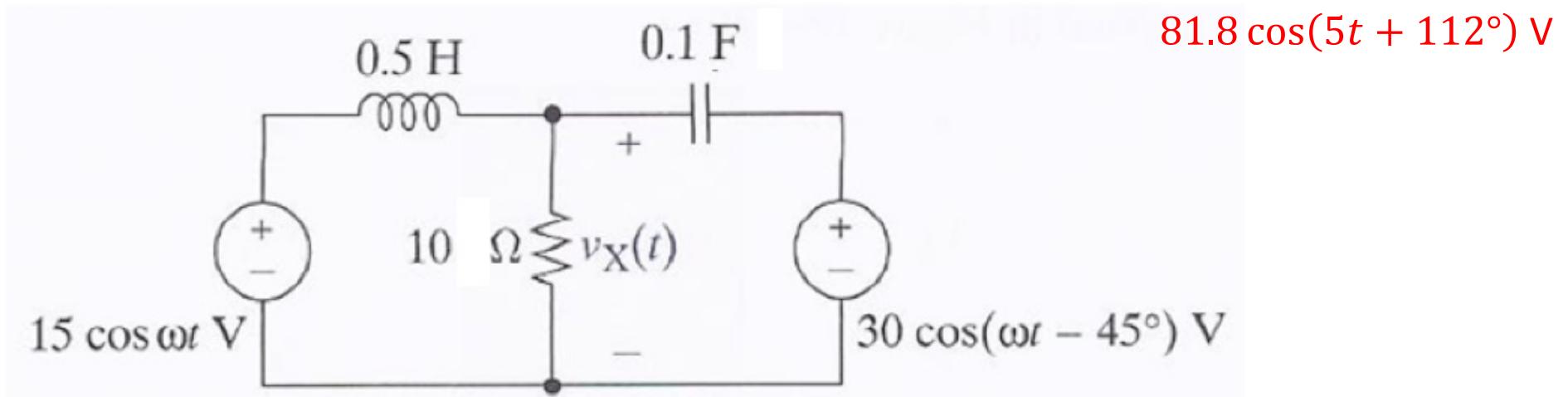Practice problem: find $v(t)$ with $\omega = 5 \text{ rad/sec}$




Practice problem: find $v_X(t)$

$$6.67 \cos(2000t - 90^\circ) V$$

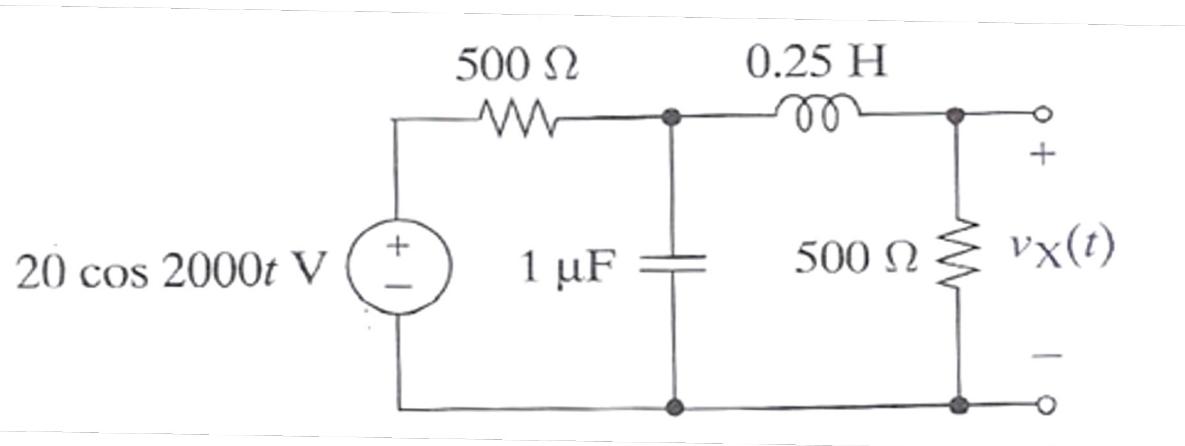


Practice problem: find $v(t)$
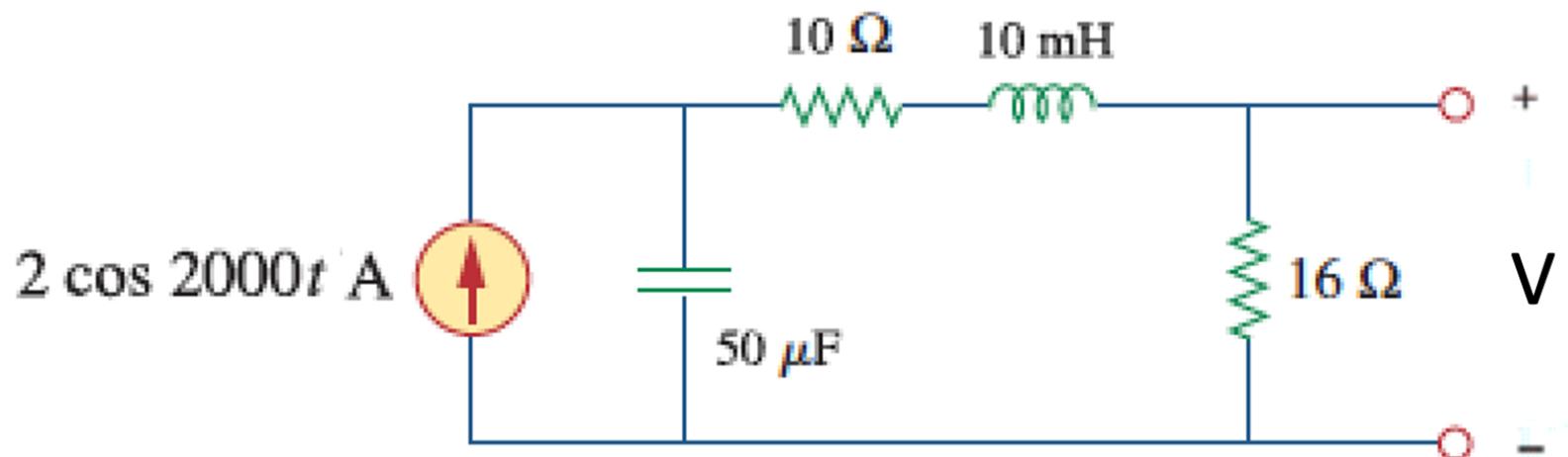
$$13.8 \cos(2000t - 115^\circ) \text{ V}$$



Practice problem: find $v(t)$

$$3.71 \cos(1000t + 21.8^\circ) V$$

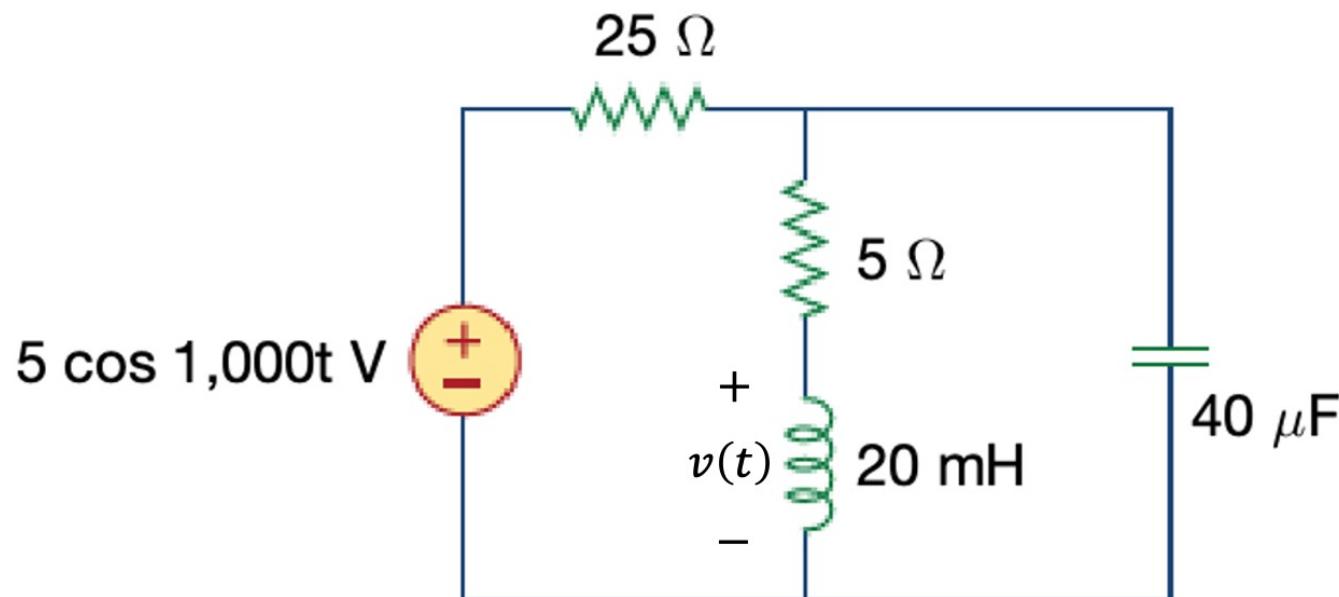

Example: find $v(t)$ if $v_g(t) = 130 \cos 10,000 t$ V,

f

