
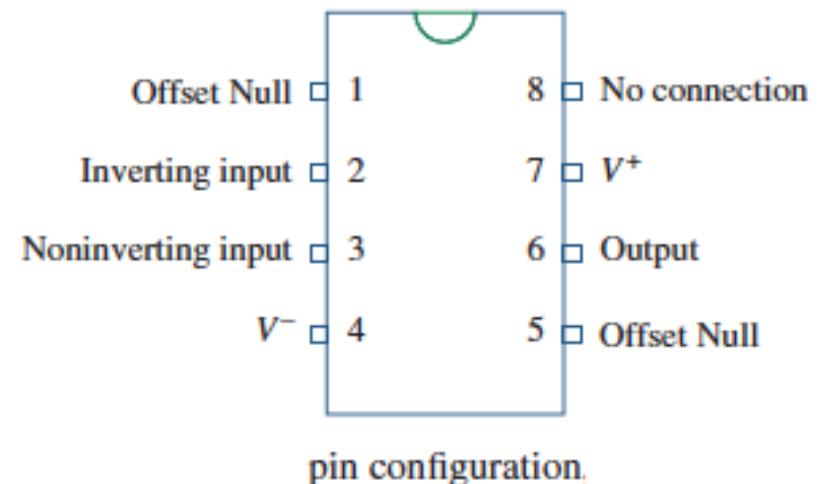


# Op Amps 1


concept, full analysis, simple model
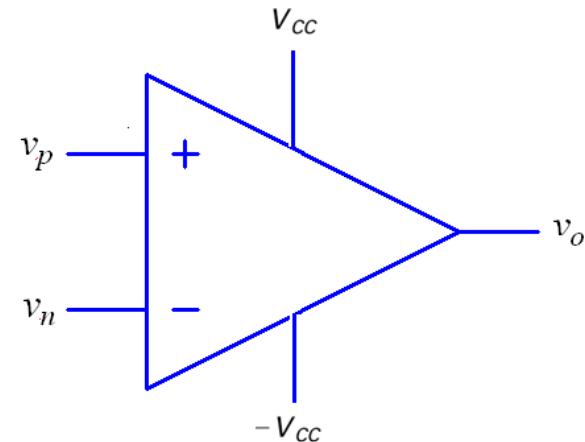
# Op Amps


- A 3-terminal device
  - Inverting input  $v_n$
  - Non-inverting input  $v_p$
  - Output  $v_o$
- Is a powered device, not unlike gates in ELE 201/202
  - Introduced in the 1960's
  - Lots of applications
- Common example is the 741
  - Cost is < \$1



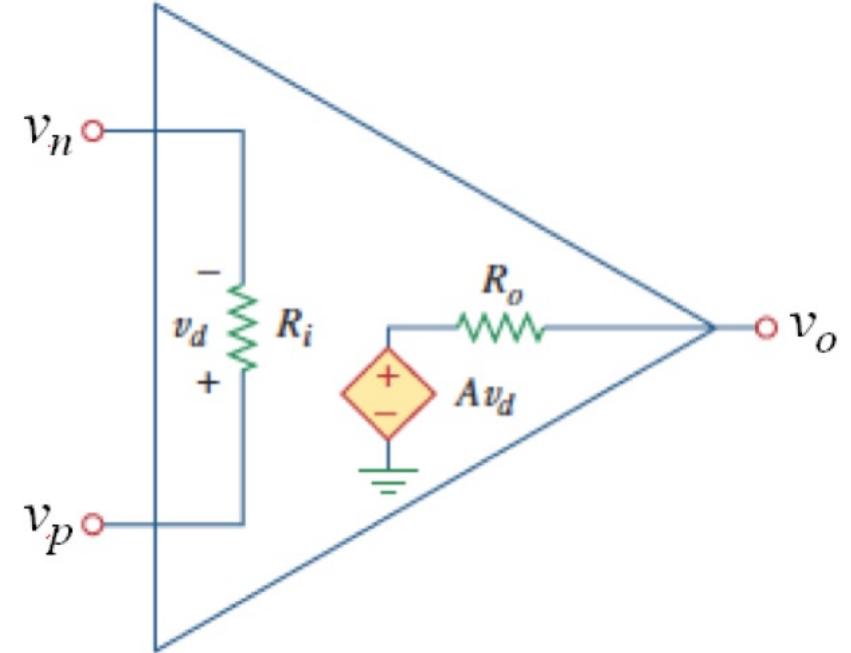
- Nominally behaves like a voltage dependent voltage source
- Simplest circuit model:
  - Dependent voltage source
    - Control voltage is  $v_d = v_p - v_n$
    - “Open loop” gain:  $A$  (is large,  $10^5$  or more)
  - Two resistors
    - “Input resistance”  $R_i$ : large ( $10^5 \Omega$  or more)
    - “Output resistance”  $R_o$ : small ( $100 \Omega$  or less)





- Experiences open loop “saturation”

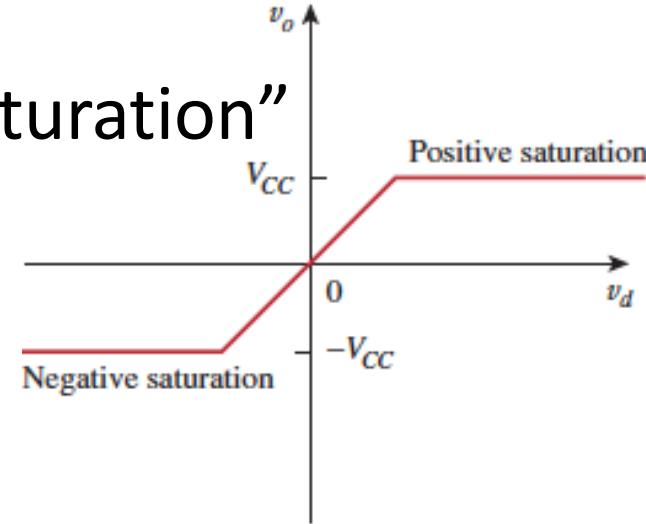

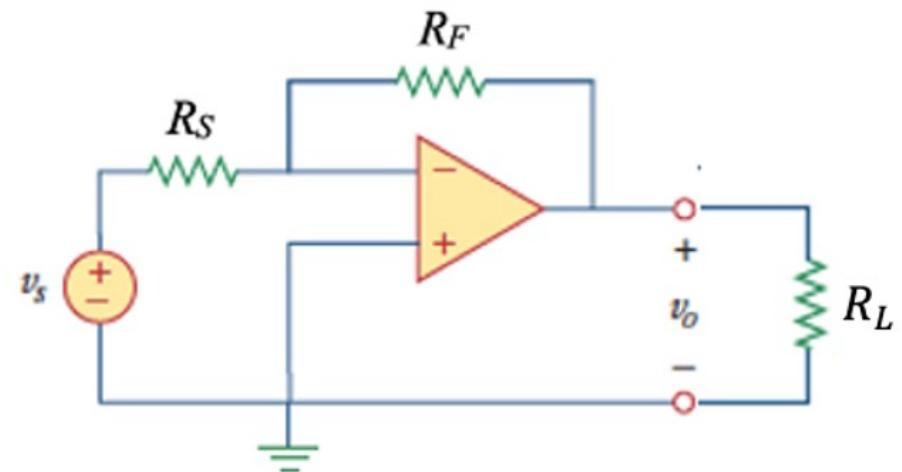
- Usually configured with “negative feedback”



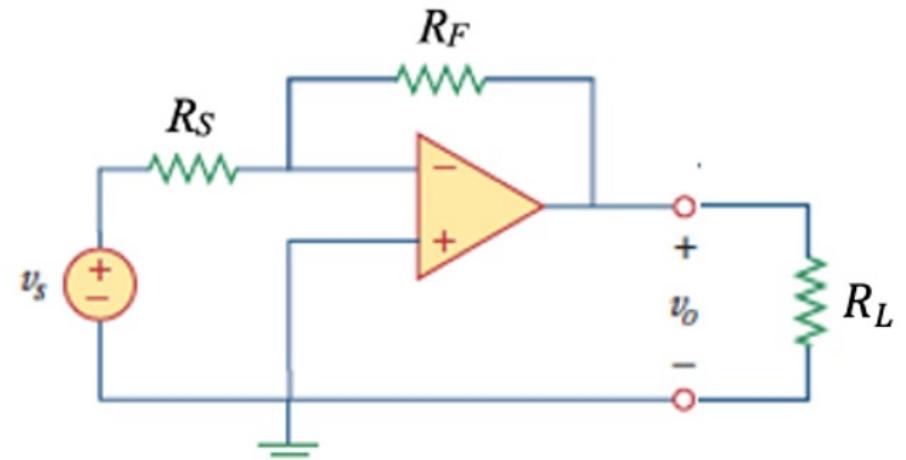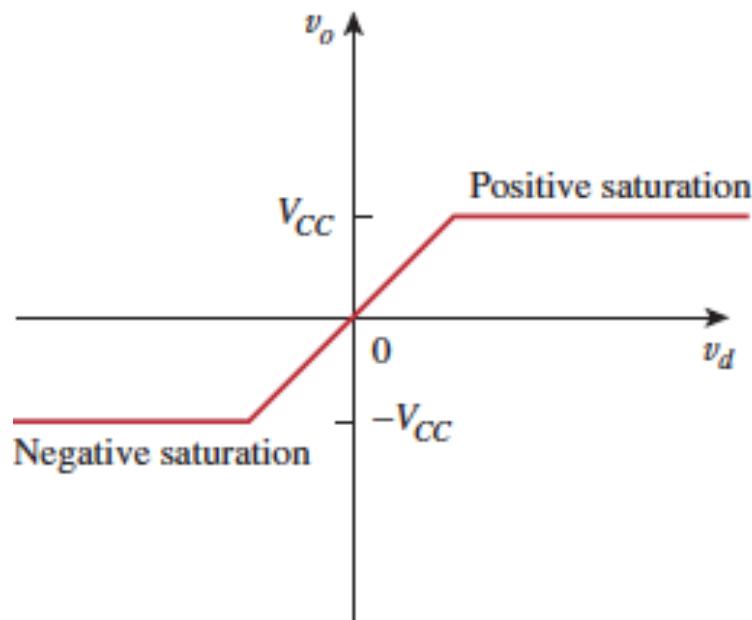
- Experiences open loop “saturation”
- Usually configured with “negative feedback”




# Sample Analysis

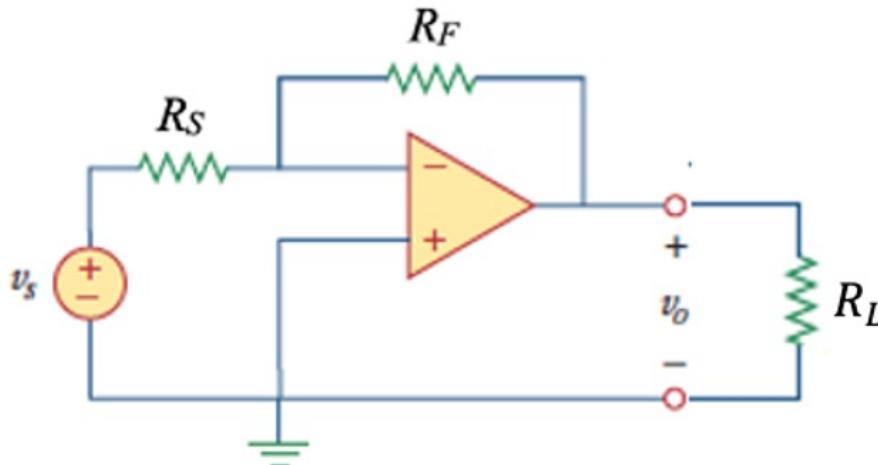

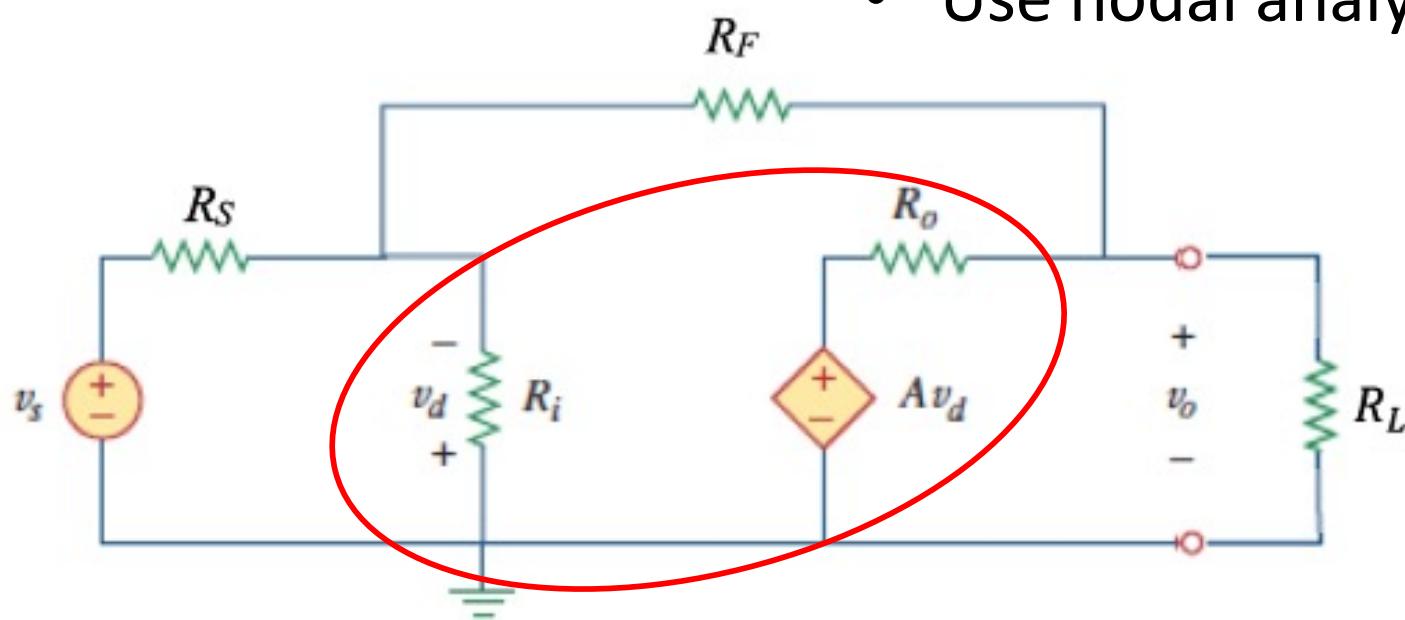- Circuit with “source”, “feedback”, and “load” resistors
- Substitute the simple model for the op amp
- Use nodal analysis




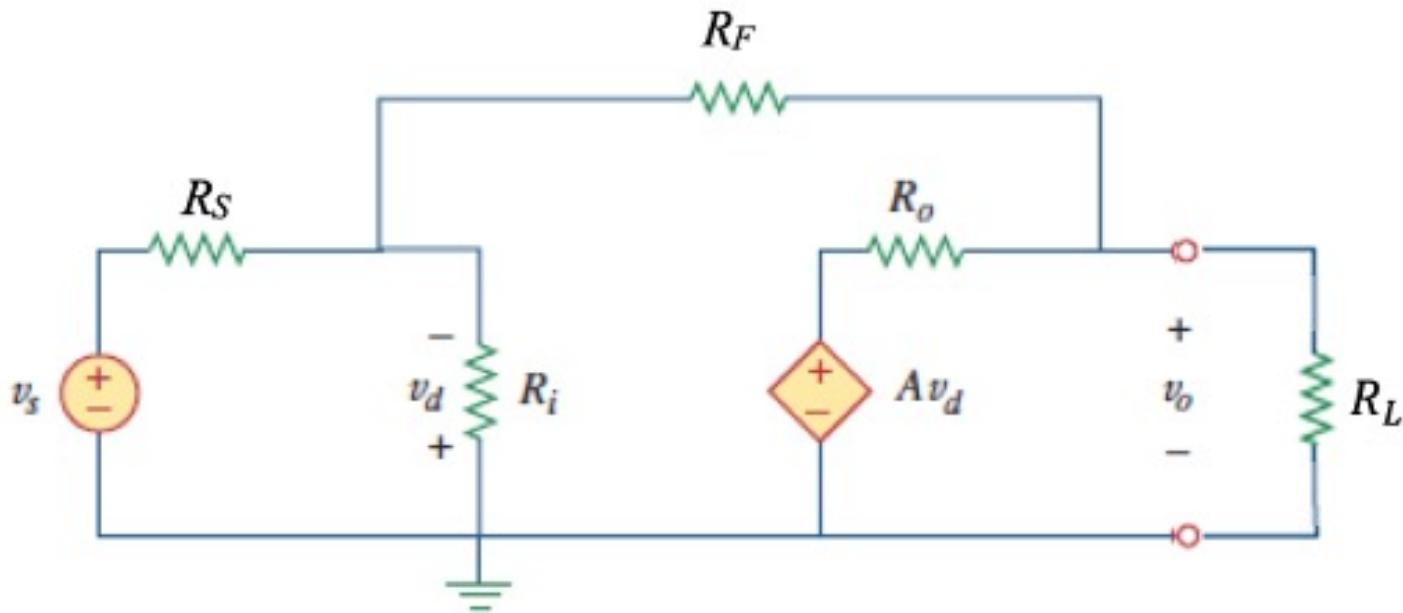

- **Nodes:** ground,  $v_o$ , and  $v_1 = -v_d$

$$\frac{v_1}{R_i} + \frac{v_1 - v_s}{R_S} + \frac{v_1 - v_o}{R_F} = 0$$

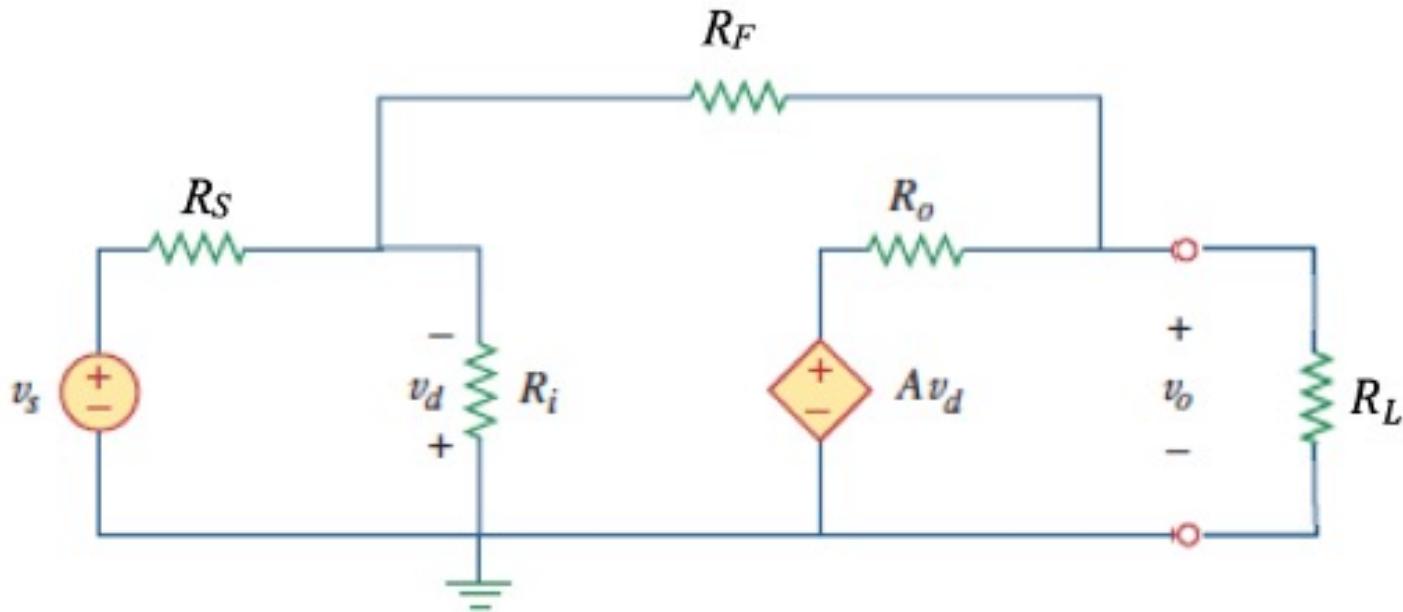
$$\frac{v_o + A v_1}{R_o} + \frac{v_o - v_1}{R_F} + \frac{v_o}{R_L} = 0$$



- After some tedious, symbolic algebra:

$$v_o = -\frac{R_i R_L (R_F A - R_o)}{R_L (R_S + R_i)(R_F + R_o) + (A + 1) R_S R_i R_L + R_o (R_S R_i + R_F R_i + R_S R_F)} v_s$$

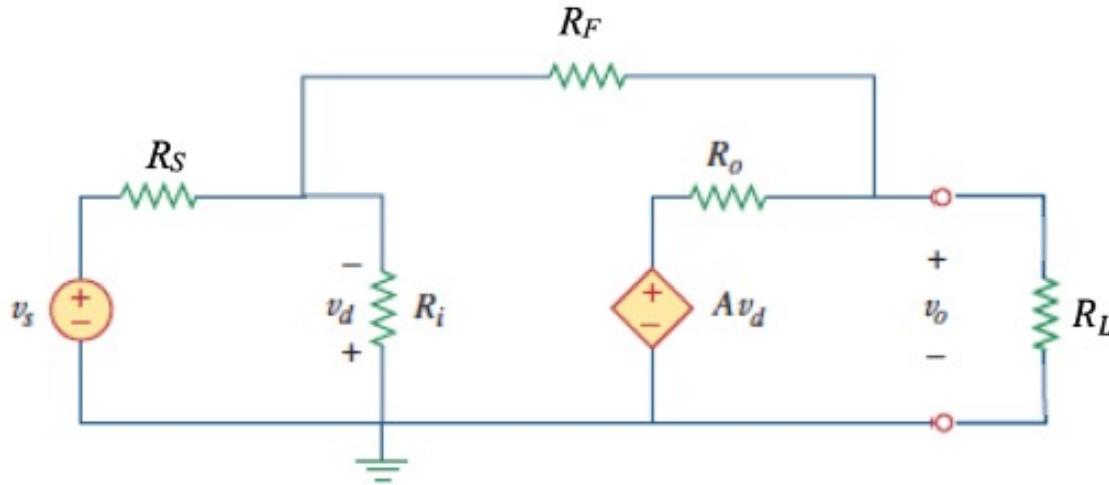- Note linearity, gain term is negative (“inverting amplifier”)



- External components:
  - $R_S = 10 \text{ k}\Omega$
  - $R_F = 20 \text{ k}\Omega$
  - $R_L = 40 \text{ k}\Omega$
- Nominal model parameters:
  - $R_i = 2 \text{ M}\Omega$
  - $R_o = 50 \Omega$
  - $A = 200,000$

$$v_o = -1.99997 v_s = -2.00 v_s$$


# Sensitivity Analysis

For  $R_S = 10 \text{ k}\Omega$ ,

$R_F = 20 \text{ k}\Omega$ , and

$R_L = 40 \text{ k}\Omega$

we have  $v_o = -2.00 v_s$

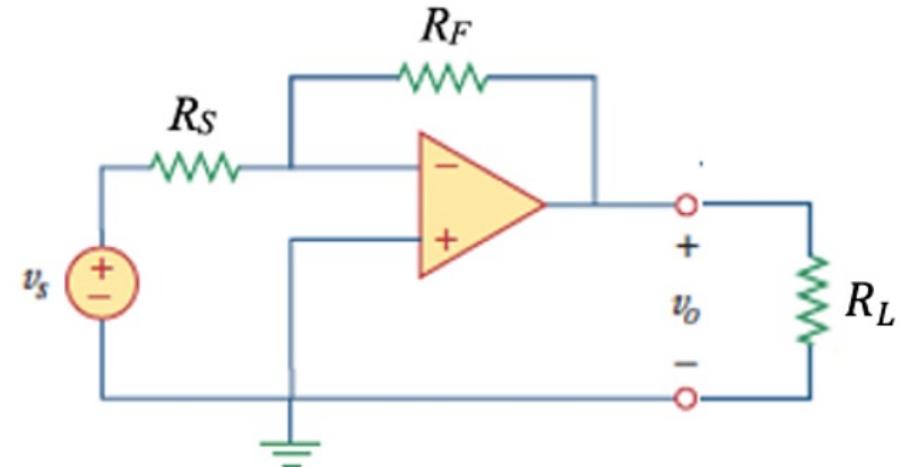

- How do the op amp's internal parameters ( $R_i, R_o$ , and  $A$ ) impact this result?
- What happens when we change the circuit's components ( $R_S, R_F$ , and  $R_L$ )?

## Sensitivity to internal values:

$R_S$	$R_F$	$R_L$	$R_i$	$R_o$	$A$	gain
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	200,000	-1.99997
10 kΩ	20 kΩ	40 kΩ	<b>1 MΩ</b>	50 Ω	200,000	-1.99997
10 kΩ	20 kΩ	40 kΩ	<b>4 MΩ</b>	50 Ω	200,000	-1.99997
10 kΩ	20 kΩ	40 kΩ	2 MΩ	<b>25 Ω</b>	200,000	-1.99997
10 kΩ	20 kΩ	40 kΩ	2 MΩ	<b>100 Ω</b>	200,000	-1.99997
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	<b>100,000</b>	<b>-1.99994</b>
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	<b>400,000</b>	<b>-1.99998</b>
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	<b>50,000</b>	<b>-1.99988</b>
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	<b>20,000</b>	<b>-1.99970</b>

Seems insensitive!

Sensitivity to circuit component values:

$R_S$	$R_F$	$R_L$	$R_i$	$R_o$	$A$	gain
10 kΩ	20 kΩ	40 kΩ	2 MΩ	50 Ω	200,000	-1.99997
10 kΩ	20 kΩ	<b>20 kΩ</b>	2 MΩ	50 Ω	200,000	-1.99997
10 kΩ	20 kΩ	<b>80 kΩ</b>	2 MΩ	50 Ω	200,000	-1.99997
10 kΩ	<b>10 kΩ</b>	40 kΩ	2 MΩ	50 Ω	200,000	<b>-0.99999</b>
10 kΩ	<b>40 kΩ</b>	40 kΩ	2 MΩ	50 Ω	200,000	<b>-3.99990</b>
10 kΩ	<b>100 kΩ</b>	40 kΩ	2 MΩ	50 Ω	200,000	<b>-9.99945</b>
<b>5 kΩ</b>	20 kΩ	40 kΩ	2 MΩ	50 Ω	200,000	<b>-3.99990</b>
<b>20 kΩ</b>	20 kΩ	40 kΩ	2 MΩ	50 Ω	200,000	<b>-0.99999</b>
<b>40 kΩ</b>	20 kΩ	40 kΩ	2 MΩ	50 Ω	200,000	<b>-0.499996</b>

Only depends upon source and feedback resistors!


# Asymptotics

- Consider the gain term when  $A$  is large,  $R_i$  is large, and  $R_o$  is small


$$-\frac{R_i R_L (R_F A - R_o)}{R_L (R_S + R_i) (R_F + R_o) + (A + 1) R_S R_i R_L + R_o (R_S R_i + R_F R_i + R_S R_F)}$$

- Then
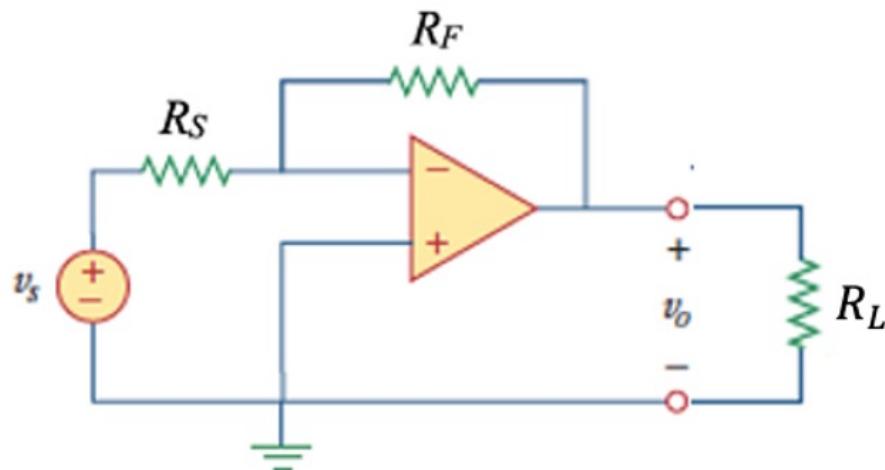
$$\frac{v_o}{v_s} \approx -\frac{R_i R_L R_F A}{(A + 1) R_S R_i R_L} \approx -\frac{R_F}{R_S}$$



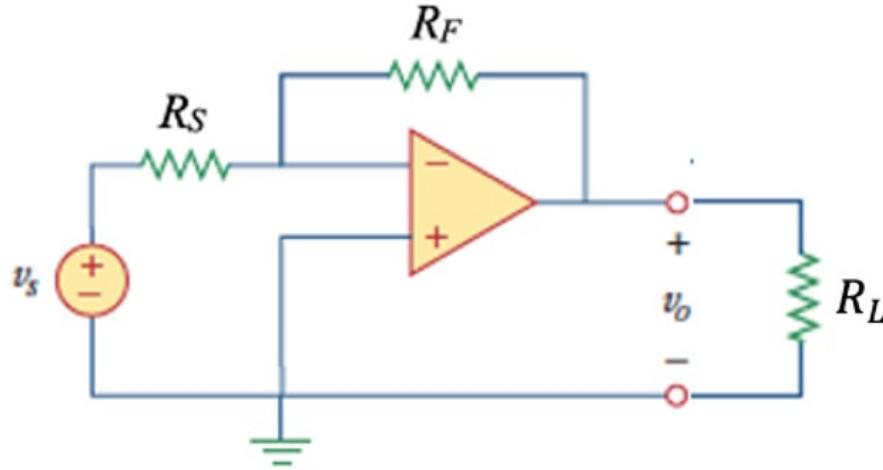- Further, consider the op amp's input side:



$$v_d = -\frac{R_i(R_L R_o + R_L R_F + R_o R_F)}{R_L(R_S + R_i)(R_F + R_o) + (A + 1)R_S R_i R_L + R_o(R_S R_i + R_F R_i + R_S R_F)} v_s$$

- For the nominal values

$$v_d = -\frac{v_s}{99,628} \approx 0$$

$$i_d = \frac{v_d}{2,000,000} \approx 0$$

## More general model:


- $v_d \approx 0$ 
  - we have a “virtual short” across the inputs

$$v_p = v_n$$


- $i_d \approx 0$ 
  - the inputs are open circuits

$$i_p = i_n = 0$$

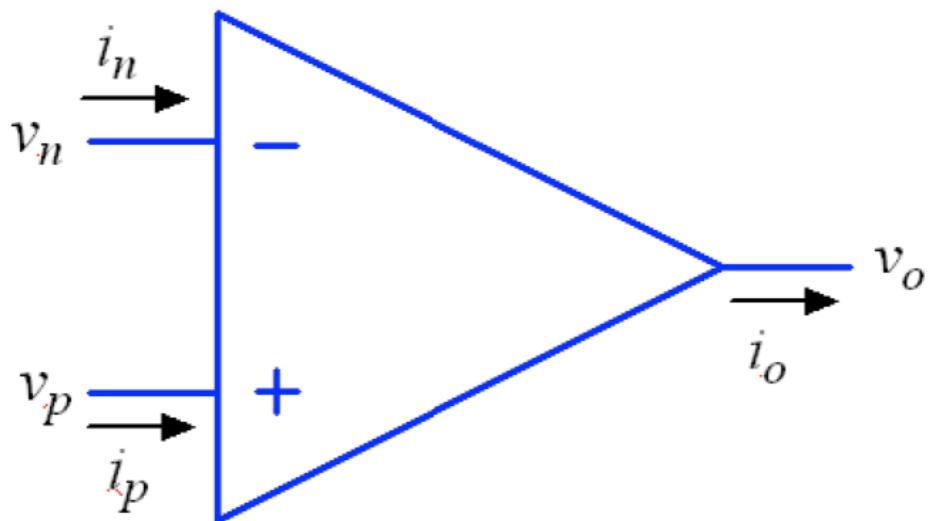- And  $i_o = ?$ 
  - The device generates whatever current is needed




# Using the Simple Model

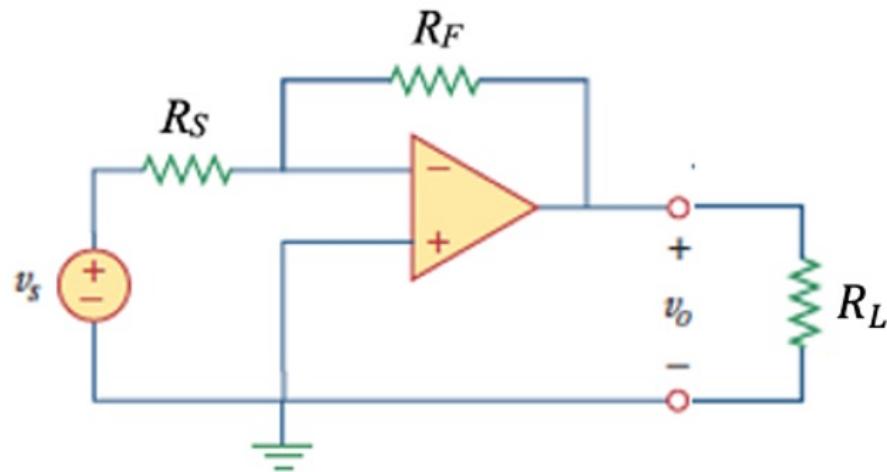

Input voltages equal  
Input currents zero

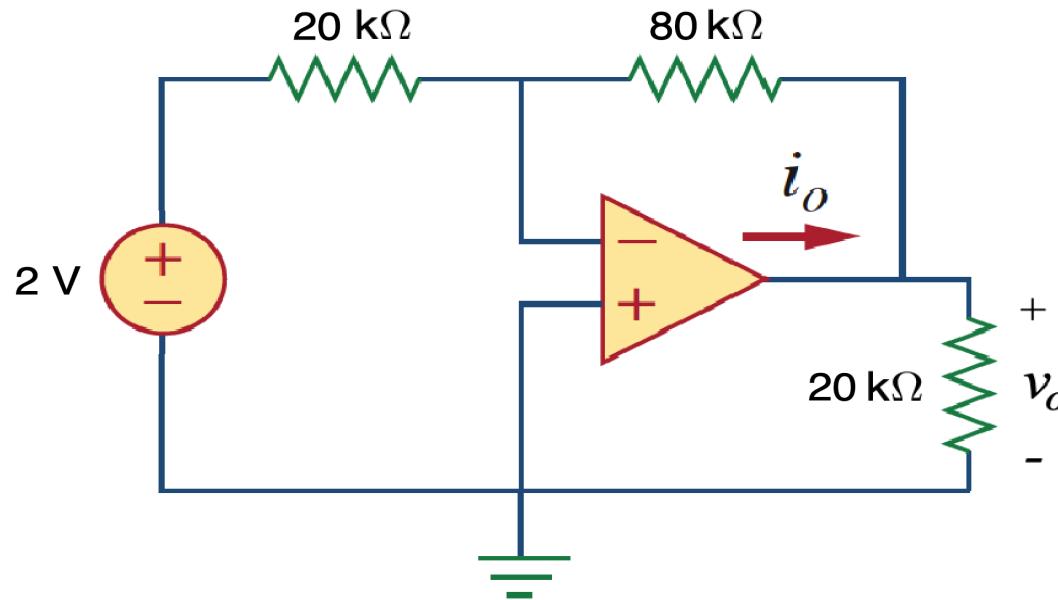**Example:** find  $v_o$  and  $i_o$


$$v_o = -8 \text{ V}, i_o = -0.5 \text{ mA}$$



Input voltages equal  
Input currents zero

Example: find  $v_o$


$$v_o = -14 V$$

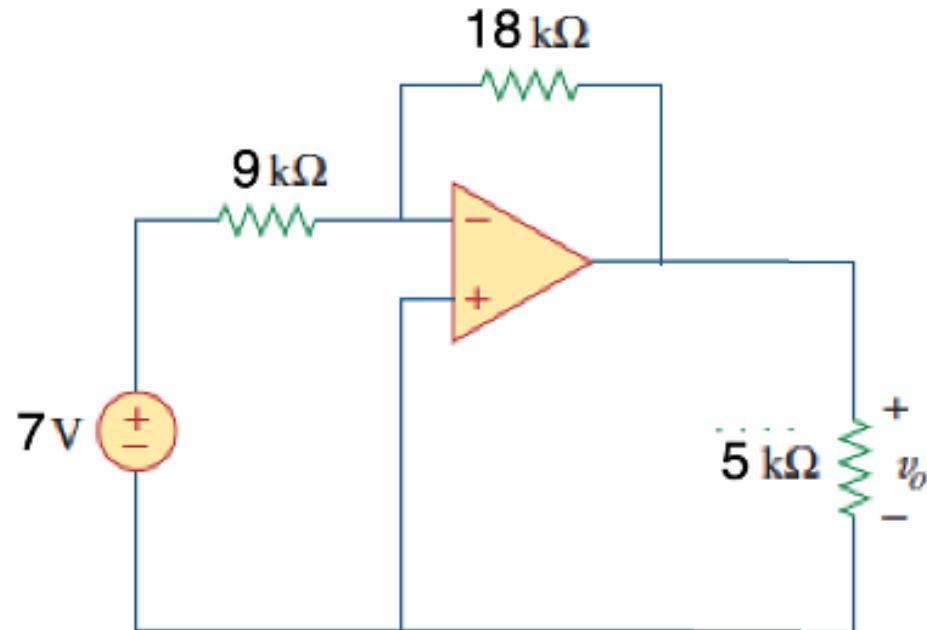

Input voltages equal  
Input currents zero

Example: find  $v_o$


$$v_o = 2.7 \text{ V}$$

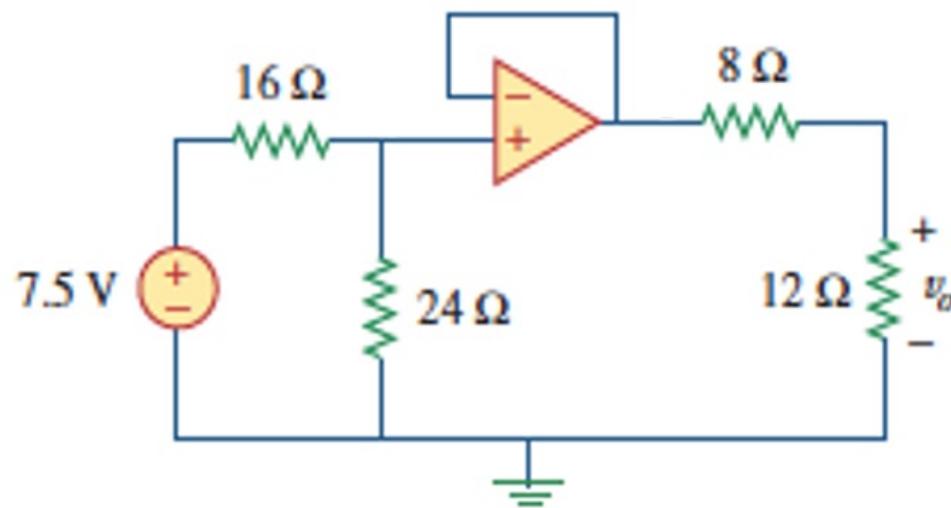

Input voltages equal  
Input currents zero

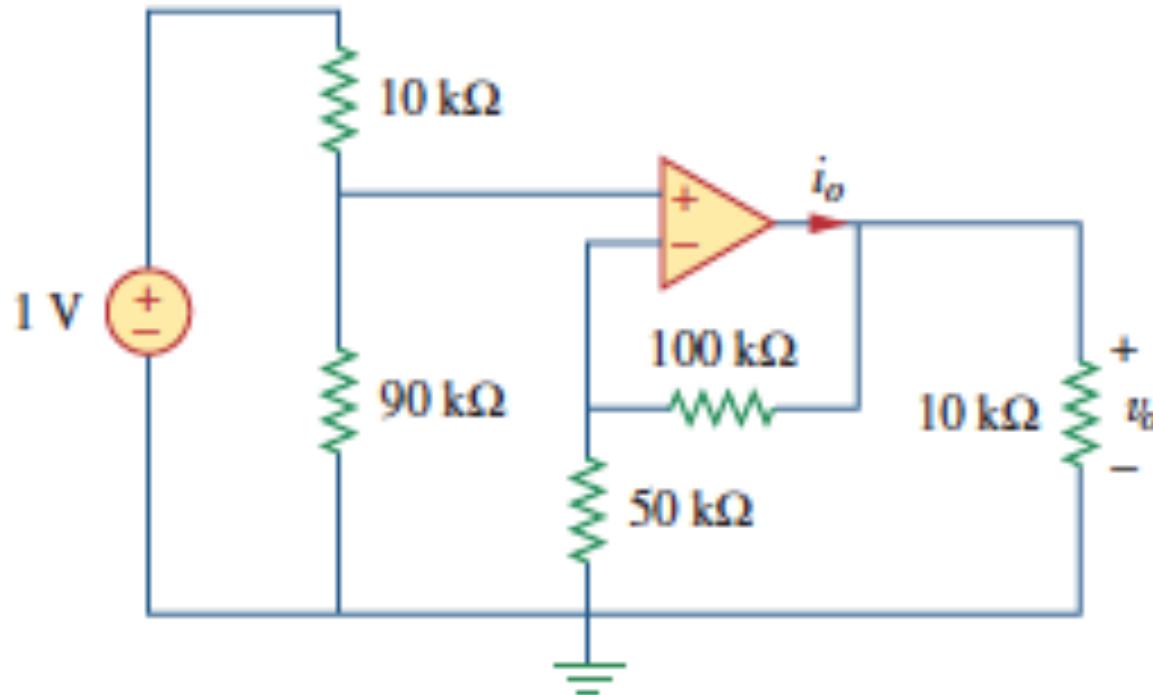Example: find  $v_o$  and  $i_o$

$$v_o = 2.7 \text{ V}, i_o = 0.2718 \text{ mA}$$




**Input voltages equal  
Input currents zero**

## Practice problem:

$$i_o = -0.5625 \text{ mA}$$

**5.19** Determine  $i_o$  in the circuit of Fig. 5.58.

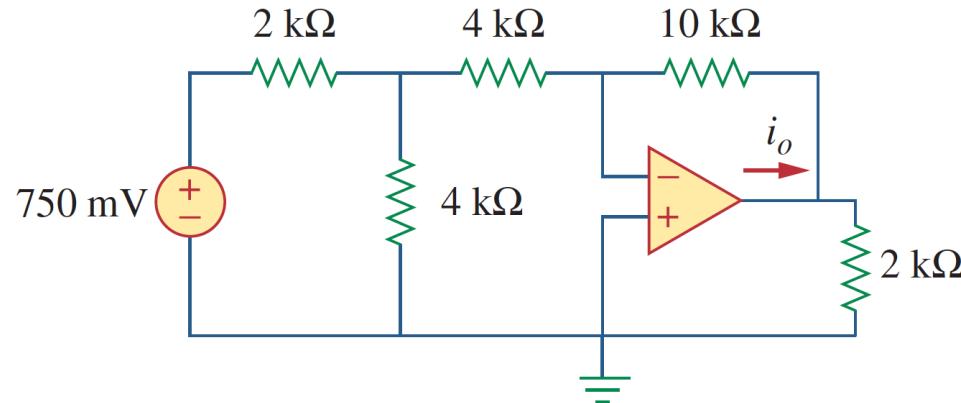

**Figure 5.58**


For Prob. 5.19.

**Input voltages equal  
Input currents zero**

## Practice problem:

$$i_x = 0.727 \text{ mA}$$


- 5.31 For the circuit in Fig. 5.69, find  $i_x$ .

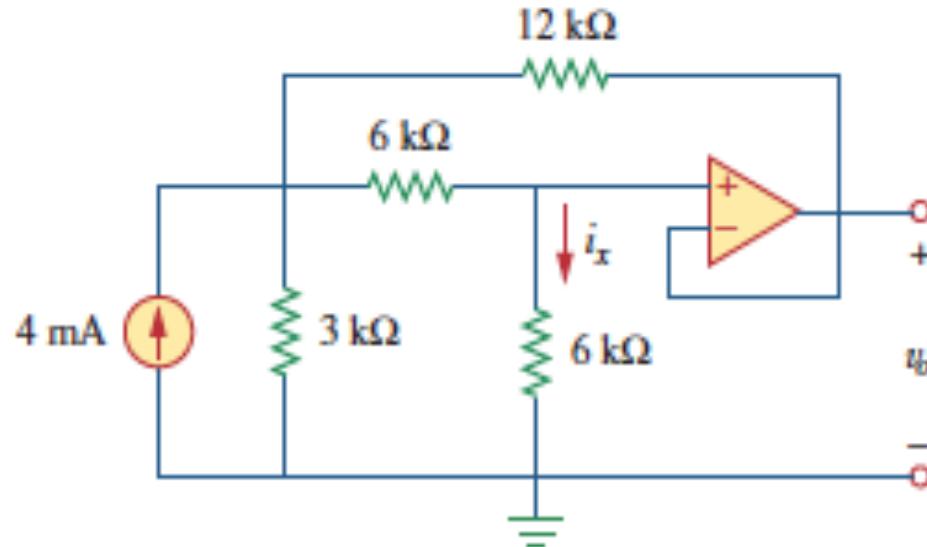

**Figure 5.69**  
For Prob. 5.31.

$$i = -0.51 \text{ mA}$$

**Practice problem:** find  $i$

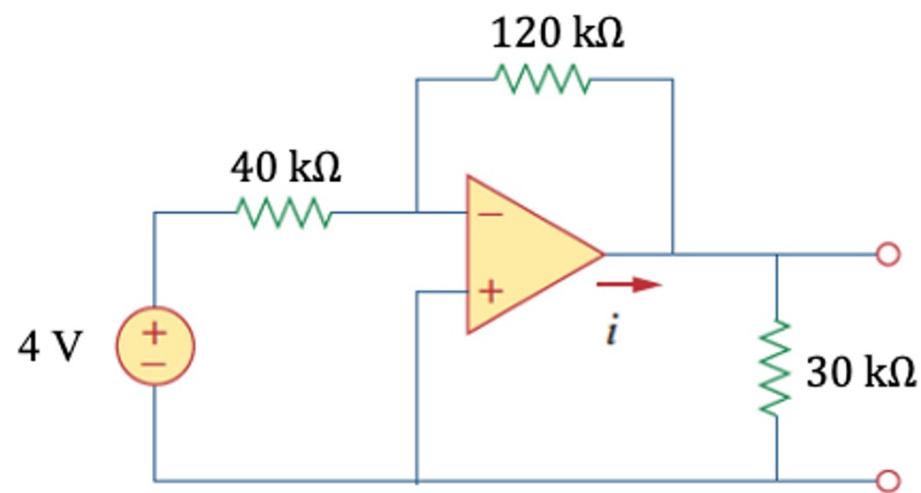

$$i_o = 0.42 \text{ mA}$$

**Practice problem:** find  $i_o$

