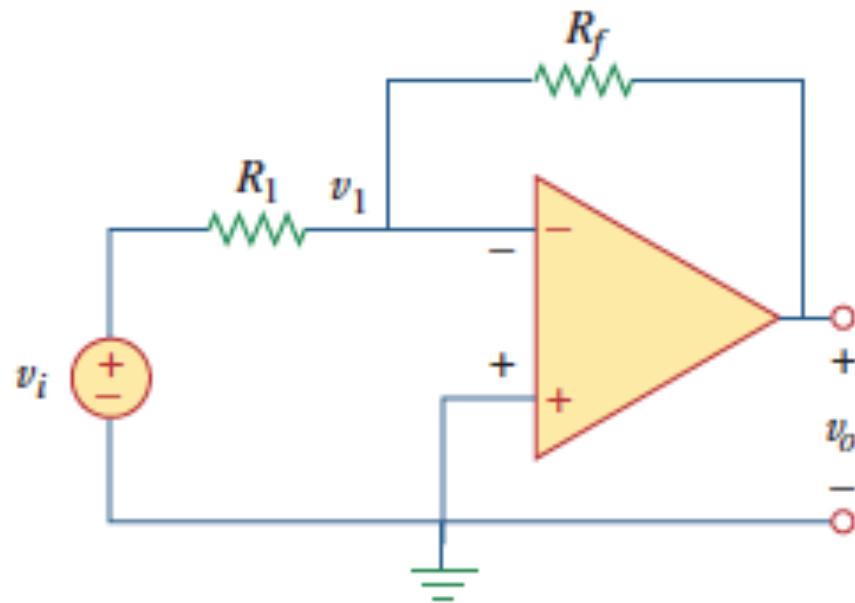


Op Amps – 2


standard configurations




Some Standard Configurations

- Exploit equal input voltages, zero input currents
- Inverting amplifier:




$$v_o = -\frac{R_f}{R_s} v_s$$


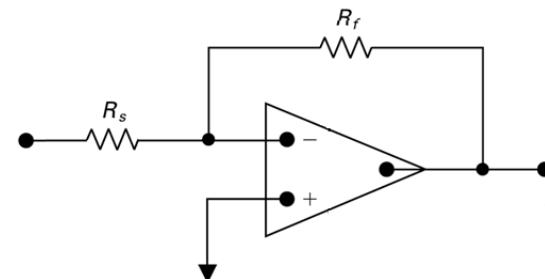


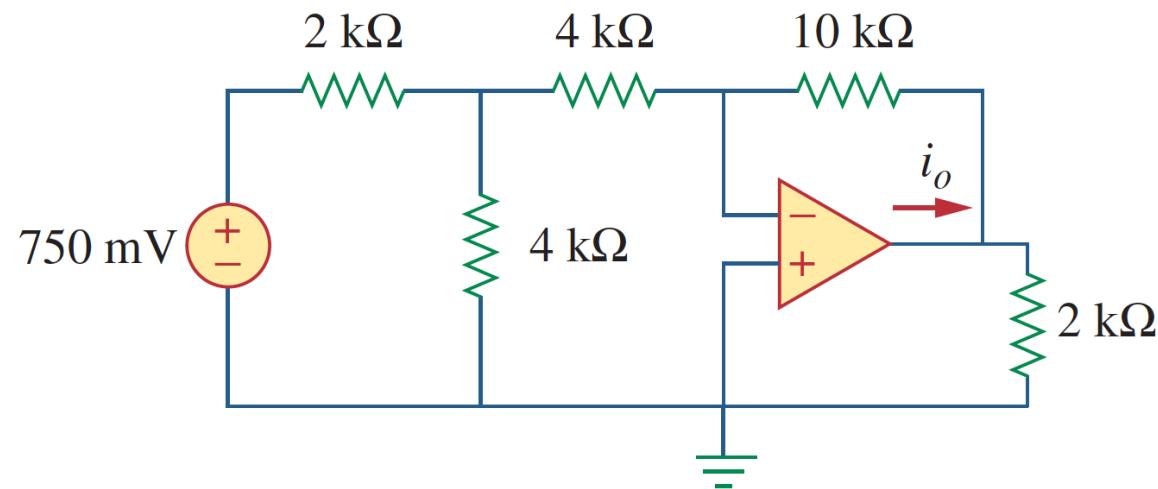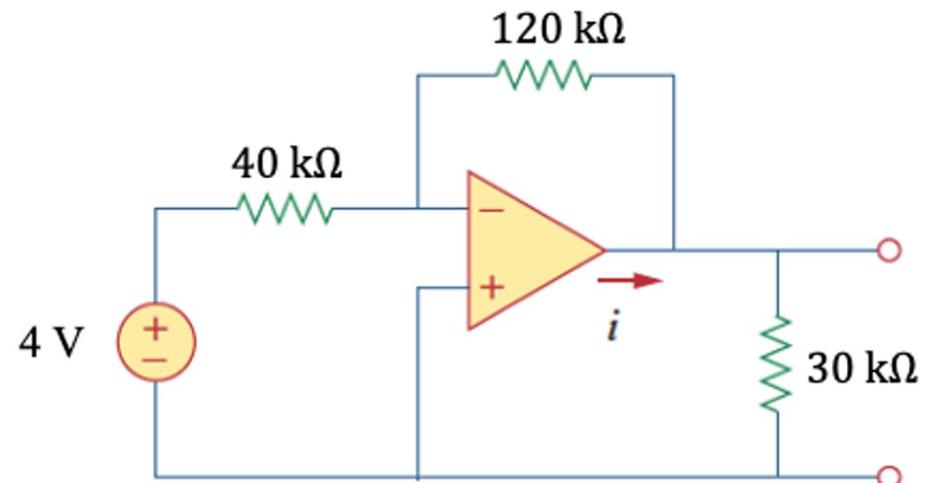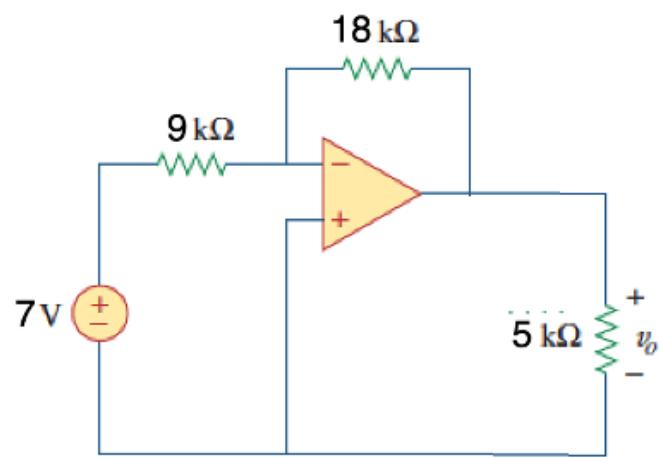


**Input voltages equal
Input currents zero**

- Summing amplifier:

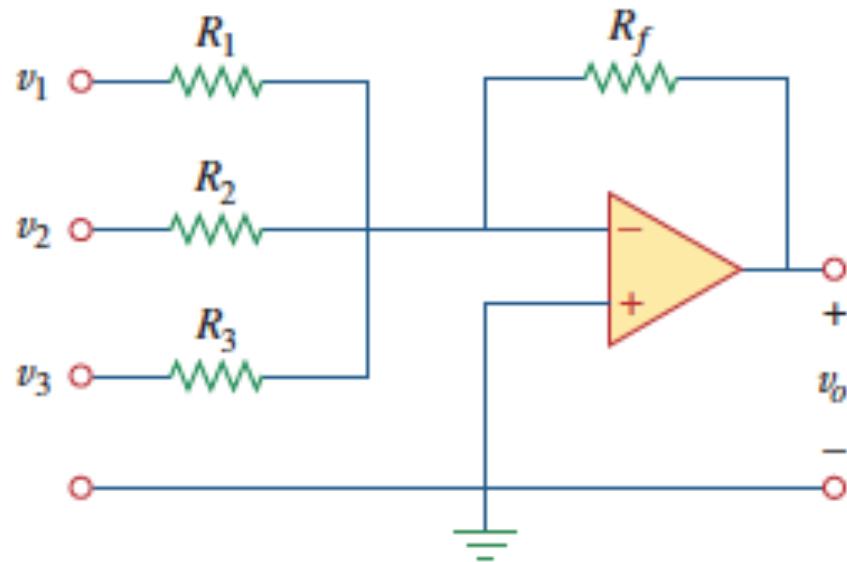

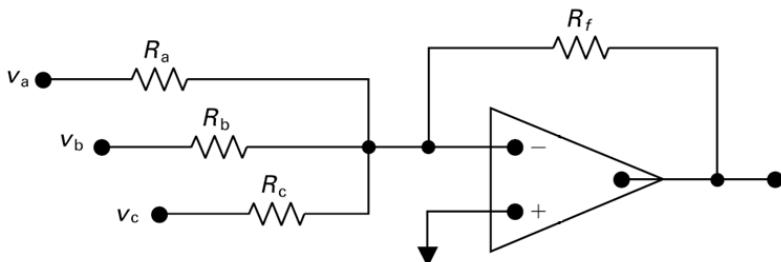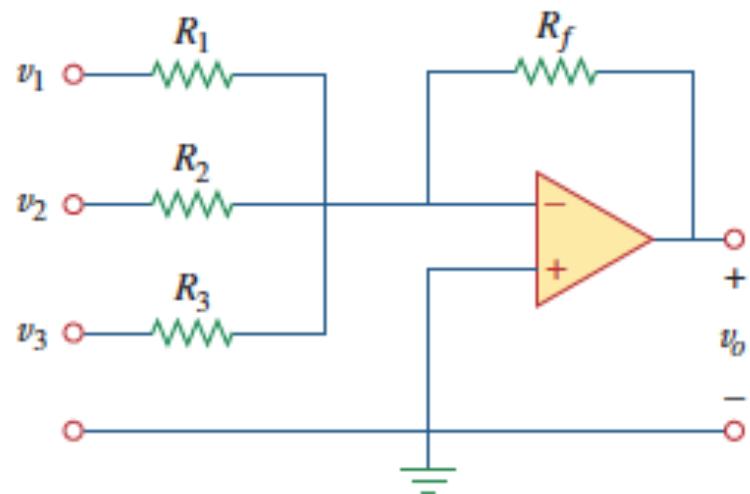

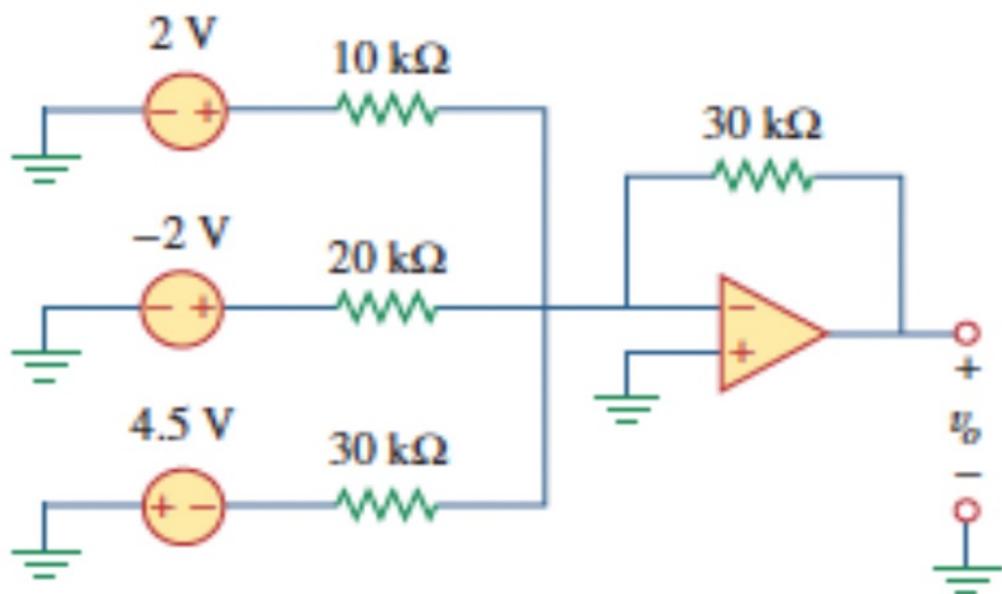
$$v_o = - \left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3 \right)$$





$$v_o = -7.5 V$$


**Input voltages equal
Input currents zero**

- Non-inverting Amplifier

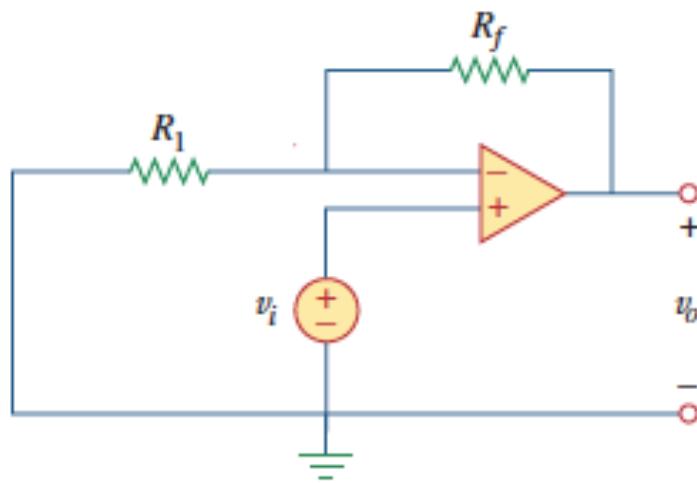

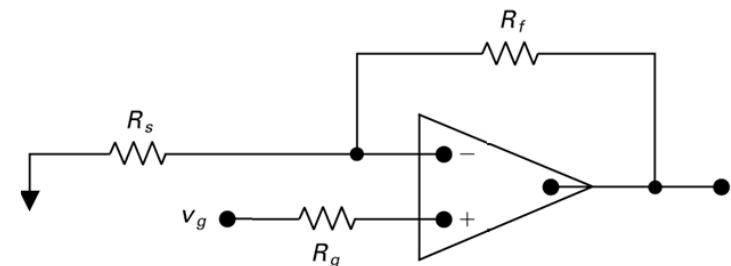
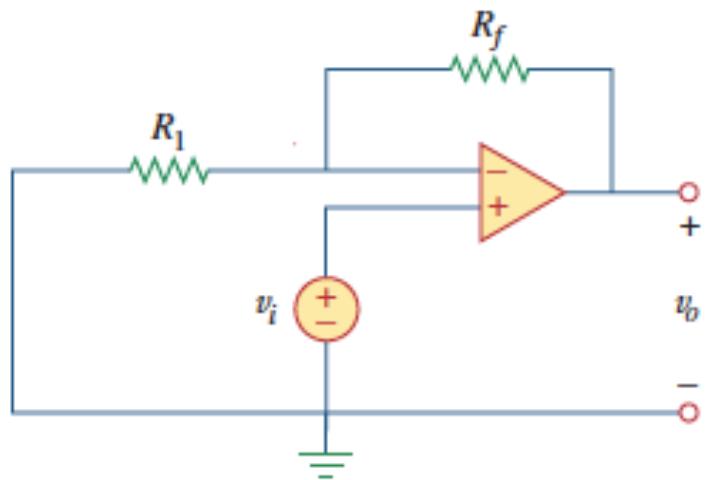

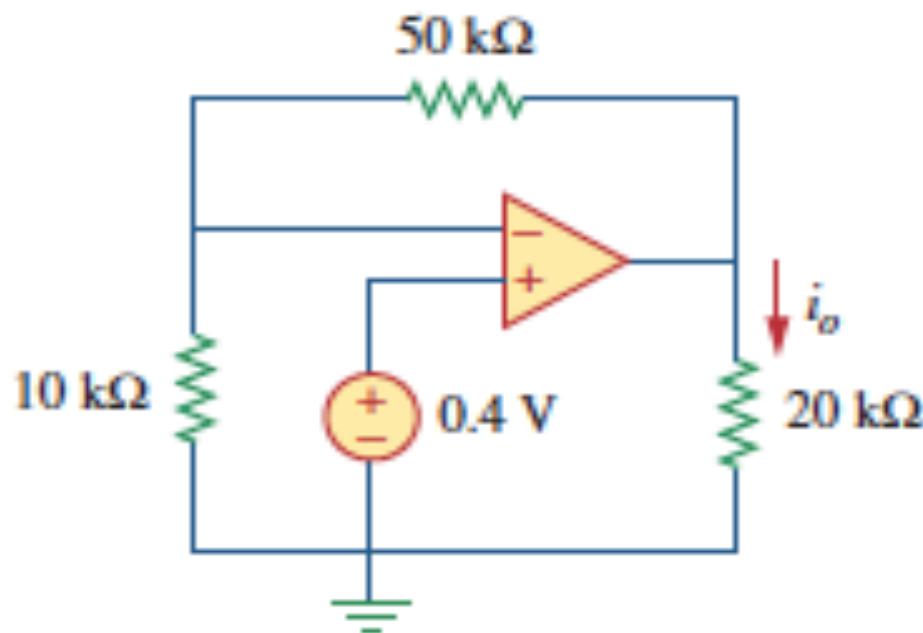
$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_s$$




$$i_o = -0.12 \text{ mA}$$



More obscure examples:

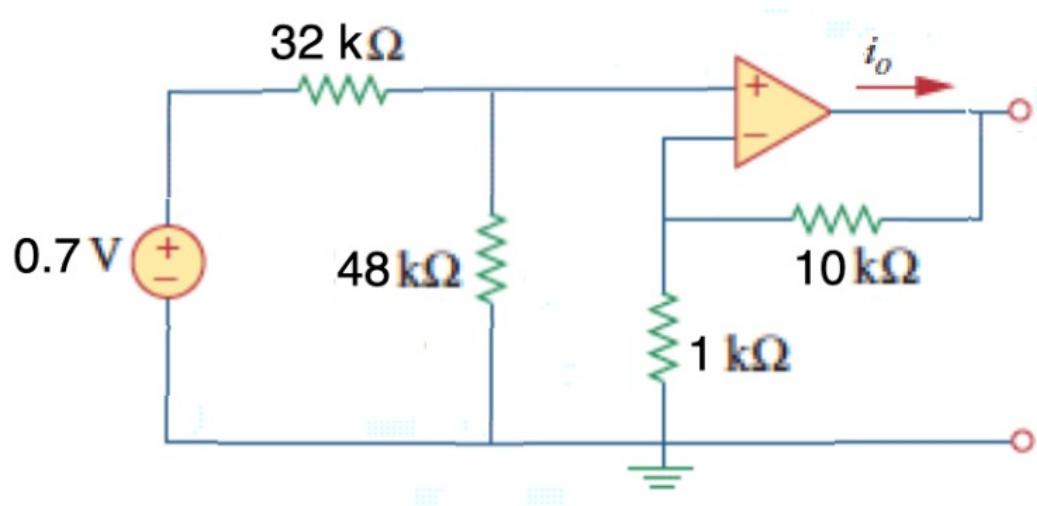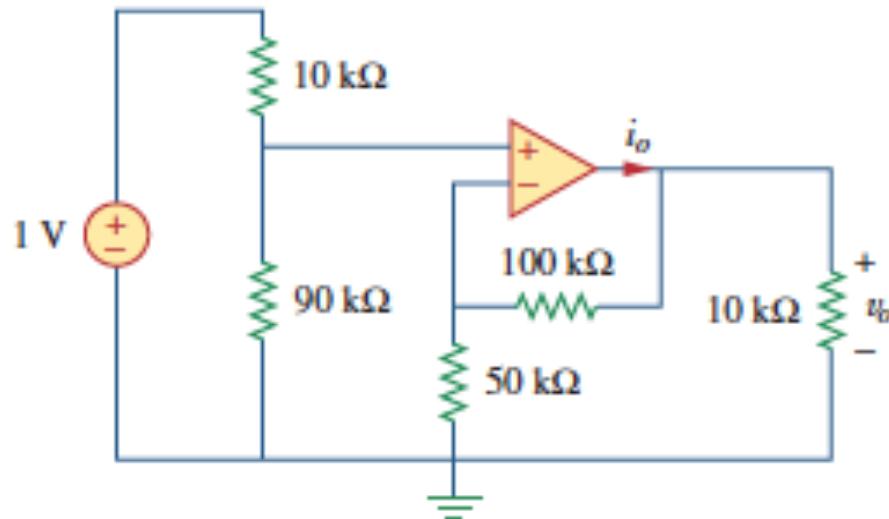


**Input voltages equal
Input currents zero**

- Difference amplifier

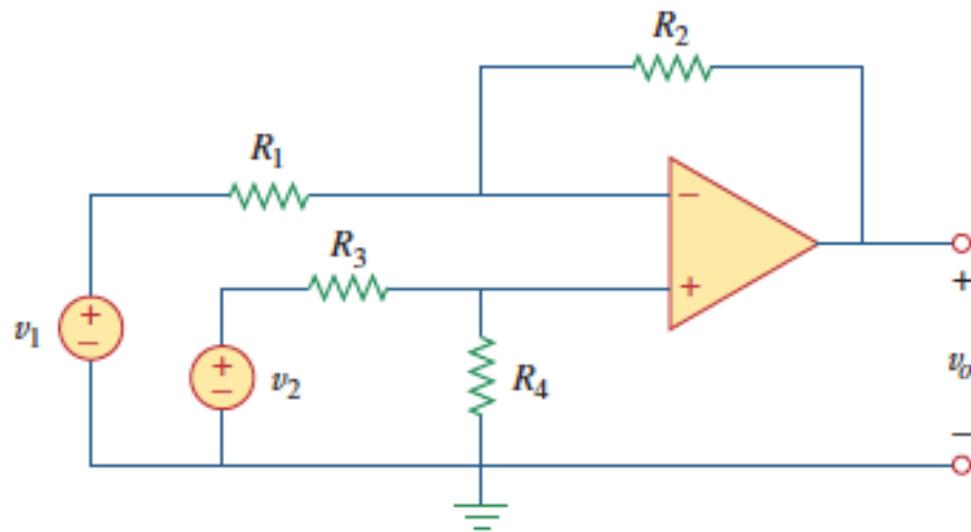

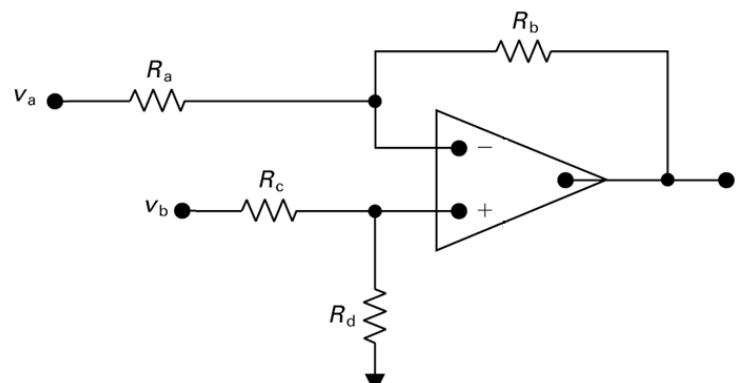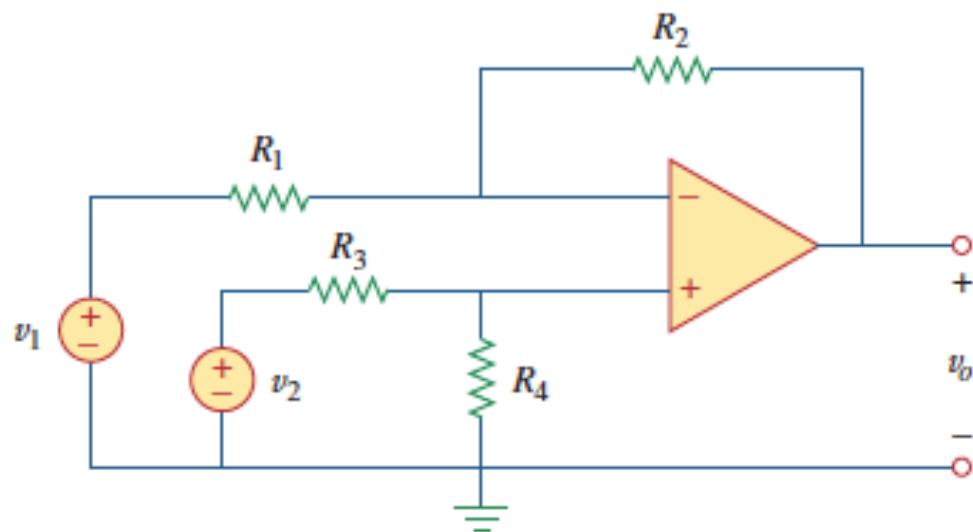


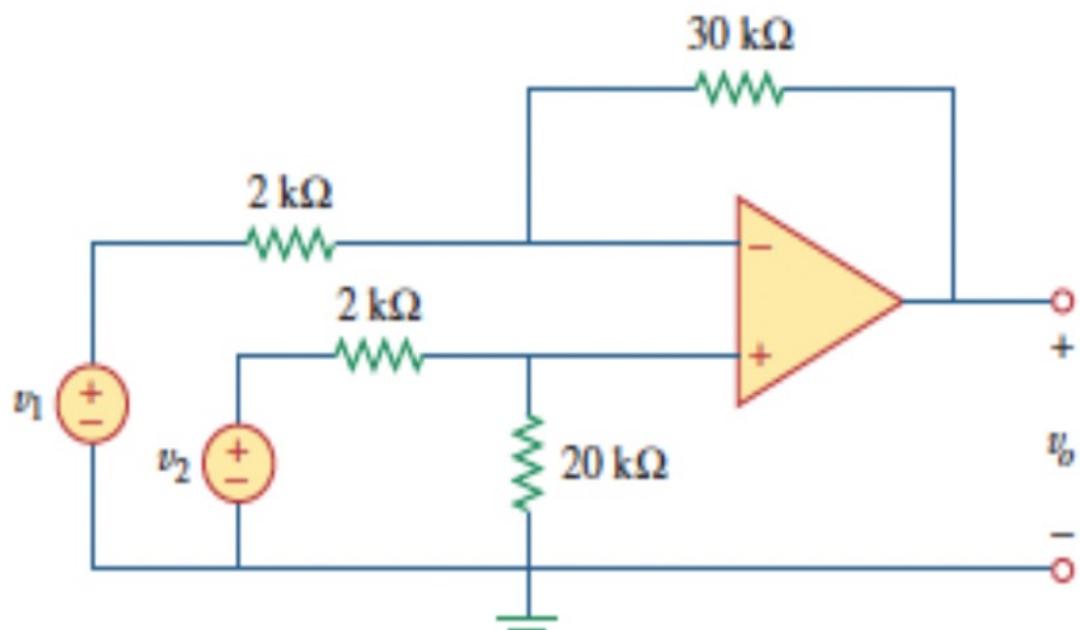
$$v_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) v_2 - \frac{R_2}{R_1} v_1$$




$$v_o = (160v_2 - 165v_1)/11$$

Input voltages equal
Input currents zero

- Voltage Follower

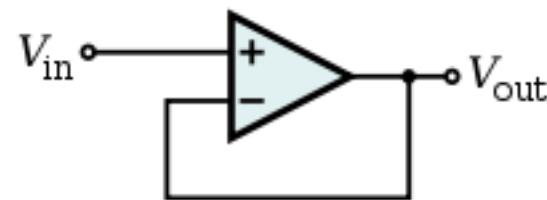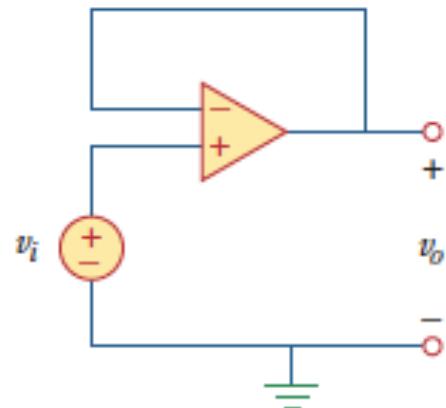


$$v_o = v_1$$

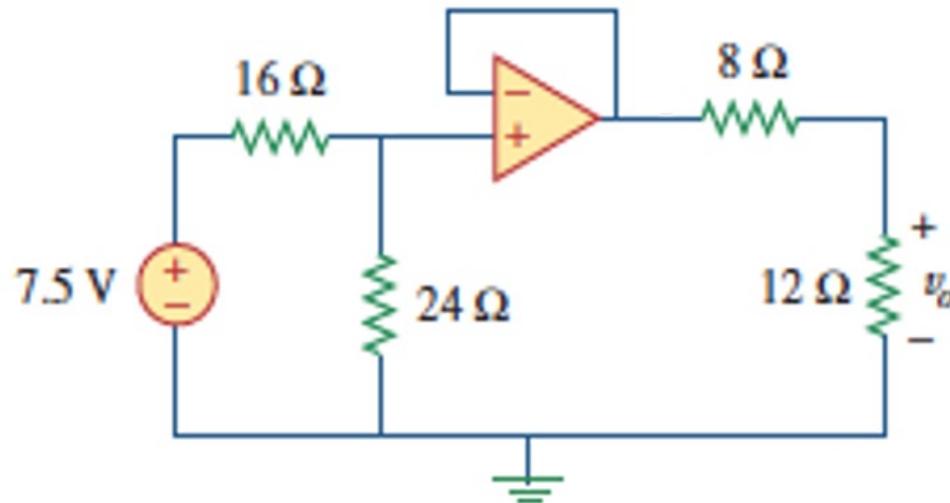


$$v_o = -3 \text{ V}$$

Practice problem: find v_o

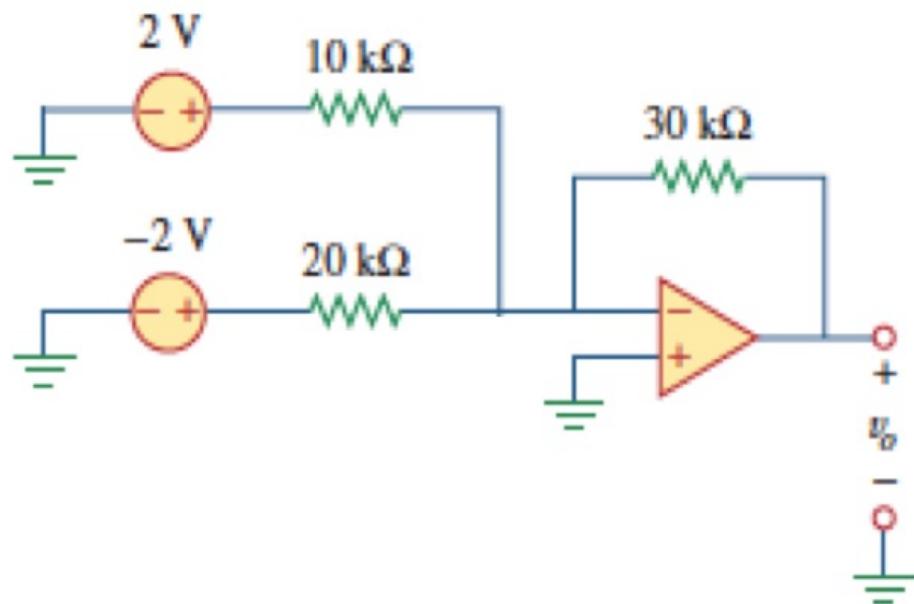


Practice problem: find v_o

$$v_o = -2(V_1 + V_2)$$

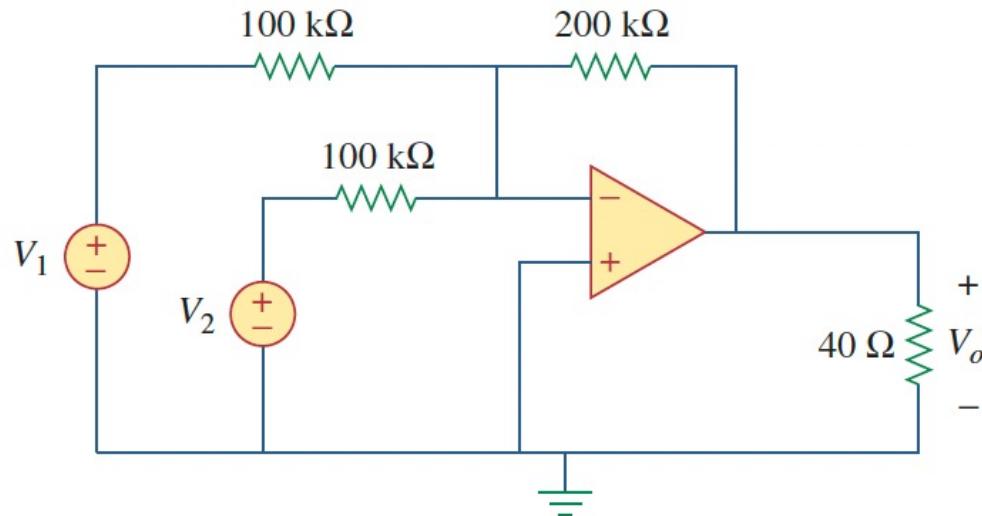


Practice problem: find v and i

$$v = 5 \text{ V}, i = -0.1 \text{ mA}$$

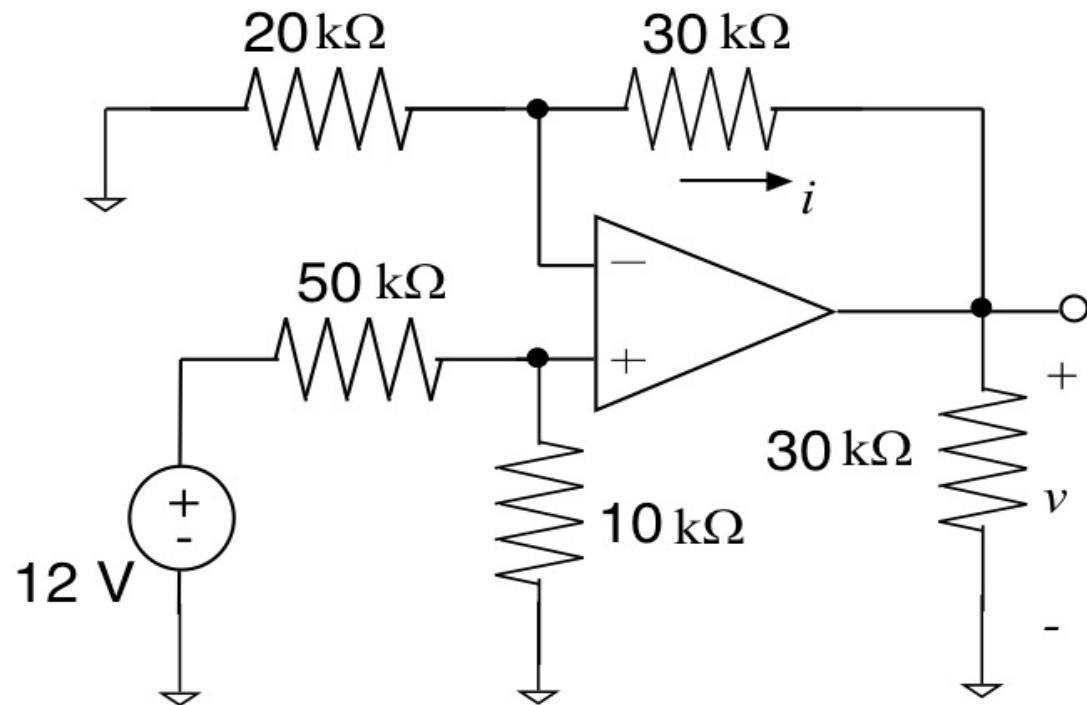

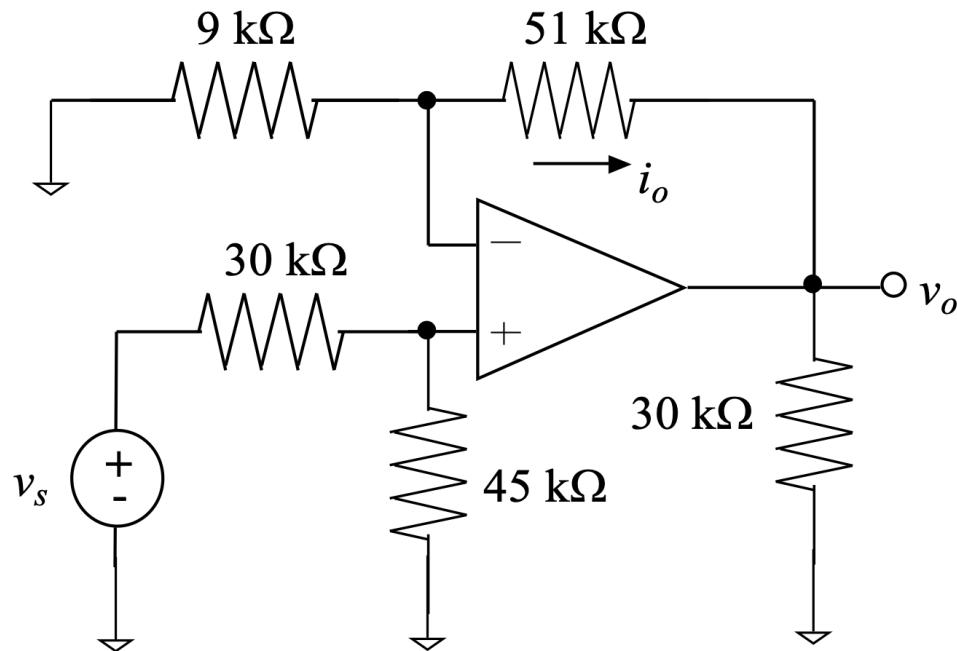
Practice problem: find v_o and i_o if $v_s = 2 V$



$$v_o = 8 V, i = -0.133 mA$$

Practice problem: find V_o

$$V_o = 2(V_2 - V_1)$$

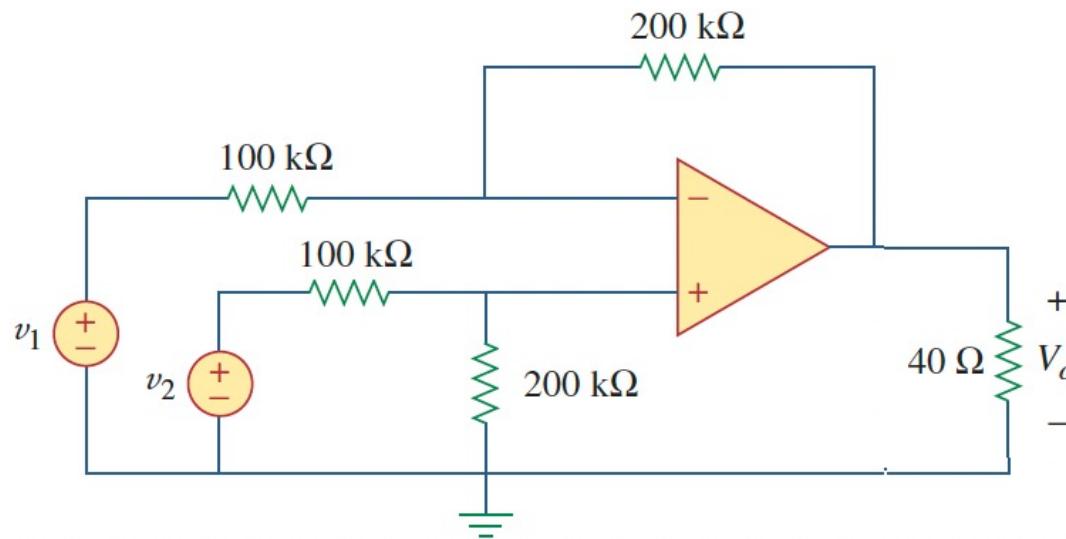

Practice problem: find v_o

$-4 V$

