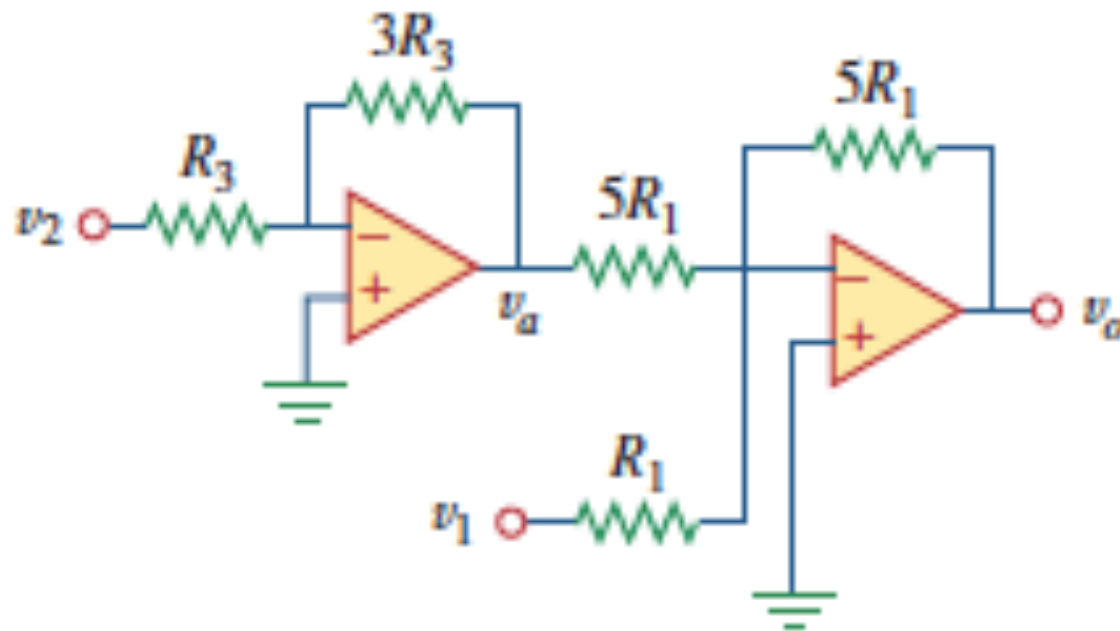


Op Amps – 3

multiple op amps, AC


Now what?

- Method is to exploit known forms and/or apply the usual rules:




$$v_o = 3v_2 - 5v_1$$

Example: find v_o

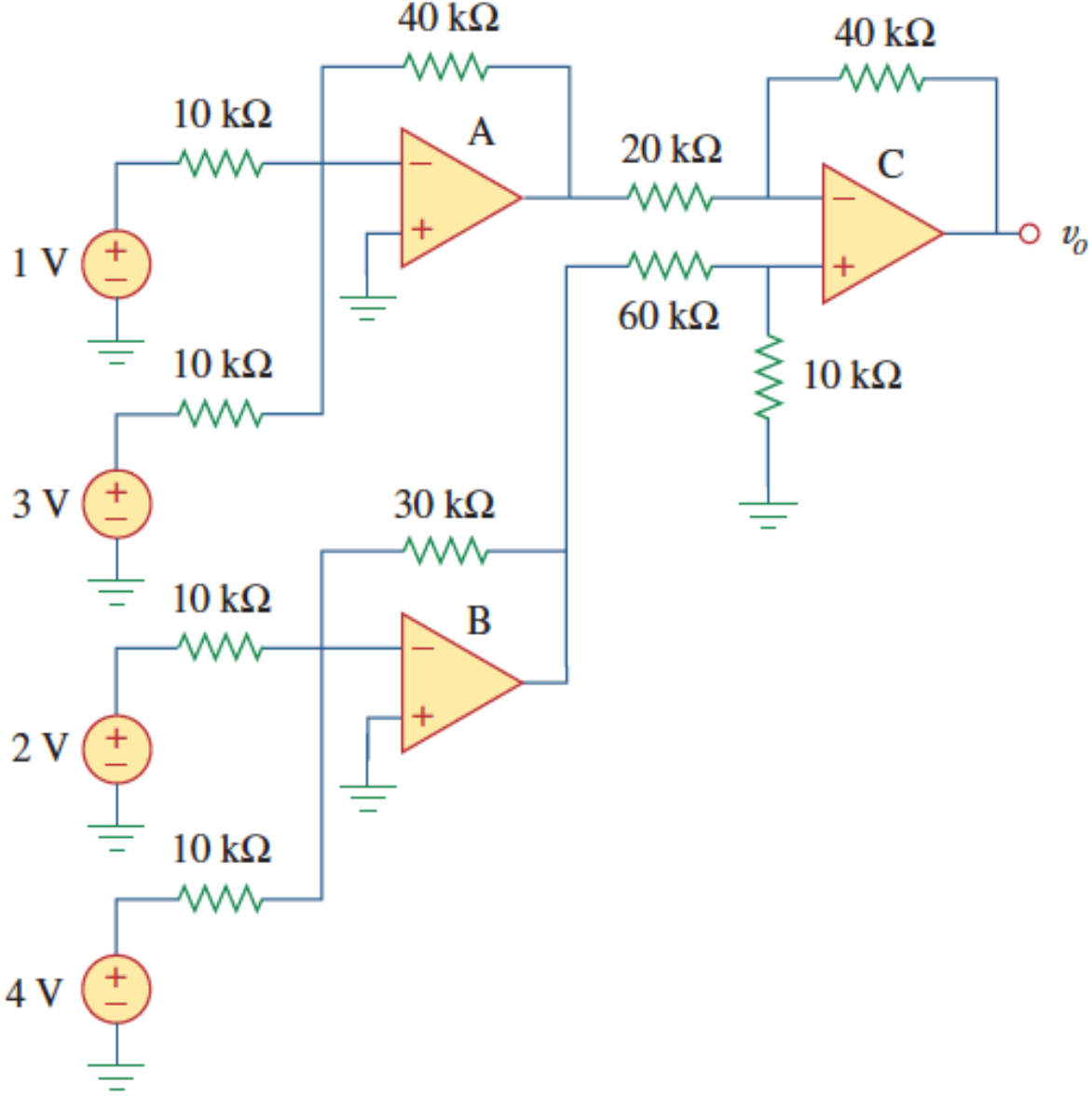



$v_o = 25.1 \text{ V}$

Example: find v_o

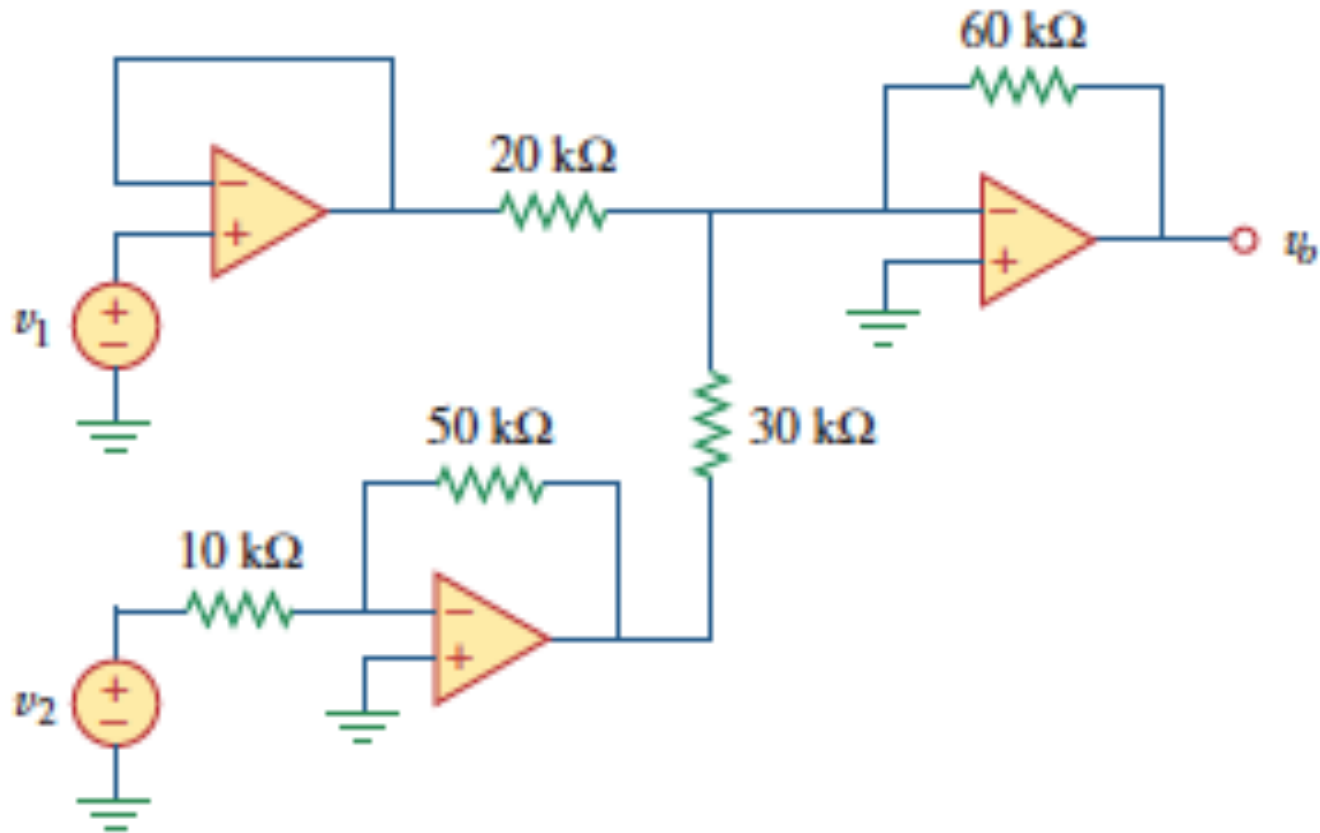


$$v_o = 10v_2 - 3v_1$$

Might have extra components:

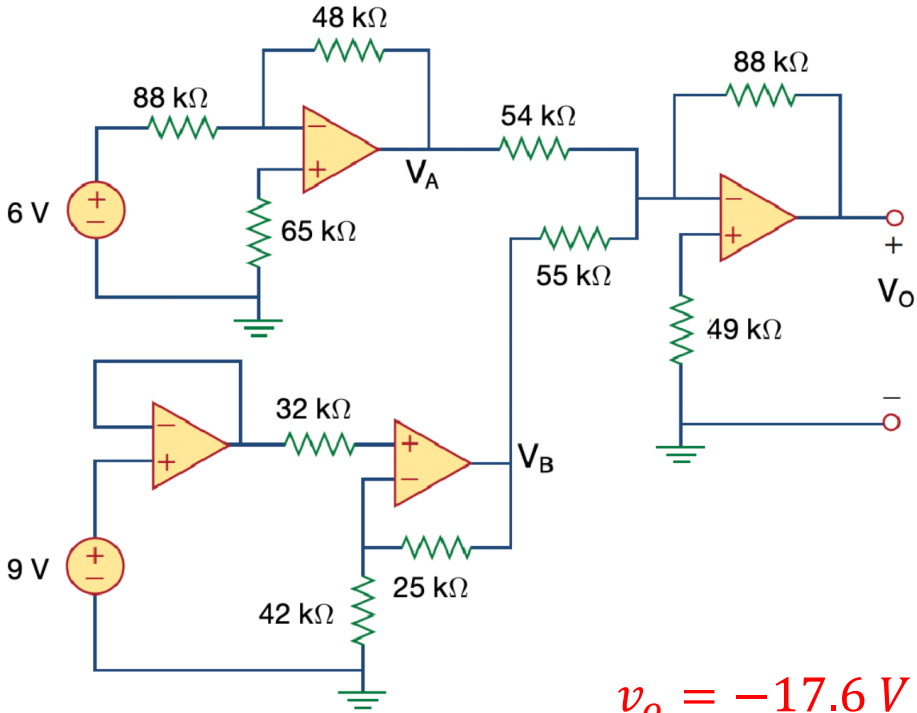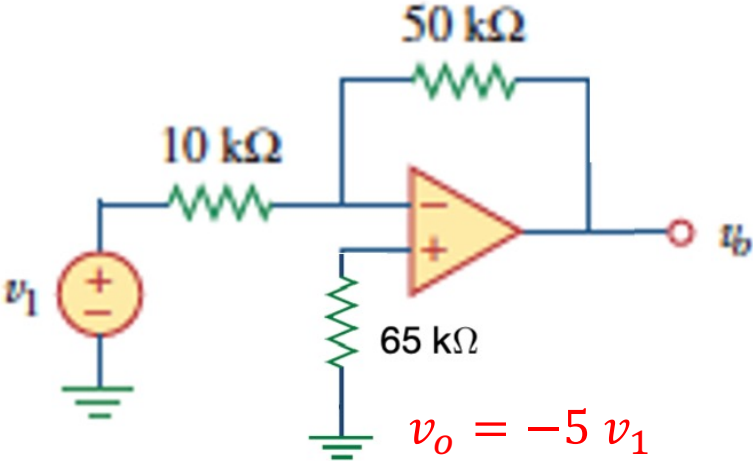

Or just be more complex

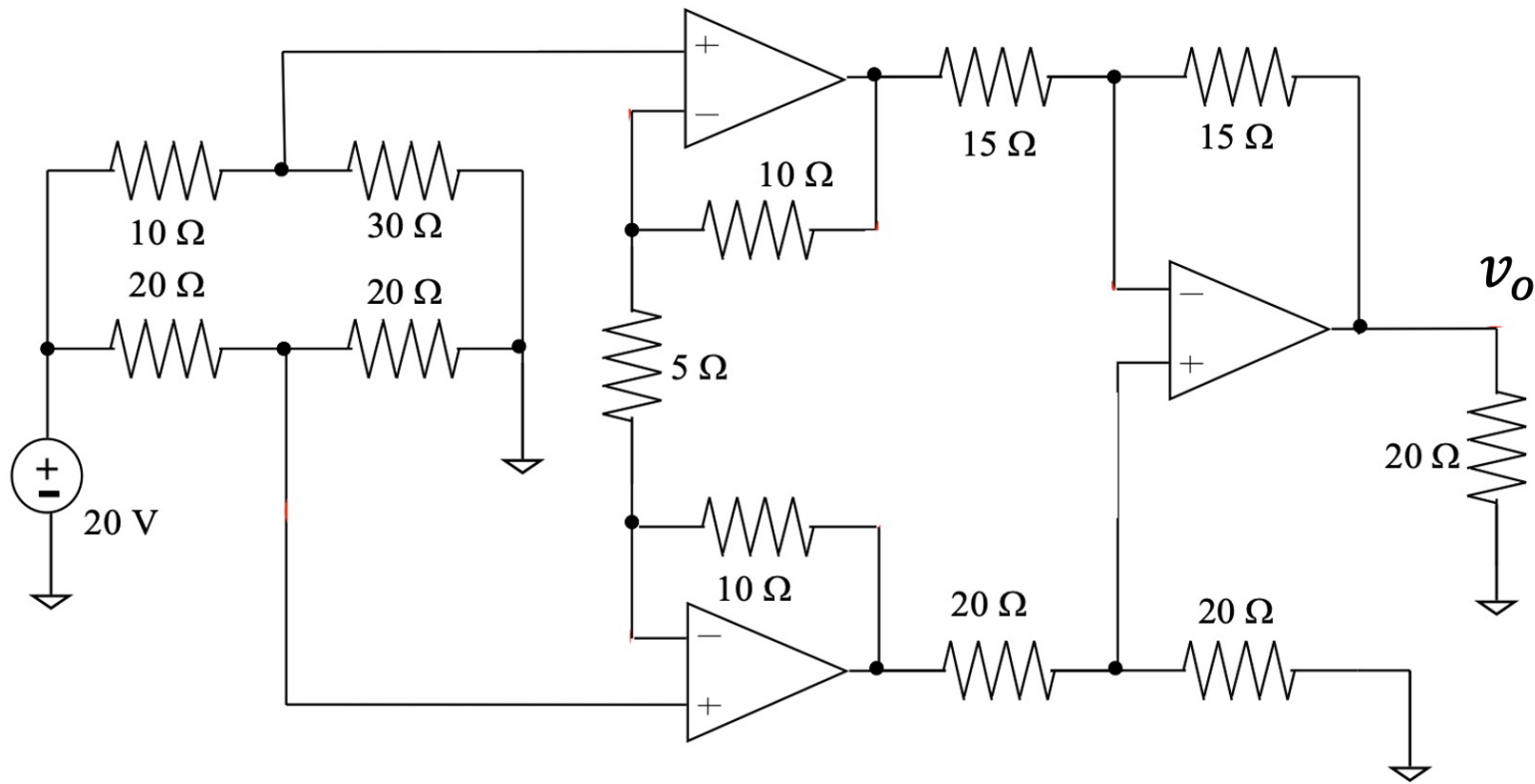


$$v_o = -25 V$$

Op Amps and AC


- Recall the inverting amplifier

$$\text{gain} = -\frac{R_f}{R_i}$$

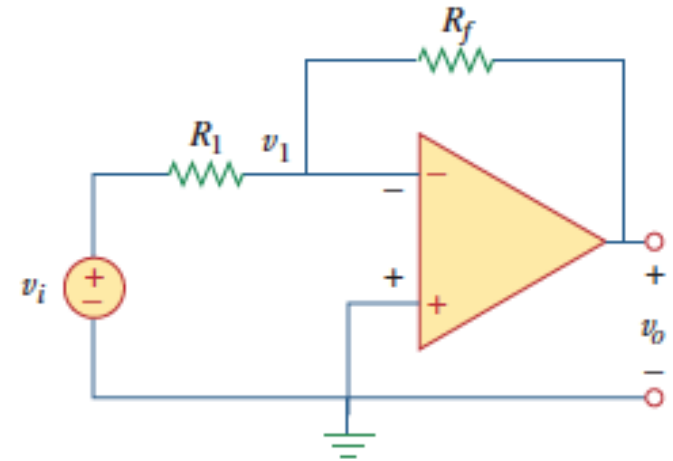


- Now, an “active” filter

$$H(\omega) = -\frac{Z_f}{Z_i}$$

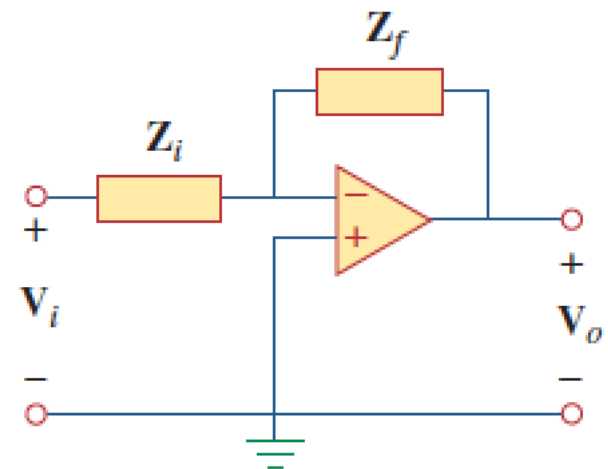


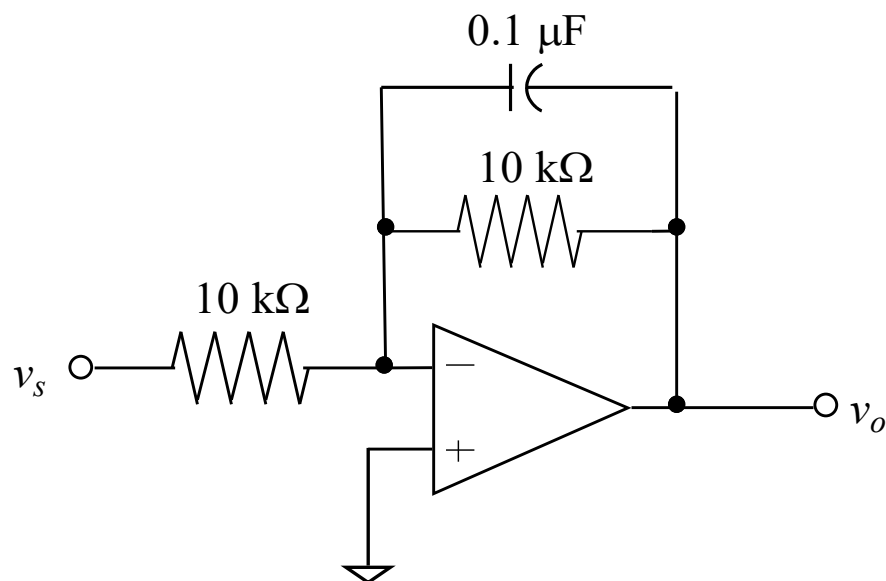Example: find v_o if $v_s(t) = 2 \cos 1000t$ V




$$v_o(t) = \sqrt{2} \cos(\omega t + 135^\circ) \text{ V}$$

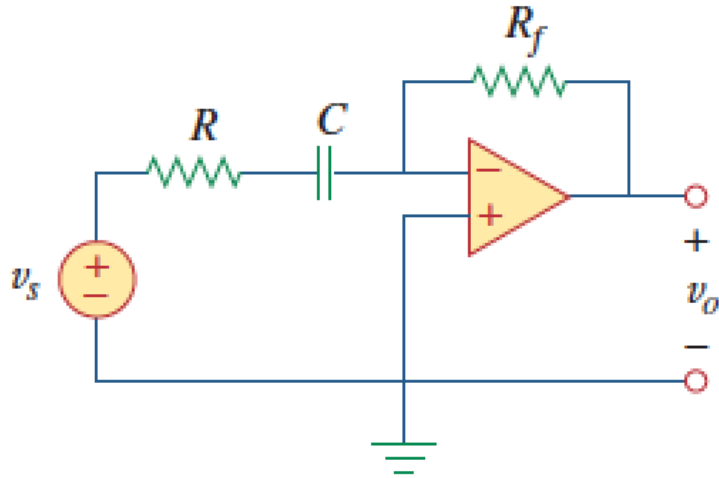Example: find v_o if $v_i(t) = A \cos \omega t$ V Is the result low pass, bandpass, or highpass?



$$v_o(t) = \frac{A\omega R_f C}{\sqrt{1+\omega^2 R_i^2 C^2}} \cos(\omega t + 180^\circ - \tan^{-1}(\omega R_i C)) \text{ V}$$


Practice problem: find v_o

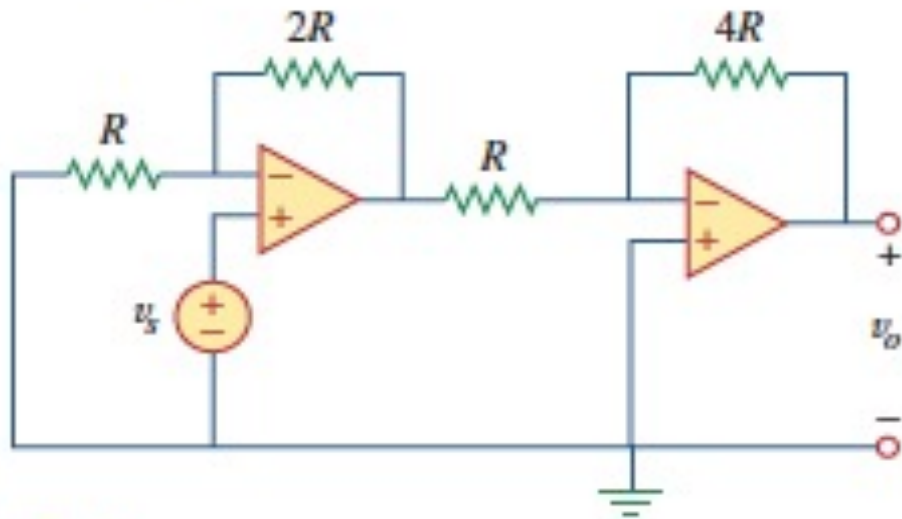

$$v_o = -12 v_s$$


$$v_o = 6(v_1 - v_2)$$

Practice problem: find v_o

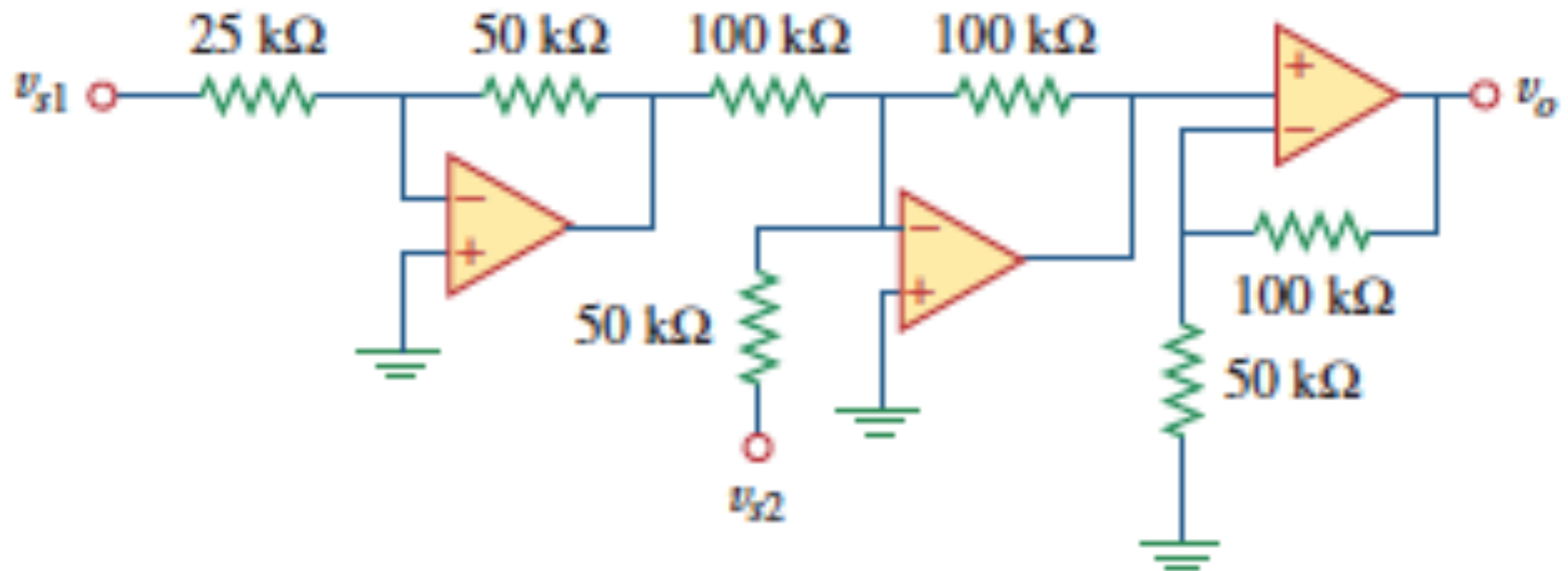


$$v_o = 21.6 \text{ mV}$$

Practice problem: find v_o

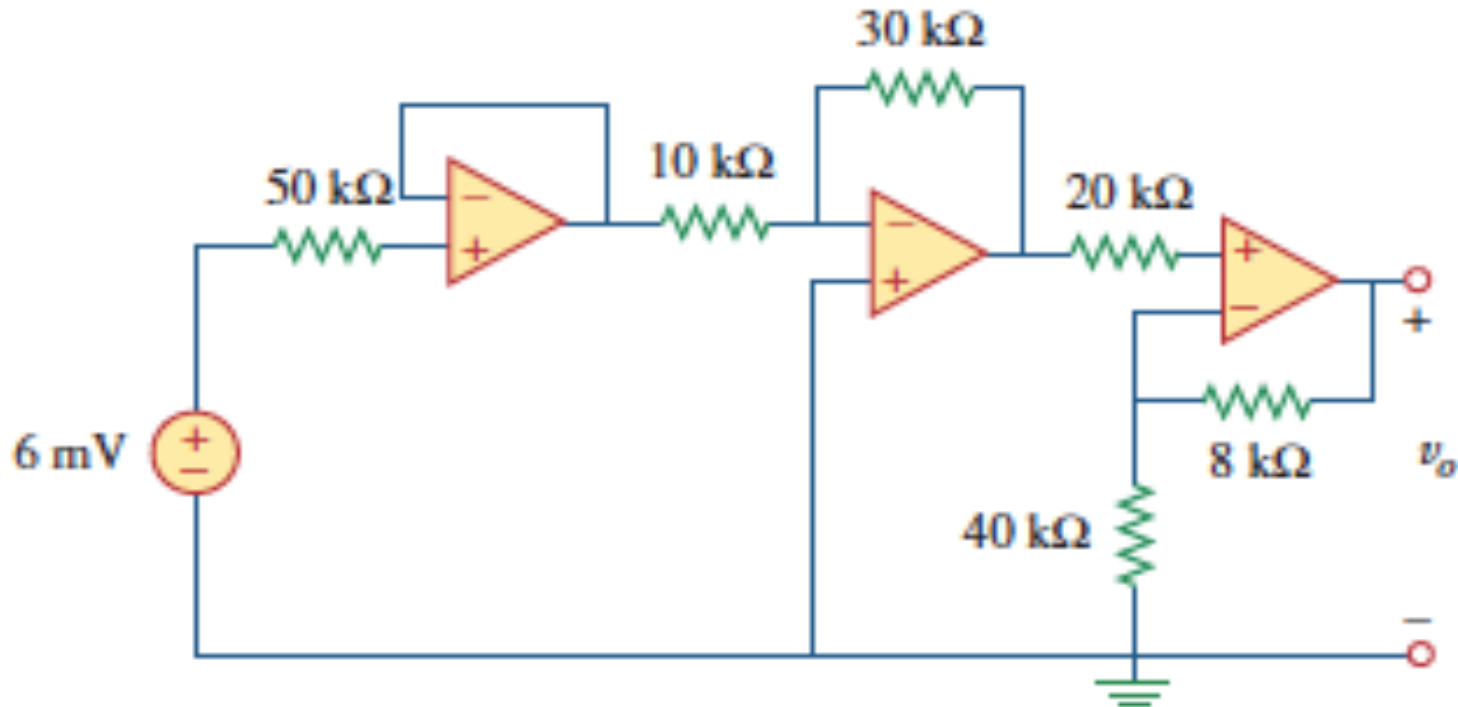


$$v_o = -0.4 V$$

Practice problem: find v_o

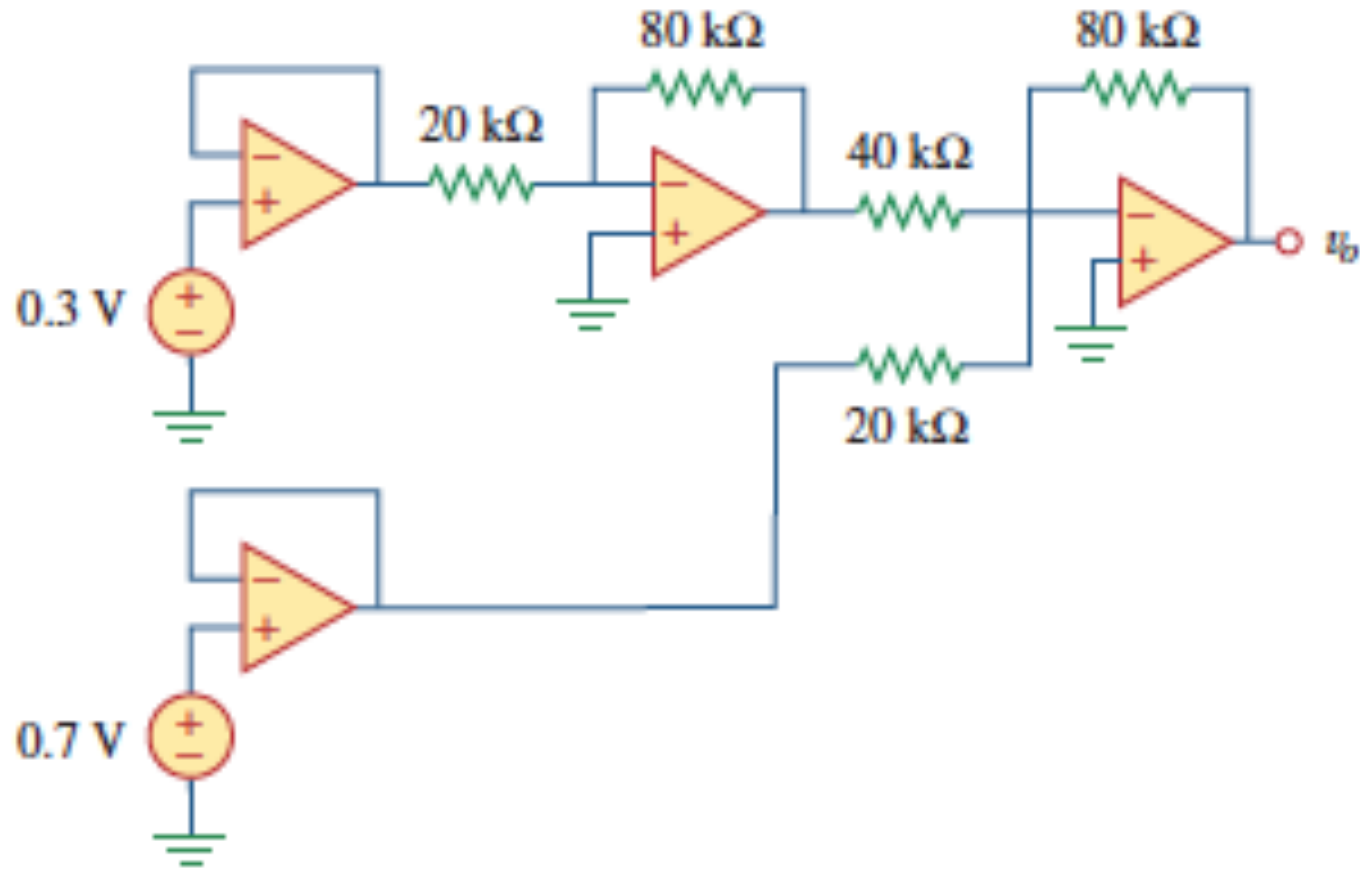


$$v_o = 21.8 V$$

Practice problem: find v_o

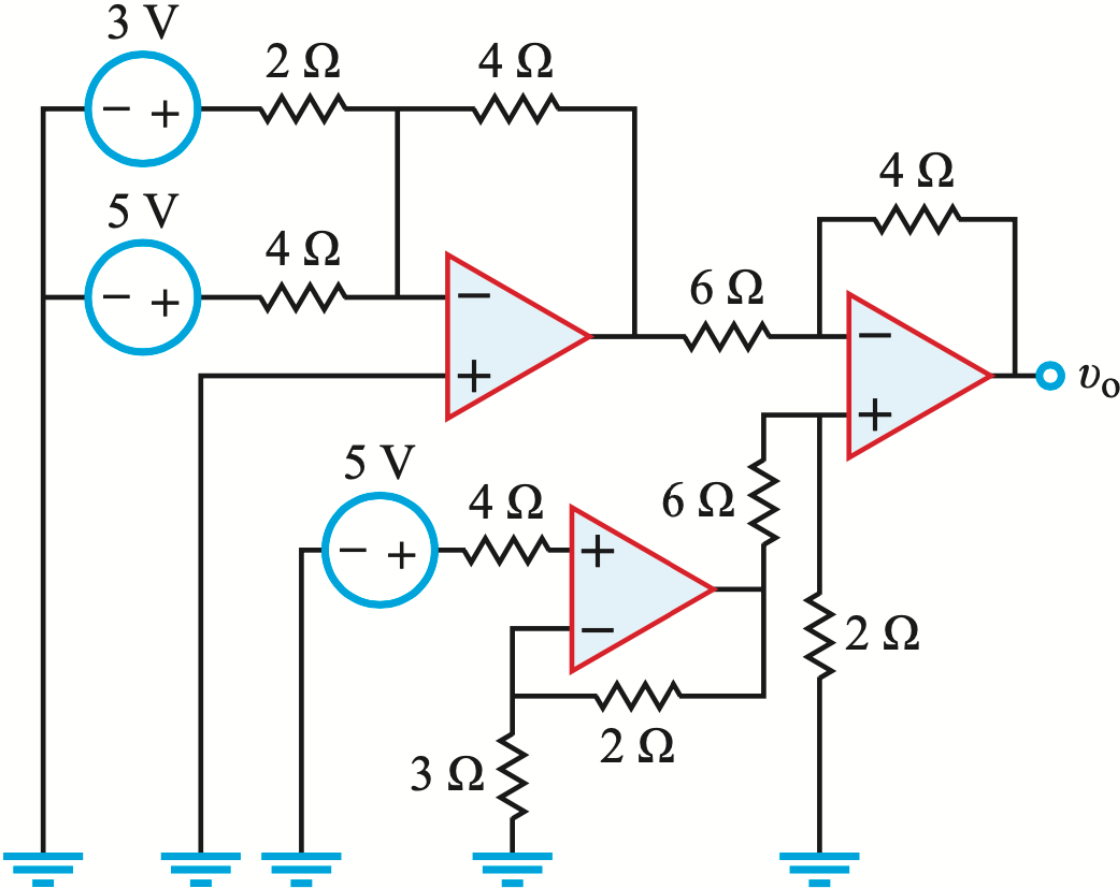


Practice problem: find $v_o(t)$

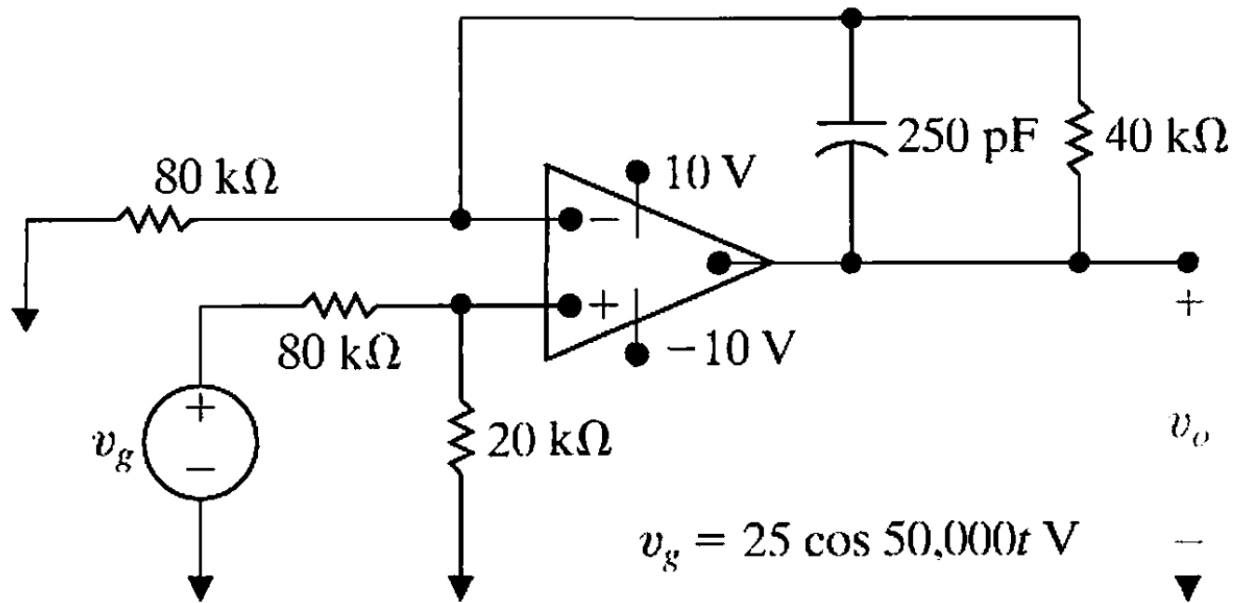

$$v_o(t) = 0.707 \cos(50,000t - 8.13^\circ)\text{ V}$$

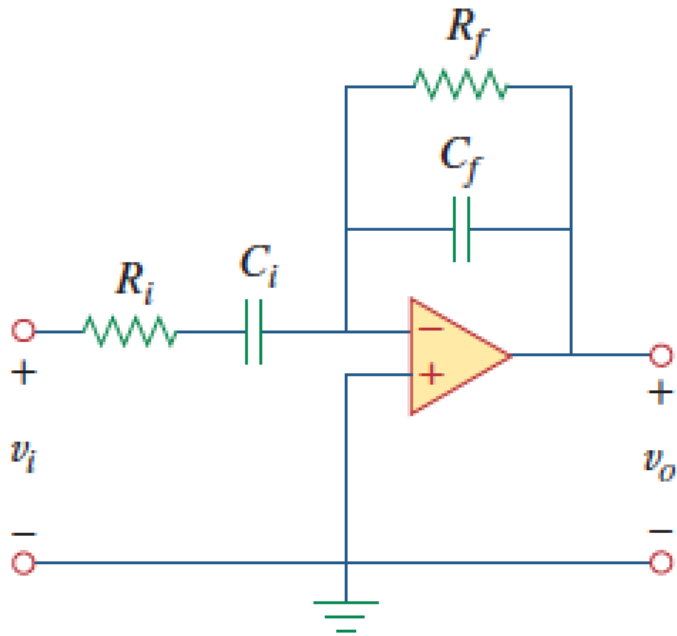
Practice problem: find v_o if $v_i(t) = A \cos \omega t$ V



$$v_o(t) = \frac{A\omega R_f C_i}{\sqrt{1+\omega^2 R_i^2 C_i^2} \sqrt{1+\omega^2 R_f^2 C_f^2}} \cos(\omega t + 270^\circ - \tan^{-1}(\omega R_i C_i) - \tan^{-1}(\omega R_f C_f)) \text{ V}$$

Practice problem:

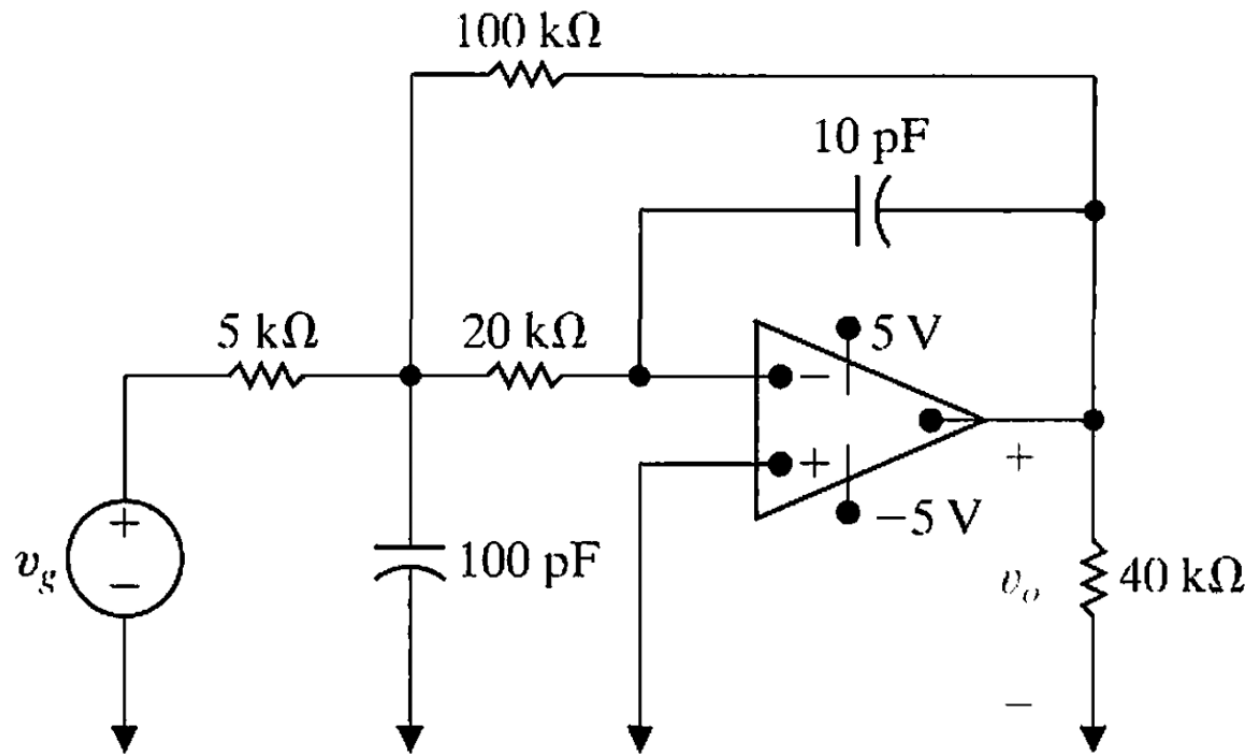2. Find the steady state output voltage (across the 40 k ohm resistor) if the source $v_g(t) = 2 \cos 10^6 t$ volts.



$$v_o(t) = 9.26 \cos(1,000,000t + 76.6^\circ) \text{ V}$$