

Theorems – 1


linearity & superposition;
transformations

Linearity & Superposition


- Linearity: for a single “input” (voltage or current), the “output” (voltage or current) is proportional to that input

$$v_o = k v_s$$

- What about multiple “input” sources?

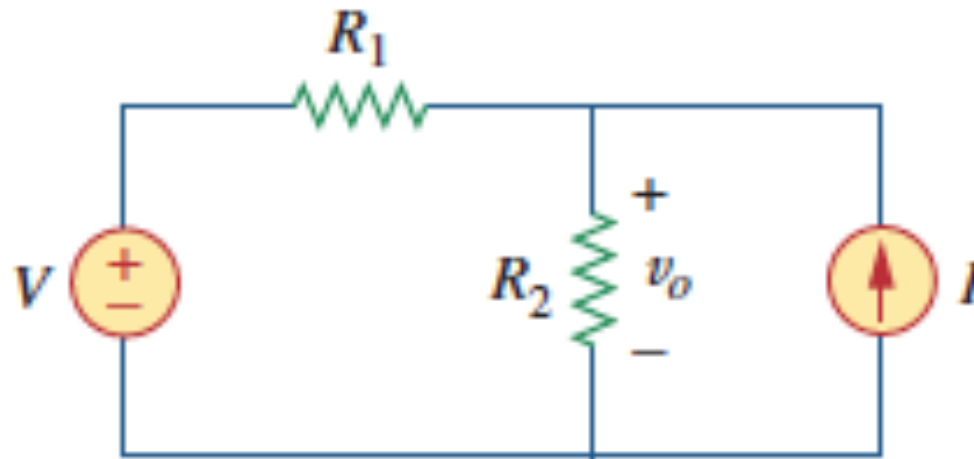

- Analyzing

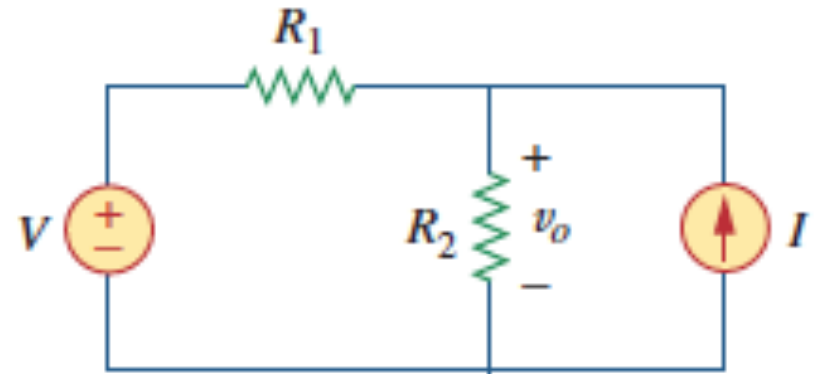

$$\frac{v_o - V}{R_1} + \frac{v_o}{R_2} - I = 0$$

or

$$v_o = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V$$

- And the idea extends to multiple “input” sources


$$v_o = k_1 v_{s1} + k_2 v_{s2}$$

“Superposition”

- We can exploit this idea to decompose problems:

– Example:

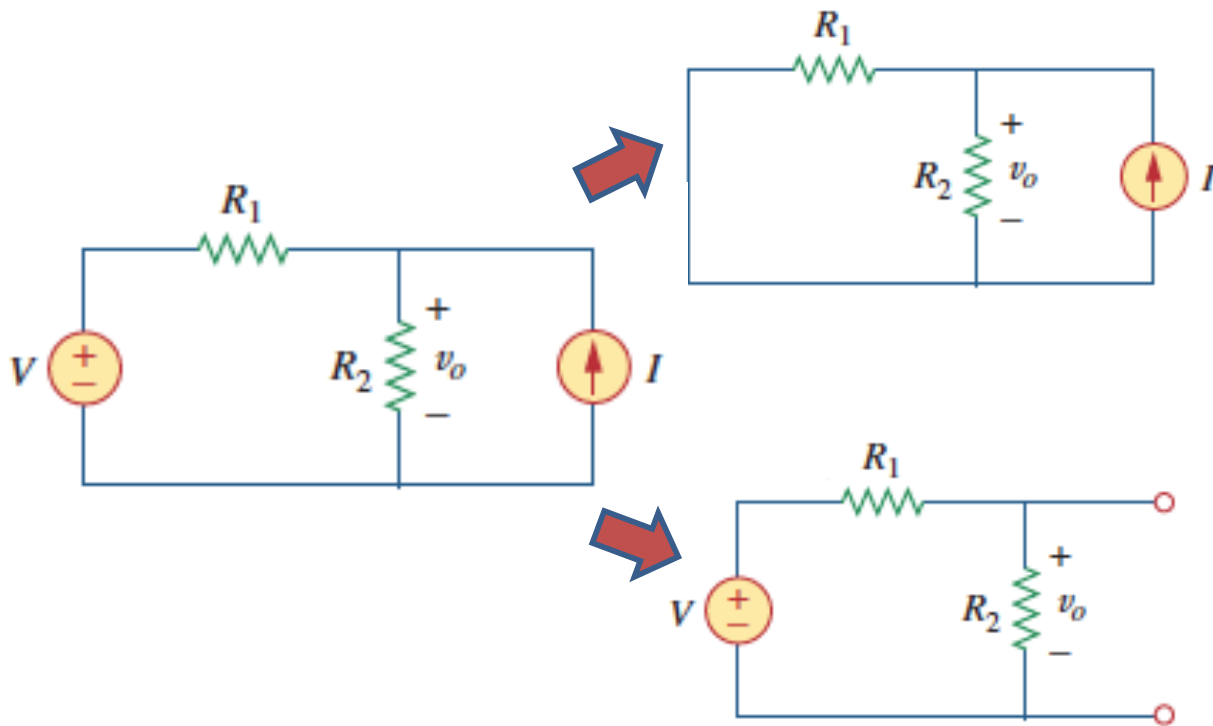
$$v_o(I, V) = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V = v_o(I, 0) + v_o(0, V)$$



$$v_o(I, 0) = \frac{R_1 R_2}{R_1 + R_2} I$$


$$v_o(0, V) = \frac{R_2}{R_1 + R_2} V$$

Example: find i

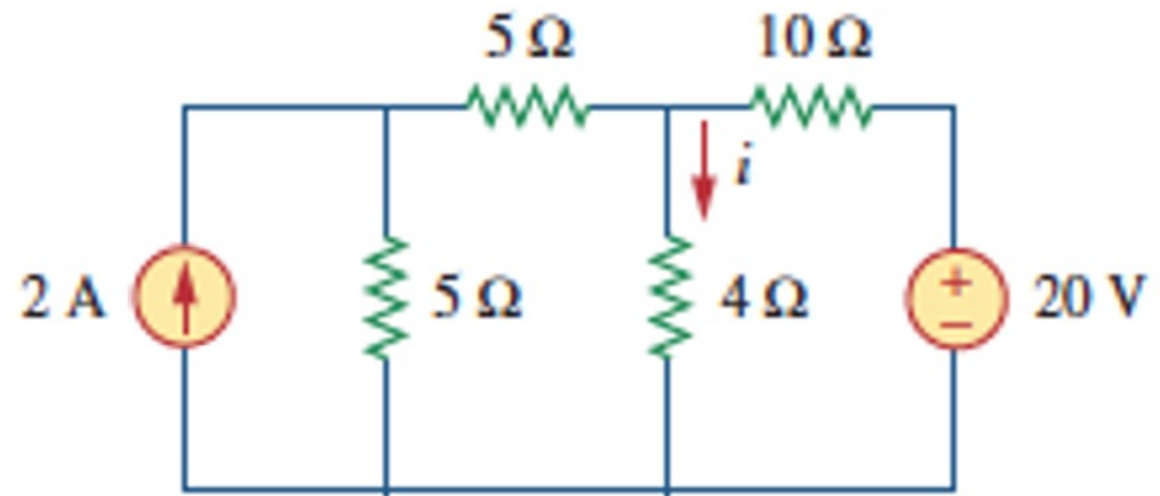


$$i = 1.67 \text{ A}$$

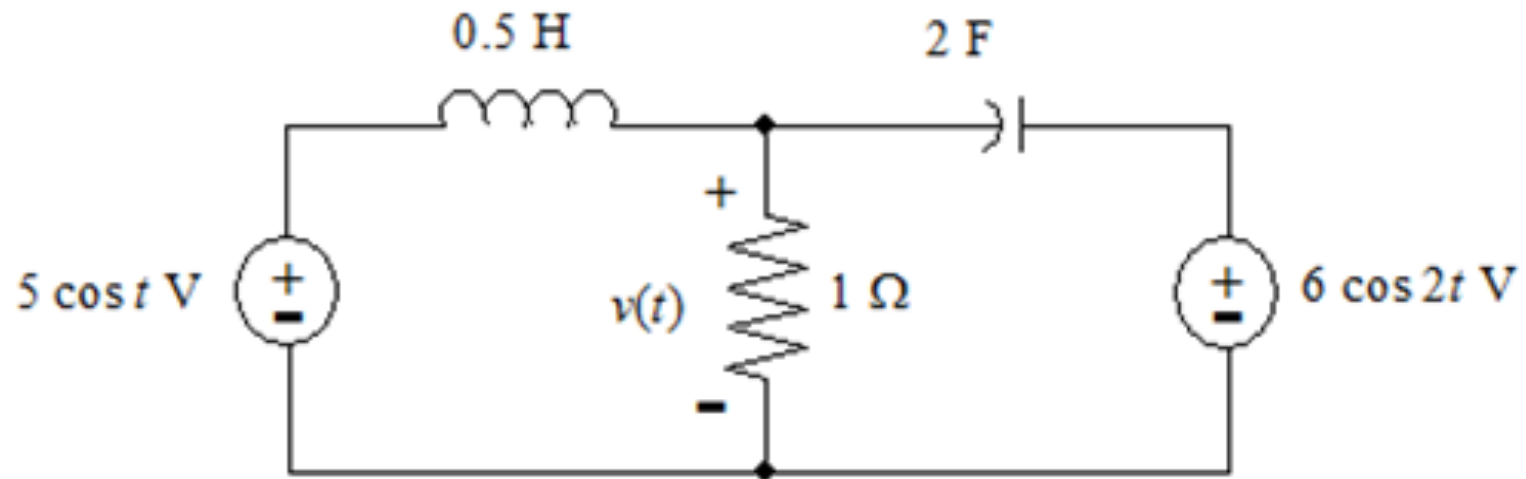Phasor example: note different frequencies




$$v(t) = 10 \cos(t - 90^\circ) + 1.2 \cos(2t + 127^\circ) \text{ V}$$


Source Transformations

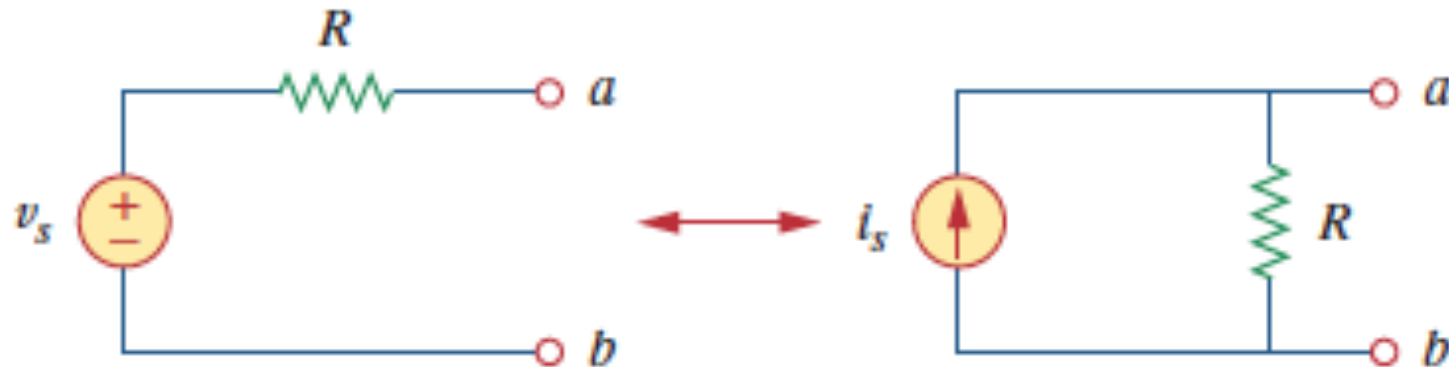

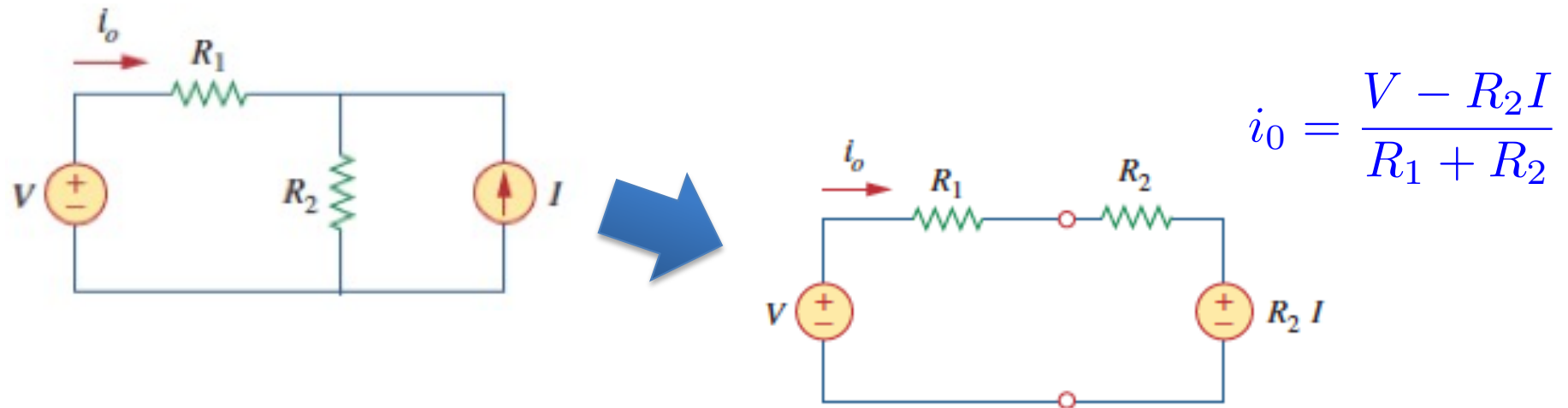- These two sub-circuits are equivalent *at the terminals a, b*
iff $v_s = R I_s$
- Utility: simplify circuit for quick analysis




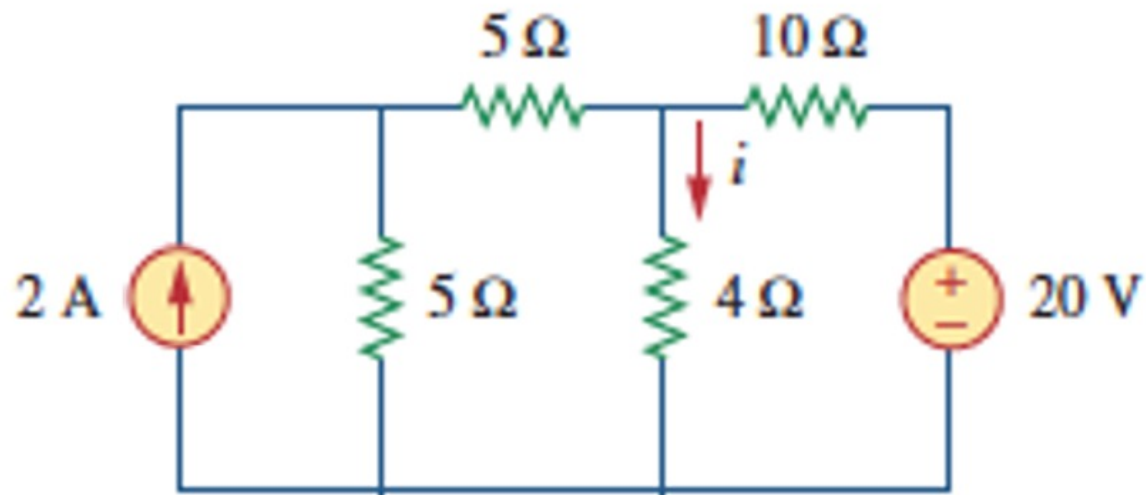Example: find i (convert to just one node)




1.67 A

Example: find $i_x(t)$

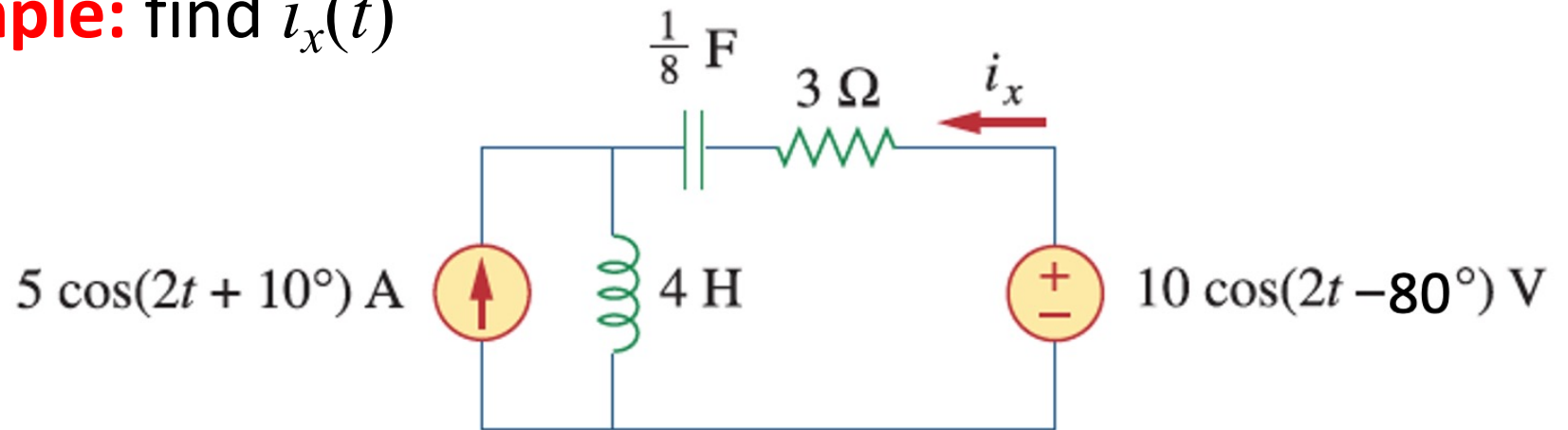


$$i_x(t) = 10 \cos(2t + 174^\circ) \text{ V}$$


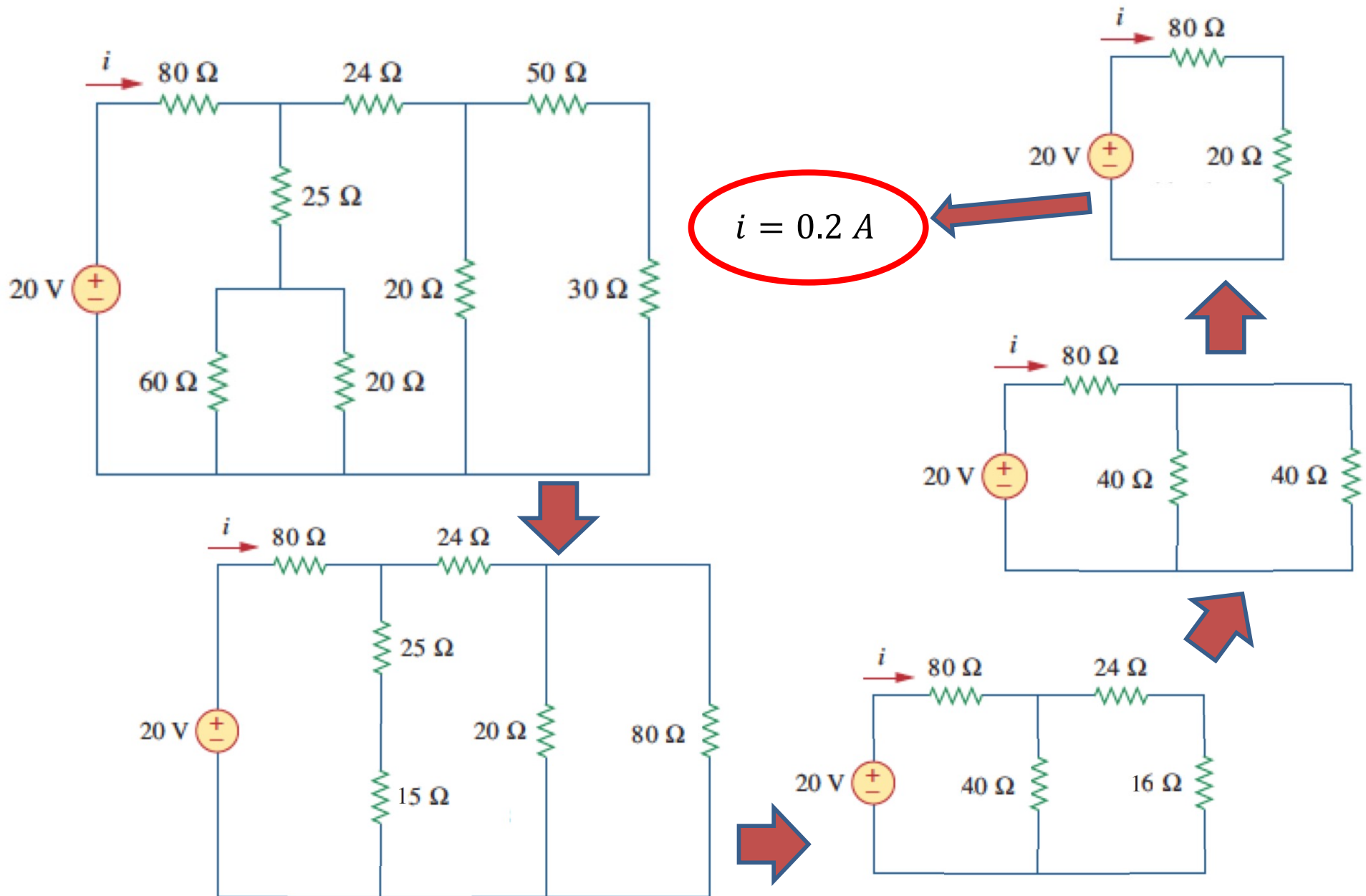
- To find i , recall series/parallel combining:








- What if there was a source present?

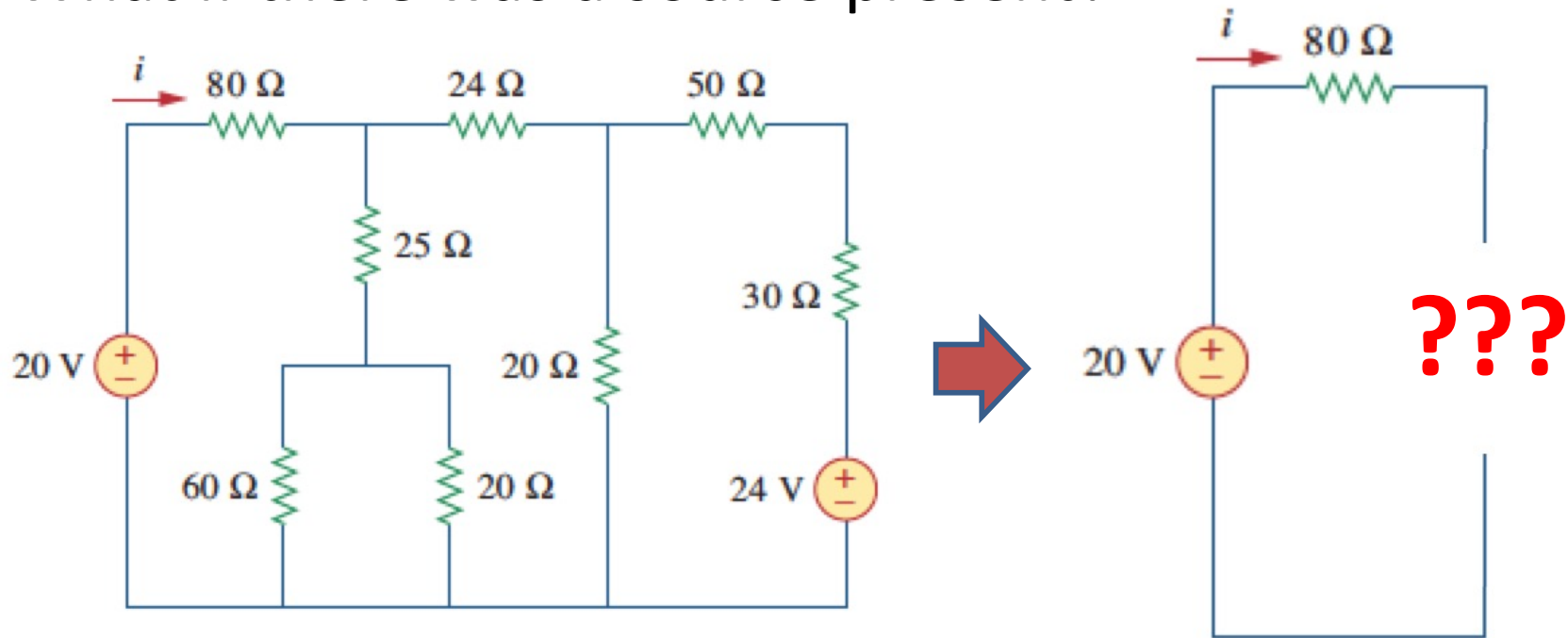


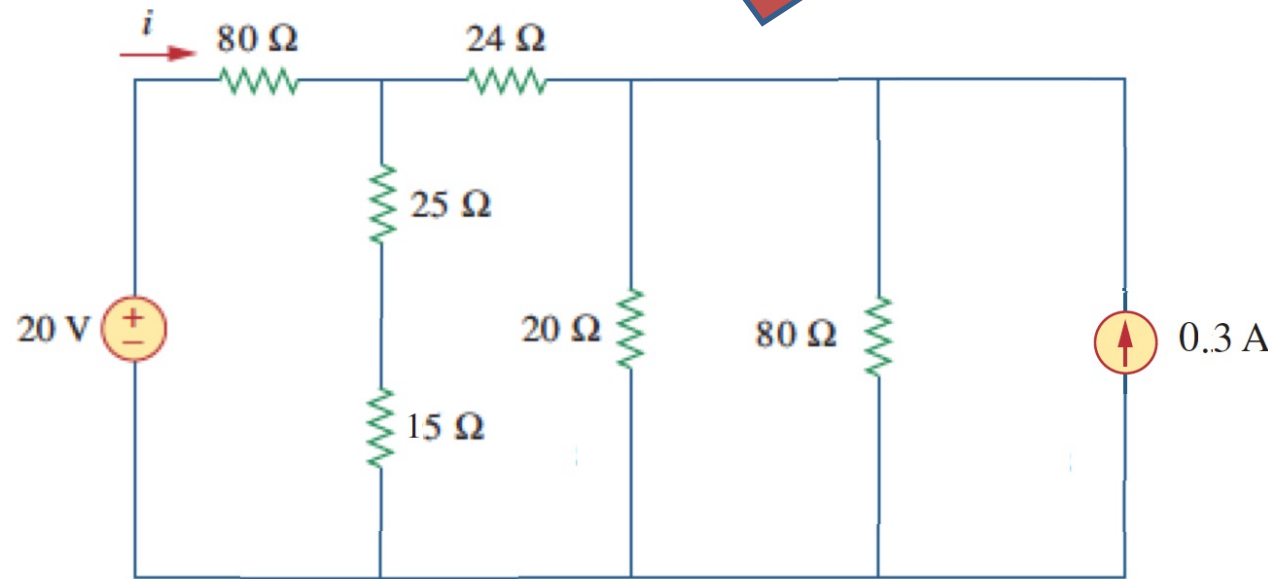
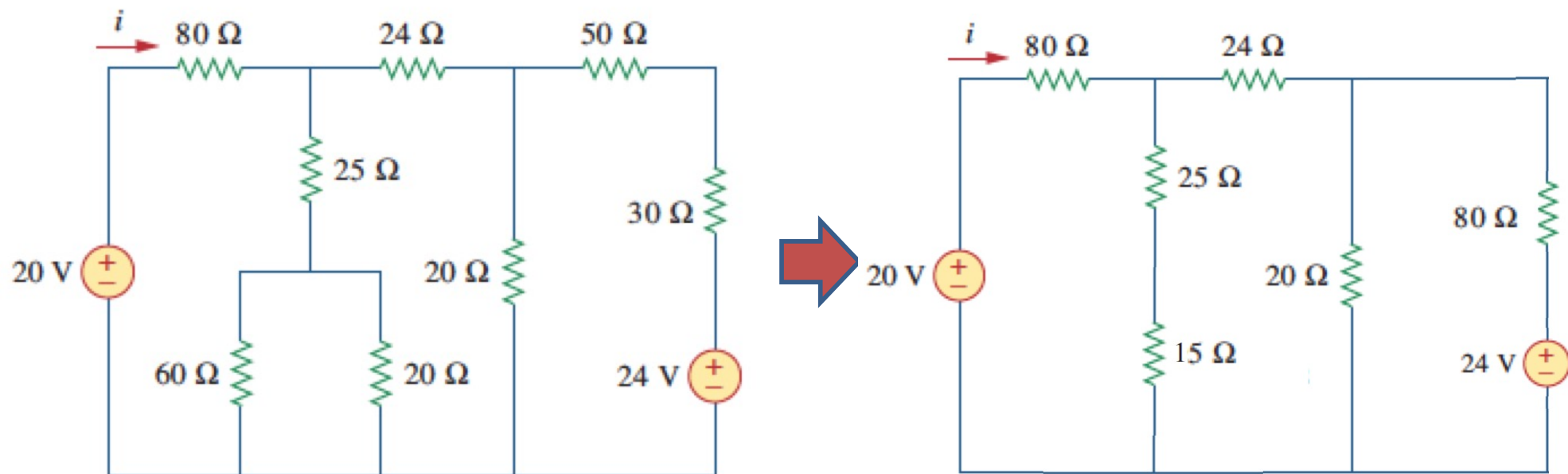
- Can combine transformations with series/parallel combining



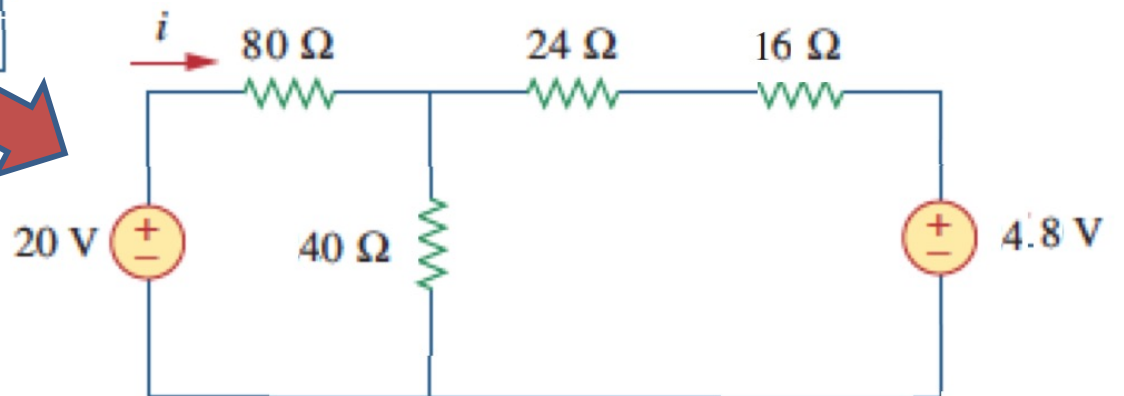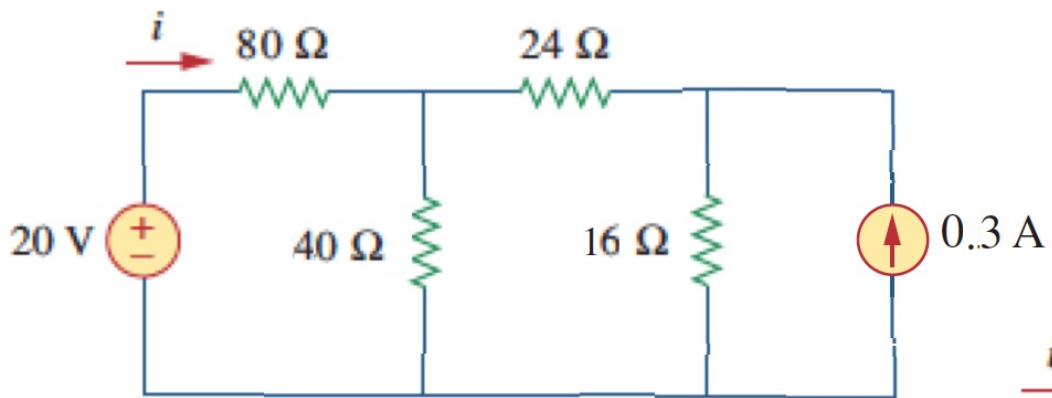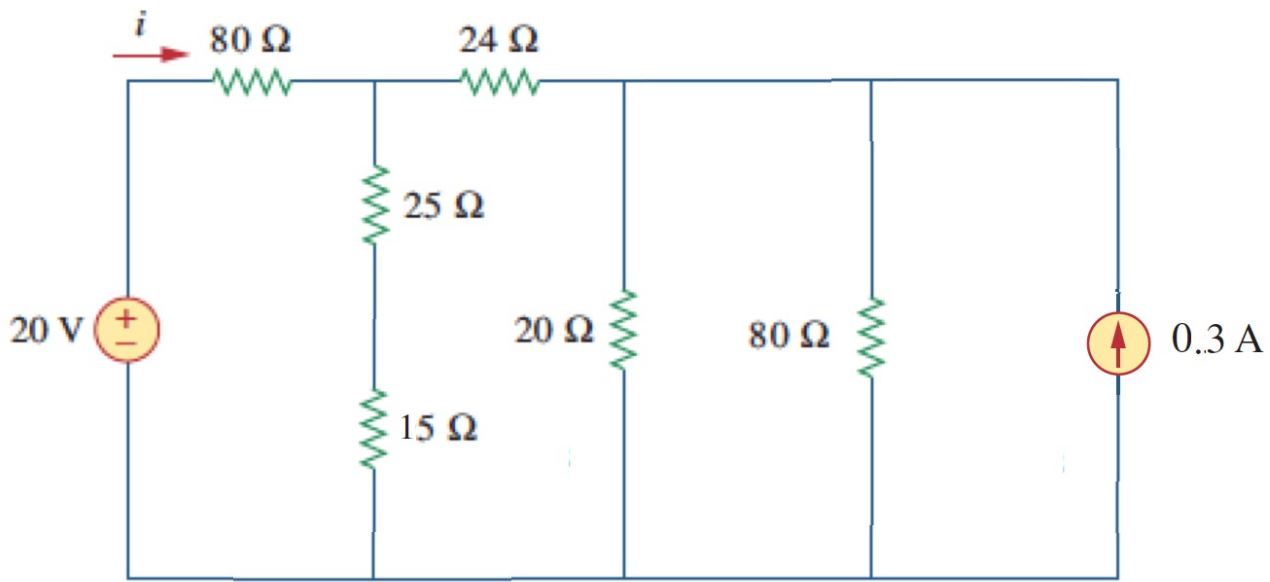


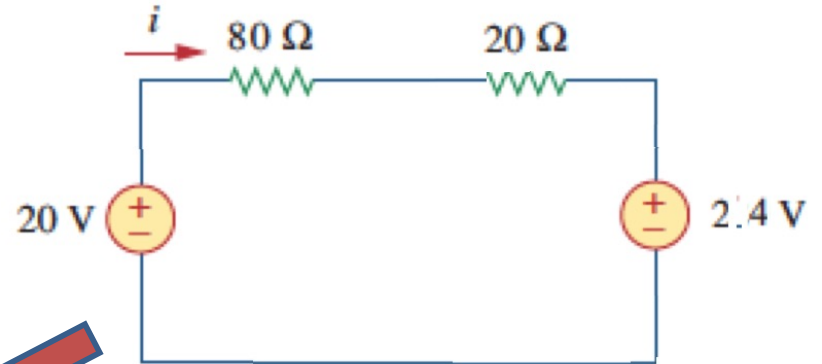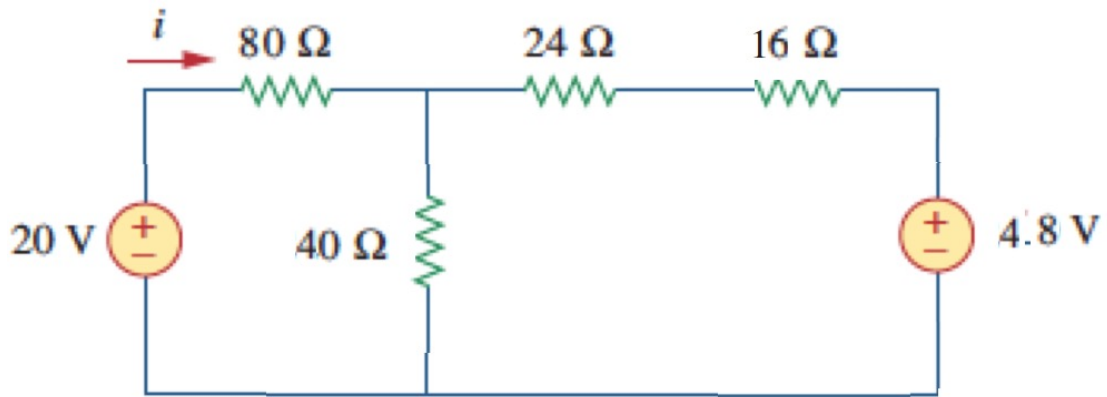

$i = 0.176\ \text{A}$

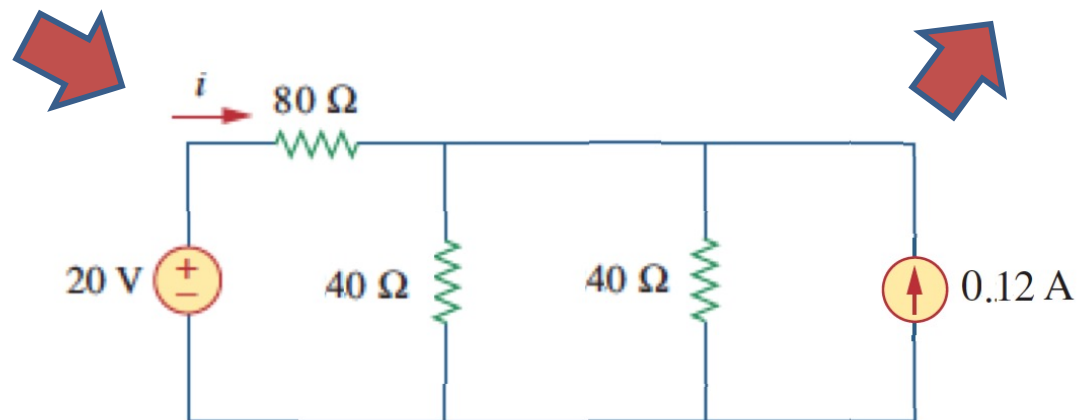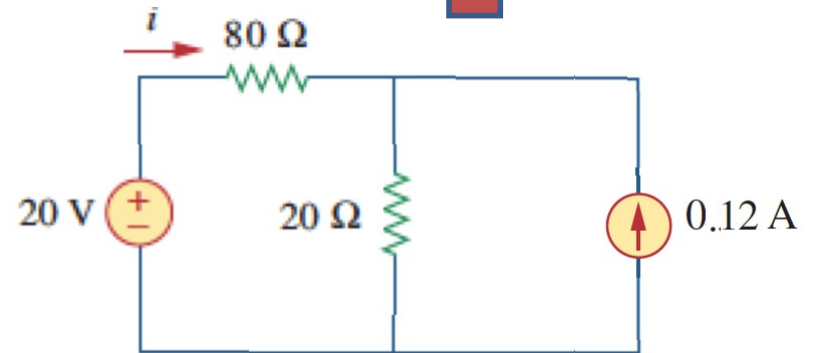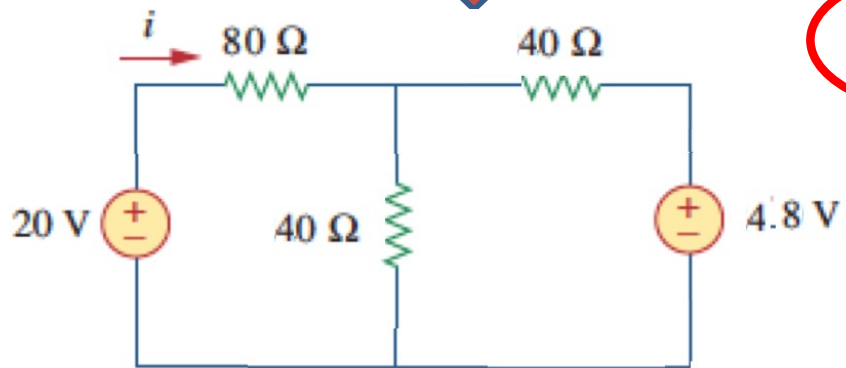


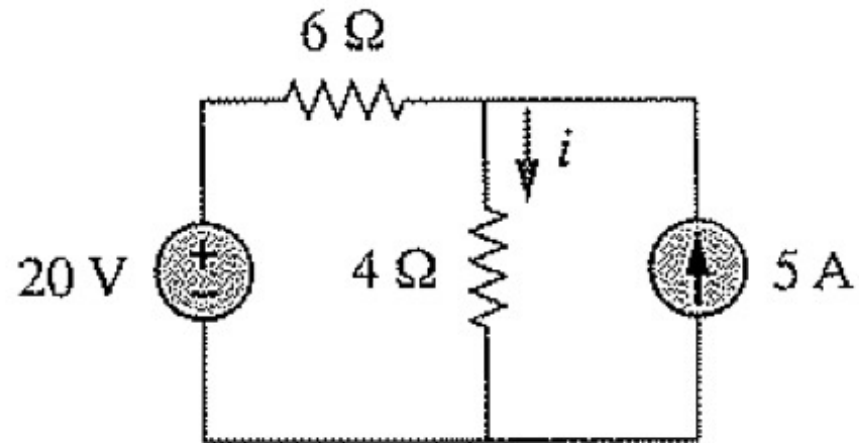Example: find i (convert to parallel current sources and then current division)




$$i = 5 A$$

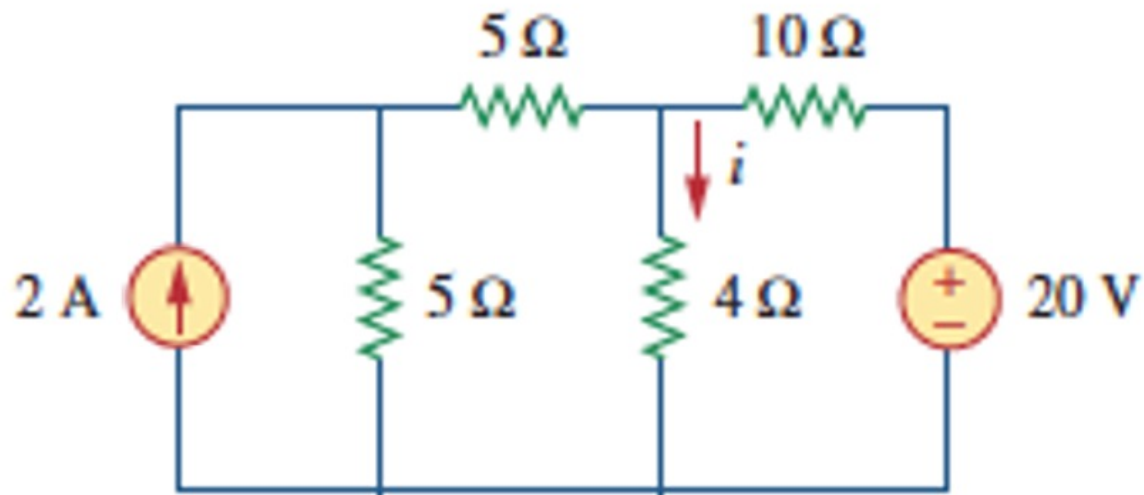Example from above: find i (use current division)




Example: find i_{Δ}

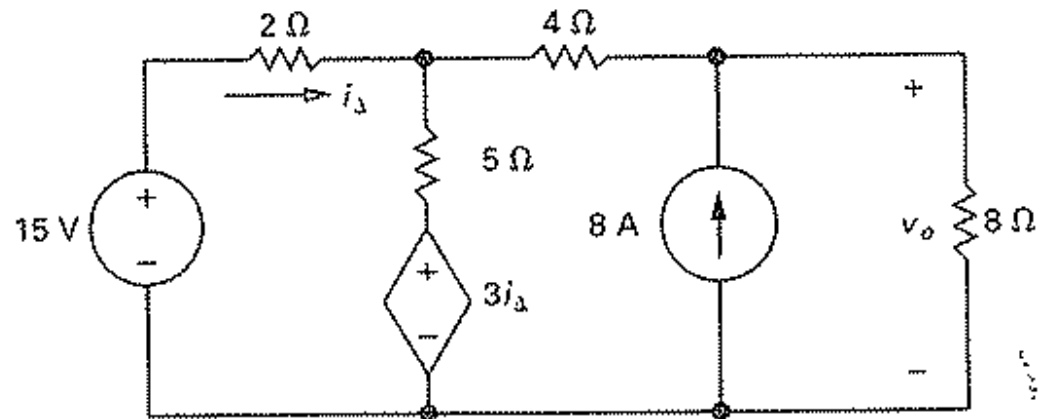

$$i_{\Delta} = \frac{223}{130} A$$


Example: find i

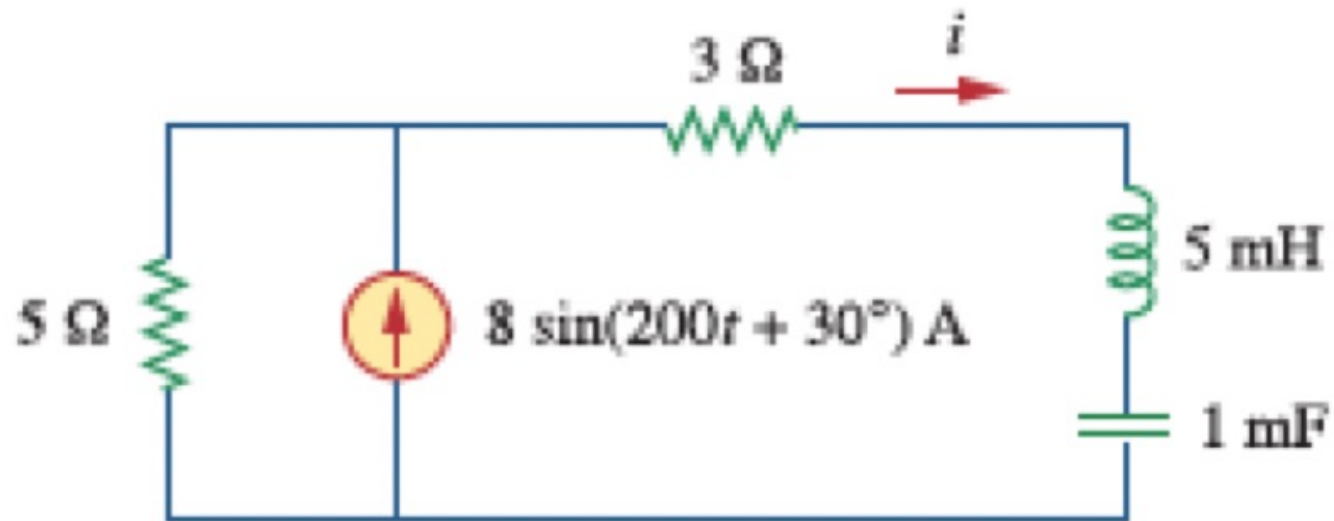

$$i(t) = 8.94 \cos(200t + 56.6^\circ) \text{ A}$$


Practice problem: find v_o and i_o

$$v_o = 8 V, \quad i_o = \frac{2}{3} A$$

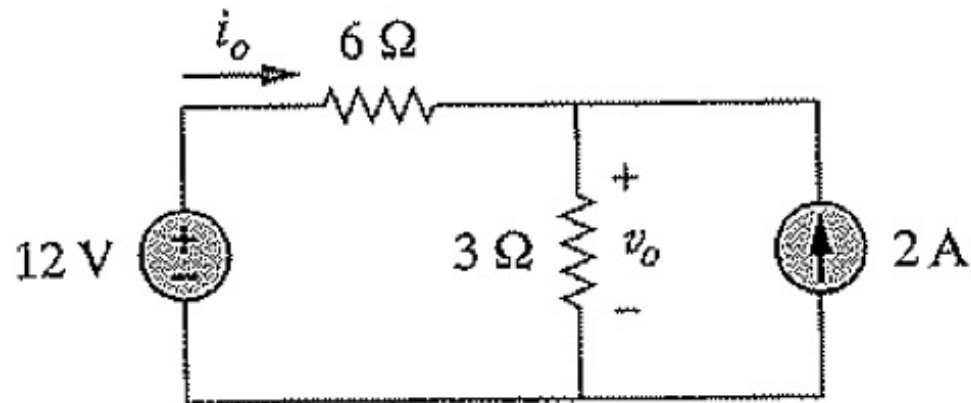


Practice problem: find i_o

$$i_o = \frac{14}{3} \text{ A}$$

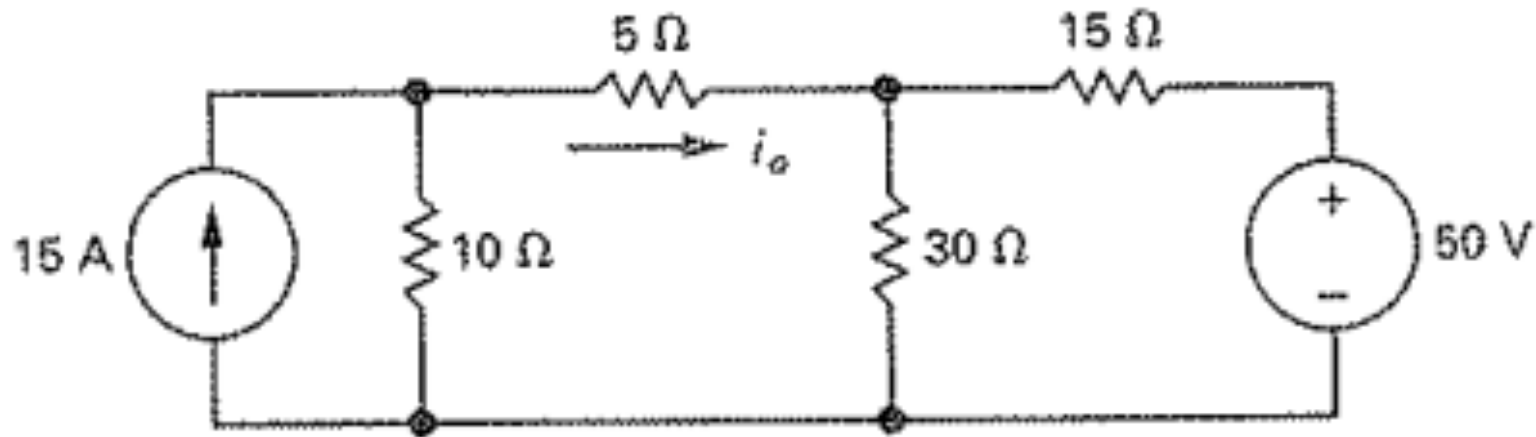


$$i_o = 1.79 \text{ A}$$

Practice problem: find i_o

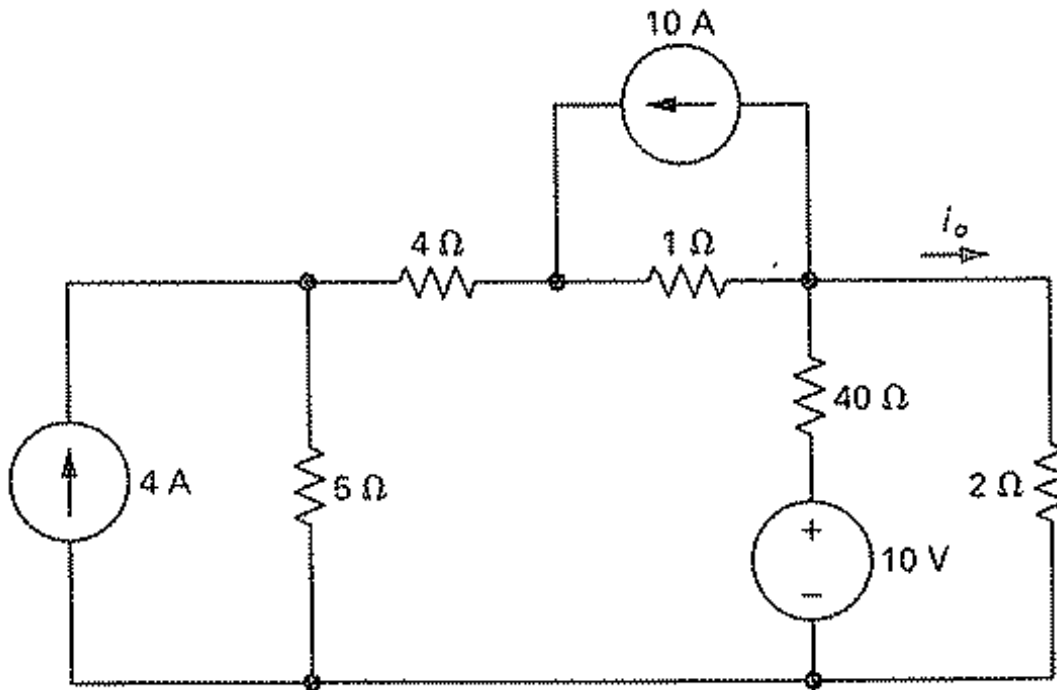

Practice problem: find v_o

$$v_o = -11 V$$

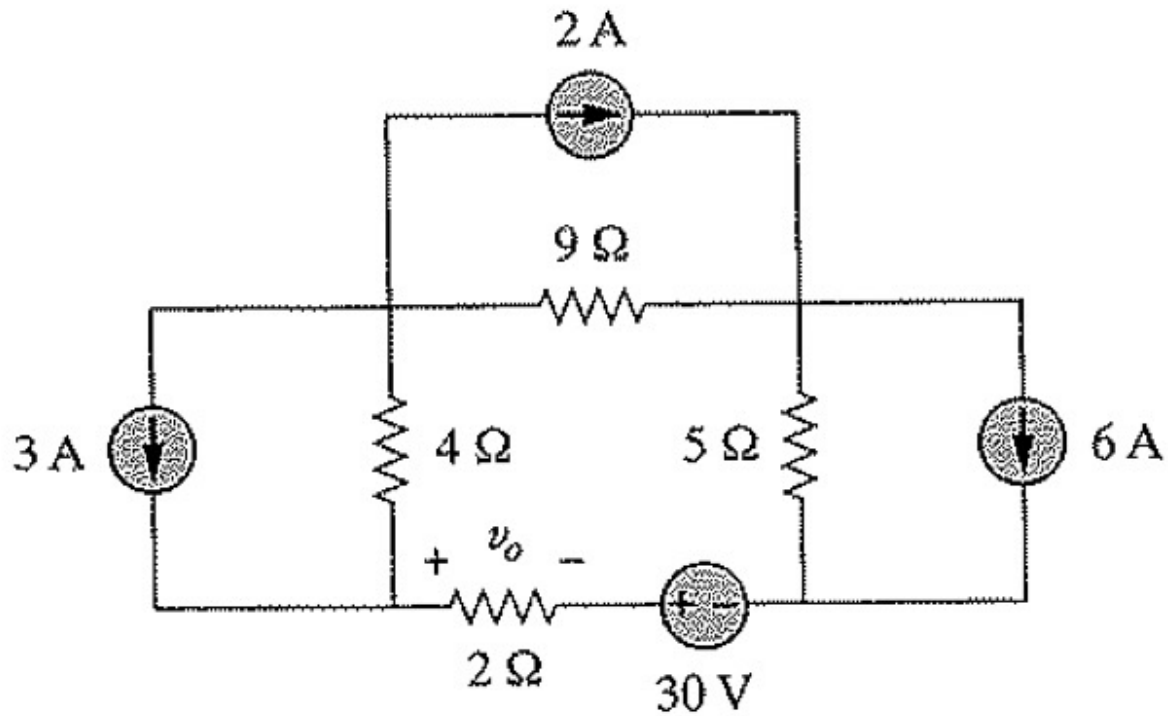

Practice problem: find v_x if
 $= v_s(t) = 50 \cos(2t + 90^\circ) \text{ V}$
and $i_s(t) = 12 \cos(2t + 10^\circ) \text{ A}$

$$v_x(t) = 129 \cos(2t + 28.76^\circ) \text{ V}$$

