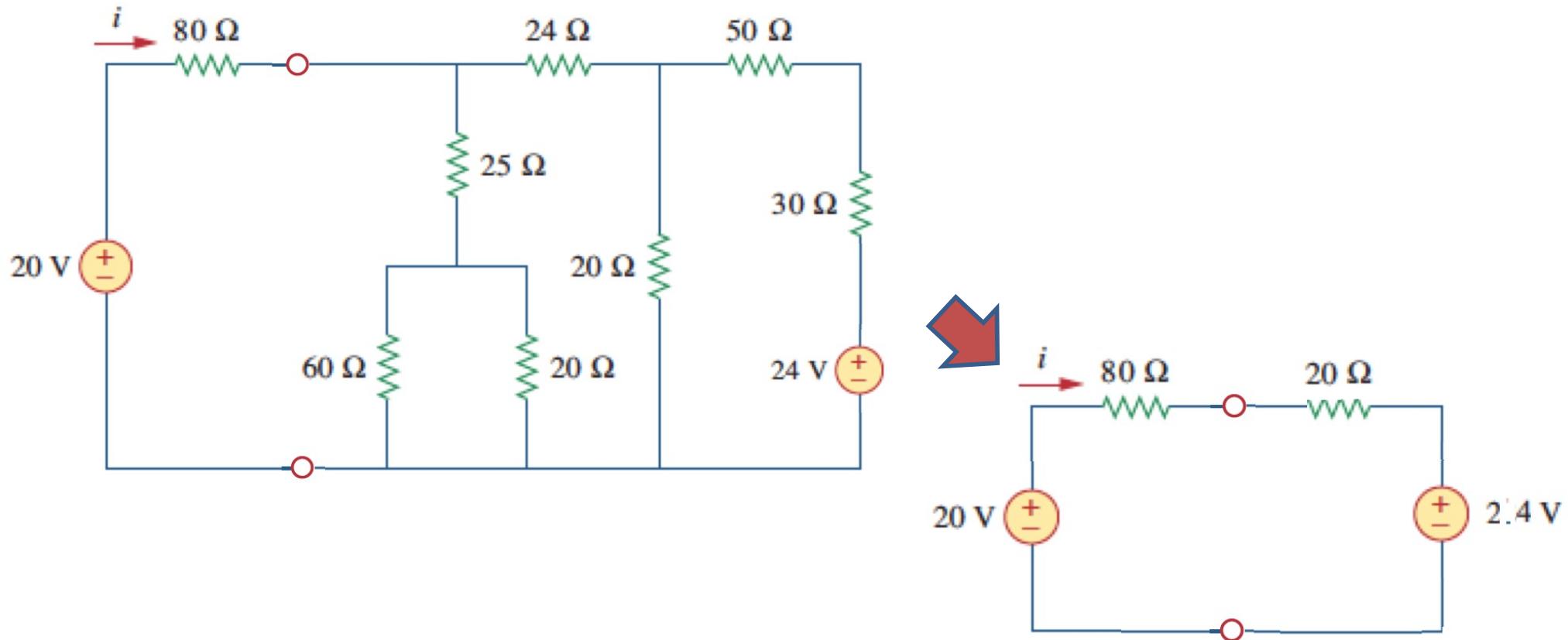


Theorems – 2

Thévenin

Thévenin Models


- Application – recall combining transformations and series/parallel methods from the last class:






Thévenin equivalent circuit \equiv electrical equivalence at any pair of terminals

- 2 parameters:

- V_{Th}
- R_{Th}


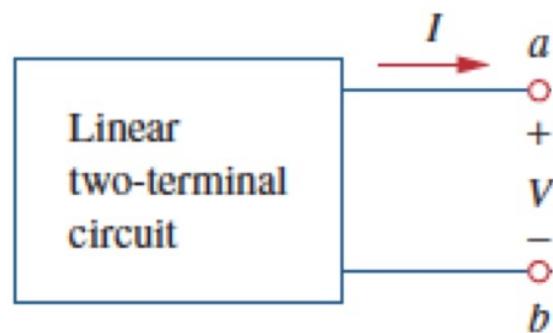


- Example:

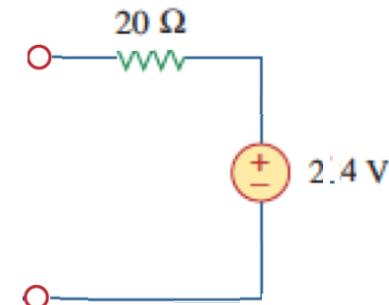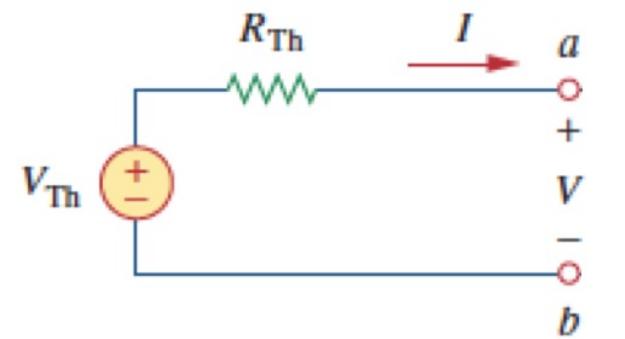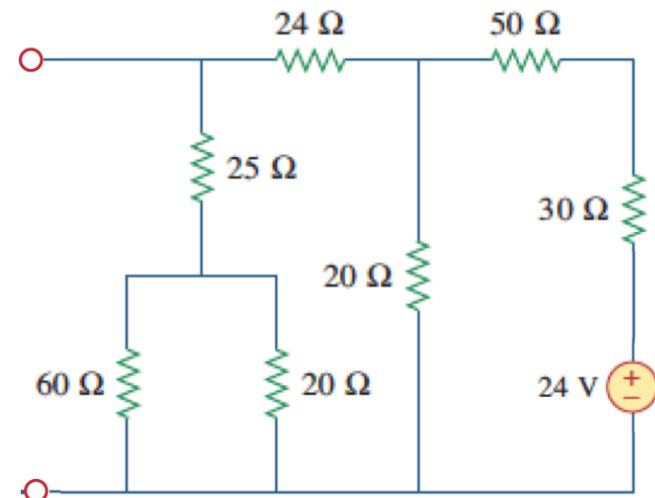


How to find V_{Th} and R_{Th} ?

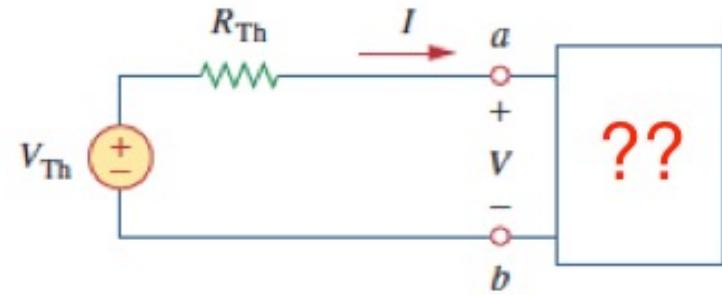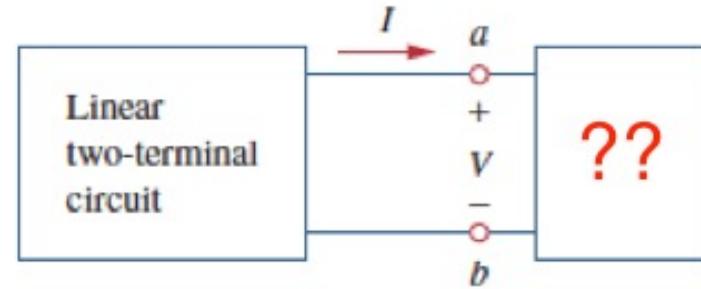- Concept: both the circuit and the model should behave the same way **no matter what** is connected at $a-b$
 - With only 2 variables in the model, we need only check **2** load situations
 - Need only match one of the V or I variables in each




Thevenin: Most Common Approach

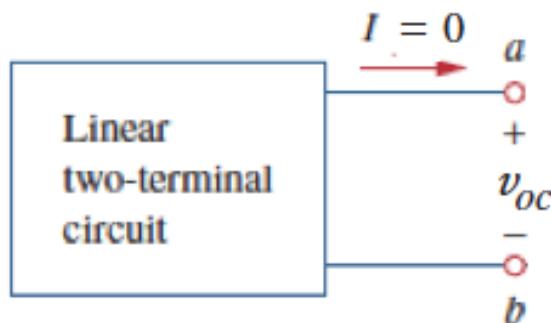- Connect nothing – “open circuit” test
 - Just need a voltmeter




Clearly

$$V_{Th} = V_{oc}$$

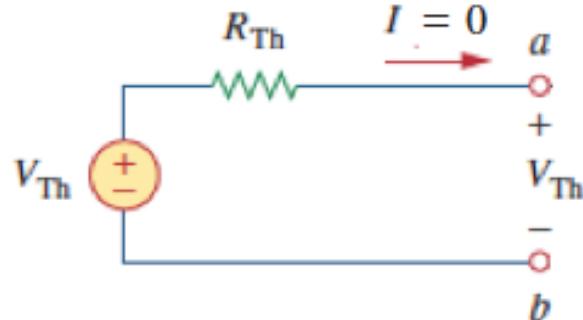


Another popular approach

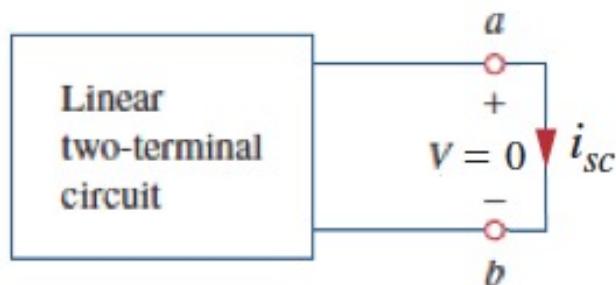- Connect a wire – “short circuit” test
 - Popular for paper analysis



$$i_{SC} = \frac{V_{Th}}{R_{Th}}$$


So

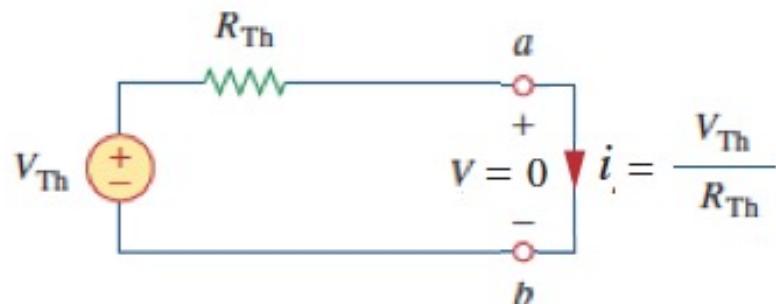

$$R_{Th} = \frac{V_{Th}}{i_{SC}} = \frac{V_{OC}}{i_{SC}}$$

Example:

- Use node analysis:

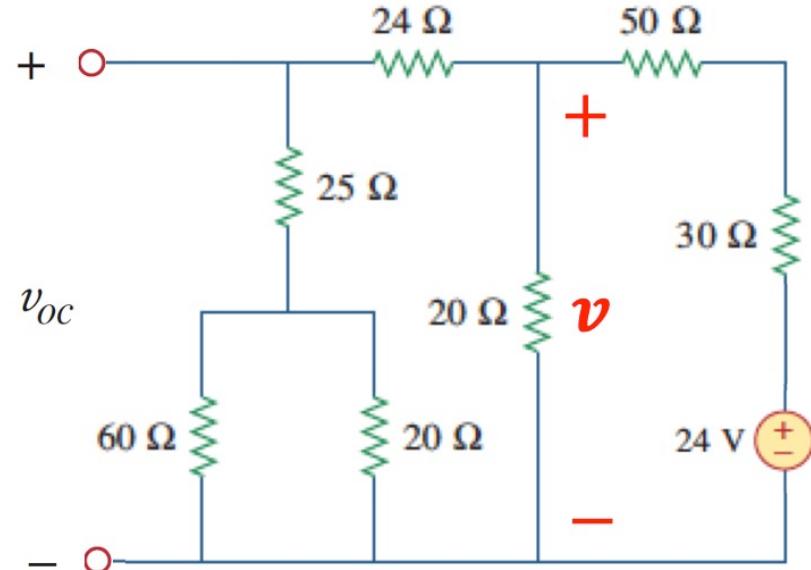


$$\frac{v}{20} + \frac{v - 24}{80} + \frac{v}{64} = 0 \quad \Rightarrow \quad v = \frac{96}{25}$$

- Then voltage division:

$$v_{oc} = \frac{40}{64}v \quad \Rightarrow \quad V_{Th} = v_{oc} = 2.4 \text{ volts}$$

Note how the short changes the circuit

- Use node analysis:

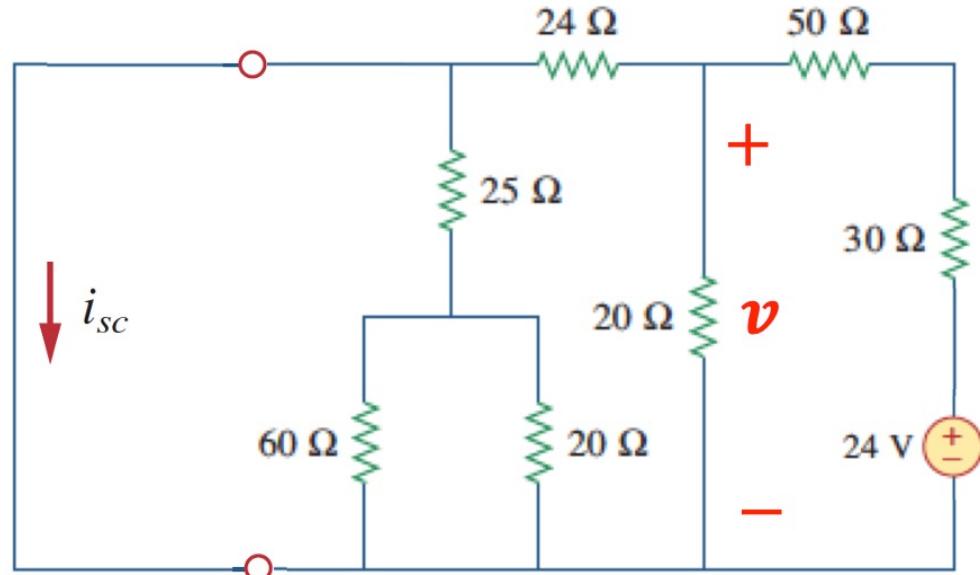


$$\frac{v}{20} + \frac{v - 24}{80} + \frac{v}{24} = 0 \Rightarrow v = \frac{72}{25}$$


- Then Ohm's Law:

$$i_{sc} = \frac{v}{24} = 0.12 \Rightarrow R_{Th} = \frac{v_{oc}}{i_{sc}} = \frac{2.4}{0.12} = 20 \Omega$$

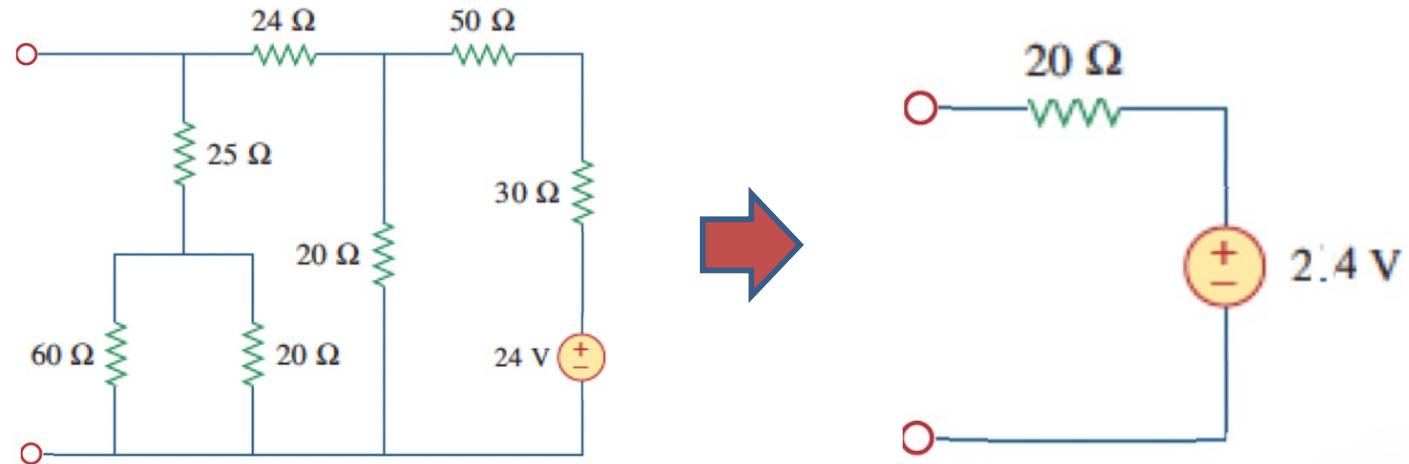So $V_{Th} = 2.4$ volts and $R_{Th} = 20 \Omega$





and

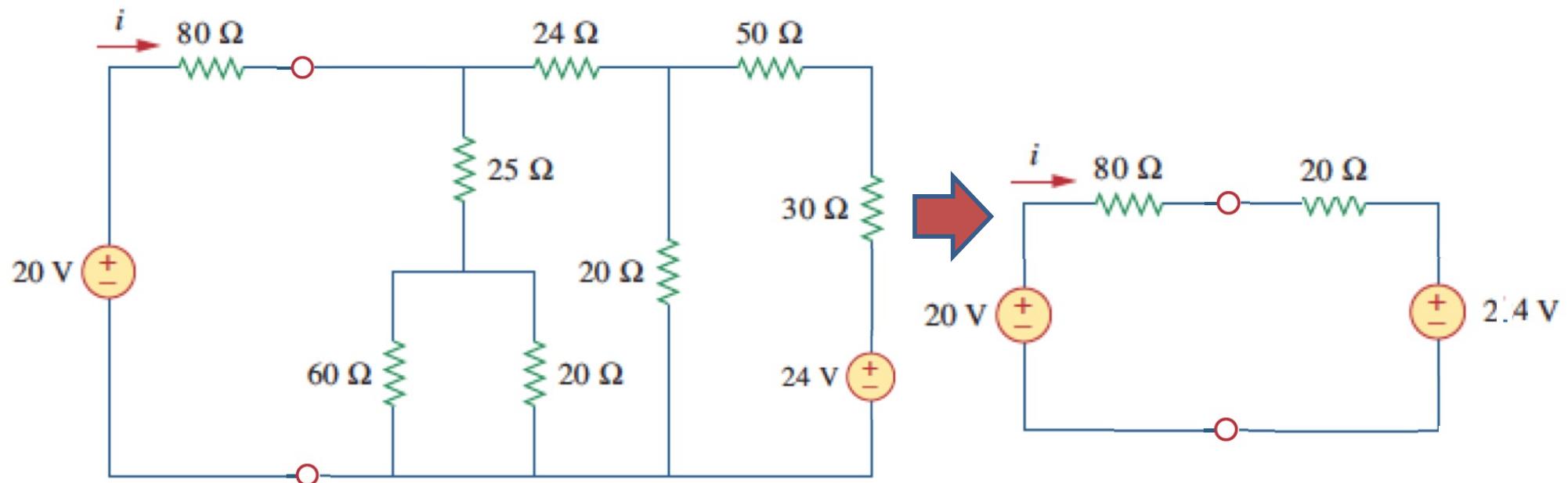

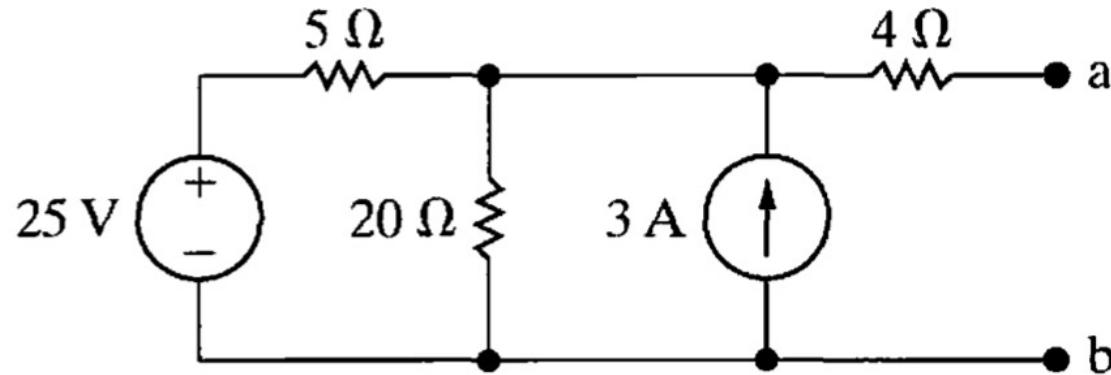Example: find V_{th} and R_{Th}

$$V_{Th} = v_{OC}$$
$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$




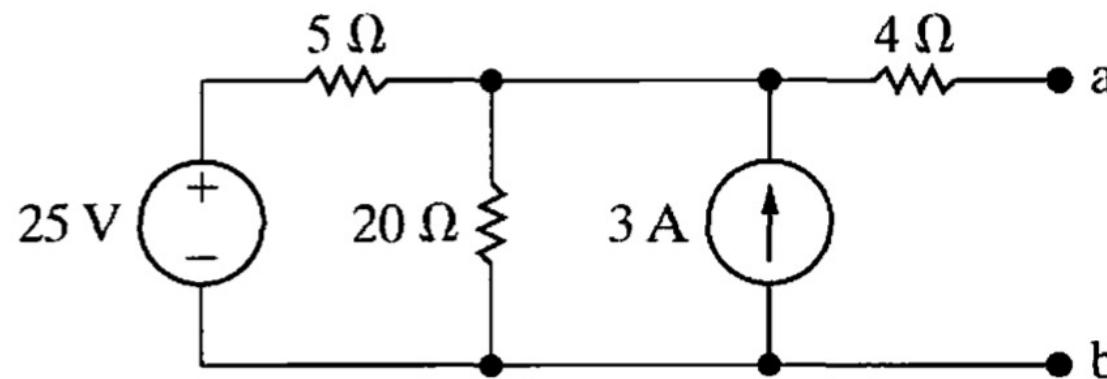


32 V, 8Ω

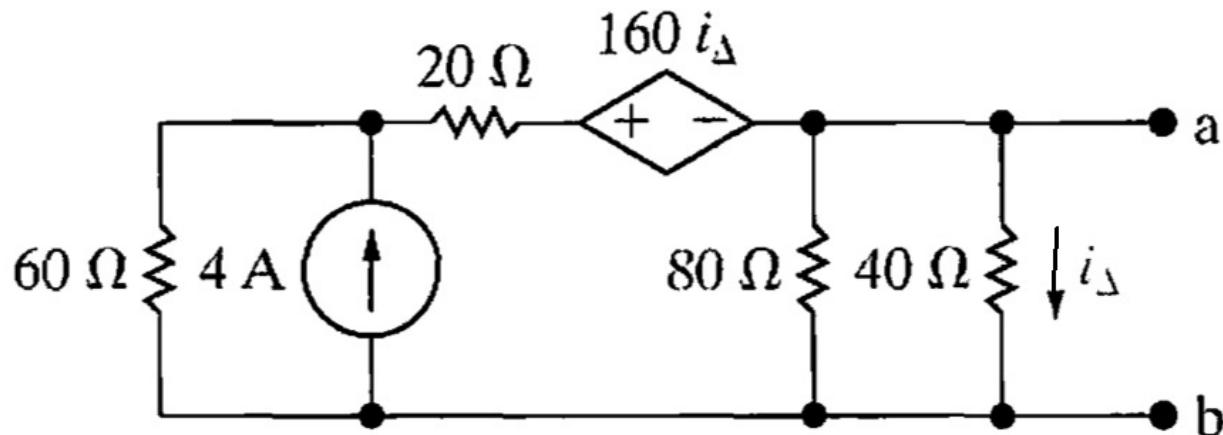Example: find V_{th} and R_{Th}


$$V_{Th} = v_{OC}$$
$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$




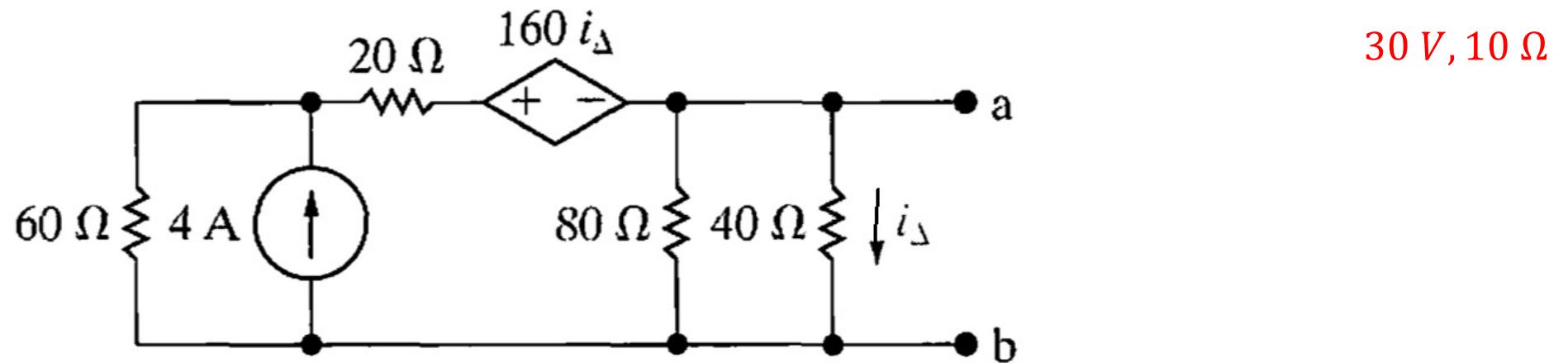

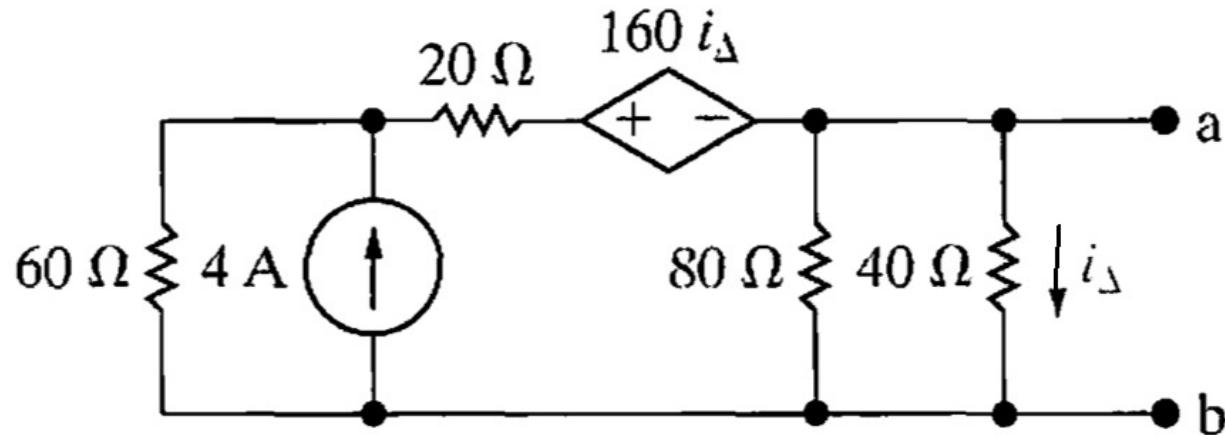Example: find V_{th} and R_{Th}


$$V_{Th} = v_{OC}$$
$$R_{Th} = \frac{v_{OC}}{i_{SC}}$$



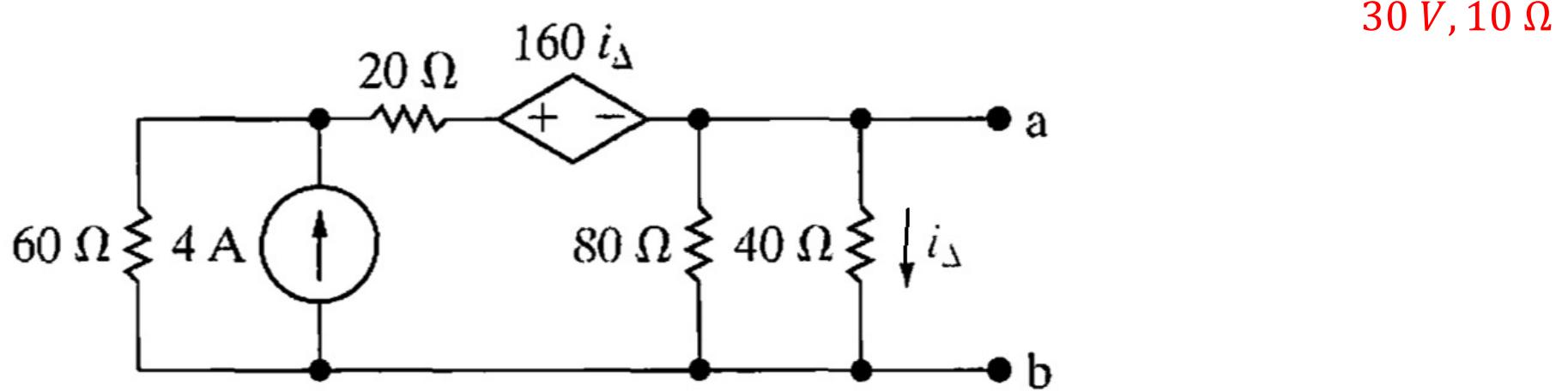


$$\frac{9}{4} V, 30 \Omega$$

Practice problem: find V_{th} and R_{Th}

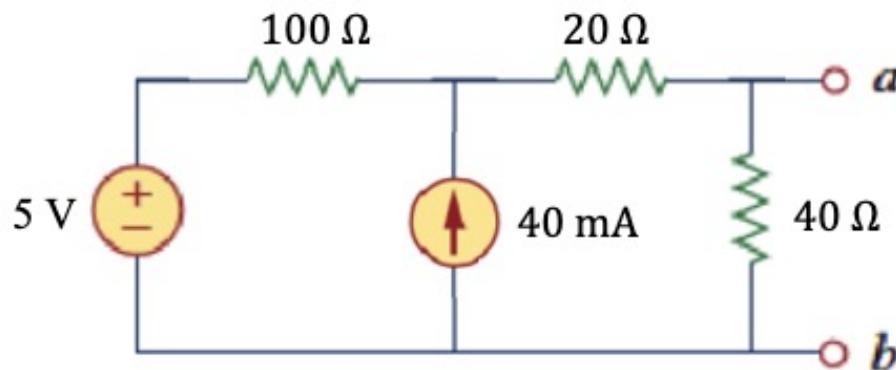


Practice problem: find V_{th} and R_{Th}

23.0 V, 44.6 Ω

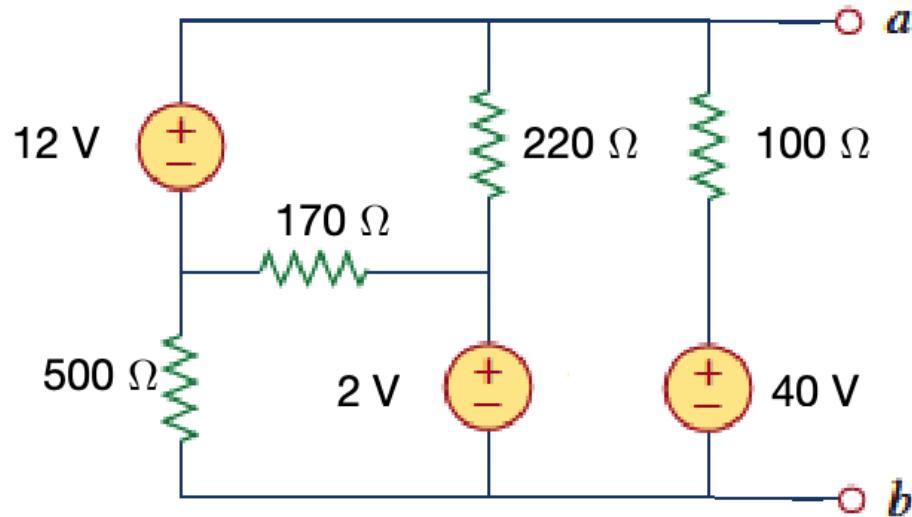

Practice problem: find V_{th} and R_{Th}

200 V, 14,3 k Ω

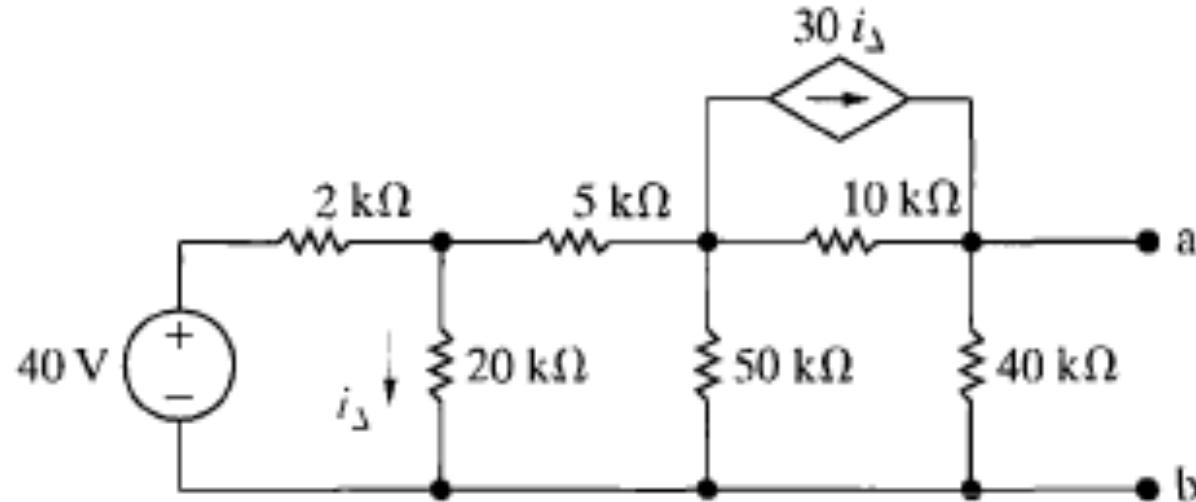

Practice problem: find V_{th} and R_{Th}

$$\frac{500}{3} V, 10 \Omega$$

