
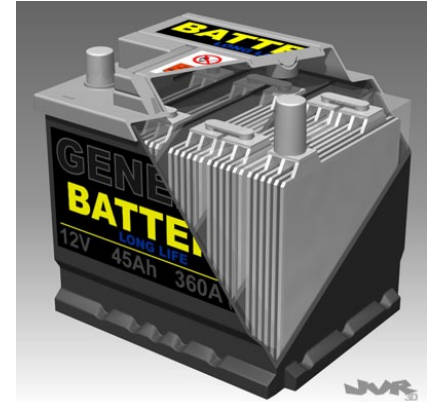


# Theorems – 3

more Thevenin; Norton
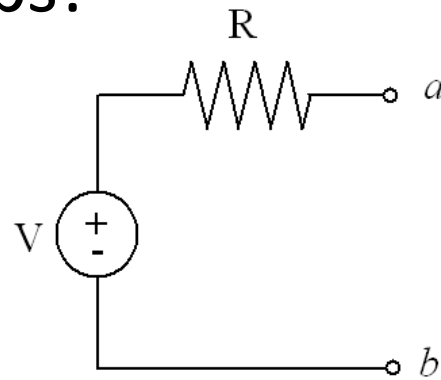
# Everyday Example

- Car battery – 12.6 volts
- Can provide 100-200 amps!
- Thévenin model:
  - 12.6 volt source
  - 0.05-0.2  $\Omega$  resistance



- “Dead” when resistance increases (age/cold)
- Short circuit measurement ? (!)
  - How to test?

# Alternative Method – Known Load



- Connect a known resistance across the terminals

$$V = \frac{R}{R_{TH} + R} V_{TH}$$

- Original relationships

$$V_{OC} = V_{TH}$$

$$V_{TH} = I_{SC} R_{TH}$$

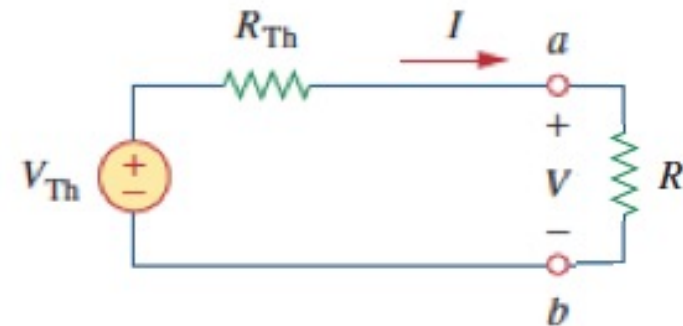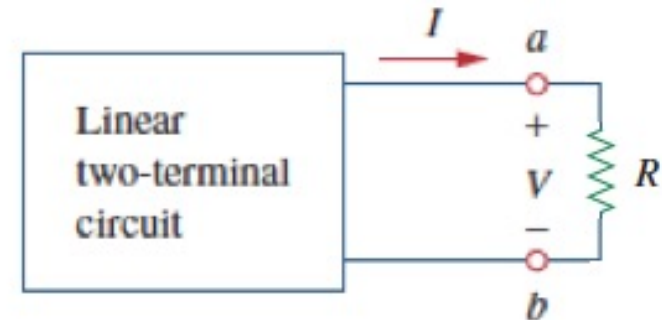

## Car battery problem – version 1:

- Open circuit test: 12.6 volts across the terminals
  
- 10  $\Omega$  precision resistor load: 12.46 volts

## Solution 1:

- Open circuit test: 12.6 volts across the terminals

$$V_{Th} = V_{oc} = 12.8 \text{ volts}$$

- 10  $\Omega$  precision resistor load: 12.46 volts

$$V = \frac{R}{R_{TH} + R} V_{TH}$$

$$12.46 = \frac{10}{R_{TH} + 10} 12.6$$

$$R_{TH} = 0.112 \Omega$$

## Car battery problem – version 2:

- 100  $\Omega$  precision resistor load: 12.45 volts
- 10  $\Omega$  precision resistor load: 12.2 volts

## Solution 2:

- 100  $\Omega$  precision resistor load: 12.45 volts
- 10  $\Omega$  precision resistor load: 12.2 volts

$$12.45 = \frac{100}{R_{TH} + 100} V_{TH} \Rightarrow 100 V_{TH} - 12.45 R_{TH} = 1245$$


$$12.2 = \frac{10}{R_{TH} + 10} V_{TH} \Rightarrow 10 V_{TH} - 12.2 R_{TH} = 122$$

Solving

$$V_{TH} = 12.48 \text{ volts} \quad R_{TH} = 0.228 \Omega$$
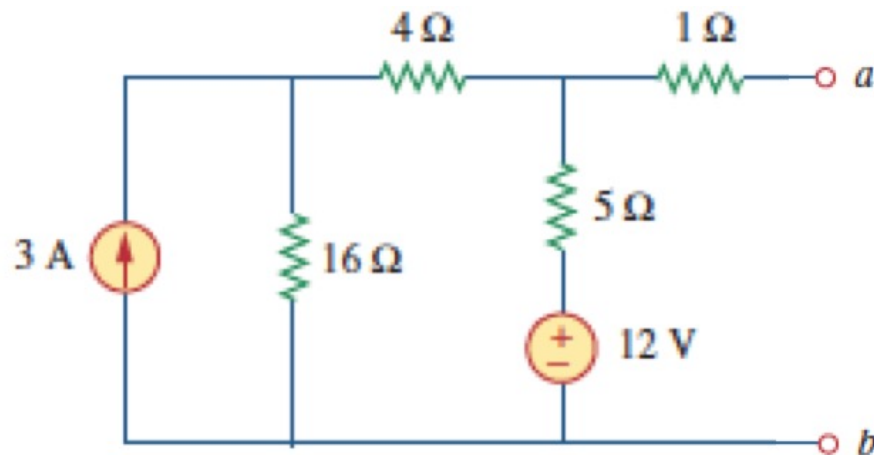
# “Ohmmeter” Test for $R_{Th}$


- If no dependent sources, then
  - Turn off independent sources
  - Compute equivalent resistance looking into terminals  $a$ - $b$




19.2 V, 5  $\Omega$



# Thévenin and Phasors

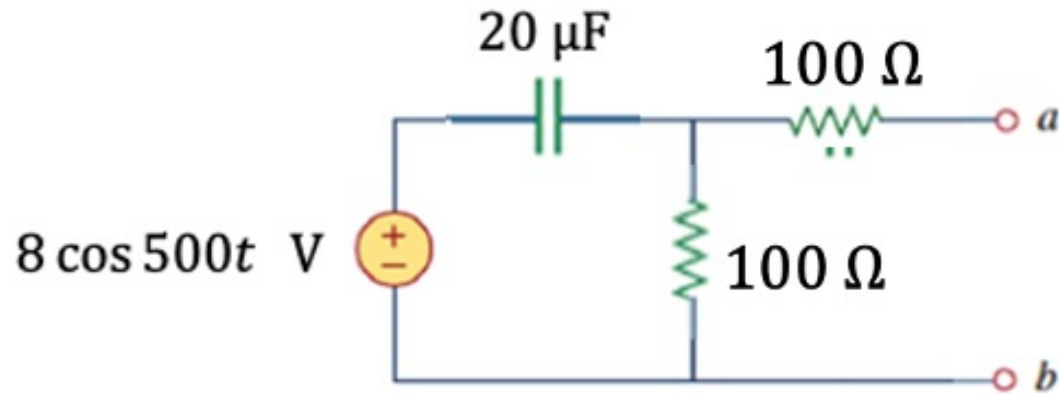


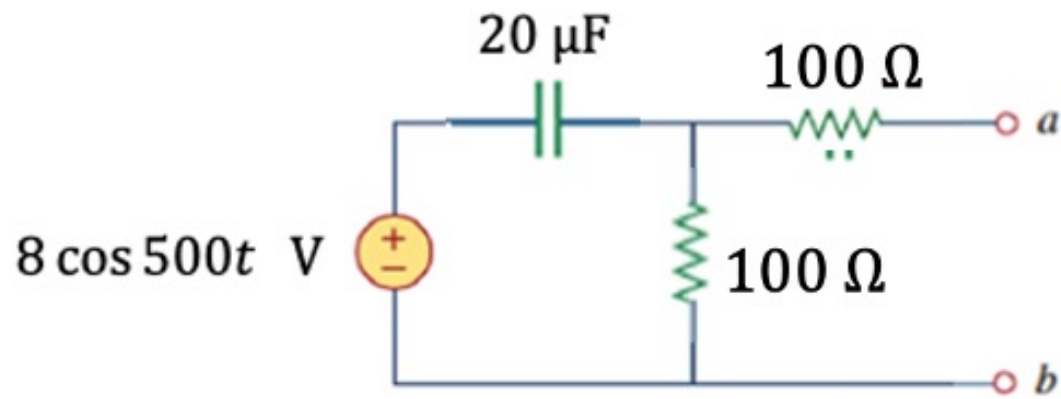



$$4\sqrt{2} \cos(500t + 45^\circ) \text{ V},$$
$$150 \Omega, 40 \mu\text{F}$$

# Norton Equivalent


- Recall source transformations, then

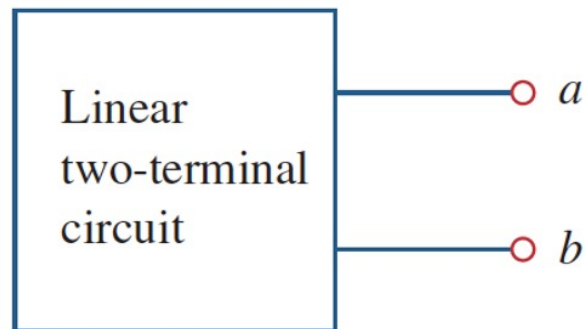


$$R_N = R_{TH}$$
$$I_n = I_{SC}$$

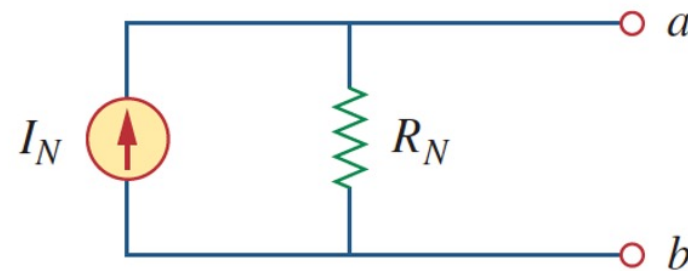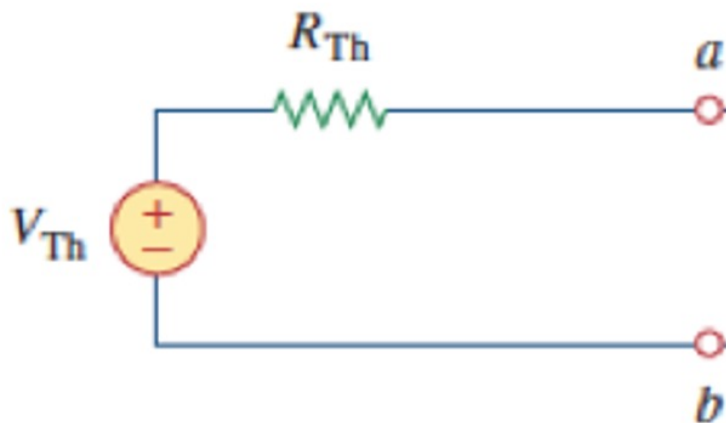


**Example:** which 2 are equivalent

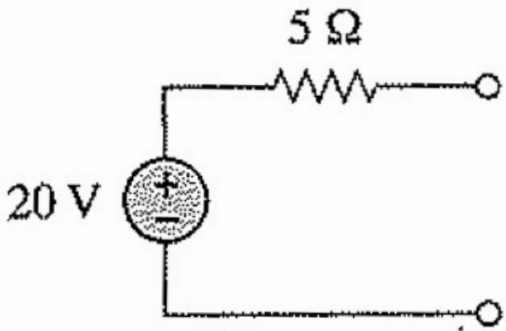


(a)

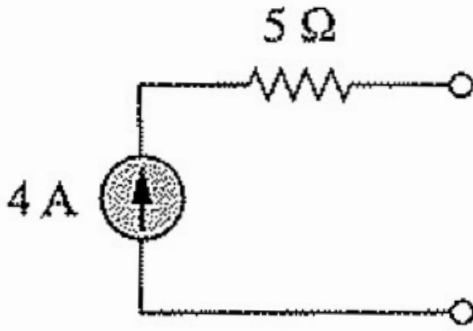

(b)

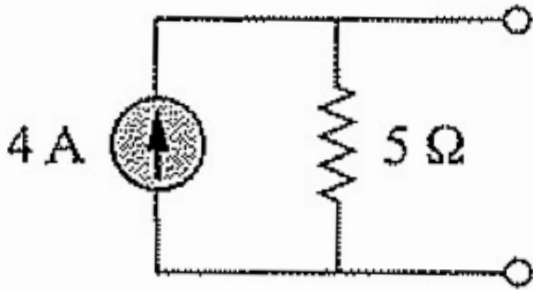



(c)

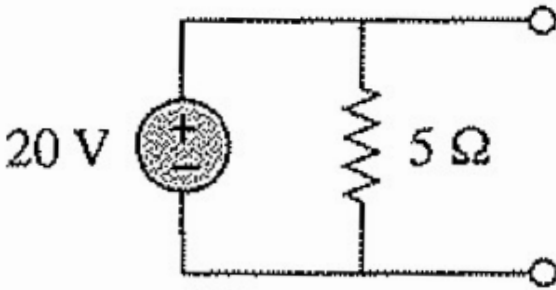

(d)


**Example:** Find  $I_N$  and  $R_N$

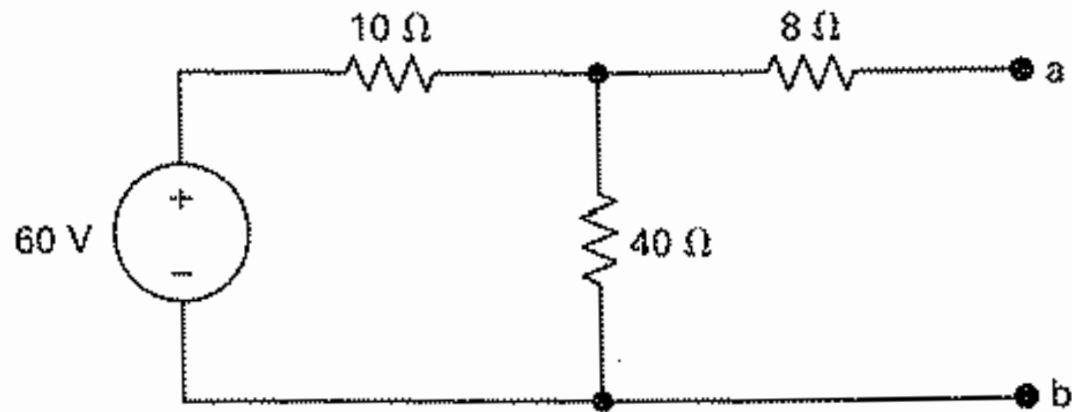

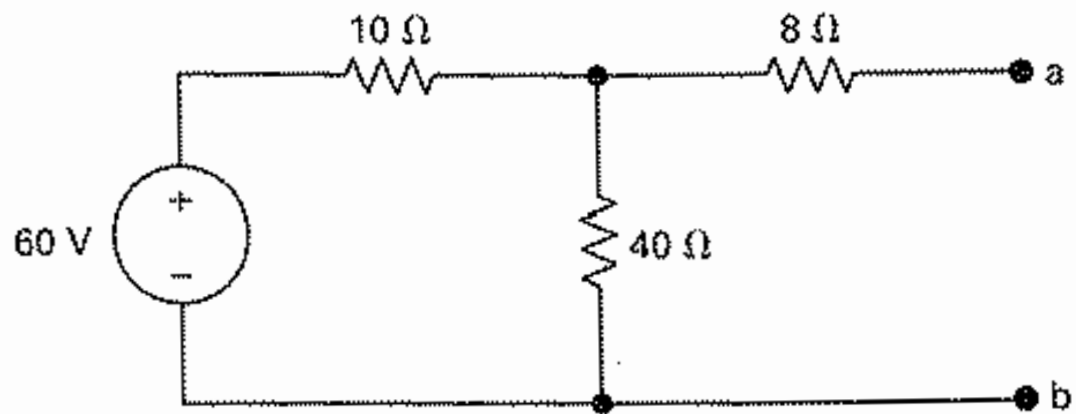


$$I_N = 3 \text{ A}, R_N = 16 \text{ } \Omega$$

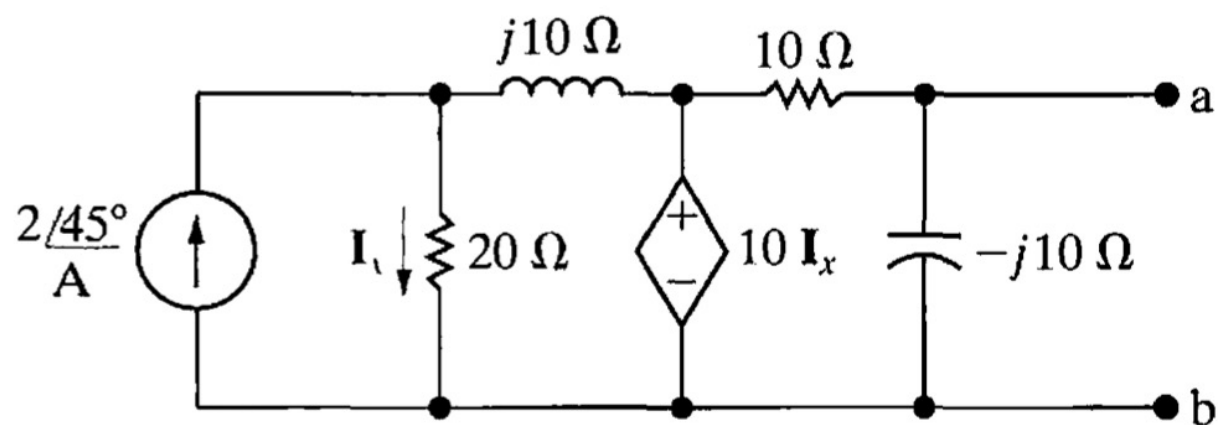**Example:** Find  $V_{Th}$  and  $Z_{Th}$  in phasor form



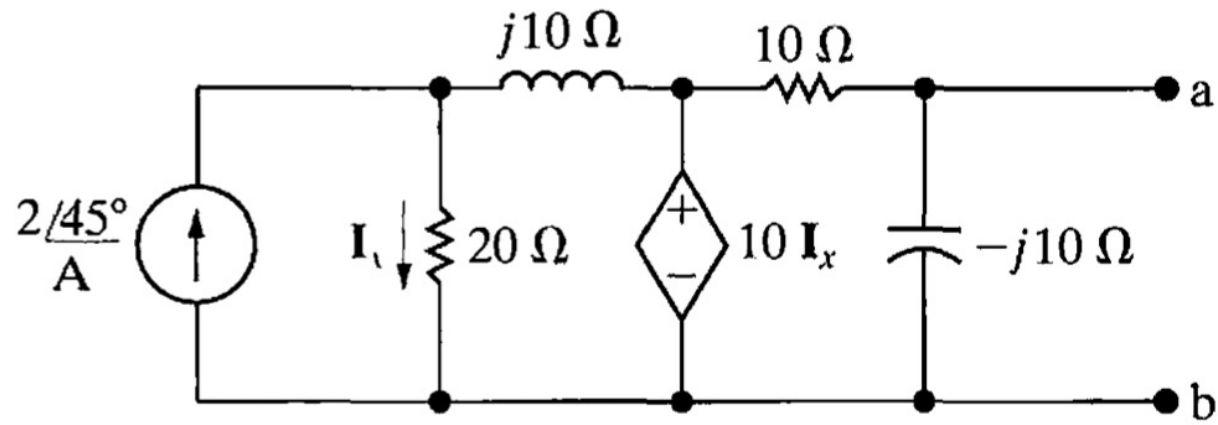
$10 \angle 45^\circ \text{ V}, 5 - 5j \Omega$






50 V, 20  $\Omega$ , 2.5 A

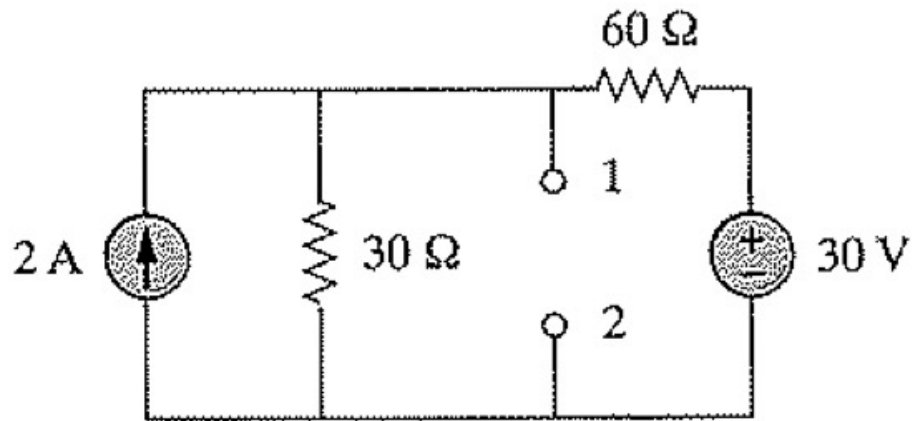**Practice problem:** find Thevenin and Norton




92 V, 28  $\Omega$ , 3.29 A

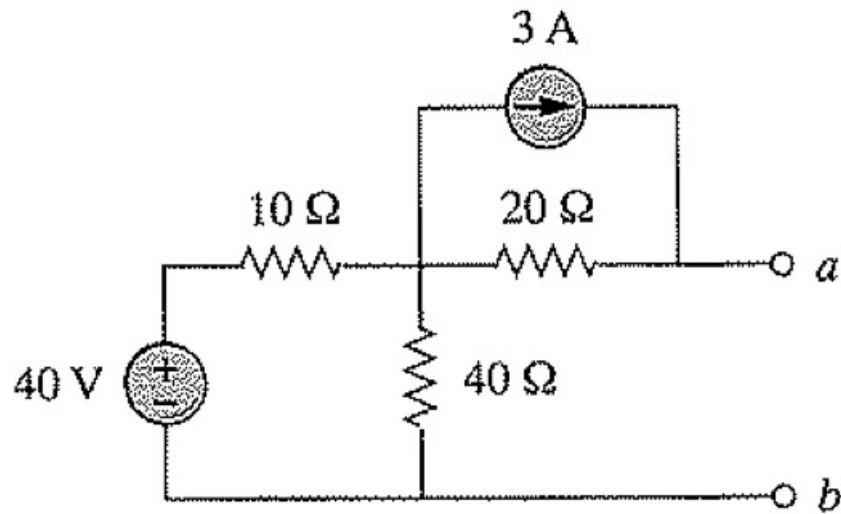**Practice problem:** find Thevenin and Norton




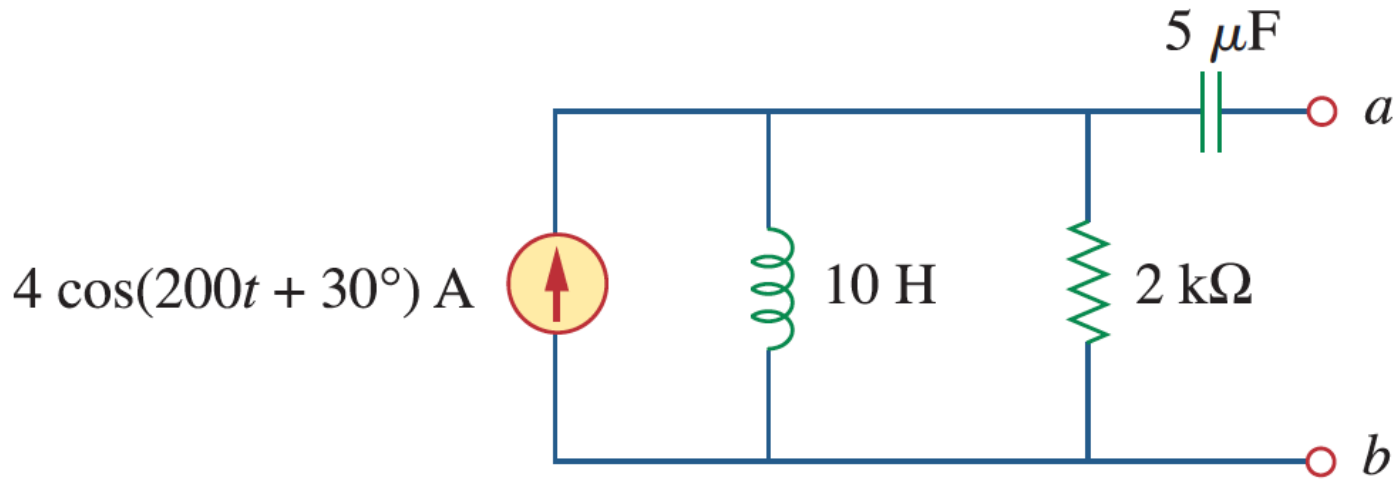**Practice problem:** find the Thevenin and Norton models




$$4000\sqrt{2} \cos(200t + 75^\circ) \text{ V},$$
$$1000 \Omega,$$
$$4\sqrt{2} \cos(200t + 75^\circ) \text{ A}$$

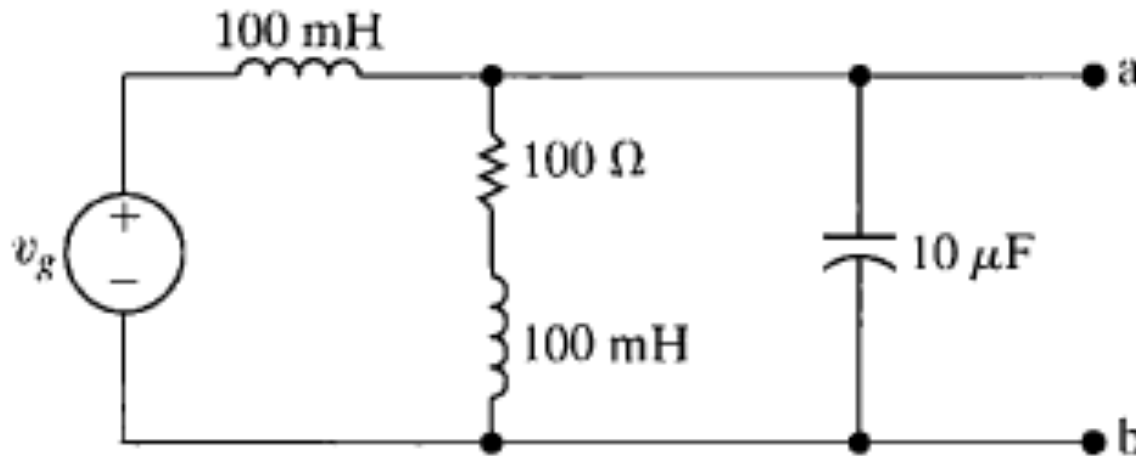**Practice problem:** find the Thevenin and Norton models if  $v_g(t) = 247.49 \cos(1000t + 45^\circ) \text{ V}$



$350 \cos 1000t \text{ V},$   
 $100 \Omega, 100 \text{ mH},$   
 $2.475 \cos(1000t - 45^\circ) \text{ A}$

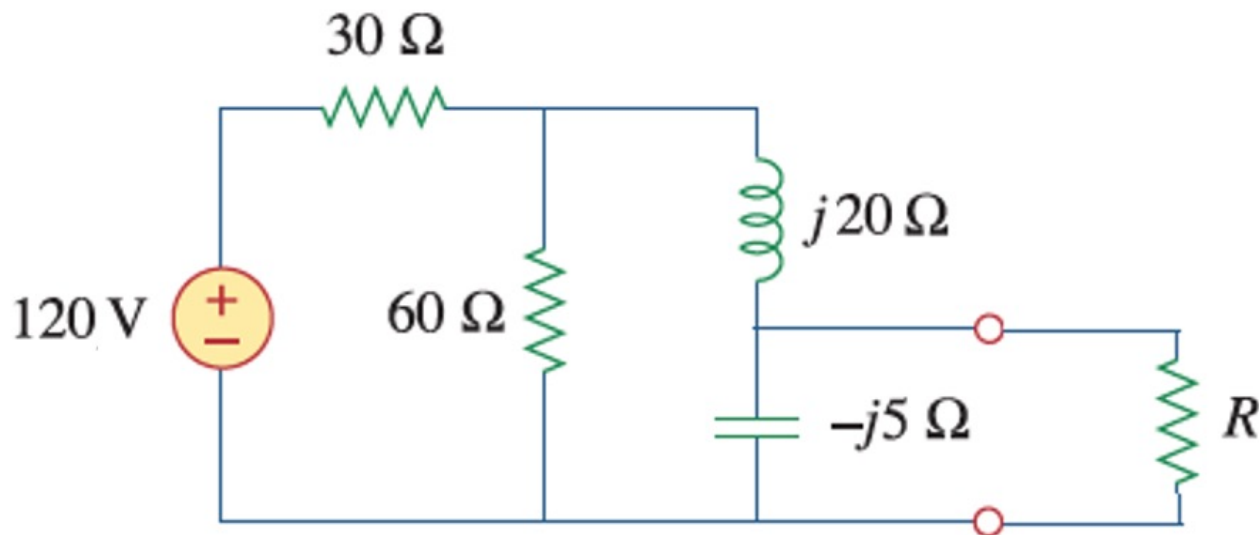**Practice problem:** find the magnitude of the current through  $R$  as a function of  $R$  – hint: first find the Thevenin equivalent



$$\frac{16}{\sqrt{(R + 0.8)^2 + 5.6^2}}$$