

1st Order Transients – 1


concepts

Where are we?

- Resistive circuits:
 - Simple elements; Kirchhoff's and Ohm's Laws
 - Nodal analysis
- Inductors and capacitors
 - Steady state (phasor) analysis
- Op amps
- Circuit theorems:
 - Thevenin/Norton, maximum power
- **Transients:**
 - **1st order circuits**
 - **2nd order circuits**
- Mesh analysis



Recall the 1st Phasor Circuit

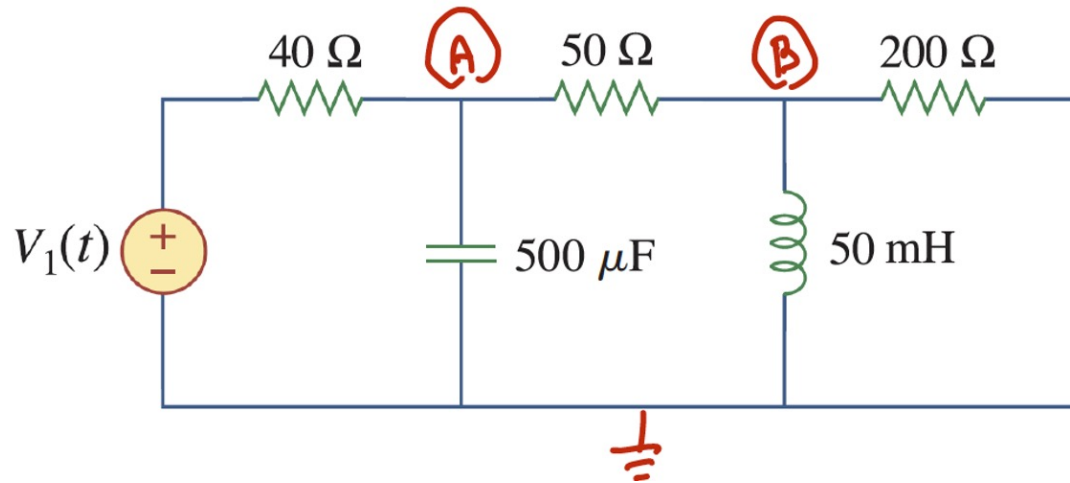

- Characterized by the 2nd order differential equations

$$\frac{d^2 A(t)}{dt^2} + 858 \frac{dA(t)}{dt} + 72,000 A(t) = 50 \frac{dV_1(t)}{dt} + 40,000 V_1(t)$$

$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 40 \frac{dV_1(t)}{dt}$$

$$\frac{d^2 A(t)}{dt^2} + 858 \frac{dA(t)}{dt} + 72,000 A(t) = 50 \frac{dV_1(t)}{dt} + 40,000 V_1(t)$$

$$\frac{d^2 B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 40 \frac{dV_1(t)}{dt}$$

- Homogeneous solutions are exponentials

$$A_{\text{homogeneous}}(t) = a_1 e^{-94.3t} + a_2 e^{-764t}$$

$$B_{\text{homogeneous}}(t) = b_1 e^{-94.3t} + b_2 e^{-764t}$$


$$\frac{d^2A(t)}{dt^2} + 858 \frac{dA(t)}{dt} + 72,000 A(t) = 50 \frac{dV_1(t)}{dt} + 40,000 V_1(t)$$

$$\frac{d^2B(t)}{dt^2} + 858 \frac{dB(t)}{dt} + 72,000 B(t) = 40 \frac{dV_1(t)}{dt}$$

- Now, imagine that $V_1(t) = V_1$ is a constant (DC) voltage source; then the particular solutions are both constants

$$A_{steady-state}(t) = a_0 \left(= \frac{5 V_1}{9} \right)$$

$$B_{steady-state}(t) = b_0 (= 0)$$

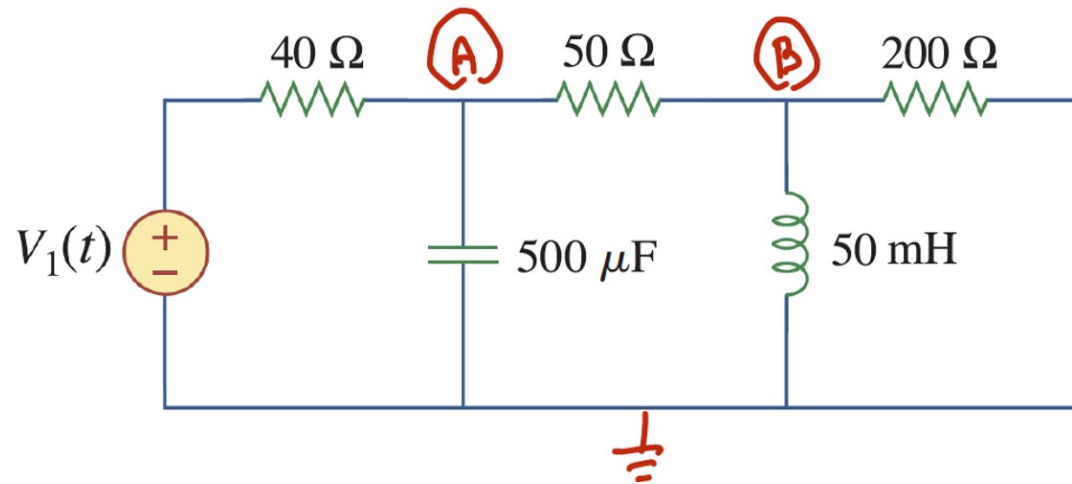

- So, combining



$$A(t) = \frac{5 V_1}{9} + a_1 e^{-94.3t} + a_2 e^{-764t}$$

$$B(t) = b_1 e^{-94.3t} + b_2 e^{-764t}$$

- Still has unknown constants

Transient Analysis

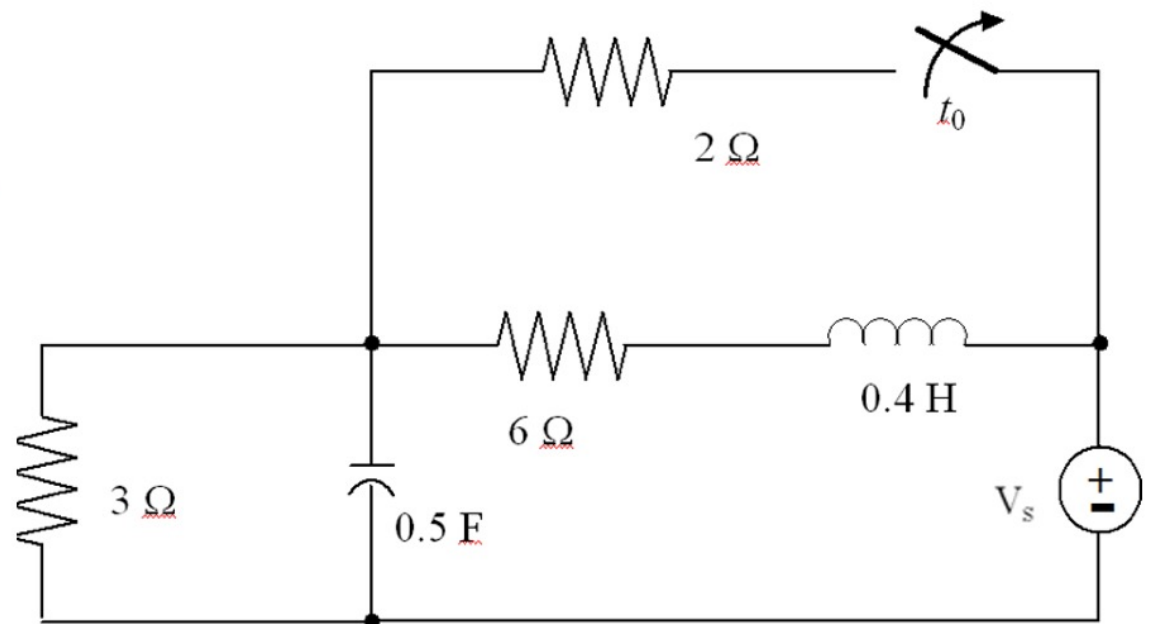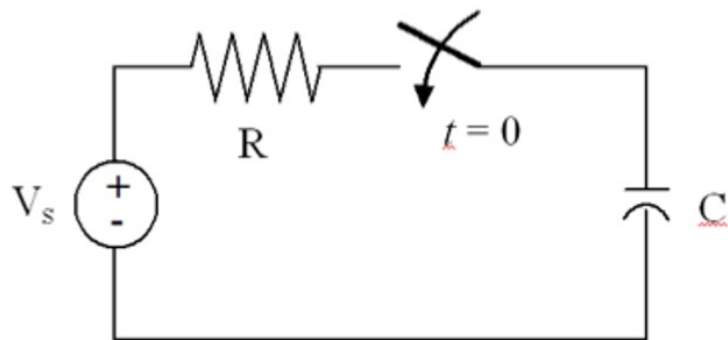- Short-term response of a circuit to “change”, typically a switching event:
 - An actual switch or sources turning on/off
 - Interest is after the switching event




- We consider the DC source case so that the forced portion is a constant; specifically, in steady state, all voltages/currents are constants, so


$$v_L = L \frac{di_L(t)}{dt} = 0 \quad \rightarrow \quad \text{inductors act as short circuits}$$


$$i_C = C \frac{dv_C(t)}{dt} = 0 \quad \rightarrow \quad \text{capacitors act as open circuits}$$

As an example:

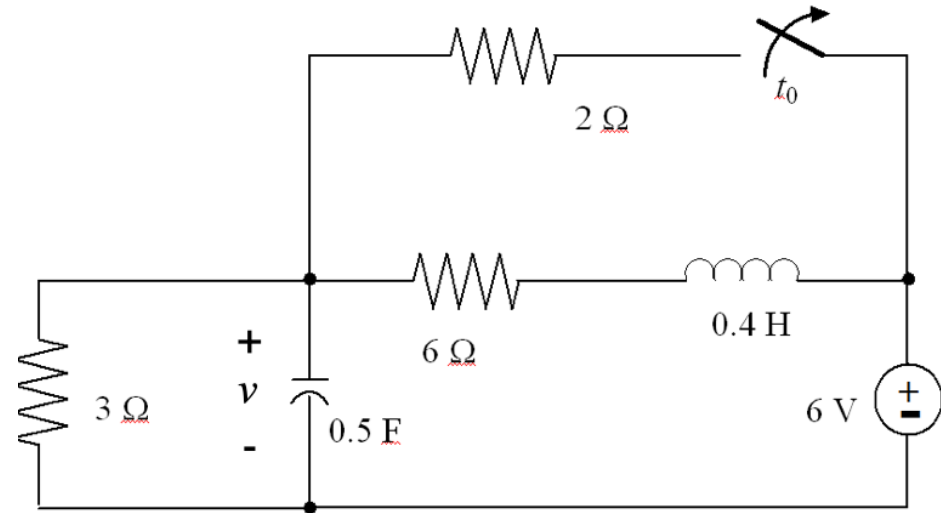


Before time t_0 , assuming steady state:


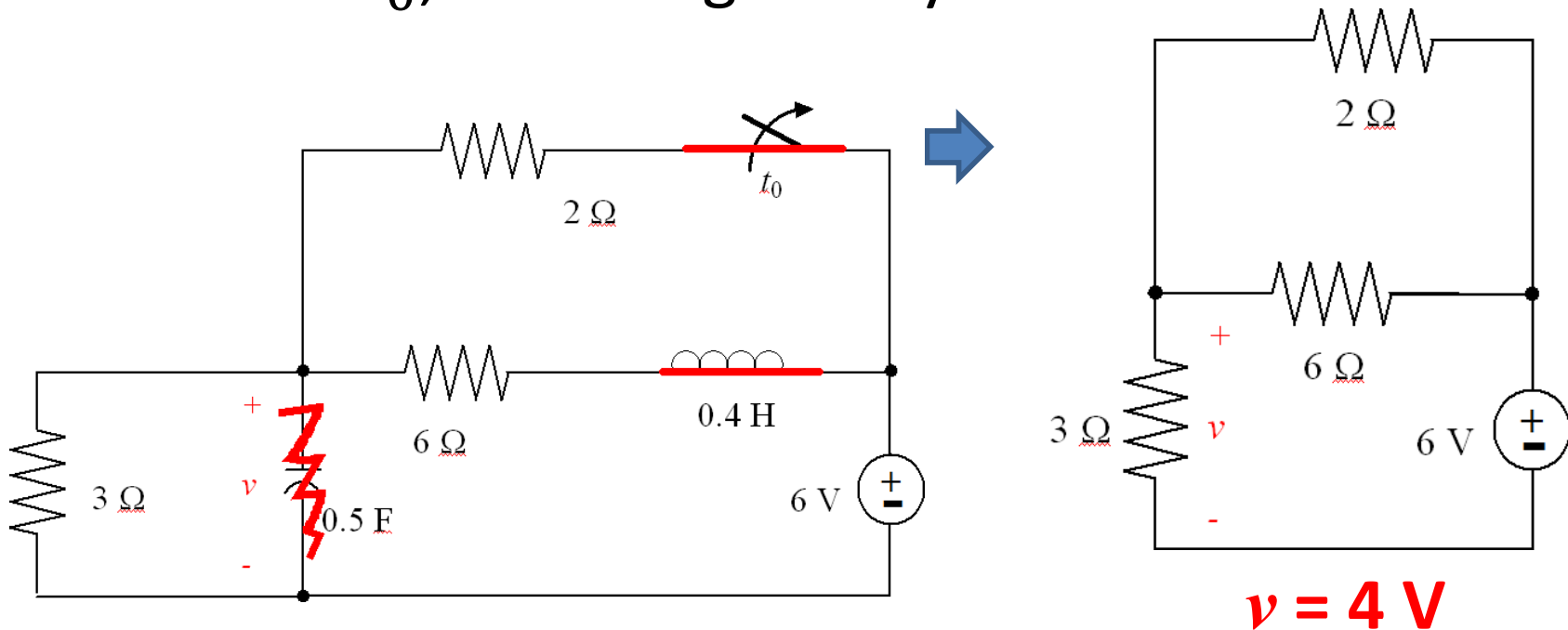


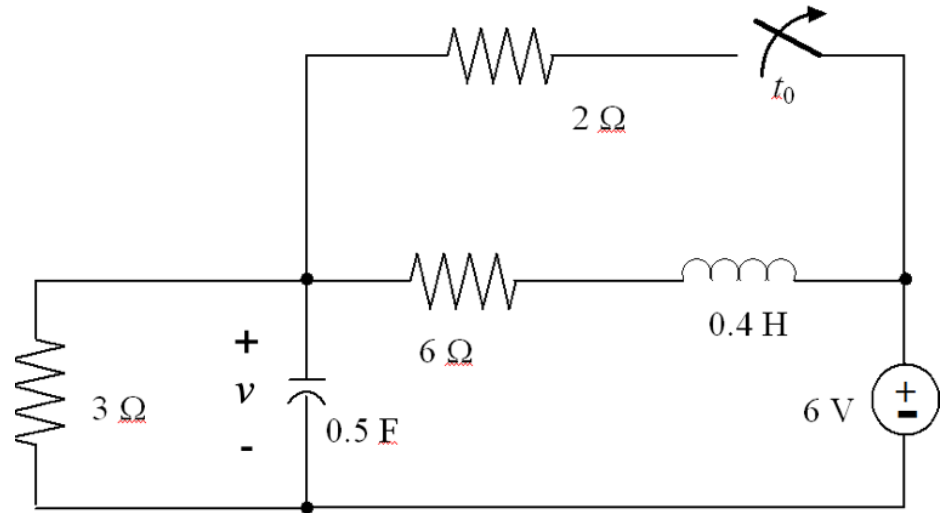


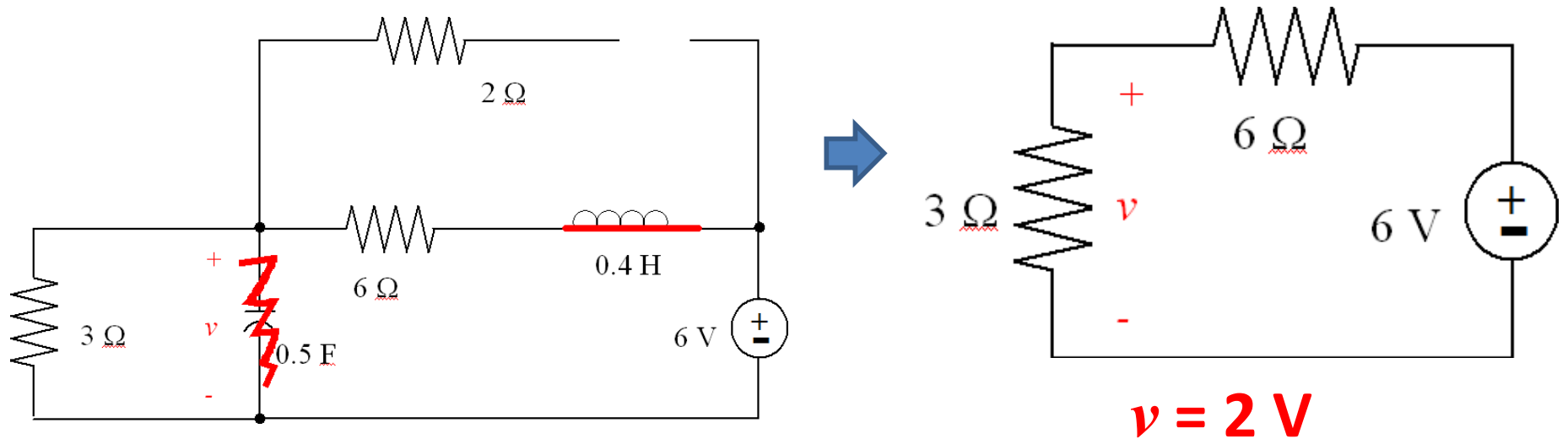And a long time after time t_0 , steady state again:



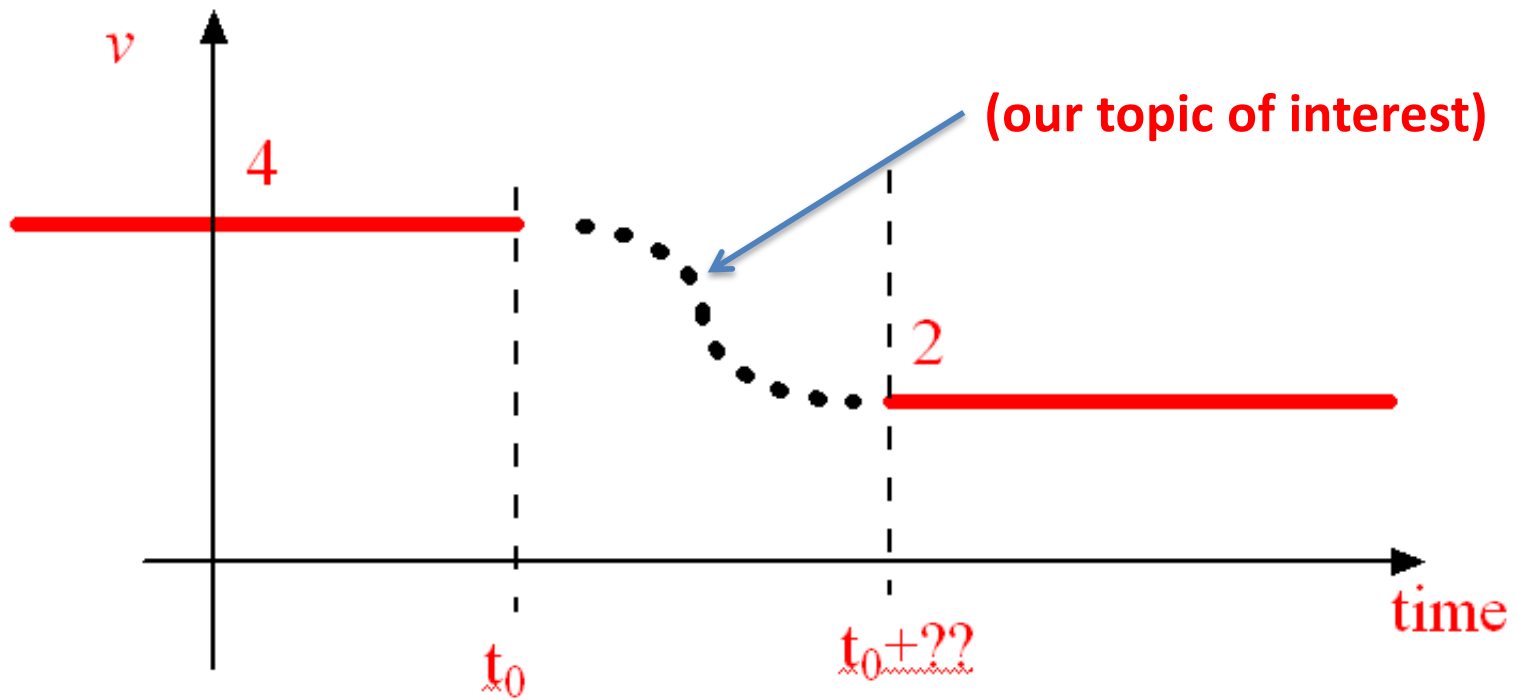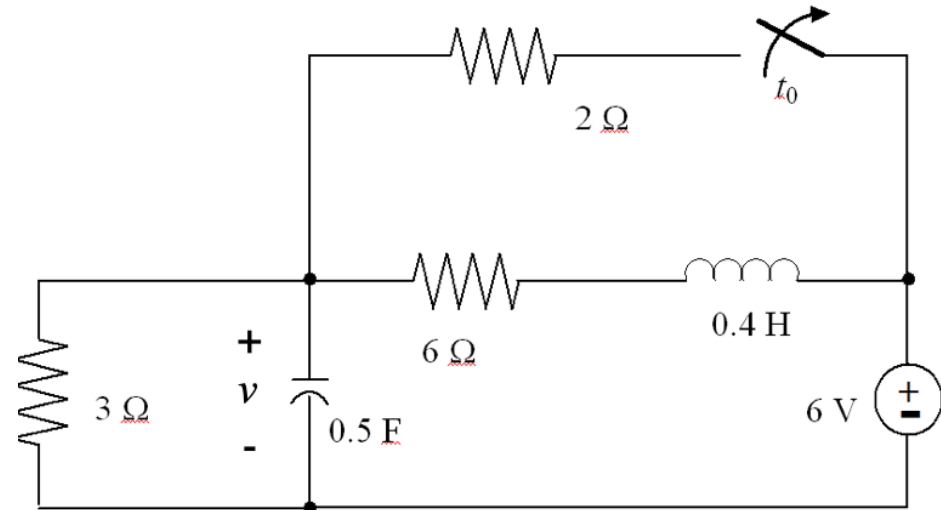The transient is what happens in between these




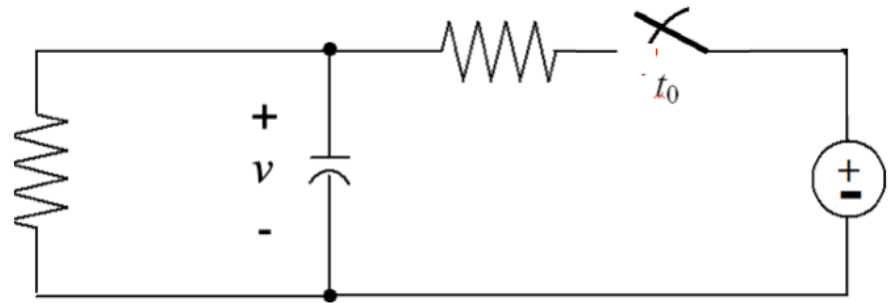

- Terminology used:
 - Natural response: circuit with no sources, initial conditions only; usually all variables go to zero
 - Step response: circuit with DC sources, zero initial conditions
 - Combined response = sum of both
- Useful facts:
 - Inductor: a short for DC; current cannot jump (is a continuous function)
 - Capacitor: an open for DC; voltage cannot jump (is a continuous function)


First Order RC Case

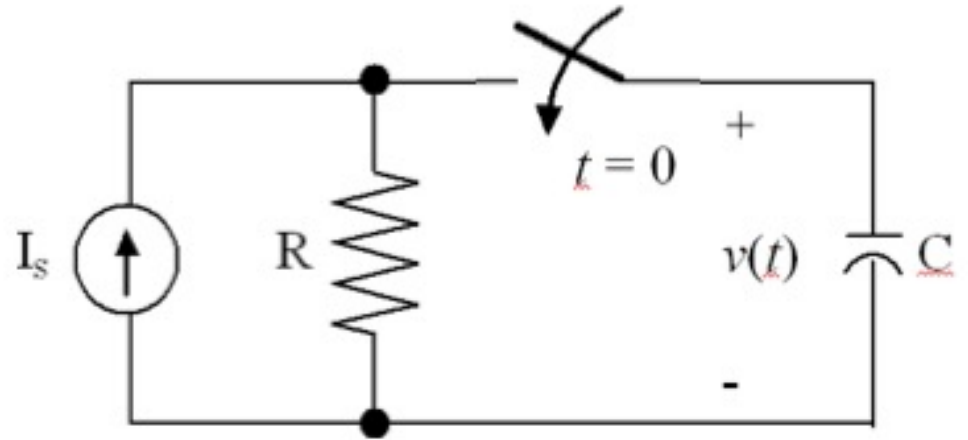- Simple circuit
- DC source
- initial capacitor voltage is v_0



- Node equation after $t = 0$:
$$\frac{dv(t)}{dt} + \frac{1}{RC}v(t) = \frac{1}{C}I_s$$
- Solution is:
$$v(t) = A e^{-\frac{1}{RC}t} + B$$
- Need to solve for A and B

$$v(t) = A e^{-t/RC} + B$$

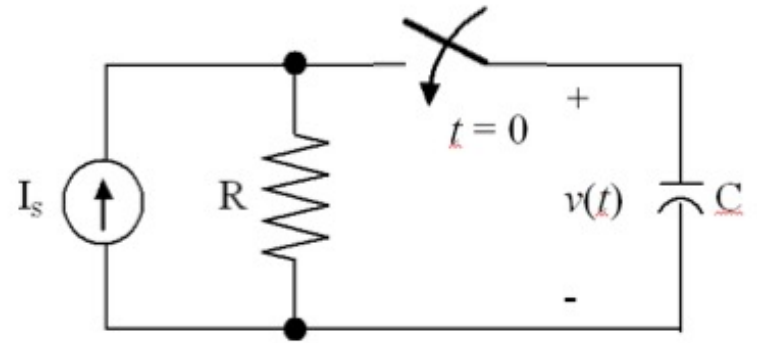

– Initial and final conditions: from the math


$$v(0) = A + B \quad v(\infty) = B$$

– So, solving

$$v(t) = (v(0) - v(\infty))e^{-t/RC} + v(\infty)$$


- Final value
 - Exploit the fact that in steady state the capacitor acts like an open

$$v(\infty) = I_s R$$

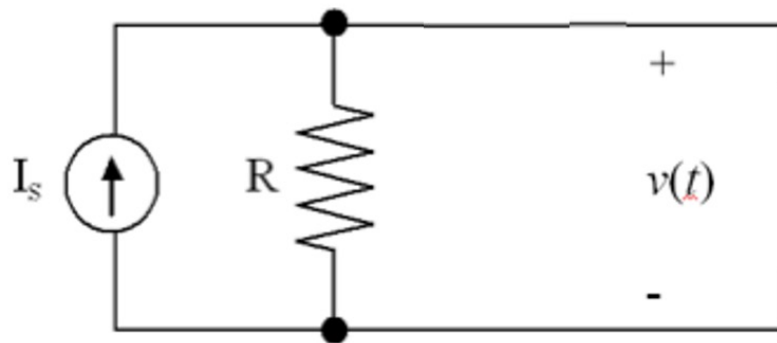

So

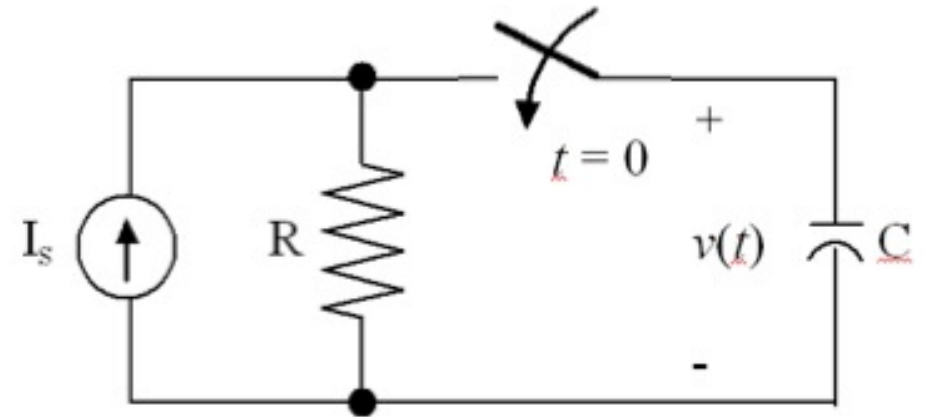
$$v(t) = (v_0 - I_s R)e^{-t/RC} + I_s R$$



- Initial condition
 - Exploit the fact that the capacitor voltage cannot take a jump

$$v(0) = v_0$$

- Consider a transformation:

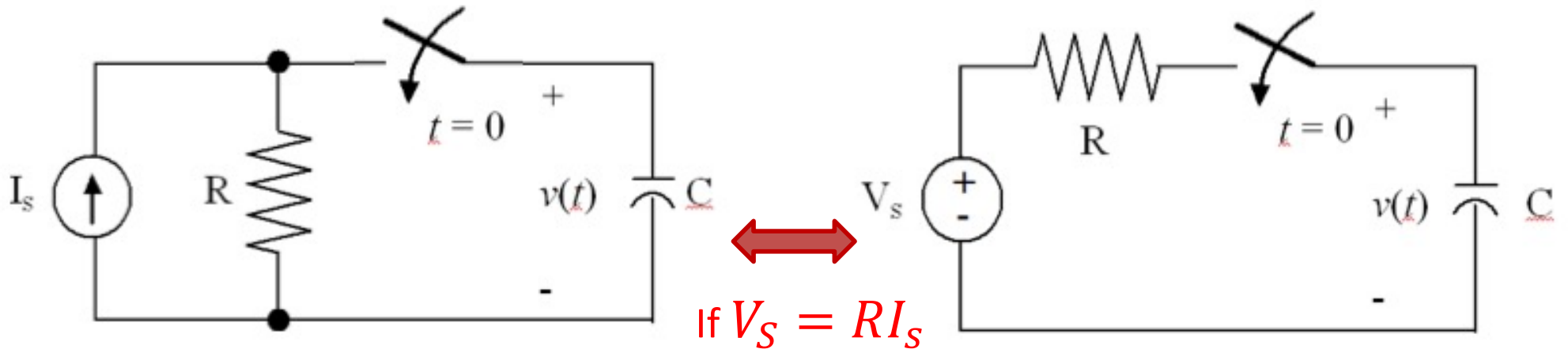

- With result

$$v(t) = (v_0 - I_s R) e^{-t/RC} + I_s R$$

$$= (v_0 - V_s) e^{-t/RC} + V_s$$