
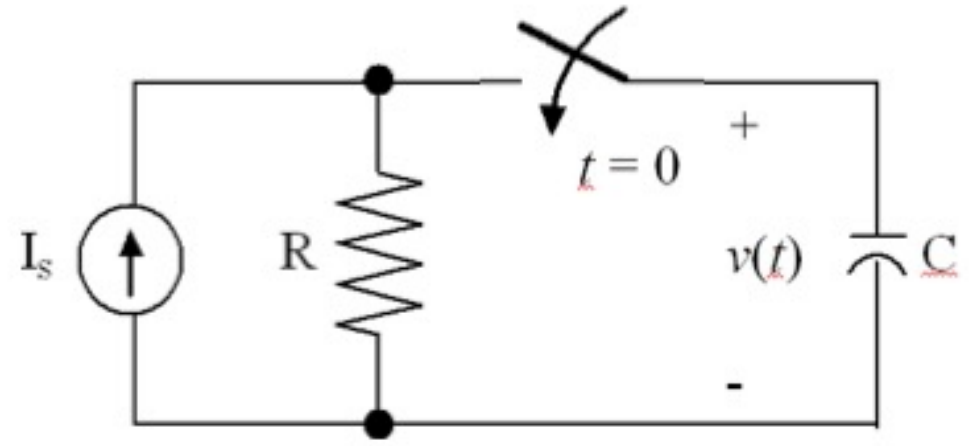


# 1<sup>st</sup> Order Transients – 2

general solution


# First Order RC Case

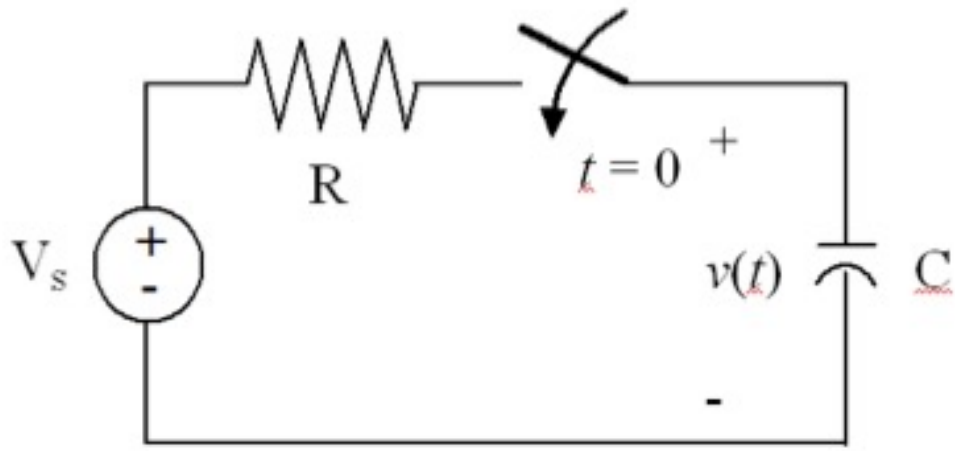


- Thevenin/Norton equivalents

- Solution 
$$v(t) = (v_0 - v_\infty) e^{-t/RC} + v_\infty$$


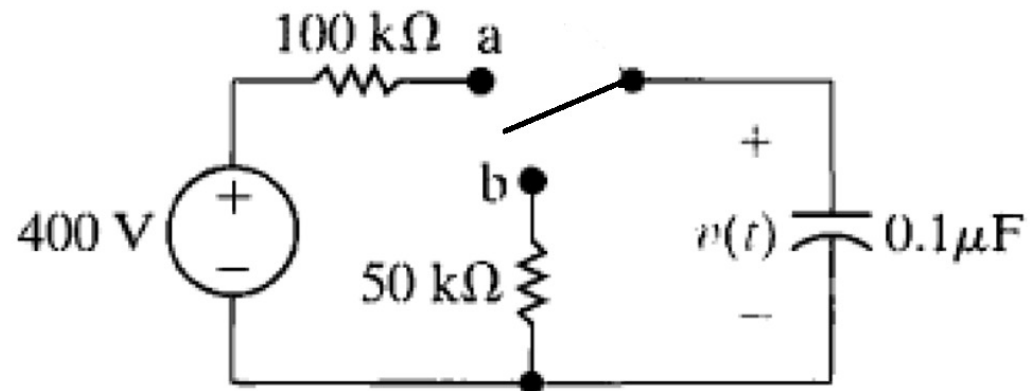
**Example:** switch changes  $a \rightarrow b$  at  $t = 0$



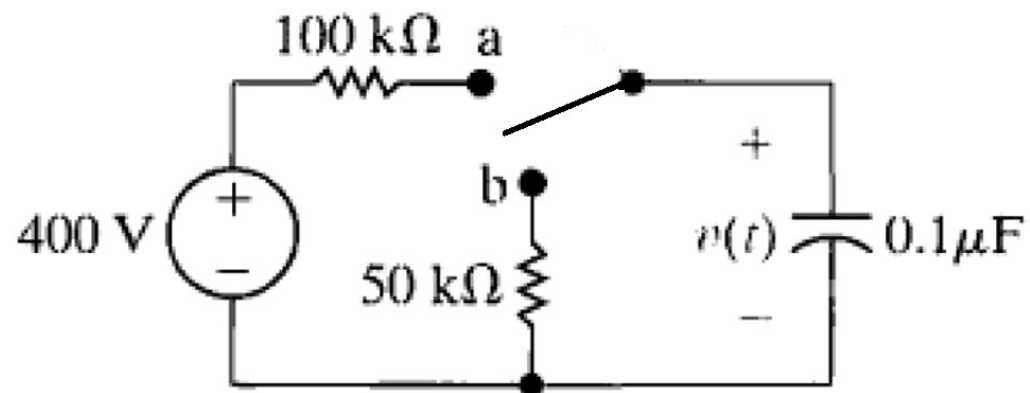**Example:** switch changes  $b \rightarrow a$  at  $t = 0$




# First Order RL Case

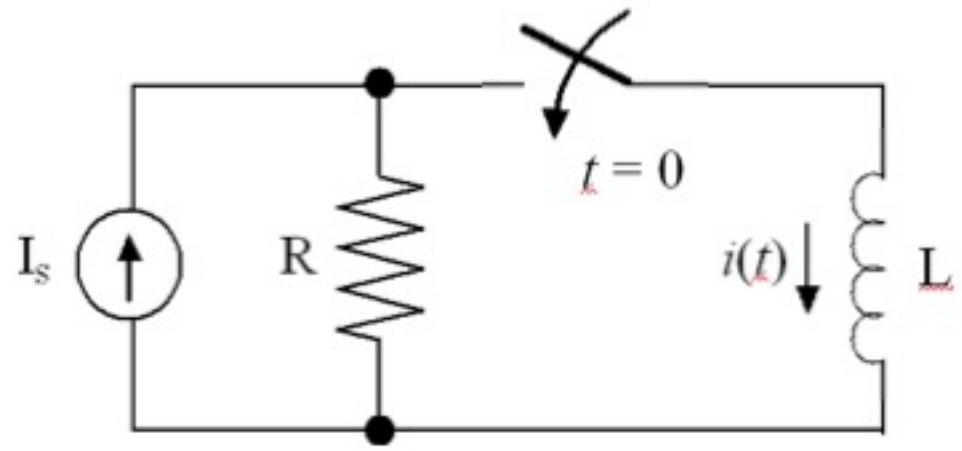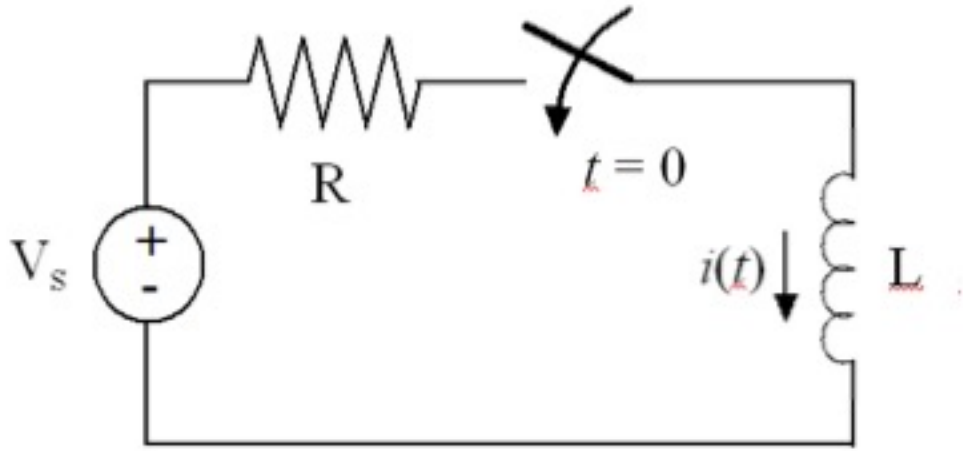


- Loop KVL equation: 
$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{1}{R} V_s$$

- Solution: 
$$i(t) = (i_0 - i_\infty) e^{-\frac{R}{L}t} + i_\infty$$

**Example:** switch opens at  $t = 0$

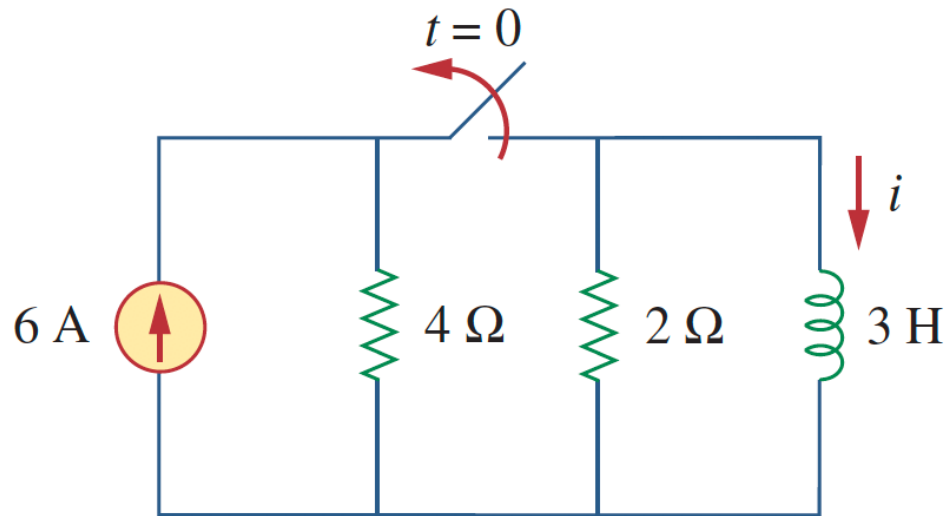

**Example:** switch closes at  $t = 0$

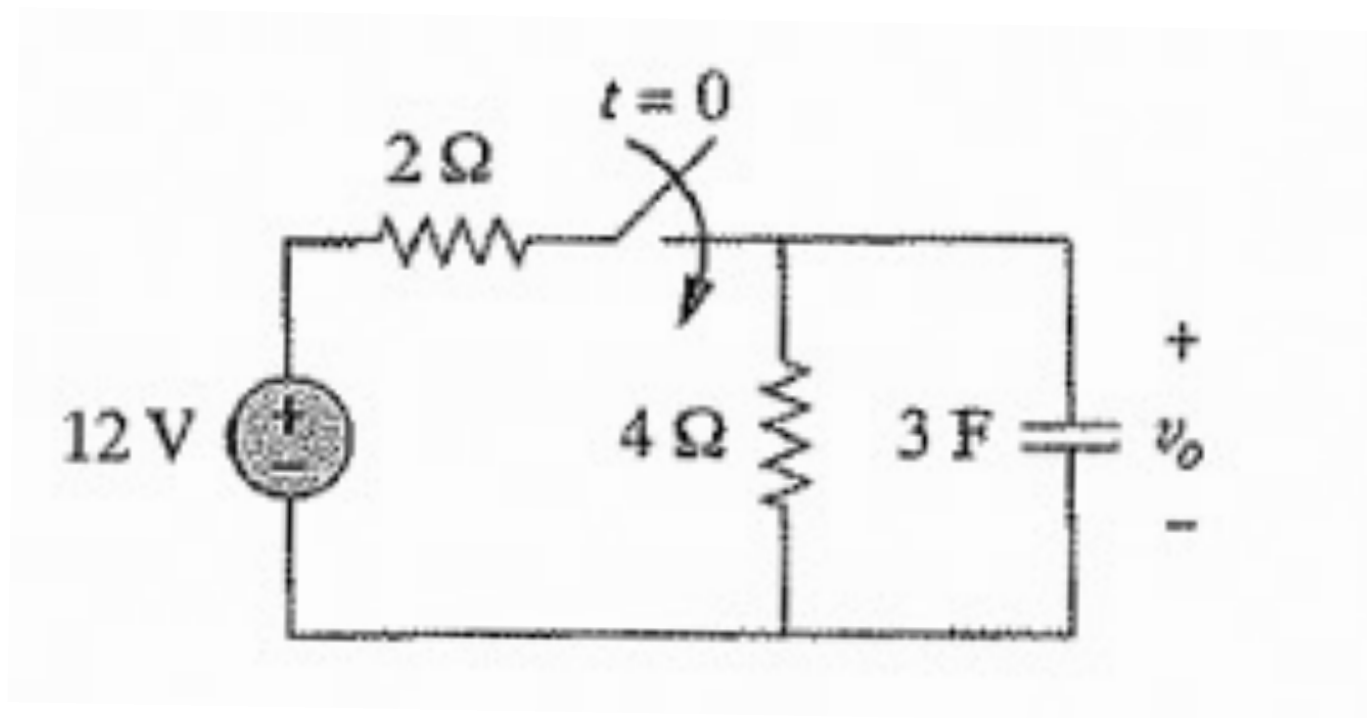

# General Result – 1st Order

- Inductor current or capacitor voltage,  $x(t)$  for  $t > 0$

$$x(t) = (\mathbf{x}_0 - \mathbf{x}_\infty) e^{-t/\tau} + \mathbf{x}_\infty$$


- Final and initial values,  $\mathbf{x}_\infty$  and  $\mathbf{x}_0$ :
  - From a DC analysis based on “open” or “short” models for C and L
  - Initial value exploits the continuity of capacitor voltages and inductor currents at  $t = 0$





$$x(t) = (x_0 - x_\infty) e^{-t/\tau} + x_\infty$$

- Time constant  $\tau$  ( $= L/R$  or  $RC$ )
- Why this form?
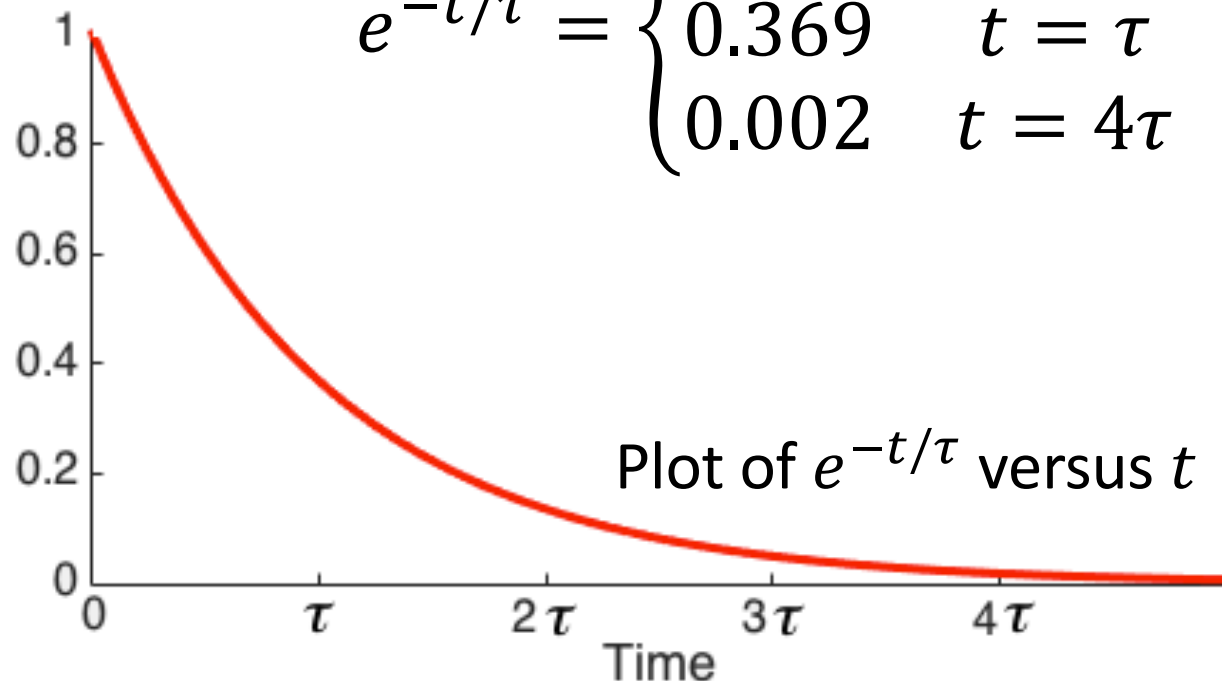
$$e^{-t/\tau} = \begin{cases} 1 & t = 0 \\ 0.369 & t = \tau \\ 0.002 & t = 4\tau \end{cases}$$




# What if the Circuit is more Complex?

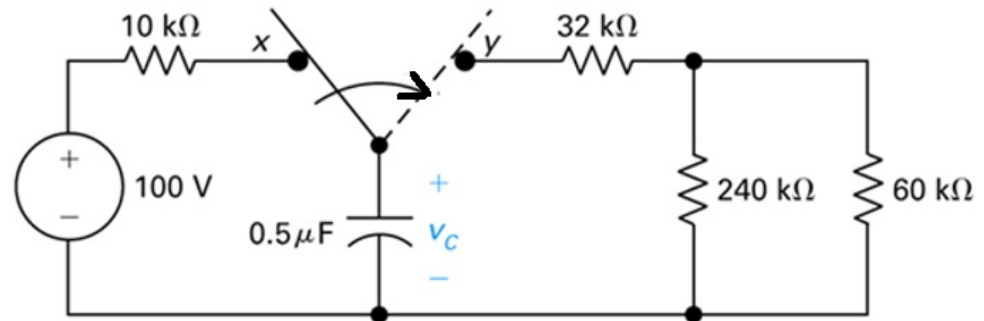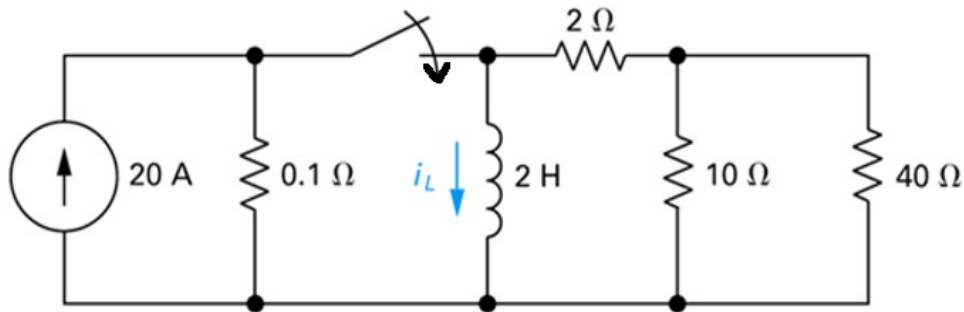

- Use the Thevenin equivalent circuit seen by L or C
  - Time constant  $\tau = L/R_{Th}$  or  $R_{Th}C$

## Worked example


– find  $i(t)$

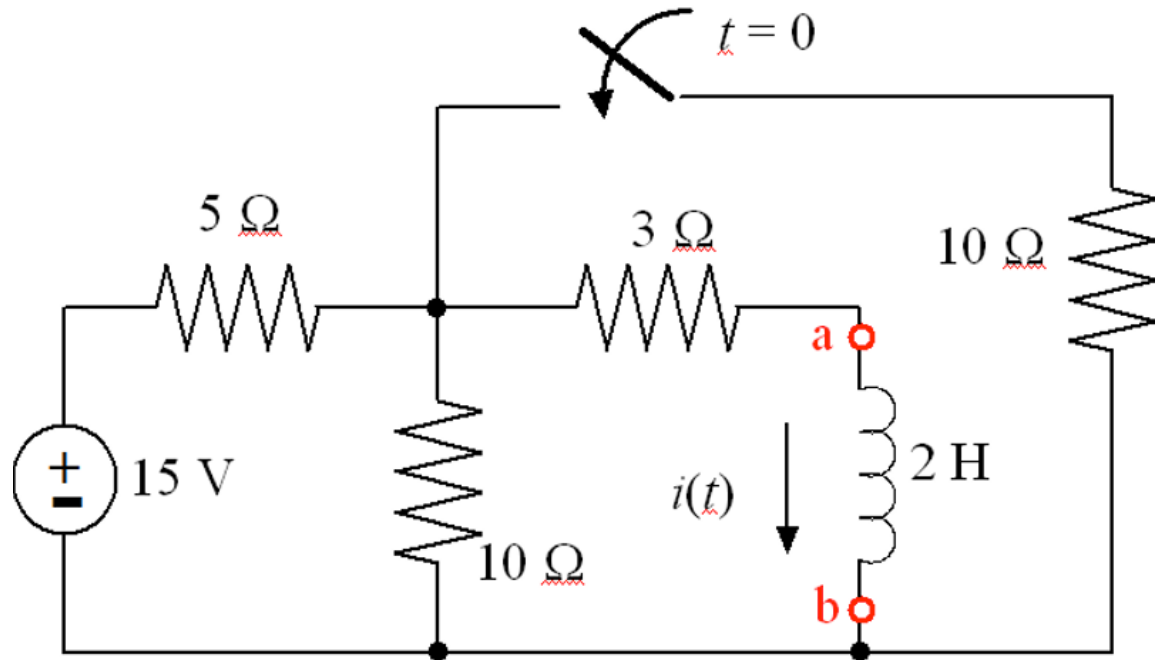

$$i(t) = (i_0 - i_\infty) e^{-t/\tau} + i_\infty$$

- Need:  $\tau$ ,  $i_\infty$ , and  $i_0$

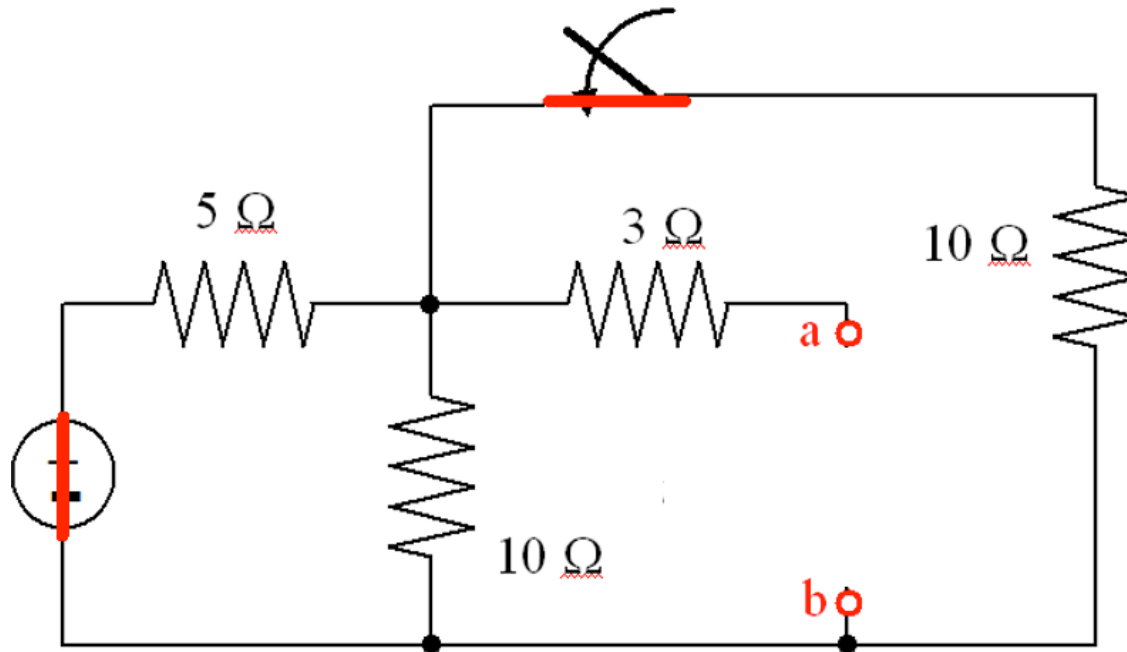
Step 1 – time constant  $\tau = \frac{L}{R_{Th}}$



$$\begin{aligned} R_{Th} &= 3 + 5 || 10 || 10 \\ &= 3 + 5 || 5 \\ &= 5.5 \Omega \end{aligned}$$

$$\tau = \frac{2}{5.5} = \frac{1}{2.75} \text{ sec}$$

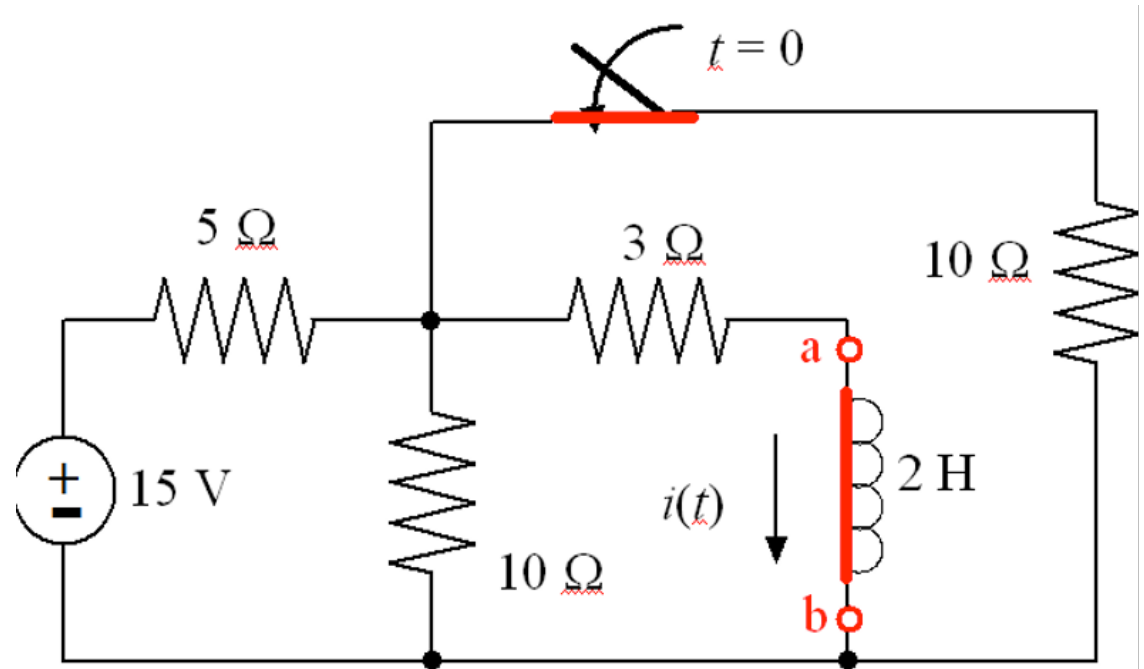
Step 2 – final value  $i_{\infty}$ ; as  $t \rightarrow \infty$



$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} + \frac{v}{10} = 0 \Rightarrow v = \frac{45}{11}$$

$$i_{\infty} = \frac{v}{3} = \frac{15}{11} = 1.36 \text{ amps}$$


Step 3 – initial value  $i_0$

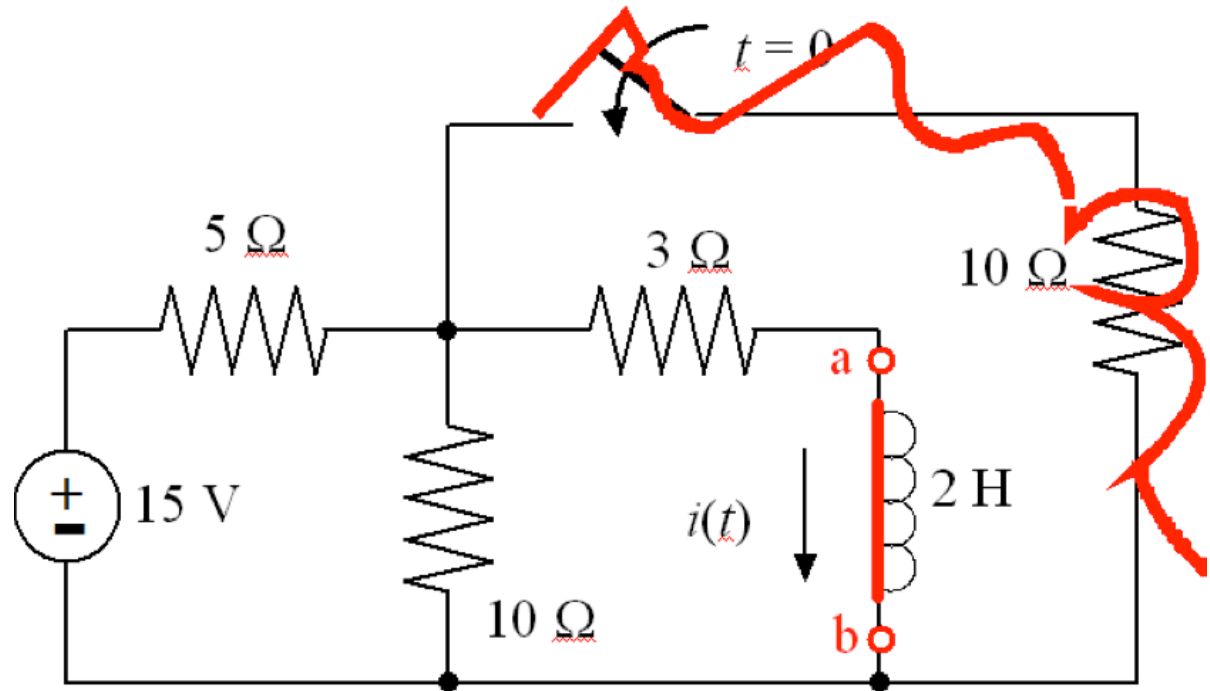


$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} = 0 \Rightarrow v = \frac{90}{19}$$

$$i_0 = \frac{v}{3} = \frac{30}{19} = 1.58 \text{ amps}$$


## Combining

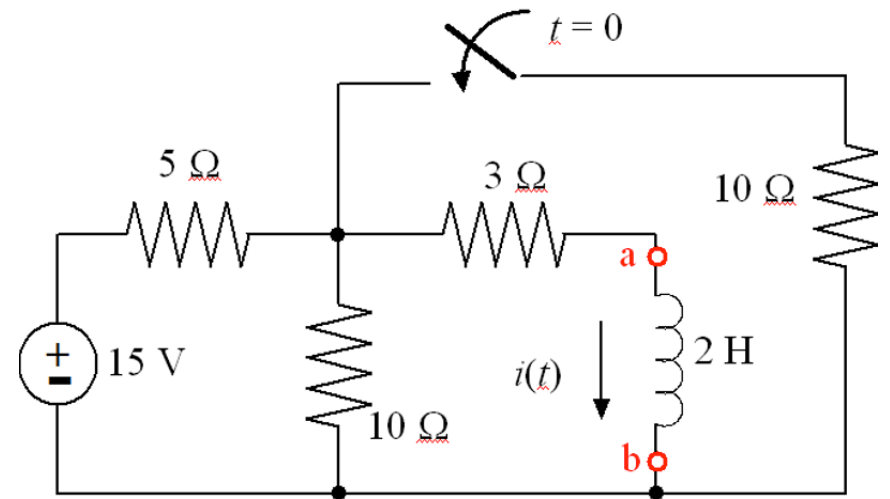

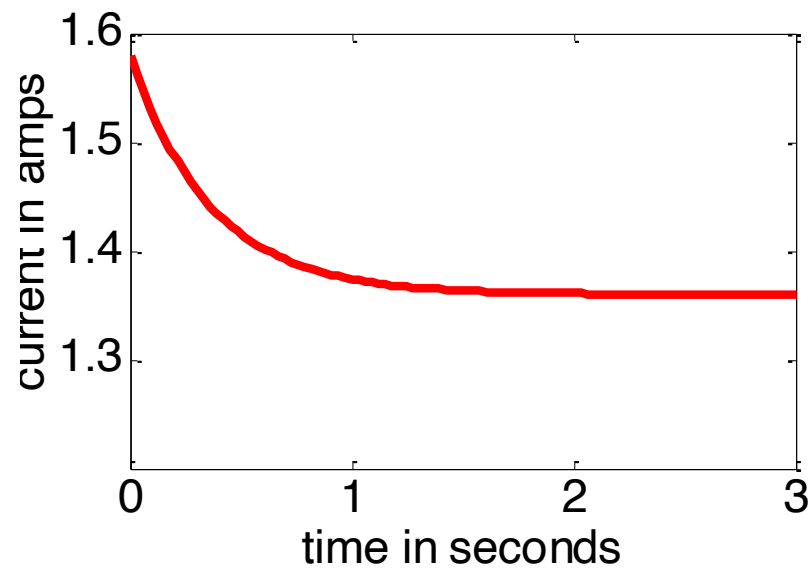
$$\begin{aligned} i(t) &= (i_0 - i_\infty) e^{-2.75 t} + i_\infty \\ &= 0.22 e^{-2.75 t} + 1.36 \text{ amps} \end{aligned}$$



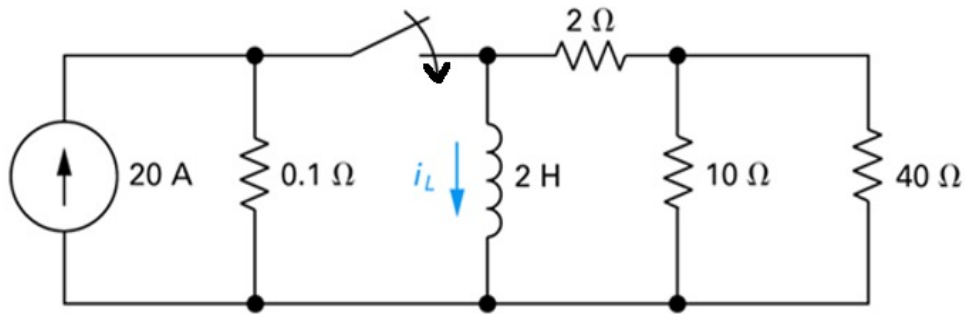**Practice problem:** find the inductor current







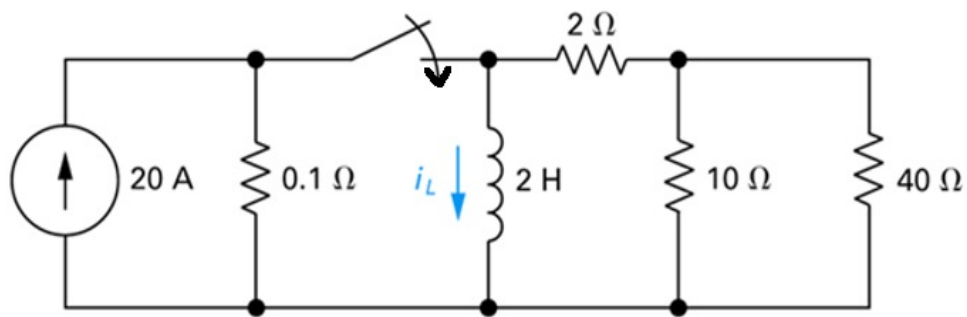

$$\begin{aligned}i(0^+) &= 0 \text{ A} \\i(\infty) &= 20 \text{ A} \\R_{Th} &= 0.0990 \text{ } \Omega\end{aligned}$$

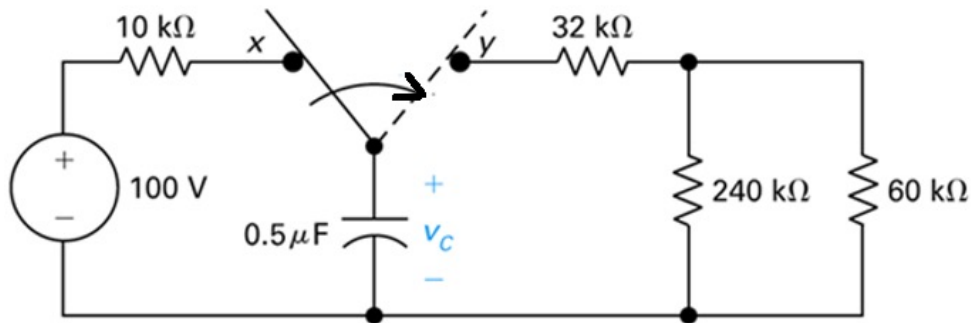**Practice problem:** find the capacitor voltage



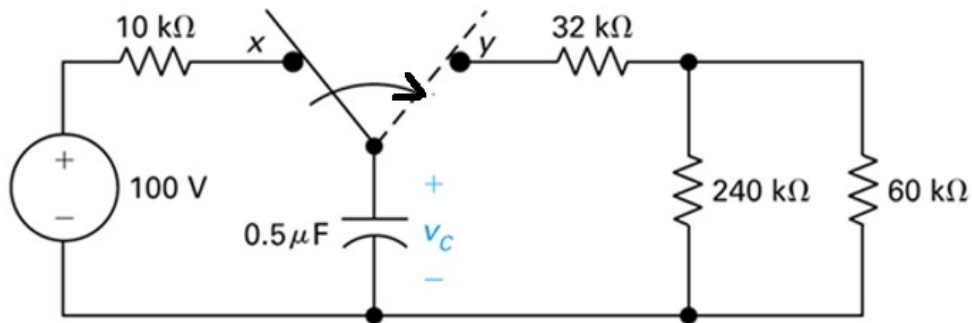

$$\begin{aligned}
 v(0^+) &= 100 \text{ V} \\
 v(\infty) &= 0 \text{ V} \\
 R_{Th} &= 80 \text{ k}\Omega
 \end{aligned}$$