
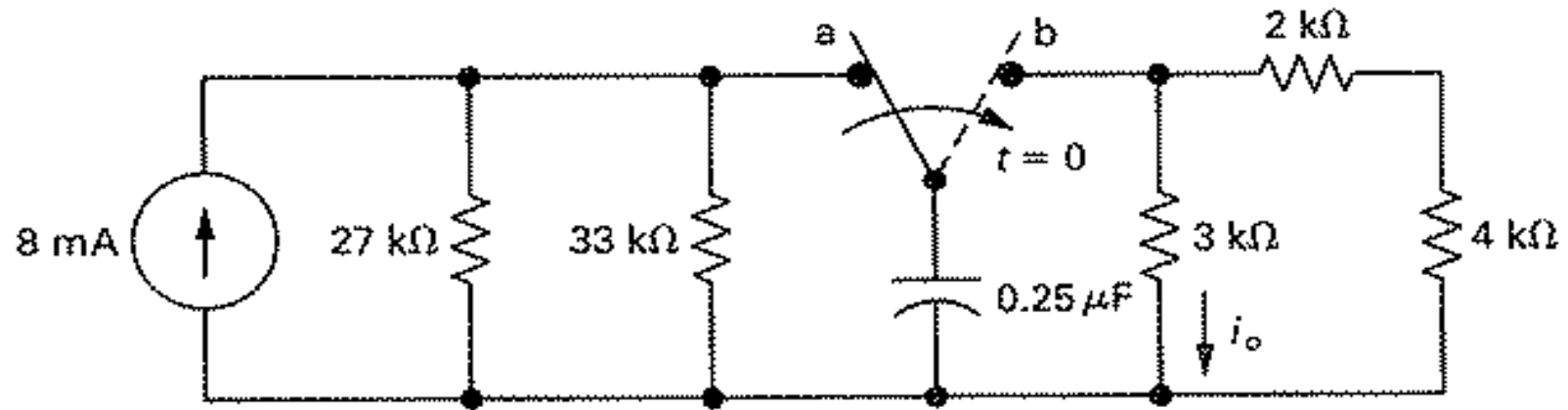


1st Order Transients – 5

more complex examples

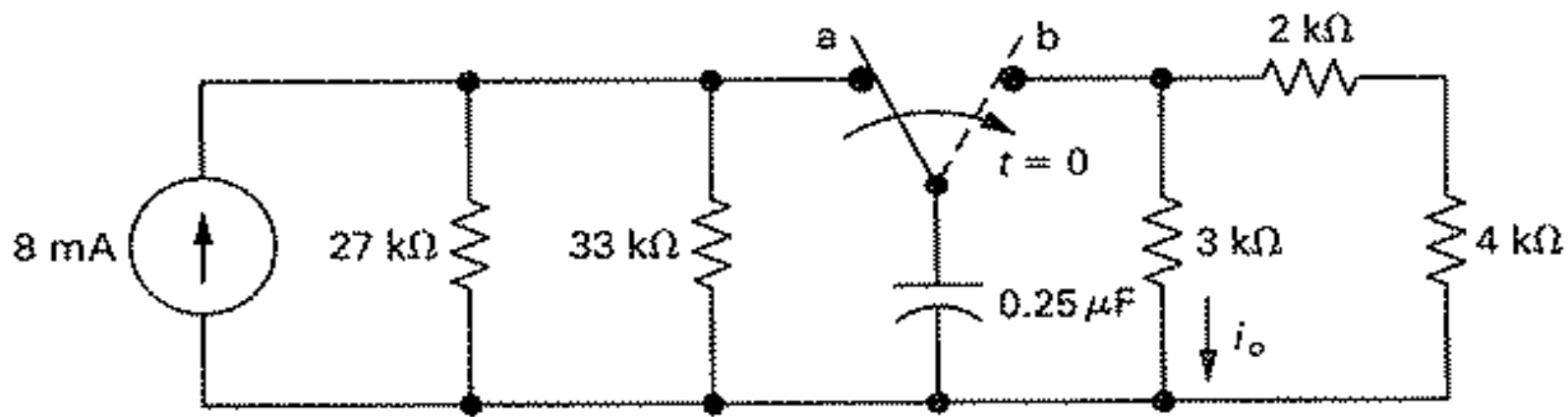
Example: What percentage of the initial energy stored in the capacitor (at time 0) is dissipated in the 4 k Ω resistor by time 250 μ sec?






36.8 %

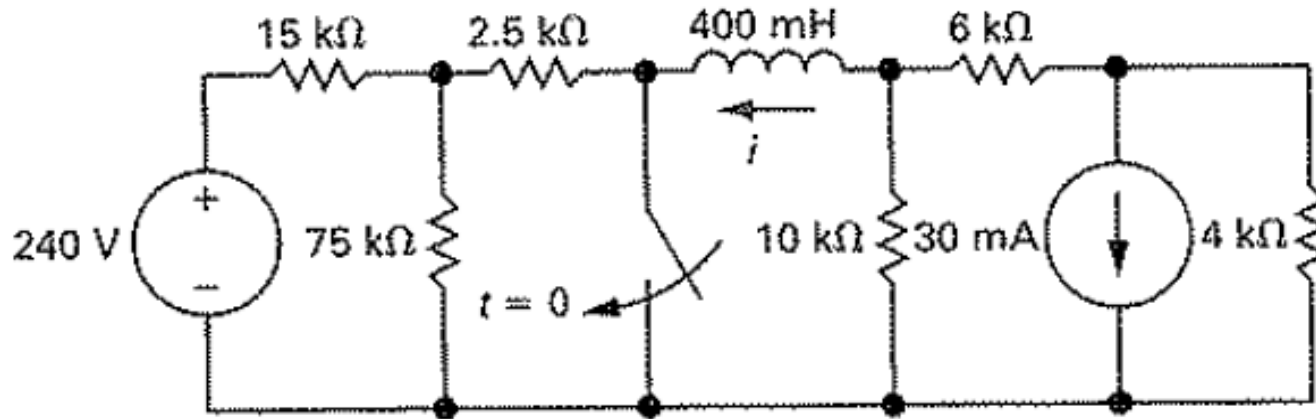
Example: find $i(t)$; this one is a bit tricky




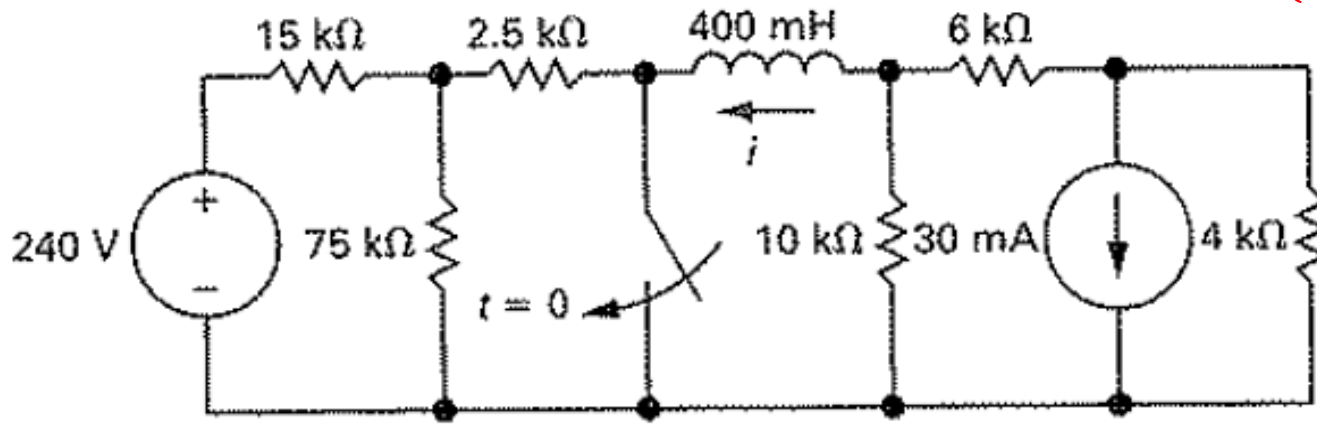

$$i(t) = -e^{12,5200t} - 12 \text{ mA}$$


Example: find $v_o(t)$

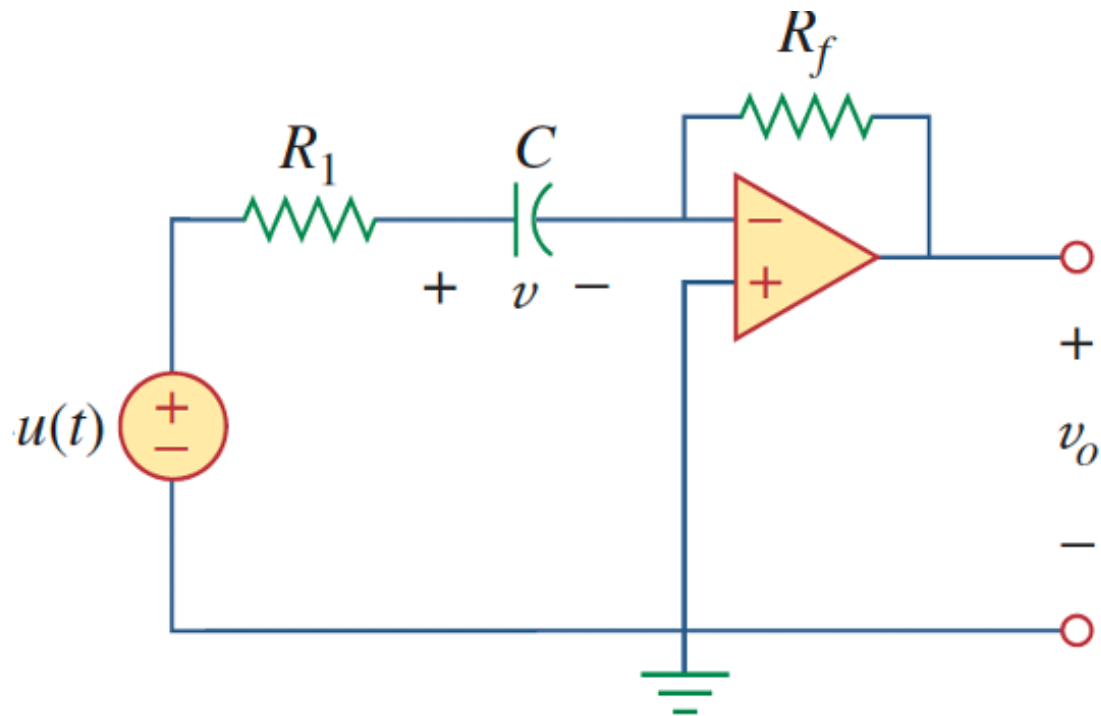


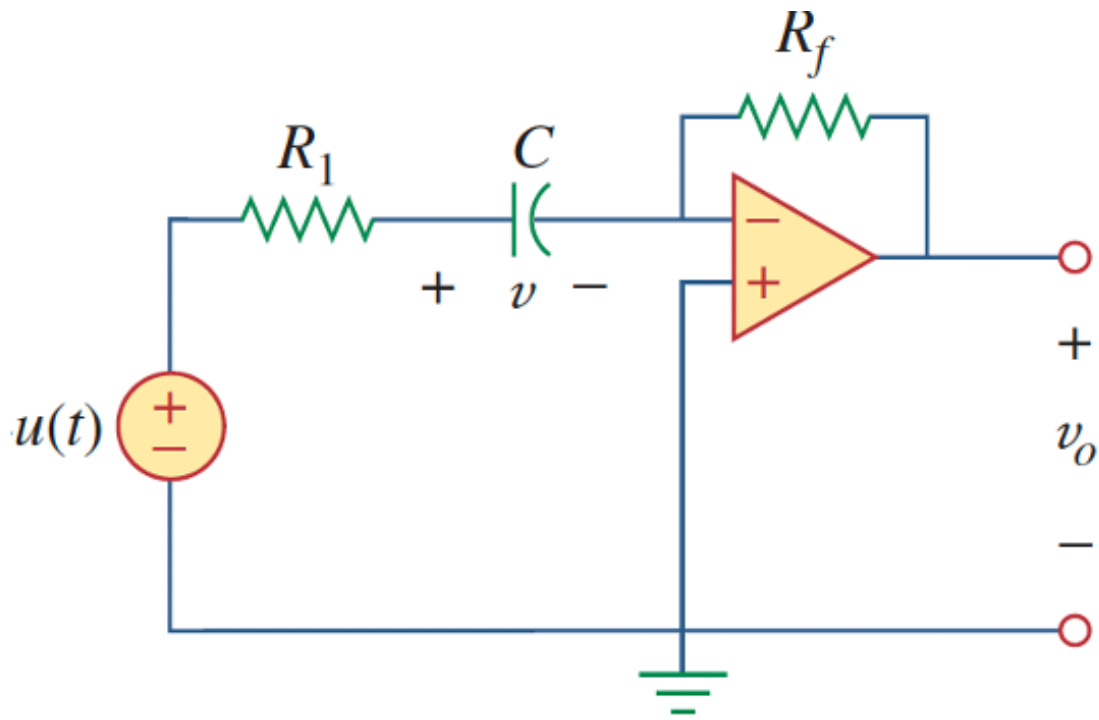

$$v_o(t) = -\frac{R_f}{R_1} e^{-t/R_1 C}$$

Example: find $i_o(t)$

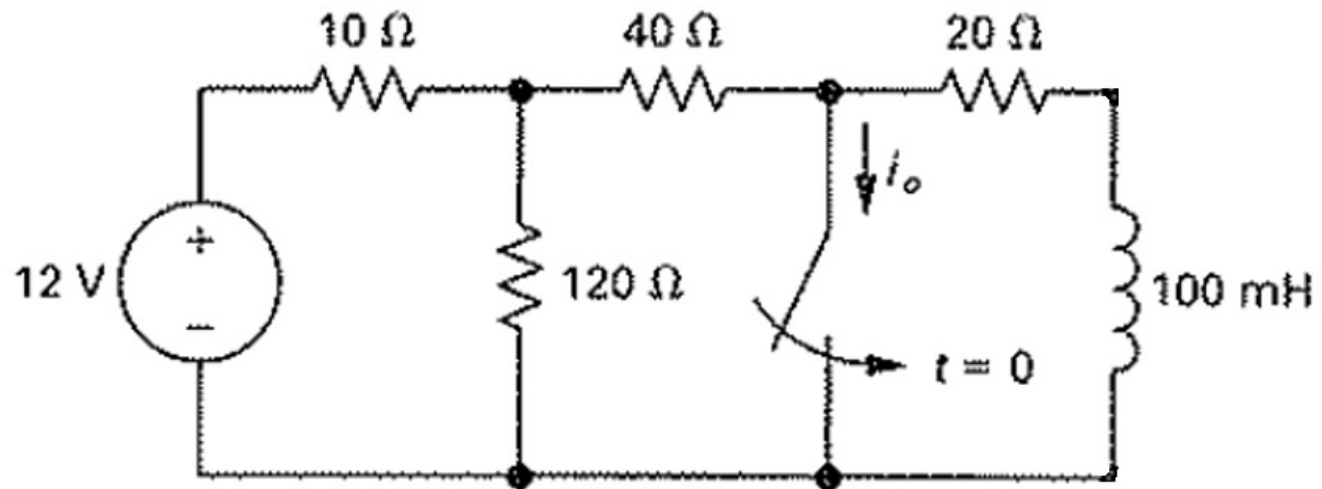

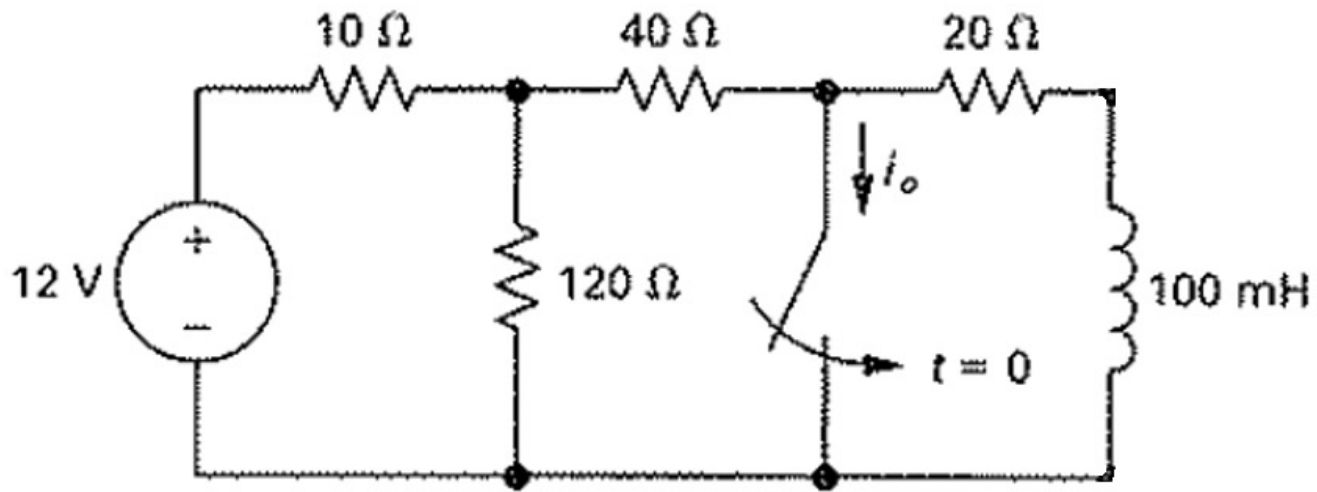


$$i_o(t) = -\frac{8}{50} e^{-200t} + \frac{9}{40} \text{ A}$$

Practice problem: find $i(t)$

$$t < 0: 0 \text{ A}$$


$$0 < t < 5: -e^{-3t} + 1 \text{ A}$$

$$t > 5: -2e^{-2.25t} + 3 \text{ A}$$

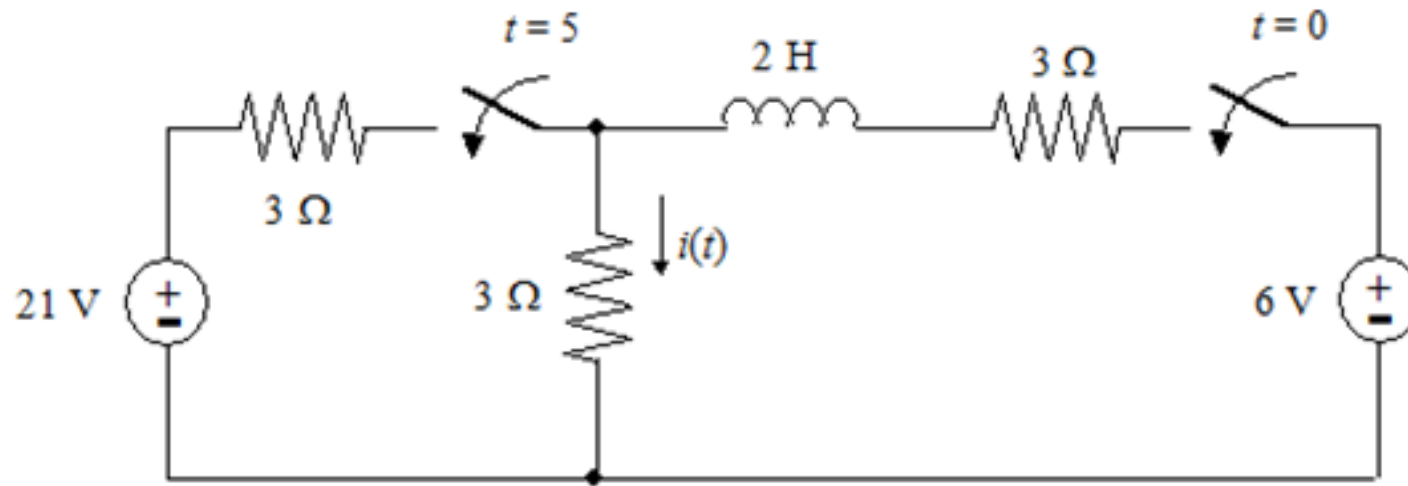


$$v(t) = -12e^{-t} \text{ V}$$

Practice problem: find $v(t)$, $t > 0$

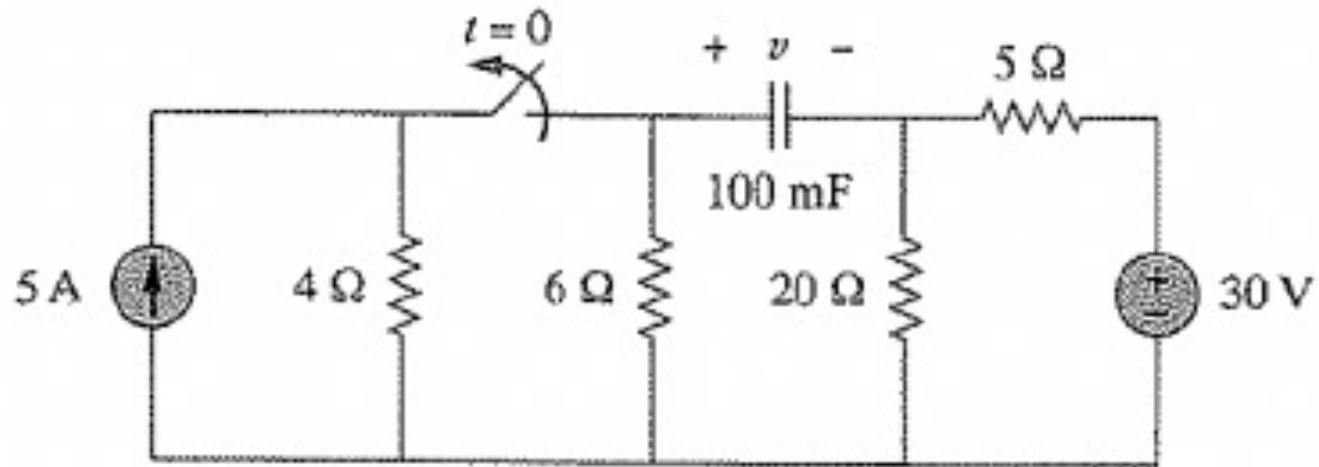

Practice problem: find $v_o(t)$, $t > 0$

$$v_o(t) = -16e^{-4000t} \text{ V}$$

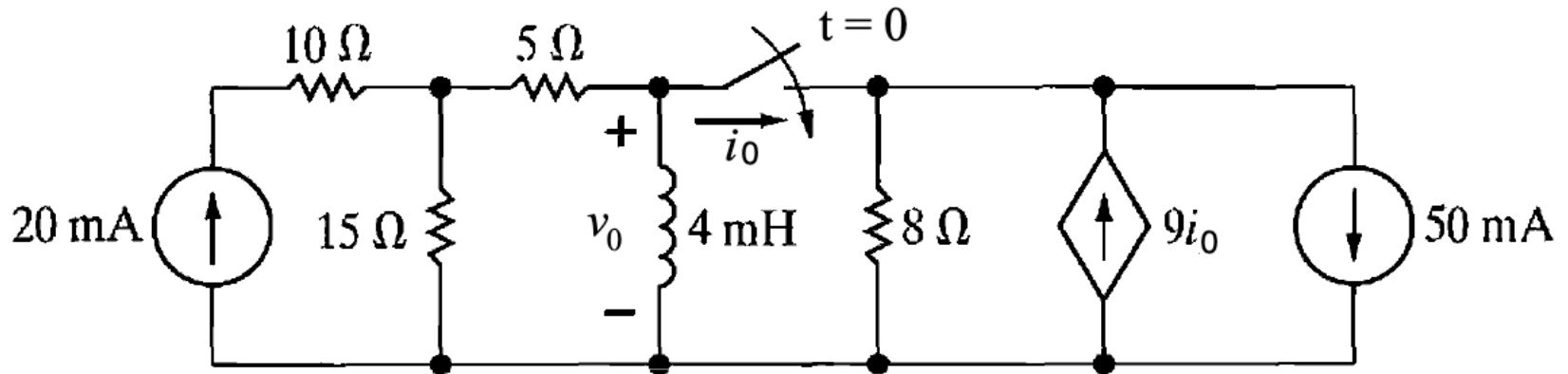

Practice problem: How much energy is stored in the capacitor at time $t = 0$? How much of this energy is dissipated by the $12\text{ k}\Omega$ resistor by time $t = 0.002$ seconds? How long does it take to dissipate 95% of the energy?

0.217 mJ
86.5 %
0.003 sec

