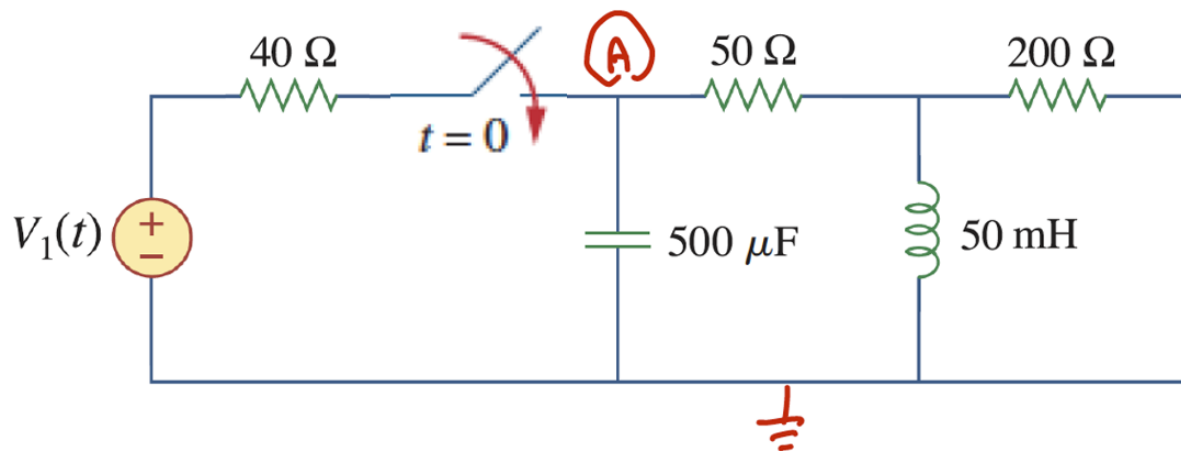


2nd Order Transients – 1

concepts

What happens with a second reactive component?


- Recall our prior example (during phasors intro)



we found $A(t) = a_0 + a_1 e^{-94.3t} + a_2 e^{-764t}$

How do we find a_0, a_1, a_2 ??

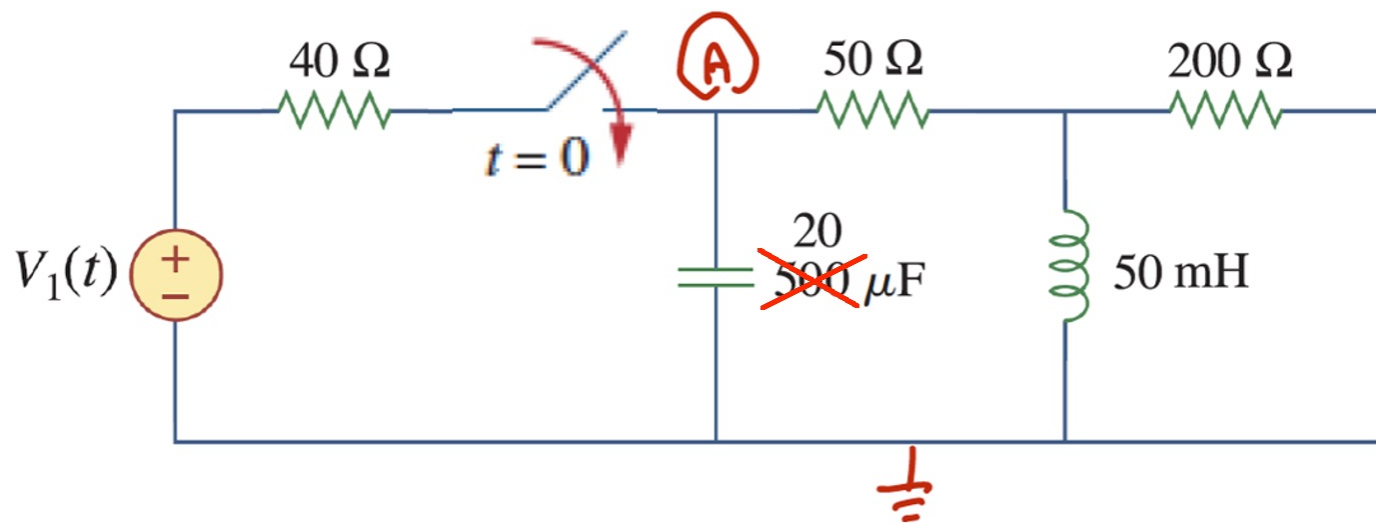And what if we decreased the capacitance?




– Characteristic polynomial becomes

$$s^2 + \mathbf{2,250} s + \mathbf{1,800,000} = 0$$

$$s = -1,125 \pm j 731$$

$$A(t) = \frac{5}{9} V_1 + a_1 e^{-1125t} \cos 731t + a_2 e^{-1125t} \sin 731t$$

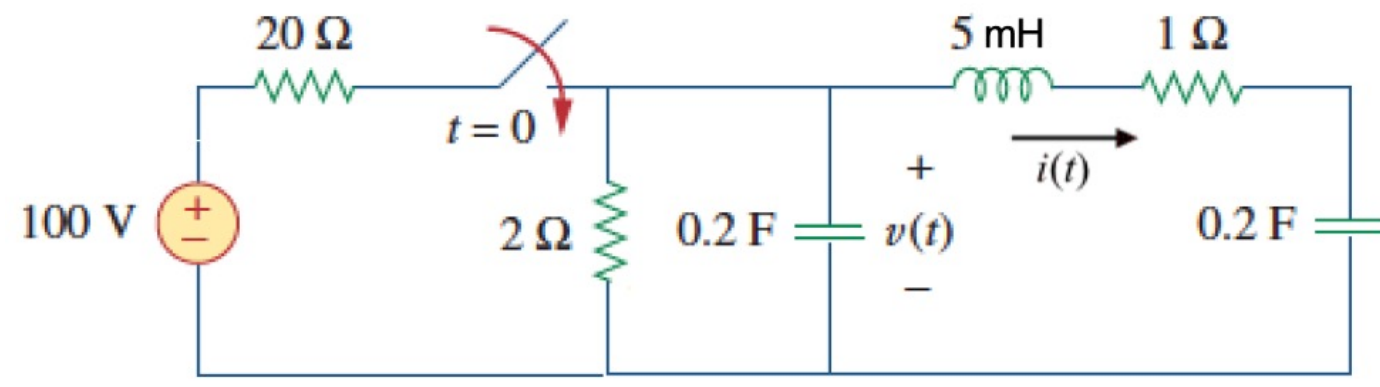
Or added more reactive components circuit:



- Define node voltage $v(t)$ and branch current $i(t)$
- KCL on the top node; solve for $i(t)$
- KVL on the right branch
- Substitute in for $i(t)$ and its derivatives
- Normalize:

See website for
the details
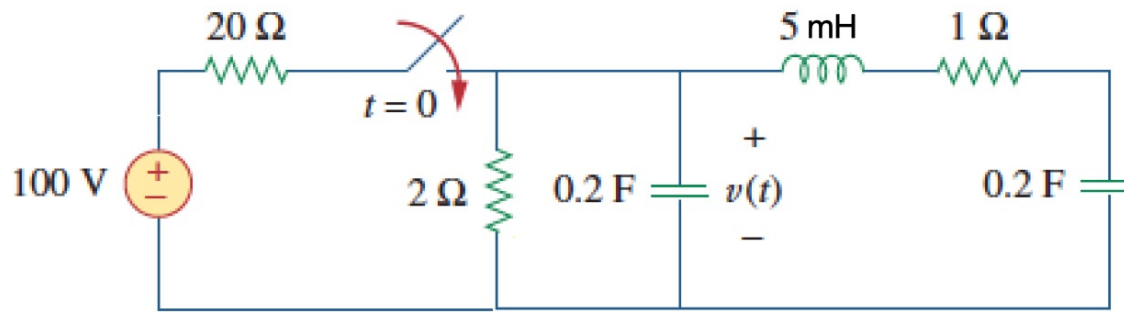
$$\frac{d^3 v}{dt^3} + 202.75 \frac{d^2 v}{dt^2} + 2550 \frac{dv}{dt} + 2750v + 250000 = 0$$



$$s^3 + 202.75 s^2 + 2550 s + 2750 = 0$$

$$v(t) = a_0 + a_1 e^{-1.19t} + a_2 e^{-12.2t} + a_3 e^{-189t}$$

– If we increase L to 25 mH:

$$v(t) = a_0 + a_1 e^{-1.19t} + a_2 e^{-20.8t} \cos 5.35t + a_3 e^{-20.8t} \sin 5.35t$$

The Takeaway

- Let n = count of distinct L's or C's (beyond trivial series or parallel combining)
- The differential equation/characteristic polynomial is n^{th} order and its coefficients depend upon the circuit topology and the component values
- There are $n+1$ terms in the solution, the steady state value and a term for each root of the characteristic polynomial, each with an unknown constant
 - Individual exponentials (real roots)
 - Pairs of exponentials with cosine or sine (complex)
- We use the n initial conditions on the inductor currents and capacitor voltages to solve for the n unknown coefficients

The Takeaway

- Let n = count of distinct L's or C's (beyond trivial series or parallel combining)
- The differential equation/characteristic polynomial is n^{th} order and its coefficients depend upon the circuit topology and the component values
- There are $n+1$ terms in the solution, the steady state value and a term for each root of the characteristic polynomial, each with an unknown constant
 - Individual exponentials (real roots)
 - Pairs of exponentials with cosine or sine (complex)
- We use the n initial conditions on the inductor currents and capacitor voltages to solve for the n unknown coefficients

The Takeaway


- Let n = count of distinct L's or C's (beyond trivial series or parallel combining)
- The differential equation/characteristic polynomial is n^{th} order and its coefficients depend upon the circuit topology and the component values
- There are $n+1$ terms in the solution, the steady state value and a term for each root of the characteristic polynomial, each with an unknown constant
 - Individual exponentials (real roots)
 - Pairs of exponentials with cosine or sine (complex)
- We use the n initial conditions on the inductor currents and capacitor voltages to solve for the n unknown coefficients

The Takeaway

- Let n = count of distinct L's or C's (beyond trivial series or parallel combining)
- The differential equation/characteristic polynomial is n^{th} order and its coefficients depend upon the circuit topology and the component values
- There are $n+1$ terms in the solution, the steady state value and a term for each root of the characteristic polynomial, each with an unknown constant
 - Individual exponentials (real roots)
 - Pairs of exponentials with cosine or sine (complex)
- We use the n initial conditions on the inductor currents and capacitor voltages to solve for the n unknown coefficients

Focus – 2 “simple” RLC circuits

Parallel:

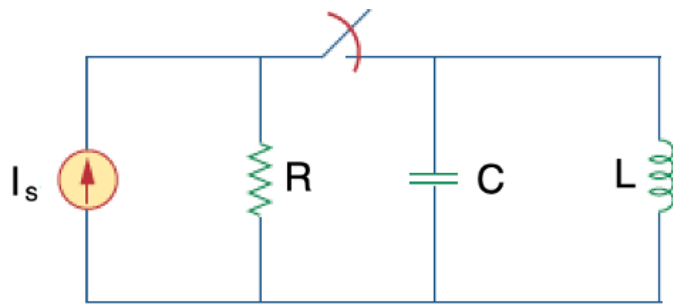


• *KCL*:

$$I_s + \frac{v}{R} + \frac{1}{L} \int^t v(s) ds + C \frac{dv}{dt} = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

Series:

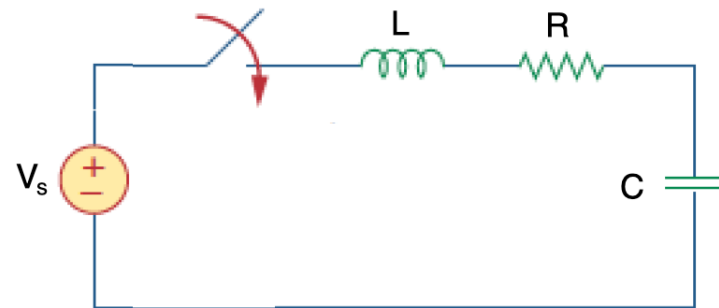

• *KVL*:

$$-V_s + Ri + L \frac{di}{dt} + \frac{1}{C} \int^t i(s) ds = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Standard notation

• Generally, $\frac{d^2x}{dt^2} + 2\alpha \frac{dx}{dt} + \omega_0^2 x = 0$

$$\alpha = \begin{cases} \frac{R}{2L} & ; \text{ series} \\ \frac{1}{2RC} & ; \text{ parallel} \end{cases} \quad \omega_0^2 = \frac{1}{LC}$$

• For $s^2 + 2\alpha s + \omega_0^2 = 0$ the homogeneous solution is

$$x(t) = Ae^{st}$$

with two values for s :

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

- Two negative real roots (s_1, s_2): (over-damped)

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

- Two equal roots (s): (critically damped)

$$x(t) = D_1 t e^{st} + D_2 e^{st} + x_\infty$$

- Complex conjugate roots ($-\alpha \pm j\omega_d$): (under-damped)

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

The “time” constant

- 1st order solution

$$x(t) = A e^{-t/\tau} + x(\infty)$$

– Transient gone in about 4τ


- 2nd order solution

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x(\infty)$$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x(\infty)$$

– duration depends upon s_1, s_2 or α

Example:

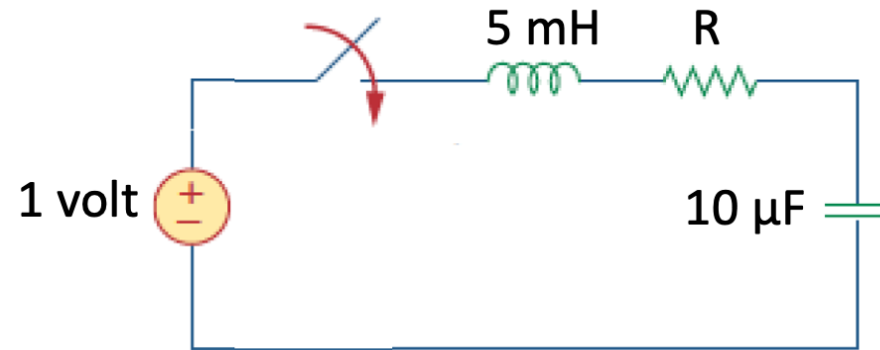

Find the form of the capacitor voltage $v(t)$ assuming $R = 100 \Omega$

Since series, the characteristic equation is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

or

$$s^2 + 20,000s + 2 \times 10^7 = 0$$


or


$$s = -18900, -1060$$

so

$$v(t) = A_1 e^{-18,900t} + A_2 e^{-1060t} + v_\infty$$

Determines rate

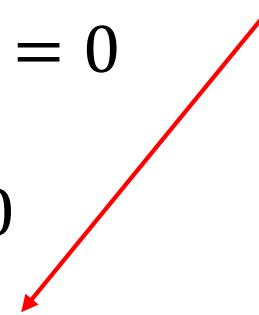

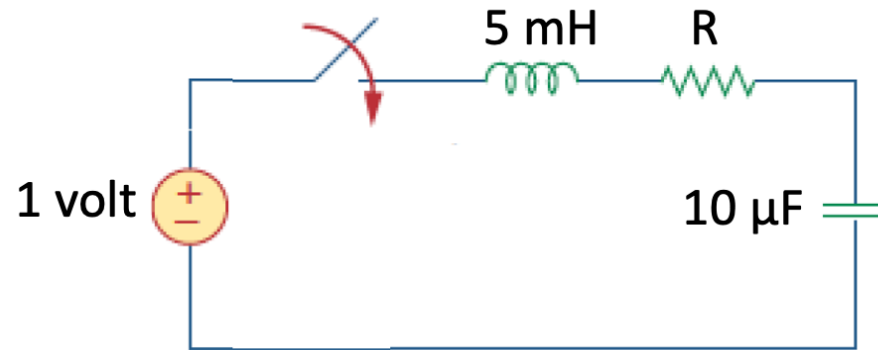

- What is R is reduced to 5 Ω ?

$$s^2 + 1000s + 2 \times 10^7 = 0$$


or


$$s = -500 \pm j 4440$$

so


$$v(t) = B_1 e^{-500t} \cos 4440t + B_2 e^{-500t} \sin 4440t + v_\infty$$

Determines rate

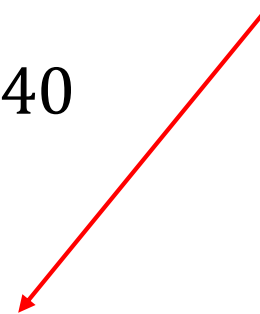

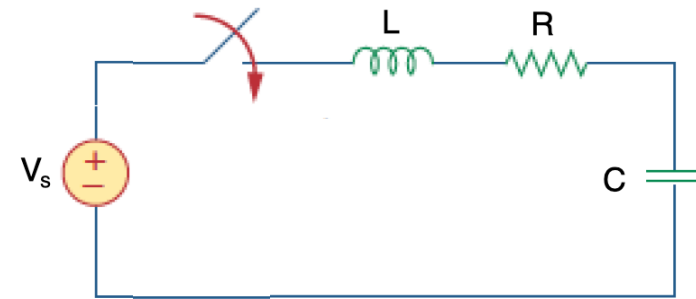

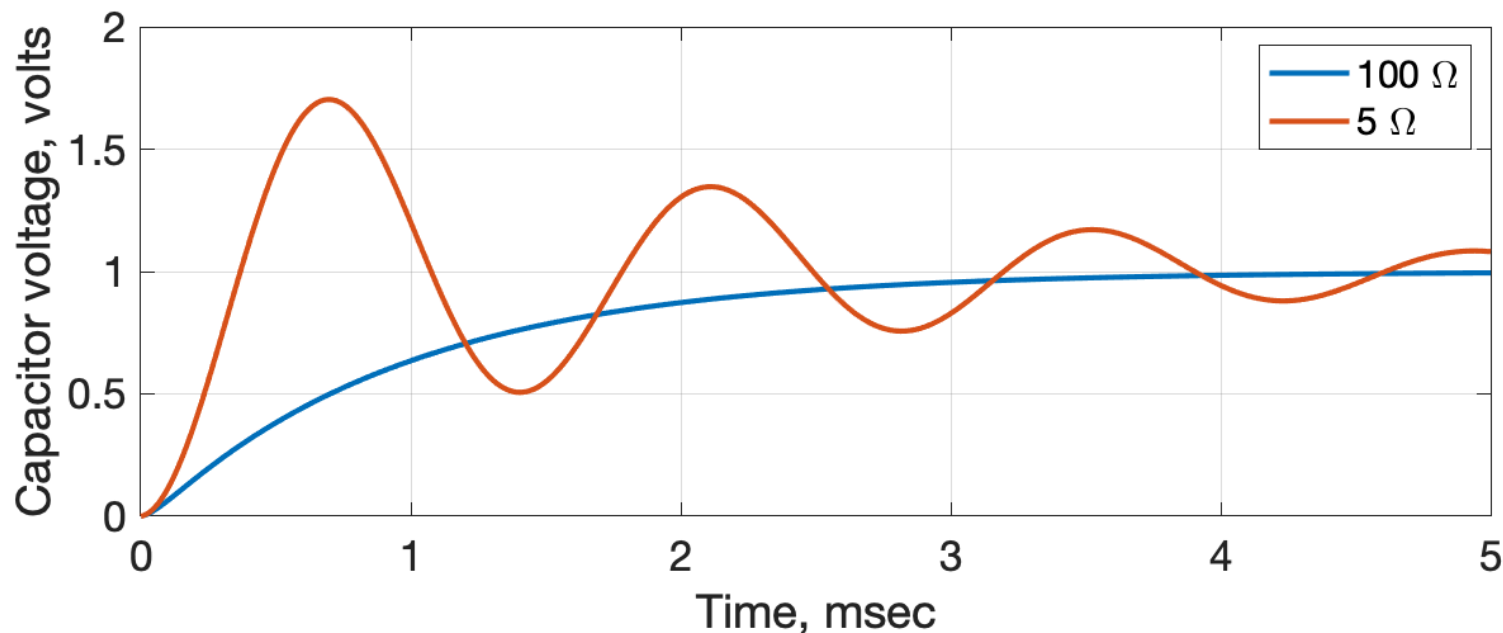
- Blue: $R = 100 \Omega$, overdamped
- Red: $R = 5 \Omega$, underdamped



- Goals for the next few days – find the **details** of these solution, including evaluation of unknown constants

Practice problem: a parallel RLC circuit consists of a $5000\ \Omega$ resistor, a $1.25\ \text{H}$ inductor, and an $8\ \text{nF}$ capacitor.

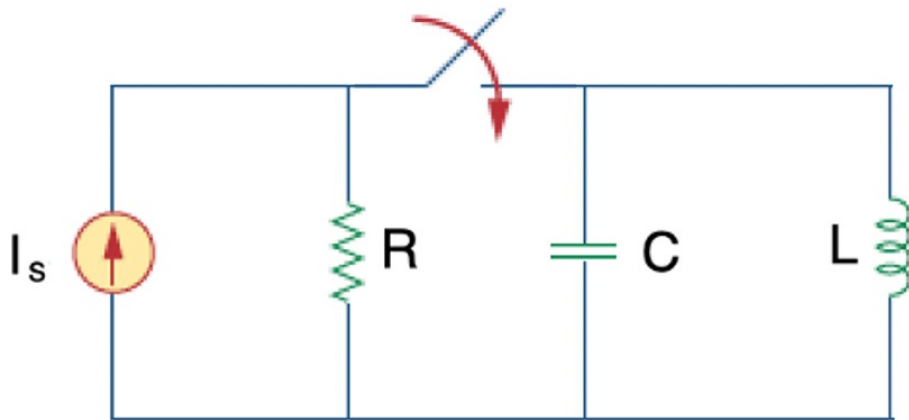
- Find the roots of the characteristic equation
- Is the response over-damped or under-damped?
- How would you need to change the resistance to get the other form of damping?



$-20,000, -50,;$ over, $R > 6250\ \Omega$

Practice problem: a series RLC circuit consists of the same 5000 Ω resistor, 1.25 H inductor, and 8 nF capacitor.

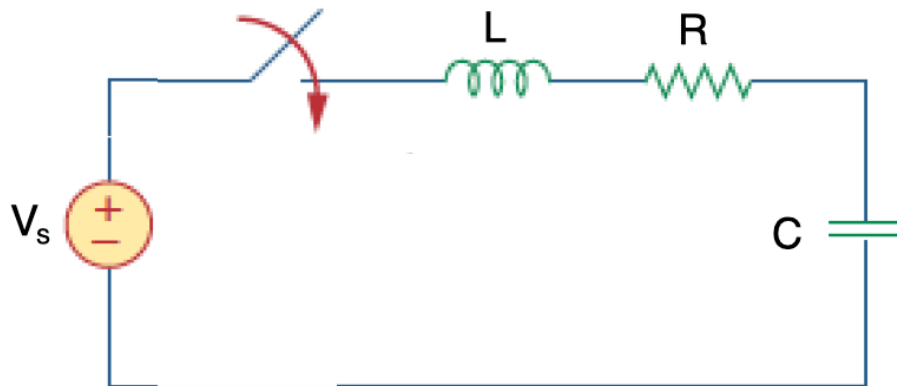- Find the roots of the characteristic equation
- Is the response over-damped or under-damped?
- How would you need to change the resistance to get the other form of damping?



$-2000 \pm j 9798$; under, $R > 25,000 \Omega$