


2nd Order Transients – 2

Form; more resistances;
initial and final conditions

So far, for “simple” RLC circuits


- Step 1 – identify type and form characteristic polynomial

Parallel

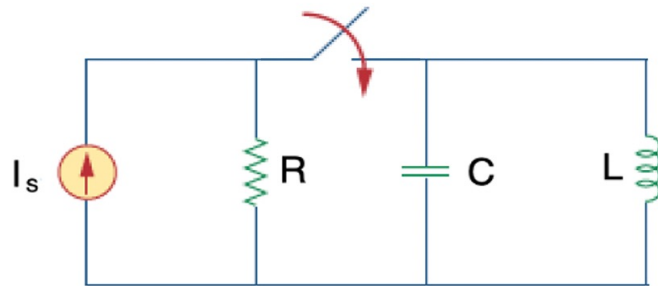

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Series

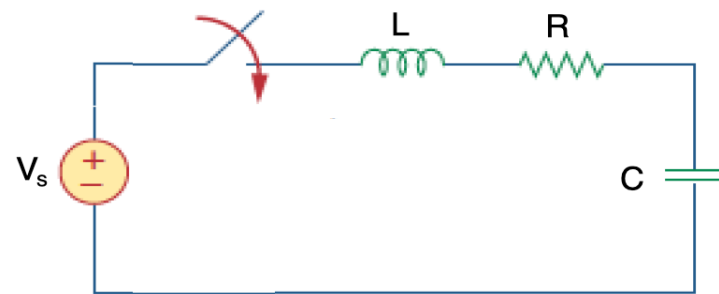

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- Step 2 – based on real vs complex roots, identify form of solution

Real roots:



$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

Complex roots:


$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

- Step 3 – use final value to evaluate x_∞
- Step 4 – the other constants?

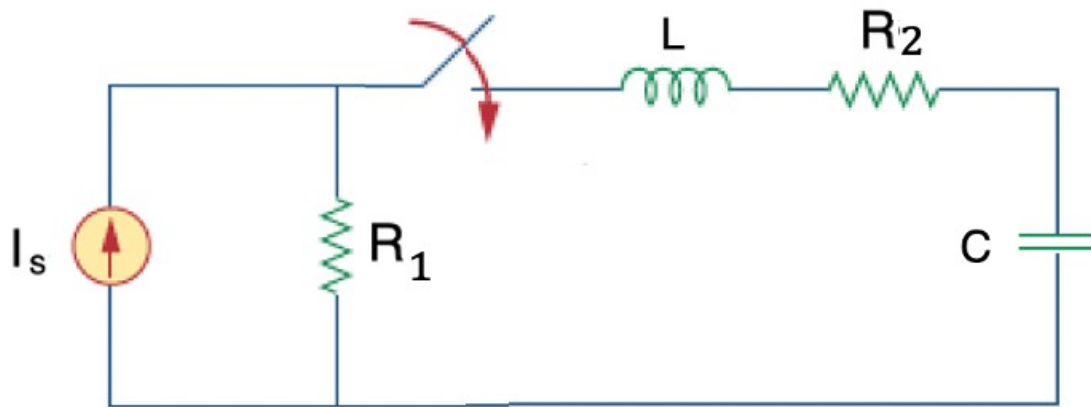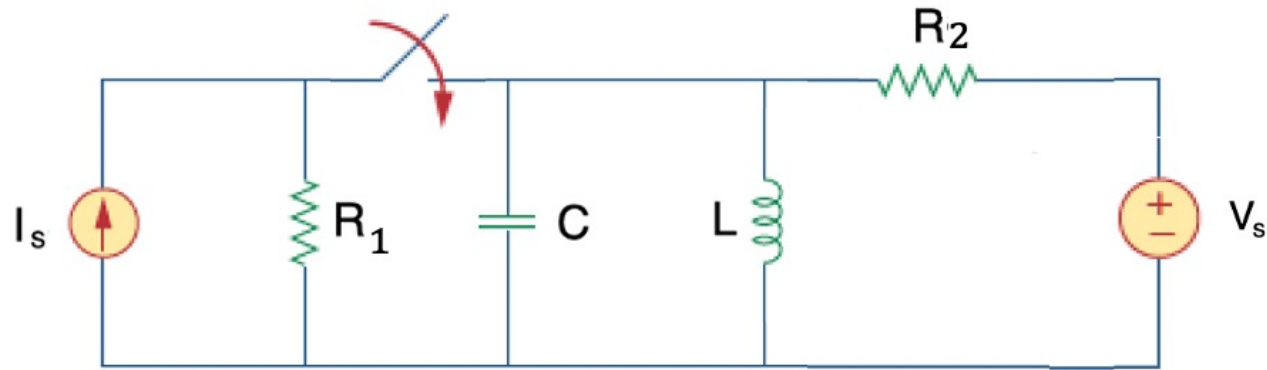
- Aside – what if we add an extra resistor?



- Or several?

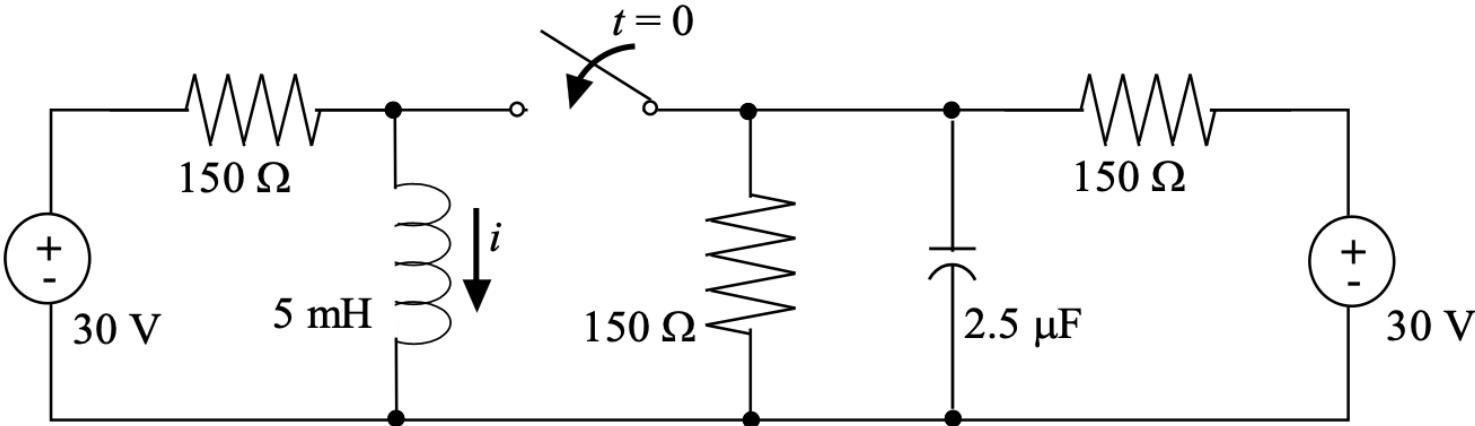

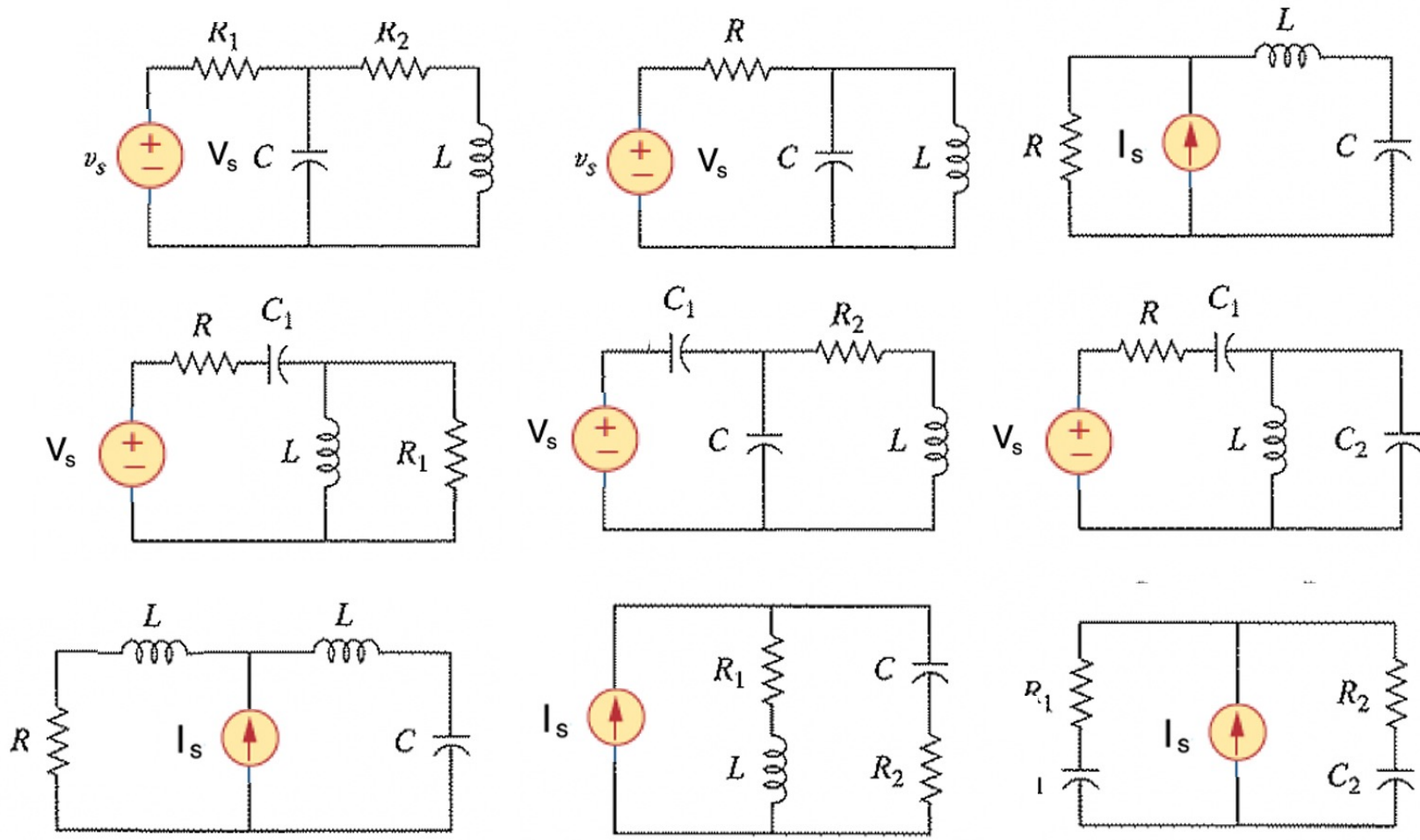
Question: Which of these circuits match our assumed 2nd order RLC circuit form? If yes, which form, series or parallel?



Initial and Final Conditions

- Just like the 1st order case:
 - From a DC analysis based on “open” or “short” models for C and L both before and after the switch event
 - Before switching event yields initial values
 - After switching event yields final values

Example:

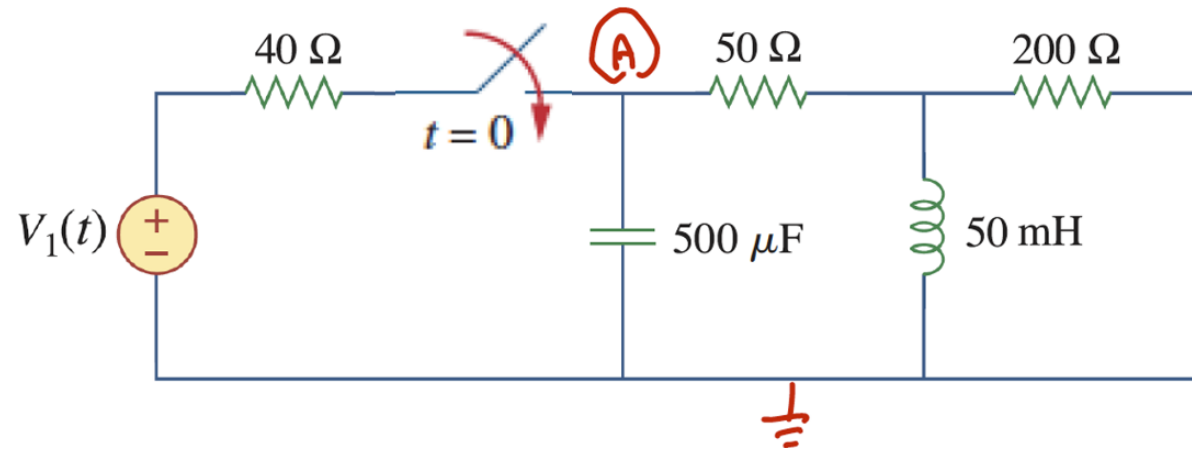


$$A(t) = a_0 + a_1 e^{-94.3t} + a_2 e^{-764t}$$

- $A(0) = 0$
- $A(\infty) = \frac{5}{9} V_1$


$$a_0 = \frac{5}{9} V_1$$

$$a_0 + a_1 + a_2 = 0$$

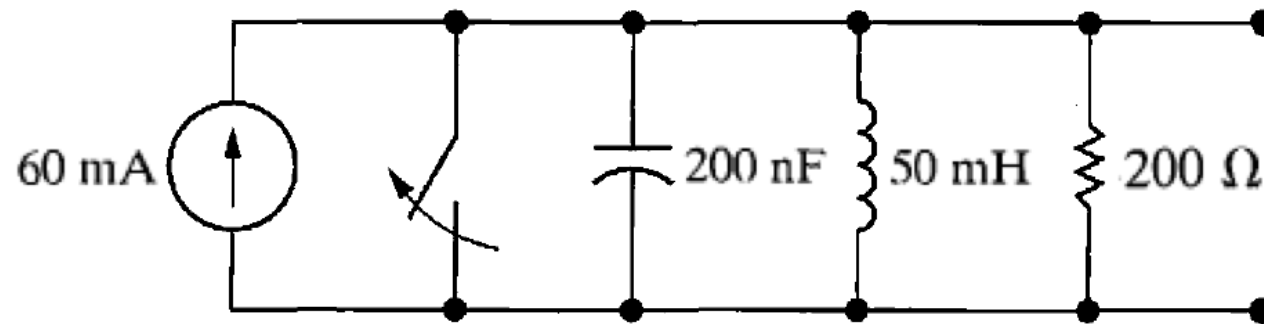
Example: Find the initial/final conditions



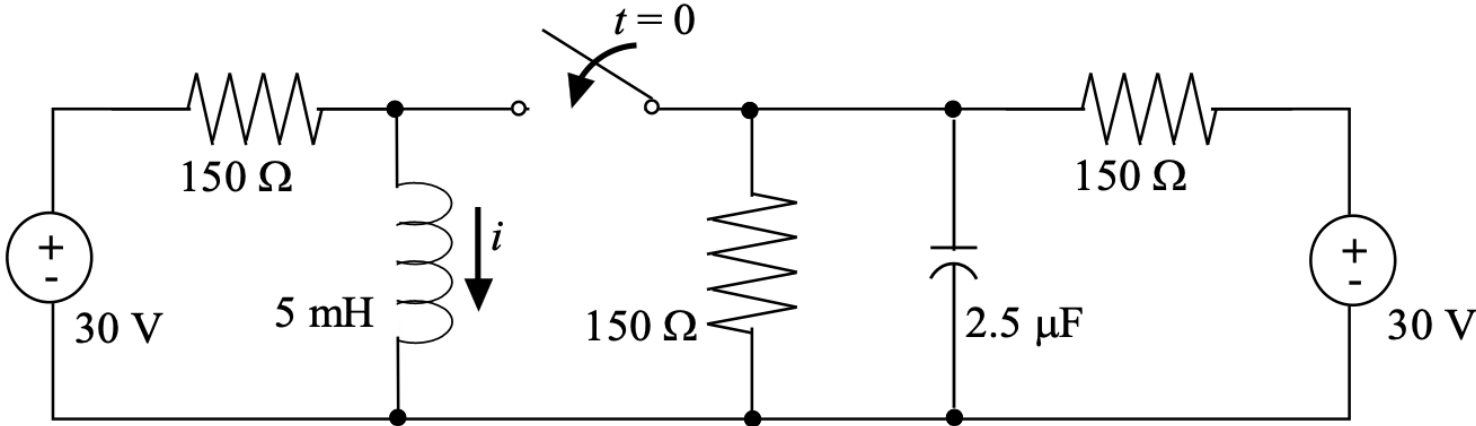
Example: Find the initial/final conditions




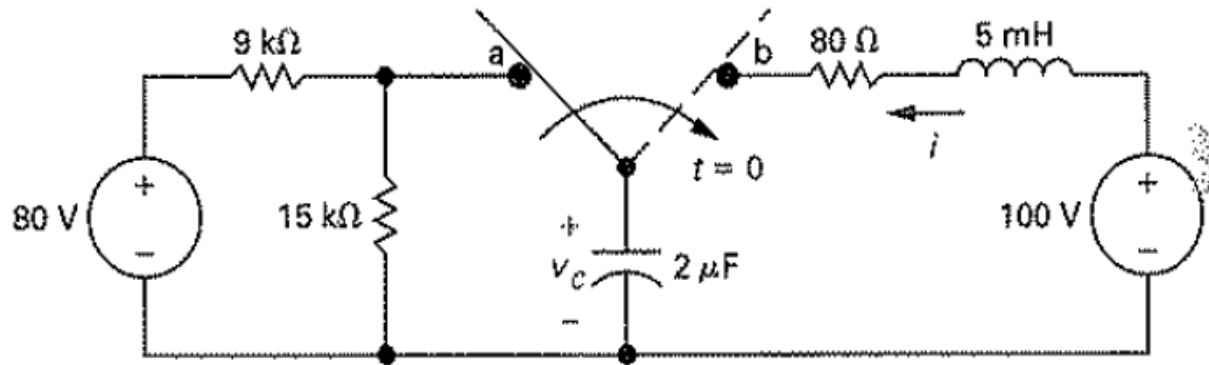Example: Find the initial/final conditions



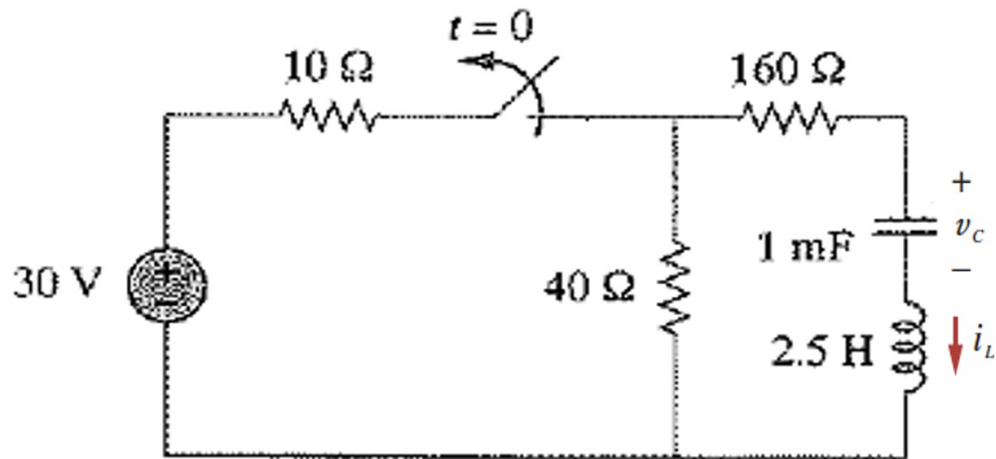Practice problem: Find the form of solution and the initial/final conditions



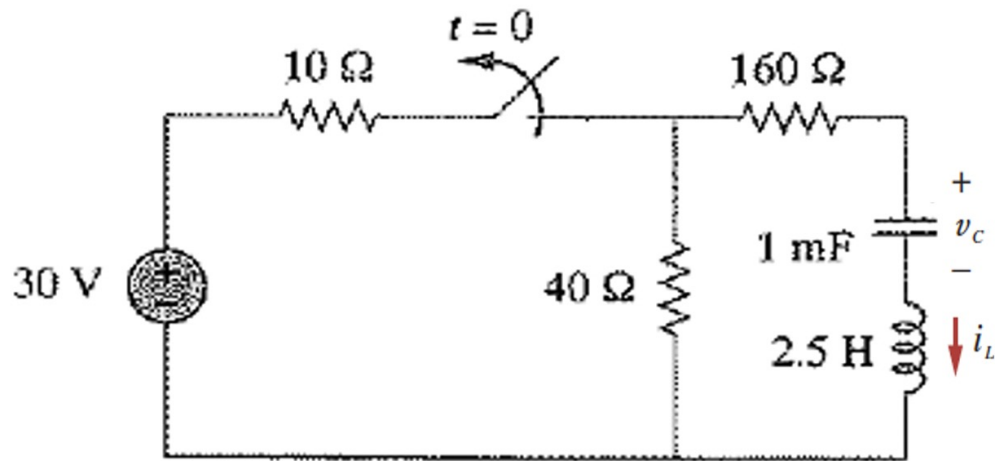

$$x(t) = A_1 e^{-5.36t} + A_2 e^{-74.6t} + x_\infty$$


$$i_L(0) = 0 \text{ A}$$


$$i_L(\infty) = 0 \text{ A}$$

$$v_C(0) = 24 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

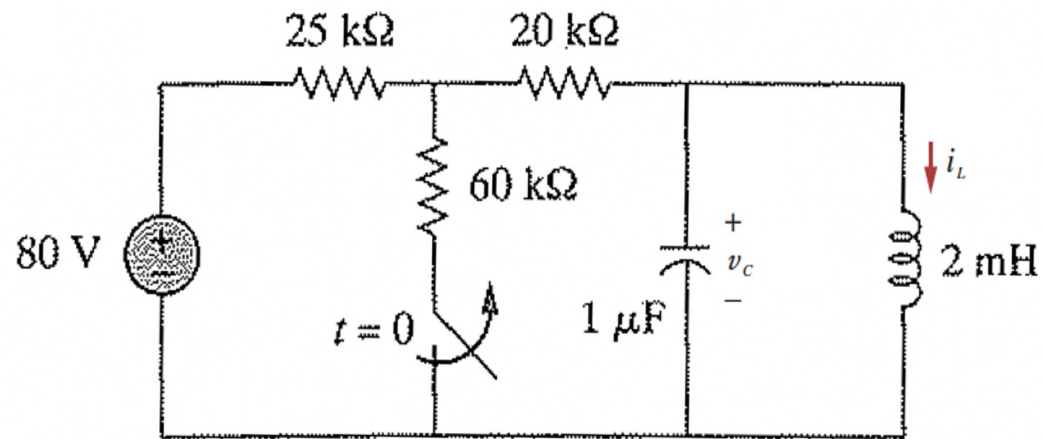Practice problem: Find the form of solution and the initial/final conditions



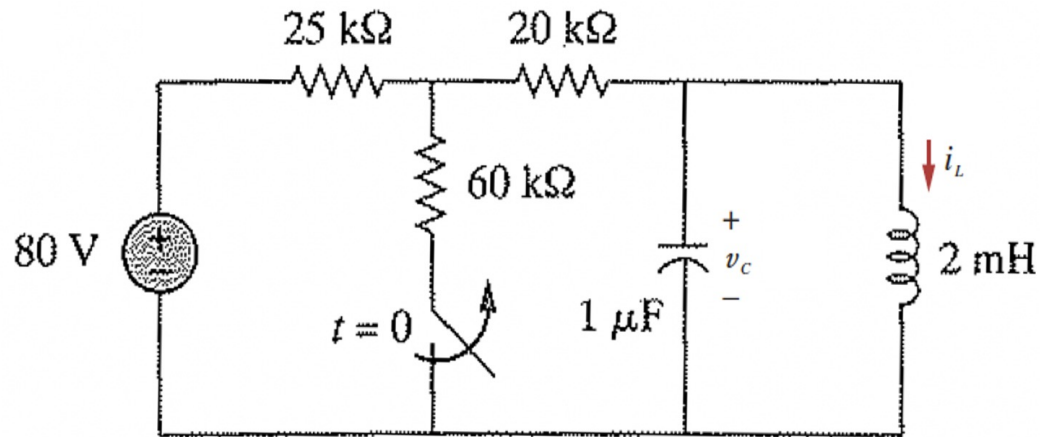

$$x(t) = B_1 e^{-11.1t} \cos 22361t + B_2 e^{-11.1t} \sin 22361t + x_\infty$$


$$i_L(0) = 1.5 \text{ A}$$


$$i_L(\infty) = \frac{16}{9} \text{ A}$$

$$v_C(0) = 0 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

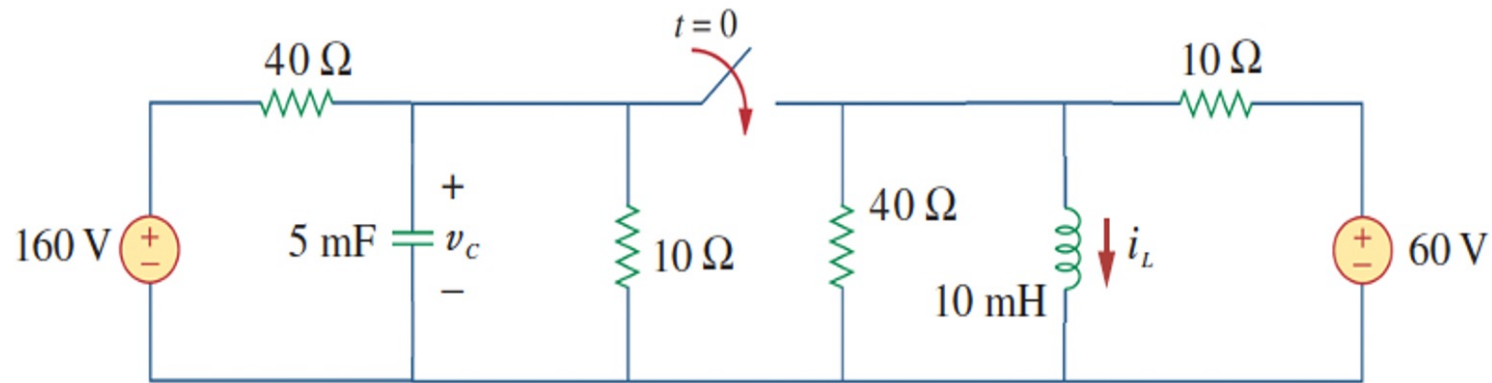Practice problem: Find the form of solution and the initial/final conditions



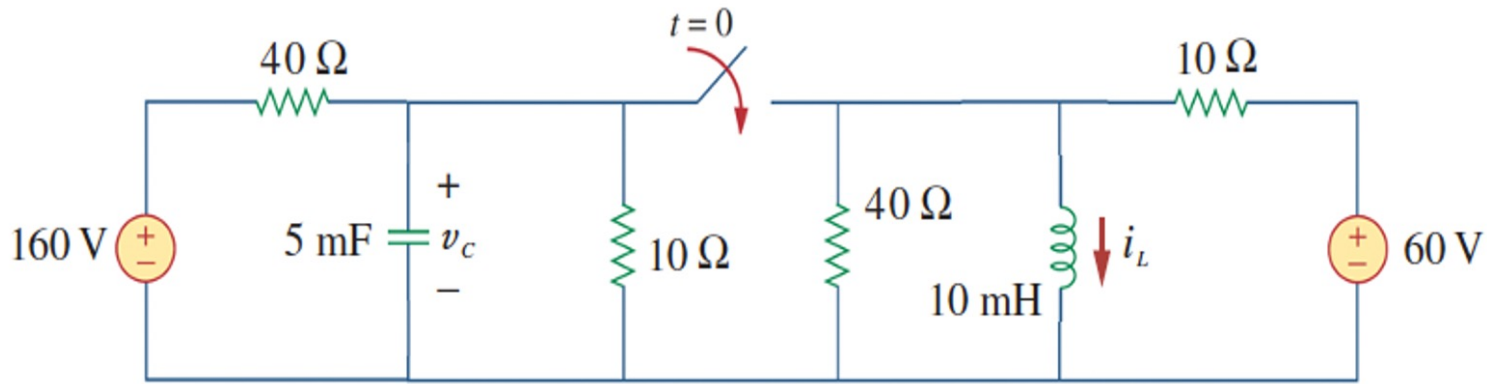

$$x(t) = B_1 e^{-25t} \cos 139t + B_2 e^{-25t} \sin 139t + x_\infty$$

$$\begin{aligned} i_L(0) &= 6 \text{ A} \\ i_L(\infty) &= 10 \text{ A} \\ v_C(0) &= 32 \text{ V} \\ v_C(\infty) &= 0 \text{ V} \end{aligned}$$