

# 2<sup>nd</sup> Order Transients – 3

the full solution

# How to find the constants?

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

- $x_\infty$  is easy
  - Short inductor, open capacitor, solve DC problem
- Initial condition ( $v_C(0)$  or  $i_L(0)$ ) is not enough

$$x(0) = A_1 + A_2 + x_\infty$$

$$x(0) = B_1 + x_\infty$$

Approach: include a derivative condition at time 0

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$x'(t) = s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}$$

$$x'(0) = s_1 A_1 + s_2 A_2$$

use with  $x(0) = A_1 + A_2 + x_\infty$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

$$x'(t) = -\alpha B_1 e^{-\alpha t} \cos \omega_d t - \alpha B_2 e^{-\alpha t} \sin \omega_d t \\ - \omega_d B_1 e^{-\alpha t} \sin \omega_d t + \omega_d B_2 e^{-\alpha t} \cos \omega_d t$$

$$x'(0) = -\alpha B_1 + \omega_d B_2$$

use with  $x(0) = B_1 + x_\infty$

# Solving

- Overdamped (2 real roots,  $s_1, s_2$ ):

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$A_1 = \frac{x'(0) - s_2[x(0) - x_\infty]}{s_1 - s_2}$$
$$A_2 = \frac{s_1[x(0) - x_\infty] - x'(0)}{s_1 - s_2}$$

- Underdamped (complex roots,  $-\alpha \pm j\omega_d$ ):

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

$$B_1 = x(0) - x_\infty$$

$$B_2 = \frac{x'(0) + \alpha[x(0) - x_\infty]}{\omega_d}$$

## Question – how do we get the derivative's value?

- Answer – Recall

For a capacitor


$$i = C \frac{dv}{dt}$$
$$\text{so } v'(0) = \frac{1}{C} i(0)$$


For an inductor

$$v = L \frac{di}{dt}$$
$$\text{so } i'(0) = \frac{1}{L} v(0)$$

Use KVL, KCL to get the capacitor current or inductor voltage

- Example – the parallel case

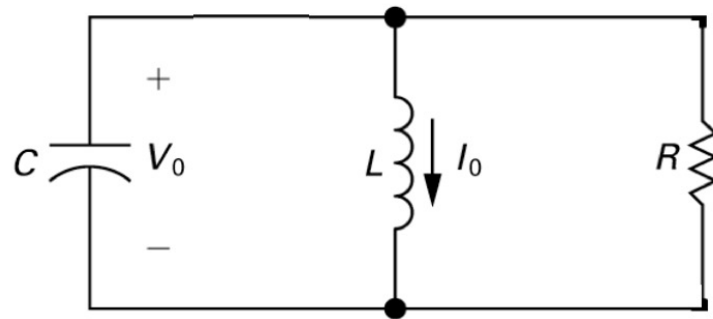

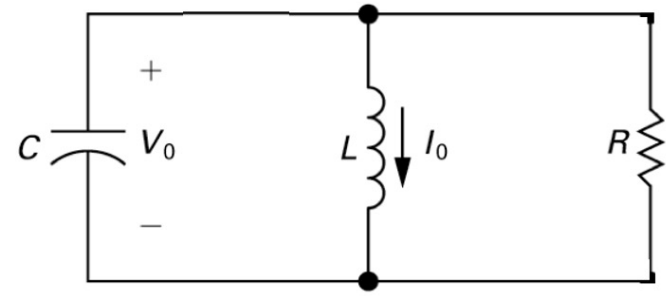

- Use KCL to find  $v_C'(0)$

$$i_C(t) + i_R(t) + i_L(t) = 0 \quad \rightarrow \quad C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} + i_L(t) = 0$$

$$v_C'(0) = -\frac{v_C(0)}{RC} - \frac{i_L(0)}{C}$$


- Use KVL to find  $i_L'(0)$

$$v_L(t) = v_C(t) \quad \rightarrow \quad L \frac{di_L(t)}{dt} = v_C(t)$$

$$i_L'(0) = \frac{v_C(0)}{L}$$

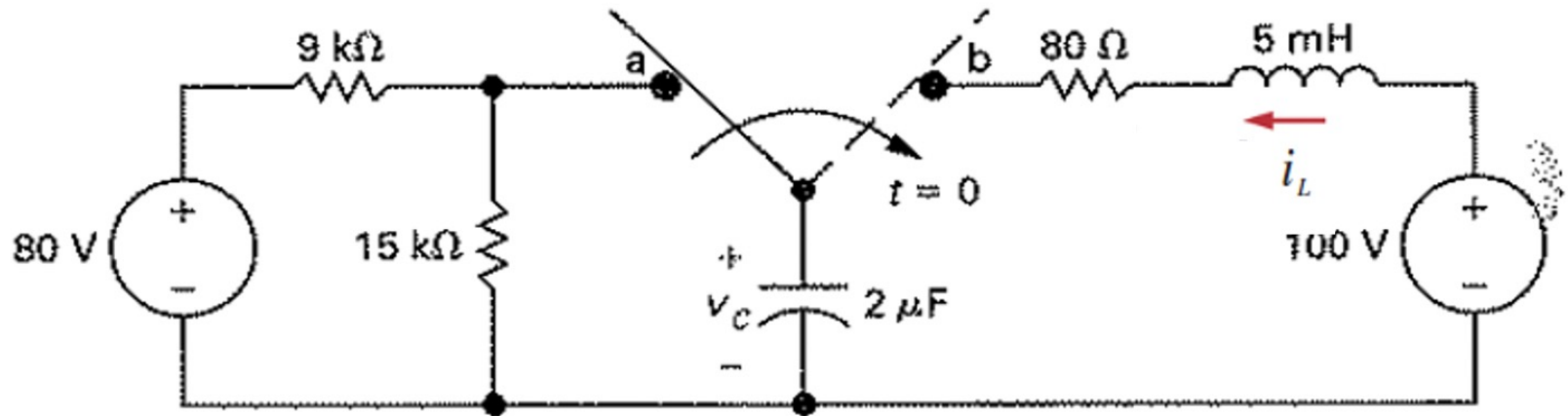
**Example:** Find the derivative conditions

$$i_L'(0) = -10,000 \text{ A/s}$$
$$v_C'(0) = 0 \text{ V/s}$$



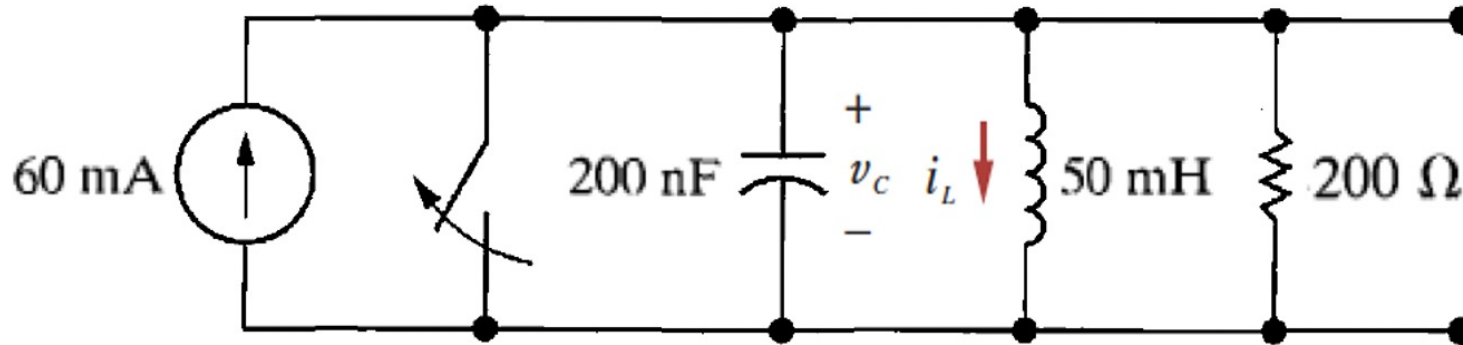**Example:** Find the derivative conditions

$$i_L'(0) = 0 \text{ A/s}$$
$$v_C'(0) = -300,000 \text{ V/s}$$






# Total Solution

1. Identify type (series/parallel) and values of R,L,C
2. Root characteristic equation, to find form
3. Find  $i_L(0)$  and  $v_C(0)$
4. For variable of interest, find  $x(0)$ ,  $x'(0)$ , and  $x(\infty)$
5. Assemble answer

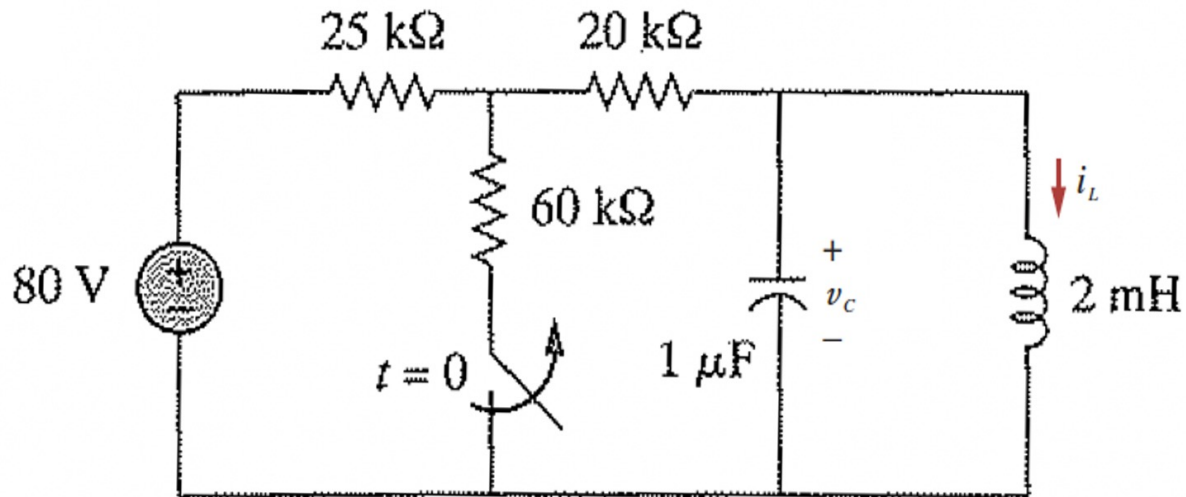**Example:** Find  $v_C(t)$

$$v_C(t) = -7.45 e^{-11.1t} \sin 22361t \text{ V}$$



# Cheat Sheet

Parallel:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Series:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Overdamped:

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$


$$A_1 = \frac{x'(0) - s_2[x(0) - x_\infty]}{s_1 - s_2} \quad A_2 = \frac{s_1[x(0) - x_\infty] - x'(0)}{s_1 - s_2}$$

Underdamped:

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$


$$B_1 = x(0) - x_\infty \quad B_2 = \frac{x'(0) + \alpha[x(0) - x_\infty]}{\omega_d}$$

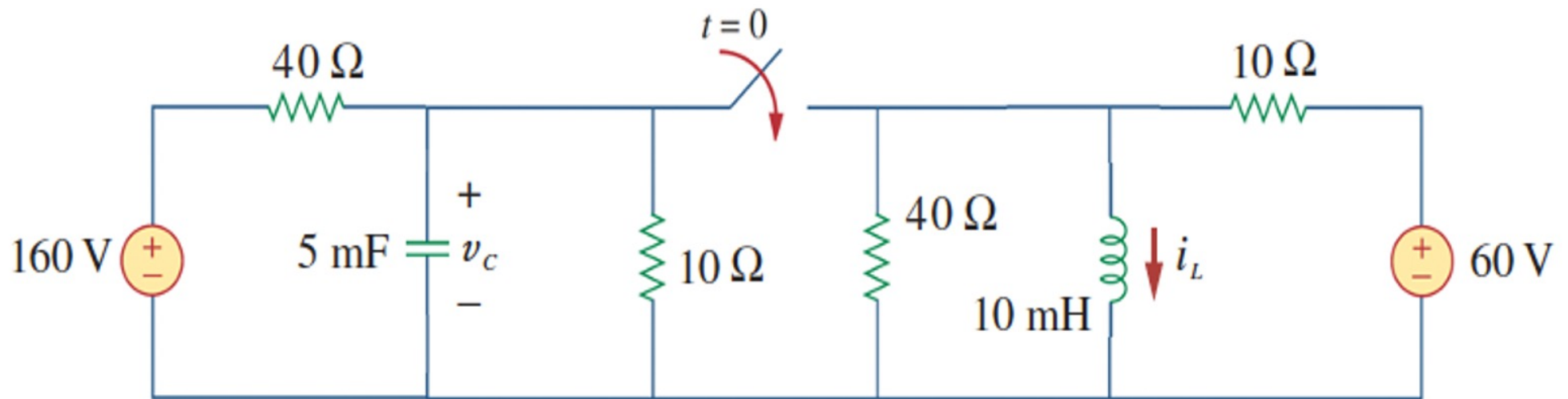**Practice problem:** Find the derivative conditions




$$i_L'(0) = 3200 \text{ A/s}$$
$$v_C'(0) = -800 \text{ V/s}$$

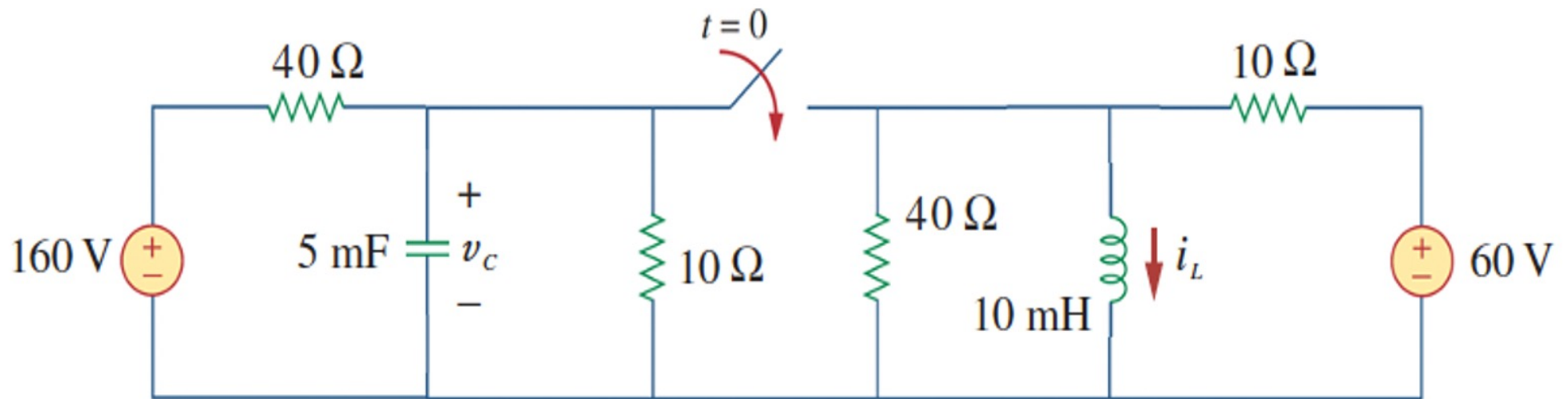**Practice problem:** Find the final form for  $i_L(t)$




$$i_L(t) = -4 e^{-25t} \cos 139t + 22.3 e^{-25t} \sin 139t + 10 \text{ A}$$

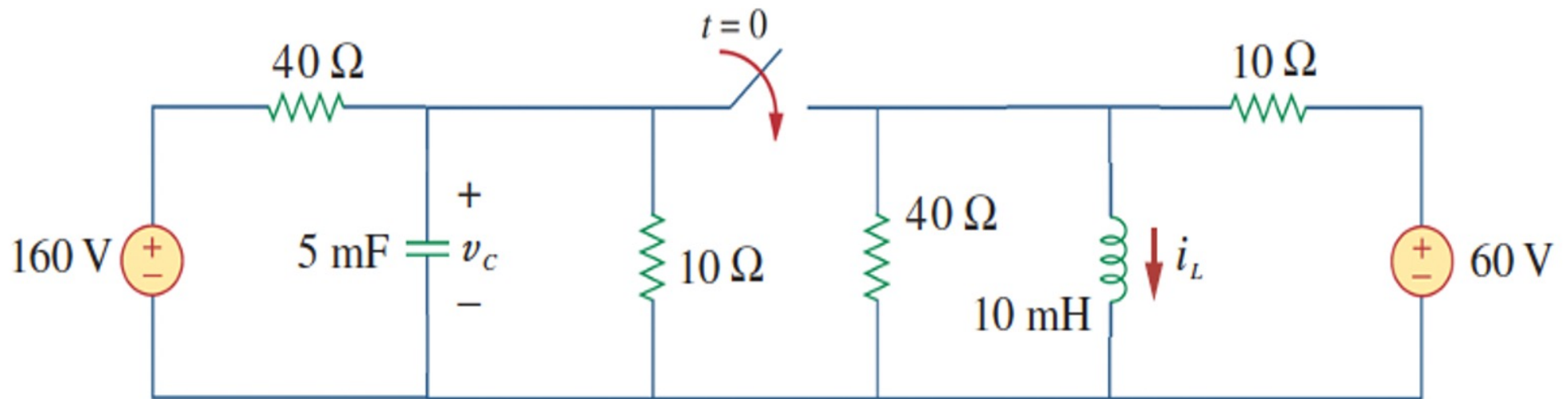**Practice problem:** Find the final form for  $v_C(t)$



$$v_C(t) = 32 e^{-25t} \cos 139t \text{ V}$$

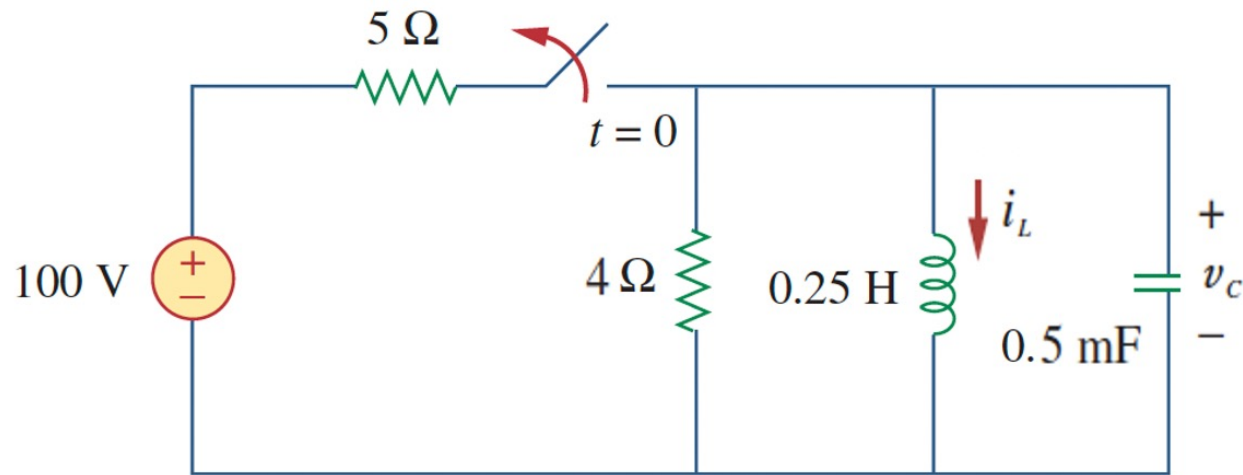
**Practice problem:** Find form and the initial, final, and derivative conditions



$$x(t) = A_1 e^{-16.6t} + A_2 e^{-483t} + x_\infty$$

$$\begin{aligned} i_L(0) &= 20 \text{ A} \\ i_L(\infty) &= 0 \text{ A} \\ i_L'(0) &= 0 \text{ A/s} \\ v_C(0) &= 0 \text{ V} \\ v_C(\infty) &= 0 \text{ V} \\ v_C'(0) &= -40,000 \text{ V/s} \end{aligned}$$

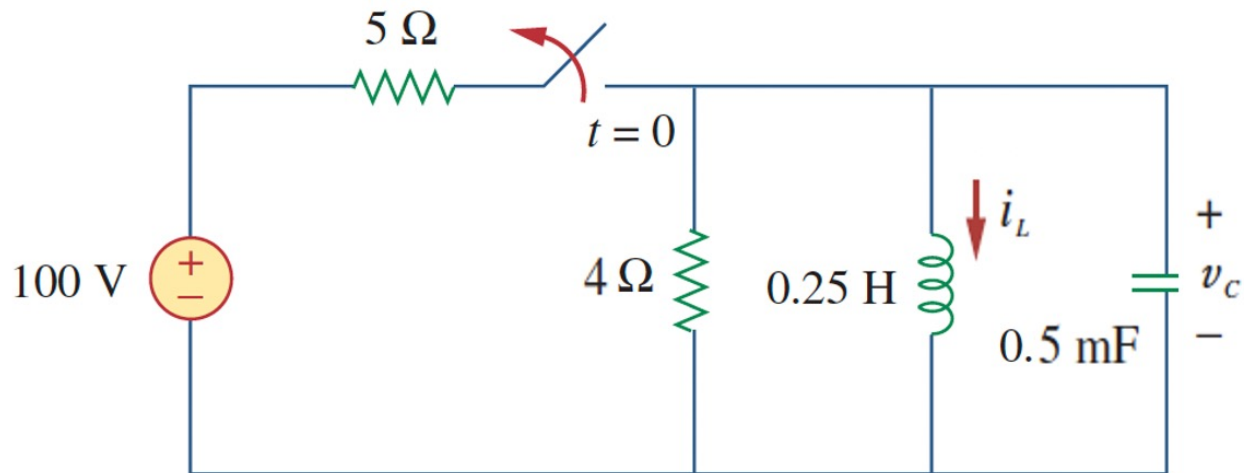
**Practice problem:** Find the final form for  $i_L(t)$



$$i_L(t) = 20.7e^{-16.6t} - 0.709e^{-483t} \text{ A}$$




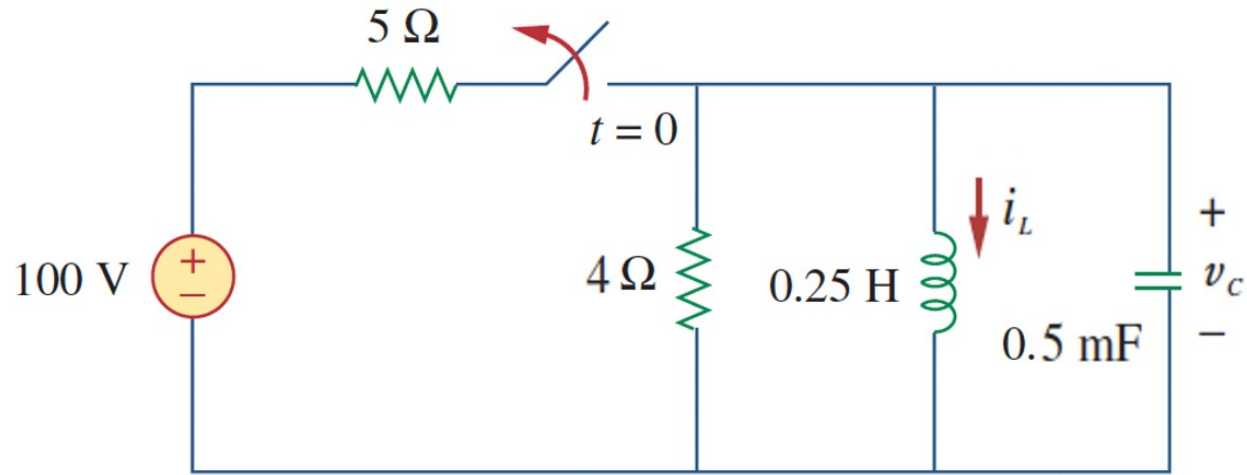**Practice problem:** Find the final form for  $v_C(t)$




$$v_C(t) = -85.7 e^{-16.6t} + 85.7 e^{-483t} \text{ V}$$

**Practice problem:** Find  $i_o(t)$

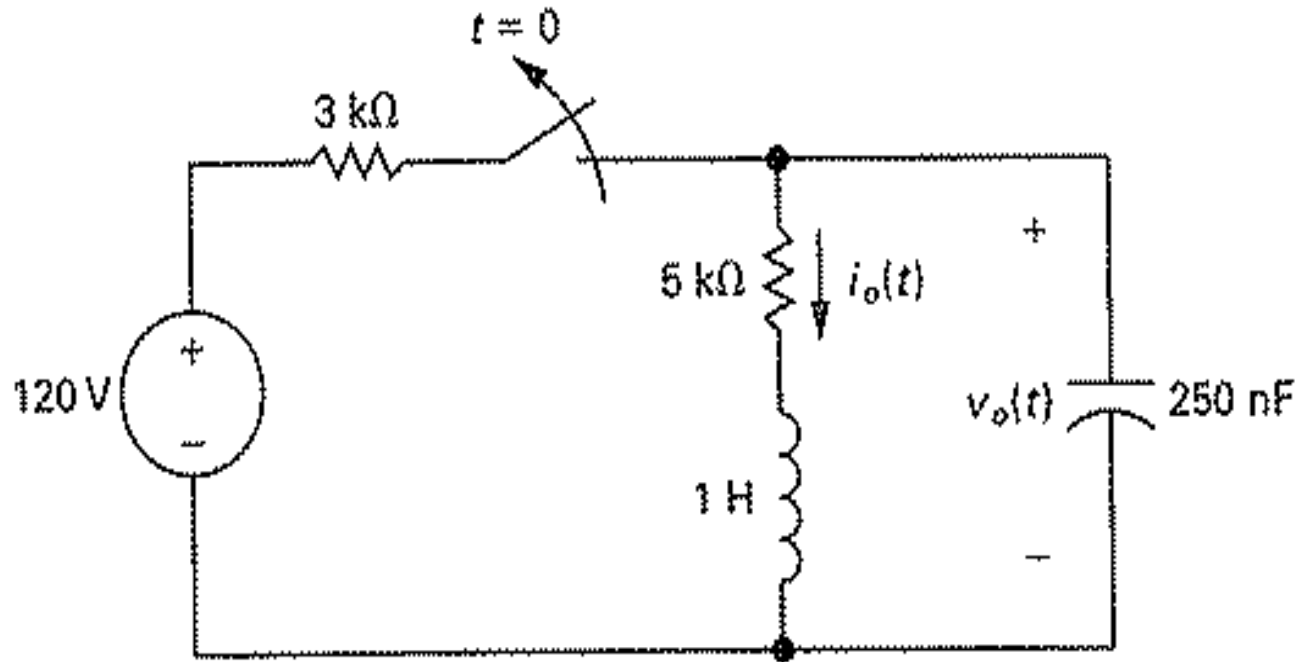

$$i_o(t) = 20 e^{-1000t} - 5 e^{-4000t} \text{ mA}$$

**Practice problem:** Find  $v(t)$

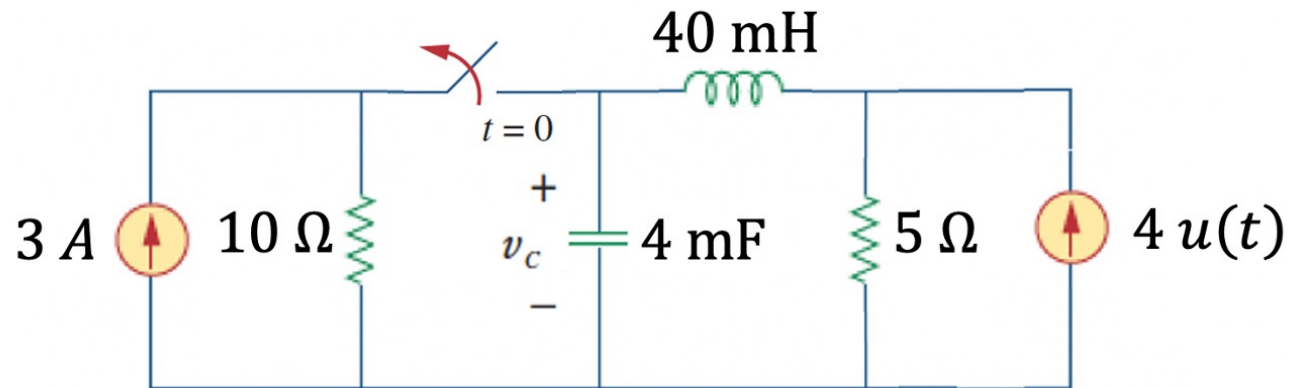

$$v(t) = 10 e^{-62.5t} \cos 48.4t + 2.58 \cdot e^{-25t} \sin 48.4t + 20\text{ A}$$