

Basics – 2


time variation; sources; resistors

Circuit Variables

Current	$i(t)$	amperes	directional
Voltage	$v(t)$	volts	directional
Power	$p(t) = v(t)i(t)$	watts	
Energy	$E(t)$	joules	

- Typically, these are time varying

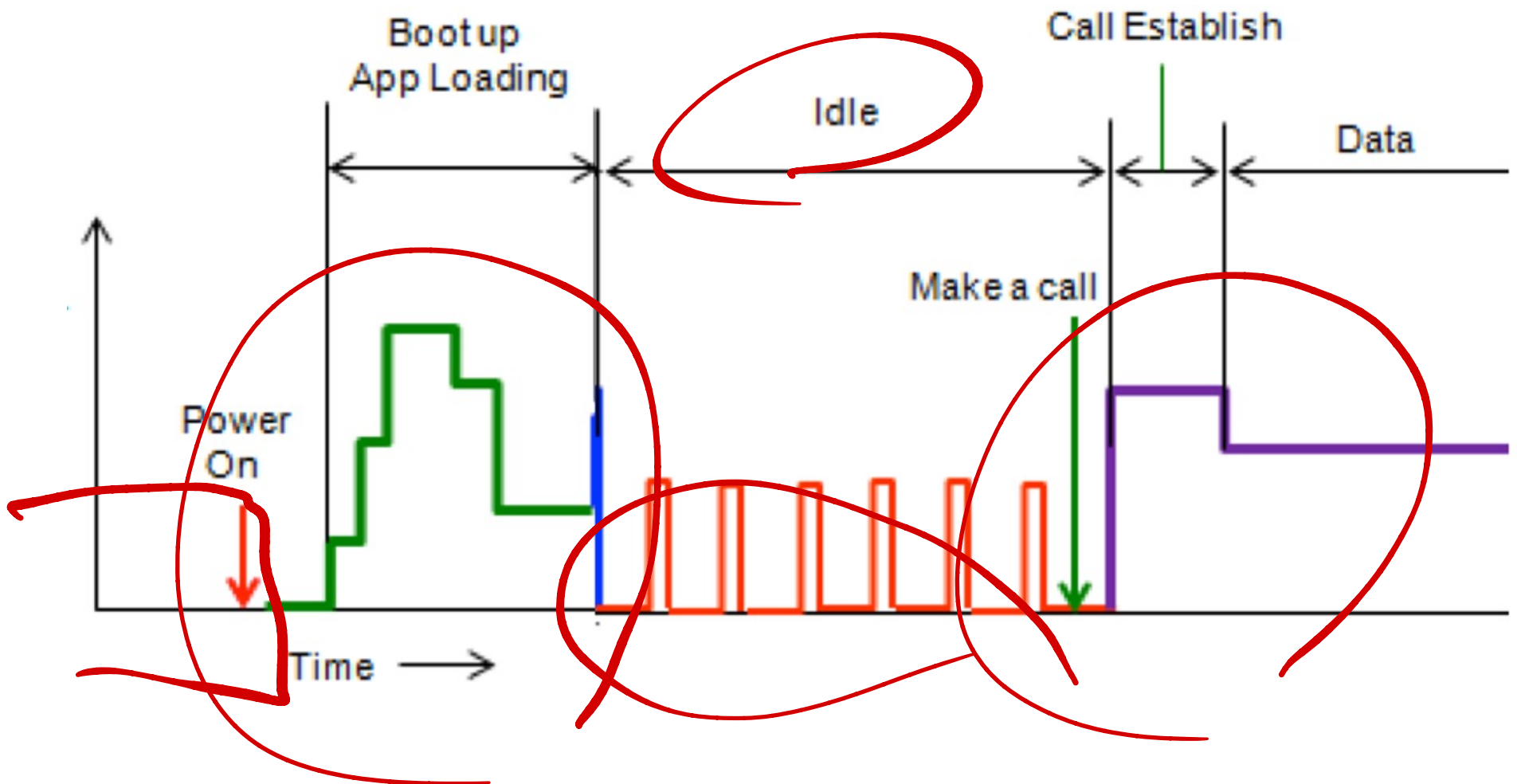- As an example – smart phone power usage



Example: I currently have a 3-year-old iMac on my desk with power consumption of 63 watts (idle) to 240 watts (active computing). A new iMac is better vis-à-vis power with levels of 43-84 Watts, respectively. Can I argue the \$1,600 price tag based upon the obvious energy savings?

- Answer:

- Assumptions:

- Low/high power usage for a typical day is 20/4
- Electricity rate of 18 cents/kWh


- Extra power over a year:

- High power: $365 * 4 * (240 - 84) = 228 \text{ kWh}$
- Low power: $365 * 20 * (63 - 43) = 146 \text{ kWh}$
- Savings per year = $(228 + 146) * 0.18 = \$67$

Example: The voltage and current at the terminals of a two-terminal circuit device for $t > 0$ seconds are

$$v(t) = 20 (1 - e^{-5t}) \text{ V}$$

$$i(t) = 10 e^{-5t} \text{ mA}$$

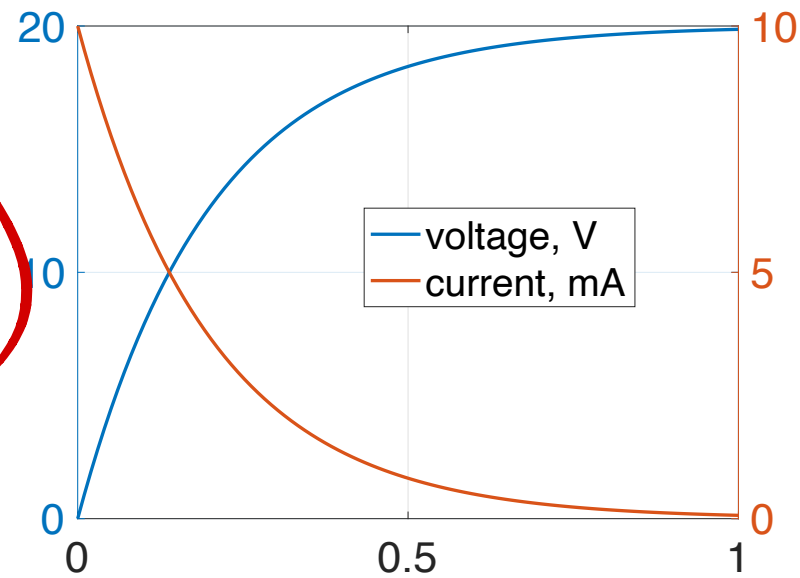


- At what time is the power being delivered to the device a maximum?
- What is that maximum?

- Answer:

- First, use the fact that power is the product of voltage and current

$$p(t) = v(t) * i(t)$$
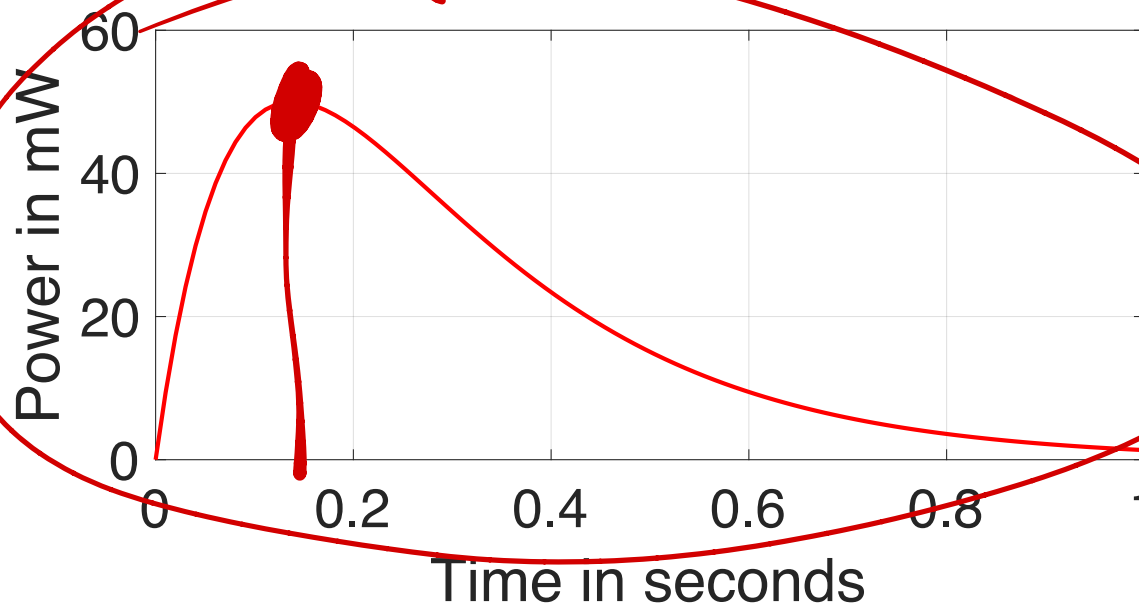
$$= 200 (e^{-5t} - e^{-10t}) \text{ mW}$$




– Calculus gets us the extreme point:

$$\frac{dp(t)}{dt} = 200 (-5e^{-5t} + 10e^{-10t})$$

• This derivative is zero when


$$t = \frac{\ln 2}{5} = 0.139 \text{ sec.}$$

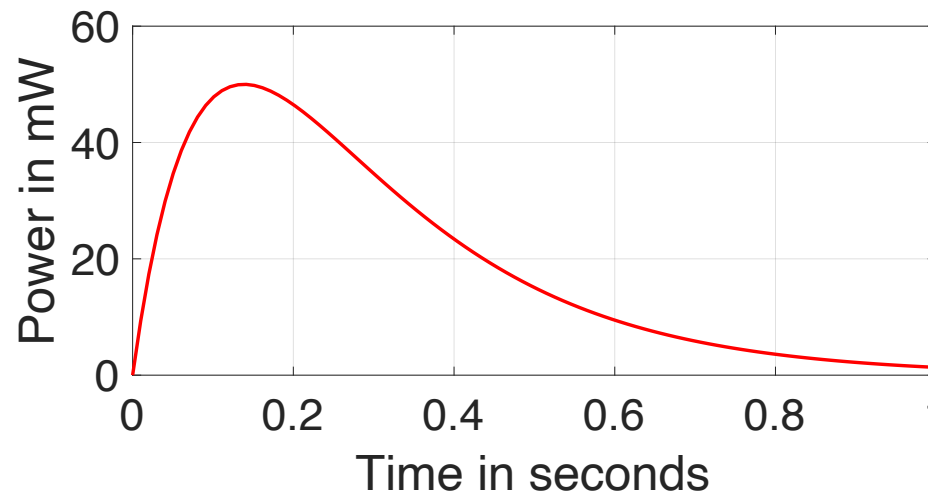– The peak is $p\left(\frac{\ln 2}{5}\right) = 50 \text{ mW}$






2 Terminal Devices

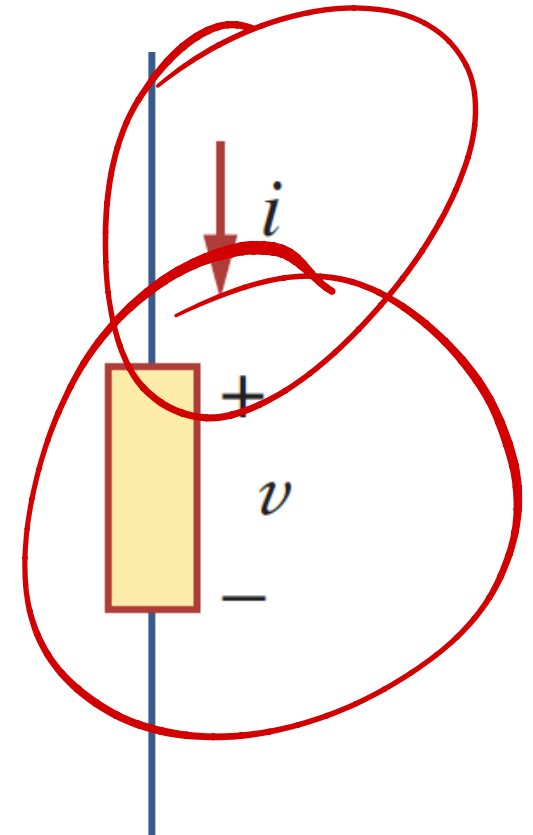- Typical components for ELE 212/215:
 - Voltage and current sources
 - Resistors, inductors, capacitors
- Each has its own v, i characteristic
- Passive sign convention
 - Power $p = v i$
 - $p > 0$ “absorbed”
 - $p < 0$ “delivered”





Sources

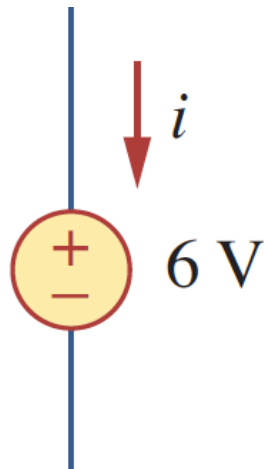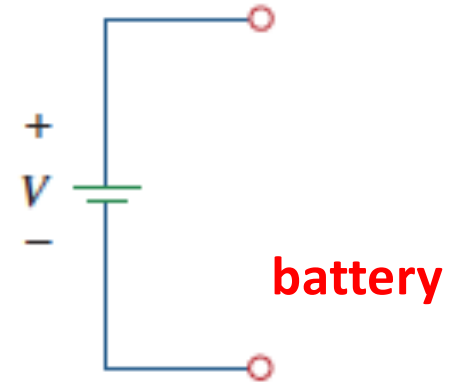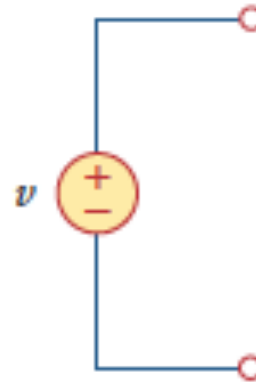- Voltage source:
 - Fixed voltage
 - Any current necessary
 - Example:



Power $p = v i$ can be positive or negative

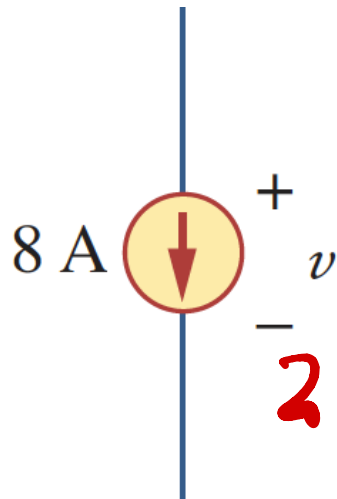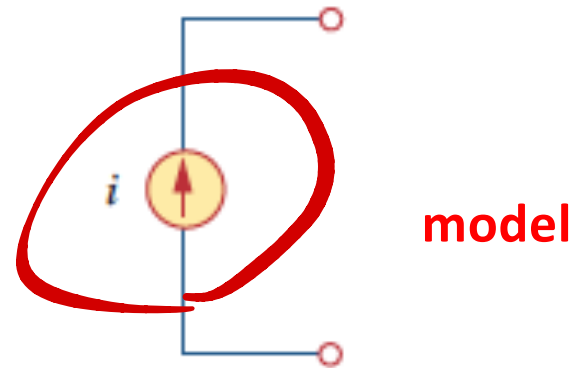- Current source:
 - Fixed current
 - Any voltage necessary
 - Example:





Power $p = v i$ can be positive or negative



Resistors

- Ohm's Law

$$v = R i$$

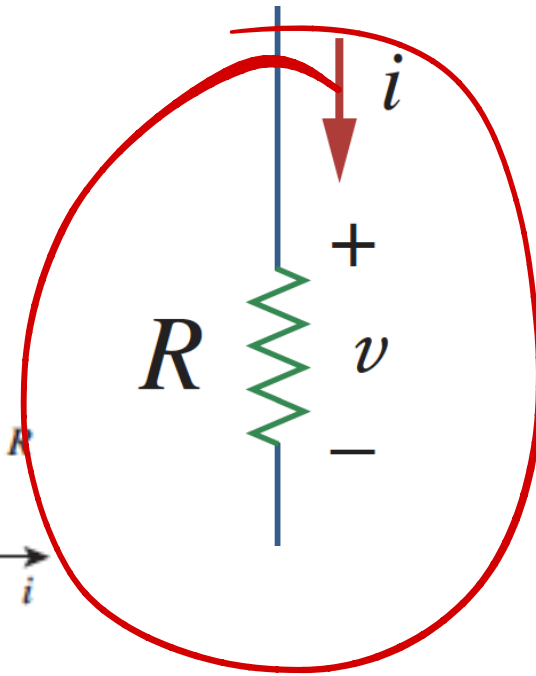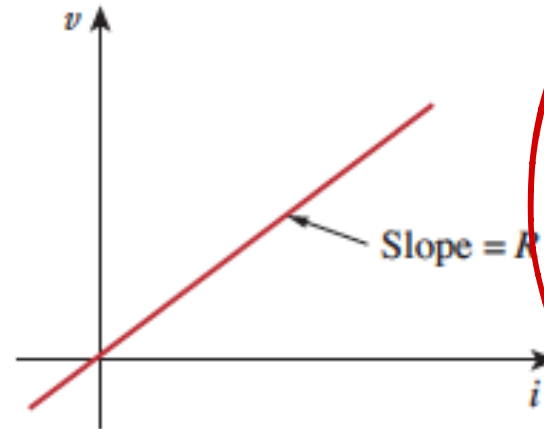

- Unit is ohms (Ω , $k\Omega$, $M\Omega$)

– Also written as $i = \frac{v}{R} = v G$

– G = conductance (mhos, Siemens, \mathcal{U})

- Power is $p = v i = R i^2 = \frac{v^2}{R} = v^2 G$

– Always positive; power is always absorbed

Example: If the current through a 60Ω resistor is 0.3 A , what is the voltage across it? How much power is it absorbing?

Ohm's Law

$$V = R \cdot i$$

$$(60)(0.3) = \underline{18 \text{ V}}$$

$$\begin{aligned} \text{Power} &= V \cdot i = 18 \cdot (.3) = 5.4 \text{ W} \\ &= \frac{V^2}{R} = \frac{18^2}{60} = \frac{324}{60} = 5.4 \text{ W} \\ &= i^2 R = (.3)^2 60 = 5.4 \text{ W} \end{aligned}$$

Issue of significant figures

- Consider computing the resistance using Ohm's Law:

$$v = 3.07 \text{ volts}$$

$$i = 29.0 \text{ milliamps}$$


then

$$R = \frac{3.07 \pm 0.01}{0.0290 \pm 0.0001} \Omega$$

$$\frac{3.07}{0.0290} = 105.862068 \Omega$$

$$R \geq \frac{3.06}{0.0291} = 105.15$$

$$R \leq \frac{3.08}{0.0289} = 106.57$$

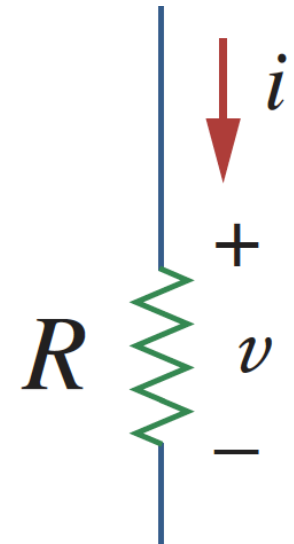

\$895

Practice problem: I'm thinking of buying an electric car. How much would I save by having a home charger versus using the publicly available charging stations?

– Assumptions:

- Average 330 miles from 82 kWh (Tesla model 3)
- Drive 15,000 miles per year
- Electricity rate of 18 cents/kWh at home vs 42 cents/kWh at the chargers

$$E/\text{yr} = \frac{15000}{330} \cdot 82 \cdot \frac{.42}{.18}$$

0.424 mA

Practice problem: If the voltage across a 33 kΩ resistor is 14 volts, what is the current through the resistor?



Ohm's Law

$$I = \frac{V}{R} = \frac{14}{33000} =$$

5 w power
printed red

137 volts

Practice problem: If a 150 k Ω resistor has a power rating (i.e. maximum power allowed) of 1/8 watt, what is the maximum voltage that can be applied across the resistor?

for resistor $P = \frac{V^2}{R} \Rightarrow V^2 = P \cdot R$

$$V = \sqrt{P \cdot R}$$
$$= \sqrt{\frac{1}{8} \cdot 150000}$$

3.57 mA

Practice problem: If the voltage across a 56Ω resistor is 200 mV, what is the current through the resistor?

34.6 mA

Practice problem: If a $100\ \Omega$ resistor is absorbing 120 mW, what is the current through the resistor?